Fundamentals of Power Electronics

R. W. Erickson

Accompanying material for instructors

The materials below are intended to be used by instructors of power electronics classes who have adopted *Fundamentals of Power Electronics* as a text. These instructors may download and use the files for educational purposes free of charge. Students and others who have purchased the text may also use the slides as an educational supplement to the text. Other uses of these materials is prohibited. All slides copyright R. W. Erickson 1997.

The slides for each chapter are contained in a .pdf file. These files can be read using the Adobe Acrobat viewer, available free from the <u>Adobe Acrobat web site</u>. Slides and overhead transpariencies covering the material of the entire book can be produced using these files.

Back

Introduction

• Chapter 1. Introduction 98kB

Part 1: Converters in Equilibrium

- Chapter 2. Principles of steady-state converter analysis 126kB
- Chapter 3. Steady-state equivalent circuit modeling, losses, and efficiency 98kB
- Chapter 4. Switch realization 201kB
- Chapter 5. The discontinuous conduction mode 96kB
- Chapter 6. Converter circuits 283kB

Part 2: Converter Dynamics and Control

- Chapter 7. Ac equivalent circuit modeling 422kB
- Chapter 8. Converter transfer functions
- Chapter 9. Controller design 365kB
- Chapter 10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode 218kB
- Chapter 11. The current programmed mode 236kB

Part 3: Magnetics

- Chapter 12. Basic magnetics theory 196kB
- Chapter 13. Filter inductor design 67kB
- Chapter 14. Transformer design 175kB

Part 4: Modern Rectifiers and Power System Harmonics

- Chapter 15. Power and harmonics in nonsinusoidal systems 91kB
- Chapter 16. Line-commutated rectifiers 130kB
- <u>Chapter 17. The ideal rectifier</u> 235kB
- Chapter 18. Low harmonic rectifier modeling and control

Part 5: Resonant Converters

- Chapter 19. Resonant conversion 325kB
- Chapter 20. Quasi-resonant converters 177kB

Appendices

- Appendix 1. RMS values of commonly-observed converter waveforms 26 kB
- Appendix 2. Magnetics design tables 26kB
- Appendix 3. Averaged switch modeling of a CCM SEPIC 41kB


Update 11/30/98 rwe

Fundamentals of Power Electronics

First Edition R. W. Erickson

Power Electronics Group, University of Colorado at Boulder

About the second edition

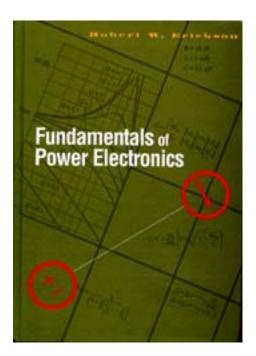

A new textbook on power electronics converters. This book is intended for use in introductory power electronics courses at the senior and first-year graduate level. It is also intended as a source for professionals working in power electronics, power conversion, and analog electronics. It emphasizes the fundamental concepts of power electronics, including averaged modeling of PWM converters and fundamentals of converter circuits and electronics, control systems, magnetics, lowharmonic rectifiers, and resonant converters.

Publisher and vitals

New York: Chapman and Hall, May 1997. Hardback ISBN 0-412-08541-0 TK7881.15.E75 1997 7"x10", 791 pages, 929 line illustrations. Note: Chapman and Hall has recently been acquired by Kluwer Academic Publishers

Note to instructors: how to obtain a copy

More information regarding contents of book

- <u>Complete Table of Contents</u>
- Abridged Table of Contents: Chapter titles only
- <u>Preface</u>

Revision to Fundamentals of Power Electronics

• Index 101kB -searchable with Adobe Acrobat

Errata, first printing

Supplementary material for instructors

- <u>Slides</u>
- Solutions to selected problems

Other supplementary material

Proximity effect: computer functions 70kB

Ferrite toroid data: Excel 5 spreadsheet

Derivation of Gg0, Eqs. (11.84) and (11.85)

Update 9/7/01 rwe

CoPEC

Colorado Power Electronics Center


University of Colorado, Boulder

About CoPEC <u>Research</u> <u>Publications</u> <u>Students</u> <u>Faculty</u> <u>Courses</u> Textbook: Fundamentals of Power Electronics

Power Electronics in the CU Boulder Electrical and Computer Engineering Department Links to Other Power Electronics Sites

Updated May 21, 2001.

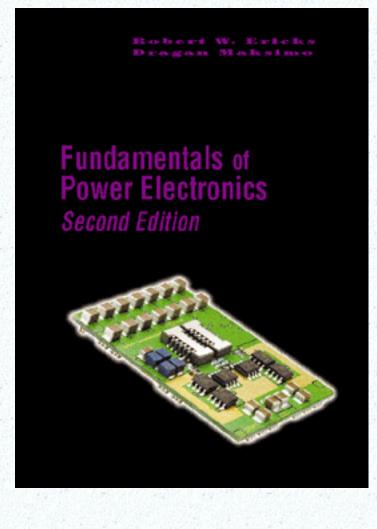Fundamentals of **Power Electronics** Second Edition



Authors: R. W. Erickson and D. Maksimovic University of Colorado, Boulder

Publisher: Kluwer Academic Publishers 912 pages ISBN 0-7923-7270-0

- First edition web site
- <u>To order directly from the</u> <u>publisher</u>
- Note to instructors: how to obtain desk copies
- Errata, second edition, first printing
- Errata, second edition, second printing
- <u>New Certificate Program in</u>
 <u>Power Electronics</u>
- **PSPICE** circuit files and library
- Courses at the University of Colorado that use the second edition
 - ECEN 5797 Power

<u>Electronics 1</u>
<u>ECEN 5807 Power</u>
<u>Electronics 2</u>
<u>ECEN 5817 Power</u>
<u>Electronics 3</u>

Major Features of the Second Edition

- New material on converter simulation using averaged switch models
- Major revision of material on current mode control, including tables of transfer functions of basic converters
- Major revision of material on averaged switch modeling
- New material covering input filter design and Middlebrook's extra element theorem
- Improved explanations of the proximity effect and MMF diagrams
- New section on design of multiplewinding magnetics using the Kg method, including new examples
- New material on soft switching, including active clamp snubbers, the ZVT full bridge converter, and ARCP
- Major revision of material on lowharmonic rectifiers, to improve flow and readability. New material on critical conduction mode control
- Major revision and simplification of the chapter on ac modeling of the discontinuous conduction mode
- Revised problems, and a solutions manual

Detailed description of revisions

- Contents
- Preface to the Second Edition
- Chapter 1 Introduction

Part 1. Converters in Equilibrium

There are no substantial changes to the chapters of Part 1.

- Chapter 2 Principles of Steady-State Converter Analysis
- Chapter 3 Steady-State Equivalent Circuit Modeling, Losses, and Efficiency
- Chapter 4 Switch Realization
- Chapter 5 The Discontinuous Conduction Mode
- Chapter 6 Converter Circuits

Part 2. Converter Dynamics and Control

• Chapter 7 AC Equivalent Circuit Modeling

Chapter 7 has been revised to improve the logical flow, including incorporation of the First Edition Appendix 3 into the chapter. The treatment of circuit averaging and averaged switch modeling (Section 7.4) has undergone major revision. Other changes include Fig. 7.4 and the related text, and Sections 7.2.2, 7.2.7.

• Chapter 8 Converter Transfer Functions

Major revisions to Chapter 8 include a new introduction, a new input filter example in Section 8.1.8, and substantial changes to the buck-boost converter example of Section 8.2.1 and the material of Sections 8.3 and 8.4.

• Chapter 9 Controller Design

Only minor changes to Chapter 9 were made.

• Chapter 10 Input Filter Design

This is an entirely new chapter that treats how input filters modify the transfer functions of a dc-dc

converter, and how to design an input filter that is adequately damped. The approach is based on Middlebrook's Extra Element Theorem (EET) of Appendix C, although it is possible to teach this chapter without use of the EET.

• Chapter 11 AC and DC Equivalent Circuit Modeling of the Discontinuous Conduction Mode

This chapter has been entirely revised and simplified.

• Chapter 12 Current Programmed Control

Treatment of the "more accurate model" in Section 12.3 has undergone a major revision. The explanation is more straightforward, and results are summarized for the basic buck, boost, and buck-boost converters. The results of simulation are used to illustrate how current programming changes the converter transfer function. The treatment of discontinuous conduction mode in Section 12.4 has been shortened.

Part 3. Magnetics

• Chapter 13 Basic Magnetics Theory

The material on the skin and proximity effects has undergone a major revision, to better introduce the concepts of the proximity effect and MMF diagrams. The summary of operation of different magnetic devices has been moved from the filter inductor design chapter into this chapter.

• Chapter 14 Inductor Design

A new section on design of multiple-winding inductors using the Kg method has been added, including two new examples. The summary of different magnetic devices has been moved to the previous chapter, and the material on winding area optimization (previously in the transformer design chapter) has been moved into this chapter.

• Chapter 15 Transformer Design

Notation regarding maximum, peak, and saturation flux density has been made more clear. The section on winding area optimization has been moved to the previous chapter.

Part 4. Modern Rectifiers, Inverters, and Power System Harmonics

Revision to Fundamentals of Power Electronics

• Chapter 16 Power and Harmonics in Nonsinusoidal Systems

Information on harmonic standards has been updated.

• Chapter 17 Line-Commutated Rectifiers

There is little change to this chapter.

• Chapter 18 Pulse-Width Modulated Rectifiers

Chapter 18 is a consolidation of Chapters 17 and 18 of the First Edition. The material has been completely reorganized, to improve its flow. A new section 18.2.2 has been added. Section 18.3.3 has been expanded, to better cover critical conduction mode control. The material on three-phase rectifier topologies has been streamlined.

Part 5. Resonant Converters

• Chapter 19 Resonant Conversion

The order of the sections has been changed, to improve readability. Section 19.4 has been modified, to include better explanation of resonant inverter/electronic ballast design, and two examples have been added. The material on the ZVT converter has been moved to Chapter 20.

• Chapter 20 Soft Switching

A new Section 20.1 compares the turn-on and turn-off transitions of diode, MOSFET, and IGBT devices under the conditions of hard switching, zero-current switching, and zero-voltage switching. The material on quasi-resonant converters is unchanged. Coverage of multi-resonant and quasi-squarewave switches has been exapanded, and includes plots of switch characteristics. A new Section 20.4 has been added, which covers soft-switching techniques. Included in Section 20.4 is an expanded explanation of the ZVT full-bridge converter, new material on active-clamp snubbers, and a short treatment of the auxiliary resonant commutated pole. The material on ac modeling of ZCS quasi-resonant converters has been dropped.

Appendices

• Appendix A RMS Values of Commonly Observed Converter Waveforms

http://ece-www.colorado.edu/~pwrelect/book/SecEd.html (5 of 6) [25/04/2002 16:42:05]

This appendix is unchanged.

• Appendix B Simulation of Converters

Appendix B is completely new. It covers SPICE simulation of converters using averaged switch models, including CCM, DCM, and current-programmed converters. This material complements the discussions of Chapters 7, 9, 11, 12, and 18. It has been placed in an appendix so that the chapter narratives are not interrupted by the details required to run a simulation program; nonetheless, the examples of this appendix are closely linked to the material covered in the chapters.

- PSPICE circuit files and library used in Appendix B
- Appendix C Middlebrook's Extra Element Theorem

This is a completely new appendix that explains the Extra Element Theorem and includes four tutorial examples. This material can be taught in conjunction with Chapter 10 and Section 19.4, if desired.

• Appendix D Magnetics Design Tables

This appendix is unchanged.

Update 12/8/00 rwe

Fundamentals of Power Electronics Second Edition

Up

To instructors of Power Electronics courses: how to obtain an examination copy

Evaluation copies are available on a 60-day approval basis.

Please submit requests in writing on department letterhead and include the following course information:

- course name and number
- estimated enrollment
- semester date
- the text currently used
- your decision date

Please direct all requests to the Textbook Marketing Department at Kluwer Academic Publishers at the Norwell (Americas) or Dordrecht (all other countries) offices:

• In the Americas:

101 Philip Drive Norwell, MA 02061 USA Telephone: (781) 871-6600 Fax: (781) 871-6528 Attention: Ulysses Guasch E-mail: ulysses.guasch@wkap.com

• All other countries:

PO Box 989 3300 AZ Dordrecht The Netherlands Telephone: (0) 31 78 6392 392 Fax: (0) 31 78 6546 474 E-mail: services@wkap.nl

Update 12/15/00 rwe

Fundamentals of Power Electronics

R. W. Erickson

Table of Contents

Back

1. Introduction

- 1.1. Introduction to power processing
- 1.2. Several applications of power electronics
- 1.3. Elements of power electronics

Part I. Converters in Equilibrium

2. Principles of steady state converter analysis

- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small-ripple approximation
- 2.3. Boost converter example
- 2.4. Cuk converter example
- 2.5. Estimating the output voltage ripple in converters containing two-pole low-pass filters
- 2.6. Summary of key points

3. Steady-state equivalent circuit modeling, losses, and efficiency

- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: Inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points

4. Switch realization

- 4.1. Switch applications
 - 4.1.1. Single quadrant switches
 - 4.1.2. Current-bidirectional two-quadrant switches
 - 4.1.3. Voltage-bidirectional two-quadrant switch

- 4.1.4. Four-quadrant switches
- 4.1.5. Synchronous rectifiers
- 4.2. A brief survey of power semiconductor devices
 - 4.2.1. Power diodes
 - 4.2.2. Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET)
 - 4.2.3. Bipolar Junction Transistor (BJT)
 - 4.2.4. Insulated Gate Bipolar Transistor (IGBT)
 - 4.2.5. Thyristors (SCR, GTO, MCT)
- 4.3. Switching loss
 - 4.3.1. Transistor switching with clamped inductive load
 - 4.3.2. Diode recovered charge
 - 4.3.3. Device capacitances, and leakage, package, and stray inductances
 - 4.3.4. Efficiency vs. switching frequency
- 4.4. Summary of key points

5. The discontinuous conduction mode

- 5.1. Origin of the discontinuous conduction mode, and mode boundary
- 5.2. Analysis of the conversion ratio M(D,K)
- 5.3. Boost converter example
- 5.4. Summary of results and key points

6. Converter circuits

- 6.1. Circuit manipulations
 - 6.1.1. Inversion of source and load
 - 6.1.2. Cascade connection of converters
 - 6.1.3. Rotation of three-terminal cell
 - 6.1.4. Differential connection of the load

6.2. A short list of converters

6.3. Transformer isolation

- 6.3.1. Full-bridge and half-bridge isolated buck converters
- 6.3.2. Forward converter
- 6.3.3. Push-pull isolated buck converter
- 6.3.4. Flyback converter
- 6.3.5. Boost-derived isolated converters
- 6.3.6. Isolated versions of the SEPIC and the Cuk converter

6.4. Converter evaluation and design

- 6.4.1. Switch stress and utilization
- 6.4.2. Design using computer spreadsheet
- 6.5. Summary of key points

Part II. Converter Dynamics and Control

7. AC modeling

- 7.1. Introduction
- 7.2. The basic ac modeling approach
 - 7.2.1. Averaging the inductor waveforms
 - 7.2.2. Discussion of the averaging approximation
 - 7.2.3. Averaging the capacitor waveforms
 - 7.2.4. The average input current
 - 7.2.5. Perturbation and linearization
 - 7.2.6. Construction of the small-signal equivalent circuit model
 - 7.2.7. Results for several basic converters
- 7.3. Example: A nonideal flyback converter

7.4. State-space averaging

- 7.4.1. The state equations of a network
- 7.4.2. The basic state-space averaged model
- 7.4.3. Discussion of the state-space averaging result
- 7.4.4. Example: State-space averaging of a nonideal buck-boost converter

7.5. Circuit averaging and averaged switch modeling

- 7.5.1. Obtaining a time-invariant circuit
- 7.5.2. Circuit averaging
- 7.5.3. Perturbation and linearization
- 7.5.4. Averaged switch modeling

7.6. The canonical circuit model

- 7.6.1. Development of the canonical circuit model
- 7.6.2. Example: Manipulation of the buck-boost converter model into canonical form
- 7.6.3. Canonical circuit parameter values for some common converters

Fundamentals of Power Electronics Table of Contents

7.7. Modeling the pulse-width modulator

7.8. Summary of key points

8. Converter transfer functions

8.1. Review of Bode plots

- 8.1.1. Single pole response
- 8.1.2. Single zero response
- 8.1.3. Right half-plane zero
- 8.1.4. Frequency inversion
- 8.1.5. Combinations
- 8.1.6. Double pole response: resonance
- 8.1.7. The low-Q approximation
- 8.1.8. Approximate roots of an arbitrary-degree polynomial
- 8.2. Analysis of converter transfer functions
 - 8.2.1. Example: Transfer functions of the boost converter
 - 8.2.2. Transfer functions of some basic dc-dc converters
 - 8.2.3. Physical origins of the RHP zero
- 8.3. Graphical construction of converter transfer functions
 - 8.3.1. Series impedances: addition of asymptotes
 - 8.3.2. Parallel impedances: inverse addition
 - 8.3.3. Another example
 - 8.3.4. Voltage divider transfer functions: division of asymptotes

8.4. Measurement of ac transfer functions and impedances

8.5. Summary of key points

9. Controller design

9.1. Introduction

9.2. Effect of negative feedback on the network transfer functions

9.2.1. Feedback reduces the transfer functions from disturbances to the output9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop

9.3. Construction of the important quantities 1/(1+T) and T/(1+T) and the closed-loop transfer

functions

9.4. Stability

- 9.4.1. The phase margin test
- 9.4.2. The relation between phase margin and closed-loop damping factor
- 9.4.3. Transient response vs. damping factor

9.5. Regulator design

- 9.5.1. Lead (PD) compensator
- 9.5.2. Lag (PI) compensator
- 9.5.3. Combined (PID) compensator
- 9.5.4. Design example

9.6. Measurement of loop gains

- 9.6.1. Voltage injection
- 9.6.2. Current injection
- 9.6.3. Measurement of unstable systems

9.7. Summary of key points

10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode

- 10.1. DCM averaged switch model
- 10.2. Small-signal ac modeling of the DCM switch network
- 10.3. Generalized switch averaging
 - 10.3.1. DCM buck converter example10.3.2. Proof of generalized averaged switch modeling

10.4. Summary of key points

11. Current programmed control

- 11.1. Oscillation for D > 0.5
- 11.2. A simple first-order model

11.2.1. Simple model via algebraic approach: buck-boost example

11.2.2. Averaged switch modeling

- 11.3. A more accurate model
 - 11.3.1. Current programmed controller model
 - 11.3.2. Example: analysis of CPM buck converter
- 11.4. Discontinuous conduction mode
- 11.5. Summary of key points

Part III. Magnetics

12. Basic magnetics theory

- 12.1. Review of basic magnetics 12.1.1. Basic relations 12.1.2. Magnetic circuits
- 12.2. Transformer modeling
 - 12.2.1. The ideal transformer
 - 12.2.2. The magnetizing inductance
 - 12.2.3. Leakage inductances
- 12.3. Loss mechanisms in magnetic devices
 - 12.3.1. Core loss 12.3.2. Low-frequency copper loss
- 12.4. Eddy currents in winding conductors
 - 12.4.1. The skin effect
 - 12.4.2. The proximity effect
 - 12.4.3. Magnetic fields in the vicinity of winding conductors: MMF diagrams
 - 12.4.4. Power loss in a layer
 - 12.4.5. Example: power loss in a transformer winding
 - 12.4.6. PWM waveform harmonics
- 12.5. Summary of key points

13. Filter inductor design

13.1. Several types of magnetic devices, their B-H loops, and core vs. copper loss

13.2. Filter inductor design constraints

- 13.2.1. Maximum flux density
- 13.2.2. Inductance
- 13.2.3. Winding area
- 13.2.4. Winding resistance
- 13.3. The core geometrical constant K_g
- 13.4. A step-by-step procedure
- 13.5. Summary of key points

14. Transformer design

- 14.1. Winding area optimization
- 14.2. Transformer design: basic constraints
 - 14.2.1. Core loss 14.2.2. Flux density 14.2.3. Copper loss 14.2.4. Total power loss vs. B_{max} 14.2.5. Optimum flux density
- 14.3. A step-by-step transformer design procedure
- 14.4. Examples
 - 14.4.1. Example 1: single-output isolated Cuk converter 14.4.2. Example 2: multiple-output full-bridge buck converter

14.5. Ac inductor design

- 14.5.1. Outline of derivation14.5.2. Step-by-step ac inductor design procedure
- 14.6. Summary

Part IV. Modern Rectifiers, and Power System Harmonics

15. Power and harmonics in nonsinusoidal systems

15.1. Average power

15.2. Root-mean-square (rms) value of a waveform

15.3. Power factor

- 15.3.1. Linear resistive load, nonsinusoidal voltage
- 15.3.2. Nonlinear dynamic load, sinusoidal voltage
- 15.4. Power phasors in sinusoidal systems
- 15.5. Harmonic currents in three-phase systems
 - 15.5.1. Harmonic currents in three-phase four-wire networks 15.5.2. Harmonic currents in three-phase three-wire networks
 - 15.5.3. Harmonic current flow in power factor correction capacitors

15.6. AC line current harmonic standards

- 15.6.1. US MIL STD 461B
- 15.6.2. International Electrotechnical Commission standard 555
- 15.6.3. IEEE/ANSI standard 519

16. Line-commutated rectifiers

- 16.1. The single-phase full wave rectifier
 - 16.1.1. Continuous conduction mode
 - 16.1.2. Discontinuous conduction mode
 - 16.1.3. Behavior when C is large
 - 16.1.4. Minimizing THD when *C* is small

16.2. The three-phase bridge rectifier

16.2.1. Continuous conduction mode 16.2.2. Discontinuous conduction mode

16.3. Phase control

- 16.3.1. Inverter mode
- 16.3.2. Harmonics and power factor
- 16.3.3. Commutation

16.4. Harmonic trap filters

16.5. Transformer connections

16.6. Summary

17. The ideal rectifier

- 17.1. Properties of the ideal rectifier
- 17.2. Realization of a near-ideal rectifier
- 17.3. Single-phase converter systems incorporating ideal rectifiers
- 17.4. RMS values of rectifier waveforms
 - 17.4.1. Boost rectifier example17.4.2. Comparison of single-phase rectifier topologies
- 17.5. Ideal three-phase rectifiers
 - 17.5.1. Three-phase rectifiers operating in CCM17.5.2. Some other approaches to three-phase rectification
- 17.6. Summary of key points

18. Low harmonic rectifier modeling and control

- 18.1. Modeling losses and efficiency in CCM high-quality rectifiers
 - 18.1.1. Expression for controller duty cycle d(t)
 - 18.1.2. Expression for the dc load current
 - 18.1.3. Solution for converter efficiency
 - 18.1.4. Design example

18.2. Controller schemes

- 18.2.1. Average current control
- 18.2.2. Feedforward
- 18.2.3. Current programmed control
- 18.2.4. Hysteretic control
- 18.2.5. Nonlinear carrier control

18.3. Control system modeling

- 18.3.1. Modeling the outer low-bandwidth control system
- 18.3.2. Modeling the inner wide-bandwidth average current controller
- 18.4. Summary of key points

Part V. Resonant converters

19. Resonant Conversion

- 19.1. Sinusoidal analysis of resonant converters
 - 19.1.1. Controlled switch network model
 - 19.1.2. Modeling the rectifier and capacitive filter networks
 - 19.1.3. Resonant tank network
 - 19.1.4. Solution of converter voltage conversion ratio $M = V/V_{\rho}$

19.2. Examples

- 19.2.1. Series resonant dc-dc converter example
- 19.2.2. Subharmonic modes of the series resonant converter
- 19.2.3. Parallel resonant dc-dc converter example

19.3. Exact characteristics of the series and parallel resonant converters

- 19.3.1. Series resonant converter
- 19.3.2. Parallel resonant converter

19.4. Soft switching

- 19.4.1. Operation of the full bridge below resonance: zero-current switching
- 19.4.2. Operation of the full bridge above resonance: zero-voltage switching
- 19.4.3. The zero voltage transition converter

19.5. Load-dependent properties of resonant converters

- 19.5.1. Inverter output characteristics
- 19.5.2. Dependence of transistor current on load
- 19.5.3. Dependence of the ZVS/ZCS boundary on load resistance
- 19.6. Summary of key points

20. Quasi-resonant converters

- 20.1. The zero-current-switching quasi-resonant switch cell
 - 20.1.1. Waveforms of the half-wave ZCS quasi-resonant switch cell
 - 20.1.2. The average terminal waveforms
 - 20.1.3. The full-wave ZCS quasi-resonant switch cell
- 20.2. Resonant switch topologies
 - 20.2.1. The zero-voltage-switching quasi-resonant switch
 - 20.2.2. The zero-voltage-switching multi-resonant switch
 - 20.2.3. Quasi-square-wave resonant switches
- 20.3. Ac modeling of quasi-resonant converters
- 20.4. Summary of key points

Appendices

Appendix 1. RMS values of commonly-observed converter waveforms

- A1.1. Some common waveforms
- A1.2. General piecewise waveform

Appendix 2. Magnetics design tables

- A2.1. Pot core data
- A2.2. EE core data
- A2.3. EC core data
- A2.4. ETD core data
- A2.5. PQ core data
- A2.6. American wire gauge data

Appendix 3. Averaged switch modeling of a CCM SEPIC

Index

Fundamentals of Power Electronics

R. W. Erickson

Table of Contents

Chapter titles only

Back

1. Introduction

Part I. Converters in Equilibrium

- 2. Principles of steady state converter analysis
- 3. Steady-state equivalent circuit modeling, losses, and efficiency
- 4. Switch realization
- 5. The discontinuous conduction mode
- 6. Converter circuits

Part II. Converter Dynamics and Control

- 7. AC modeling
- 8. Converter transfer functions
- 9. Controller design
- 10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
- 11. Current programmed control

Part III. Magnetics

- 12. Basic magnetics theory
- 13. Filter inductor design
- 14. Transformer design

Part IV. Modern Rectifiers, and Power System Harmonics

- 15. Power and harmonics in nonsinusoidal systems
- 16. Line-commutated rectifiers

Fundamentals of Power Electronics Table of Contents Chapter titles only

17. The ideal rectifier

18. Low harmonic rectifier modeling and control

Part V. Resonant Converters

- 19. Resonant conversion
- 20. Quasi-resonant converters

Appendices

Appendix 1. RMS values of commonly-observed converter waveforms

Appendix 2. Magnetics design tables

Appendix 3. Averaged switch modeling of a CCM SEPIC

Index

Preface

Fundamentals of Power Electronics

R. W. Erickson

Back

In many university curricula, the power electronics field has evolved beyond the status of comprising one or two special-topics courses. Often there are several courses dealing with the power electronics field, covering the topics of converters, motor drives, and power devices, with possibly additional advanced courses in these areas as well. There may also be more traditional power-area courses in energy conversion, machines, and power systems. In the breadth vs. depth tradeoff, it no longer makes sense for one textbook to attempt to cover all of these courses; indeed, each course should ideally employ a dedicated textbook. This text is intended for use in introductory power electronics courses on converters, taught at the senior or first-year graduate level. There is sufficient material for a one year course or, at a faster pace with some material omitted, for two quarters or one semester.

The first class on converters has been called a way of enticing control and electronics students into the power area via the "back door". The power electronics field is quite broad, and includes fundamentals in the areas of

- Converter circuits and electronics
- Control systems
- Magnetics
- Power applications
- Design-oriented analysis

This wide variety of areas is one of the things which makes the field so interesting and appealing to newcomers. This breadth also makes teaching the field a challenging undertaking, because one cannot assume that all students enrolled in the class have solid prerequisite knowledge in so many areas. Indeed, incoming students may have individual backgrounds in the power, control, or electronics areas, but rarely in all three. Yet it is usually desired to offer the class to upper-division undergraduate and entering graduate students. Hence, in teaching a class on converters (and in writing a textbook), there are two choices:

- 1. Avoid the problem of prerequisites, by either (a) assuming that the students have all of the prerequisites and discussing the material at a high level (suitable for an advanced graduate class), or (b) leaving out detailed discussions of the various contributing fields.
- 2. Attack the problem directly, by teaching or reviewing material from prerequisite areas as it is

needed. This material can then be directly applied to power electronics examples. This approach is suitable for a course in the fourth or fifth year, in which fundamentals are stressed.

Approach (2) is employed here. Thus, the book is not intended for survey courses, but rather, it treats fundamental concepts and design problems in sufficient depth that students can actually build converters. An attempt is made to deliver specific results. Completion of core circuits and electronics courses is the only prerequisite assumed; prior knowledge in the areas of magnetics, power, and control systems is helpful but not required.

In the power electronics literature, much has been made of the incorporation of other disciplines such as circuits, electronic devices, control systems, magnetics, and power applications, into the power electronics field. Yet the field has evolved, and now is more than a mere collection of circuits and applications linked to the fundamentals of other disciplines. There is a set of fundamentals that are unique to the field of power electronics. It is important to identify these fundamentals, and to explicitly organize our curricula, academic conferences, and other affairs around these fundamentals. This book is organized around the fundamental principles, while the applications and circuits are introduced along the way as examples.

A concerted effort is made to teach converter modeling. Fundamental topics covered include:

- Fundamentals of PWM converter analysis, including the principles of inductor volt-second balance and capacitor charge balance, and the small-ripple approximation (Chapter 2).
- Converter modeling, including the use of the dc transformer model, to predict efficiency and losses (Chapter 3).
- Realization of switching elements using semiconductor devices. One-, two-, and four-quadrant switches. A brief survey of power semiconductor devices (Chapter 4).
- An up-to-date treatment of switching losses and their origins. Diode stored charge, device capacitances, and ringing waveforms (Chapter 4).
- Origin and steady-state analysis of the discontinuous conduction mode (Chapter 5).
- Converter topologies (Chapter 6).
- The use of averaging to model converter small-signal ac behavior. Averaged switch modeling (Chapter 7).
- Converter small-signal ac transfer functions, including the origins of resonances and right half-plane zeroes. Control-to-output and line-to-output transfer functions, and output impedance (Chapter 8).
- A basic discussion of converter control systems, including objectives, the system block diagram, and the effect of feedback on converter behavior (Chapter 9).
- Ac modeling of the discontinuous conduction mode. Quantitative behavior of DCM small-signal transfer functions (Chapter 10).
- Current-programmed control. Oscillation for D > 0.5. Equivalent circuit modeling (Chapter 11).
- Basic magnetics, including inductor and transformer modeling, and loss mechanisms in high-frequency power magnetics (Chapter 12).
- An understanding of what determines the size of power inductors and transformers. Power inductor and transformer design issues (Chapters 13 and 14).
- Harmonics in power systems (Chapter 15).
- A modern viewpoint of rectifiers, including harmonics, power factor, and mitigation techniques in conventional rectifiers, and operation of sophisticated low-harmonic rectifiers (Chapters 16-18).
- Analysis and modeling of low-harmonic rectifiers (Chapters 17-18).
- Resonant inverters and dc-dc converters: approximate analysis techniques, characteristics of basic converters, and

Fundamentals of Power Electronics Preface

load-dependent properties (Chapter 19).

- Zero voltage switching, zero current switching, and the zero-voltage-transition converter (Chapter 19).
- Resonant switch converters, including basic operation, efficiency and losses, and ac modeling (Chapter 20).

On teaching averaged converter modeling: I think that this is one of the important fundamentals of the field, and hence we should put serious effort into teaching it. Although we in the academic community may debate how to rigorously justify averaging, nonetheless it is easy to teach the students to average: Just average all of the waveforms over one switching period. In particular, for the continuous conduction mode, average the inductor voltages and capacitor currents over one switching period, ignoring the ripple. That's all that is required, and I have found that students quickly and easily learn to average waveforms. The results are completely general, they aren't limited to SPDT switches, and they can easily be used to refine the model by inclusion of losses, dynamics, and control variations. To model dynamics, it is also necessary to linearize the resulting equations. But derivation of small-signal models is nothing new to the students --they have already seen this in their core electronics classes, as well as in numerous math courses and perhaps also in energy conversion. It isn't necessary to teach full-blown state-space averaging, but I have included an optional (with asterisk) section on this for the graduate students. I personally prefer to initially skip Sections 7.4 and 7.5. After covering Chapters 8 and 9, I return to cover Sections 7.4 and 7.5 before teaching Chapters 10 and 11.

Averaging aside, it is also important to teach modeling in a pedagogically sound way. The object is to describe the important properties of the converter, in a simple and clear way. The dc transformer represents the basic function of a dc-dc converter, and so the modeling process should begin with a dc transformer having a turns ratio equal to the conversion ratio of the converter. For example, the model of the buck-boost converter ought to contain a buck transformer cascaded by a boost transformer, or perhaps the two transformers combined into a single D : D' transformer. This first-order model can later be refined if desired, by addition of loss elements, dynamic elements, etc.

The design-oriented analysis methods of R. D. Middlebrook have been well accepted by a significant portion of the power electronics community. While the objective of this text is the introduction of power electronics rather than design-oriented analysis, the converter analyses and examples are nonetheless done in a design-oriented way. Approximations are often encouraged, and several of the techniques of design-oriented analysis are explicitly taught in parts of Chapters 8 and 9. We need to teach our students how to apply our academic theory to real-world, and hence complicated, problems. Design-oriented analysis is the missing link.

Chapter 8 contains a "review" of Bode diagrams, including resonant responses and right half-plane zeroes. Also included is material on design-oriented analysis, in the context of converter transfer functions. The Bode diagram material is covered in more depth than in prerequisite classes. I have found that the material of Chapter 8 is especially popular with continuing education students who are practicing engineers. I recommend at least quickly covering this chapter in lecture. Those instructors who choose to skip some or all of Chapter 8 can assign it as reading, and hold students responsible for the material. In a similar manner, Chapter 9 contains a "review" of classical control systems, in the context of switching regulators. This chapter explicitly makes the connection between the small-signal converter models

derived in other chapters, and their intended application. Many power area students are unfamiliar with this material, and even control-area students comment that they learned something from the designoriented approach.

Parts III, IV, and V can be covered in any order. Part III includes a review of basic magnetics, a discussion of proximity loss, and an introduction to the issues governing design of magnetic devices. The inclusion of step-by-step design procedures may be somewhat controversial; however, these procedures explicitly illustrate the issues inherent in magnetics design. Student tendencies towards cookbook mentality are mitigated by the inclusion of homework problems that cannot be solved using the given step-by-step procedures. Part IV, entitled "Modern rectifiers," covers the issues of power system harmonics, generation of harmonics by conventional rectifiers, and low-harmonic rectifiers. Chapters 17 and 18 cover low-harmonic rectifiers in depth, including converter analysis and modeling, and rectifier control systems. Resonant converters are treated in Part V. There have been a tremendous number of papers written on resonant converters, most of which are very detailed and complicated. Indeed, the complexity of resonant converter behavior makes it challenging to teach this subject in depth. Two somewhat introductory chapters are included here. State-plane analysis is omitted, and is left for an advanced graduate class. In Chapter 19, resonant inverters and dc-dc converters are introduced and are analyzed via the sinusoidal approximation. Soft switching is described, in the context of both resonant converters and the zero-voltage transition converter. Some resonant network theorems are also presented, which yield insight into the design of resonant inverters with reduced circulating currents, with zerovoltage switching over a wide range of load currents, and with desired output characteristics. Resonant switch converters are introduced and modeled in Chapter 20.

Most chapters include both short analysis problems, and longer analysis and/or design problems. References are given at the end of each chapter; these are not intended to be exhaustive bibliographies, but rather are a starting place for additional reading.

This text has evolved from course notes developed over thirteen years of teaching power electronics at the University of Colorado, Boulder. These notes, in turn, were heavily influenced by my previous experience as a graduate student at the California Institute of Technology, under the direction of Profs. Slobodan Cuk and R. D. Middlebrook, to whom I am grateful. In addition, I appreciate the numerous helpful technical discussions and suggestions of my colleague at the University of Colorado, Prof. Dragan Maksimovic. I would also like to thank the following individuals for their suggestions: Prof. Arthur Witulski (University of Arizona, Tucson), Prof. Sigmund Singer (Tel-Aviv University, Israel), Dr. Michael Madigan, and Carlos Oliveira.

Robert W. Erickson Boulder, Colorado INDEX

Air gap in coupled inductor, 502 in flyback transformer, 503 in inductor, 464-466, 498, 505, 509 in transformer, 469 A_{L} (mH/1000 turns), 509 American wire gauge (AWG) data, 755-756 design examples, 527, 531 Amorphous alloys, 473 Ampere's law, 457-458 Amp-second balance (see Capacitor charge balance) Apparent power, 550 Artificial ramp circuit, 415 effect on CPM boost low-harmonic rectifier, 637-639 effect on line-to-output transfer function of CCM buck, 437-438 effect on small-signal CCM models, 428-438 effect on small-signal DCM models, 438-447 effect on stability of CPM controllers, 414-418 Asymptotes (see Bode plots) Audiosusceptibility $G_{ye}(s)$ (see Line-to-output transfer function) Average current control feedforward, 635-636 in low-harmonic rectifier systems, 593-598, 634-636, 649, 650-652 modeling of, 649-652 Averaged switch modeling, 239-245, 390-403 of current-programmed CCM converters, 423-428 of current-programmed DCM converters, 438-447 in discontinuous conduction mode, 370-390 equivalent circuit modeling of switching loss, 241-245 examples nonideal buck converter, 241-245 DCM buck converter, 393-400 CCM SEPIC, 757-762 generalization of, 390-403 of ideal CCM switch networks, 242, 377, 757-762 of ideal DCM switch networks, 377 of quasi-resonant converters, 732-737 Average power and Fourier series, 542-543 modeled by power source element, 375-379, 423-428, 438-447 in nonsinusoidal systems, 542-555 predicted by averaged models, 57 power factor, 546-550 sinusoidal phasor diagram, 550-551 Averaging approximation, discussion of, 195-196, 200-202 averaged switch modeling, 239-245 basic approach, 198-209

capacitor charge balance, 24 circuit. 231-245 to find dc component, 6, 16 flyback ac model, 209-218 inductor volt-second balance, 22-23 introduction to, 193-198 modeling efficiency and loss via, 57 to model rectifier output, 645-647 to model 3ø converters, 611-614 of quasi-resonant converters ac modeling, 732-737 dc analysis, 712-728 state-space, 218-231 Battery charger, 9, 70 B-H loop in an ac inductor, 499-500 in a conventional transformer, 153, 500-501 in a coupled inductor, 501-502 in a filter inductor, 497-499 in a flyback transformer, 502-503 modeling of, 458-460 Bidirectional dc-dc converters, 70 Bipolar junction transistor (BJT) breakdown mechanisms in. 86-87 construction and operation of, 82-87 current crowding, 85-86 Darlington-connected, 87 idealized switch characteristics, 65-66 on resistance, 53, 82 quasi-saturation, 82-83, 86 storage time, 84 stored minority charge in, 82-86 switching waveforms, 83-86 Bode plots (see also Harmonic trap filters, sinusoidal approximation) asymptote analytical equations, 275-276 CCM buck-boost example, 289-292 combinations, 272-276 complex poles, 276-282 frequency inversion, 271-272 graphical construction of, 296-309 addition, 296-301 closed-loop transfer functions, 329-332 division, 307-309 parallel combination, 301-307 parallel resonance, 301-303 series resonance, 298-303 impedance graph paper, 307 nonminimum phase zero, 269-271 reactance graph paper, 307 real pole, 263-268 real zero, 268-269 RHP zero. 269-271 transfer functions of buck, boost, buck-boost, 292-293 Body diode (see MOSFET)

Boost converter (see also Bridge configuration, Push-pull isolated converters) active switch utilization in. 179, 608 averaged switch model, DCM, 380-381 circuit-averaged model, 233-239 current-programmed averaged switch model, CCM, 424-425 averaged switch model, DCM, 443-444 small-signal ac model, CCM, 427-428, 430-431 small-signal ac model, DCM, 445-447 as inverted buck converter, 136-137 as low-harmonic rectifier, 594-597, 605-609, 617, 627-634 nonideal analysis of, 43-51, 53-57 quasi-resonant ZCS, 722-723 small-signal ac model CCM, 208-210, 251 DCM, 385-390 steady-state analysis of. CCM, 24-29 DCM, 121-125 transfer functions, CCM, 292-293 Bridge configuration (dc-dc converters) boost-derived full bridge, 171-172 buck-derived full bridge, 154-157 buck-derived half bridge, 157-159 full bridge transformer design example, 528-531 minimization of transformer copper loss in, 516-517 Bridge configuration (inverters) single phase, 7-8, 142-145, 148-150 three phase, 70, 143-148 Buck-boost converter (see also Flyback converter) 3øac-dc rectifier, 615-616, 619 averaged switch model, DCM, 370-381 as cascaded buck and boost converters, 138-141 current-programmed averaged switch model, DCM, 438-444 more accurate model, CCM, 430-432 simple model, CCM, 419-423 small-signal ac model, DCM, 445-447 dc-3øac inverter, 71-72, 615-616 DCM characteristics, 115, 127-129, 381 as low-harmonic rectifier, 598-599 manipulation of ac model into canonical form, 248-251 nonideal, state-space averaged model of, 227-232 noninverting version, 139, 148-149 as rotated three-terminal cell, 141-142 small-signal ac model, CCM, 208-210, 251 small-signal ac model, DCM, 382-388 transfer functions, CCM, 289-293 transformer isolation in, 166-171 Buck converter (see also Bridge configuration, Forward converter, Push-pull isolated converters), 6, 15-23, 34-35 active switch utilization in. 179 averaged switch model, 239-245 current-programmed

averaged switch model, CCM, 423-427 averaged switch model, DCM, 442-447 small-signal ac model, CCM, 421-427, 431-438 small-signal ac model, DCM, 442-447 equivalent circuit modeling of, small-signal ac, CCM, 208-210, 251 small-signal ac, DCM, 385-388, 393-400 steady-state, CCM, 51-53 steady-state, DCM, 380-381 as high power factor rectifier single phase, 599 three phase, 614-615 multi-resonant realization, 729 quasi-square-wave resonant realizations, 730-731 quasi-resonant realizations ac modeling of, 732-737 zero current switching, 662-663, 712-722, 723-724 zero voltage switching, 728 small-signal ac model ČCM, 208-210, 251 DCM, 385-390 steady-state analysis of, CCM, 17-22, 23, 34-35, 51-53 DCM, 111-121, 380-381 switching loss in, 94-101, 241-245 employing synchronous rectifier, 73-74 transfer functions, CCM, 292-293 Buck² converter, 149, 151 Buck 3ø inverter (see Voltage source inverter) Canonical circuit model, 245-251 via generalized switch averaging, 402-403 manipulation into canonical form, 248-251 parameters for buck, boost, buck-boost, 251 physical development of, 245-248 transfer functions predicted by, 247-248, 292-293 Capacitor amp-second balance (see Capacitor charge balance) Capacitor charge balance boost converter example, 27 Cuk converter example, 31-32 definition, 24 in discontinuous conduction mode, 115 nonideal boost converter examples, 45, 55 Capacitor voltage ripple boost converter example, 28-29 buck converter example, 34-35 in converters containing two-pole filters, 34-35 Cuk converter example, 32-34 Cascade connection of converters, 138-141 Characteristic value α (current programmed mode), 414, 417-418, 435-436 Charge balance (see Capacitor charge balance) Circuit averaging (see also Averaged switch modeling), 231-245 averaging step, 235 boost converter example, 233-238

linearization, 235-238 obtaining a time-invariant network, 234-235 summary of, 231-233 Commutation failure, 574 notching, 575 in 3ø phase controlled rectifier, 573-575 Compensators (see also Control system design) design example, 346-354 lag, 343-345 lead, 340-340, 350-351 PD, 340-343, 350-351 PI, 343-345 PID, 345-346, 352-354 Complex power, 550-551 Computer power supply, 8-9 Computer spreadsheet, design using, 180-183 Conduction loss (see Copper loss, Semiconductor conduction loss) Conductivity modulation, 75, 79, 82, 87, 90 Control system design (see also Compensators, Negative feedback), 323-368 compensation, 340-346 construction of closed-loop transfer functions, 326-332 design example, 346-354 for low-harmonic rectifiers approaches, 634-652 modeling, 645-652 phase margin test. 333-334 vs. closed-loop damping factor, 334-338 stability, 332-339 voltage regulator block diagram, 324-325, 328, 347-349 design specifications, 339-340 Control-to-output transfer function as predicted by canonical model, 248 of CCM buck, boost, and buck-boost converters, 292-293 of current programmed converters, 422, 427-428, 434-437, 446 of DCM converters, 387-390, 396-399 of quasi-resonant converters, 733, 736 Conversion ratio M (see also Switch conversion ratio μ) of boost, 18, 26, 127, 381 of buck, 18, 120, 381 of buck-boost, 18, 128, 381 of Cuk converter, 32, 381 of loss-free resistor networks, 376-381 in low-harmonic rectifiers, 593-595 modeling of, 40-43 of quasi-resonant converters, 711, 720-723 of parallel resonant converter, 676-678, 686-689 of SEPIC, 151, 381 of series resonant converter, 671-674, 679-686 via sinusoidal approximation, 670 Copper loss

allocation of window area to minimize, 513-517, 519 high frequency effects skin effect, 475-476 proximity effect, 476-490 inductor design to meet specified, 503-509 low frequency, 474 modeling in converters, 43-53 Core loss, 471-474, 518 Coupled inductors in Cuk converter, 494-495, 501 in multiple-output buck-derived converters, 501-502, 511 Crossover frequency, 330-334 Cuk converter 3øac-dc converter, 615-616 active switch utilization of, 179 as cascaded boost and buck converters, 141 conversion ratio M(D), 32, 381 DCM averaged switch model of, 379-381 as low-harmonic rectifier, 597-599, 608 as rotated three-terminal cell, 141-142 steady-state analysis of, 29-34 transformer design example, 524-528 with transformer isolation, 176-177 Current-fed bridge, 148, 150 Current injection, 359-360 Current programmed control, 408-451 ac modeling of via averaged switch modeling, CCM, 423-428 via averaged switch modeling, DCM, 438-447 CCM more accurate model, 428-438 CCM simple approximation, 418-428 artificial ramp, 414-418 controller circuit, 409, 415 controller small-signal block diagram, 428-432 in half-bridge buck converters, 159, 410 in low harmonic rectifiers, 636-639 oscillation for D > 0.5, 411-418in push-pull buck converters, 166, 410 Current ripple (*see* inductor current ripple) Current sense circuit, isolated, 187-188 Current source inverter (CSI), 146, 148 Cycloconverter, 1, 72 Damping factor ζ (see also Q-factor), 277 Dc conversion ratio (see Conversion ratio M) Dc link, 10 Dc transformer model in averaged switch models, 237-244, 760-762 in canonical model, 245-247, 250-251 in circuit averaged models, 237-238 comparison with DCM model, 377 derivation of, 40-43 equivalence with dependent sources, 41 manipulation of circuits containing, 41-42, 48-49

in a nonideal boost converter, 48-49, 56 in a nonideal buck converter, 52-53 in small-signal ac CCM models, 208-210 Decibel. 262 Delta-wye transformer connection, 582-583 Dependent power source (see Power source element) Derating factor, 180 Design-oriented analysis, techniques of analytical expressions for asymptotes, 275-276 approximate factorization, 285-288 doing algebra on the graph, 296-309 frequency inversion, 271-272 graphical construction of Bode plots, 296-309 of closed-loop transfer functions, 329-332 low Q approximation, 282-284 philosophy of, 261, 306-307 Differential connection of load polyphase inverter, 143-148 single-phase inverter, 142-143 Diode antiparallel, 67 characteristics of, 78 fast recovery, 77 forward voltage drop (see also Semiconductor conduction losses), 53-57, 77 freewheeling, 67 parallel operation of, 77-78 recovered charge Q_r , 76, 97-100, 692, 729 recovery mechanisms, 76-77, 98-100 Schottky, 74, 77, 101 soft recovery, 98-99 snubbing of, 99 switching loss, 97-100, 101-103, 692 switching waveforms, 75-77, 98-100, 101-102 zero current switching of, 101-103, 690-692, 696, 725-726 zero voltage switching of, 692-696, 725-726, 729, 734 Discontinuous conduction mode (DCM) B-H loop, effect on, 503-504 boost converter example, 121-127 buck converter example, 111-121 buck-boost converter example, 370-381 in current programmed converters, 438-447 equivalent circuit modeling of, 369-381, 438-444 in forward converter, 159 in line-commutated rectifiers, 564-568, 569-570 in low-harmonic rectifiers boost rectifier, single phase, 594-597 single-switch, three-phase, 615-619 mode boundary in boost rectifier, 594-697 vs. K, 111-115, 121-122, 128 vs. load current and R_{a} , 381 origin of, 111-115 in parallel resonant converter, 687-689

in PWM converters, 110-134, 369-407, 438-447 in series resonant converter, 681-683 small-signal ac modeling of, 382-403 Displacement factor, 548, 550-551 Distortion factor (see also Total harmonic distortion), 548-550 of single-phase rectifier, 548, 563-566 Distributed power system, 9 Doing algebra on the graph (see Graphical construction of Bode plots) Duty ratio complement of, 16 definition of, 15-16 EC core data, 754 Eddy currents in magnetic cores, 472 in winding conductors, 474-477 EE core data, 753 Effective resistance R_e in DCM averaged switch model, 374-381 in loss-free resistor model. 374-381 in resonant converter models with capacitive filter network, 666-668 with inductive filter network, 674-676 Emulated resistance R_{e} , 590-593 Efficiency, 2 averaged switch modeling, predicted by, 245 of boost converter as low-harmonic rectifier, 632-634 nonideal dc-dc, 49-51, 56 calculation via averaged model, 49-51, 56 vs. switching frequency, 103-104 Equivalent circuit modeling by canonical circuit model, 245-251 of CCM converters operating in steady-state, 40-61 of converters having pulsating input currents, 51-53 of current programmed switch networks CCM, 423-428 DCM. 438-447 small-signal models, 421-422, 423-428, 445-447 of flyback converter, CCM, 168, 216-218 of ideal rectifiers, 590-593, 608-611 of ideal dc-dc converters, 40-42 of inductor copper loss, 43-51 small-signal models ČCM, 207-209, 230-232 DCM, 382-390 current programmed, 421-422, 424-428, 438-447 of switching loss, 241-245 of switch networks CCM, 239-242 DCM, 370-381 of systems containing ideal rectifiers, 602 Equilibrium (see Steady state) Equivalent series resistance (esr) of capacitor, 554-555 ETD core data, 754

Evaluation and design of converters, 177-183 Experimental techniques measurement of impedances, 312-314 measurement of loop gains by current injection, 359-360 by voltage injection, 357-359 of an unstable system, 360-361 measurement of small-signal transfer functions, 309-311 Factorization, approximate approximate roots of arbitrary-degree polynomial, 282-288 graphical construction of Bode diagrams, 296-309 low-Q approximation, 282-284 Faraday's law, 456-457 Feedback (see Control system design, Negative feedback) Ferrite applications of, 499, 525, 528 core loss, 472, 473-474, 518 core tables, 751-755 saturation flux density, 459, 473 Fill factor (see K.) Filter inductor *B-H* loop of, 497, 499 design of derivation of procedure, 503-508 step-by-step procedure, 508-509 Flux **Φ**, 456 Flux density B definition, 456 saturation value B_{sat} , 458-459 Flux-linkage balance (*see* Inductor volt-second balance) Flyback converter (see also Buck-boost converter) active switch utilization, 178-179 derivation of, 166-167 nonideal, ac modeling of, 209-218 single-switch rectifier, 3øac-dc DCM, 623 spreadsheet design example, 180-183 steady-state analysis of, 166-170 two transistor version, 185-186 utilization of flyback transformer, 170-171 Flyback transformer, 166-167, 170-173, 502-503, 619 Forced commutation of SCRs, 90 Forward converter (see also Buck converter), 159-164 active switch utilization, 179 spreadsheet design example, 180-183 steady-state analysis of, 159-164 transformer reset mechanisms, 162-163 transformer utilization in, 164 two transistor version, 163-164 Four-quadrant switches (see Switch) Freewheeling diode, 67 Frequency modulator, 732-733 Gate turn-off thyristor (GTO), 92 Generalized switch averaging, 390-403

Geometrical constant (see K_g , K_{gfe}) Graphical construction of Bode plots (see also Bode plots, Design-oriented analysis) of converter transfer functions, 307-309 division, 307-309 of harmonic trap filters, 576-582 parallel combinations, 301-307 parallel resonance, 301-303 of parallel resonant converter, 677 series combinations, 296-301 series resonance, 298-301 of series resonant converter, 671-672 Grounding problems, 312-314 Gyrator, 682-683 Harmonic correction, 621 Harmonic loss factor F_{H} , 488-490 Harmonics in power systems average power vs. Fourier series, 542-543 distortion factor, 548 harmonic standards, 555-559 neutral currents, 552-553 power factor, 546-550 root-mean-square value of waveform, 543-546 rectifier harmonics, 548-550 in three-phase systems, 551-555 total harmonic distortion, 548 Harmonic trap filters, 575-582 bypass resistor, 580-582 parallel resonance in, 577-579 reactive power in, 582 H-bridge, 7-8, 142-145, 148-150 Hold-up time, 601 Hot spot formation, 77-78, 85-86 Hysteresis loss P_H , 471-472 Hysteretic control, 639-641 Ideal rectifier (see also Low harmonic rectifiers), 590-626 in converter systems, 599-604 properties of, 590-593 realization of single phase, 593-599 three phase, 608-622 rms values of waveforms in, 604-608 IEC-555, 556-557 IEEE/ANSI standard 519, 557-559 Impedance graph paper, 307 Inductor copper loss (see Copper loss) Inductor current ripple in ac inductor, 499-500 boost example, 28 buck example, 21 calculation of, 21 in converters containing two-pole filters, 34-36 Cuk converter example, 32-33 in filter inductor, 497-499

magnitude vs. DCM, 111-113 Inductor design ac inductor design derivation, 531-533 step-by-step procedure, 533-534 filter inductor design derivation, 503-508 step-by-step procedure, 508-509 Inductor volt-second balance boost example, 25-26 buck example, 22-23 Cuk converter example, 31-32 definition, 22 in discontinuous conduction mode, 115 Input port, converter ac modeling of, 203 boost static characteristics, 596-597, 639 modeling of, via state-space averaging, 200, 227, 231 steady-state modeling of, 51-53 Inrush current, 601-602 Insulated-gate bipolar transistor (IGBT) construction and operation of, 87-90 current tailing in, 88-89, 96-97 equivalent circuit, 88 forward voltage drop, modeling of, 89 idealized switch characteristics, 65-66 parallel operation of, 89 switching loss in, 96-97 Inversion of source and load, 136-137 Inverters, 1 high frequency, 659-662, 697-705 line commutated, 572-573 single phase, 7-8, 68-69 sinusoidal analysis of resonant converters, 664-670, 697-705 three phase, 70, 143-148 Iron laminations, 459, 473 K, dimensionless parameter critical value $K_{crit}(D)$, 114-115, 121-122, 128 in current programmed mode analysis, 438 and DCM boundary, 114-115, 121-122, 128 in line-commutated rectifier analysis, 565-566 in steady-state DCM analysis, 120, 127-128 K_{a} , core geometrical constant definition of, 507-507, 751 ferrite core tables of, 752-755 filter inductor design procedure using, 508-509 K_{ofe} , ac core geometrical constant ac inductor design procedure using, 531-534 definition of, 521, 751 ferrite core tables of, 752-755 transformer design using, derivation, 517-521 examples, 524-531 step-by-step procedure, 521-524

 K_{I} , rectifier dimensionless parameter, 565-566 K_{u} , window utilization factor, 507 LCC resonant converter dependence of transistor current on load, 701-702 introduction to, 659-661 ZVS/ZCS boundary, 703-705 Lenz's law, 457, 472, 475 Linear ripple approximation (see Small ripple approximation) Line-to-output transfer function $G_{\nu g}(s)$ of the buck, boost, and buck-boost converters in CCM, 292-293 canonical model, as predicted by, 247-248 closed-loop, 326-327, 331-332 control system design of, 340, 353-354 of current-programmed converters, 422, 427-428, 437-438 of DCM converters, 387-388 of quasi-resonant converters, 736 Litz wire, 487 Loop gain (see also Control system design, Negative feedback) definition. 327 measurement of, 355-361 Loss-free resistor model averaged switch model of discontinuous conduction mode, 374-381 ideal rectifier model single phase, 590-593 three phase, 608-611 Low harmonic rectifiers (see also Ideal rectifiers) controller schemes average current control, 634-636 current programmed control, 636-640 feedforward, 635-636 hysteretic control, 639-641 nonlinear carrier control, 641-645 modeling of efficiency and losses, 627-634 low-bandwidth control loop, 645-650 wide-bandwidth average current control loop, 650-652 rms calculations in, 604-609 Low Q approximation, 282-284 Magnetic circuits, 463-466 Magnetic field H, 455-456 Magnetic path length $l_{\rm m}$ definition, 461 ferrite core tables, 752-755 Magnetics, 453-538 ac inductor design, 531-534 basic relations, 455-462 copper loss, 474 core loss, 471-474 ferrite core tables, 752-755 filter inductor design, 503-509 magnetic circuits, 463-466 magnetic devices, types of, 497-503 optimizing B_{max} to minimize total loss, 520-521 optimizing window allocation to minimize copper loss, 513-517

proximity effect, 476-490 transformer basics, 152-154, 466-471 transformer design, 517-531 Magnetizing current, 152-153, 458-469 Magnetomotive force (MMF) definition, 455-456 MMF diagrams, 479-482 Majority carrier devices (see also MOSFET, Schottky diode), 74-75 Matrix converter, 72-73 Meal length per turn (*MLT*) definition, 507-508 ferrite core tables, 752-755 Measurement of transfer functions and loop gains (see Experimental techniques) MIL-STD-461B, 556 Minority carrier devices (see also Bipolar junction transistor, Diode, Gate turn-off thyristor, Insulated-gate bipolar transistor, MOS-controlled thyristor, Silicon controlled rectifier), 74-75 Modulation index, 613-614 MOS-controlled thyristor (MCT), 92-94 MOSFET body diode, 67-68, 79-80 conduction loss, modeling of, 53-57, 209-218 construction and operation of, 78-82 on resistance, 53-57, 79-82 switching loss owing to C_{ds} , 100-101 as synchronous rectifier, 73-74 terminal capacitances, 81 typical characteristics, 80-82 zero-voltage and zero-current switching of, 689-696 Motor drive system, 9-10 Multiplying controller (see also Average current control, Current programmed control), 596 Multi-resonant switch single-switch 3ø buck rectifier, 620-621 zero-voltage switching dc-dc, 729 Negative feedback (*see also* Control system design) effects of, on network transfer functions, 326-329 objectives of, 193-194, 323-326 reduction of disturbances by, 327-329 reduction of sensitivity to variations in forward gain by, 329 Nonlinear carrier control, 641-645 Nonminimum-phase zero (see Right half-plane zero) Output characteristics of the parallel resonant converter, 689 of resonant inverters, 699-700 of the series resonant converter, 685-686 Overshoot, 338-340 Parallel resonant converter analysis via sinusoidal approximation, 664-670, 674-678 dependence of transistor current on load, 702 exact characteristics continuous conduction mode, 686-687 control plane, 689 discontinuous conduction mode, 687-689 output plane, 689

```
introduction to, 659-660
       as a low harmonic rectifier. 597
Permeability µ
       definition, 458-460
       of free space, \mu_0, 458
       relative, \mu_r, 458
Phase asymptotes
       of complex poles, 279-282
       inverted forms, 272
       of real pole, 266-268
       of real zero, 269
       of RHP zero, 270
Phase control
       of resonant converters, 659
       of three-phase rectifiers, 570-575
       of zero-voltage transition dc-dc converter, 696
Phase margin
       vs. closed-loop damping factor, 334-338
       stability test, 333-334
Poles
       complex, Bode plots of, 276-282
       the low Q approximation, 282-284
       real, Bode plots of, 263-268
Pot core data, 752
Powdered iron, 459, 473
Power factor (see also Total harmonic distortion, Displacement factor, Distortion factor)
       definition of. 546-550
       of bridge rectifier, single phase, 566
       of peak detection rectifier, 548-550
       of phase-controlled rectifier, three phase, 573
Power sink element (see Power source element)
Power source element
       in averaged switch models
               current programmed mode, CCM, 423-428
               current programmed mode, DCM, 438-447
               discontinuous conduction mode, 370-382
       definition of. 375-377
       in ideal rectifier model, 592, 599-603, 608-610
       linearization of, 384-385, 425-426
       in loss-free resistor model, 376-379
       properties of, 375-377
PQ core data, 755
Proximity effect
       conductor spacing factor \eta, 478
       interleaving, effect on, 485-487
       layer copper loss, 482-483
       Litz wire, effect of, 487
       MMF diagrams, 479-482
       PWM waveform harmonics, 487-490
       simple explanation, 476-478
       transformer design procedure, accounting for, 519
       winding loss, total, 483-487
```

Pulse width modulation (PWM), 6-8, 17 modulator ac model, 253-254 operation of modulator, 252 spectrum of PWM waveform, 194-195 Push-pull isolated converters based on boost converter, 173 based on buck converter, 164-166, 410 Watkins-Johnson converter, 173 Q factor, 277-282 canonical model, predicted by, 309 closed-loop, vs. phase margin, 334-338 of the CCM buck, boost, and buck-boost converters, 293 the low Q approximation, 282-284 vs. overshoot, 338-339 of parallel resonant circuit, 303 of series resonant circuit, 300-301 Quasi-resonant converters (see also Multi-resonant switch, Quasi-square-wave switch) ac modeling of, 732-737 single-switch 3ø buck rectifiers multi-resonant, 620-621 zero current switching, 619-620 zero-current switching dc-dc full wave, 723-724 half wave, 713-723 zero-voltage switching dc-dc, 726-728 Quasi-square-wave converters, 730-731 Quasi-static approximation, 661 Quiescent operating point, 196-197, 204, 225 Reactance graph paper (*see* Impedance graph paper) Reactive power definition, 550-551 in harmonic trap filters, 582 in phase-controlled rectifiers, 573 Rectifiers (see also Ideal rectifiers, Low harmonic rectifiers), 1 energy storage in single-phase, 599-604 high quality, 541 ideal. 590-626 line-commutated phase control of, 570-575 single-phase, 548-550, 562-568 three-phase, 568-575 three-phase transformer connections in, 582-584 twelve pulse, 582-584 in resonant dc-dc converter, 666-668, 674-676 Regulator system (see also Control system design), 192-193, 323-326, 634-645 Reluctance, 463-466 Resonance Bode plots of complex poles, 276-282 graphical construction examples, 296-309 the low-Q approximation, 282-284 parallel resonant network, 301-307 series resonant network, 301-307 Resonant converters (see also Quasi-resonant converters, Multi-resonant converters, Quasisquare-wave converters, Zero voltage transition converter), 659-710

analysis of, via sinusoidal approximation, 664-679 LCČ, 659-661, 701-705 parallel, 597, 659-660, 674-678, 686-690, 702 resonant link, 662 series, 659-674, 679-686, 690-695, 702 Resonant link converters, 662 Resonant switches (see Quasi-resonant converters, Multi-resonant switch, Quasi-squarewave converters) Right half-plane zero Bode plot of, 269-271 physical origins of, 294-295 Ripple, switching, 17-19, 111-113, 194-196 Root mean square value of commonly-observed converter waveforms, 743-750 vs. Fourier series, 543-546 of near-ideal rectifier currents, table of, 609 of near-ideal rectifier waveforms, 604-609 Rotation of three-terminal cell, 141-142 Saturation of inductors, 462, 465-466 of magnetic materials, 458-460 of transformers, 153-154, 469 Schottky diode, 74, 77, 101 Semiconductor conduction loss boost converter example, 53-57 inclusion in ac model, 209-218 with synchronous rectifier, 73-74 Semiconductor cost, 180 Semiconductor power devices (see also Bipolar junction transistor, Diode, Gate turn-off thyristor, Insulated-gate bipolar transistor, MOS-controlled thyristor, Schottky diode, Silicon controlled rectifier), 62-109 charge control of, 75, 83-85, 94, 98, 101-103 conductivity modulation, 75 majority vs. minority carriers, 74-75 realization of switches using, 62-74 SEPIC (see Single-ended primary inductance converter) Series pass regulator, 4-5 Series resonant converter analysis via sinusoidal approximation, 664-674 dependence of transistor current on load, 702 exact characteristics continuous conduction mode, 679-681 control plane, 684 even discontinuous conduction mode, 682 odd discontinuous conduction mode, 681 output plane, 685-686 introduction to, 659-664 subharmonic modes in, 673-674 zero-current switching in, 690-692 zero-voltage switching in, 692-695 Silicon area (see Switch stress) Silicon controlled rectifier (SCR) construction and characteristics of, 89-92 equivalent circuit, 90

inverter grade, 91 Silicon steel, 459, 473 Single-ended primary inductance converter (SEPIC), 38, 148 averaged switch model of continuous conduction mode, 757-762 discontinuous conduction mode, 379-381 conversion ratio M(D), 151, 381 inverse of, 151, 176 as low-harmonic rectifier, 597-599, 608-609 transformer isolation in, 174-176 Single quadrant switch definitions, 63-64 implementation, 64-67 origins of DCM, 110-113 Sinusoidal approximation, 663, 664-679 Sinusoidal PWM, 612-614 Skin effect (see also Proximity effect), 472-476 Slope compensation (see Artificial ramp) Small ripple approximation in ac modeling approach, 198, 223-224 and average power loss, prediction of, 57 boost example, 25 buck example, 20 Cuk converter example, 30-31 definition, 19 in discontinuous conduction mode, 116 failure of, in two-pole filters, 34-36 Small-signal ac modeling via averaged switch modeling, 239-245 via circuit averaging, 231-245 of CCM converters, 193-260 of current programmed converters, 418-447 of DCM converters, 382-403 via generalized switch averaging, 390-403 of low harmonic rectifiers, 645-652 of quasi-resonant converters, 732-737 of resonant converters, 678 via state-space averaging, 218-231 Snubber networks, 86, 94, 99, 696 Soft switching (see also Zero current switching, Zero voltage switching), 689-696 Spacecraft power system, 9 Spreadsheet design of converters, 180-183 State equations of a network, 218-221 State-space averaging, 218-231 discussion, 223-226 example: nonideal buck-boost converter, 227-231 summary of result, 221-222 Steady state inductor current waveform, 22 operating point, 196-197, 204, 225 Subharmonic modes of series resonant converter, 673-674 number ξ, 679

Switch averaged modeling of, 239-245, 377, 390-403 current-bidirectional two-quadrant, 67-70 four-quadrant, 71-73 ideal SPDT in converters, 4-6, 15-16, 24, 29 ideal SPST, 62-63 passive vs. active, 64-65, 91 power dissipated by ideal, 6, 17 quasi-resonant, 711-737 realization of, using semiconductor devices, 62-74 single-quadrant, 64-67 synchronous rectifier, 73-74 voltage-bidirectional two-quadrant, 70-71 Switch conversion ratio u definition, 392 DCM buck example, 395-401 in generalized canonical model, 405 of multi-resonant switch, 729 of quasi-resonant switches full-wave ZCS, 723-724 full-wave ZVS, 727 half-wave ZCS, 713, 720-721 half-wave ZVS, 727 small-signal ac modeling using, 732-737 of quasi-square-wave switches, 731 Switched mode, 3-4 Switching frequency converter efficiency vs., 103-104 definition of, 16 transformer size vs., 527 Switching harmonics (see also Ripple, switching), 6 removal of via averaging, 194-196 Switching loss (see also Soft switching, Zero current switching, Zero voltage switching) averaged switch modeling of, 241-245, 259-260 with clamped inductive load, 94-97 and current tailing, 96-97 and device capacitances, 100-101 and diode recovered charge, 97-100, 101-103 effect on converter efficiency, 103-104 and ringing waveforms, 101-103 and stray inductances, 100-101 Switch stress S, 177-180 Switch utilization U, 177-180 Synchronous rectifier, 73-74 Temperature rise in a converter, 2 in magnetics, 752 Thyristor (see Gate turn-off thyristor, MOS-controlled thyristor, Silicon controlled rectifier) Topologies of converters (see also Boost, Bridge configuration, Buck, Buck-boost, Cuk converter, Forward converter, Transformer-isolated converters, etc.) Cascade connections, 138-141 Converter synthesis, 146-150

Differential connection of load, 142-146 Evaluation and comparison, 177-183, 608-609 Inversion of source and load, 136-137 Low-harmonic single-phase rectifiers, 593-599 Low-harmonic three-phase rectifiers, 608-621 Quasi-resonant converters, 724-731 Resonant converters, 659-664 Rotation of three-terminal cell, 141-142 Transformer isolation, 150-177 Total harmonic distortion (THD) of current-programmed rectifiers, 639 definition. 550 vs. distortion factor, 550-551 IEEE-519 limits, 559-561 of peak detection rectifier, 551-552 of single-phase bridge rectifiers, 551-552, 566-570 of three-phase bridge rectifiers, 571-572, 575 Transfer functions (see also Bode plots) of the buck, boost, and buck-boost converters, 292-293 of current programmed converters, 422-423, 427, 436-438, 446-447 of DCM converters, 388-390 graphical construction of, 296-309 of low-harmonic rectifiers, 649-650, 651 measurement of, 309-311 predicted by canonical model, 247-248, 292-293 Transformer connections in three-phase rectifiers, 582-584 Transformer-isolated converters, 150-177 boost-derived topologies, 171-173 Cuk converter, 176-177 evaluation and comparison of, 177-183 flyback, 166-171 forward, 159-164 full bridge buck-derived, 154-157 half-bridge buck-derived, 157-159 multiple outputs and cross regulation, 151-152 push-pull buck-derived, 164-166 SEPIC. 174-176 transformer model, 152-154, 466-471 use of volt-second balance in, 153-154, 156-157 Transformers *B-H* loop in, 153, 500-501 design of, derivation of procedure, 517-521 examples, 524-531 step-by-step procedure, 521-524 winding area optimization, 513-517 flyback transformer, 166-167 leakage inductance, 154, 469-471 magnetizing inductance, 152-154, 468-469 modeling of, 152-154, 466-471 SEPIC transformer, 174-175 volt-second balance in, 153-154, 156-157 Triplen harmonics in three-phase four-wire networks, 552-553

in three-phase inverter modulation schemes, 614 in three-phase rectifier circuits, 568-569 in three-phase three-wire networks, 553-554 Twelve-pulse rectifier, 582-584 Two-quadrant switches (see Switch) Universal-input rectifiers, 602 Variable-speed ac drive, 7-8 Voltage conversion ratio (see Conversion ratio M) Voltage injection, 357-359 Voltage-source inverter, 70, 146-147 Volt-second balance (*see* Inductor volt-second balance) Watkins-Johnson converter, 148, 150, 173 inverse of, 148, 150 isolated push-pull, 173 Window area W_A allocation of, to minimize total copper loss, 513-517 definition, 506-507 ferrite core tables, 752-755 Window utilization factor K_{μ} , 507 Wire area A_w inductor design, 506-507, 509 American wire gauge (AWG) table, 755-756 Zero-current switching (ZCS), 662 in quasi-resonant converters, 712-726 in quasi-square-wave converters, 730-731 in series resonant converter, 690-692 in single-switch three-phase low-harmonic rectifiers, 619-621 ZCS/ZVS boundary, 702-705 Zero-voltage switching (ZVS), 662 in LCC resonant converter, 703-705 in multi-resonant converters, 729 in quasi-resonant converters, 726-728 in quasi-square-wave converters, 730-731 in series resonant converter, 692-695 in single-switch three-phase low-harmonic rectifiers, 619-621 in zero-voltage transition converter, 695-696 ZVS/ZCS boundary, 702-705 Zero-voltage transition buck-derived converter, 695-696

Fundamentals of Power Electronics

Errata, first edition

Back

Errors can be reported for inclusion on this list by sending email to <u>Bob Erickson</u>. Please include page number and a short description.

- Page ii, small-print disclaimer near bottom of page contains two misspelled words
- Page 10, paragraph beginning "Design of the converter..." "line-to-transfer functions" should read "line-to-output transfer functions"
- Page 49, Eq. (3.19) RHS of equation should be divided by R
- Page 86, Fig. 4.35(a) Units of horizontal axis should be A
- Page 172, Fig. 6.36 The bottom of the figure is cut off. Transistor Q_4 conducts during the first subinterval of every switching period.
- Page 180, third line under heading 6.4.2 typo "votlage" should read "voltage"
- Page 181, Table 6.2 Values of L and C are missing. The values are: L = 25.96 uH, C = 25.0 uF.
- Page 188, problem 6.8(d) Forward voltage drops of diodes D₁ and D₂ are equal to 0.7 V.
- Page 237, second line following Eq. (7.126) "small" should read "smaller"
- Page 241, third paragraph, first line reads "valiables" -- should read "variables"
- Page 250, Equation (7.144) should read: e(s) = (Vg - V) - sLI/DD' (plus sign should be minus sign)
- Page 275, Figure 8.15
 Phase asymptote for frequencies between 10*f₁ and f₂/10 should be +90 deg instead of -90 deg.
- Pages 289-293, Equation (8.112) and Table 8.2 Missing factor of *D*' in Eq. (8.112). Mistake propagates to Eqs. (8.113), (8.121), (8.123), (8.124), (8.127), and Fig. 8.26. Buck-boost G_{d0} entry in Table 8.2 is also incorrect. Corrected Section 8.2.1 and Table 8.2 are in attached pdf file.
- Page 300, line following Eq. (8.144) Should read: "Subsitution of Eq. (8.142) into Eq. (8.144) leads to"
- Page 311, last sentence

is missing a period

- Page 333, fourth line following Eq. (9.20) reads "simple" -- should be "simply"
- Page 347, first line of text Equation reference should read "Eq. (7.149)"
- Page 366, Problem 9.8, last sentence of paragraph (before (a)) should read "The pulse-width modulator circuit obeys Eq. (7.149)." -- not "(7.132)"
- Page 385, Table 10.2 g_2 for the buck-boost converter is equal to $2/MR_e$
- Page 419, Figure 11.12(a) $i_g(t)$ is the current flowing out of the source $v_g(t)$
- Page 427, Figure 11.20 Value of ac resistance is inverted. The value should read: -*R/D*^2
- Page 488, second paragraph, fourth sentence Change "greater" to "smaller", so that the sentence reads: "The skin depth *d* is smaller for high frequencies..."
- Page 516, Equations (14.14) and (14.15) Summation limits should be *j* = 1 to *k*
- Page 519, Equation (14.28) should contain a factor of 4 in denominator
- Page 534, Equation (14.84) should read: $B_{pk} = B_{max} + LI_{dc}/nA_c$
- Page 546, Equation (15.14)
 Power loss should be (rms voltage)² / Rshunt
- Page 548, last sentence change "displacement factor" to "distortion factor"
- Page 576, end of first sentence after Eq. (16.12) i_s should read i_r
- Page 637, Equation (18.27) Corrected version is in <u>attached pdf file</u>.
- Page 654, Figure 18.20, and Problem 18.2 Flyback transformer turns ratio is 1:1
- Appendix 3, page 760, Figure A3.3 Polarity of dependent current source should be reversed.

update 10/25/99

Fundamentals of Power Electronics

R. W. Erickson

Solutions to Selected Problems

Solutions to selected problems at the end of chapters in the text *Fundamentals of Power Electronics* are listed below. These are intended as an educational supplement to the text, for the use of students who have purchased the book. All files copyright R. W. Erickson 1998.

These files can be read using the Adobe Acrobat viewer, available free from the Adobe Acrobat web site.

<u>Up</u>

Chapter 2

- <u>Problem 2.2</u> 144kB. Analysis of a SEPIC in a voltage regulator application.
- <u>Problem 2.3</u> 168kB. Inductor current and capacitor voltage ripples in the SEPIC.

Chapter 3

- Problem 3.3 192kB. Modeling efficiency and losses in a buck converter with input filter.
- <u>Problem 3.6</u> 148kB. Comparison of boost and buck-boost converters in a voltage step-up application.

Chapter 4

• <u>Problem 4.4</u> 196kB. Switch realization in a converter that is probably unfamiliar.

Chapter 5

- <u>Problem 5.5</u> 81kB. CCM/DCM boundary for the Cuk converter.
- <u>Problem 5.6</u> 184kB. Solution of the Cuk converter in DCM.

Chapter 6

• <u>Problem 6.1</u> 144kB. Analysis of a tapped-inductor boost converter.

Chapter 8

• <u>Sample problem</u> 164kB. A solved problem on transfer function asymptotes, similar to problems 8.1 - 8.4.

Chapter 12

• <u>Problem 12.1</u> 116kB. Magnetic circuit analysis.

Update 11/23/98 rwe

Proximity Effect Functions

The functions below were used to generate Figs. 12.35, 12.36, and 12.38. The functions are written in Microsoft Visual Basic, and were called by an Excel spreadsheet. The functions can be easily modified for other programming languages.

Functions Gone and Gtwo implement Eq. (12.73). Function FR(phi, M) is identical to Eq. (12.84). Figure 12.32 is a plot of FR for various values of M and φ . Figure 12.33 is a plot of FR(phi, M)/phi.


Function Pj(Phi1, M, j, D) is a normalized version of Eq. (12.89), the power loss in harmonic *j*. Function FH(phi1, M, D) coincides with Eq. (12.90) and (12.91). The series is summed numerically.

The copper loss in a winding is evaluated as follows. First, the dc and fundamental components of the current waveform are evaluated using Eq. (12.86). Then the functions FH and FR are evaluated. Finally, the results are plugged into Eq. (12.92).

```
Option Explicit
Function cosh(x)
     \cosh = 0.5 * (\exp(x) + \exp(-x))
End Function
Function sinh(x)
     \sinh = 0.5 * (\exp(x) - \exp(-x))
End Function
Function Gone(phi)
     Gone = (sinh(2 * phi) + Sin(2 * phi)) / (cosh(2 * phi) -
          Cos(2 * phi))
End Function
Function Gtwo(phi)
     Gtwo = (sinh(phi) * Cos(phi) + cosh(phi) * Sin(phi)) /
           (\cosh(2 * \text{phi}) - \cos(2 * \text{phi}))
End Function
Function FR(phi, M)
     FR = phi * (Gone(phi) + 2 / 3 * (M * M - 1) * (Gone(phi) - 2
           * Gtwo(phi)))
End Function
Function pi()
     pi = 3.14159265
End Function
Function Pj(phi1, M, j, D)
     Dim sj, Ga
     sj = Sqr(j)
     Ga = Gone(phi1 * sj)
     Pj = (1 / (j * sj)) * (Sin(j * pi() * D)) ^ 2 * (Ga + 2 / 3 * C)
           (M * M - 1) * (Ga - 2 * Gtwo(phi1 * sj)))
End Function
```


```
Function FH(phi1, M, D)
     Dim P1, Ptot, Pke, Pko, Peps, j, Pk
P1 = Pj(phi1, M, 1, D)
      Pko = P1
     Pke = Pj(phi1, M, 2, D)
      Pk = Pko + Pke
      Ptot = P1
      Peps = P1 * 0.0002
      j = 3
      Ďо
            Pko = Pj(phi1, M, j, D)
            j = j + 1
Pke = Pj(phi1, M, j, D)
            Pk = Pke + Pko
            Ptot = Ptot + Pk
     j = j + 1
Loop Until Pk < Peps
      FH = Ptot / P1
End Function
```

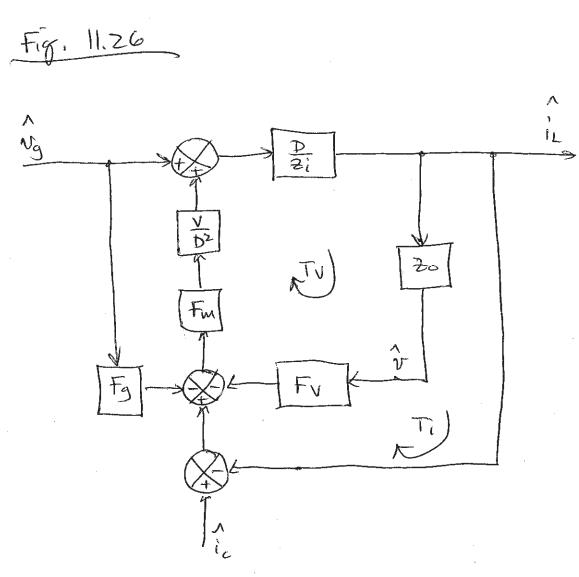Perivation of line-to-output transfer RWÉrickson function, P. 437, Eqs. (11.84) and (11.85)



ove method: manipulate ing so it appears as a disturbance (see section 9.2.1 and Figr 9.4(6)) =) push ing blocks so the ing signal comes in in near the output (at the pickoff point ______) [2]

push the Fg path upwards;

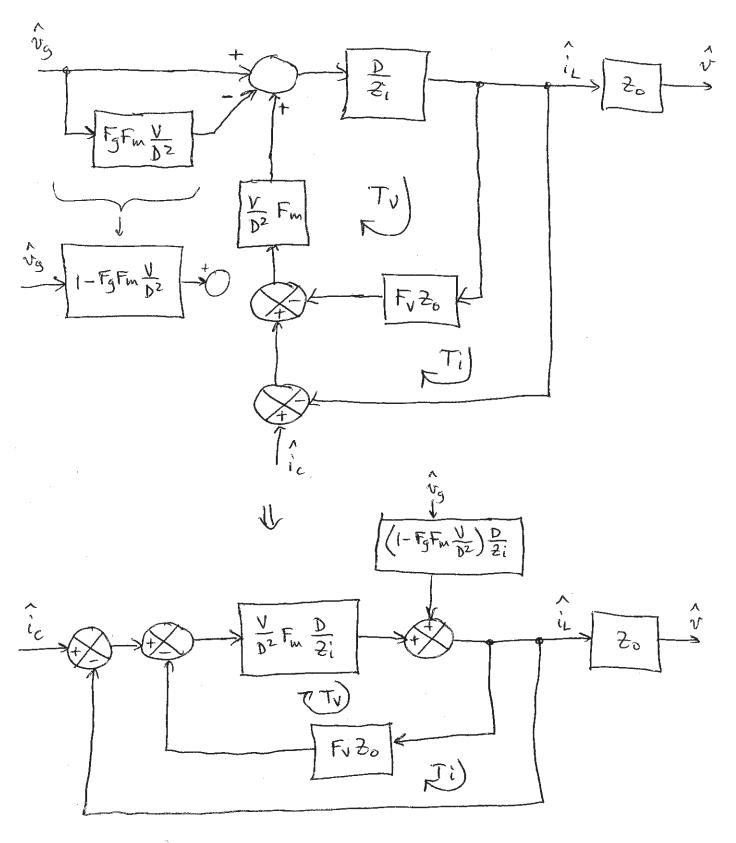

2

so $\frac{\hat{v}}{\hat{v}_{g}} = \left(1 - F_{g}F_{m}\frac{V}{D^{2}}\right)\frac{D}{2i}\cdot 2_{0}\cdot \frac{1}{1+T_{V}}\cdot \frac{1}{1+T_{i}} = \frac{G_{go}}{1+T_{i}}$ with $T_{V} = \frac{V}{D^{2}}F_{m}\frac{D}{2i}F_{V}2_{0}$, $T_{i} = \frac{1}{F_{V}2_{0}}\frac{T_{V}}{1+T_{V}}$

The disturbance is enters at a summing hode
that is internal to both the Ty and Ti loops.
Hence,
$$\frac{\hat{v}}{\hat{v}_g} = (1 - F_3 F_m \frac{V}{D^2}) \frac{P}{Z_i} \frac{2}{20} \cdot \frac{1}{1+T_V} \cdot \frac{1}{1+T_i}$$

gain when $T_i \rightarrow 0$ and $T_V \rightarrow 0$
In Eqs. (11.84) and (11.85) this transfer function
is written as
 $\frac{G_{50}}{1+T_i}$
with $G_{50} = (1 - F_3 F_m \frac{V}{D^2}) \frac{P}{Z_i} \frac{2}{20}$
 $1 + T_V$

. 2


Fundamentals of Power Electronics

Robert W. Erickson University of Colorado, Boulder

Chapter 1: Introduction

- 1.1. Introduction to power processing
- 1.2. Some applications of power electronics
- 1.3. Elements of power electronicsSummary of the course

1.1 Introduction to Power Processing

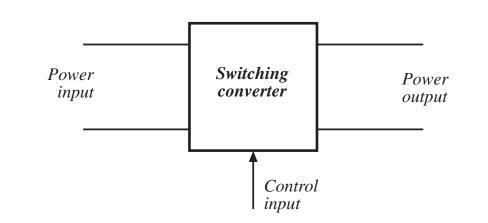


Dc-dc conversion:Change andAc-dc rectification:Possibly conDc-ac inversion:Produce sinu
magnitud

Change and control voltage magnitude Possibly control dc voltage, ac current Produce sinusoid of controllable magnitude and frequency

Ac-ac cycloconversion: Change and control voltage magnitude and frequency

Control is invariably required

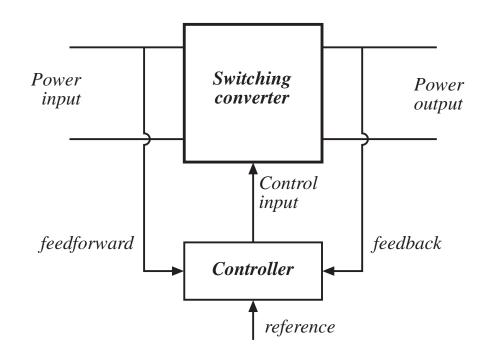


High efficiency is essential


 $\eta = \frac{P_{out}}{P_{in}}$

$$P_{loss} = P_{in} - P_{out} = P_{out} \left(\frac{1}{\eta} - 1\right)$$

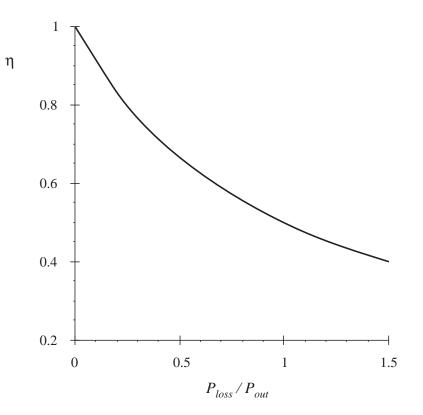High efficiency leads to low power loss within converter
Small size and reliable operation is then feasible
Efficiency is a good measure of converter performance




A high-efficiency converter

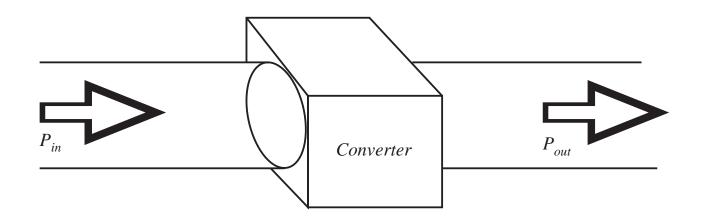


A goal of current converter technology is to construct converters of small size and weight, which process substantial power at high efficiency

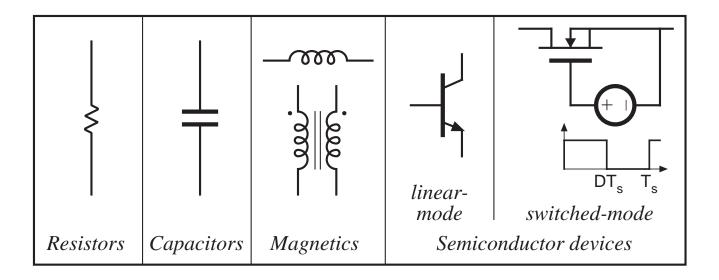Devices available to the circuit designer




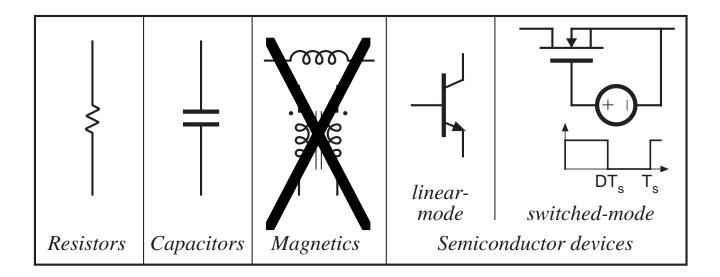Devices available to the circuit designer




Signal processing: avoid magnetics

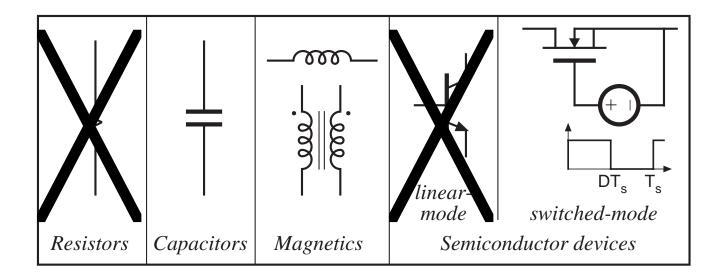Devices available to the circuit designer




Power processing: avoid lossy elements

Power loss in an ideal switch

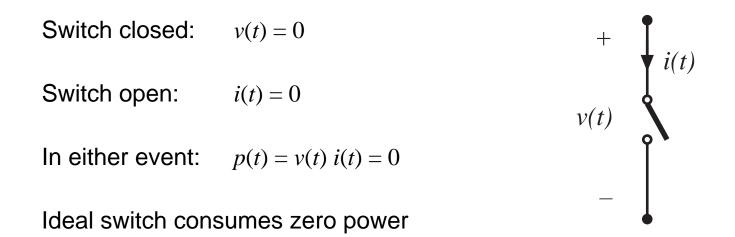


A simple dc-dc converter example

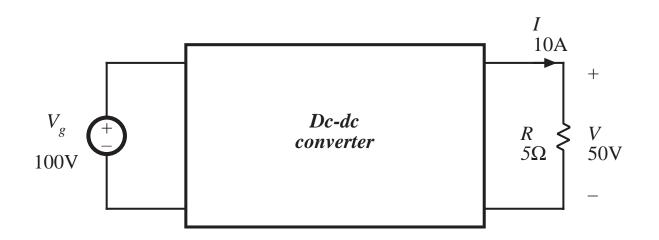

Input source: 100V Output load: 50V, 10A, 500W How can this converter be realized?


Dissipative realization

Resistive voltage divider

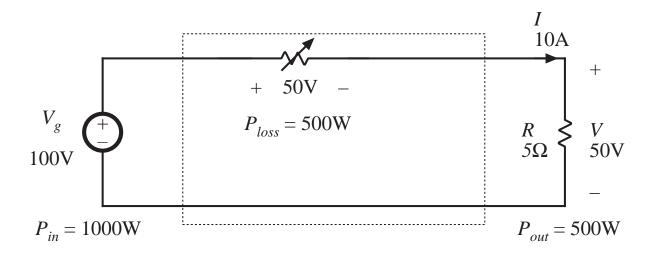


Dissipative realization

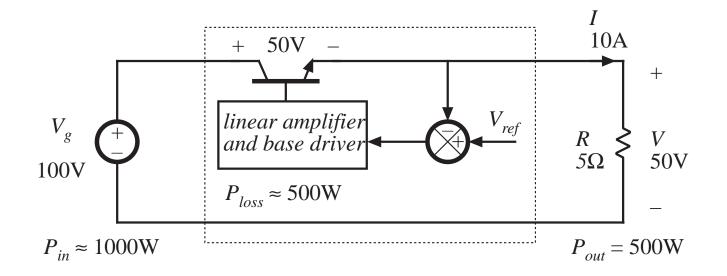Series pass regulator: transistor operates in active region




Use of a SPDT switch

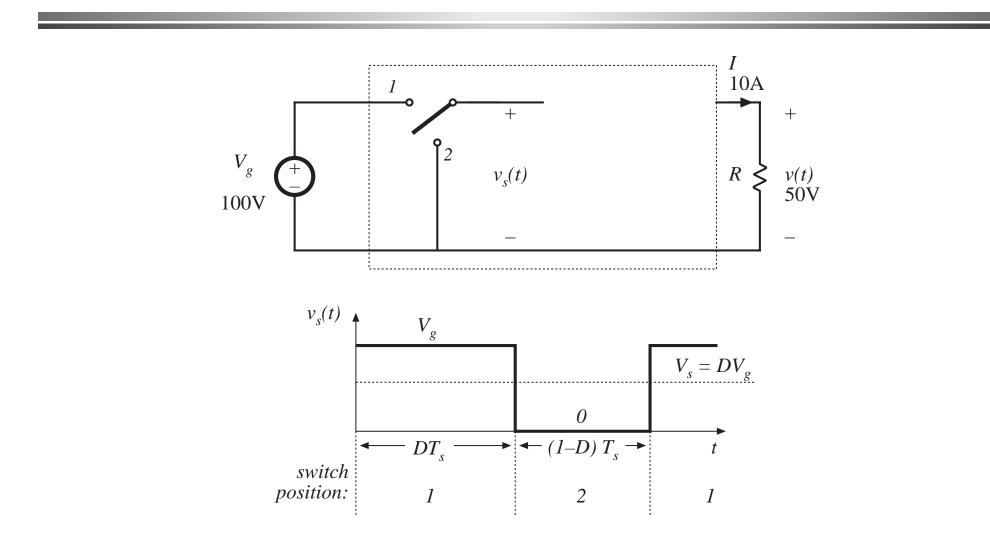

Fundamentals of Power Electronics

Chapter 1: Introduction

The switch changes the dc voltage level

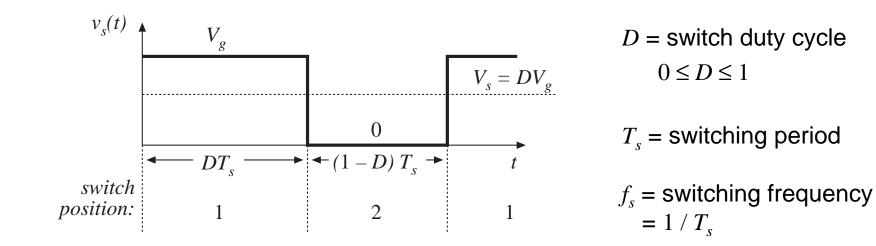


DC component of $v_s(t)$ = average value:

$$V_s = \frac{1}{T_s} \int_0^{T_s} v_s(t) \, dt = DV_g$$

Fundamentals of Power Electronics

Addition of low pass filter

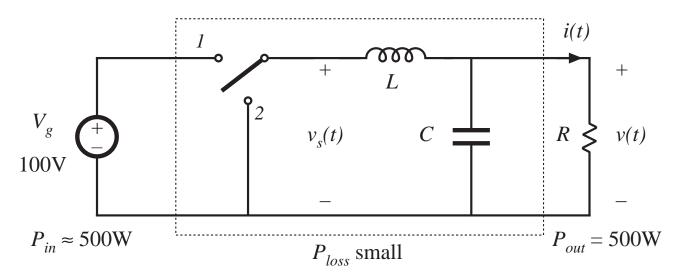
Addition of (ideally lossless) *L*-*C* low-pass filter, for removal of switching harmonics:




- Choose filter cutoff frequency f_0 much smaller than switching frequency f_s
- This circuit is known as the "buck converter"

Fundamentals of Power Electronics

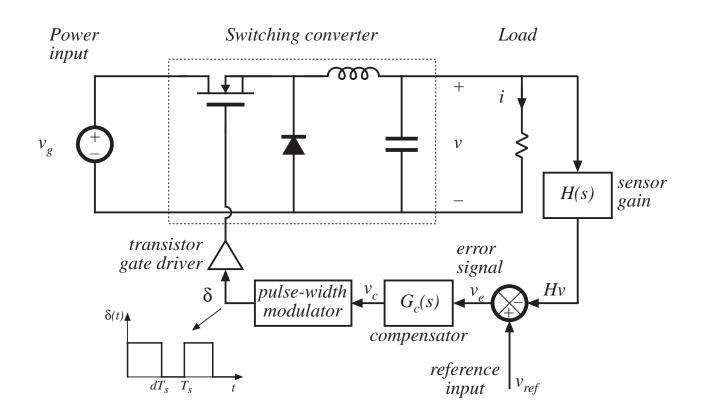Addition of control system for regulation of output voltage




The boost converter

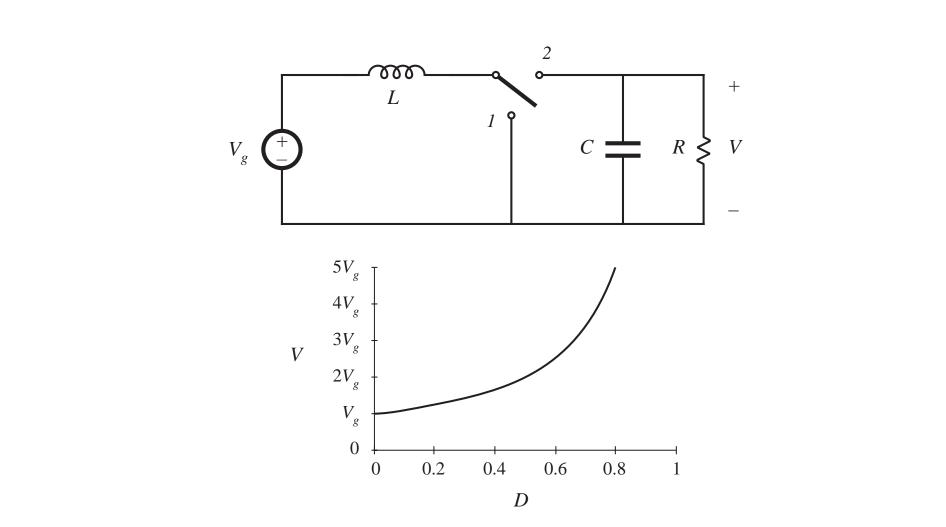

Fundamentals of Power Electronics

Chapter 1: Introduction

A single-phase inverter

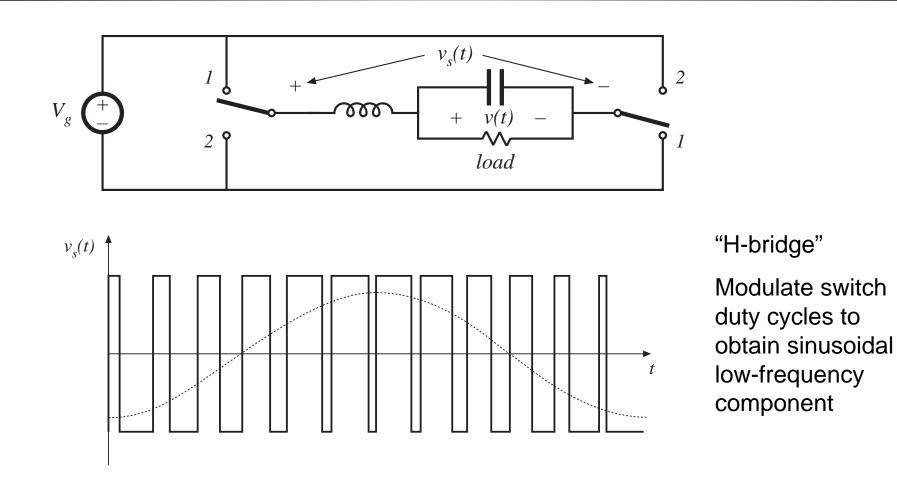


1.2 Several applications of power electronics


Power levels encountered in high-efficiency converters

- less than 1 W in battery-operated portable equipment
- tens, hundreds, or thousands of watts in power supplies for computers or office equipment
- kW to MW in variable-speed motor drives
- 1000 MW in rectifiers and inverters for utility dc transmission lines


A computer power supply system

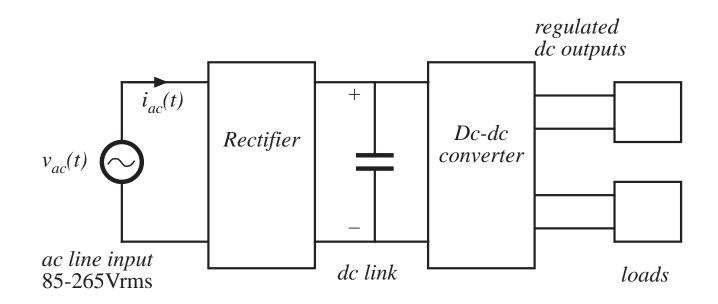

A spacecraft power system

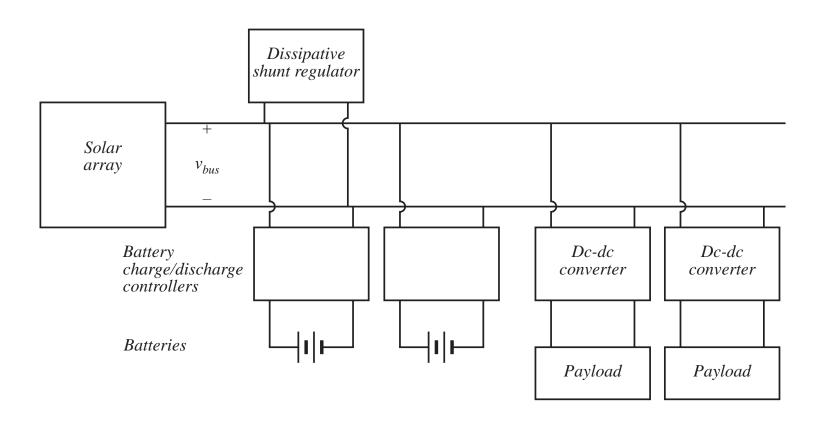

A variable-speed ac motor drive system

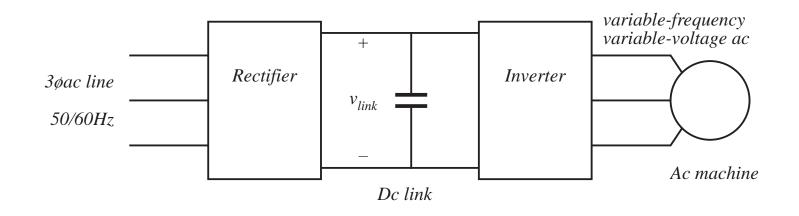


1.3 Elements of power electronics

Power electronics incorporates concepts from the fields of analog circuits electronic devices control systems power systems magnetics electric machines numerical simulation


Part I. Converters in equilibrium

Inductor waveforms

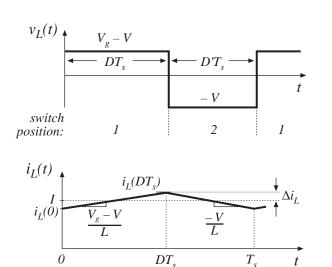


Discontinuous conduction mode Transformer isolation

Averaged equivalent circuit

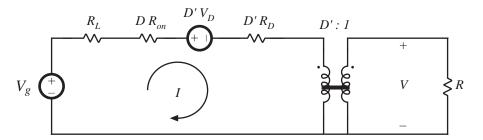


Predicted efficiency

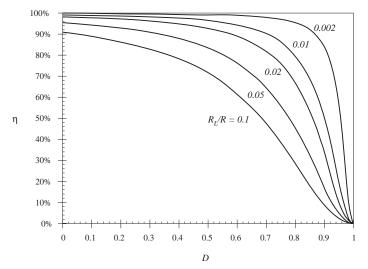

Chapter 1: Introduction

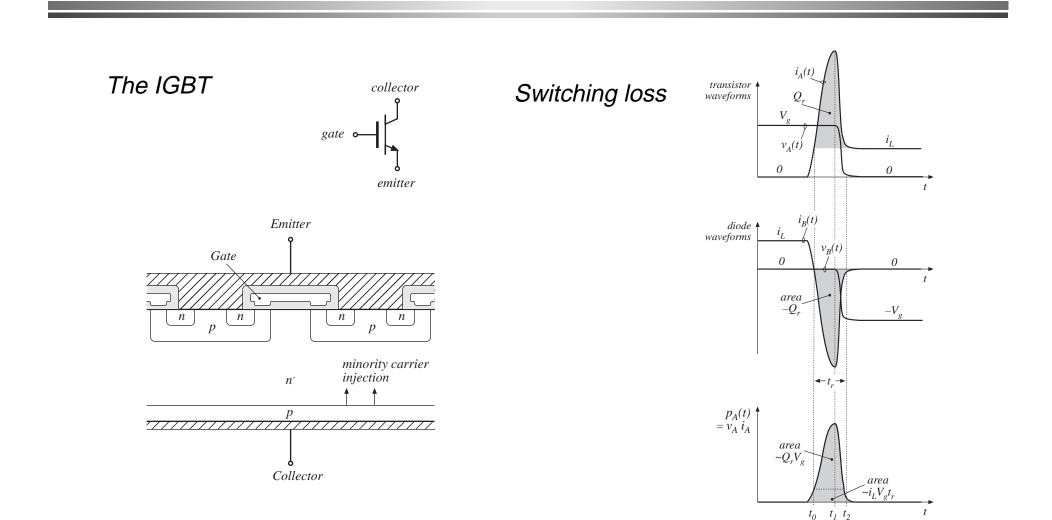Switch realization: semiconductor devices




Fundamentals of Power Electronics

Part I. Converters in equilibrium

- 2. Principles of steady state converter analysis
- 3. Steady-state equivalent circuit modeling, losses, and efficiency
- 4. Switch realization
- 5. The discontinuous conduction mode
- 6. Converter circuits

Part II. Converter dynamics and control

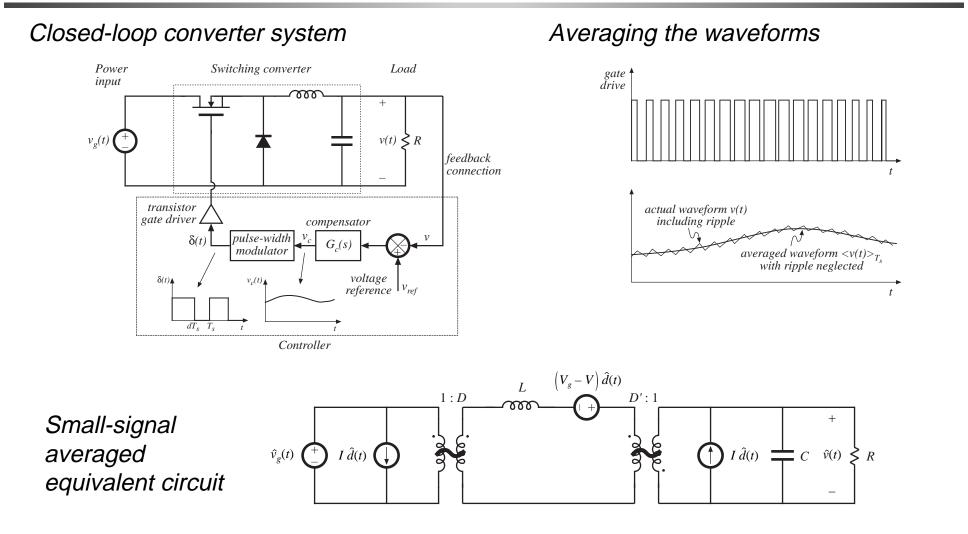


Fundamentals of Power Electronics

Part II. Converter dynamics and control

- 7. Ac modeling
- 8. Converter transfer functions
- 9. Controller design
- 10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
- 11. Current-programmed control

Part III. Magnetics

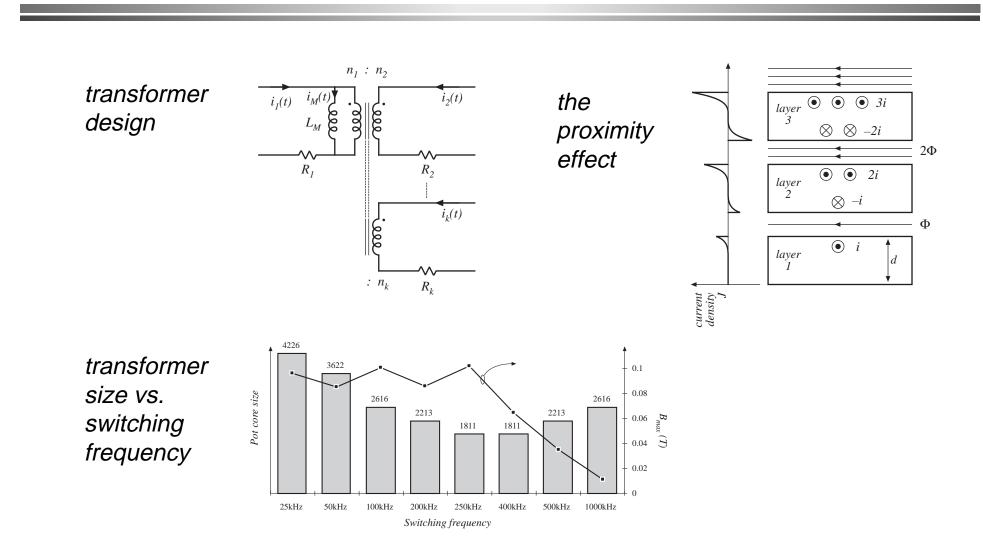


Fundamentals of Power Electronics

Chapter 1: Introduction

Part III. Magnetics

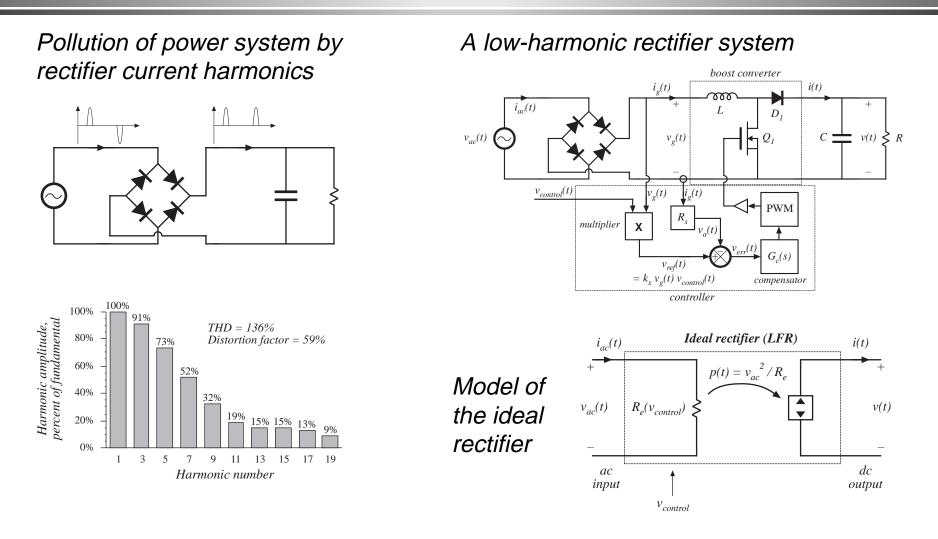- 12. Basic magnetics theory
- 13. Filter inductor design
- 14. Transformer design

Part IV. Modern rectifiers, and power system harmonics




Fundamentals of Power Electronics

Part IV. Modern rectifiers, and power system harmonics

- 15. Power and harmonics in nonsinusoidal systems
- 16. Line-commutated rectifiers
- 17. The ideal rectifier
- 18. Low harmonic rectifier modeling and control

Part V. Resonant converters

The series resonant converter

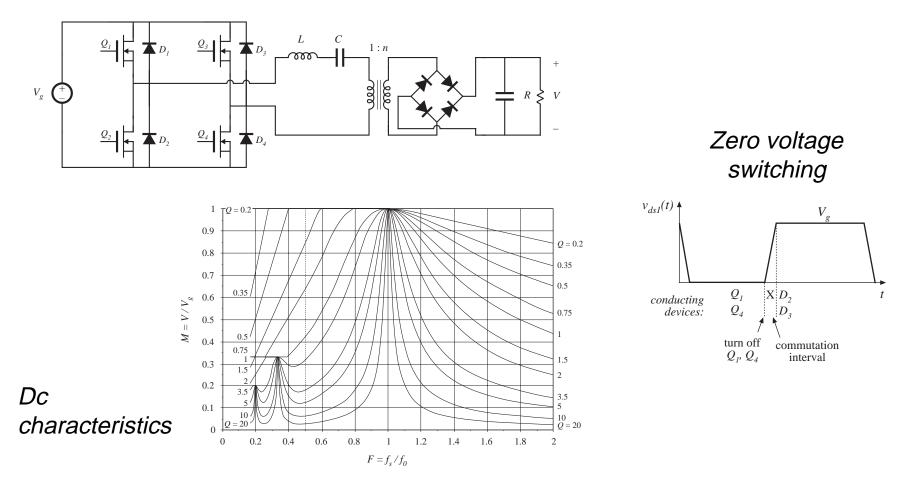

Fundamentals of Power Electronics


Part V. Resonant converters

- 19. Resonant conversion
- 20. Quasi-resonant converters

Chapter 2 Principles of Steady-State Converter Analysis

- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation
- 2.3. Boost converter example
- 2.4. Cuk converter example
- 2.5. Estimating the ripple in converters containing twopole low-pass filters
- 2.6. Summary of key points


2.1 Introduction **Buck converter**

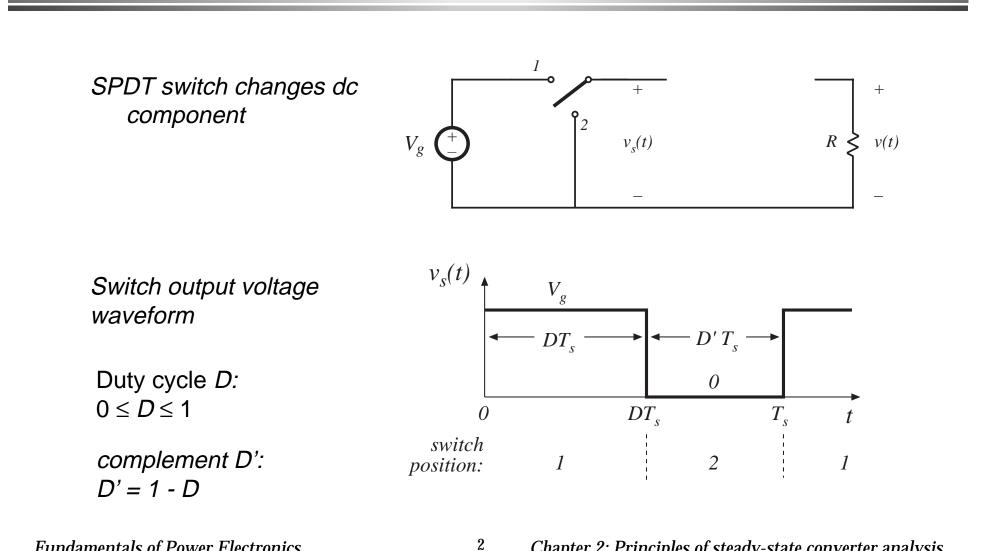

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis

Dc component of switch output voltage

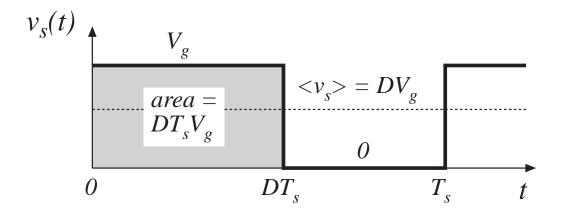

Fourier analysis: Dc component = average value

$$\left\langle v_{s} \right\rangle = \frac{1}{T_{s}} \int_{0}^{T_{s}} v_{s}(t) dt$$


 $\left\langle v_{s} \right\rangle = \frac{1}{T_{s}} \left(DT_{s}V_{g} \right) = DV_{g}$

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis

3

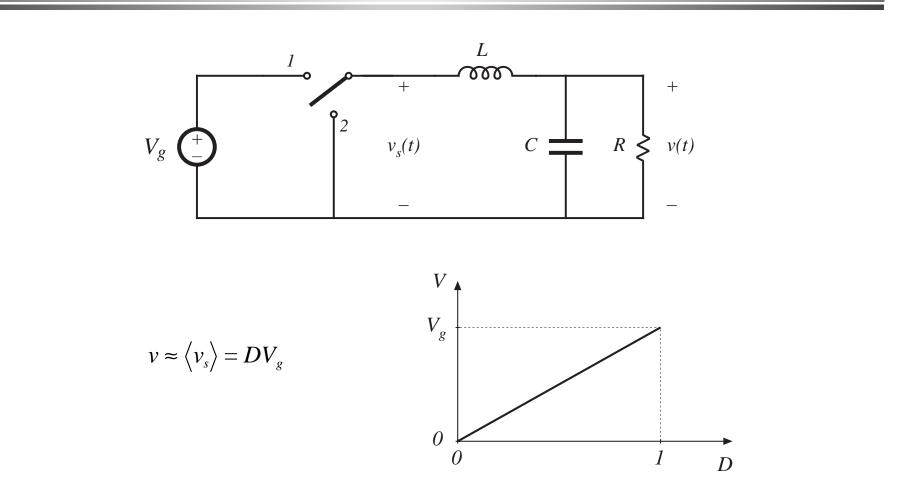Insertion of low-pass filter to remove switching harmonics and pass only dc component




4

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis

Three basic dc-dc converters

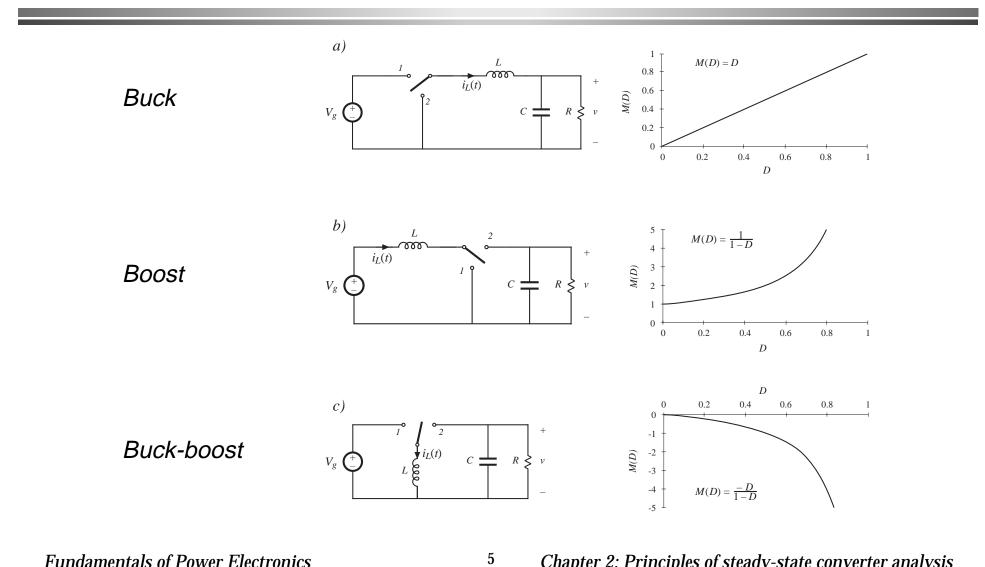

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis


Objectives of this chapter

- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of *inductor volt-second balance* and *capacitor charge (amp-second) balance*
- Introduce the key *small ripple approximation*
- Develop simple methods for selecting filter element values

6


• Illustrate via examples

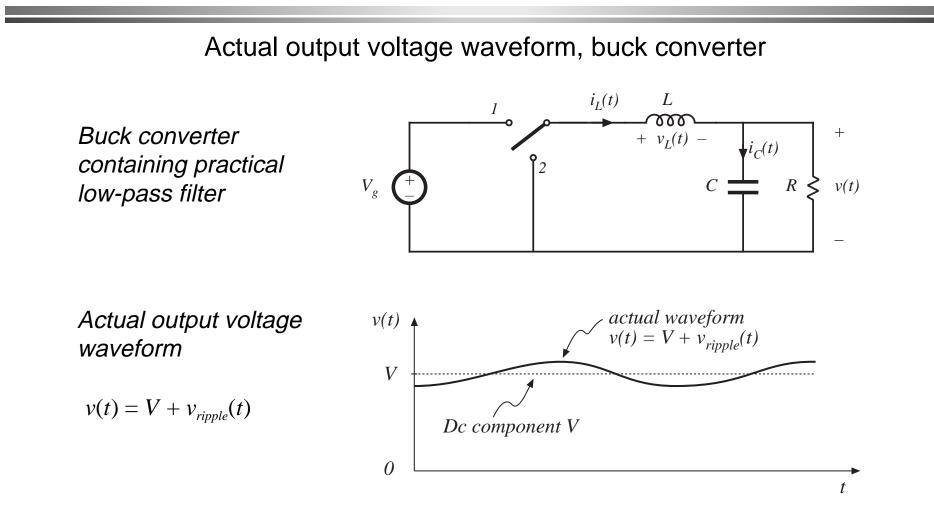2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation



7

The small ripple approximation

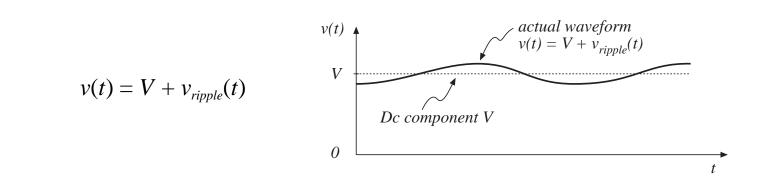


In a well-designed converter, the output voltage ripple is small. Hence, the waveforms can be easily determined by ignoring the ripple:

$$\left\| v_{ripple} \right\| << V$$
$$v(t) \approx V$$

Fundamentals of Power Electronics


Chapter 2: Principles of steady-state converter analysis

Buck converter analysis: inductor current waveform

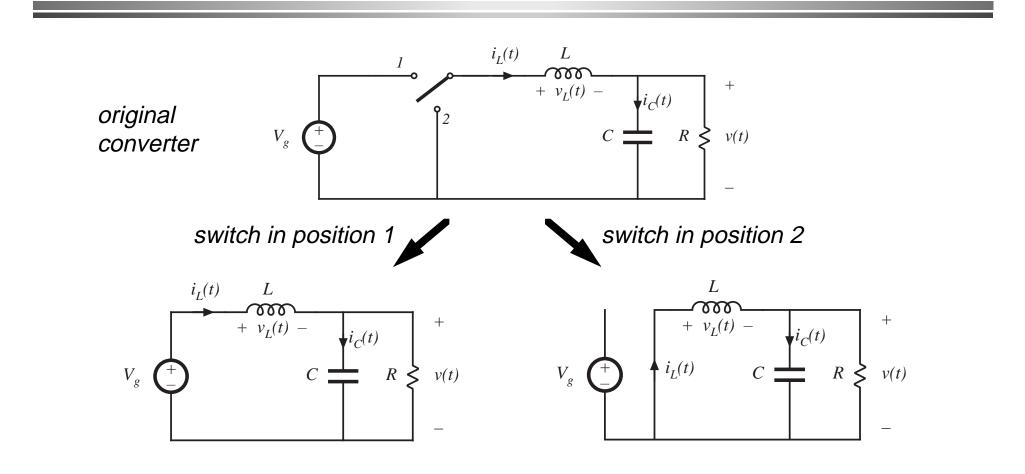

Chapter 2: Principles of steady-state converter analysis

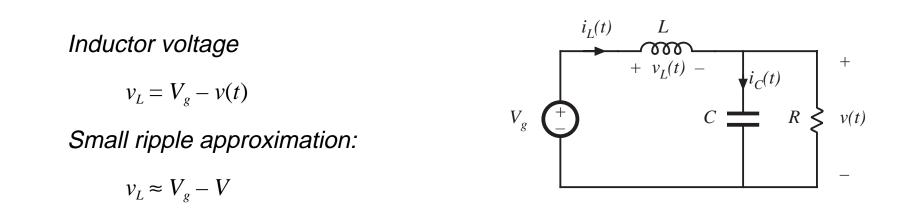Inductor voltage and current Subinterval 1: switch in position 1



Knowing the inductor voltage, we can now find the inductor current via

$$v_L(t) = L \, \frac{di_L(t)}{dt}$$

Solve for the slope:


$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} \approx \frac{V_g - V}{L}$$

⇒ The inductor current changes with an essentially constant slope

Fundamentals of Power Electronics

¹⁰ Chapter 2: Principles of steady-state converter analysis

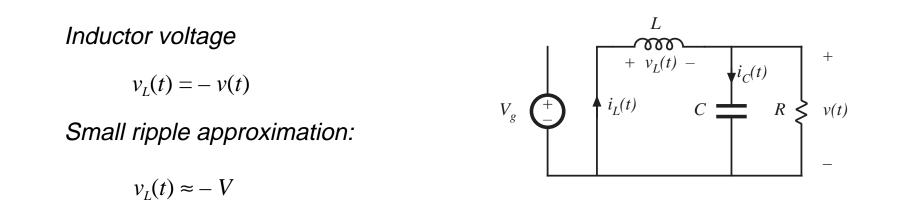Inductor voltage and current Subinterval 2: switch in position 2



Knowing the inductor voltage, we can again find the inductor current via


$$v_L(t) = L \, \frac{di_L(t)}{dt}$$

Solve for the slope:

 $\frac{di_{L}(t)}{dt} \approx -\frac{V}{L} \qquad \qquad \Rightarrow \quad The inductor current changes with an essentially constant slope$

11 Chapter 2: Principles of steady-state converter analysis


Inductor voltage and current waveforms

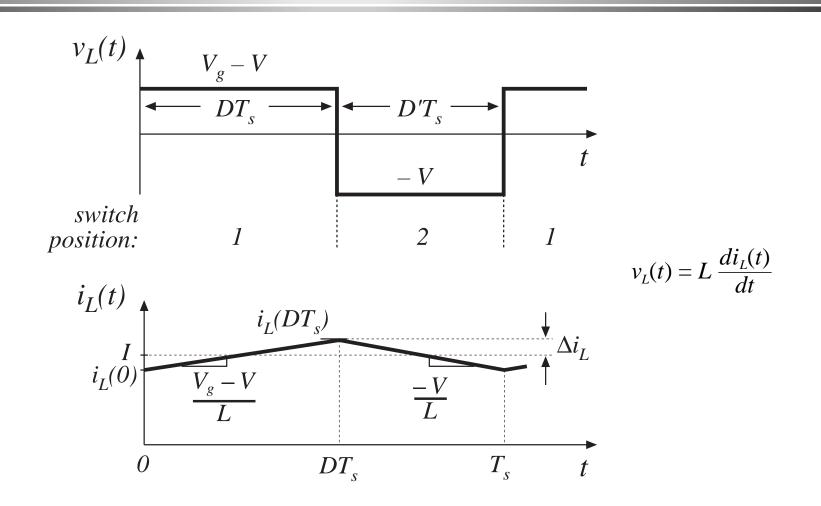

Fundamentals of Power Electronics

¹² *Chapter 2: Principles of steady-state converter analysis*

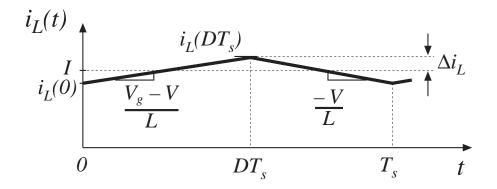Determination of inductor current ripple magnitude



 $(change in i_L) = (slope)(length of subinterval)$ $\left(2\Delta i_L\right) = \left(\frac{V_g - V}{L}\right) \left(DT_s\right)$


$$\Rightarrow \qquad \Delta i_L = \frac{V_g - V}{2L} DT_s \qquad \qquad L = \frac{V_g - V}{2\Delta i_L} DT_s$$

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis

13

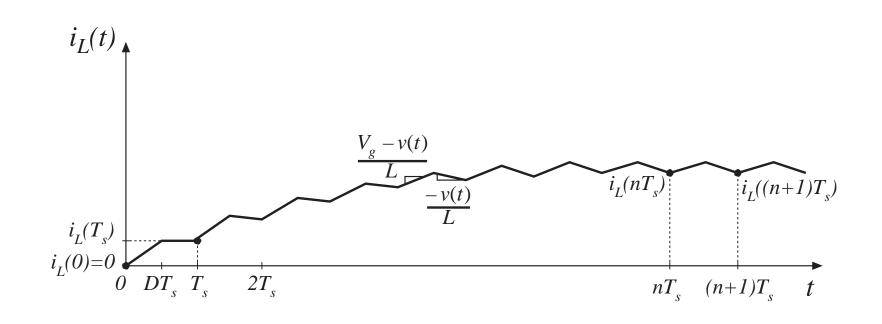Inductor current waveform during turn-on transient



When the converter operates in equilibrium:

 $i_L((n+1)T_s) = i_L(nT_s)$

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis

The principle of inductor volt-second balance: Derivation

Inductor defining relation:

$$v_L(t) = L \, \frac{di_L(t)}{dt}$$

Integrate over one complete switching period:

$$i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$

In periodic steady state, the net change in inductor current is zero:

$$0=\int_0^{T_s}v_L(t)\ dt$$


Hence, the total area (or volt-seconds) under the inductor voltage waveform is zero whenever the converter operates in steady state. An equivalent form:

$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) \ dt = \left\langle v_L \right\rangle$$

The average inductor voltage is zero in steady state.

Inductor volt-second balance: Buck converter example

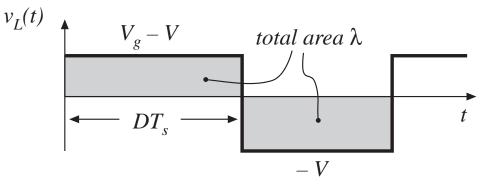Inductor voltage waveform, previously derived:



Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) \, dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$

Average voltage is

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

Equate to zero and solve for V:

$$0 = DV_g - (D + D')V = DV_g - V \qquad \Rightarrow \qquad V = DV_g$$

The principle of capacitor charge balance: Derivation

Capacitor defining relation:

$$i_C(t) = C \, \frac{dv_C(t)}{dt}$$

Integrate over one complete switching period:


$$v_C(T_s) - v_C(0) = \frac{1}{C} \int_0^{T_s} i_C(t) dt$$

In periodic steady state, the net change in capacitor voltage is zero:


$$0 = \frac{1}{T_s} \int_0^{T_s} i_C(t) \, dt = \left\langle i_C \right\rangle$$

Hence, the total area (or charge) under the capacitor current waveform is zero whenever the converter operates in steady state. The average capacitor current is then zero.

2.3 Boost converter example

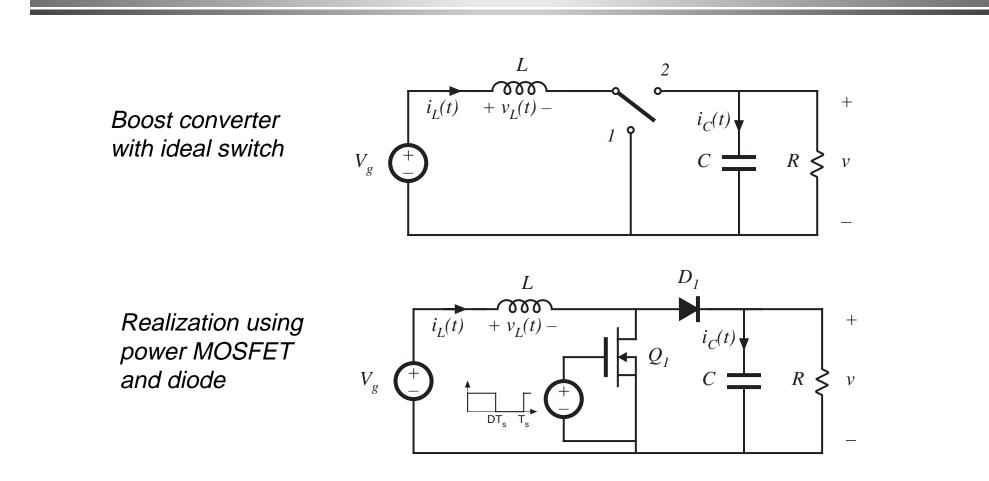

Boost converter analysis

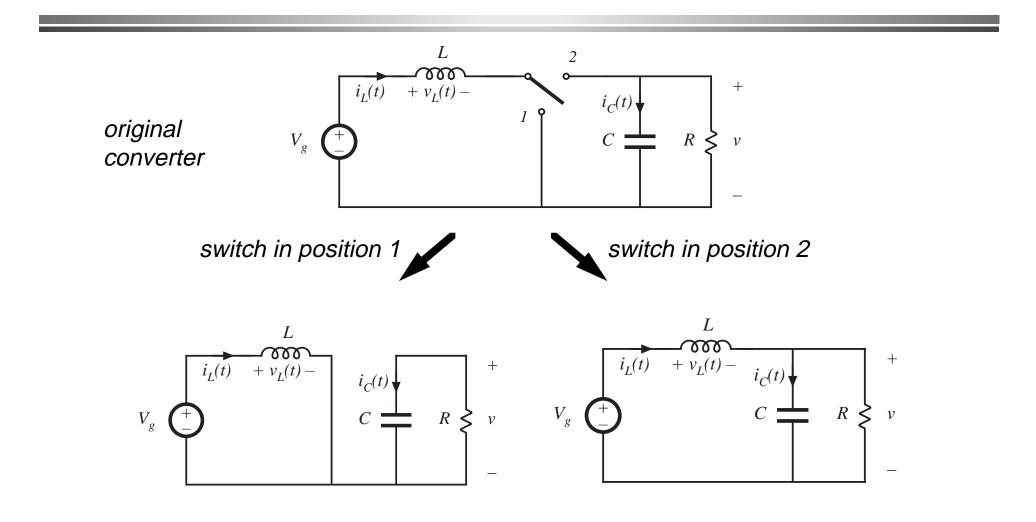

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis


Subinterval 1: switch in position 1

Inductor voltage and capacitor current

$$v_L = V_g$$
$$i_C = -v / R$$

Small ripple approximation:

$$v_L = V_g$$
$$i_C = -V / R$$

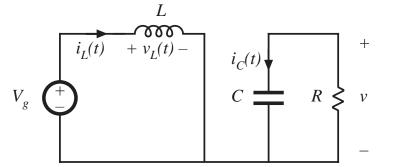


Subinterval 2: switch in position 2

Inductor voltage and capacitor current


$$v_L = V_g - v$$
$$i_C = i_L - v / R$$


Small ripple approximation:

$$v_L = V_g - V$$
$$i_C = I - V / R$$

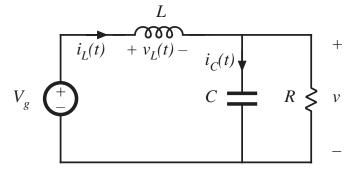

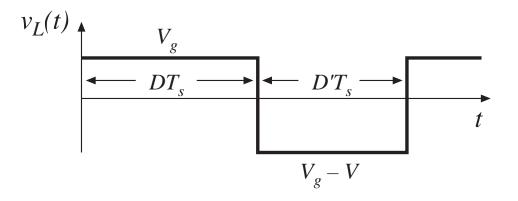Inductor voltage and capacitor current waveforms



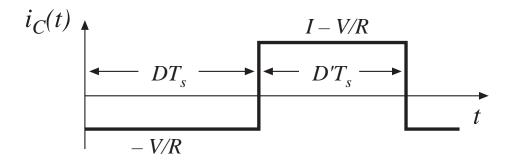

Fundamentals of Power Electronics

² Chapter 2: Principles of steady-state converter analysis

22

Inductor volt-second balance

23

Net volt-seconds applied to inductor over one switching period:

$$\int_0^{T_s} v_L(t) \, dt = (V_g) \, DT_s + (V_g - V) \, D'T_s$$

Equate to zero and collect terms:


$$V_g (D + D') - V D' = 0$$

Solve for V:


$$V = \frac{V_g}{D'}$$

The voltage conversion ratio is therefore
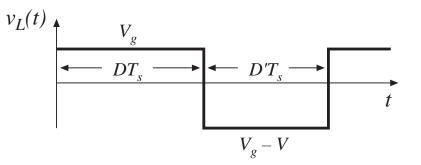
$$M(D) = \frac{V}{V_g} = \frac{1}{D'} = \frac{1}{1 - D}$$



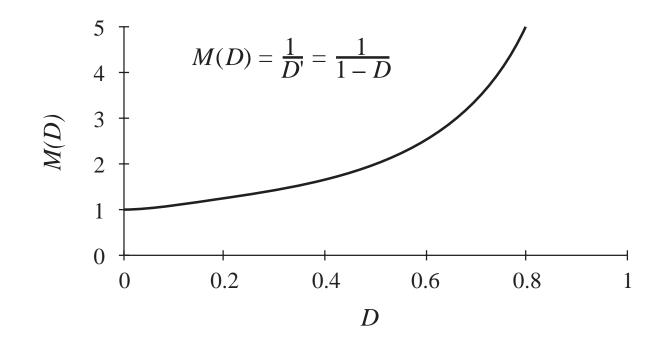Conversion ratio M(D) of the boost converter



Determination of inductor current dc component

Capacitor charge balance:

$$\int_{0}^{T_{s}} i_{C}(t) dt = (-\frac{V}{R}) DT_{s} + (I - \frac{V}{R}) D'T_{s}$$

Collect terms and equate to zero:

$$-\frac{V}{R}\left(D+D'\right)+I\,D'=0$$


Solve for *I*:


$$I = \frac{V}{D' R}$$

Eliminate V to express in terms of V_g :

$$I = \frac{V_g}{D'^2 R}$$

Fundamentals of Power Electronics

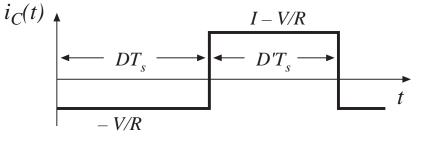

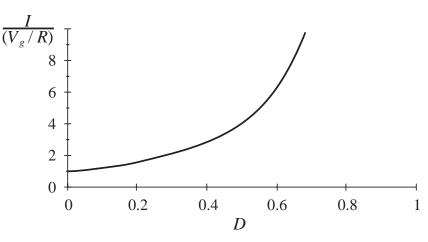

Chapter 2: Principles of steady-state converter analysis


Determination of inductor current ripple

Inductor current slope during subinterval 1:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g}{L}$$

Inductor current slope during subinterval 2:
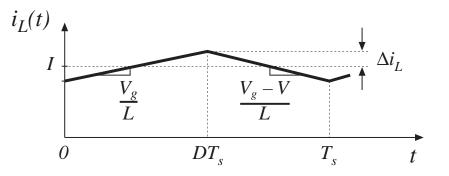
$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g - V}{L}$$



Change in inductor current during subinterval 1 is (slope) (length of subinterval):

$$2\Delta i_{L} = \frac{V_{g}}{L} DT_{s}$$

Solve for peak ripple:

Fundamentals of Power Electronics

 $\Delta i_L = \frac{V_g}{2L} DT_s$

26 Chapter 2: Principles of steady-state converter analysis


Determination of capacitor voltage ripple

Capacitor voltage slope during subinterval 1:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{-V}{RC}$$

Capacitor voltage slope during subinterval 2:
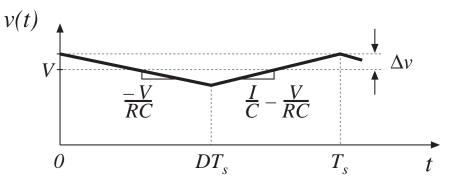
$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{I}{C} - \frac{V}{RC}$$



Change in capacitor voltage during subinterval 1 is (slope) (length of subinterval):


$$-2\Delta v = \frac{-V}{RC} DT_s$$

Solve for peak ripple:

$$\Delta v = \frac{V}{2RC} DT_s$$

- Choose *C* such that desired voltage ripple magnitude is obtained
- In practice, capacitor *equivalent series resistance* (esr) leads to increased voltage ripple
 - 27 Chapter 2: Principles of steady-state converter analysis


2.4 Cuk converter example

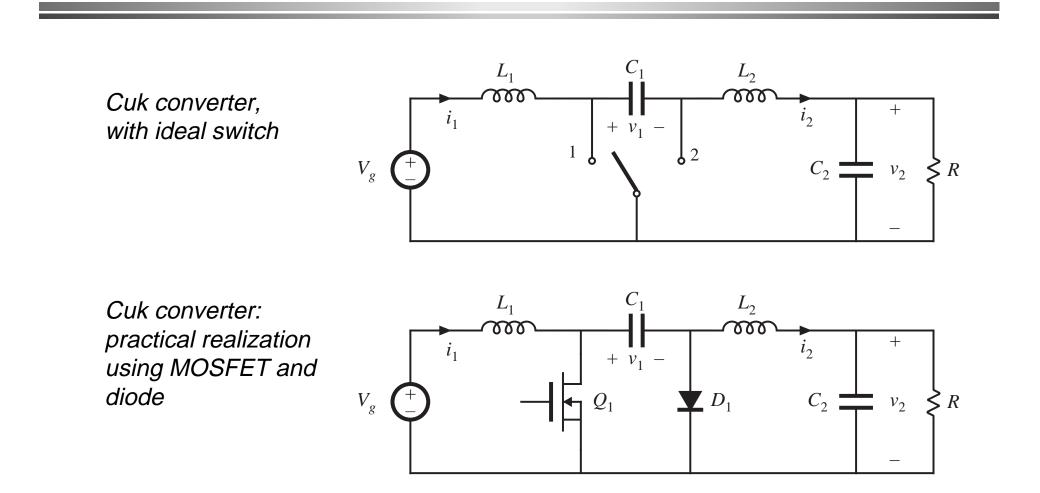

Fundamentals of Power Electronics

⁸ Chapter 2: Principles of steady-state converter analysis

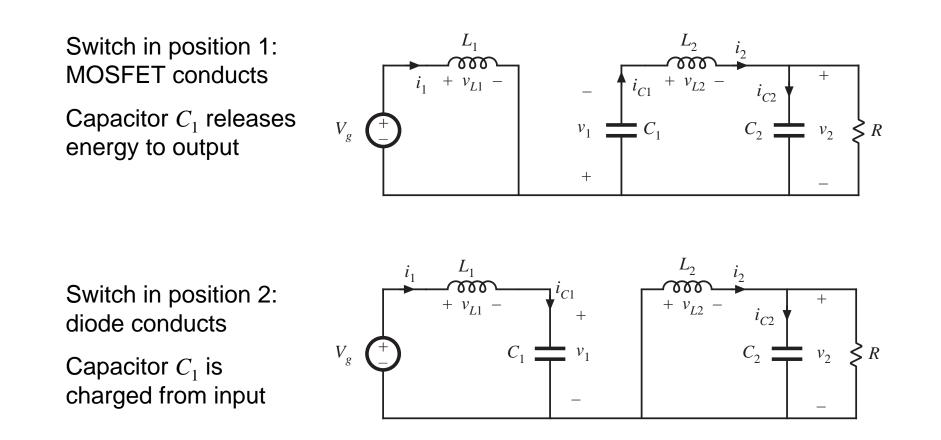Cuk converter circuit with switch in positions 1 and 2



⁹ Chapter 2: Principles of steady-state converter analysis

Waveforms during subinterval 1 MOSFET conduction interval


Inductor voltages and capacitor currents:

$$v_{L1} = V_g$$

$$v_{L2} = -v_1 - v_2$$

$$i_{C1} = i_2$$

$$i_{C2} = i_2 - \frac{v_2}{R}$$

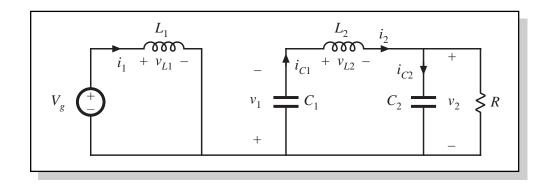

Small ripple approximation for subinterval 1:

$$v_{L1} = V_g$$

$$v_{L2} = -V_1 - V_2$$


$$i_{C1} = I_2$$

$$i_{C2} = I_2 - \frac{V_2}{R}$$

Waveforms during subinterval 2 Diode conduction interval

Inductor voltages and capacitor currents:
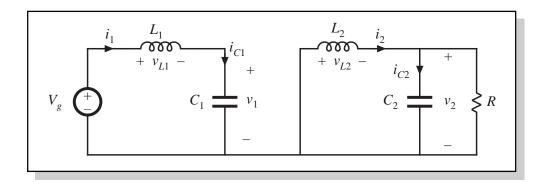
$$v_{L1} = V_g - v_1$$
$$v_{L2} = -v_2$$
$$i_{C1} = i_1$$
$$i_{C2} = i_2 - \frac{v_2}{R}$$




Small ripple approximation for subinterval 2:

$$v_{L1} = V_g - V_1$$
$$v_{L2} = -V_2$$
$$i_{C1} = I_1$$
$$i_{C2} = I_2 - \frac{V_2}{R}$$

The principles of inductor volt-second and capacitor charge balance state that the average values of the periodic inductor voltage and capacitor current waveforms are zero, when the converter operates in steady state. Hence, to determine the steady-state conditions in the converter, let us sketch the inductor voltage and capacitor current waveforms, and equate their average values to zero.

Waveforms:

Inductor voltage $v_{L1}(t)$

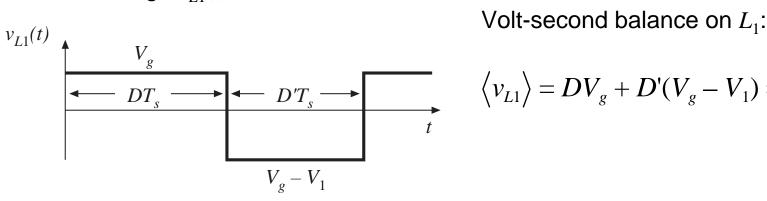


$$\left\langle v_{L1} \right\rangle = DV_g + D'(V_g - V_1) = 0$$


Fundamentals of Power Electronics

32 *Chapter 2: Principles of steady-state converter analysis*

Equate average values to zero

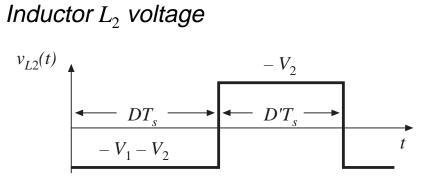

Capacitor C₁ current

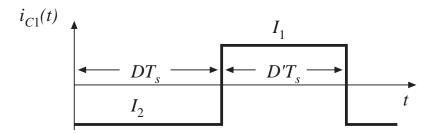

Average the waveforms:

$$\langle v_{L2} \rangle = D(-V_1 - V_2) + D'(-V_2) = 0$$


 $\langle i_{C1} \rangle = DI_2 + D'I_1 = 0$

Equate average values to zero


Capacitor current $i_{C2}(t)$ waveform

Note: during both subintervals, the capacitor current i_{C2} is equal to the difference between the inductor current i_2 and the load current V_2/R . When ripple is neglected, i_{C2} is constant and equal to zero.

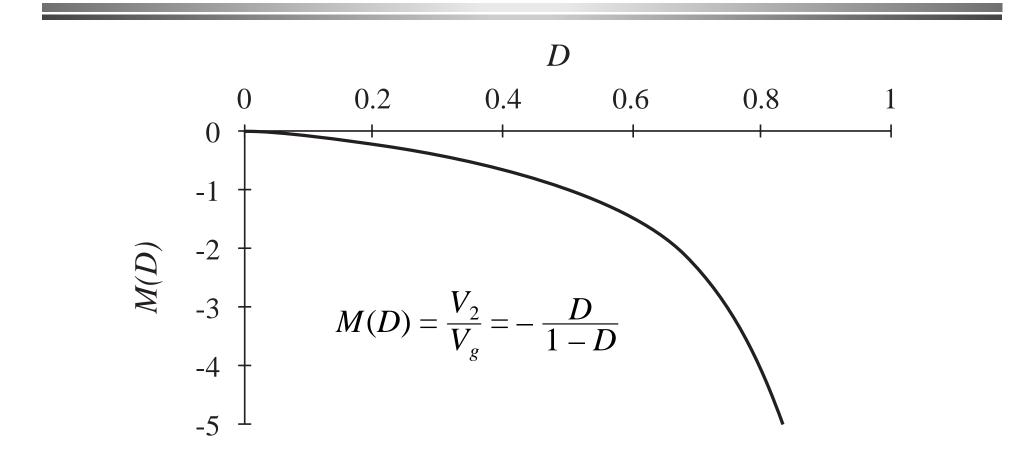
Cuk converter conversion ratio $M = V/V_g$



Inductor current waveforms

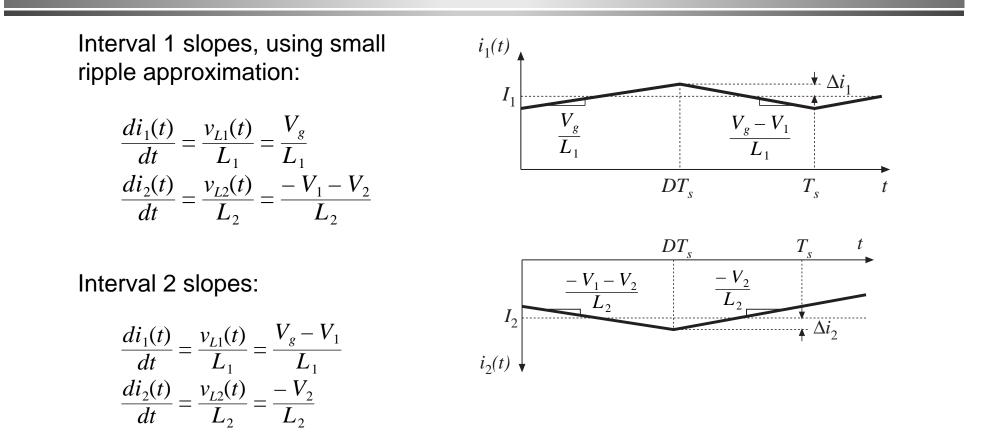

Capacitor C_1 waveform

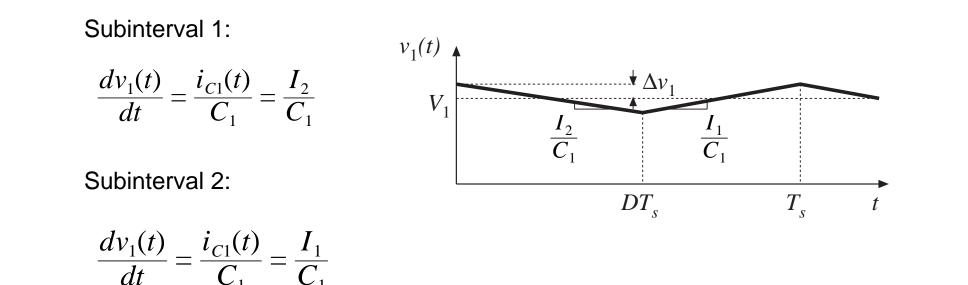

Ripple magnitudes

Analysis results


Use dc converter solution to simplify:

$$\Delta i_1 = \frac{V_g DT_s}{2L_1} \qquad \Delta i_1 = \frac{V_g DT_s}{2L_1}$$
$$\Delta i_2 = \frac{V_1 + V_2}{2L_2} DT_s \qquad \Delta i_2 = \frac{V_g DT_s}{2L_2}$$
$$\Delta v_1 = \frac{-I_2 DT_s}{2C_1} \qquad \Delta v_1 = \frac{V_g D^2 T_s}{2D'RC_1}$$

Q: How large is the output voltage ripple?

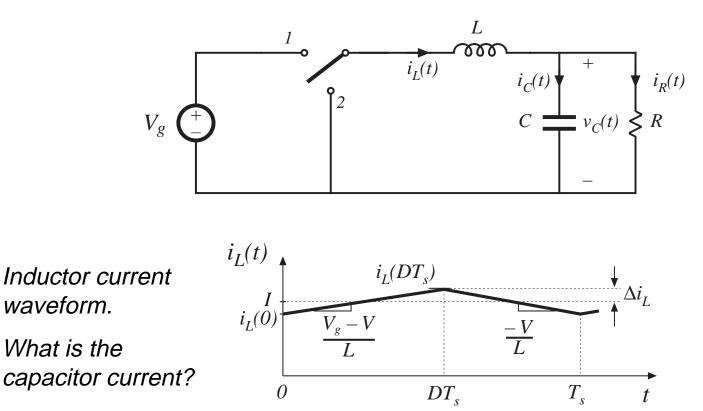2.5 Estimating ripple in converters containing two-pole low-pass filters

Buck converter example: Determine output voltage ripple




Fundamentals of Power Electronics


⁹ Chapter 2: Principles of steady-state converter analysis

39

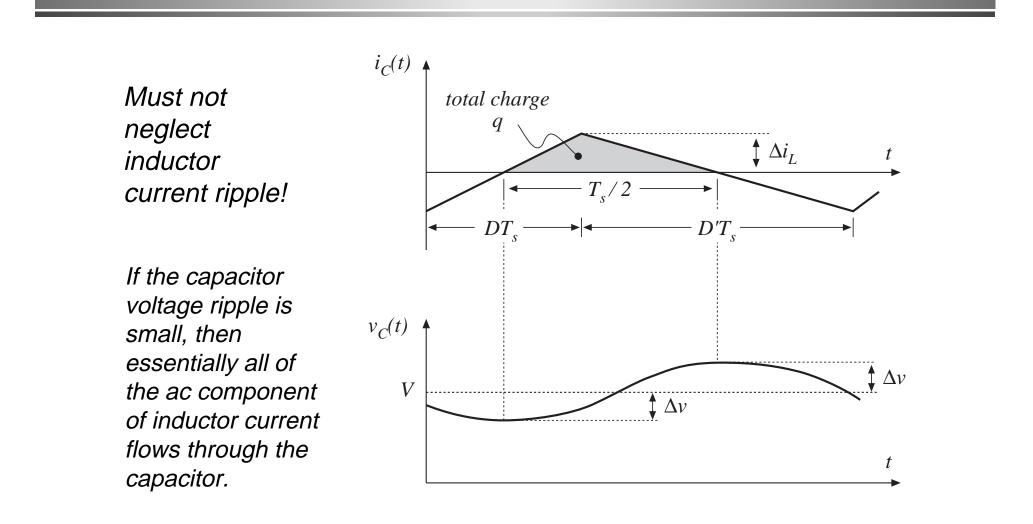Capacitor current and voltage, buck example



Estimating capacitor voltage ripple Δv

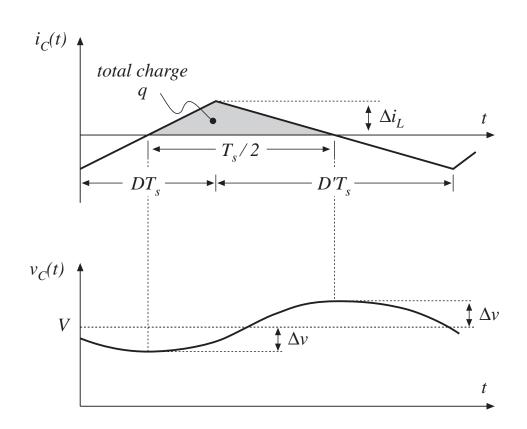


Current $i_C(t)$ is positive for half of the switching period. This positive current causes the capacitor voltage $v_C(t)$ to increase between its minimum and maximum extrema. During this time, the total charge q is deposited on the capacitor plates, where

 $q = C (2\Delta v)$

(change in charge) = C (change in voltage)

Estimating capacitor voltage ripple Δv

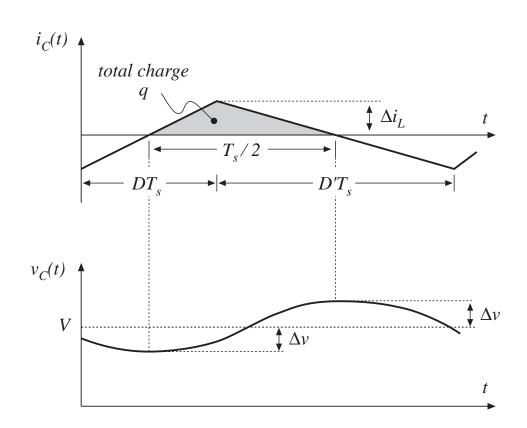

The total charge q is the area of the triangle, as shown:


$$q=\frac{1}{2}\Delta i_L \frac{T_s}{2}$$

Eliminate q and solve for Δv :

$$\Delta v = \frac{\Delta i_L T_s}{8 C}$$

Note: in practice, capacitor equivalent series resistance (esr) further increases Δv .

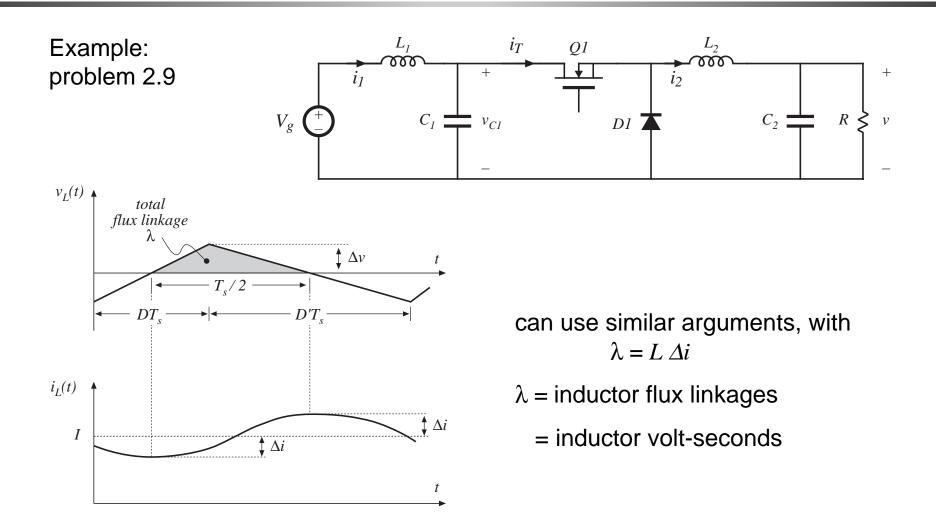Inductor current ripple in two-pole filters



Fundamentals of Power Electronics

43

Chapter 2: Principles of steady-state converter analysis

2.6 Summary of Key Points


- The dc component of a converter waveform is given by its average value, or the integral over one switching period, divided by the switching period. Solution of a dc-dc converter to find its dc, or steadystate, voltages and currents therefore involves averaging the waveforms.
- 2. The linear ripple approximation greatly simplifies the analysis. In a welldesigned converter, the switching ripples in the inductor currents and capacitor voltages are small compared to the respective dc components, and can be neglected.
- 3. The principle of inductor volt-second balance allows determination of the dc voltage components in any switching converter. In steady-state, the average voltage applied to an inductor must be zero.

- 4. The principle of capacitor charge balance allows determination of the dc components of the inductor currents in a switching converter. In steady-state, the average current applied to a capacitor must be zero.
- By knowledge of the slopes of the inductor current and capacitor voltage waveforms, the ac switching ripple magnitudes may be computed. Inductance and capacitance values can then be chosen to obtain desired ripple magnitudes.
- 6. In converters containing multiple-pole filters, continuous (nonpulsating) voltages and currents are applied to one or more of the inductors or capacitors. Computation of the ac switching ripple in these elements can be done using capacitor charge and/or inductor flux-linkage arguments, without use of the small-ripple approximation.
- Converters capable of increasing (boost), decreasing (buck), and inverting the voltage polarity (buck-boost and Cuk) have been described. Converter circuits are explored more fully in a later chapter.

Chapter 3. Steady-State Equivalent Circuit Modeling, Losses, and Efficiency

- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points

3.1. The dc transformer model

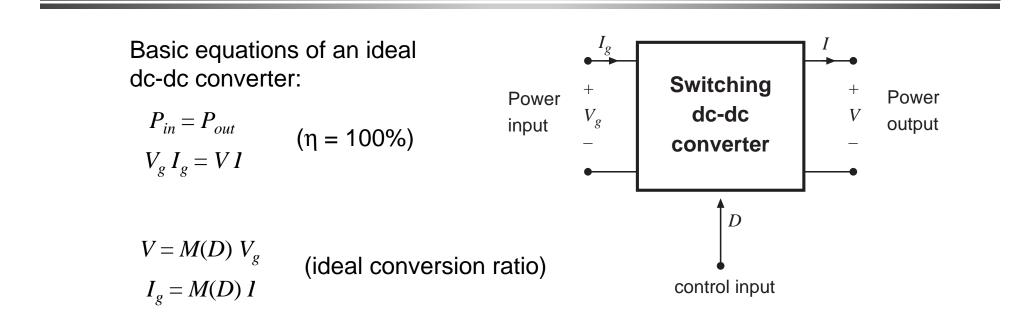


These equations are valid in steady-state. During transients, energy storage within filter elements may cause $P_{in} \neq P_{out}$

Fundamentals of Power Electronics

² Chapter 3: Steady-state equivalent circuit modeling, ...

Equivalent circuits corresponding to ideal dc-dc converter equations

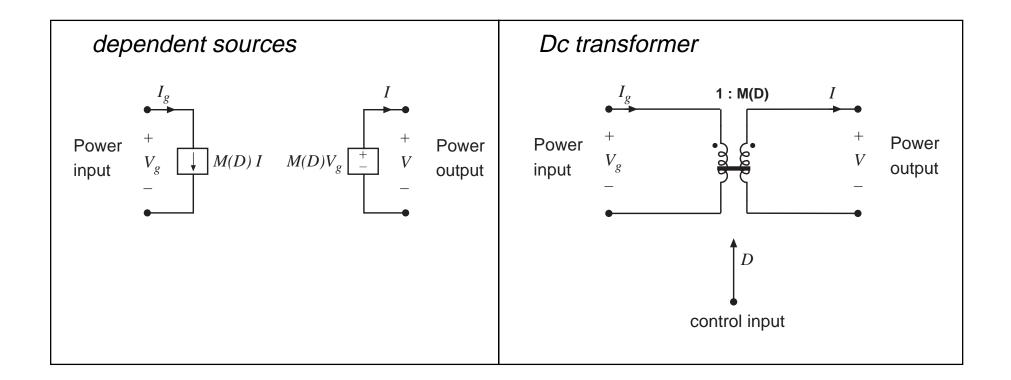
 $P_{in} = P_{out}$ $V_g I_g = V I$ $V = M(D) V_g$ $I_g = M(D) I$



3

Chapter 3: Steady-state equivalent circuit modeling, ...

The dc transformer model

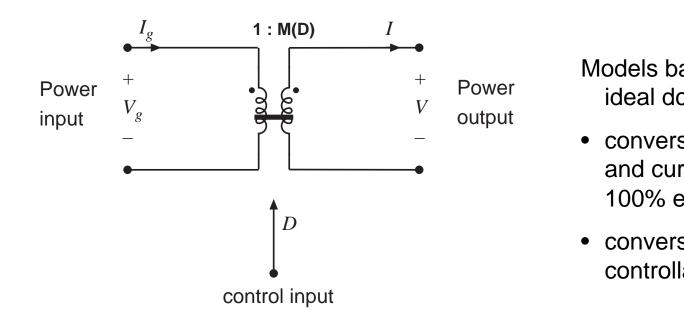

Models basic properties of ideal dc-dc converter:


- conversion of dc voltages and currents, ideally with 100% efficiency
- conversion ratio *M* controllable via duty cycle
- Solid line denotes ideal transformer model, capable of passing dc voltages and currents

4


• Time-invariant model (no switching) which can be solved to find dc components of converter waveforms

Example: use of the dc transformer model


1. Original system

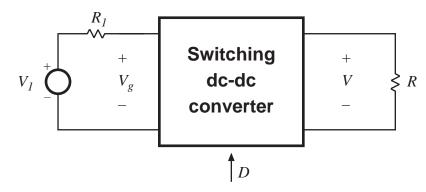

2. Insert dc transformer model

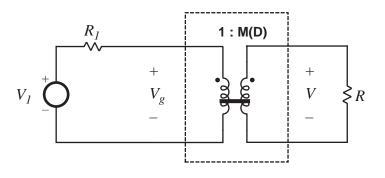

3. Push source through transformer

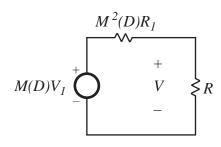

4. Solve circuit

$$V = M(D) V_1 \frac{R}{R + M^2(D) R_1}$$

Fundamentals of Power Electronics

5

Chapter 3: Steady-state equivalent circuit modeling, ...


3.2. Inclusion of inductor copper loss

Dc transformer model can be extended, to include converter nonidealities.

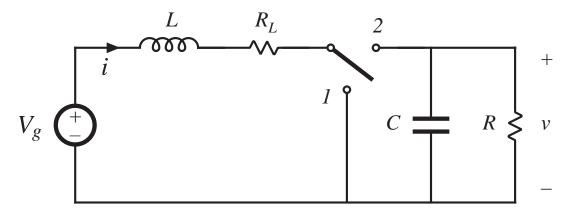Example: inductor copper loss (resistance of winding):



Insert this inductor model into boost converter circuit:




Fundamentals of Power Electronics

Chapter 3: Steady-state equivalent circuit modeling, ...

6

Analysis of nonideal boost converter

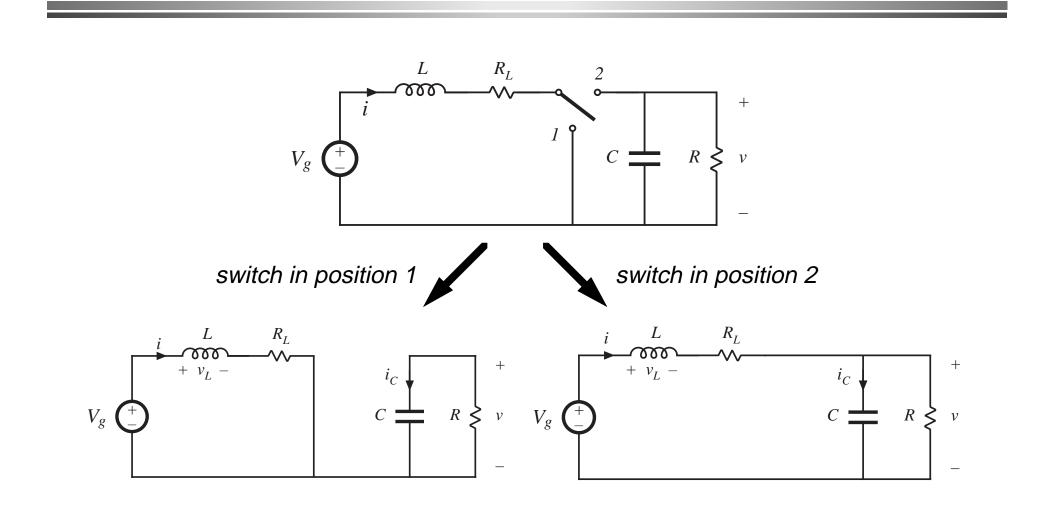


Fundamentals of Power Electronics

Circuit equations, switch in position 1

8

Inductor current and capacitor voltage:

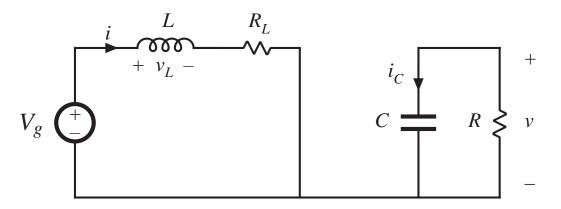
 $v_L(t) = V_g - i(t) R_L$ $i_C(t) = -v(t) / R$



Small ripple approximation:

$$v_L(t) = V_g - I R_L$$
$$i_C(t) = -V / R$$

Circuit equations, switch in position 2

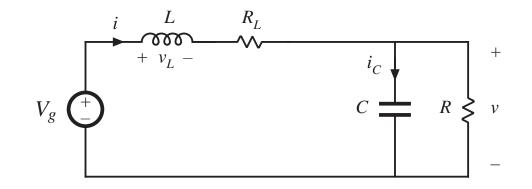

$$v_L(t) = V_g - i(t) R_L - v(t) \approx V_g - I R_L - V$$
$$i_C(t) = i(t) - v(t) / R \approx I - V / R$$

Fundamentals of Power Electronics

Inductor voltage and capacitor current waveforms

Average inductor voltage:

$$\left\langle v_L(t) \right\rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt$$
$$= D(V_g - I R_L) + D'(V_g - I R_L - V)$$

Inductor volt-second balance:


$$0 = V_g - I R_L - D'V$$

Average capacitor current:

$$\langle i_C(t) \rangle = D (-V/R) + D' (I - V/R)$$


Capacitor charge balance:

$$0 = D'I - V / R$$

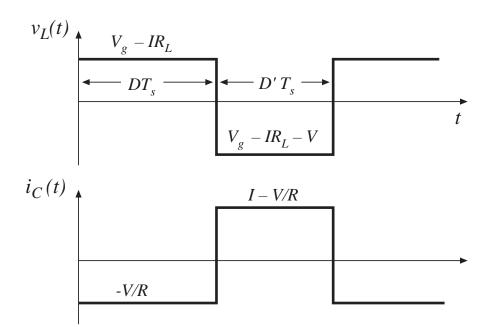

Fundamentals of Power Electronics

Solution for output voltage

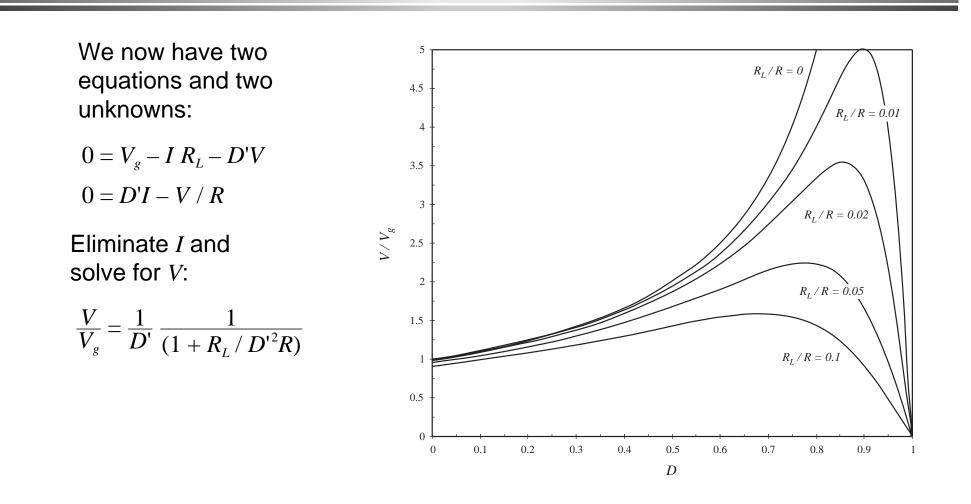

Fundamentals of Power Electronics

3.3. Construction of equivalent circuit model

Results of previous section (derived via inductor volt-sec balance and capacitor charge balance):

$$\langle v_L \rangle = 0 = V_g - I R_L - D'V$$


 $\langle i_C \rangle = 0 = D'I - V / R$

View these as loop and node equations of the equivalent circuit. Reconstruct an equivalent circuit satisfying these equations

Inductor voltage equation

$$\langle v_L \rangle = 0 = V_g - I R_L - D'V$$

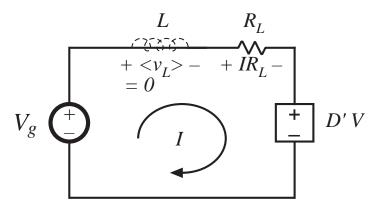- Derived via Kirchoff's voltage law, to find the inductor voltage during each subinterval
- Average inductor voltage then set to zero
- This is a loop equation: the dc components of voltage around a loop containing the inductor sum to zero




- *IR_L* term: voltage across resistor of value *R_L* having current *I*
- *D'V* term: for now, leave as dependent source

Capacitor current equation


 $\langle i_c \rangle = 0 = D'I - V / R$

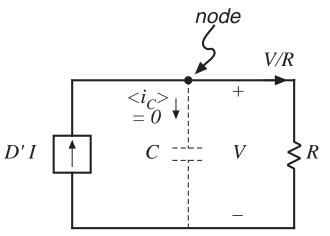- Derived via Kirchoff's current law, to find the capacitor current during each subinterval
- Average capacitor current then set to zero
- This is a node equation: the dc components of current flowing into a node connected to the capacitor sum to zero



- V/R term: current through load resistor of value R having voltage V
- *D'I* term: for now, leave as dependent source

Complete equivalent circuit

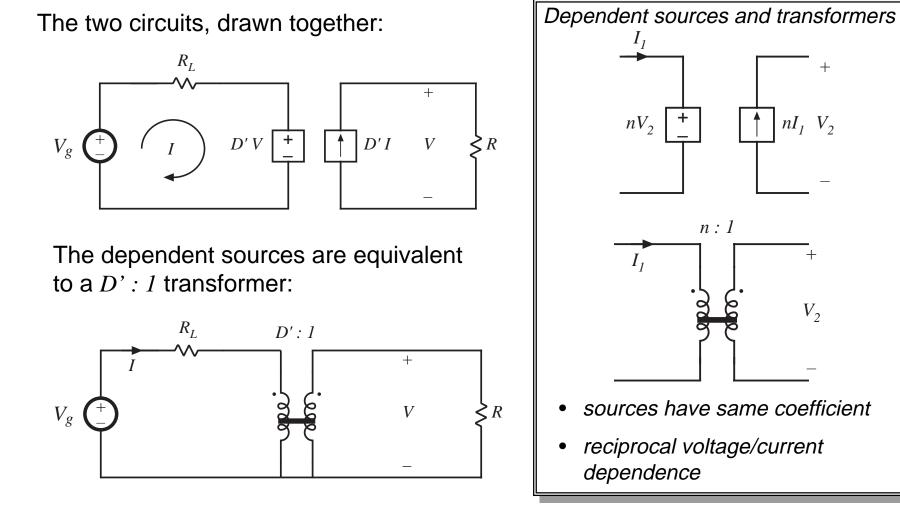


Fundamentals of Power Electronics

15


Chapter 3: Steady-state equivalent circuit modeling, ...

Solution of equivalent circuit

Converter equivalent circuit

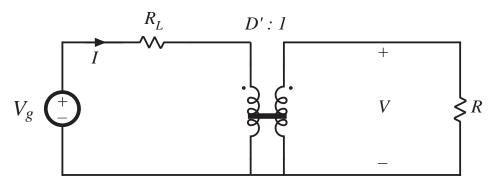

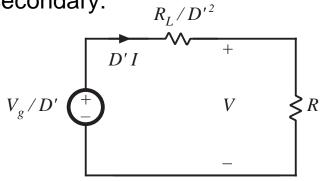Refer all elements to transformer secondary: $p_{\mu} \neq D^{\prime 2}$




Fundamentals of Power Electronics


Solution for output voltage using voltage divider formula:

$$V = \frac{V_g}{D'} \frac{R}{R + \frac{R_L}{{D'}^2}} = \frac{V_g}{D'} \frac{1}{1 + \frac{R_L}{{D'}^2 R}}$$

Solution for input (inductor) current

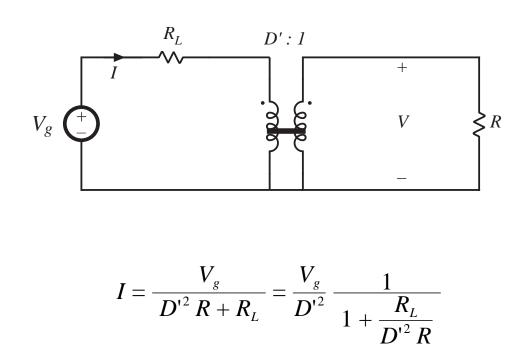


Solution for converter efficiency

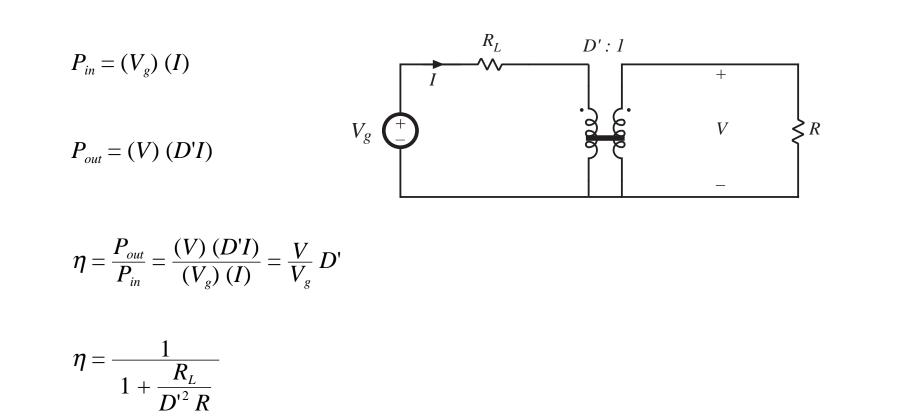

Fundamentals of Power Electronics

Efficiency, for various values of R_L

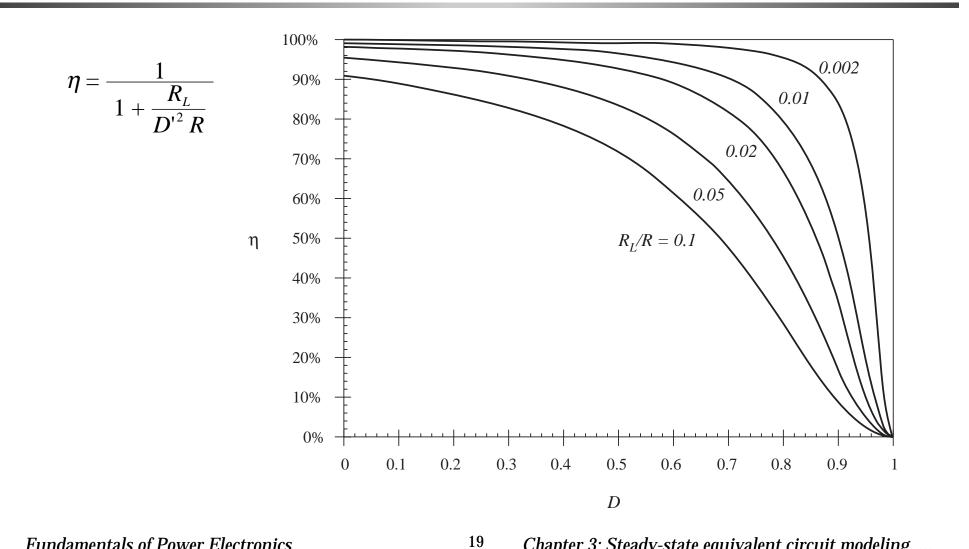


Fundamentals of Power Electronics

Chapter 3: Steady-state equivalent circuit modeling, ...

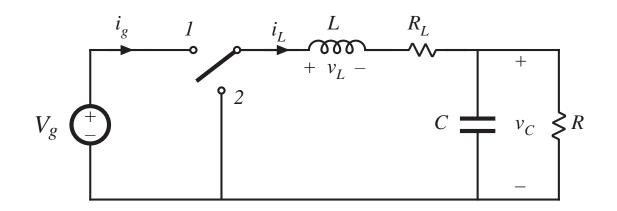3.4. How to obtain the input port of the model

Buck converter example —use procedure of previous section to derive equivalent circuit




Average inductor voltage and capacitor current:

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C$$
 $\langle i_C \rangle = 0 = I_L - V_C / R$

Fundamentals of Power Electronics

Construct equivalent circuit as usual
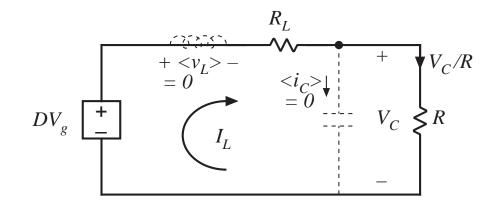
$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C$$
 $\langle i_C \rangle = 0 = I_L - V_C / R$




What happened to the transformer?

• Need another equation

Modeling the converter input port

Input current waveform $i_g(t)$:

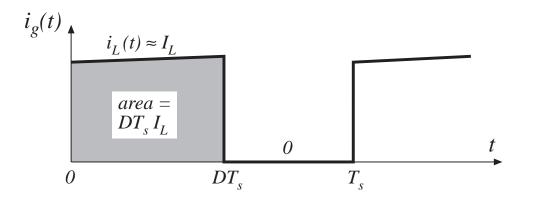


Dc component (average value) of $i_g(t)$ is

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$

Fundamentals of Power Electronics


Input port equivalent circuit
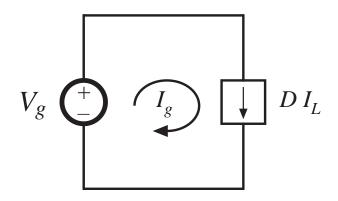
$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$




Complete equivalent circuit, buck converter

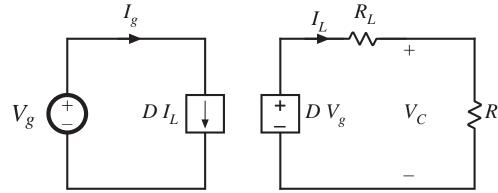Input and output port equivalent circuits, drawn together:



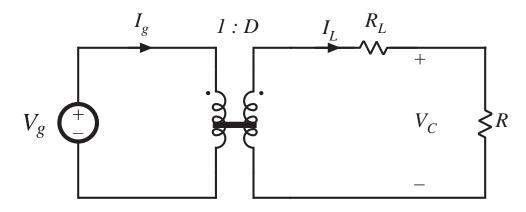
Replace dependent sources with equivalent dc transformer:



Fundamentals of Power Electronics

3.5. Example: inclusion of semiconductor conduction losses in the boost converter model

Boost converter example

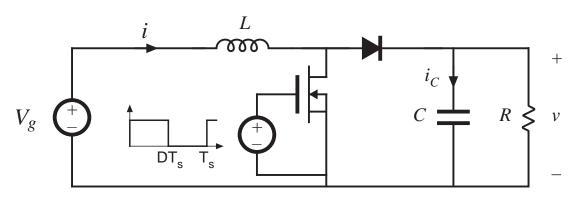


Models of on-state semiconductor devices:

MOSFET: on-resistance R_{on}

Diode: constant forward voltage V_D plus on-resistance R_D


Insert these models into subinterval circuits

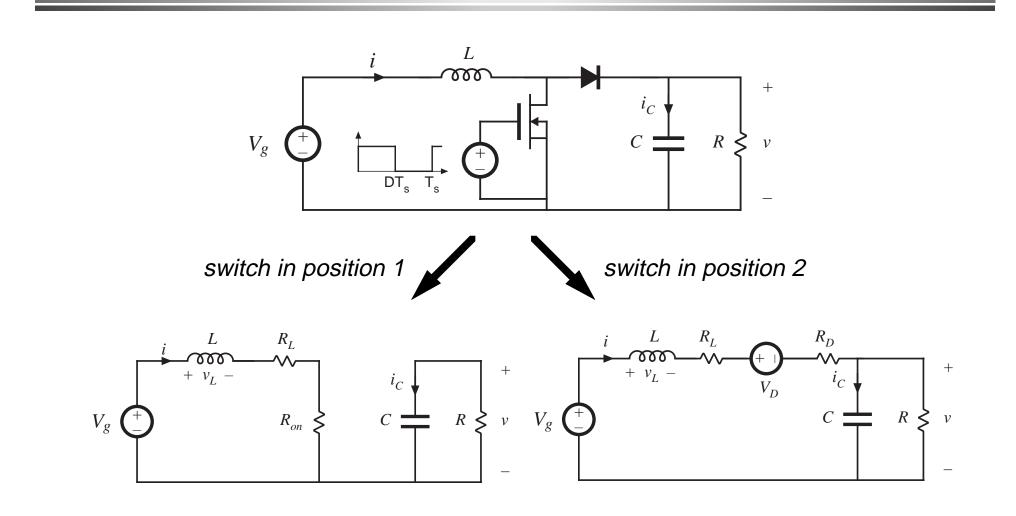Boost converter example: circuits during subintervals 1 and 2



Fundamentals of Power Electronics

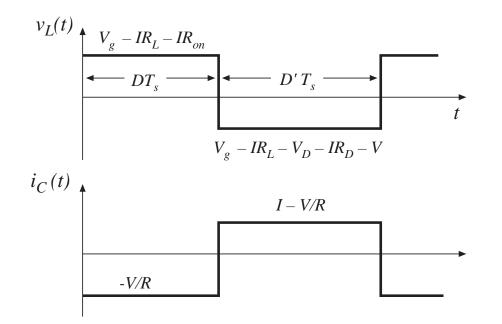
Average inductor voltage and capacitor current




$$\left\langle v_L \right\rangle = D(V_g - IR_L - IR_{on}) + D'(V_g - IR_L - V_D - IR_D - V) = 0$$
$$\left\langle i_C \right\rangle = D(-V/R) + D'(I - V/R) = 0$$

Fundamentals of Power Electronics

Construction of equivalent circuits

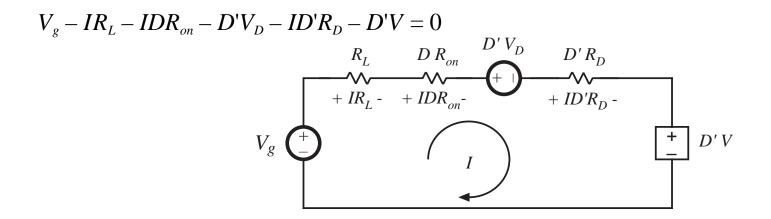

D'I - V/R = 0

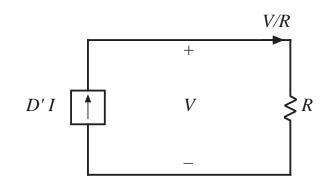


Fundamentals of Power Electronics

Chapter 3: Steady-state equivalent circuit modeling, ...


28

Complete equivalent circuit

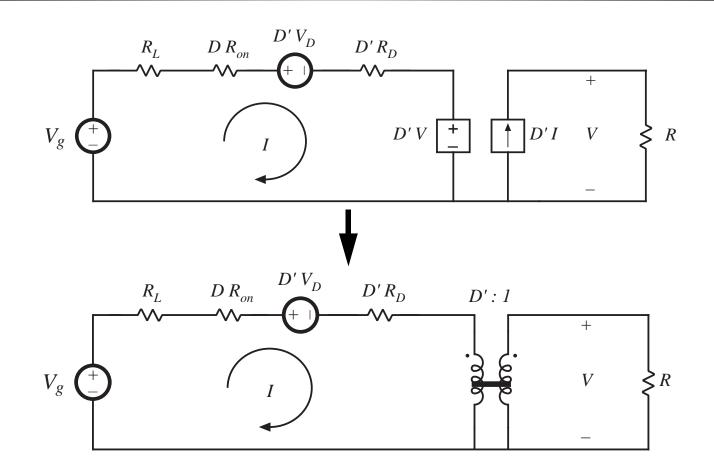

Fundamentals of Power Electronics


Solution for output voltage

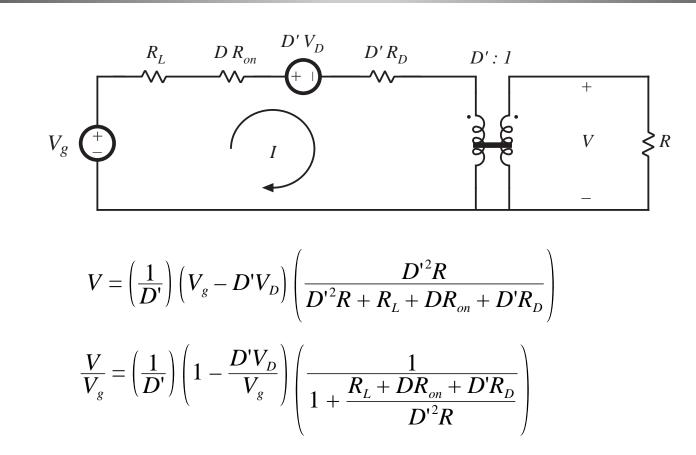

Fundamentals of Power Electronics

⁰ Chapter 3: Steady-state equivalent circuit modeling, ...

Solution for converter efficiency

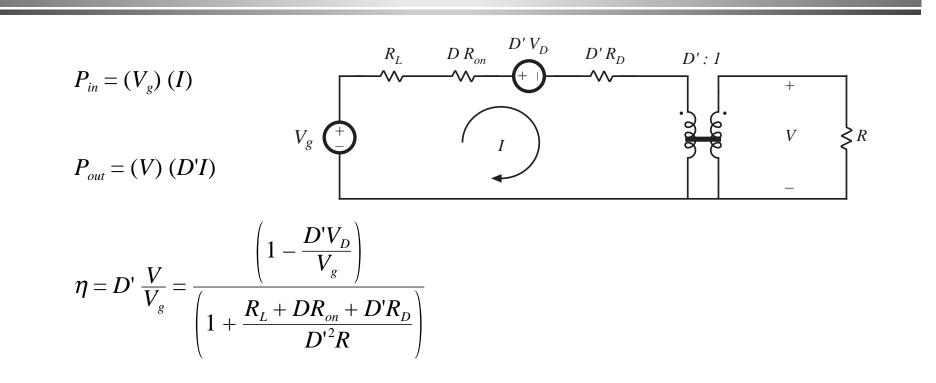

Conditions for high efficiency:


$$V_g / D' >> V_D$$
and
$$D'^2 R >> R_L + DR_{on} + D'R_D$$

Fundamentals of Power Electronics

Accuracy of the averaged equivalent circuit in prediction of losses

- Model uses average currents and voltages
- To correctly predict power loss in a resistor, use rms values
- Result is the same, provided ripple is small

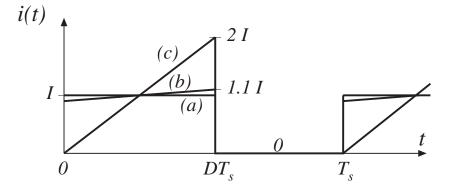MOSFET current waveforms, for various ripple magnitudes:



Inductor current ripple	MOSFET rms current	A verage power loss in R_{on}
(a) $\Delta i = 0$	$I\sqrt{D}$	$D I^2 R_{on}$
(b) $\Delta i = 0.1 I$	$(1.00167) I \sqrt{L}$	$(1.0033) D I^2 R_{on}$
(c) $\Delta i = I$	$(1.155) I \sqrt{D}$	$(1.3333) D I^2 R_{on}$

Fundamentals of Power Electronics

³² Chapter 3: Steady-state equivalent circuit modeling, ...

Summary of chapter 3

- The dc transformer model represents the primary functions of any dc-dc converter: transformation of dc voltage and current levels, ideally with 100% efficiency, and control of the conversion ratio *M* via the duty cycle *D*. This model can be easily manipulated and solved using familiar techniques of conventional circuit analysis.
- 2. The model can be refined to account for loss elements such as inductor winding resistance and semiconductor on-resistances and forward voltage drops. The refined model predicts the voltages, currents, and efficiency of practical nonideal converters.
- 3. In general, the dc equivalent circuit for a converter can be derived from the inductor volt-second balance and capacitor charge balance equations. Equivalent circuits are constructed whose loop and node equations coincide with the volt-second and charge balance equations. In converters having a pulsating input current, an additional equation is needed to model the converter input port; this equation may be obtained by averaging the converter input current.

Chapter 4. Switch Realization

4.1. Switch applications

Single-, two-, and four-quadrant switches. Synchronous rectifiers

4.2. A brief survey of power semiconductor devices


Power diodes, MOSFETs, BJTs, IGBTs, and thyristors

4.3. Switching loss

Transistor switching with clamped inductive load. Diode recovered charge. Stray capacitances and inductances, and ringing. Efficiency vs. switching frequency.

4.4. Summary of key points


SPST (single-pole single-throw) switches

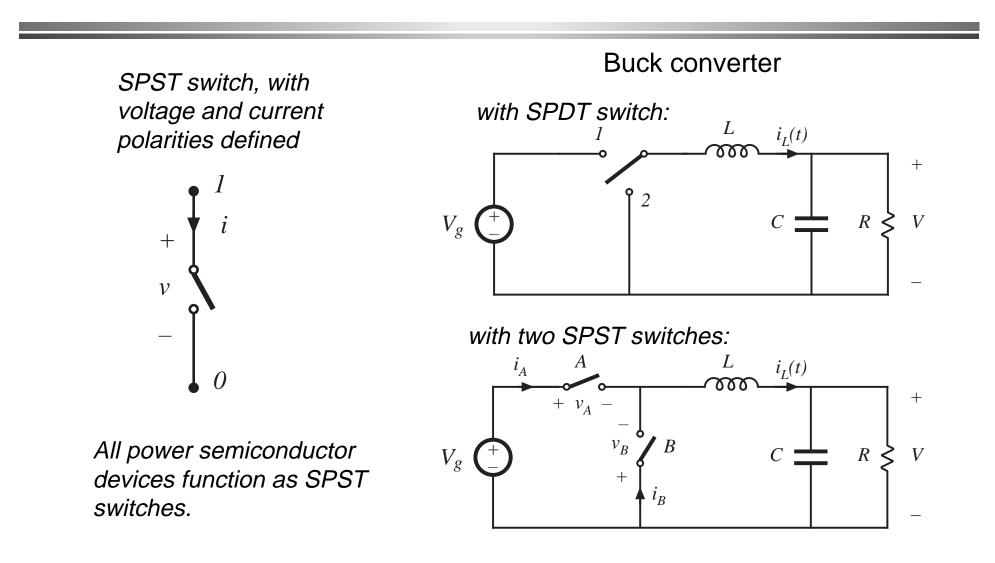


Realization of SPDT switch using two SPST switches

- A nontrivial step: two SPST switches are not exactly equivalent to one SPDT switch
- It is possible for both SPST switches to be simultaneously ON or OFF
- Behavior of converter is then significantly modified —discontinuous conduction modes (ch. 5)
- Conducting state of SPST switch may depend on applied voltage or current —for example: diode

Quadrants of SPST switch operation

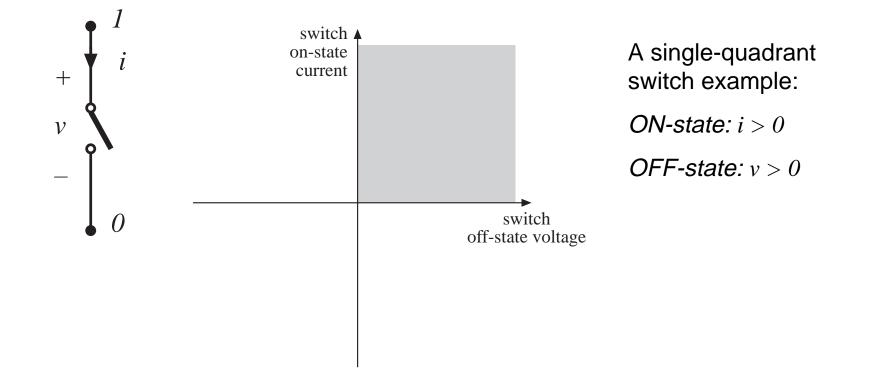


Some basic switch applications

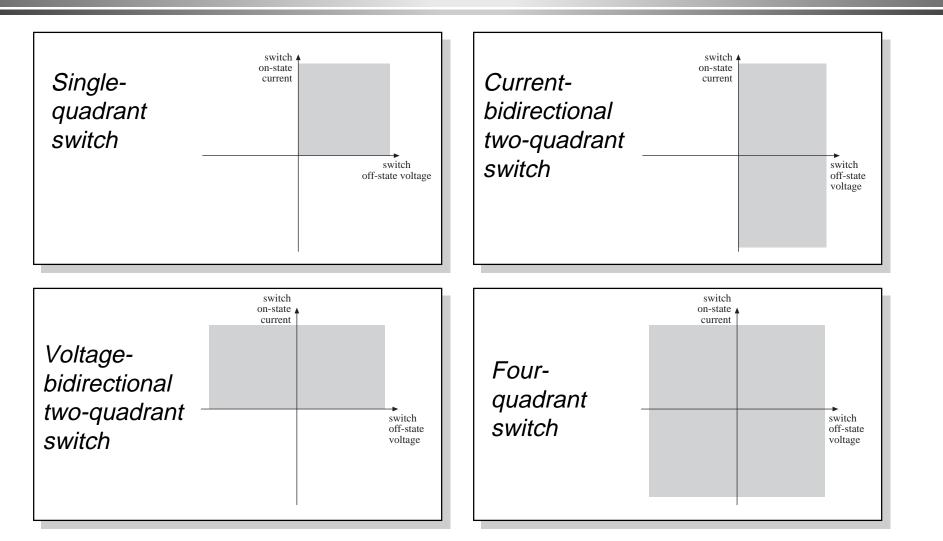

Fundamentals of Power Electronics

4.1.1. Single-quadrant switches

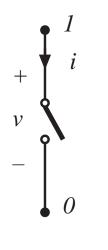


Active switch: Switch state is controlled exclusively by a third terminal (control terminal).

Passive switch: Switch state is controlled by the applied current and/or voltage at terminals 1 and 2.

SCR: A special case — turn-on transition is active, while turn-off transition is passive.


Single-quadrant switch: on-state i(t) and off-state v(t) are unipolar.

The diode

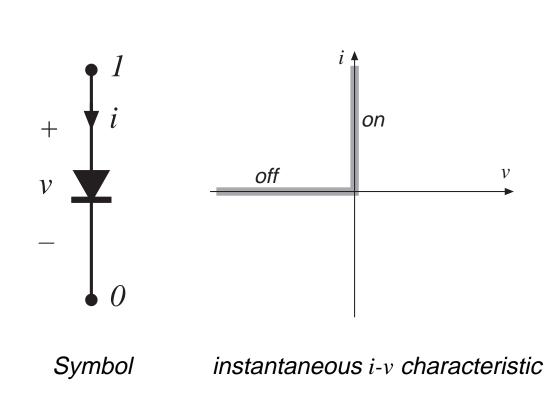


- A passive switch
- Single-quadrant switch:
- can conduct positive onstate current
- can block negative offstate voltage
- provided that the intended on-state and off-state operating points lie on the diode i-v characteristic, then switch can be realized using a diode

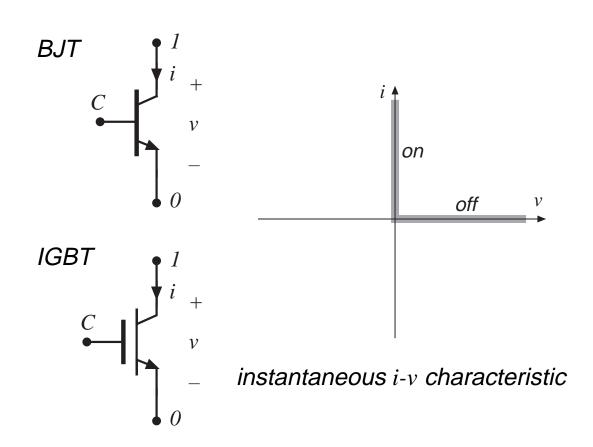The Bipolar Junction Transistor (BJT) and the Insulated Gate Bipolar Transistor (IGBT)



- An active switch, controlled by terminal C
- Single-quadrant switch:
- can conduct positive onstate current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the transistor i-v characteristic, then switch can be realized using a BJT or IGBT

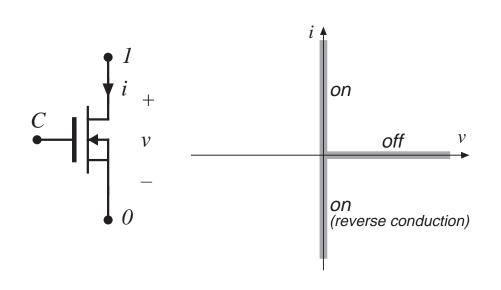The Metal-Oxide Semiconductor Field Effect Transistor (MOSFET)



Symbol instantaneous i-*v characteristic*

- An active switch, controlled by terminal C
- Normally operated as singlequadrant switch:
- can conduct positive on-state current (can also conduct negative current in some circumstances)
- can block positive off-state voltage
- provided that the intended onstate and off-state operating points lie on the MOSFET *i*-v characteristic, then switch can be realized using a MOSFET


Realization of switch using transistors and diodes

Buck converter example $i_L(t)$ $+ v_A$ + v_B B C V_g R VSwitch A: transistor l_B Switch B: diode i_A i_B switch A SPST switch switch B l_L on on ι_L operating points switch A switch B off off V_{ϱ} $-V_g$ v_A v_B Switch A Switch B


Fundamentals of Power Electronics

Chapter 4: Switch realization

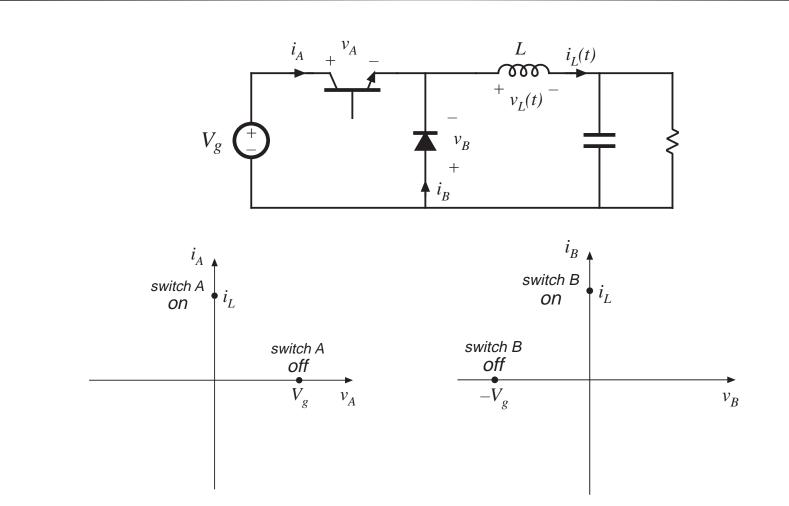Realization of buck converter using single-quadrant switches



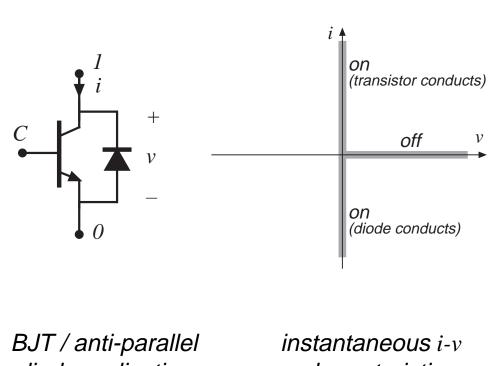4.1.2. Current-bidirectional two-quadrant switches




diode realization


characteristic

- Usually an active switch, controlled by terminal C
- Normally operated as twoquadrant switch:
- can conduct positive or negative on-state current
- can block positive off-state ٠ voltage
- provided that the intended onstate and off-state operating points lie on the composite *i*-v characteristic, then switch can be realized as shown


Two quadrant switches

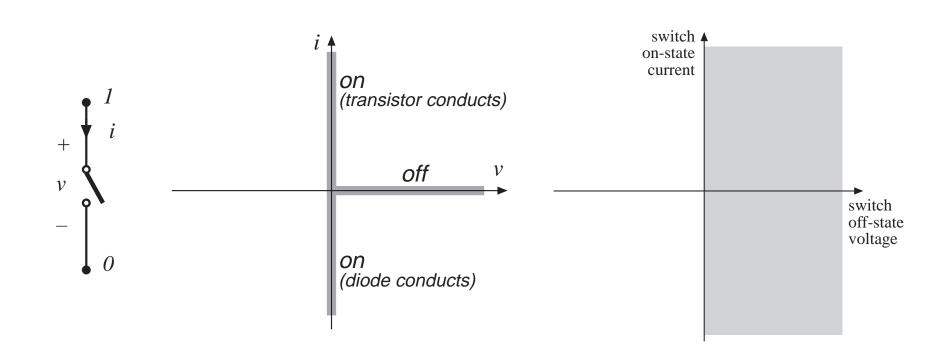

MOSFET body diode

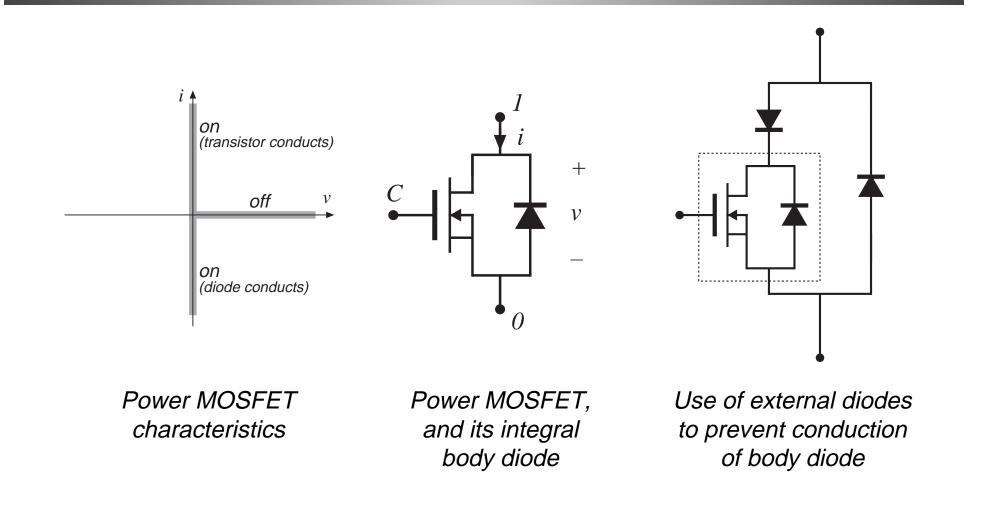


A simple inverter

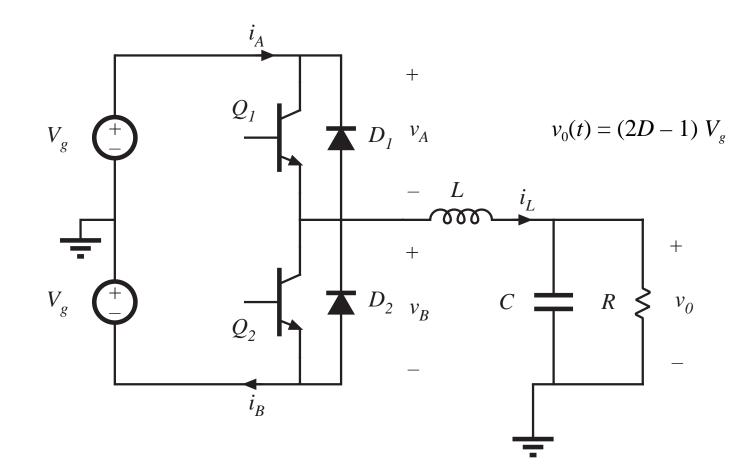

Inverter: sinusoidal modulation of *D*

 $v_0(t) = (2D - 1) V_g$

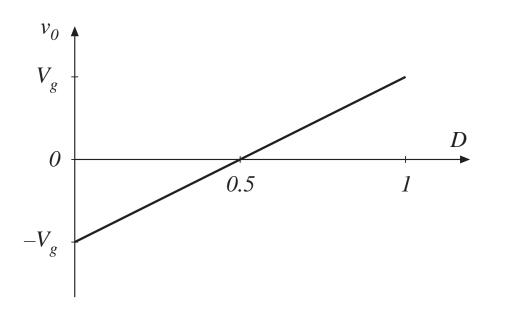

Sinusoidal modulation to produce ac output:


 $D(t) = 0.5 + D_m \sin(\omega t)$

The resulting inductor current variation is also sinusoidal:

$$i_L(t) = \frac{v_0(t)}{R} = (2D - 1) \frac{V_g}{R}$$


Hence, current-bidirectional two-quadrant switches are required.

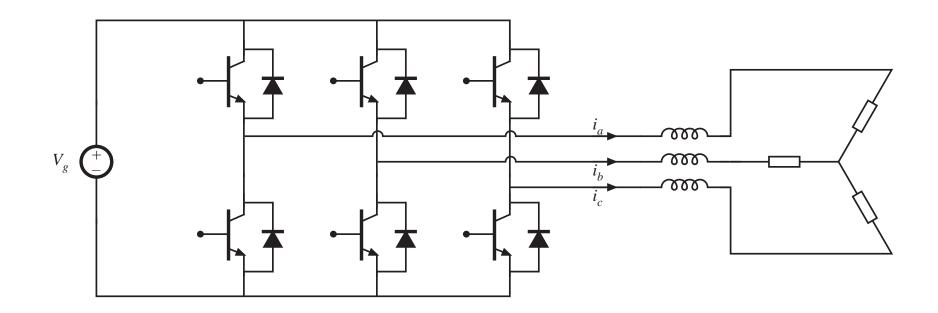The dc-3øac voltage source inverter (VSI)




Switches must block dc input voltage, and conduct ac load current.

Bidirectional battery charger/discharger

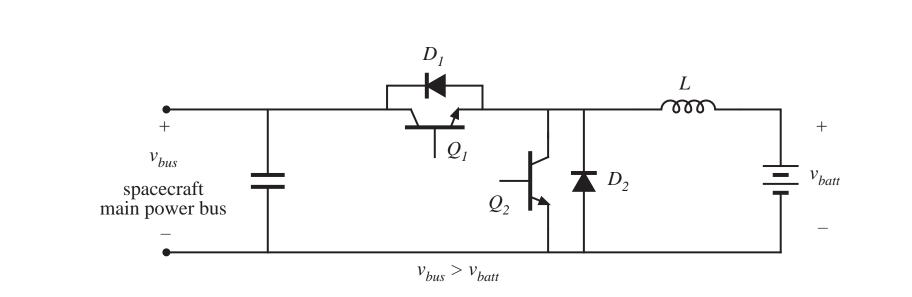


A dc-dc converter with bidirectional power flow.

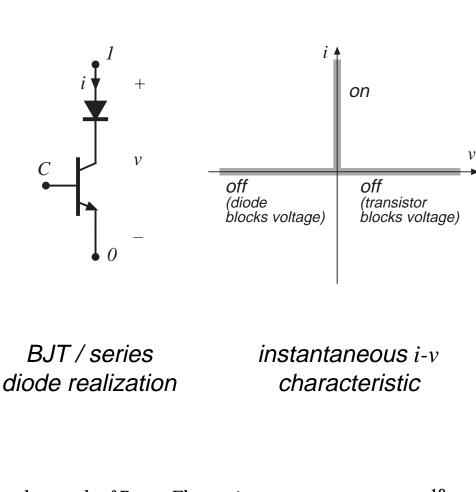4.1.3. Voltage-bidirectional two-quadrant switches




- Usually an active switch, controlled by terminal C
- Normally operated as twoquadrant switch:
- can conduct positive on-state current
- can block positive or negative off-state voltage
- provided that the intended onstate and off-state operating points lie on the composite *i*-v characteristic, then switch can be realized as shown
- The SCR is such a device, without controlled turn-off

Two-quadrant switches

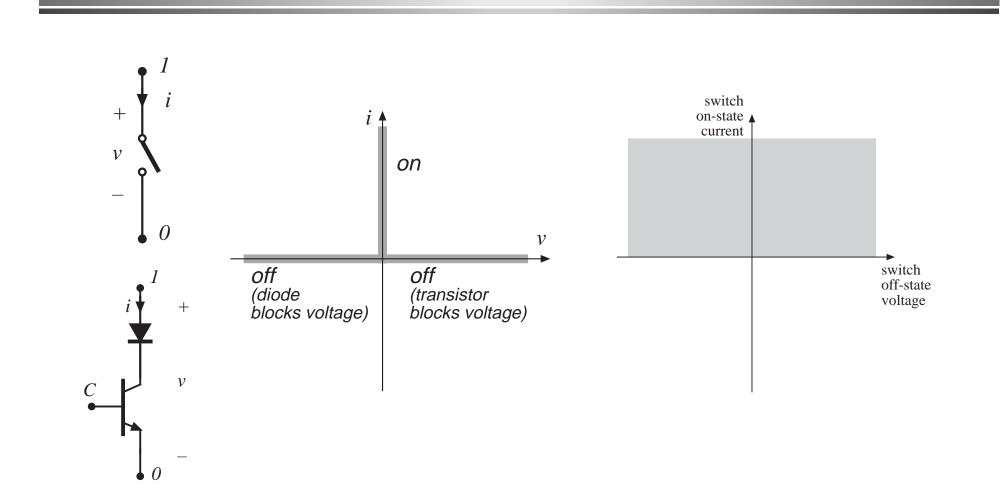

A dc-3øac buck-boost inverter

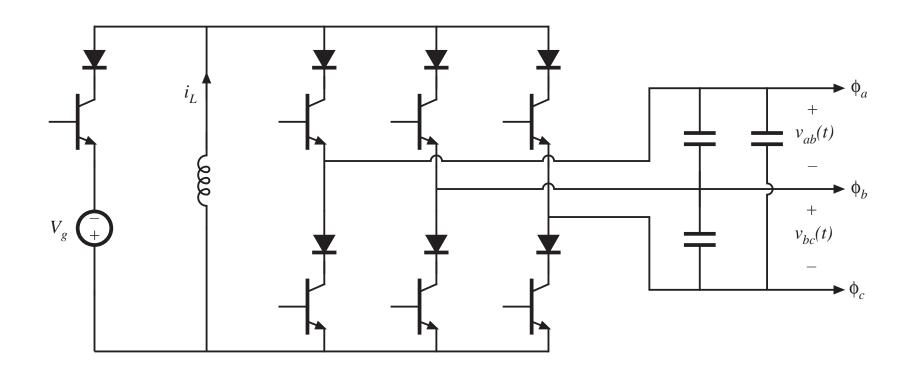


Requires voltage-bidirectional two-quadrant switches.

Another example: boost-type inverter, or current-source inverter (CSI).


Fundamentals of Power Electronics

4.1.4. Four-quadrant switches

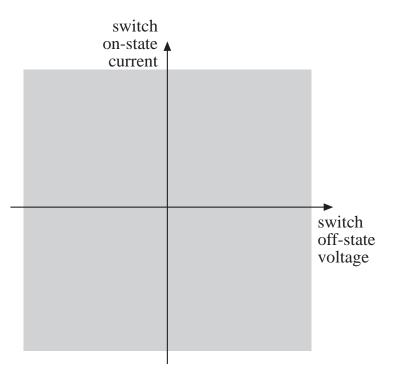


- Usually an active switch, controlled by terminal C
- can conduct positive or negative on-state current
- can block positive or negative off-state voltage

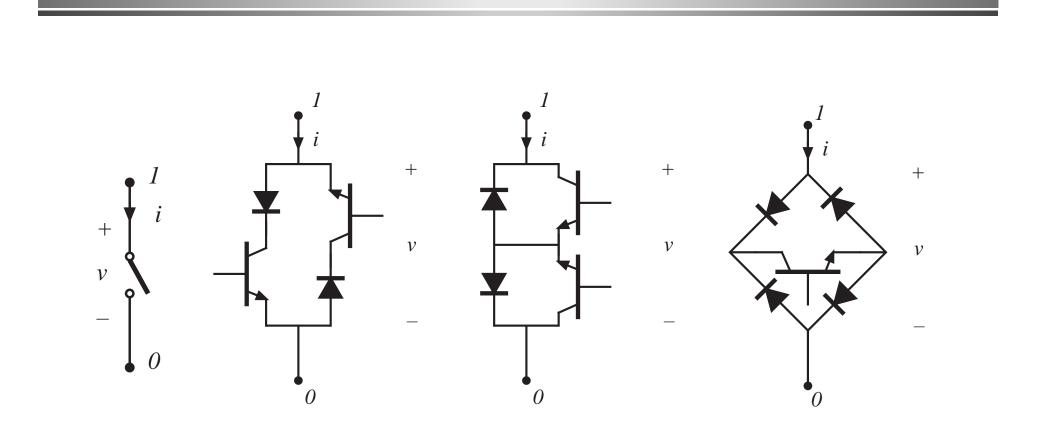Three ways to realize a four-quadrant switch




A 3øac-3øac matrix converter

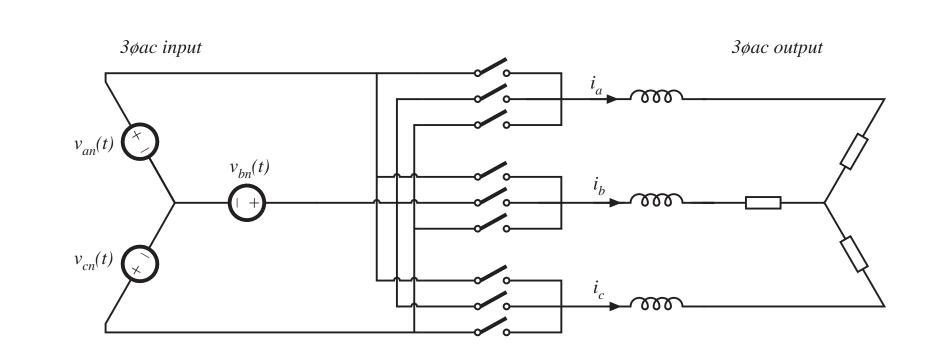


- All voltages and currents are ac; hence, four-quadrant switches are required.
- Requires nine four-quadrant switches

4.1.5. Synchronous rectifiers

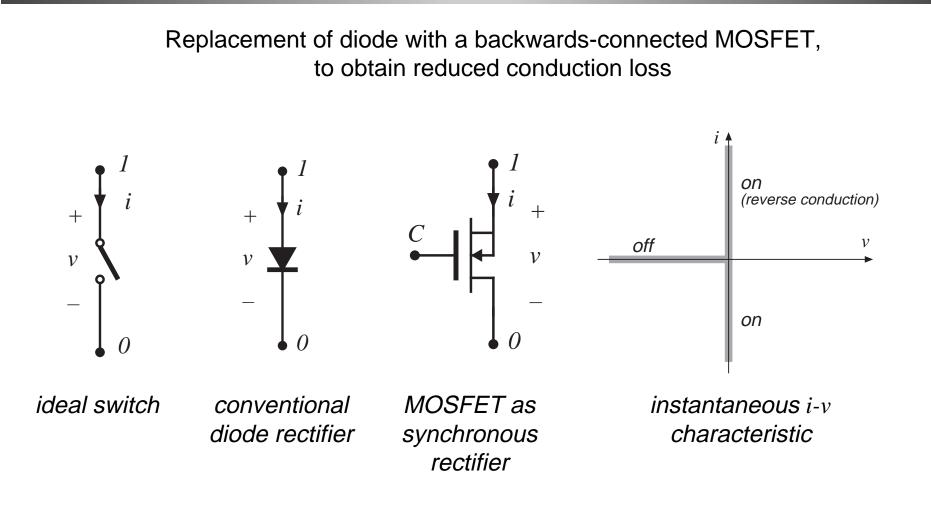

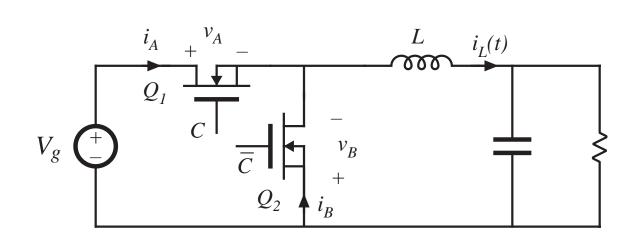Buck converter with synchronous rectifier




- MOSFET Q₂ is controlled to turn on when diode would normally conduct
- Semiconductor conduction loss can be made arbitrarily small, by reduction of MOSFET onresistances
- Useful in lowvoltage high-current applications

4.2. A brief survey of power semiconductor devices

- Power diodes
- Power MOSFETs
- Bipolar Junction Transistors (BJTs)
- Insulated Gate Bipolar Transistors (IGBTs)
- Thyristors (SCR, GTO, MCT)
- On resistance vs. breakdown voltage vs. switching times
- Minority carrier and majority carrier devices

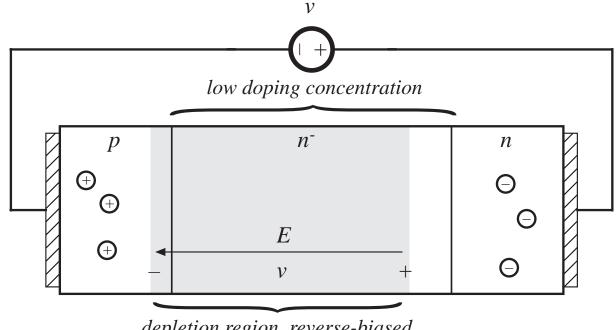
4.2.1. Power diodes

A power diode, under reverse-biased conditions:



depletion region, reverse-biased


Forward-biased power diode

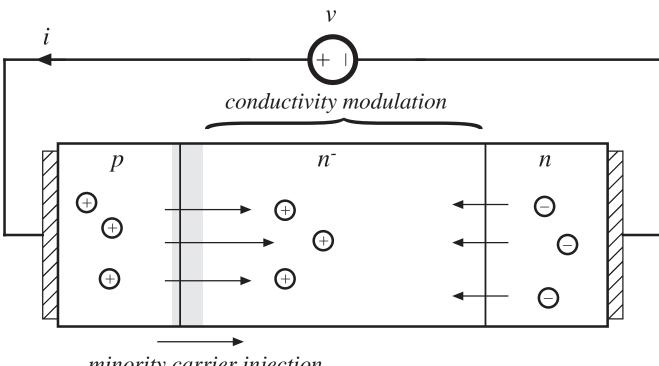

minority carrier injection

Fundamentals of Power Electronics

Typical diode switching waveforms

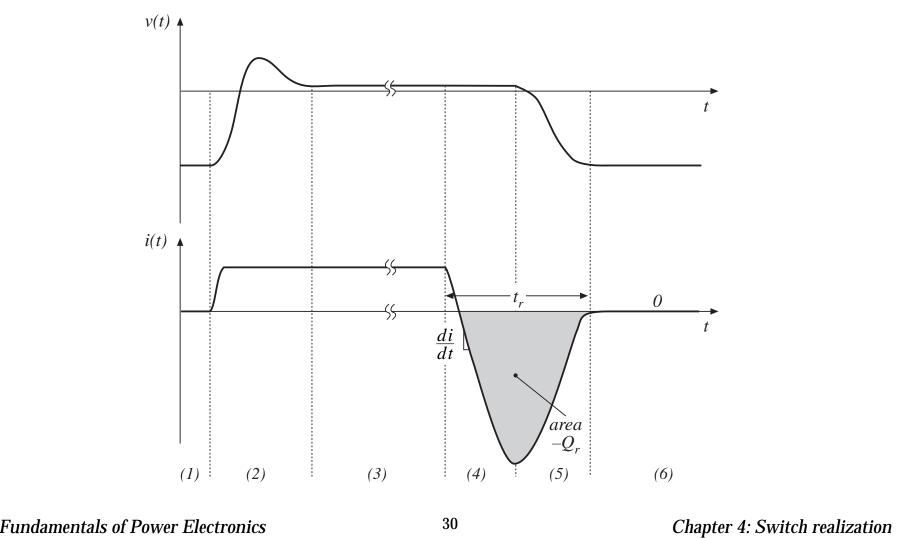

Fundamentals of Power Electronics

Types of power diodes

Standard recovery

Reverse recovery time not specified, intended for 50/60Hz

Fast recovery and ultra-fast recovery

Reverse recovery time and recovered charge specified

Intended for converter applications

Schottky diode

A majority carrier device

Essentially no recovered charge

Model with equilibrium *i*-v characteristic, in parallel with

depletion region capacitance


Restricted to low voltage (few devices can block 100V or more)

Characteristics of several commercial power rectifier diodes

Part number	Rated max voltage	Rated avg current	V_F (typical)	$t_r(max)$
Fast recovery re	ctifiers			
1N3913	400V	30A	1.1V	400ns
SD453N25S20PC	2500V	400A	2.2V	2µs
Ultra-fast recov	ery rectifiers			
MUR815	150V	8A	0.975V	35ns
MUR1560	600V	15A	1.2V	60ns
RHRU100120	1200V	100A	2.6V	60ns
Schottky rectifi	ers			
MBR6030L	30V	60A	0.48V	
444CNQ045	45V	440A	0.69V	
30CPQ150	150V	30A	1.19V	


Fundamentals of Power Electronics

4.2.2. The Power MOSFET

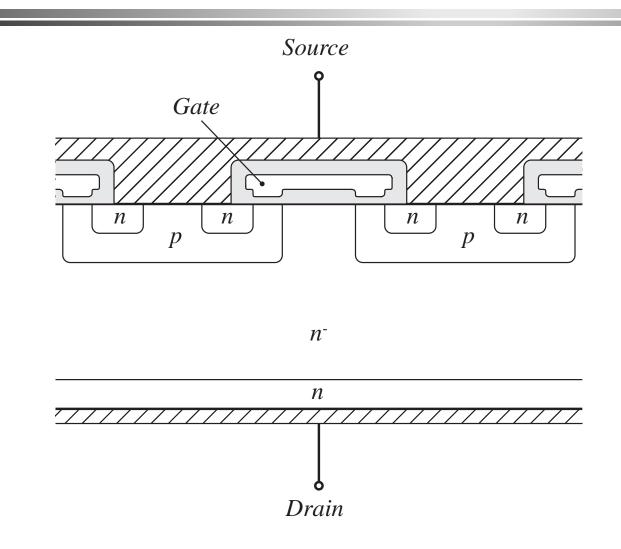


- Gate lengths approaching one micron
- Consists of many small enhancementmode parallelconnected MOSFET cells, covering the surface of the silicon wafer
- Vertical current flow
- n-channel device is shown

MOSFET: Off state

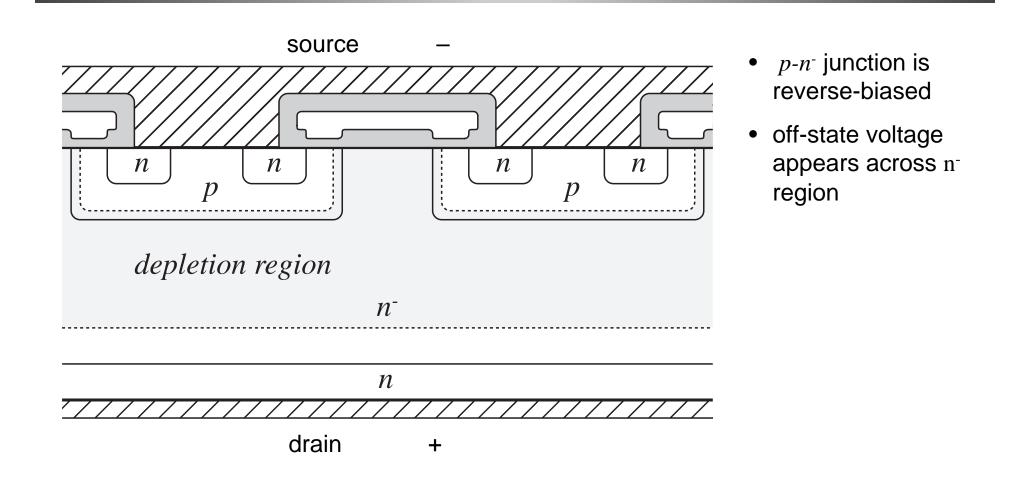


Fundamentals of Power Electronics

MOSFET: on state

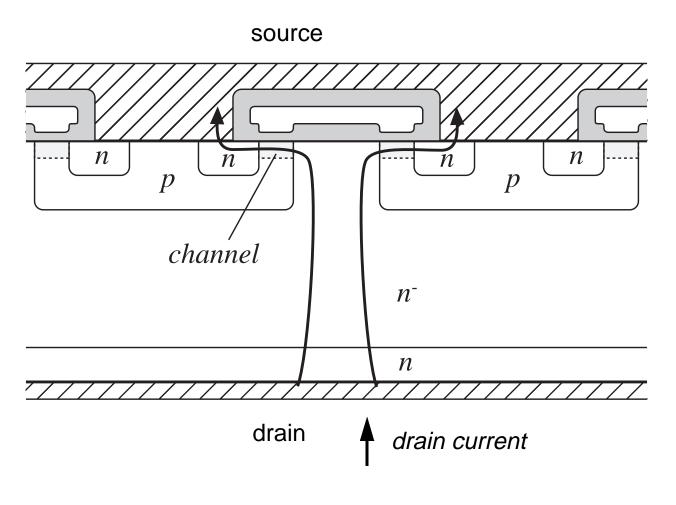


- *p-n*⁻ junction is slightly reversebiased
- positive gate voltage induces conducting channel
- drain current flows through n⁻ region and conducting channel
- on resistance = total resistances of n⁻ region, conducting channel, source and drain contacts, etc.

MOSFET body diode

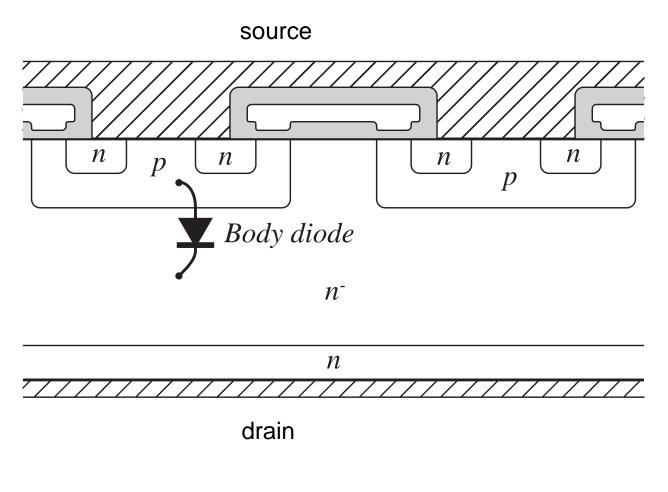

- *p*-*n*⁻ junction forms an effective diode, in parallel with the channel
- negative drain-tosource voltage can forward-bias the body diode
- diode can conduct the full MOSFET rated current
- diode switching speed not optimized —body diode is slow, Q_r is large

Typical MOSFET characteristics

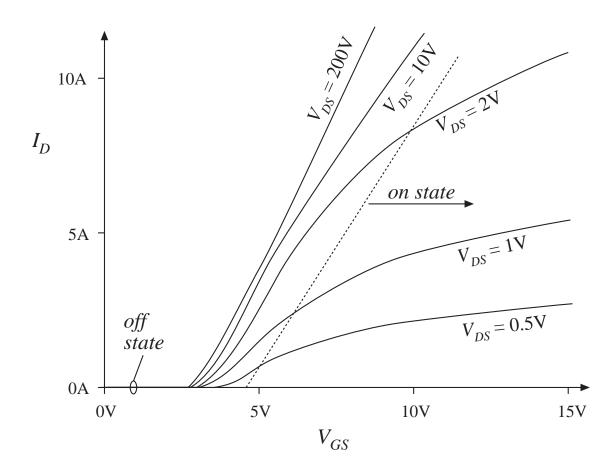


- Off state: $V_{GS} < V_{th}$
- On state: $V_{GS} >> V_{th}$
- MOSFET can conduct peak currents well in excess of average current rating characteristics are unchanged
- on-resistance has positive temperature coefficient, hence easy to parallel

Fundamentals of Power Electronics

Chapter 4: Switch realization

A simple MOSFET equivalent circuit

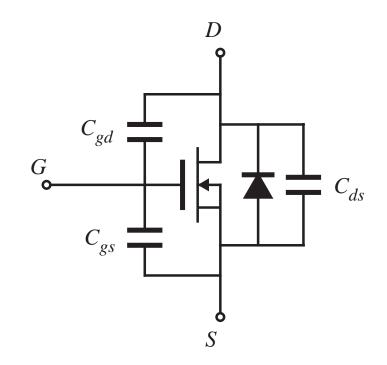

•
$$C_{gs}$$
: large, essentially constant

•
$$C_{gd}$$
: small, highly nonlinear

• C_{ds} : intermediate in value, highly nonlinear

 switching times determined by rate at which gate driver charges/ discharges C_{gs} and C_{gd}

$$C_{ds}(v_{ds}) = \frac{C_0}{\sqrt{1 + \frac{v_{ds}}{V_0}}}$$

$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C_0}{\sqrt{v_{ds}}}$$


Characteristics of several commercial power MOSFETs

Part number	Rated max voltage	Rated avg current	R _{on}	Q_g (typical)	
IRFZ48	60V	50A	0.018Ω	110nC	
IRF510	100V	5.6A	0.54Ω	8.3nC	
IRF540	100V	28A	0.077Ω	72nC	
APT10M25BNR	100V	75A	0.025Ω	171nC	
IRF740	400V	10A	0.55Ω	63nC	
MTM15N40E	400V	15A	0.3Ω	110nC	
APT5025BN	500V	23A	0.25Ω	83nC	
APT1001RBNR	1000V	11A	1.0Ω	150nC	

MOSFET: conclusions


- A majority-carrier device: fast switching speed
- Typical switching frequencies: tens and hundreds of kHz
- On-resistance increases rapidly with rated blocking voltage
- Easy to drive
- The device of choice for blocking voltages less than 500V
- 1000V devices are available, but are useful only at low power levels (100W)
- Part number is selected on the basis of on-resistance rather than current rating

4.2.3. Bipolar Junction Transistor (BJT)

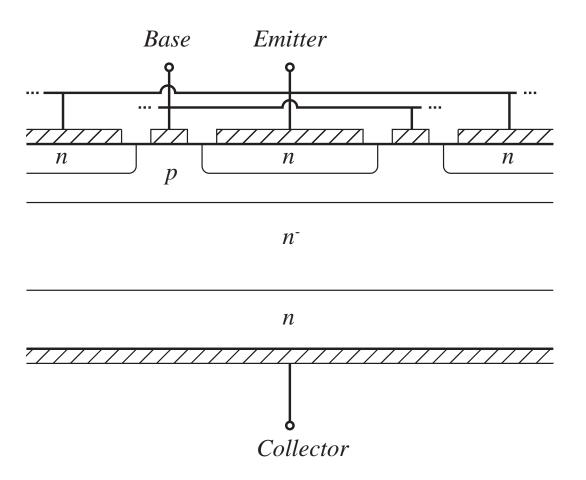

- Interdigitated base and emitter contacts
- Vertical current flow
- npn device is shown
- minority carrier device
- on-state: base-emitter and collector-base junctions are both forward-biased
- on-state: substantial minority charge in p and n⁻ regions, conductivity modulation


BJT switching times

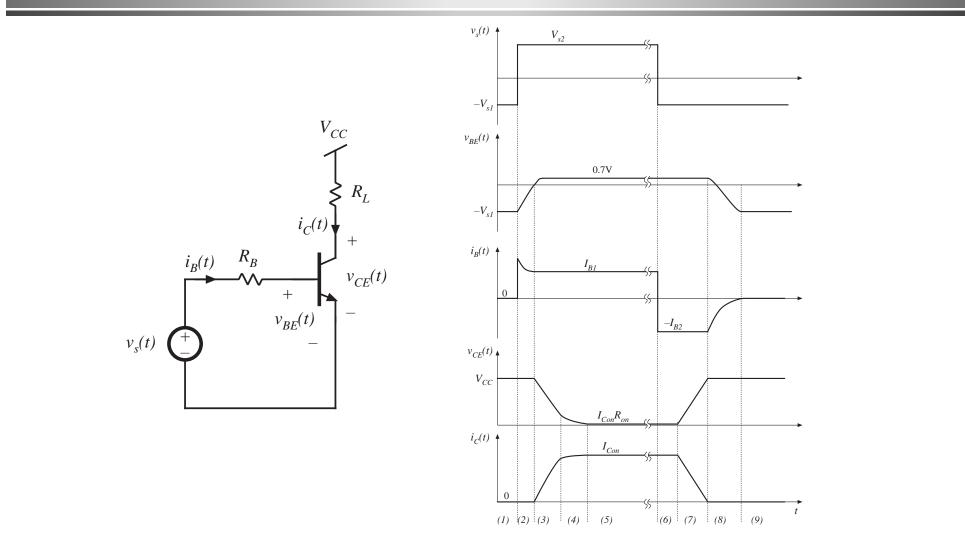


Fundamentals of Power Electronics

Chapter 4: Switch realization

Ideal base current waveform

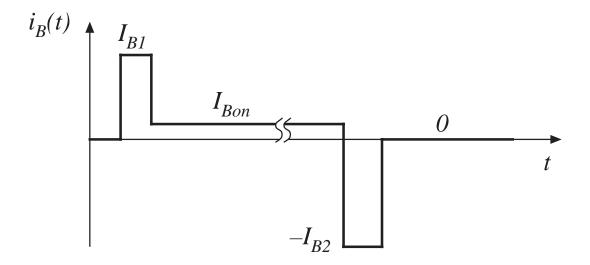


Current crowding due to excessive I_{B2}

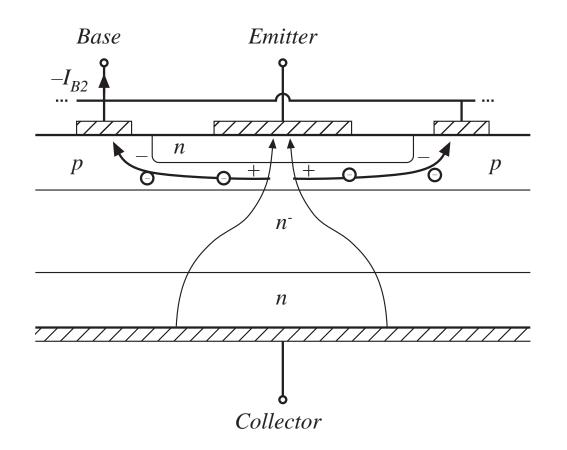

can lead to formation of hot spots and device failure


BJT characteristics

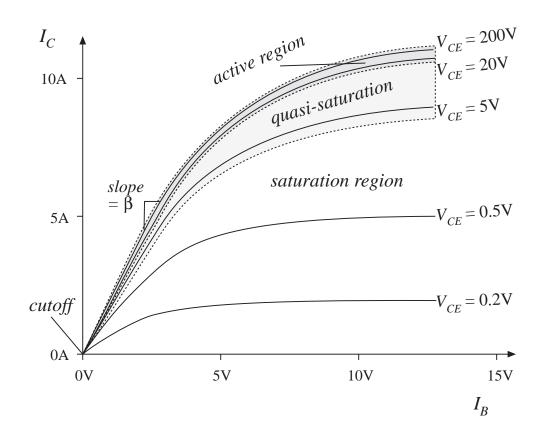

- Off state: $I_B = 0$
- On state: $I_B > I_C / \beta$
- Current gain β decreases rapidly at high current.
 Device should not be operated at instantaneous currents exceeding the rated value

Fundamentals of Power Electronics

Breakdown voltages

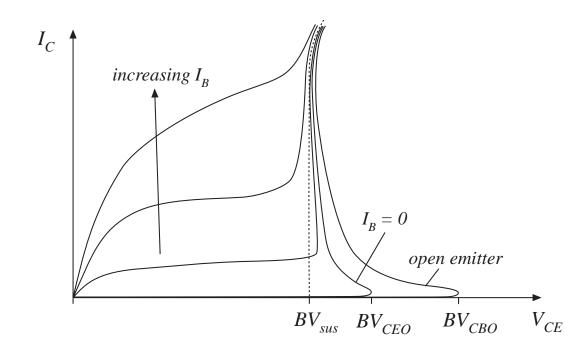


 BV_{CBO} : avalanche breakdown voltage of base-collector junction, with the emitter open-circuited

 BV_{CEO} : collector-emitter breakdown voltage with zero base current

 BV_{sus} : breakdown voltage observed with positive base current

In most applications, the offstate transistor voltage must not exceed BV_{CEO} .

Darlington-connected BJT

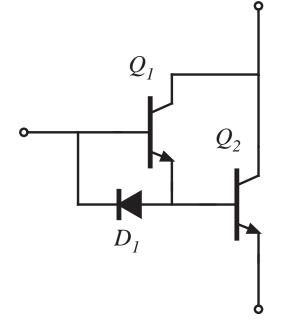


- Increased current gain, for high-voltage applications
- In a monolithic Darlington device, transistors Q₁ and Q₂ are integrated on the same silicon wafer
- Diode *D*₁ speeds up the turn-off process, by allowing the base driver to actively remove the stored charge of both *Q*₁ and *Q*₂ during the turn-off transition

Conclusions: BJT


- BJT has been replaced by MOSFET in low-voltage (<500V) applications
- BJT is being replaced by IGBT in applications at voltages above 500V
- A minority-carrier device: compared with MOSFET, the BJT exhibits slower switching, but lower on-resistance at high voltages

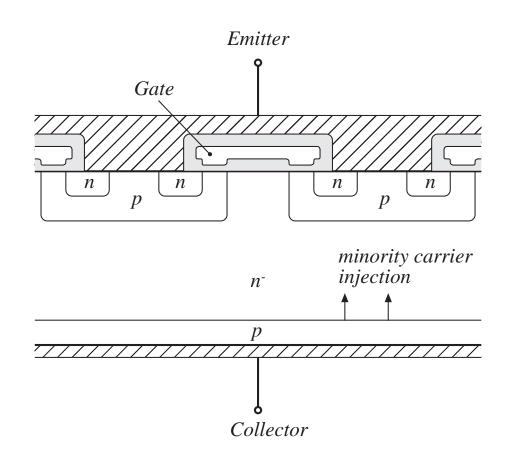4.2.4. The Insulated Gate Bipolar Transistor (IGBT)




- A four-layer device
- Similar in construction to MOSFET, except extra p region
- On-state: minority carriers are injected into n⁻ region, leading to conductivity modulation
- compared with MOSFET: slower switching times, lower on-resistance, useful at higher voltages (up to 1700V)

The IGBT

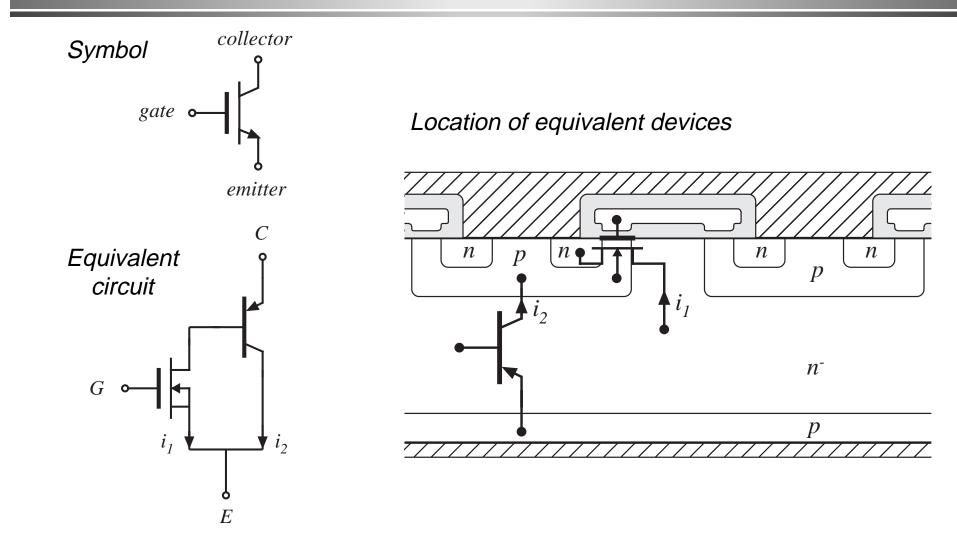

Fundamentals of Power Electronics

Current tailing in IGBTs

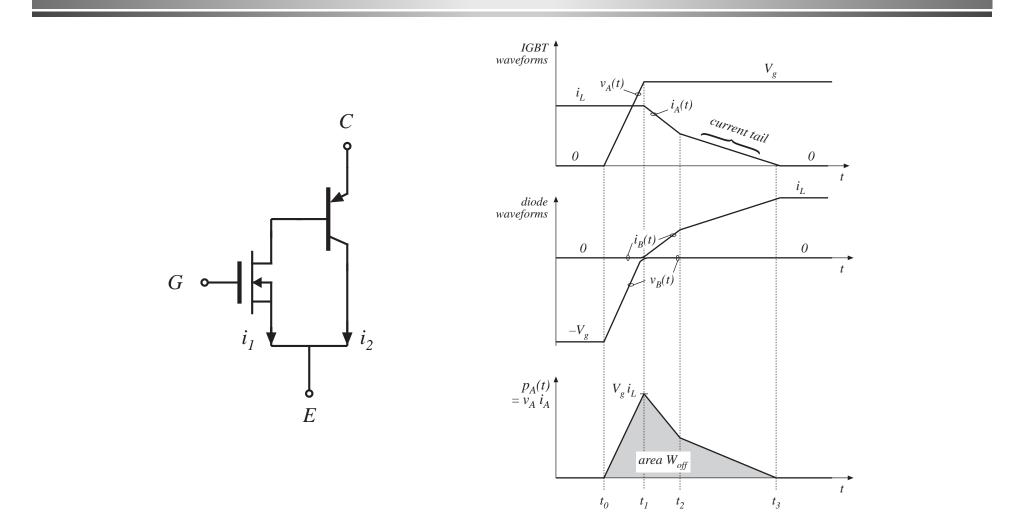

Fundamentals of Power Electronics

Chapter 4: Switch realization


Characteristics of several commercial devices

Part number	Rated max voltage	Rated avg current	V_F (typical)	$t_f(typical)$
Single-chip dev	ices			
HGTG32N60E2	600V	32A	2.4V	0.62µs
HGTG30N120D2	1200V	30A	3.2A	0.58µs
Multiple-chip p	ower modules			
CM400HA-12E	600V	400A	2.7V	0.3µs
CM300HA-24E	1200V	300A	2.7V	0.3µs

Conclusions: IGBT

- Becoming the device of choice in 500-1700V applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current —easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance. 2-4V typical
- Easy to drive —similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing —next generation: 2500V

4.2.5. Thyristors (SCR, GTO, MCT)

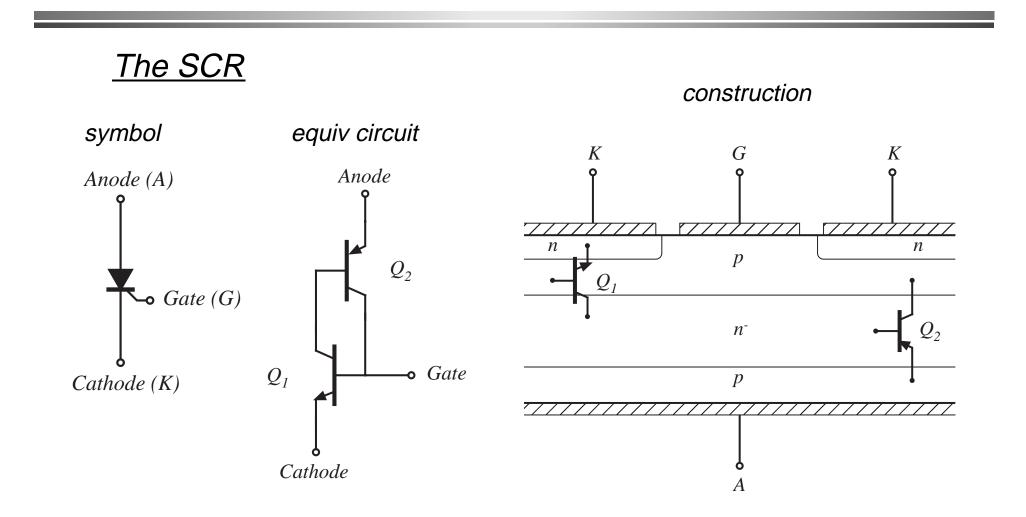


Fundamentals of Power Electronics

Chapter 4: Switch realization


The Silicon Controlled Rectifier (SCR)

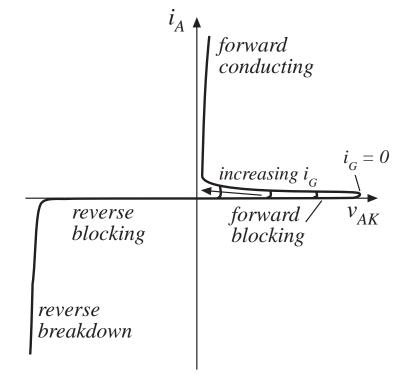- Positive feedback —a latching device
- A minority carrier device
- Double injection leads to very low on-resistance, hence low forward voltage drops attainable in very high voltage devices
- Simple construction, with large feature size
- Cannot be actively turned off
- A voltage-bidirectional two-quadrant switch
- 5000-6000V, 1000-2000A devices



Why the conventional SCR cannot be turned off via gate control

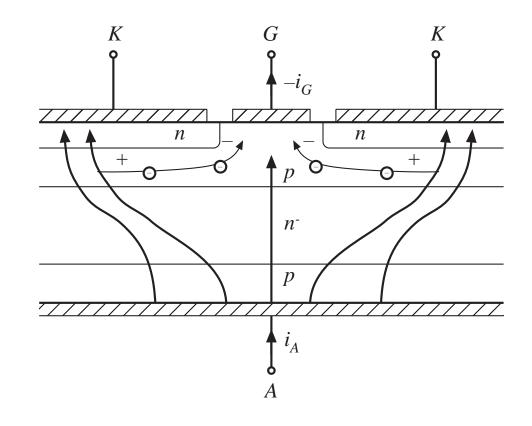- Large feature size
- Negative gate current induces lateral voltage drop along gate-cathode junction
- Gate-cathode junction becomes reverse-biased only in vicinity of gate contact



The Gate Turn-Off Thyristor (GTO)


- An SCR fabricated using modern techniques —small feature size
- Gate and cathode contacts are highly interdigitated
- Negative gate current is able to completely reverse-bias the gatecathode junction

Turn-off transition:


- Turn-off current gain: typically 2-5
- Maximum controllable on-state current: maximum anode current that can be turned off via gate control. GTO can conduct peak currents well in excess of average current rating, but cannot switch off

The MOS-Controlled Thyristor (MCT)

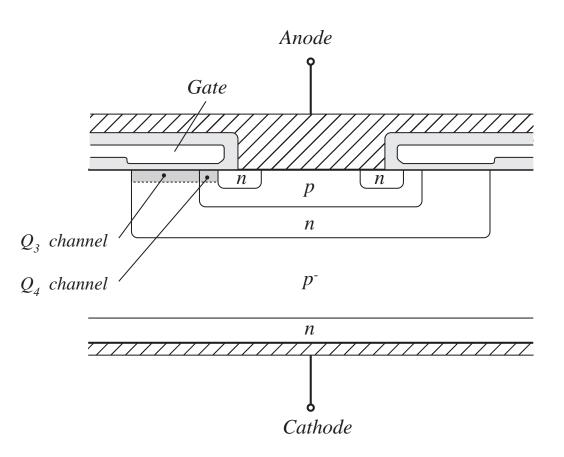- Still an emerging device, but some devices are commercially available
- p-type device
- A latching SCR, with added built-in MOSFETs to assist the turn-on and turn-off processes
- Small feature size, highly interdigitated, modern fabrication



The MCT: equivalent circuit

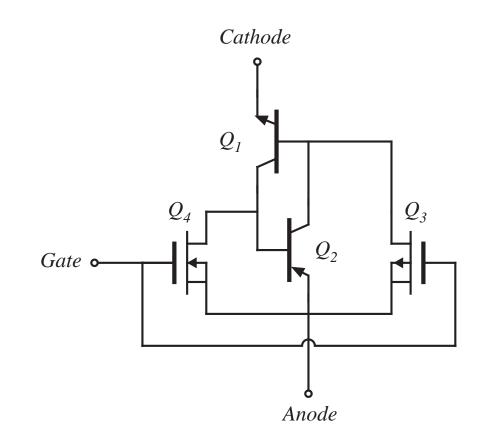

- Negative gate-anode voltage turns p-channel MOSFET Q₃ on, causing Q₁ and Q₂ to latch ON
- Positive gate-anode voltage turns n-channel MOSFET Q₄ on, reversebiasing the base-emitter junction of Q₂ and turning off the device
- Maximum current that can be interrupted is limited by the on-resistance of Q_4


Summary: Thyristors

- The thyristor family: double injection yields lowest forward voltage drop in high voltage devices. More difficult to parallel than MOSFETs and IGBTs
- The SCR: highest voltage and current ratings, low cost, passive turn-off transition
- The GTO: intermediate ratings (less than SCR, somewhat more than IGBT). Slower than IGBT. Slower than MCT. Difficult to drive.
- The MCT: So far, ratings lower than IGBT. Slower than IGBT. Easy to drive. Second breakdown problems? Still an emerging device.

4.3. Switching loss

- Energy is lost during the semiconductor switching transitions, via several mechanisms:
 - Transistor switching times
 - Diode stored charge
 - Energy stored in device capacitances and parasitic inductances
- Semiconductor devices are *charge controlled*
- Time required to insert or remove the controlling charge determines switching times

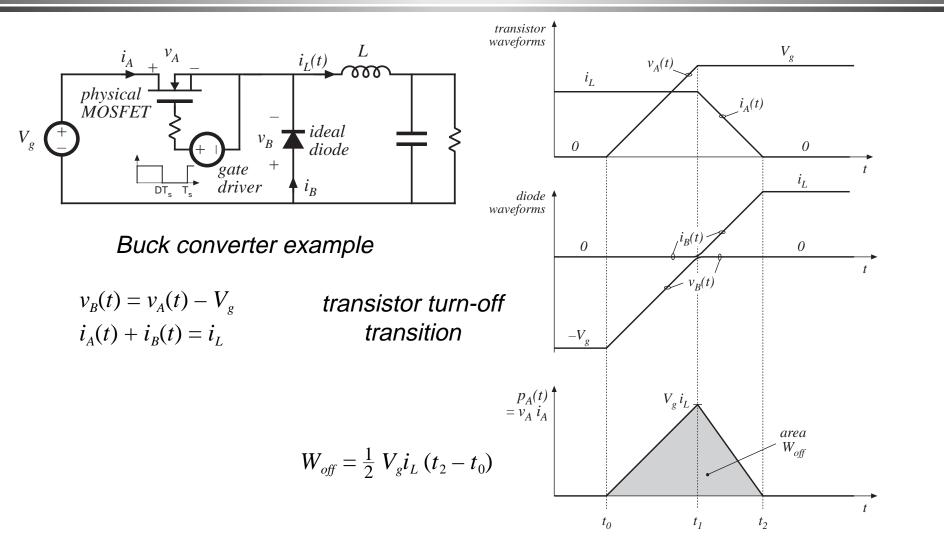4.3.1. Transistor switching with clamped inductive load



Fundamentals of Power Electronics

Chapter 4: Switch realization

Switching loss induced by transistor turn-off transition


Energy lost during transistor turn-off transition:

$$W_{off} = \frac{1}{2} V_{g} i_{L} (t_{2} - t_{0})$$

Similar result during transistor turn-on transition. Average power loss:


$$P_{sw} = \frac{1}{T_s} \int_{\substack{switching \\ transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$

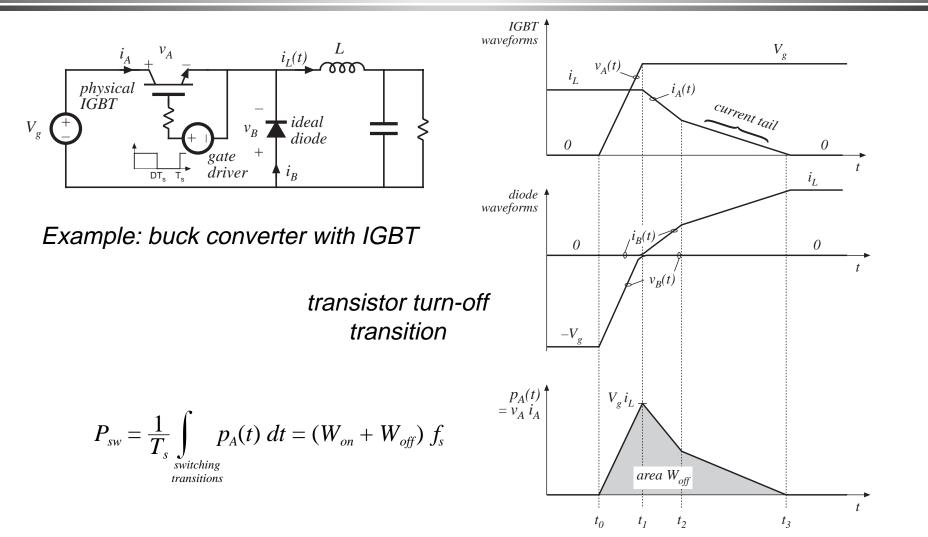Switching loss due to current-tailing in IGBT




Fundamentals of Power Electronics

4.3.2. Diode recovered charge

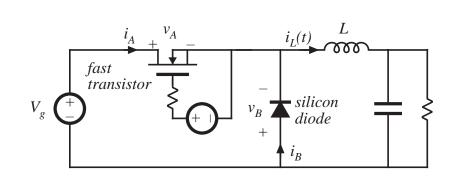


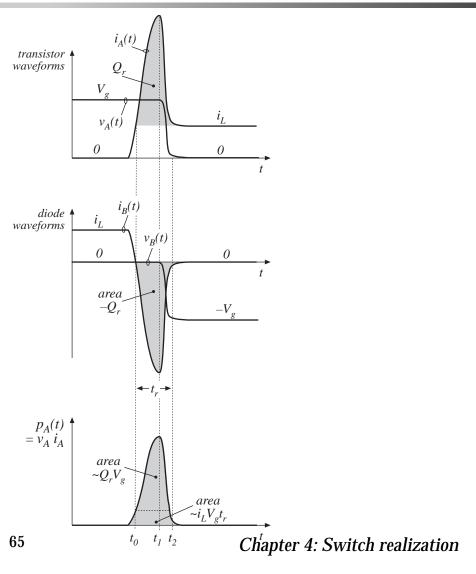- Diode recovered stored charge Q_r flows through transistor during transistor turn-on transition, inducing switching loss
- Q_r depends on diode on-state forward current, and on the rate-of-change of diode current during diode turn-off transition



Fundamentals of Power Electronics

Switching loss calculation

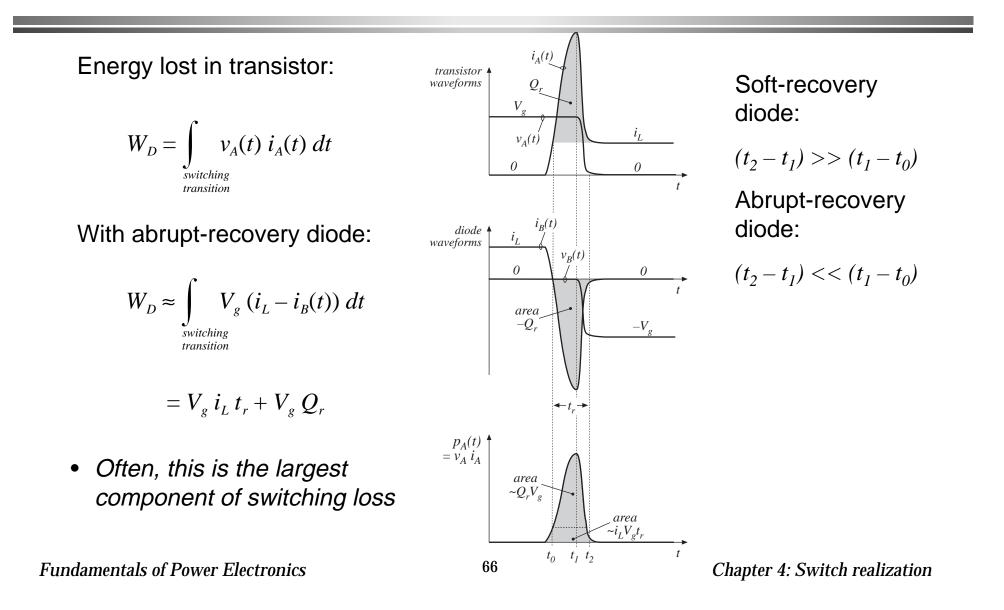

4.3.3. Device capacitances, and leakage, package, and stray inductances


- Capacitances that appear effectively in parallel with switch elements are shorted when the switch turns on. Their stored energy is lost during the switch turn-on transition.
- Inductances that appear effectively in series with switch elements are open-circuited when the switch turns off. Their stored energy is lost during the switch turn-off transition.

Total energy stored in linear capacitive and inductive elements:

$$W_{C} = \sum_{\substack{\text{capacitive}\\elements}} \frac{1}{2} C_{i} V_{i}^{2} \qquad \qquad W_{L} = \sum_{\substack{\text{inductive}\\elements}} \frac{1}{2} L_{j} I_{j}^{2}$$

Example: semiconductor output capacitances

Buck converter example

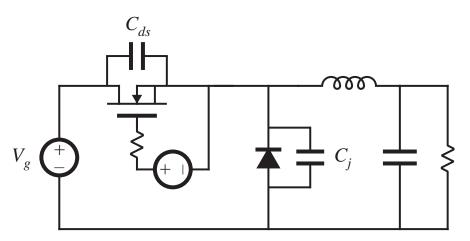

Energy lost during MOSFET turn-on transition (assuming linear capacitances):

$$W_C = \frac{1}{2} \left(C_{ds} + C_j \right) V_g^2$$

MOSFET nonlinear C_{ds}

Approximate dependence of incremental C_{ds} on v_{ds} :

$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C_0}{\sqrt{v_{ds}}}$$

Energy stored in C_{ds} at $v_{ds} = V_{DS}$:

$$W_{Cds} = \int v_{ds} \, i_C \, dt = \int_0^{V_{DS}} v_{ds} \, C_{ds}(v_{ds}) \, dv_{ds}$$
$$W_{Cds} = \int_0^{V_{DS}} C_0'(v_{ds}) \, \sqrt{v_{ds}} \, dv_{ds} = \frac{2}{3} \, C_{ds}(V_{DS}) \, V_{DS}^2$$

— same energy loss as linear capacitor having value $\frac{4}{3}C_{ds}(V_{DS})$

Some other sources of this type of switching loss

Schottky diode

- Essentially no stored charge
- Significant reverse-biased junction capacitance


Transformer leakage inductance

- Effective inductances in series with windings
- A significant loss when windings are not tightly coupled


Interconnection and package inductances


- Diodes
- Transistors
- A significant loss in high current applications

Ringing induced by diode stored charge

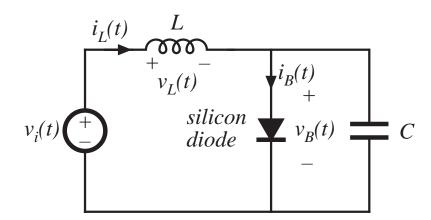

- Diode is forward-biased while $i_L(t) > 0$
- Negative inductor current removes diode stored charge Q_r
- When diode becomes reverse-biased, negative inductor current flows through capacitor *C*.
- Ringing of *L*-*C* network is damped by parasitic losses. Ringing energy is lost.

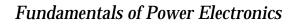

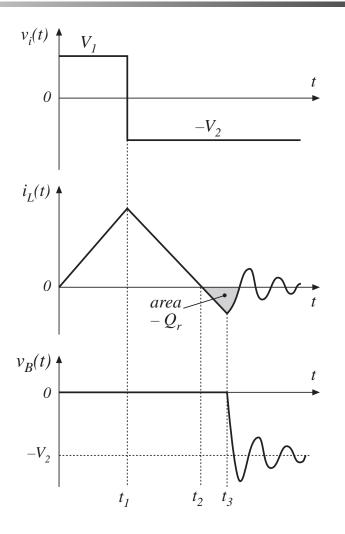

Chapter 4: Switch realization

Energy associated with ringing

 $Q_r = -\int_{t_0}^{t_3} i_L(t) dt$

Energy stored in inductor during interval $t_2 \le t \le t_3$: $W_L = \int_{t_2}^{t_3} v_L(t) i_L(t) dt$

Applied inductor voltage during interval $t_2 \le t \le t_3$: $v_L(t) = L \frac{di_L(t)}{dt} = -V_2$


Hence,

$$W_L = \int_{t_2}^{t_3} L \, \frac{di_L(t)}{dt} \, i_L(t) \, dt = \int_{t_2}^{t_3} (-V_2) \, i_L(t) \, dt$$

$$W_L = \frac{1}{2} L i_L^2(t_3) = V_2 Q_r$$

Recovered charge is

Fundamentals of Power Electronics

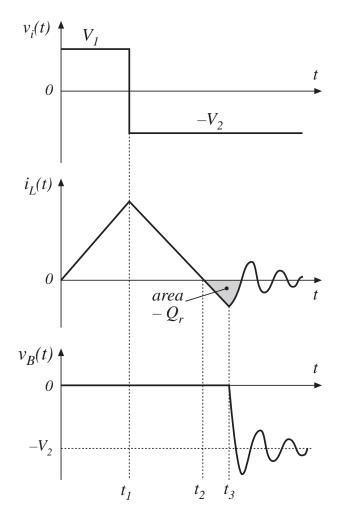

4.3.4. Efficiency vs. switching frequency

Add up all of the energies lost during the switching transitions of one switching period:

$$W_{tot} = W_{on} + W_{off} + W_D + W_C + W_L + \dots$$

Average switching power loss is

$$P_{sw} = W_{tot} f_{sw}$$


Total converter loss can be expressed as

$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$

where

 P_{fixed} = fixed losses (independent of load and f_{sw}) P_{cond} = conduction losses

Efficiency vs. switching frequency

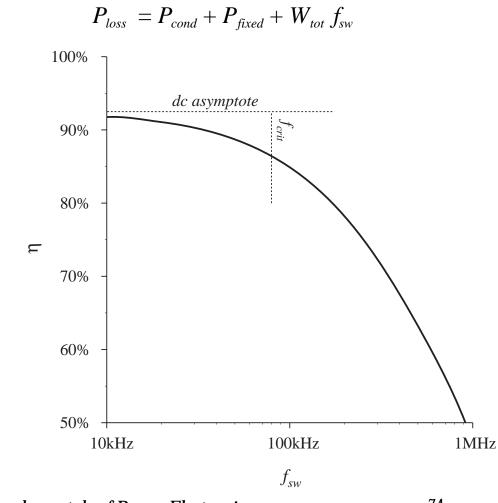

Switching losses are equal to the other converter losses at the critical frequency

$$f_{crit} = \frac{P_{cond} + P_{fixed}}{W_{tot}}$$

This can be taken as a rough upper limit on the switching frequency of a practical converter. For $f_{sw} > f_{crit}$, the efficiency decreases rapidly with frequency.

Fundamentals of Power Electronics

Summary of chapter 4

- 1. How an SPST ideal switch can be realized using semiconductor devices depends on the polarity of the voltage which the devices must block in the off-state, and on the polarity of the current which the devices must conduct in the on-state.
- 2. Single-quadrant SPST switches can be realized using a single transistor or a single diode, depending on the relative polarities of the off-state voltage and on-state current.
- 3. Two-quadrant SPST switches can be realized using a transistor and diode, connected in series (bidirectional-voltage) or in anti-parallel (bidirectional-current). Several four-quadrant schemes are also listed here.
- 4. A "synchronous rectifier" is a MOSFET connected to conduct reverse current, with gate drive control as necessary. This device can be used where a diode would otherwise be required. If a MOSFET with sufficiently low R_{on} is used, reduced conduction loss is obtained.

Summary of chapter 4

- 5. Majority carrier devices, including the MOSFET and Schottky diode, exhibit very fast switching times, controlled essentially by the charging of the device capacitances. However, the forward voltage drops of these devices increases quickly with increasing breakdown voltage.
- 6. Minority carrier devices, including the BJT, IGBT, and thyristor family, can exhibit high breakdown voltages with relatively low forward voltage drop. However, the switching times of these devices are longer, and are controlled by the times needed to insert or remove stored minority charge.
- 7. Energy is lost during switching transitions, due to a variety of mechanisms. The resulting average power loss, or switching loss, is equal to this energy loss multiplied by the switching frequency. Switching loss imposes an upper limit on the switching frequencies of practical converters.

Summary of chapter 4

- 8. The diode and inductor present a "clamped inductive load" to the transistor. When a transistor drives such a load, it experiences high instantaneous power loss during the switching transitions. An example where this leads to significant switching loss is the IGBT and the "current tail" observed during its turn-off transition.
- 9. Other significant sources of switching loss include diode stored charge and energy stored in certain parasitic capacitances and inductances. Parasitic ringing also indicates the presence of switching loss.

Chapter 5. The Discontinuous Conduction Mode


- 5.1. Origin of the discontinuous conduction mode, and mode boundary
- 5.2. Analysis of the conversion ratio M(D,K)
- 5.3. Boost converter example
- 5.4. Summary of results and key points

Introduction to Discontinuous Conduction Mode (DCM)

- Occurs because switching ripple in inductor current or capacitor voltage causes polarity of applied switch current or voltage to reverse, such that the current- or voltage-unidirectional assumptions made in realizing the switch are violated.
- Commonly occurs in dc-dc converters and rectifiers, having singlequadrant switches. May also occur in converters having two-quadrant switches.
- Typical example: dc-dc converter operating at light load (small load current). Sometimes, dc-dc converters and rectifiers are purposely designed to operate in DCM at all loads.
- Properties of converters change radically when DCM is entered:
 M becomes load-dependent
 Output impedance is increased
 Dynamics are altered
 - Control of output voltage may be lost when load is removed

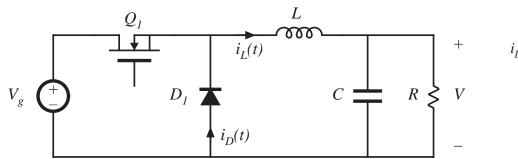5.1. Origin of the discontinuous conduction mode, and mode boundary

Buck converter example, with single-quadrant switches




Minimum diode current is $(I - \Delta i_L)$ Dc component I = V/RCurrent ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD'T_s}{2L}$$


Note that *I* depends on load, but Δi_L does not.

Fundamentals of Power Electronics

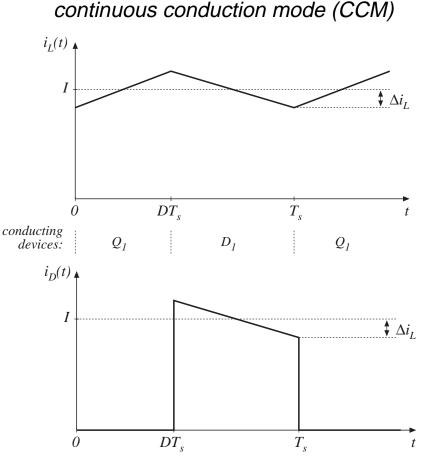

Chapter 5: Discontinuous conduction mode


Reduction of load current

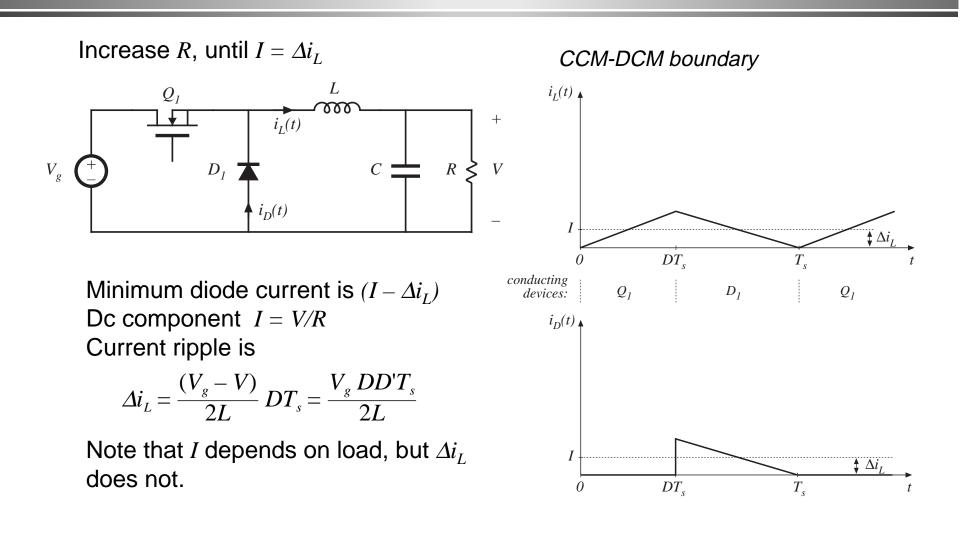

Fundamentals of Power Electronics

4

Further reduce load current

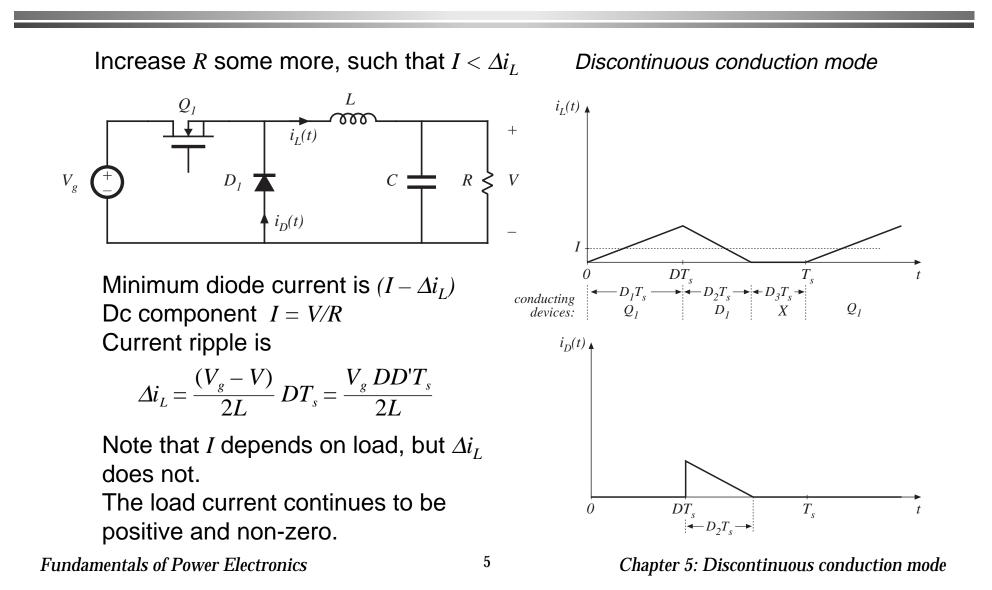

Mode boundary

 $I > \Delta i_L \quad for \ CCM$ $I < \Delta i_L \quad for \ DCM$

Insert buck converter expressions for *I* and Δi_L :

$$\frac{DV_g}{R} < \frac{DD'T_sV_g}{2L}$$

Simplify:

$$\frac{2L}{RT_s} < D'$$

This expression is of the form

$$K < K_{crit}(D) \quad for \ DCM$$

where $K = \frac{2L}{RT_s} \quad and \quad K_{crit}(D) = D^{T}$

Fundamentals of Power Electronics

K and K_{crit} vs. D

for *K* < 1: for *K* > 1: $K > K_{crit}$: CCM 2 $K < K_{crit}$: 2 $K > K_{crit}$: $K = 2L/RT_s$ DCM ССМ $\frac{K_{crit}(D)}{1-D} = 1-D$ $\frac{K_{crit}(D)}{1-D} = 1-D$ 1 1 $K = 2L/RT_s$ 0 0 D 0 D 0 1

7

Critical load resistance R_{crit}

Solve K_{crit} equation for load resistance *R*:

$$R < R_{crit}(D) \quad for \ CCM$$
$$R > R_{crit}(D) \quad for \ DCM$$
where
$$R_{crit}(D) = \frac{2L}{D'T_s}$$

Summary: mode boundary

$K > K_{crit}(D)$	or	$R < R_{crit}(D)$	for CCM
$K < K_{crit}(D)$	or	$R > R_{crit}(D)$	for DCM

Table 5.1. CCM-DCM mode boundaries for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	$\max_{0 \le D \le 1} (K_{crit})$	$R_{crit}(D)$	$\min_{0 \le D \le 1} (R_{crit})$
Buck	(1 - D)	1	$\frac{2L}{(1-D)T_s}$	$2 \frac{L}{T_s}$
Boost	$D (1 - D)^2$	$\frac{4}{27}$	$\frac{2L}{D\left(1-D\right)^2 T_s}$	$\frac{27}{2} \frac{L}{T_s}$
Buck-boost	$(1 - D)^2$	1	$\frac{2L}{\left(1-D\right)^2 T_{\rm s}}$	$2 \frac{L}{T_s}$

5.2. Analysis of the conversion ratio *M*(*D*,*K*)

Analysis techniques for the discontinuous conduction mode:

Inductor volt-second balance

$$\langle v_L \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = 0$$

Capacitor charge balance

$$\left\langle i_{C}\right\rangle = \frac{1}{T_{s}}\int_{0}^{T_{s}}i_{C}(t) dt = 0$$


Small ripple approximation sometimes applies:

```
v(t) \approx V because \Delta v \ll V
```

```
i(t) \approx I is a poor approximation when \Delta i > I
```

Converter steady-state equations obtained via charge balance on each capacitor and volt-second balance on each inductor. Use care in applying small ripple approximation.

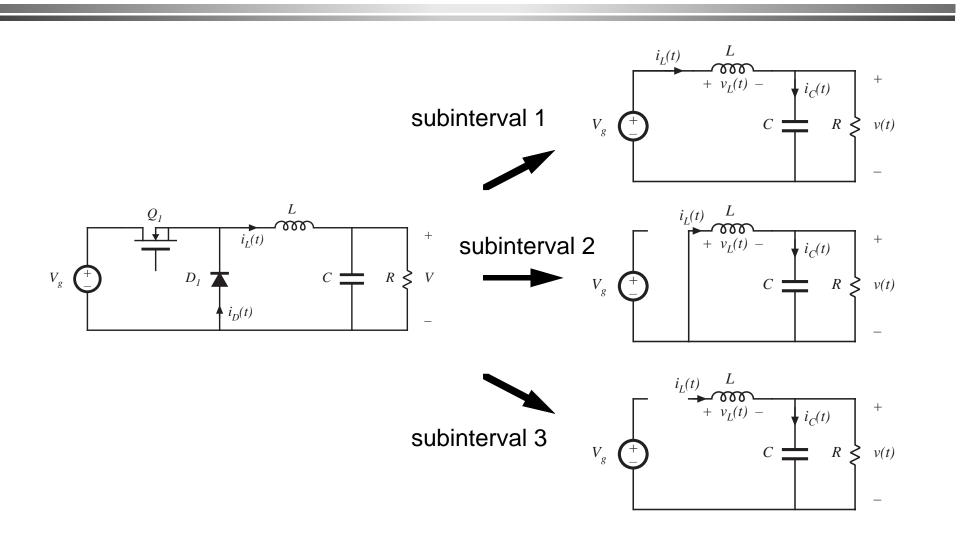Example: Analysis of DCM buck converter *M*(*D*,*K*)




$$v_L(t) = V_g - v(t)$$
$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation for v(t) (but not for i(t)!):

$$v_L(t) \approx V_g - V$$

 $i_C(t) \approx i_L(t) - V / R$

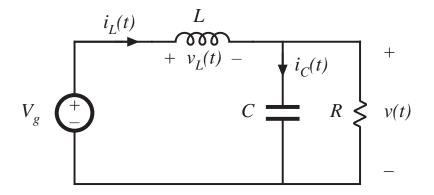

 V_{g}

$$v_L(t) = -v(t)$$


$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation for v(t) but not for i(t):

of for
$$i(t)$$
:

$$i_C(t) \approx i_L(t) - V / R$$

 $v_L(t) \approx -$

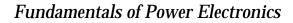


v(t)

$$v_L = 0, \quad i_L = 0$$


 $i_C(t) = i_L(t) - v(t) / R$

Small ripple approximation:

$$v_L(t) = 0$$
$$i_C(t) = -V / R$$

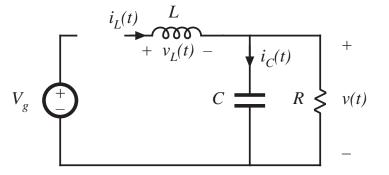

Inductor volt-second balance

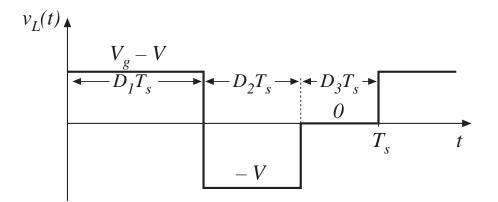

Volt-second balance:

$$\langle v_L(t) \rangle = D_1(V_g - V) + D_2(-V) + D_3(0) = 0$$

Solve for *V*:

$$V = V_g \frac{D_1}{D_1 + D_2}$$

note that D_2 is unknown

Fundamentals of Power Electronics

15

Capacitor charge balance

node equation:

$$i_L(t) = i_C(t) + V / R$$


capacitor charge balance:

$$\langle i_C \rangle = 0$$

hence

$$\langle i_L \rangle = V / R$$

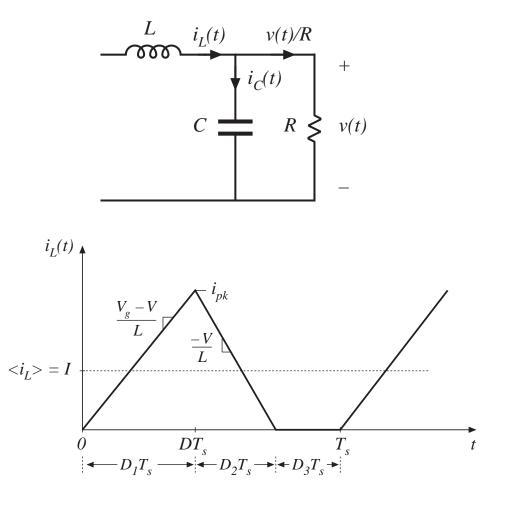must compute dc component of inductor current and equate to load current (for this buck converter example)



Inductor current waveform

 $\frac{V_g - V}{L}$

 $-D_1T_s$

 $i_L(t)$

 $< i_L > = I$

peak current: $i_L(D_1T_s) = i_{pk} = \frac{V_g - V}{L} D_1T_s$ average current: $\langle i_L \rangle = \frac{1}{T_s} \int_0^{T_s} i_L(t) dt$

triangle area formula:

$$\int_0^{T_s} i_L(t) \, dt = \frac{1}{2} \, i_{pk} \, (D_1 + D_2) T_s$$

$$\left\langle i_L \right\rangle = \left(V_g - V \right) \frac{D_1 T_s}{2L} \left(D_1 + D_2 \right)$$

equate dc component to dc load current:

 $\overrightarrow{DT}_{s} \qquad T_{s}$

$$\frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V)$$

Solution for *V*

Two equations and two unknowns (V and D_2):


$$V = V_g \frac{D_1}{D_1 + D_2}$$
 (from inductor volt-second balance)
$$\frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V)$$
 (from capacitor charge balance)

Eliminate D_2 , solve for V:

$$\frac{V}{V_g} = \frac{2}{1 + \sqrt{1 + 4K / D_1^2}}$$


where $K = 2L / RT_s$
valid for $K < K_{crit}$

Buck converter M(D,K)

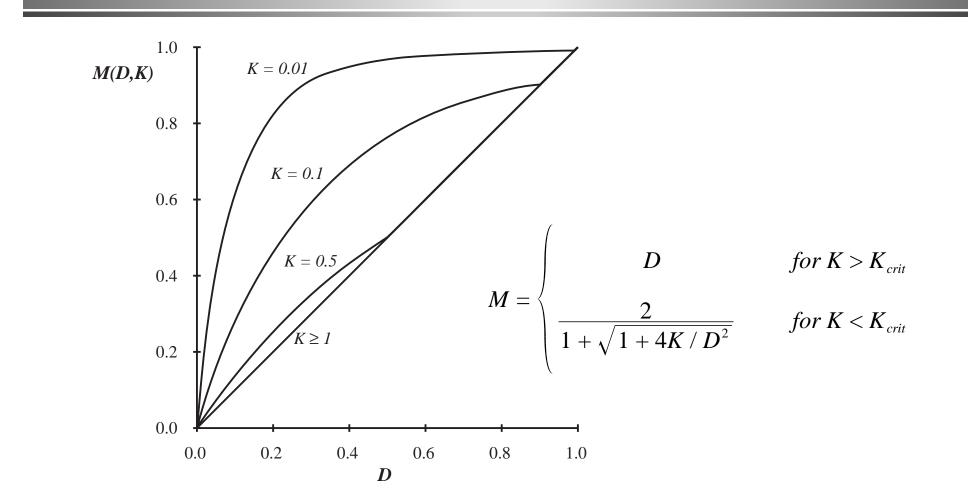

Fundamentals of Power Electronics

5.3. Boost converter example

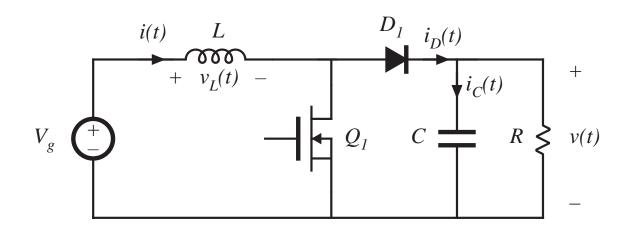

Mode boundary:


Previous CCM soln:

$$I > \Delta i_{L} \quad for \ CCM$$
$$I < \Delta i_{L} \quad for \ DCM$$


$$I = \frac{V_g}{D'^2 R} \qquad \Delta i_L = \frac{V_g}{2L} DT_s$$

Fundamentals of Power Electronics

Mode boundary

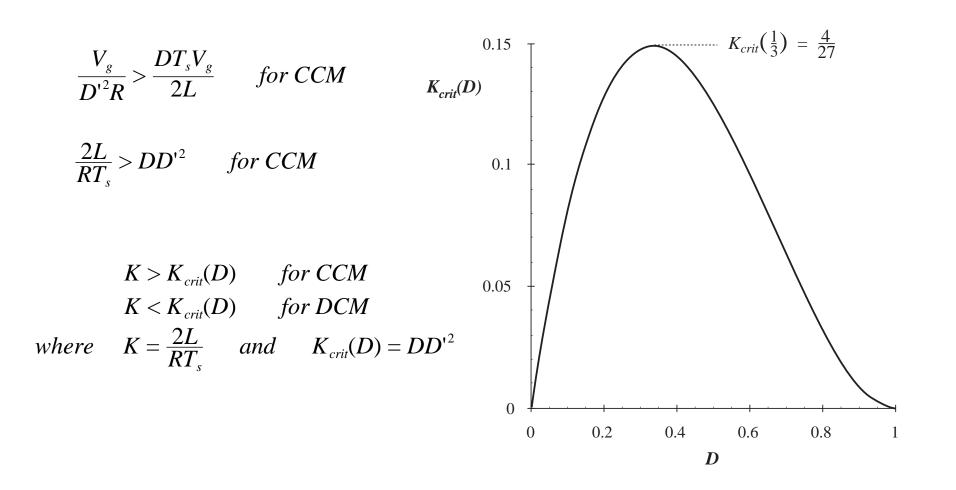



Mode boundary

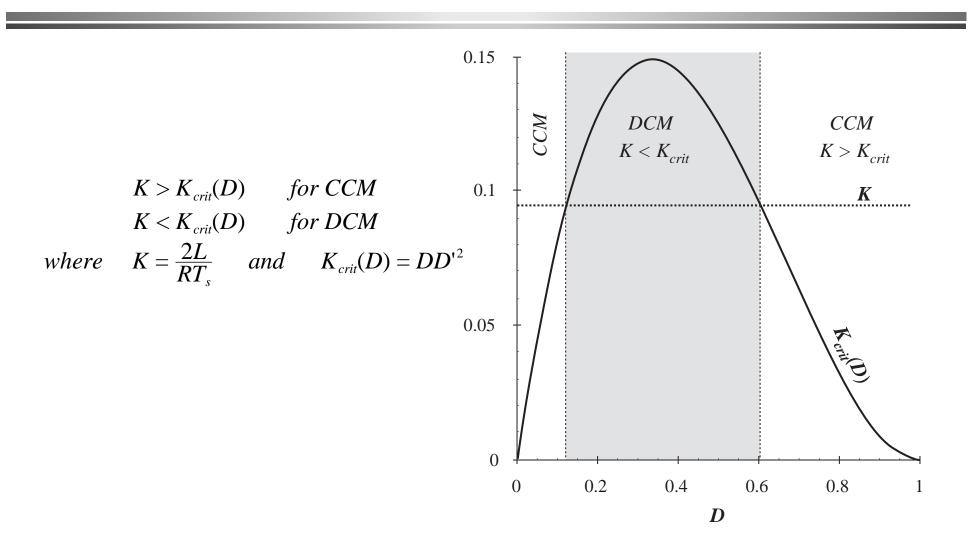



Fundamentals of Power Electronics

Conversion ratio: DCM boost

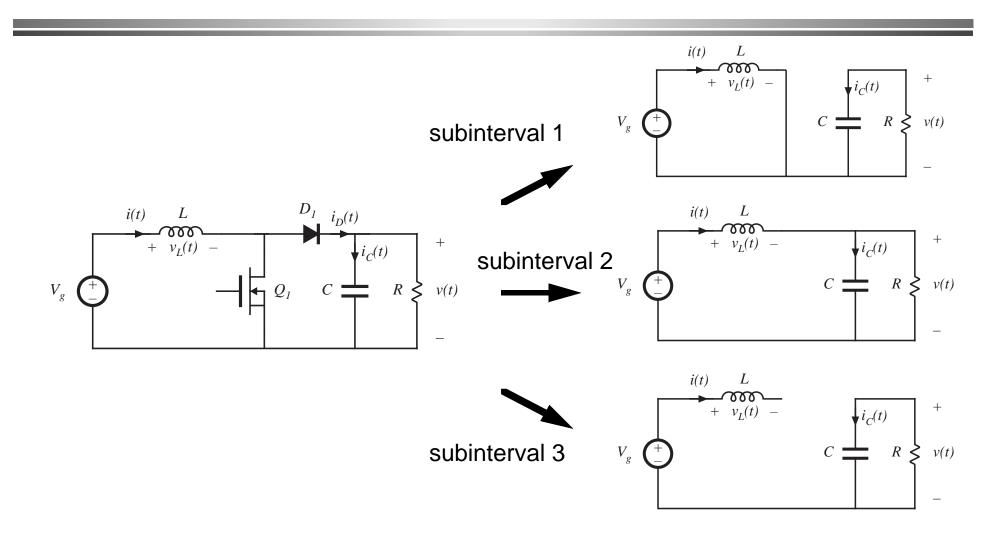


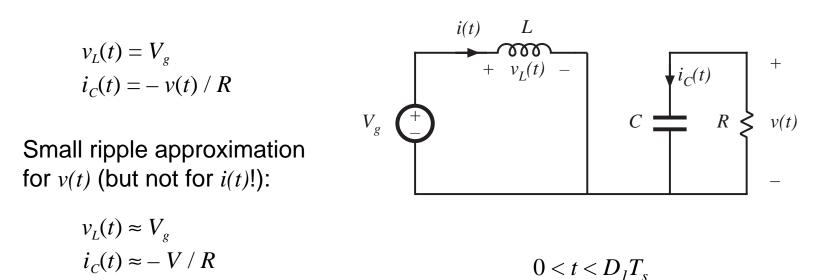

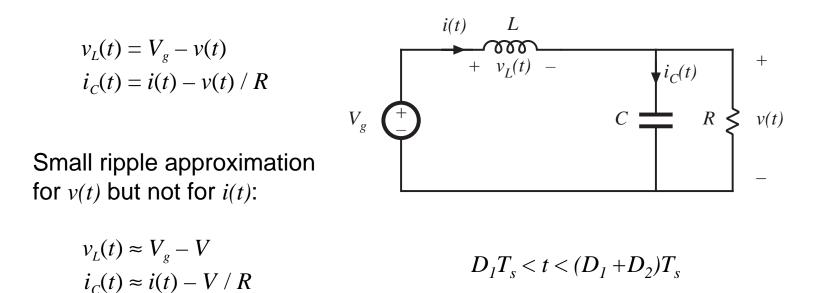

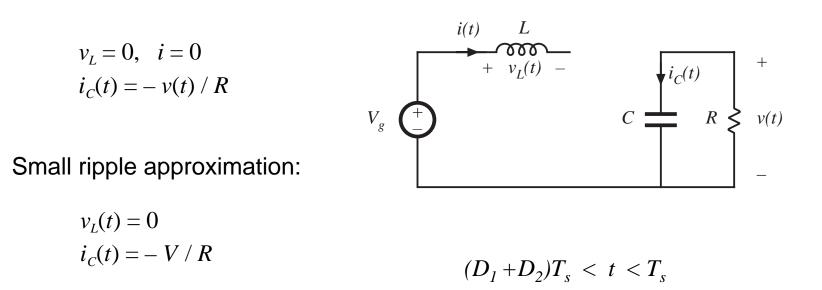

Inductor volt-second balance

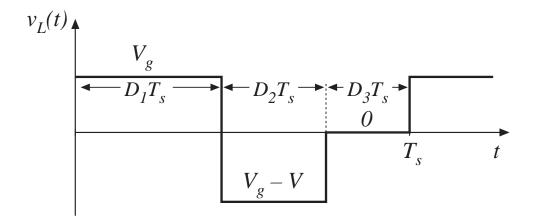

Volt-second balance:

$$D_1 V_g + D_2 (V_g - V) + D_3 (0) = 0$$

Solve for *V*:

$$V = \frac{D_1 + D_2}{D_2} V_g$$

note that D_2 is unknown

Fundamentals of Power Electronics

Capacitor charge balance

node equation:

$$i_D(t) = i_C(t) + v(t) / R$$


capacitor charge balance:

$$\langle i_C \rangle = 0$$

hence

$$\langle i_D \rangle = V / R$$

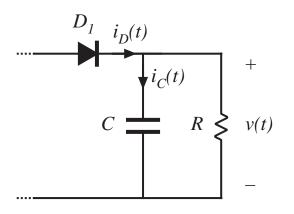must compute dc component of diode current and equate to load current (for this boost converter example)



Inductor and diode current waveforms

peak current:


$$i_{pk} = \frac{V_g}{L} D_1 T_s$$

average diode current:

$$\left\langle i_D \right\rangle = \frac{1}{T_s} \int_0^{T_s} i_D(t) dt$$

triangle area formula:
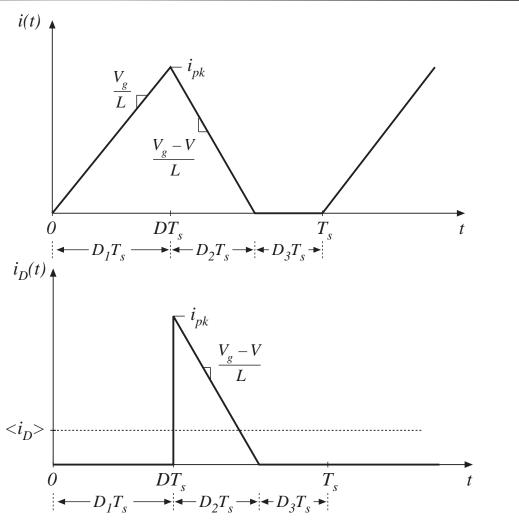
$$\int_0^{T_s} i_D(t) \, dt = \frac{1}{2} \, i_{pk} \, D_2 T_s$$



Fundamentals of Power Electronics

Equate diode current to load current

average diode current:

$$\langle i_D \rangle = \frac{1}{T_s} \left(\frac{1}{2} i_{pk} D_2 T_s \right) = \frac{V_g D_1 D_2 T_s}{2L}$$

equate to dc load current:

$$\frac{V_g D_1 D_2 T_s}{2L} = \frac{V}{R}$$

Solution for *V*

Two equations and two unknowns (V and D_2):

$V = \frac{D_1 + D_2}{D_2} V_g$	(from inductor volt-second balance)	
$\frac{V_g D_1 D_2 T_s}{2L} = \frac{V}{R}$	(from capacitor charge balance)	

Eliminate D_2 , solve for V. From volt-sec balance eqn:

$$D_2 = D_1 \frac{V_g}{V - V_g}$$

Substitute into charge balance eqn, rearrange terms:

$$V^{2} - VV_{g} - \frac{V_{g}^{2}D_{1}^{2}}{K} = 0$$

Solution for *V*

$$V^2 - VV_g - \frac{V_g^2 D_1^2}{K} = 0$$

Use quadratic formula:

$$\frac{V}{V_g} = \frac{1 \pm \sqrt{1 + 4D_1^2 / K}}{2}$$


Note that one root leads to positive *V*, while other leads to negative *V*. Select positive root:

$$\frac{V}{V_g} = M(D_1, K) = \frac{1 + \sqrt{1 + 4D_1^2 / K}}{2}$$

where	$K = 2L / RT_s$
valid for	$K < K_{crit}(D)$

Transistor duty cycle D = interval 1 duty cycle D_1

Boost converter characteristics

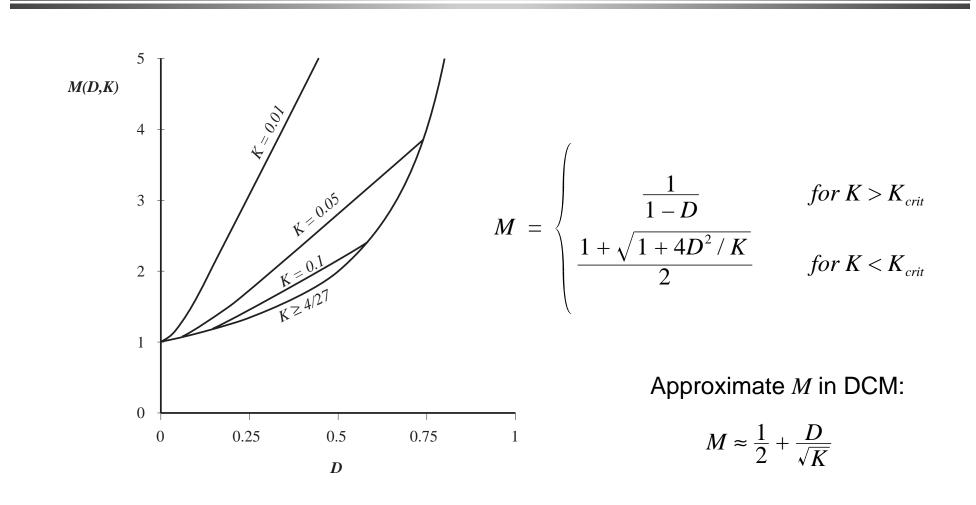

Fundamentals of Power Electronics


Summary of DCM characteristics

Table 5.2. Summary of CCM-DCM characteristics for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	DCM M(D,K)	$DCM D_2(D, K)$	CCM M(D)
Buck	(1 - D)	$\frac{2}{1+\sqrt{1+4K/D^2}}$	$\frac{K}{D}M(D,K)$	D
Boost	$D (1 - D)^2$	$\frac{1+\sqrt{1+4D^2/K}}{2}$	$\frac{K}{D}M(D,K)$	$\frac{1}{1-D}$
Buck-boost	$(1 - D)^2$	$-\frac{D}{\sqrt{K}}$	\sqrt{K}	$-\frac{D}{1-D}$

with $K = 2L / RT_s$. DCM occurs for $K < K_{crit}$.

Summary of DCM characteristics

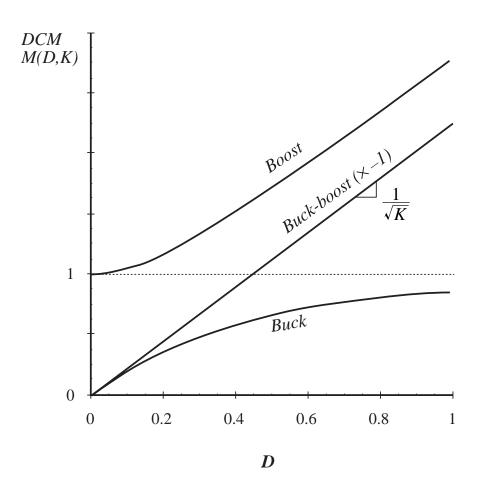

- DCM buck and boost characteristics are asymptotic to M = 1 and to the DCM buck-boost characteristic
- DCM buck-boost characteristic is linear
- CCM and DCM characteristics intersect at mode boundary. Actual *M* follows characteristic having larger magnitude
- DCM boost characteristic is nearly linear

Summary of key points

- 1. The discontinuous conduction mode occurs in converters containing current- or voltage-unidirectional switches, when the inductor current or capacitor voltage ripple is large enough to cause the switch current or voltage to reverse polarity.
- 2. Conditions for operation in the discontinuous conduction mode can be found by determining when the inductor current or capacitor voltage ripples and dc components cause the switch on-state current or off-state voltage to reverse polarity.
- 3. The dc conversion ratio *M* of converters operating in the discontinuous conduction mode can be found by application of the principles of inductor volt-second and capacitor charge balance.

Summary of key points


- 4. Extra care is required when applying the small-ripple approximation. Some waveforms, such as the output voltage, should have small ripple which can be neglected. Other waveforms, such as one or more inductor currents, may have large ripple that cannot be ignored.
- 5. The characteristics of a converter changes significantly when the converter enters DCM. The output voltage becomes loaddependent, resulting in an increase in the converter output impedance.

Chapter 6. Converter Circuits

- 6.1. Circuit manipulations
- 6.2. A short list of converters
- 6.3. Transformer isolation
- 6.4. Converter evaluation and design
- 6.5. Summary of key points

- Where do the boost, buck-boost, and other converters originate?
- How can we obtain a converter having given desired properties?
- What converters are possible?
- How can we obtain transformer isolation in a converter?
- For a given application, which converter is best?

6.1. Circuit manipulations

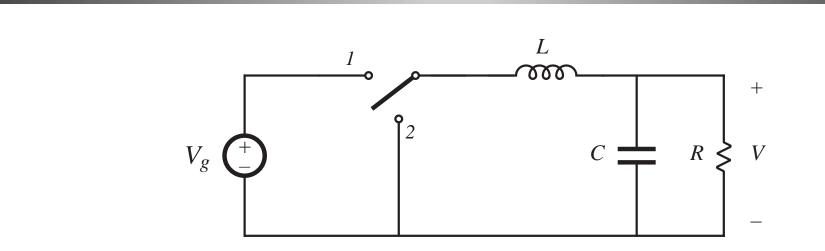


Begin with buck converter: derived in chapter 1 from first principles

- Switch changes dc component, low-pass filter removes switching harmonics
- Conversion ratio is M = D

6.1.1. Inversion of source and load


Interchange power input and output ports of a converter

Buck converter example $V_2 = DV_1$

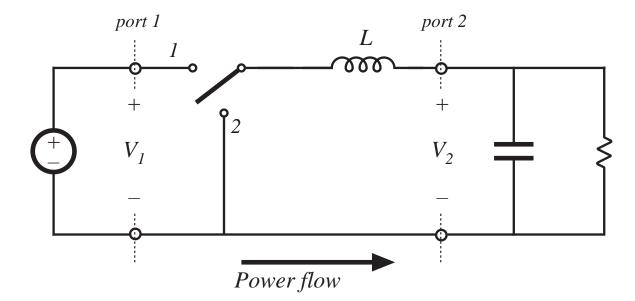

Inversion of source and load

Interchange power source and load:

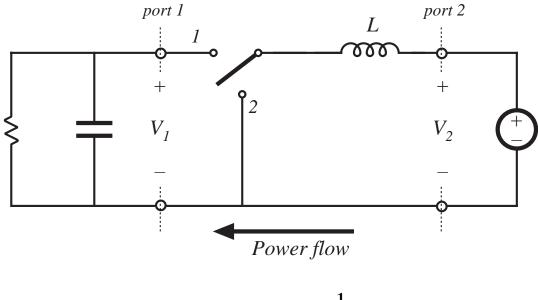


$$V_2 = DV_1 \qquad \qquad V_1 = \frac{1}{D} V_2$$

Realization of switches as in chapter 4


- Reversal of power flow requires new realization of switches
- Transistor conducts when switch is in position 2
- Interchange of *D* and *D*'

$$V_1 = \frac{1}{D'} V_2$$

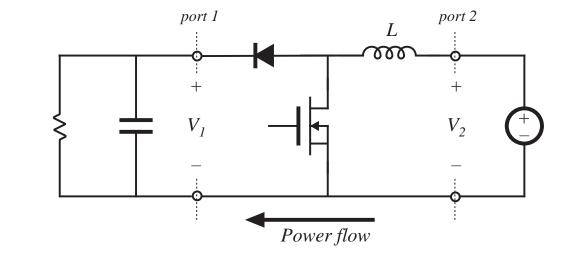

Inversion of buck converter yields boost converter


6.1.2. Cascade connection of converters

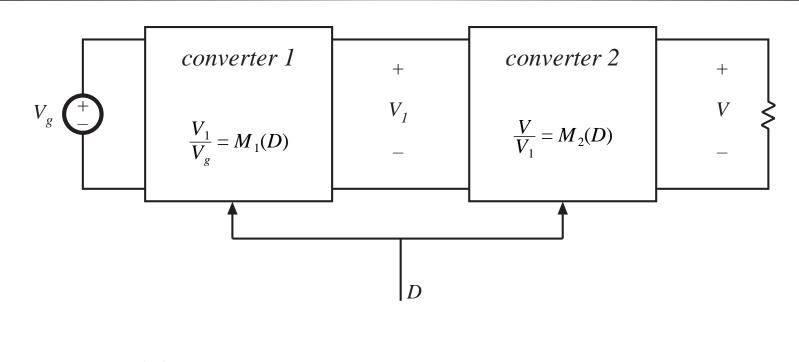


$$V_1 = M_1(D) V_g$$

 $V = M_2(D) V_1$
 $\longrightarrow \frac{V}{V_g} = M(D) = M_1(D) M_2(D)$


Example: buck cascaded by boost

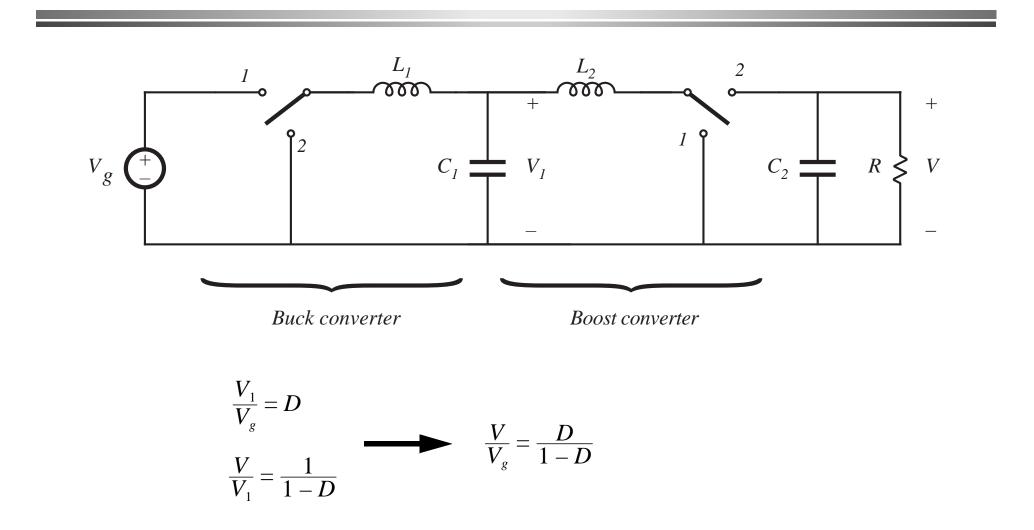

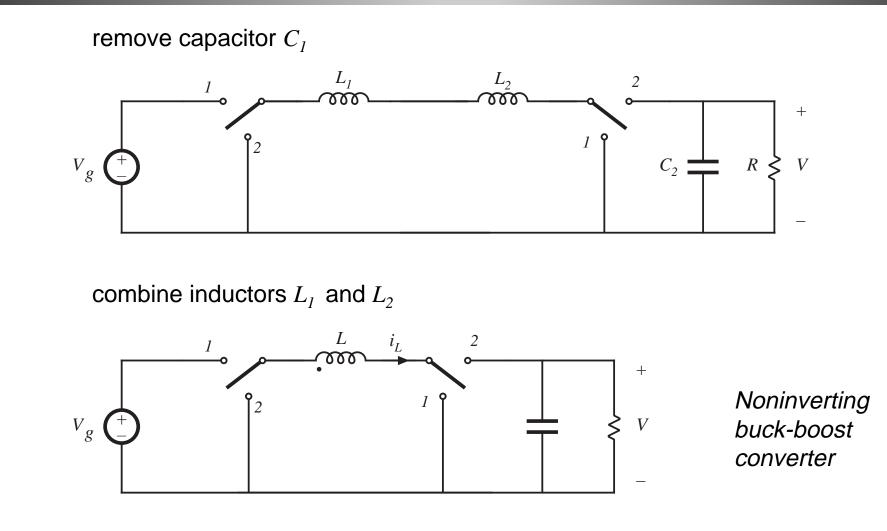
Buck cascaded by boost: simplification of internal filter




Noninverting buck-boost converter

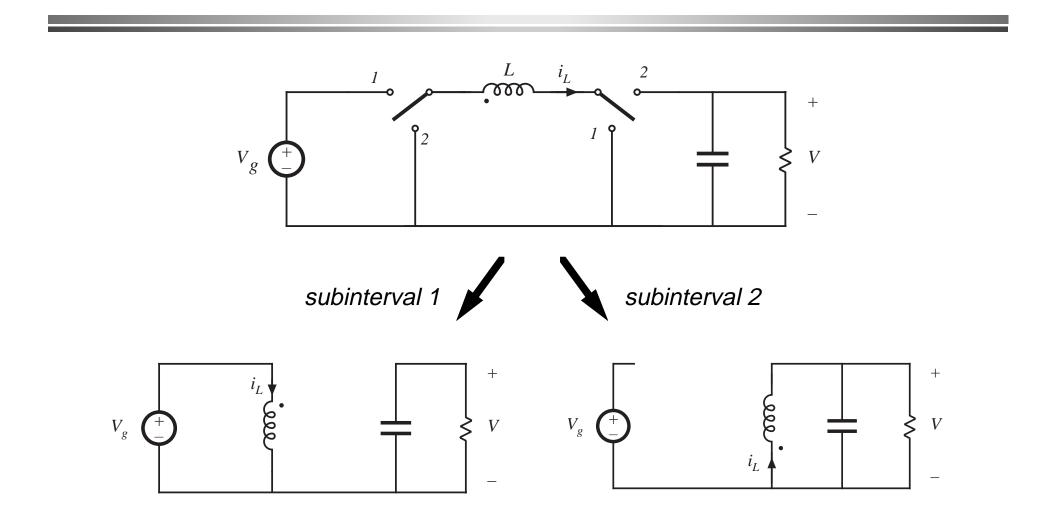

Reversal of output voltage polarity

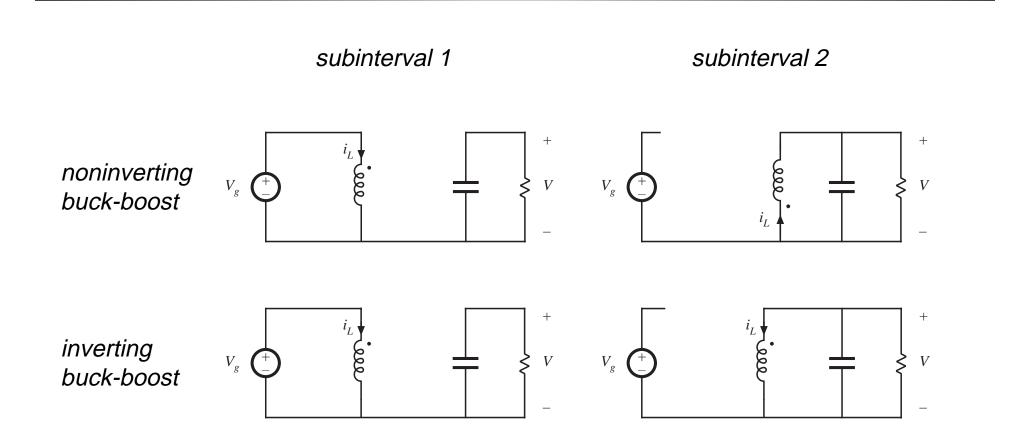

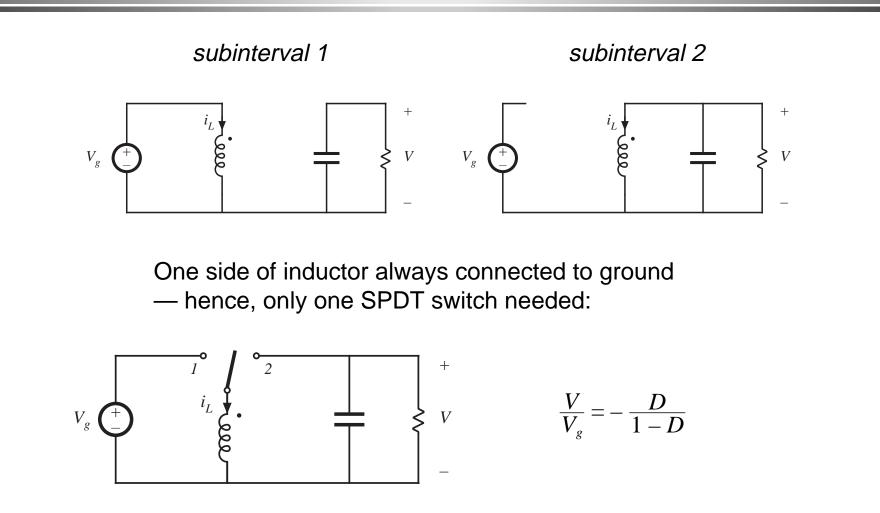
Reduction of number of switches: inverting buck-boost



Discussion: cascade connections

- Properties of buck-boost converter follow from its derivation as buck cascaded by boost
 - Equivalent circuit model: buck 1:*D* transformer cascaded by boost *D*':1 transformer
 - Pulsating input current of buck converter
 - Pulsating output current of boost converter
- Other cascade connections are possible
 - Cuk converter: boost cascaded by buck


6.1.3. Rotation of three-terminal cell

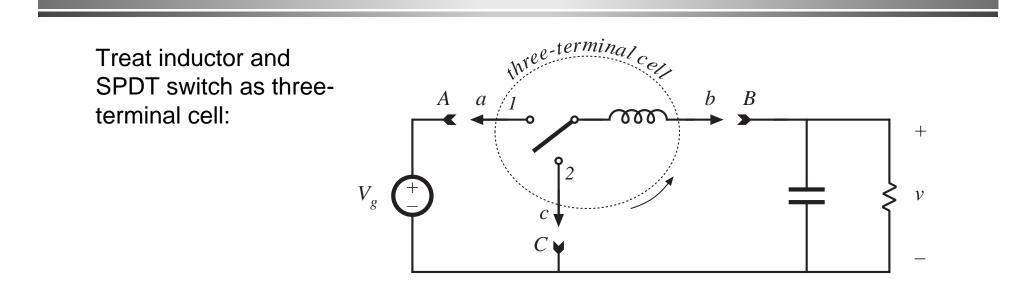

Three-terminal cell can be connected between source and load in three nontrivial distinct ways:

a-A b-B c-C	buck converter
a-C b-A c-B	boost converter
a-A b-C c-B	buck-boost converter

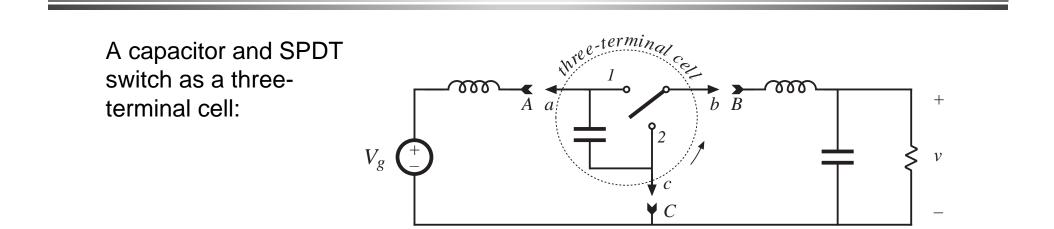
Rotation of a dual three-terminal network




Three-terminal cell can be connected between source and load in three nontrivial distinct ways:

a-A b-B c-C	buck converter with L-C input filter
a-C b-A c-B	boost converter with L-C output filter
a-A b-C c-B	Cuk converter

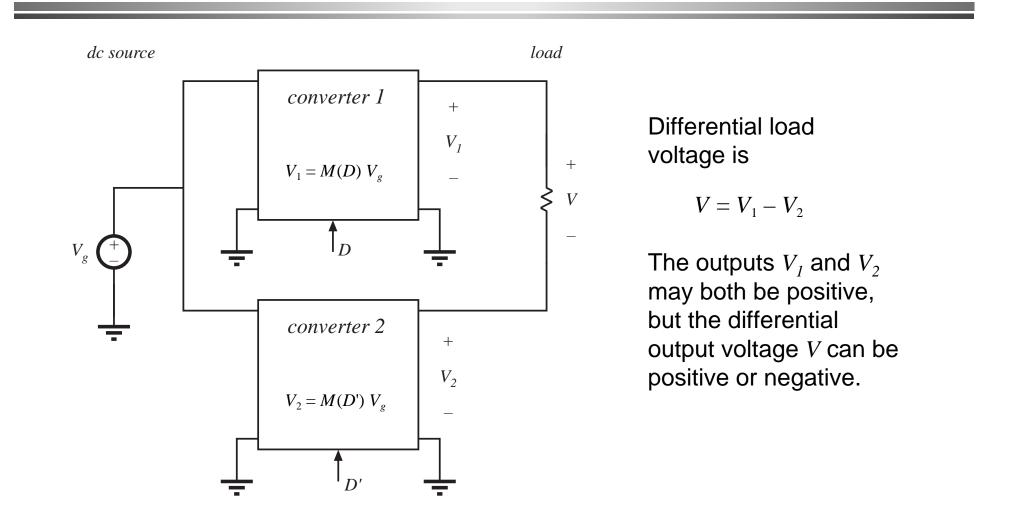6.1.4. Differential connection of load to obtain bipolar output voltage



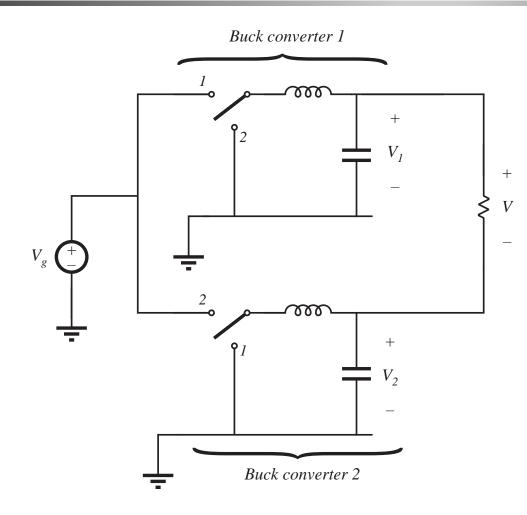Differential connection using two buck converters



Converter #1 transistor driven with duty cycle D

Converter #2 transistor driven with duty cycle

complement D'

Differential load voltage is

$$V = DV_g - D'V_g$$


Simplify:

$$V = (2D - 1) V_g$$


Conversion ratio *M*(*D*), differentially-connected buck converters

 $V = (2D - 1) V_g$ M(D)0 0.5 1 D _ 1

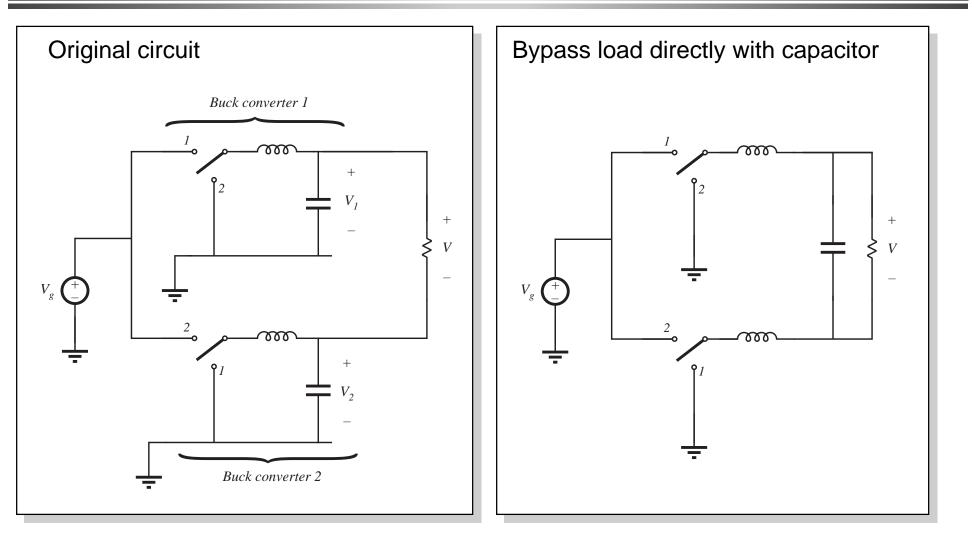
Simplification of filter circuit, differentially-connected buck converters



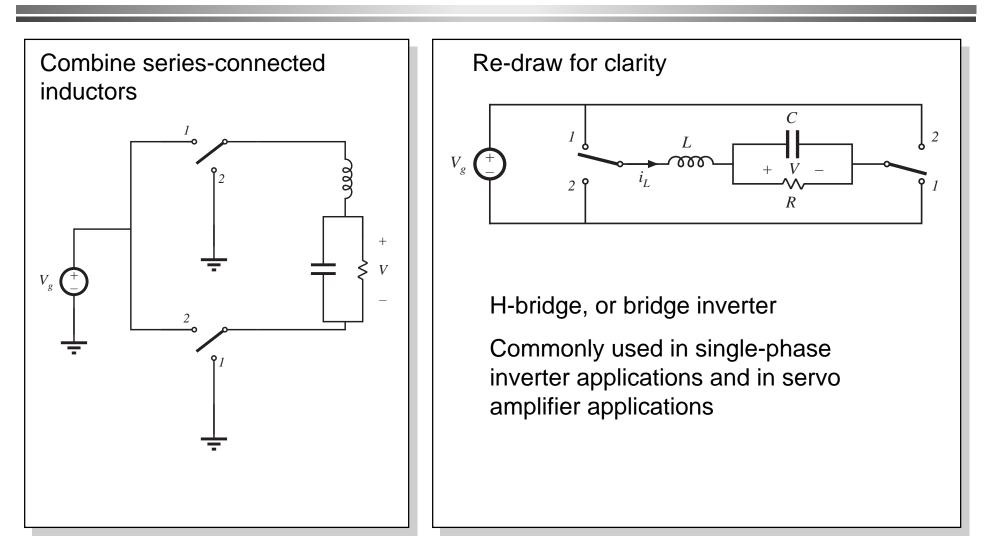Simplification of filter circuit, differentially-connected buck converters



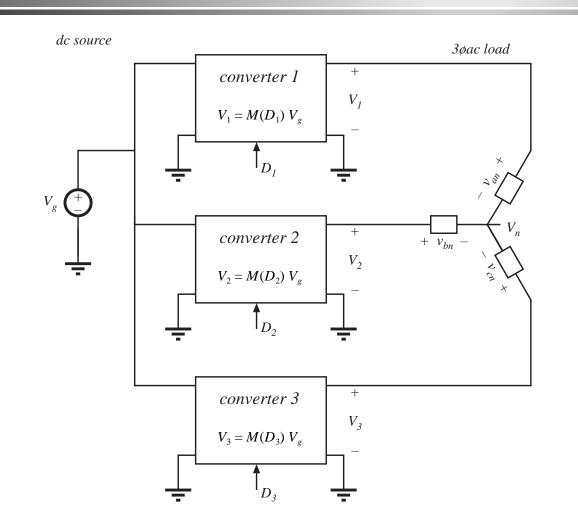Differential connection to obtain 3ø inverter



With balanced 3ø load, neutral voltage is


$$V_n = \frac{1}{3} (V_1 + V_2 + V_3)$$

Phase voltages are

$$V_{an} = V_1 - V_n$$
$$V_{bn} = V_2 - V_n$$
$$V_{cn} = V_3 - V_n$$

Control converters such that their output voltages contain the same dc biases. This dc bias will appear at the neutral point Vn. It then cancels out, so phase voltages contain no dc bias.

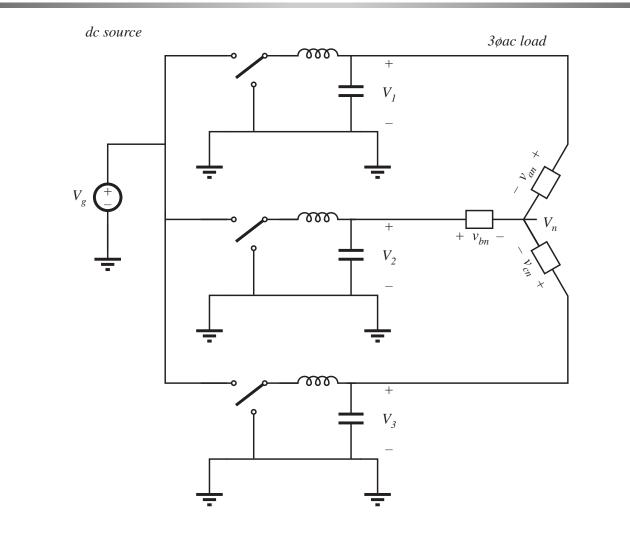3ø differential connection of three buck converters



3ø differential connection of three buck converters

Re-draw for clarity: $dc \ source$ $3ac \ load$ $v_g + v_g + v_{g} +$

"Voltage-source inverter" or buck-derived three-phase inverter

6.2. A short list of converters

An infinite number of converters are possible, which contain switches embedded in a network of inductors and capacitors

Two simple classes of converters are listed here:

- Single-input single-output converters containing a single inductor. The switching period is divided into two subintervals. This class contains eight converters.
- Single-input single-output converters containing two inductors. The switching period is divided into two subintervals. Several of the more interesting members of this class are listed.


Single-input single-output converters containing one inductor

- Use switches to connect inductor between source and load, in one manner during first subinterval and in another during second subinterval
- There are a limited number of ways to do this, so all possible combinations can be found
- After elimination of degenerate and redundant cases, eight converters are found:

dc-dc converters

	buck	boost	buck-boost	noninverting buck-boost	
dc-ac converters					
	bridge		Watkins-Johnson		
ac-dc converters					
	current-f	ed bridge	inver	se of Watkins-Johnson	

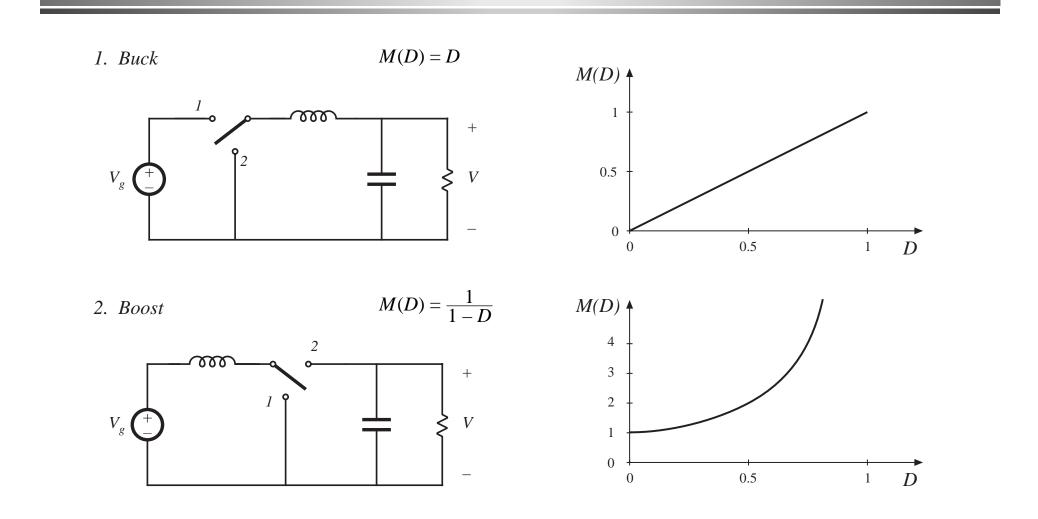
Converters producing a unipolar output voltage



Fundamentals of Power Electronics

Chapter 6: Converter circuits

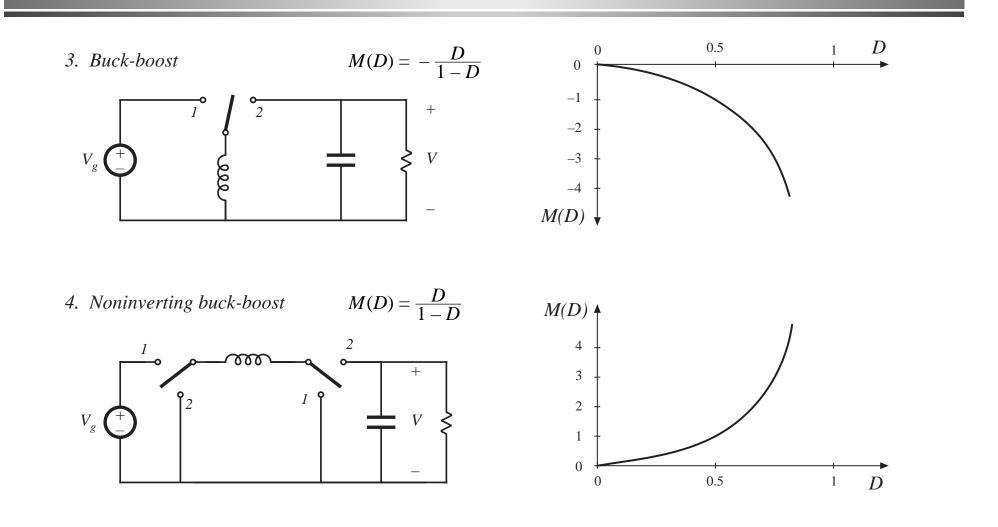
Converters producing a unipolar output voltage




Fundamentals of Power Electronics

Chapter 6: Converter circuits

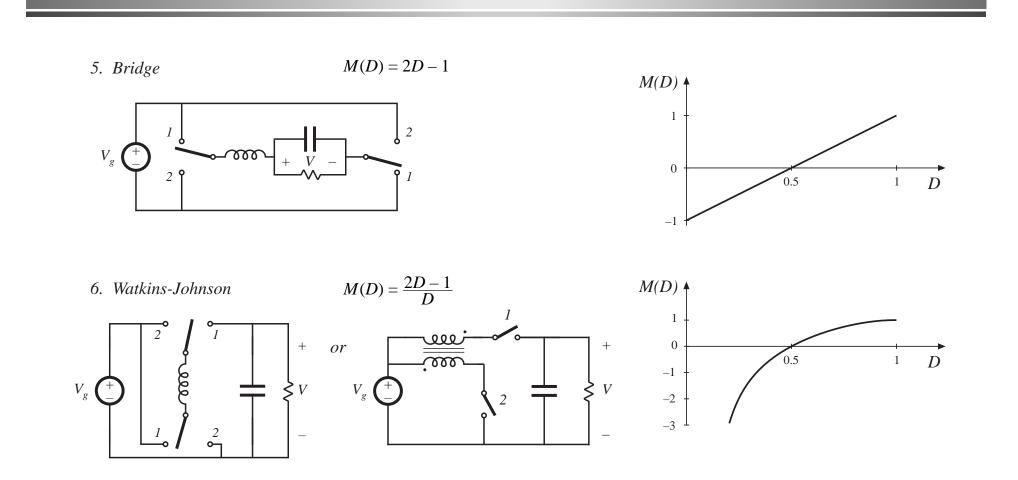
Converters producing a bipolar output voltage suitable as dc-ac inverters



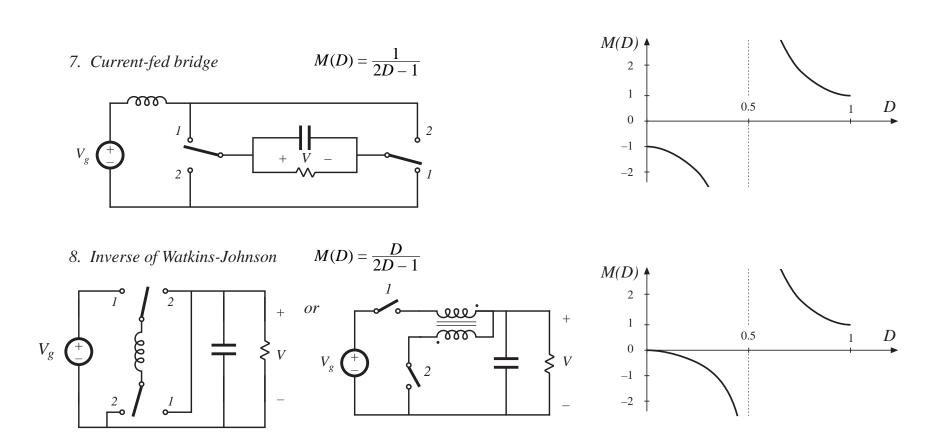Converters producing a bipolar output voltage suitable as ac-dc rectifiers



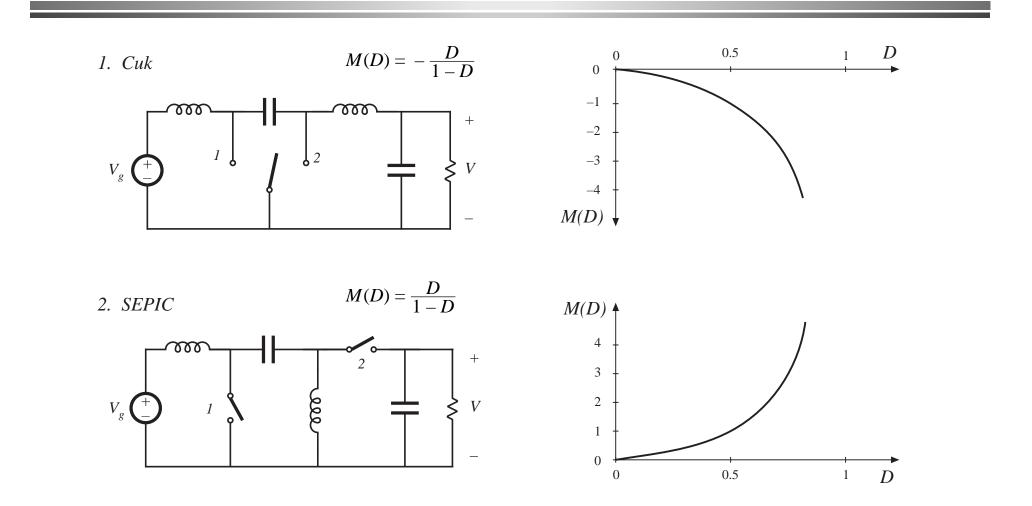
Several members of the class of two-inductor converters



Fundamentals of Power Electronics

Chapter 6: Converter circuits

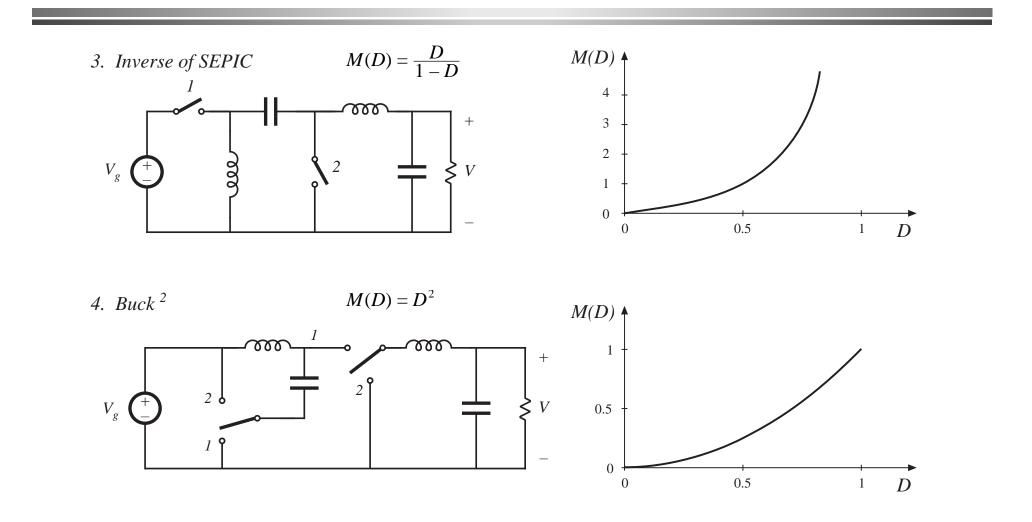Several members of the class of two-inductor converters



Fundamentals of Power Electronics


Chapter 6: Converter circuits

6.3. Transformer isolation

Objectives:


- Isolation of input and output ground connections, to meet safety requirements
- Reduction of transformer size by incorporating high frequency isolation transformer inside converter
- Minimization of current and voltage stresses when a large step-up or step-down conversion ratio is needed use transformer turns ratio
- Obtain multiple output voltages via multiple transformer secondary windings and multiple converter secondary circuits

A simple transformer model

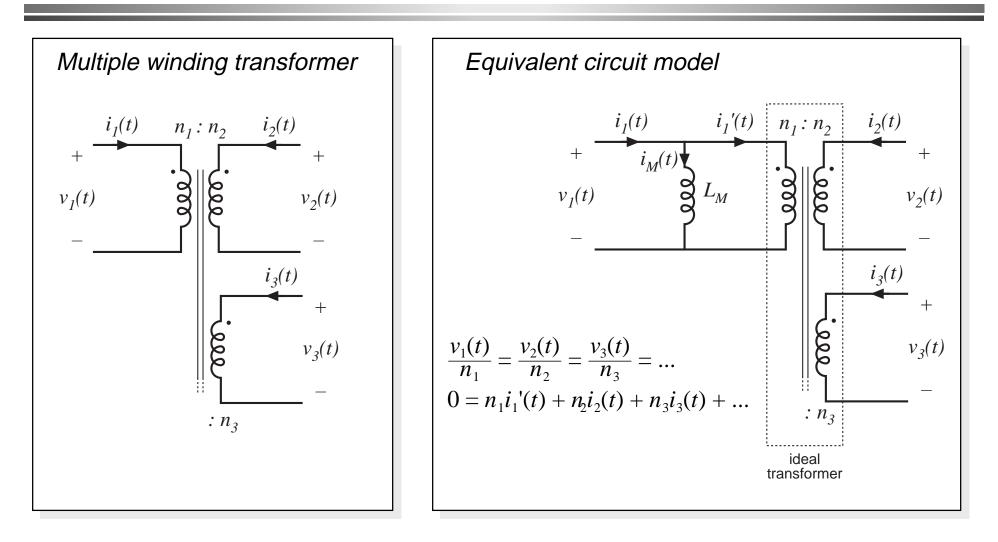

The magnetizing inductance L_M

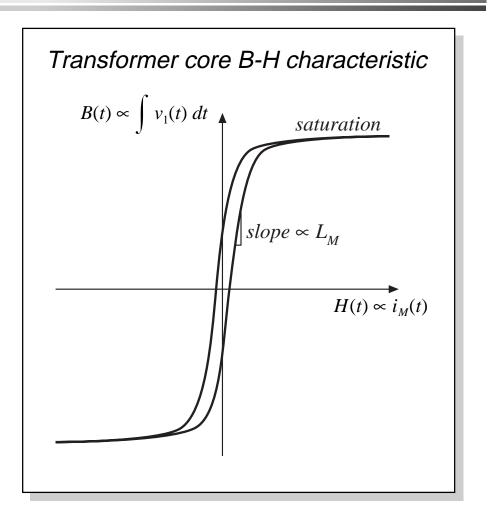- Models magnetization of transformer core material
- Appears effectively in parallel with windings
- If all secondary windings are disconnected, then primary winding behaves as an inductor, equal to the magnetizing inductance
- At dc: magnetizing inductance tends to short-circuit. Transformers cannot pass dc voltages
- Transformer saturates when magnetizing current i_M is too large



Volt-second balance in L_M

The magnetizing inductance is a real inductor, obeying


$$v_1(t) = L_M \frac{di_M(t)}{dt}$$

integrate:

$$i_M(t) - i_M(0) = \frac{1}{L_M} \int_0^t v_1(\tau) d\tau$$

Magnetizing current is determined by integral of the applied winding voltage. The magnetizing current and the winding currents are independent quantities. Volt-second balance applies: in steady-state, $i_M(T_s) = i_M(0)$, and hence
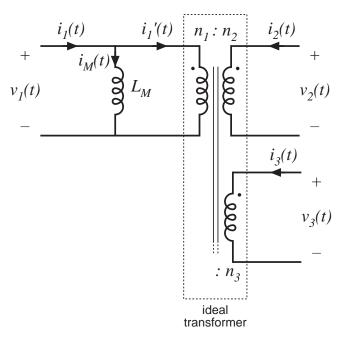
$$0=\frac{1}{T_s}\int_0^{T_s}v_1(t)\ dt$$




Transformer reset


- "Transformer reset" is the mechanism by which magnetizing inductance volt-second balance is obtained
- The need to reset the transformer volt-seconds to zero by the end of each switching period adds considerable complexity to converters
- To understand operation of transformer-isolated converters:
 - replace transformer by equivalent circuit model containing magnetizing inductance
 - analyze converter as usual, treating magnetizing inductance as any other inductor
 - apply volt-second balance to all converter inductors, including magnetizing inductance

6.3.1. Full-bridge and half-bridge isolated buck converters


Full-bridge isolated buck converter

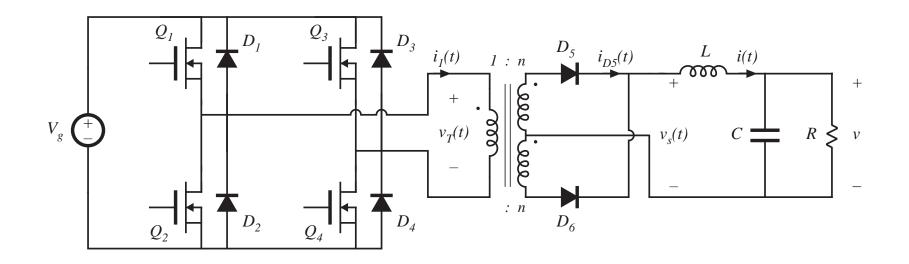

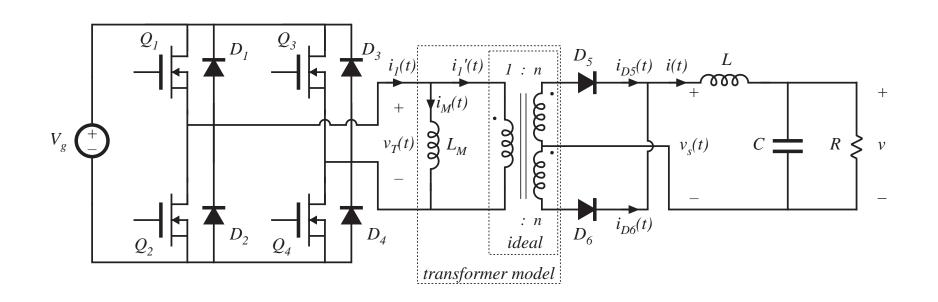Full-bridge, with transformer equivalent circuit



Full-bridge: waveforms

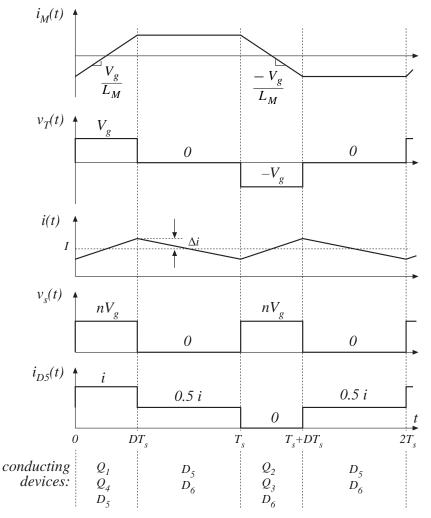

- During first switching period: transistors Q₁ and Q₄ conduct for time DT_s, applying voltseconds V_g DT_s to primary winding
- During next switching period: transistors Q₂ and Q₃ conduct for time DT_s, applying voltseconds -V_g DT_s to primary winding
- Transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities?

Effect of nonidealities on transformer volt-second balance

Volt-seconds applied to primary winding during first switching period:

 $(V_g - (Q_1 \text{ and } Q_4 \text{ forward voltage drops}))(Q_1 \text{ and } Q_4 \text{ conduction time})$

Volt-seconds applied to primary winding during next switching period:

 $-(V_g - (Q_2 \text{ and } Q_3 \text{ forward voltage drops}))(Q_2 \text{ and } Q_3 \text{ conduction time})$


These volt-seconds never add to *exactly* zero.

Net volt-seconds are applied to primary winding

Magnetizing current slowly increases in magnitude


Saturation can be prevented by placing a capacitor in series with primary, or by use of current programmed mode (chapter 11)

Operation of secondary-side diodes

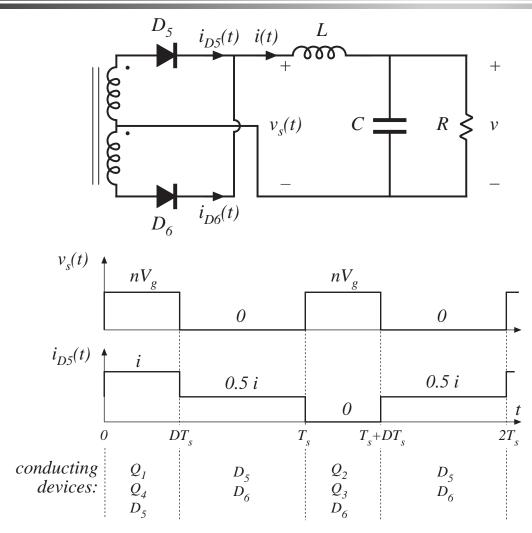

- During second (D') subinterval, both secondary-side diodes conduct
- Output filter inductor current divides approximately equally between diodes
- Secondary amp-turns add to approximately zero
- Essentially no net magnetization of transformer core by secondary winding currents

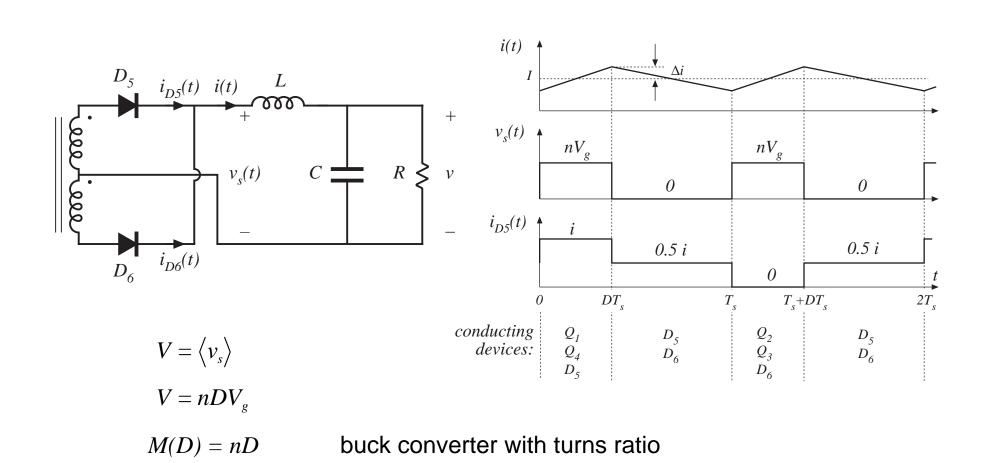
Volt-second balance on output filter inductor



Fundamentals of Power Electronics


41

Half-bridge isolated buck converter

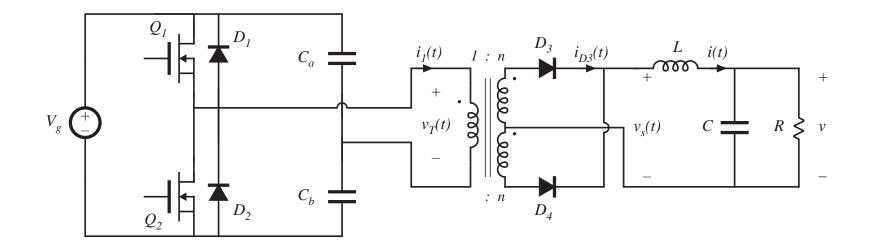


- Replace transistors Q_3 and Q_4 with large capacitors
- Voltage at capacitor centerpoint is $0.5V_g$
- $v_s(t)$ is reduced by a factor of two
- M = 0.5 nD

6.3.2. Forward converter

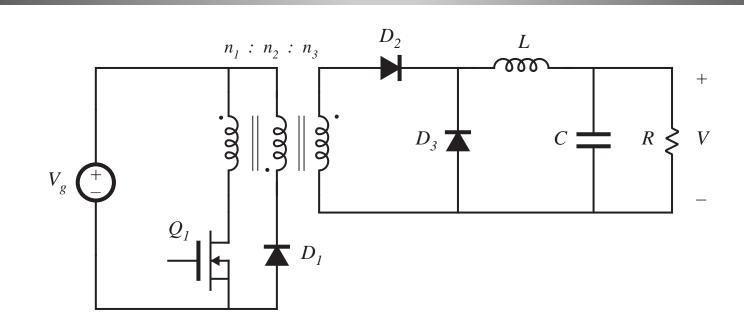


- Buck-derived transformer-isolated converter
- Single-transistor and two-transistor versions
- Maximum duty cycle is limited
- Transformer is reset while transistor is off

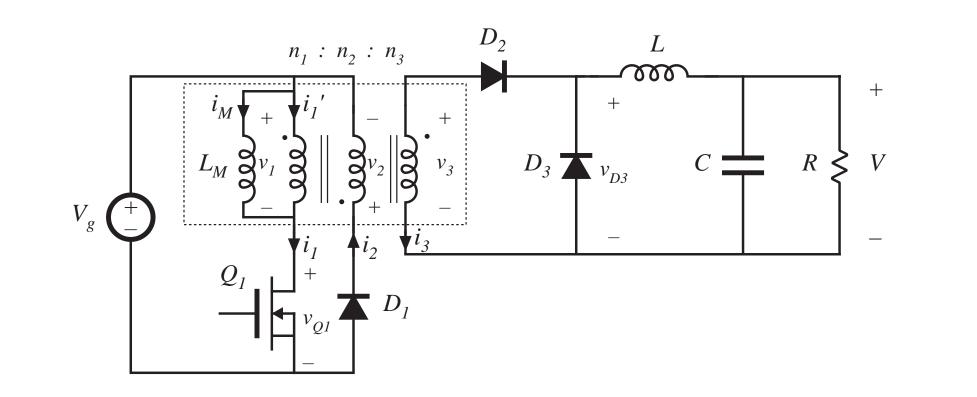Forward converter with transformer equivalent circuit




Forward converter: waveforms

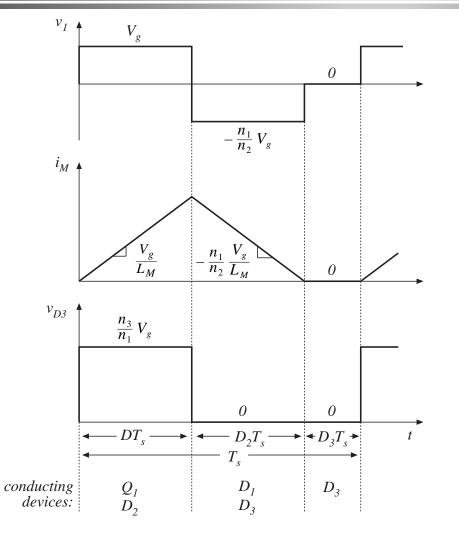


- Magnetizing current, in conjunction with diode D₁, operates in discontinuous conduction mode
- Output filter inductor, in conjunction with diode D₃, may operate in either CCM or DCM

Fundamentals of Power Electronics


Subinterval 1: transistor conducts

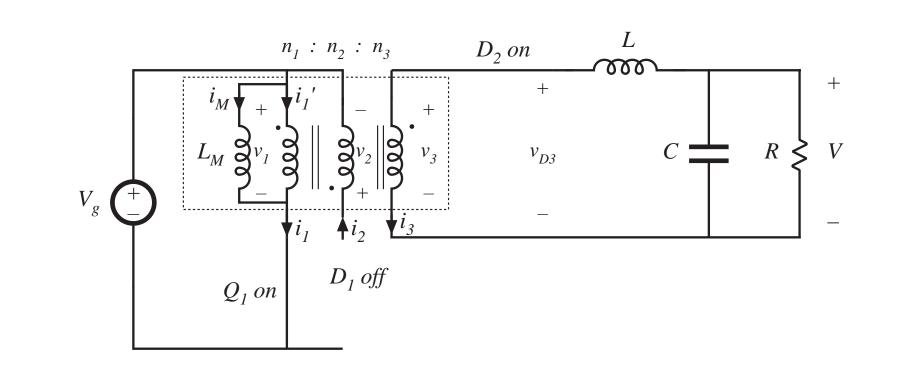


Subinterval 2: transformer reset

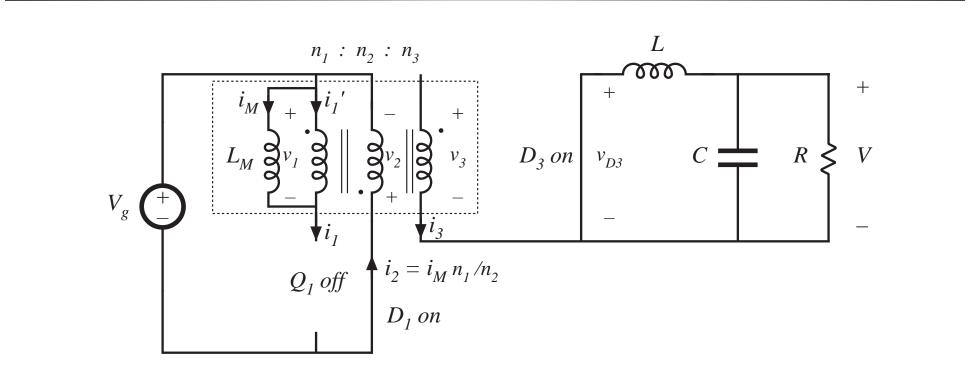

Subinterval 3

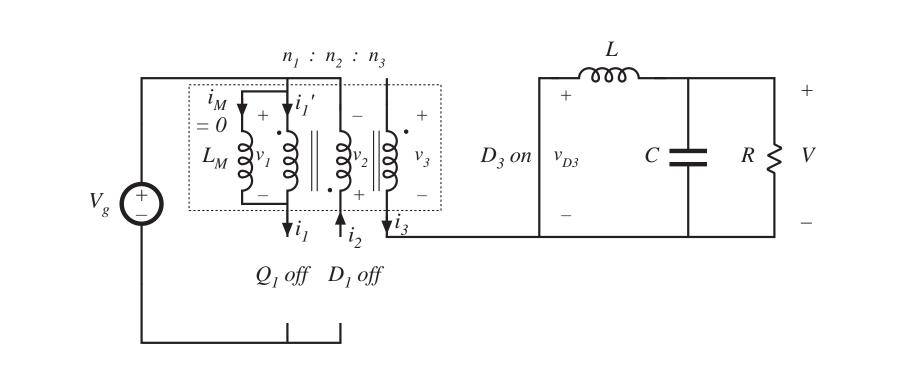

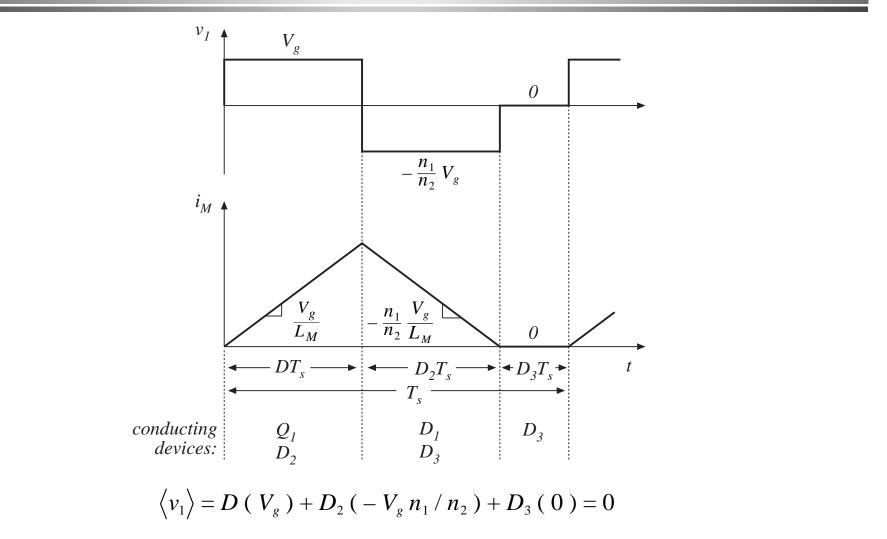Magnetizing inductance volt-second balance



Fundamentals of Power Electronics

Transformer reset

From magnetizing current volt-second balance:

$$\langle v_1 \rangle = D(V_g) + D_2(-V_g n_1 / n_2) + D_3(0) = 0$$

Solve for D_2 :

$$D_2 = \frac{n_2}{n_1} D$$

 D_3 cannot be negative. But $D_3 = 1 - D - D_2$. Hence


$$D_{3} = 1 - D - D_{2} \ge 0$$
$$D_{3} = 1 - D \left(1 + \frac{n_{2}}{n_{1}}\right) \ge 0$$

Solve for *D*

$$D \le \frac{1}{1 + \frac{n_2}{n_1}}$$
 for $n_1 = n_2$: $D \le \frac{1}{2}$


Fundamentals of Power Electronics

What happens when D > 0.5

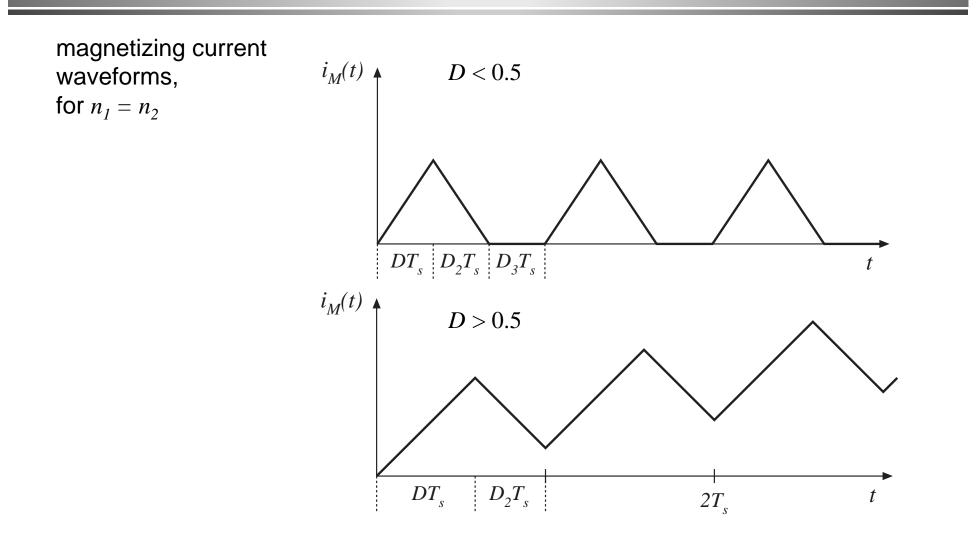

Fundamentals of Power Electronics

Conversion ratio *M*(*D*)

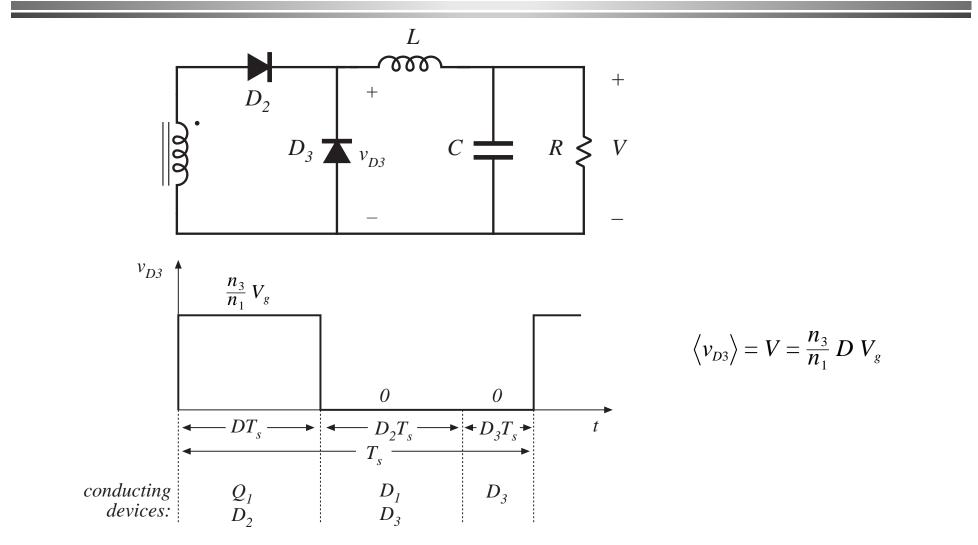

Fundamentals of Power Electronics

Maximum duty cycle vs. transistor voltage stress

Maximum duty cycle limited to

$$D \le \frac{1}{1 + \frac{n_2}{n_1}}$$

which can be increased by increasing the turns ratio n_2 / n_1 . But this increases the peak transistor voltage:


$$\max v_{Q1} = V_g \left(1 + \frac{n_1}{n_2} \right)$$

For
$$n_1 = n_2$$

 $D \le \frac{1}{2}$ and $\max v_{Q1} = 2V_g$

Fundamentals of Power Electronics


The two-transistor forward converter

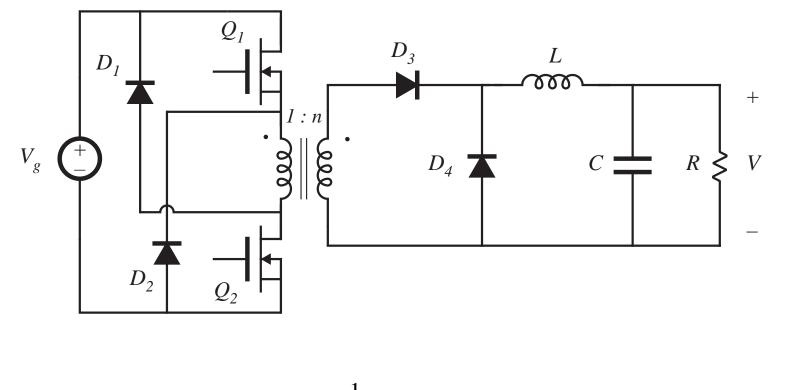

$$V = nDV_g \qquad D \le \frac{1}{2} \qquad \max v_{Q1} = \max v_{Q2} = V_g$$


Fundamentals of Power Electronics

6.3.3. Push-pull isolated buck converter

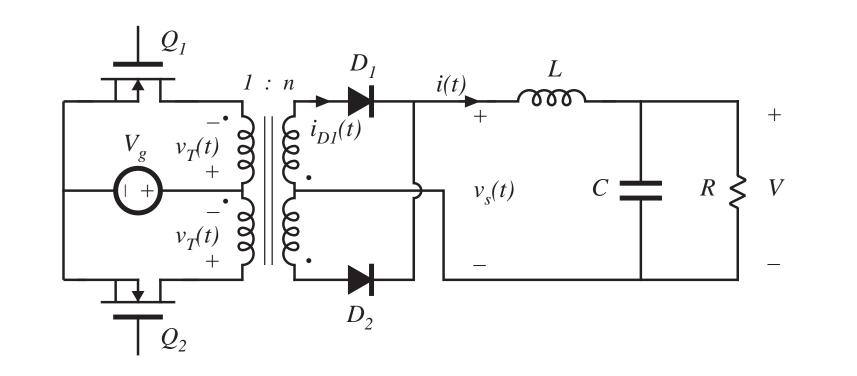

 $V = nDV_g \qquad \qquad 0 \le D \le 1$


Waveforms: push-pull

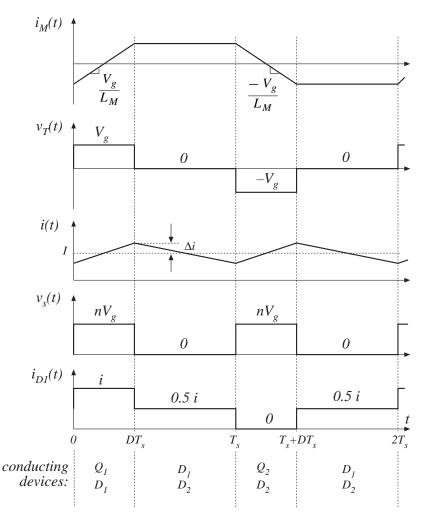


- Used with low-voltage inputs
- Secondary-side circuit identical to full bridge
- As in full bridge, transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities on transformer volt-second balance?
- Current programmed control can be used to mitigate transformer saturation problems. Duty cycle control not recommended.

Fundamentals of Power Electronics


6.3.4. Flyback converter

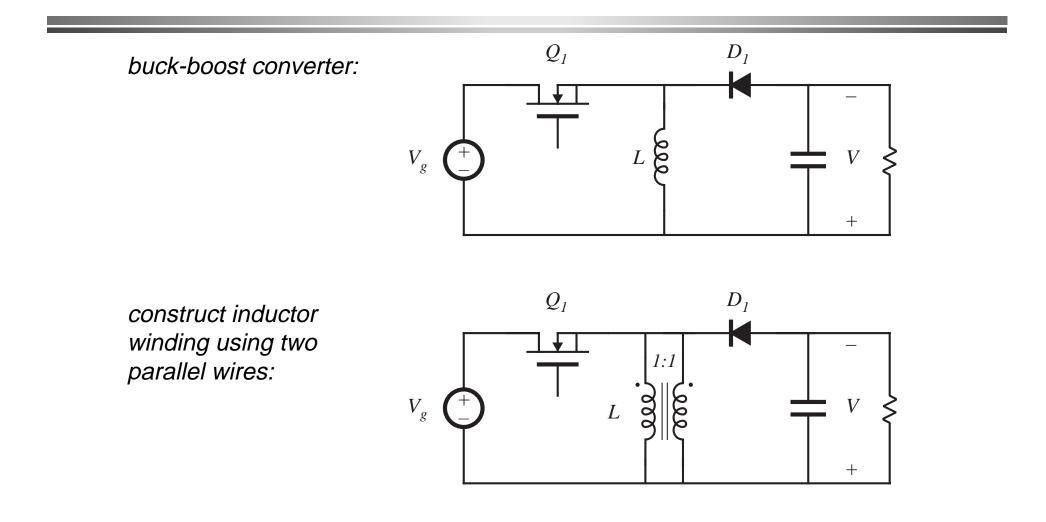

Derivation of flyback converter, cont.

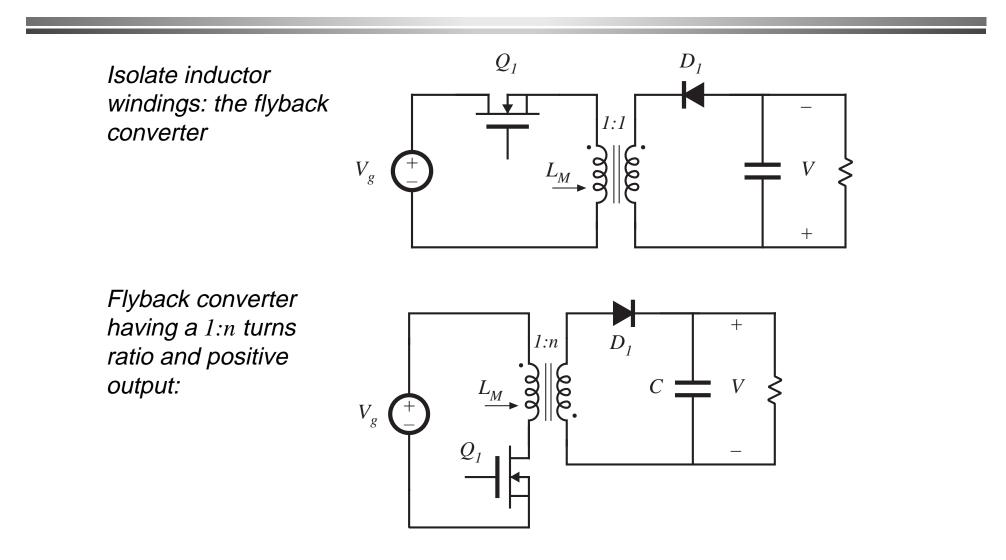


The "flyback transformer"

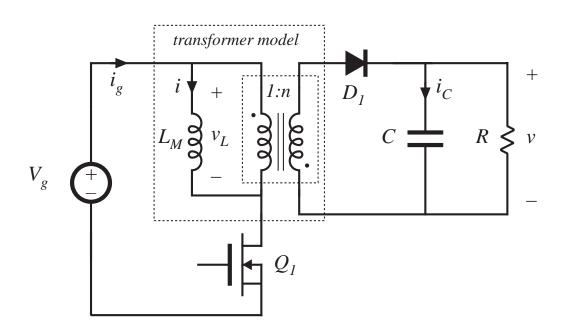

- A two-winding inductor
- Symbol is same as transformer, but function differs significantly from ideal transformer
- Energy is stored in magnetizing inductance
- Magnetizing inductance is relatively small
- Current does not simultaneously flow in primary and secondary windings
- Instantaneous winding voltages follow turns ratio
- Instantaneous (and rms) winding currents do not follow turns ratio
- Model as (small) magnetizing inductance in parallel with ideal transformer


Subinterval 1

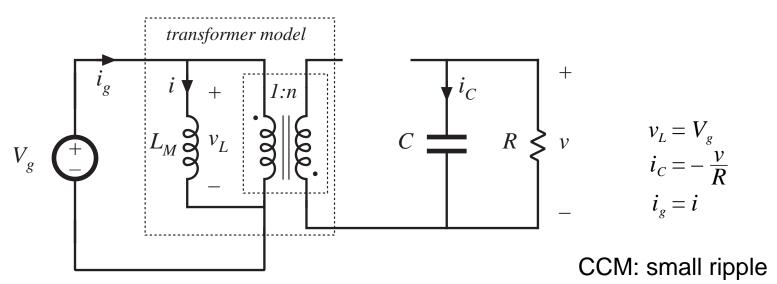

CCM: small ripple approximation leads to

$$v_L = V_g$$
$$i_C = -\frac{V}{R}$$
$$i_g = I$$


Subinterval 2

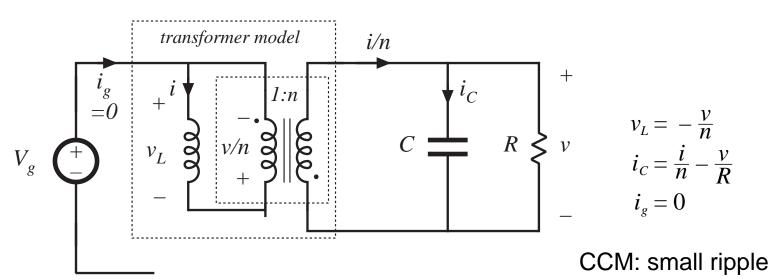

CCM: small ripple approximation leads to

$$v_L = -\frac{V}{n}$$
$$i_C = \frac{I}{n} - \frac{V}{R}$$
$$i_g = 0$$

CCM Flyback waveforms and solution

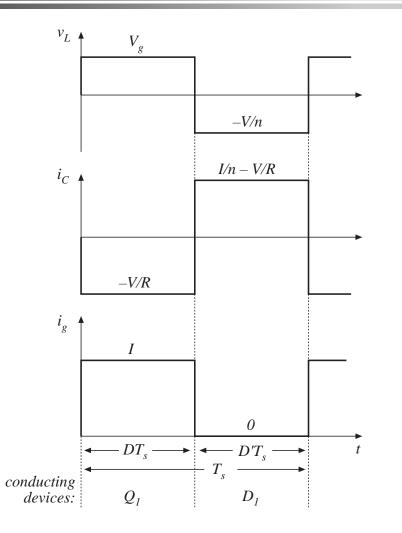

Volt-second balance:

$$\left\langle v_L \right\rangle = D\left(V_g\right) + D'\left(-\frac{V}{n}\right) = 0$$

Conversion ratio is

$$M(D) = \frac{V}{V_g} = n \frac{D}{D'}$$

Charge balance:

$$\left\langle i_{C}\right\rangle = D\left(-\frac{V}{R}\right) + D'\left(\frac{I}{n} - \frac{V}{R}\right) = 0$$

Dc component of magnetizing current is


$$I = \frac{nV}{D'R}$$

Dc component of source current is

$$I_{g} = \left\langle i_{g} \right\rangle = D \left(I \right) + D' \left(0 \right)$$

Fundamentals of Power Electronics

Equivalent circuit model: CCM Flyback

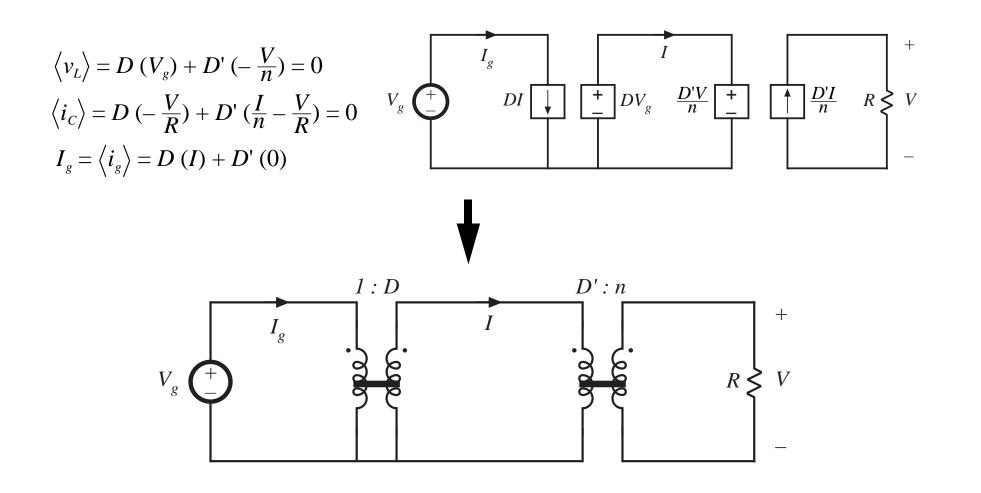

Discussion: Flyback converter


- Widely used in low power and/or high voltage applications
- Low parts count
- Multiple outputs are easily obtained, with minimum additional parts
- Cross regulation is inferior to buck-derived isolated converters
- Often operated in discontinuous conduction mode
- DCM analysis: DCM buck-boost with turns ratio

6.3.5. Boost-derived isolated converters

- A wide variety of boost-derived isolated dc-dc converters can be derived, by inversion of source and load of buck-derived isolated converters:
 - full-bridge and half-bridge isolated boost converters
 - inverse of forward converter: the "reverse" converter
 - push-pull boost-derived converter


Of these, the full-bridge and push-pull boost-derived isolated converters are the most popular, and are briefly discussed here.

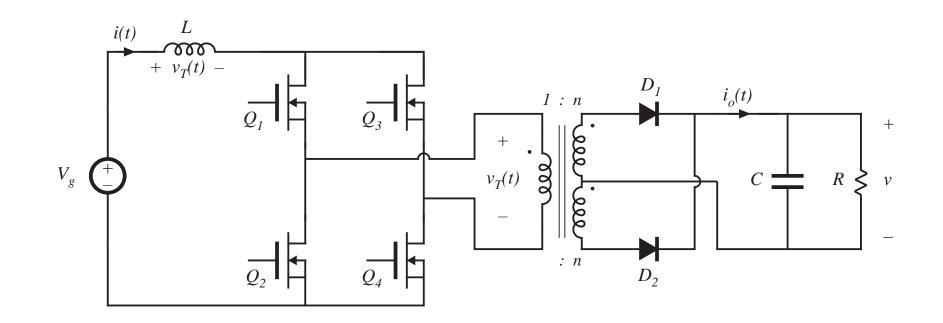Full-bridge transformer-isolated boost-derived converter




- Circuit topologies are equivalent to those of nonisolated boost converter
- With 1:1 turns ratio, inductor current i(t) and output current $i_o(t)$ waveforms are identical to nonisolated boost converter

Transformer reset mechanism

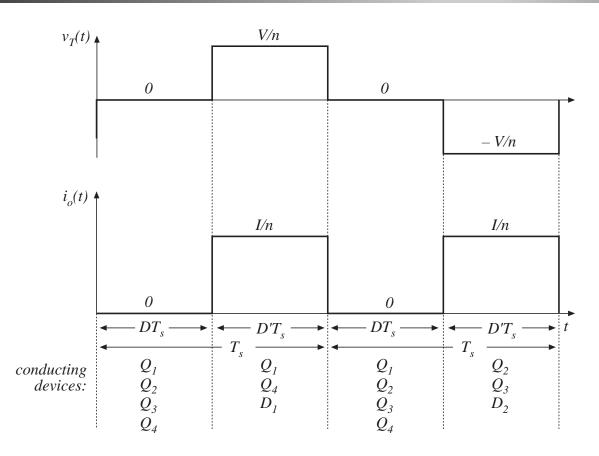

- As in full-bridge buck topology, transformer voltsecond balance is obtained over two switching periods.
- During first switching period: transistors Q₁ and Q₄ conduct for time DT_s, applying volt-seconds VDT_s to secondary winding.
- During next switching period: transistors Q₂ and Q₃ conduct for time DT_s, applying volt-seconds -VDT_s to secondary winding.

Conversion ratio *M*(*D*)

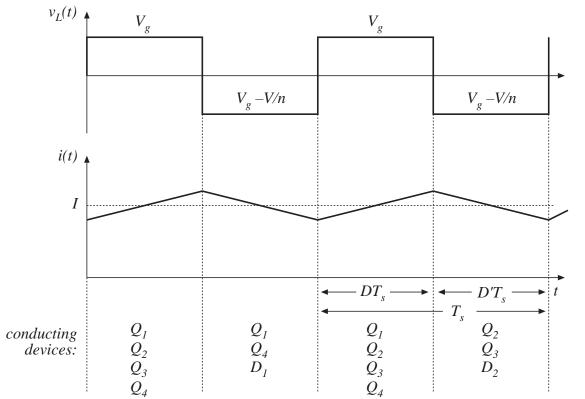

Application of volt-second balance to inductor voltage waveform:


$$\left\langle v_{L}\right\rangle = D\left(V_{g}\right) + D'\left(V_{g} - V / n\right) = 0$$

Solve for M(D):

$$M(D) = \frac{V}{V_g} = \frac{n}{D'}$$

-boost with turns ratio n


Push-pull boost-derived converter

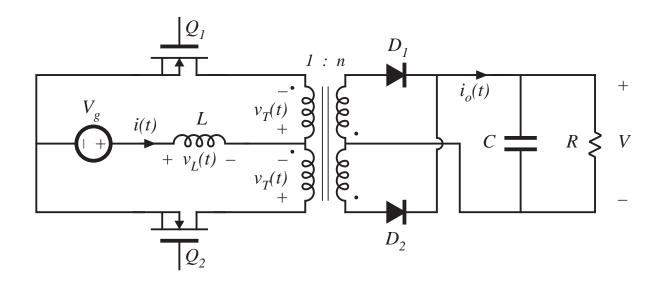


 $M(D) = \frac{V}{V_g} = \frac{n}{D'}$

Fundamentals of Power Electronics

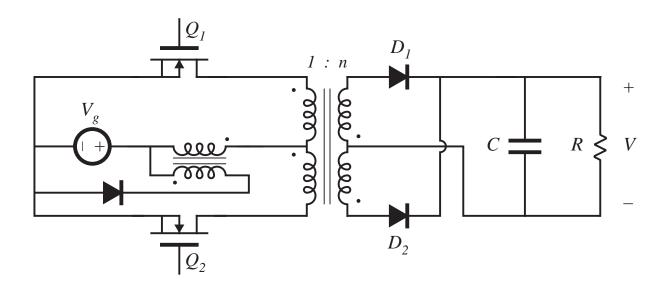
Push-pull converter based on Watkins-Johnson converter



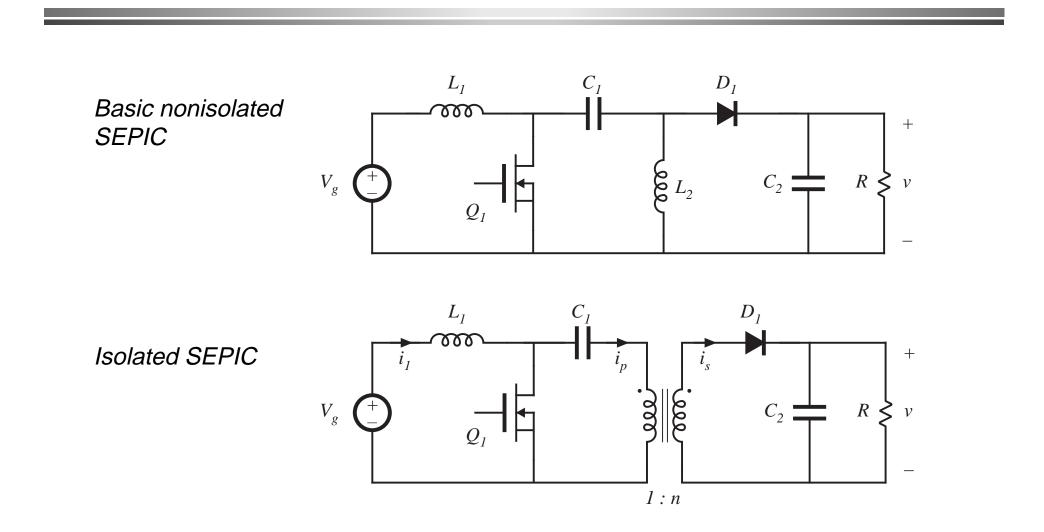6.3.6. Isolated versions of the SEPIC and Cuk converter




Isolated SEPIC

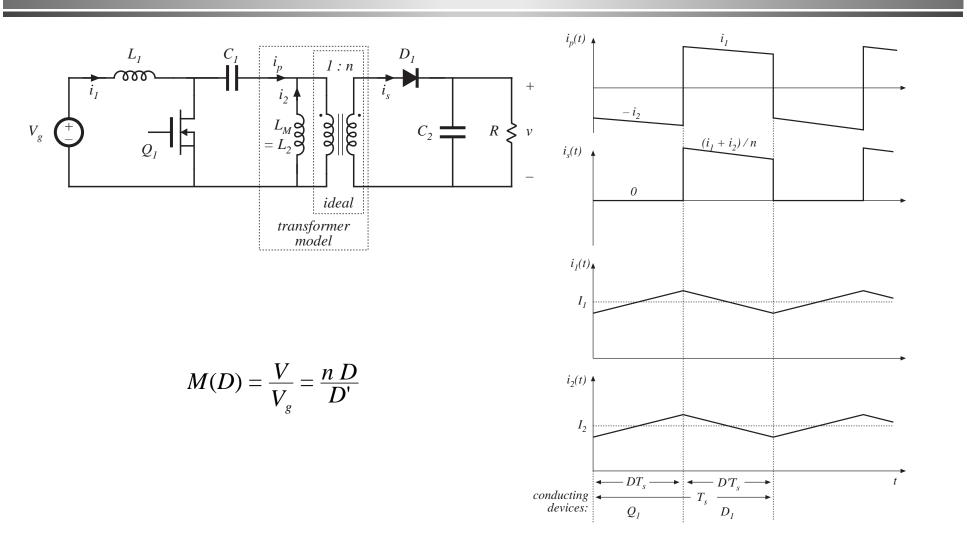


Fundamentals of Power Electronics

Inverse SEPIC

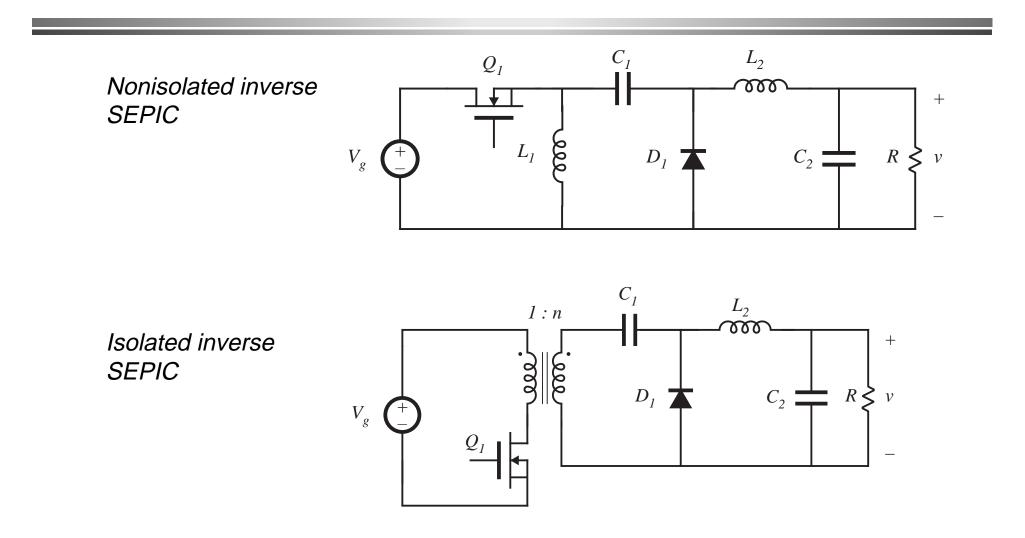


Obtaining isolation in the Cuk converter

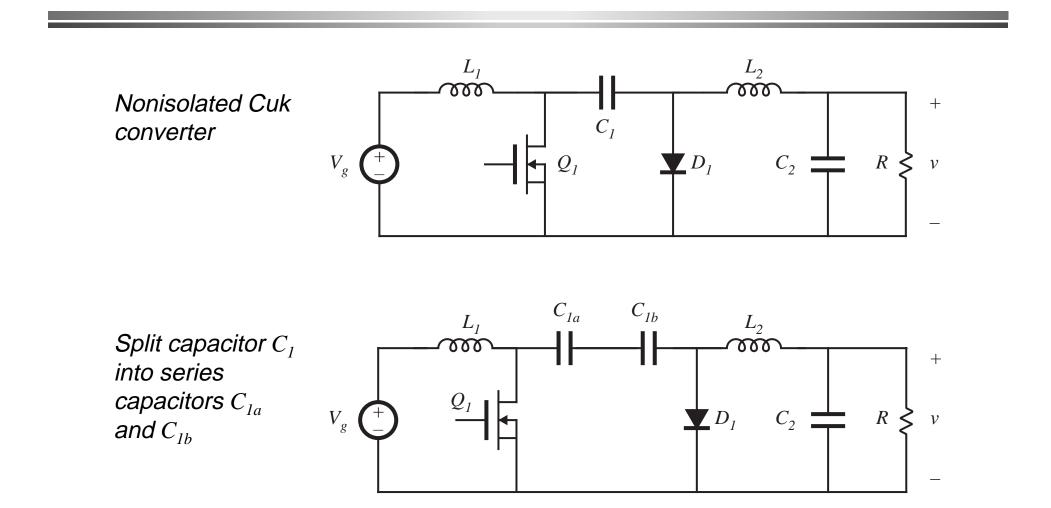

Fundamentals of Power Electronics

Isolated Cuk converter

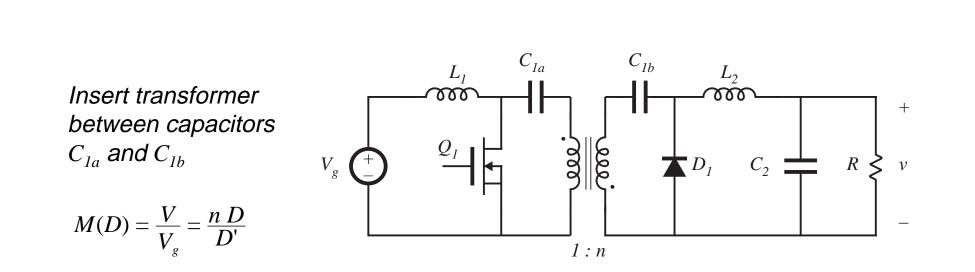

Discussion

- Capacitors C_{1a} and C_{1b} ensure that no dc voltage is applied to transformer primary or secondary windings
- Transformer functions in conventional manner, with small magnetizing current and negligible energy storage within the magnetizing inductance

6.4. Converter evaluation and design

For a given application, which converter topology is best?

There is no ultimate converter, perfectly suited for all possible applications

Trade studies

- Rough designs of several converter topologies to meet the given specifications
- An unbiased quantitative comparison of worst-case transistor currents and voltages, transformer size, etc.

Comparison via switch stress, switch utilization, and semiconductor cost

Spreadsheet design

6.4.1. Switch stress and switch utilization

- Largest single cost in a converter is usually the cost of the active semiconductor devices
- Conduction and switching losses associated with the active semiconductor devices often dominate the other sources of loss
- This suggests evaluating candidate converter approaches by comparing the voltage and current stresses imposed on the active semiconductor devices.
- Minimization of total switch stresses leads to reduced loss, and to minimization of the total silicon area required to realize the power devices of the converter.

Total active switch stress S

In a converter having k active semiconductor devices, the total active switch stress S is defined as

$$S = \sum_{j=1}^{k} V_j I_j$$

where

 V_j is the peak voltage applied to switch j,

 I_j is the rms current applied to switch j (peak current is also sometimes used).

In a good design, the total active switch stress is minimized.

Active switch utilization *U*

It is desired to minimize the total active switch stress, while maximizing the output power P_{load} .

The active switch utilization U is defined as

$$U = \frac{P_{load}}{S}$$

The active switch utilization is the converter output power obtained per unit of active switch stress. It is a converter figure-of-merit, which measures how well a converter utilizes its semiconductor devices.

Active switch utilization is less than 1 in transformer-isolated converters, and is a quantity to be maximized.

Converters having low switch utilizations require extra active silicon area, and operate with relatively low efficiency.

Active switch utilization is a function of converter operating point.

CCM flyback example: Determination of *S*

During subinterval 2, the transistor blocks voltage $V_{Q1,pk}$ equal to V_g plus the reflected load voltage:


$$V_{Q1,pk} = V_g + V / n = \frac{V_g}{D'}$$

Transistor current coincides with $i_g(t)$. RMS value is

$$I_{Q1,rms} = I \sqrt{D} = \frac{P_{load}}{V_g \sqrt{D}}$$

Switch stress *S* is
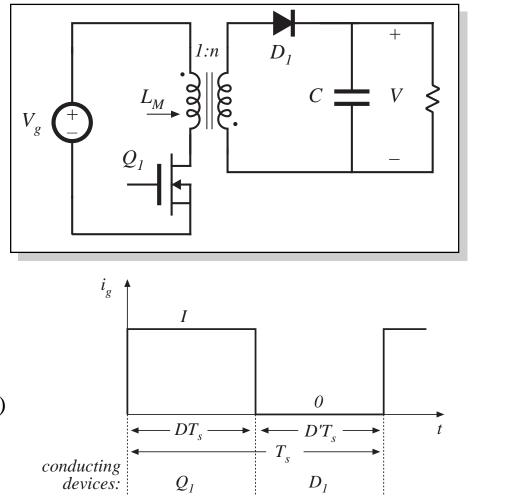
$$S = V_{Q1,pk} I_{Q1,rms} = (V_g + V / n) (I \sqrt{D})$$



Fundamentals of Power Electronics

Chapter 6: Converter circuits

CCM flyback example: Determination of *U*

Express load power P_{load} in terms of V and I:


$$P_{load} = D' V \frac{I}{n}$$


Previously-derived expression for *S*:

$$S = V_{Q1,pk} I_{Q1,rms} = (V_g + V / n) (I \sqrt{D})$$

Hence switch utilization U is

$$U = \frac{P_{load}}{S} = D' \sqrt{D}$$

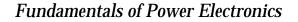

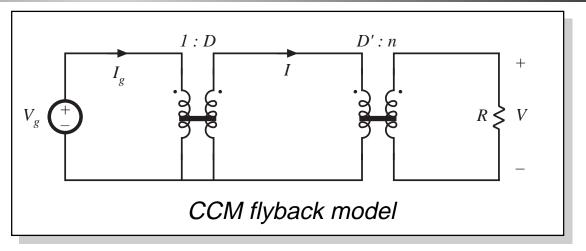

Flyback example: switch utilization *U*(*D*)


For given V, V_g , P_{load} , the designer can arbitrarily choose D. The turns ratio n must then be chosen according to

$$n = \frac{V}{V_g} \frac{D'}{D}$$

Single operating point design: choose D = 1/3.

small *D* leads to large transistor current

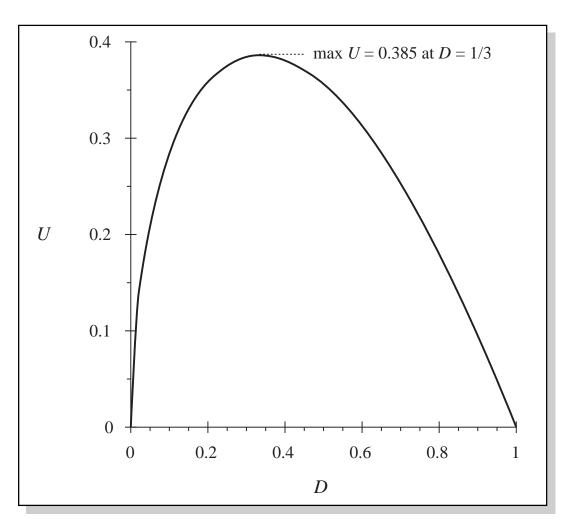large *D* leads to large transistor voltage



Comparison of switch utilizations of some common converters

Converter	U(D)	$\max U(D)$	$\max U(D)$ occurs at D =
Buck	\sqrt{D}	1	1
Boost	$rac{D'}{\sqrt{D}}$	∞	0
Buck-boost, flyback, nonisolated SEPIC, isolated SEPIC, nonisolated Cuk, isolated Cuk	$D'\sqrt{D}$	$\frac{2}{3\sqrt{3}} = 0.385$	$\frac{1}{3}$
Forward, $n_1 = n_2$	$\frac{1}{2}\sqrt{D}$	$\frac{1}{2\sqrt{2}} = 0.353$	$\frac{1}{2}$
Other isolated buck-derived converters (full- bridge, half-bridge, push-pull)	$\frac{\sqrt{D}}{2\sqrt{2}}$	$\frac{1}{2\sqrt{2}} = 0.353$	1
Isolated boost-derived converters (full bridge, push-pull)	$\frac{D'}{2\sqrt{1+D}}$	$\frac{1}{2}$	0

Table 6.1. Active switch utilizations of some common dc-dc converters, single operating point.

Switch utilization : Discussion

- Increasing the range of operating points leads to reduced switch utilization
- Buck converter

can operate with high switch utilization (U approaching 1) when D is close to 1

Boost converter

can operate with high switch utilization (U approaching ∞) when D is close to 1

- Transformer isolation leads to reduced switch utilization
- Buck-derived transformer-isolated converters
 - $U \leq 0.353$

should be designed to operate with *D* as large as other considerations allow

transformer turns ratio can be chosen to optimize design

Switch utilization: Discussion

 Nonisolated and isolated versions of buck-boost, SEPIC, and Cuk converters


 $U \leq 0.385$

Single-operating-point optimum occurs at D = 1/3

Nonisolated converters have lower switch utilizations than buck or boost

Isolation can be obtained without penalizing switch utilization

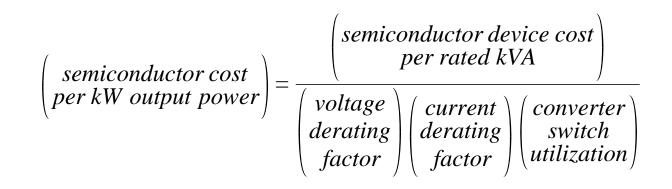Active semiconductor cost vs. switch utilization



(semiconductor device cost per rated kVA) = cost of device, divided by product of rated blocking voltage and rms current, in \$/kVA. Typical values are less than \$1/kVA

(voltage derating factor) and (current derating factor) are required to obtain reliable operation. Typical derating factors are 0.5 - 0.75

Typical cost of active semiconductor devices in an isolated dc-dc converter: \$1 - \$10 per kW of output power.

6.4.2. Converter design using computer spreadsheet

Given ranges of V_g and P_{load} , as well as desired value of V and other quantities such as switching frequency, ripple, etc., there are two basic engineering design tasks:

- Compare converter topologies and select the best for the given specifications
- Optimize the design of a given converter

A computer spreadsheet is a very useful tool for this job. The results of the steady-state converter analyses of chapters 1-6 can be entered, and detailed design investigations can be quickly performed:

- Evaluation of worst-case stresses over a range of operating points
- Evaluation of design tradeoffs

Spreadsheet design example


Specifications

maximum input voltage V_g	390V
minimum input voltage V_g	260V
output voltage V	15V
maximum load power P_{load}	200W
minimum load power P_{load}	20W
switching frequency f_s	100kHz
maximum output ripple Δv	0.1V


- Input voltage: rectified 230Vrms ±20%
- Regulated output of 15V
- Rated load power 200W
- Must operate at 10% load
- Select switching frequency of 100kHz
- Output voltage ripple $\leq 0.1V$

Compare single-transistor forward and flyback converters in this application Specifications are entered at top of spreadsheet

Forward converter design, CCM

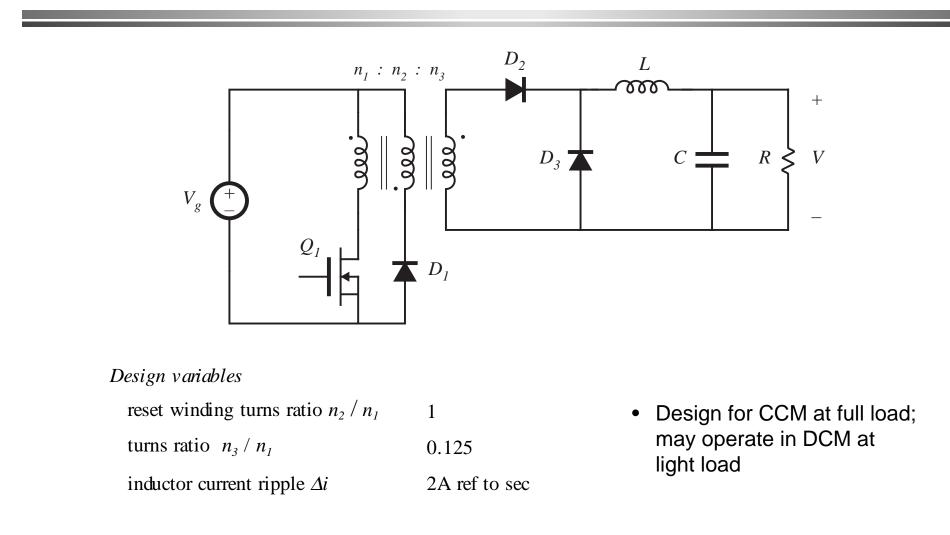

Flyback converter design, CCM

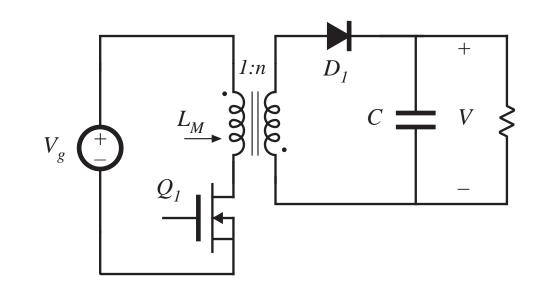

Design variables

turns ratio n_2 / n_1

inductor current ripple Δi

3A ref to sec

0.125

 Design for CCM at full load; may operate in DCM at light load

Enter results of converter analysis into spreadsheet (Forward converter example)

Maximum duty cycle occurs at minimum V_g and maximum P_{load} . Converter then operates in CCM, with

$$D = \frac{n_1}{n_3} \frac{V}{V_g}$$

Inductor current ripple is

$$\Delta i = \frac{D' V T_s}{2 L}$$

Solve for *L*:

$$L = \frac{D' V T_s}{2 \Delta i}$$

 Δi is a design variable. For a given Δi , the equation above can be used to determine *L*. To ensure CCM operation at full load, Δi should be less than the full-load output current. *C* can be found in a similar manner.

Fundamentals of Power Electronics

Forward converter example, continued

Check for DCM at light load. The solution of the buck converter operating in DCM is

$$V = \frac{n_3}{n_1} V_g \frac{2}{\sqrt{1 + 4K / D^2}}$$

with
$$K = 2 L / R T_s$$
, and $R = V^2 / P_{load}$

These equations apply equally well to the forward converter, provided that all quantities are referred to the transformer secondary side.

Solve for *D*:

$$D = \frac{2\sqrt{K}}{\sqrt{\left(\frac{2n_3V_g}{n_1V} - 1\right)^2 - 1}} \quad in DCM \qquad D = \frac{n_1}{n_3} \frac{V}{V_g} \quad in CCM$$

at a given operating point, the actual duty cycle is the small of the values calculated by the CCM and DCM equations above. Minimum D occurs at minimum P_{load} and maximum V_g .

Fundamentals of Power Electronics

More regarding forward converter example

Worst-case component stresses can now be evaluated.

Peak transistor voltage is

$$\max v_{Q1} = V_g \left(1 + \frac{n_1}{n_2} \right)$$

Rms transistor current is

$$I_{Q1, rms} = \frac{n_3}{n_1} \sqrt{D} \sqrt{I^2 + (\Delta i)^2 / 3} \approx \frac{n_3}{n_1} \sqrt{D} I$$

(this neglects transformer magnetizing current)

Other component stresses can be found in a similar manner. Magnetics design is left for a later chapter.

Results: forward and flyback converter spreadsheets

Forward converter design, CCM		Flyback converter design, CCM	
Design variables		Design variables	
reset winding turns ratio n_2 / n_1	1	turns ratio n_2 / n_1	0.125
turns ratio n_3 / n_1	0.125	inductor current ripple Δi	3A ref to sec
inductor current ripple Δi	2A ref to sec		
Results		Results	
maximum duty cycle D	0.462	maximum duty cycle D	0.316
minimum D, at full load	0.308	minimum <i>D</i> , at full load	0.235
minimum D, at minimum load	0.251	minimum D, at minimum load	0.179
Worst-case stresses		Worst-case stresses	
peak transistor voltage v_{Ql}	780V	peak transistor voltage v_{QI}	510V
rms transistor current i_{QI}	1.13A	rms transistor current i_{Ql}	1.38A
transistor utilization U	0.226	transistor utilization U	0.284
peak diode voltage v_{DI}	49V	peak diode voltage v_{DI}	64V
rms diode current i_{DI}	9.1A	rms diode current i_{DI}	16.3A
peak diode voltage v_{D2}	49V	peak diode current i_{Dl}	22.2A
rms diode current i_{D2}	11.1A		
rms output capacitor current i_C	1.15A	rms output capacitor current i_c	9.1A

Fundamentals of Power Electronics

Chapter 6: Converter circuits

Discussion: transistor voltage

Flyback converter

Ideal peak transistor voltage: 510V

Actual peak voltage will be higher, due to ringing causes by transformer leakage inductance

An 800V or 1000V MOSFET would have an adequate design margin

Forward converter

Ideal peak transistor voltage: 780V, 53% greater than flyback

MOSFETs having voltage rating greater than 1000V are not available (in 1995) —when ringing due to transformer leakage inductance is accounted for, this design will have an inadequate design margin

Fix: use two-transistor forward converter, or change reset winding turns ratio

A conclusion: reset mechanism of flyback is superior to forward

Fundamentals of Power Electronics

Discussion: rms transistor current

Forward

1.13A worst-case

transistor utilization 0.226

Flyback

1.38A worst case, 22% higher than forward

transistor utilization 0.284

CCM flyback exhibits higher peak and rms currents. Currents in DCM flyback are even higher

Discussion: secondary-side diode and capacitor stresses

Forward

peak diode voltage 49V

rms diode current 9.1A / 11.1A

rms capacitor current 1.15A

Flyback

peak diode voltage 64V

rms diode current 16.3A

peak diode current 22.2A

rms capacitor current 9.1A

Secondary-side currents, especially capacitor currents, limit the practical application of the flyback converter to situations where the load current is not too great.

Summary of key points

- The boost converter can be viewed as an inverse buck converter, while the buck-boost and Cuk converters arise from cascade connections of buck and boost converters. The properties of these converters are consistent with their origins. Ac outputs can be obtained by differential connection of the load. An infinite number of converters are possible, and several are listed in this chapter.
- 2. For understanding the operation of most converters containing transformers, the transformer can be modeled as a magnetizing inductance in parallel with an ideal transformer. The magnetizing inductance must obey all of the usual rules for inductors, including the principle of volt-second balance.

Summary of key points

- 3. The steady-state behavior of transformer-isolated converters may be understood by first replacing the transformer with the magnetizing-inductance-plus-ideal-transformer equivalent circuit. The techniques developed in the previous chapters can then be applied, including use of inductor volt-second balance and capacitor charge balance to find dc currents and voltages, use of equivalent circuits to model losses and efficiency, and analysis of the discontinuous conduction mode.
- 4. In the full-bridge, half-bridge, and push-pull isolated versions of the buck and/or boost converters, the transformer frequency is twice the output ripple frequency. The transformer is reset while it transfers energy: the applied voltage polarity alternates on successive switching periods.

Summary of key points

- 5. In the conventional forward converter, the transformer is reset while the transistor is off. The transformer magnetizing inductance operates in the discontinuous conduction mode, and the maximum duty cycle is limited.
- 6. The flyback converter is based on the buck-boost converter. The flyback transformer is actually a two-winding inductor, which stores and transfers energy.
- 7. The transformer turns ratio is an extra degree-of-freedom which the designer can choose to optimize the converter design. Use of a computer spreadsheet is an effective way to determine how the choice of turns ratio affects the component voltage and current stresses.
- 8. Total active switch stress, and active switch utilization, are two simplified figures-of-merit which can be used to compare the various converter circuits.

Part II Converter Dynamics and Control

- 7. AC equivalent circuit modeling
- 8. Converter transfer functions
- 9. Controller design
- 10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
- 11. Current programmed control

Chapter 7. AC Equivalent Circuit Modeling

- 7.1. Introduction
- 7.2. The basic ac modeling approach
- 7.3. Example: A nonideal flyback converter
- 7.4. State-space averaging
- 7.5. Circuit averaging and averaged switch modeling
- 7.6. The canonical circuit model
- 7.7. Modeling the pulse-width modulator
- 7.8. Summary of key points

7.1. Introduction

3

Objective: maintain v(t)equal to an accurate, constant value V.


There are disturbances:

- in $v_g(t)$
- in *R*

There are uncertainties:

- in element values
- in V_g
- in *R*

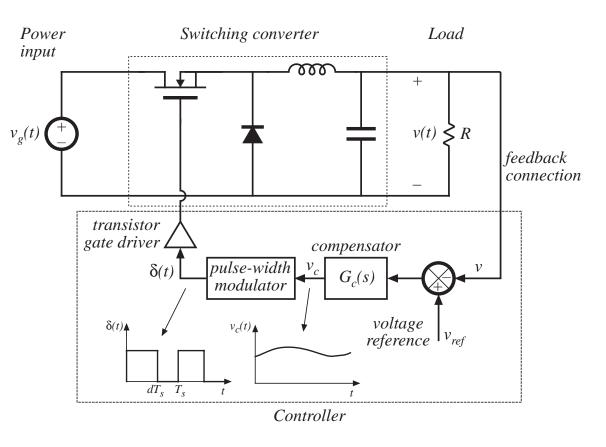A simple dc-dc regulator system, employing a buck converter



Fundamentals of Power Electronics

Applications of control in power electronics

Dc-dc converters

Regulate dc output voltage.

Control the duty cycle d(t) such that v(t) accurately follows a reference signal v_{ref} .

Dc-ac inverters

Regulate an ac output voltage.

Control the duty cycle d(t) such that v(t) accurately follows a reference signal $v_{ref}(t)$.

Ac-dc rectifiers

Regulate the dc output voltage.

Regulate the ac input current waveform.

Control the duty cycle d(t) such that $i_g(t)$ accurately follows a reference signal $i_{ref}(t)$, and v(t) accurately follows a reference signal v_{ref} .

Fundamentals of Power Electronics

Chapter 7: AC equivalent circuit modeling

Objective of Part II

Develop tools for modeling, analysis, and design of converter control systems

Need dynamic models of converters:

How do ac variations in $v_g(t)$, *R*, or d(t) affect the output voltage v(t)?

What are the small-signal transfer functions of the converter?

- Extend the steady-state converter models of Chapters 2 and 3, to include CCM converter dynamics (Chapter 7)
- Construct converter small-signal transfer functions (Chapter 8)
- Design converter control systems (Chapter 9)
- Model converters operating in DCM (Chapter 10)
- Current-programmed control of converters (Chapter 11)

Modeling


- Representation of physical behavior by mathematical means
- Model dominant behavior of system, ignore other insignificant phenomena
- Simplified model yields physical insight, allowing engineer to design system to operate in specified manner
- Approximations neglect small but complicating phenomena
- After basic insight has been gained, model can be refined (if it is judged worthwhile to expend the engineering effort to do so), to account for some of the previously neglected phenomena

Neglecting the switching ripple


Suppose the duty cycle is modulated sinusoidally:

 $d(t) = D + D_m \cos \omega_m t$

where D and D_m are constants, $|D_m| \ll D$, and the modulation frequency ω_m is much smaller than the converter switching frequency $\omega_s = 2\pi f_s$. The resulting variations in transistor gate drive signal and converter output voltage:

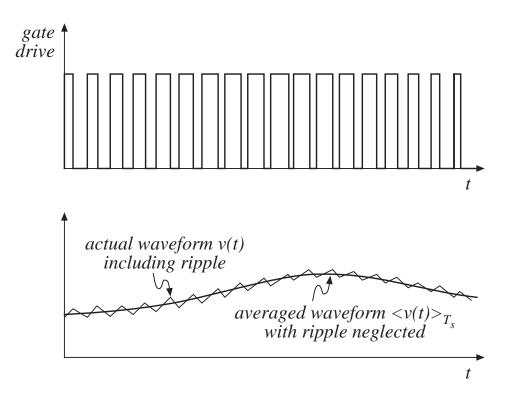

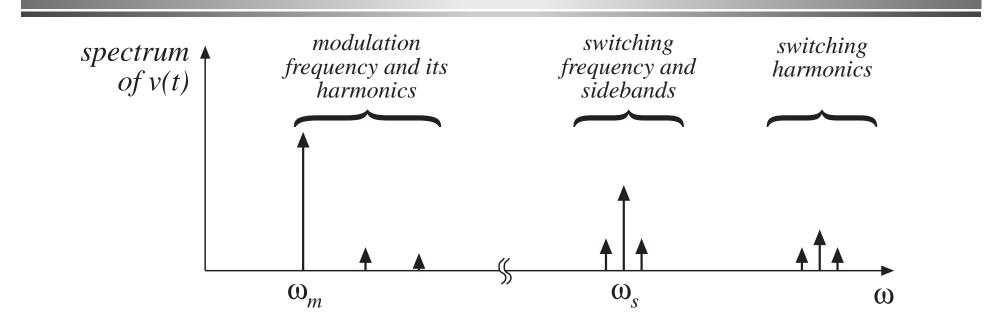Output voltage spectrum with sinusoidal modulation of duty cycle



Contains frequency components at:

- Modulation frequency and its harmonics
- Switching frequency and its harmonics
- Sidebands of switching frequency

With small switching ripple, highfrequency components (switching harmonics and sidebands) are small.

If ripple is neglected, then only lowfrequency components (modulation frequency and harmonics) remain.

Objective of ac converter modeling

- Predict how low-frequency variations in duty cycle induce lowfrequency variations in the converter voltages and currents
- Ignore the switching ripple
- Ignore complicated switching harmonics and sidebands

Approach:

Remove switching harmonics by averaging all waveforms over one switching period

Averaging to remove switching ripple

Average over one switching period to remove switching ripple:

$$L \frac{d\left\langle i_{L}(t)\right\rangle_{T_{s}}}{dt} = \left\langle v_{L}(t)\right\rangle_{T_{s}}$$
$$C \frac{d\left\langle v_{C}(t)\right\rangle_{T_{s}}}{dt} = \left\langle i_{C}(t)\right\rangle_{T_{s}}$$

where

$$\left\langle x_{L}(t)\right\rangle_{T_{s}}=\frac{1}{T_{s}}\int_{t}^{t+T_{s}}x(\tau) d\tau$$

Note that, in steady-state,

$$\left\langle v_L(t) \right\rangle_{T_s} = 0$$
$$\left\langle i_C(t) \right\rangle_{T_s} = 0$$

by inductor volt-second balance and capacitor charge balance.

Nonlinear averaged equations


The averaged voltages and currents are, in general, nonlinear functions of the converter duty cycle, voltages, and currents. Hence, the averaged equations

$$L \frac{d\left\langle i_{L}(t)\right\rangle_{T_{s}}}{dt} = \left\langle v_{L}(t)\right\rangle_{T_{s}}$$
$$C \frac{d\left\langle v_{C}(t)\right\rangle_{T_{s}}}{dt} = \left\langle i_{C}(t)\right\rangle_{T_{s}}$$


constitute a system of nonlinear differential equations.

Hence, must linearize by constructing a small-signal converter model.

Small-signal modeling of the BJT

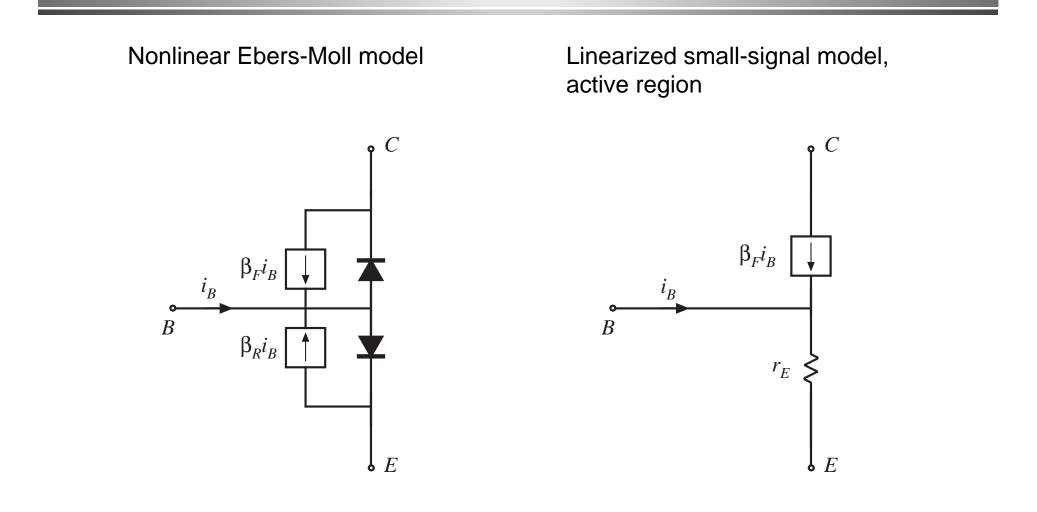


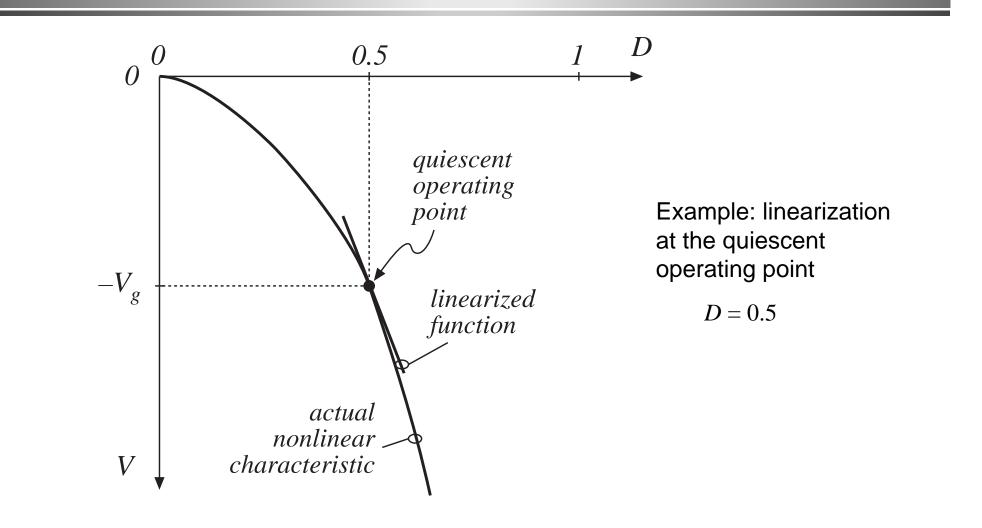Buck-boost converter: nonlinear static control-to-output characteristic



Result of averaged small-signal ac modeling


Small-signal ac equivalent circuit model

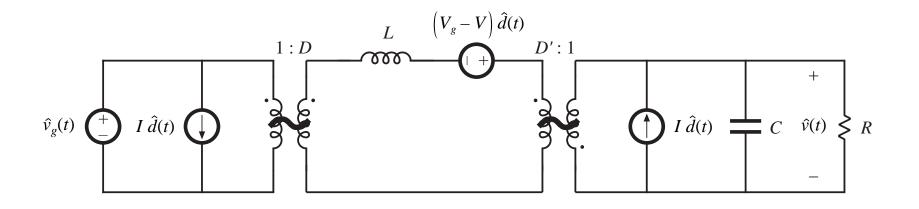

buck-boost example

7.2. The basic ac modeling approach

Buck-boost converter example

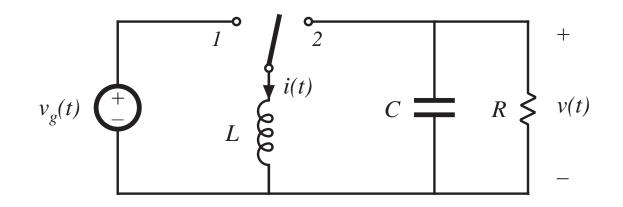


Switch in position 1

Inductor voltage and capacitor current are:

$$v_L(t) = L \frac{di(t)}{dt} = v_g(t)$$
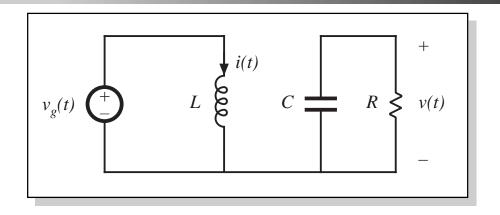
$$i_C(t) = C \frac{dv(t)}{dt} = -\frac{v(t)}{R}$$




Small ripple approximation: replace waveforms with their low-frequency averaged values:

$$v_L(t) = L \frac{di(t)}{dt} \approx \left\langle v_g(t) \right\rangle_{T_s}$$
$$i_C(t) = C \frac{dv(t)}{dt} \approx -\frac{\left\langle v(t) \right\rangle_{T_s}}{R}$$

Fundamentals of Power Electronics

Chapter 7: AC equivalent circuit modeling

Switch in position 2

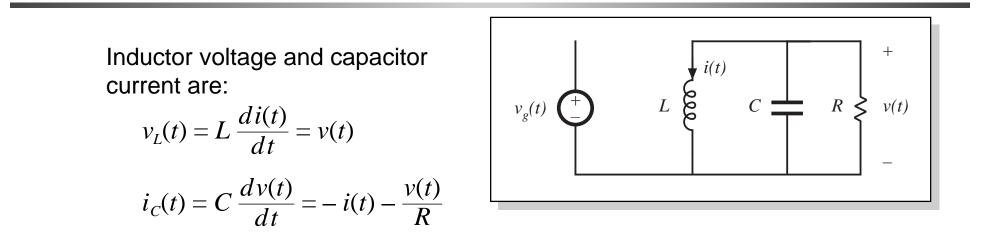

Small ripple approximation: replace waveforms with their low-frequency averaged values:

$$v_{L}(t) = L \frac{di(t)}{dt} \approx \left\langle v(t) \right\rangle_{T_{s}}$$
$$i_{C}(t) = C \frac{dv(t)}{dt} \approx -\left\langle i(t) \right\rangle_{T_{s}} - \frac{\left\langle v(t) \right\rangle_{T_{s}}}{R}$$


7.2.1 Averaging the inductor waveforms

Inductor voltage waveform

Low-frequency average is found by evaluation of

$$\left\langle x_{L}(t)\right\rangle_{T_{s}}=\frac{1}{T_{s}}\int_{t}^{t+T_{s}}x(\tau)d\tau$$

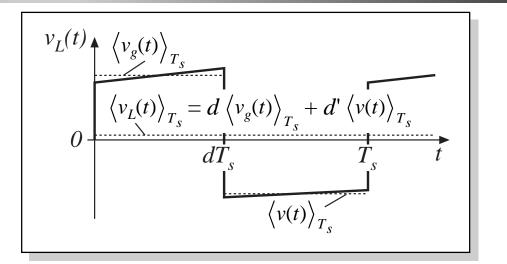Average the inductor voltage in this manner:



$$\left\langle v_L(t) \right\rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} v_L(\tau) d\tau \approx d(t) \left\langle v_g(t) \right\rangle_{T_s} + d'(t) \left\langle v(t) \right\rangle_{T_s}$$

Insert into Eq. (7.2):

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} + d'(t) \langle v(t) \rangle_{T_s}$$

This equation describes how the low-frequency components of the inductor waveforms evolve in time.

Fundamentals of Power Electronics


Chapter 7: AC equivalent circuit modeling

7.2.2 Discussion of the averaging approximation

Use of the average inductor voltage allows us to determine the net change in inductor current over one switching period, while neglecting the switching ripple.

In steady-state, the average inductor voltage is zero (volt-second balance), and hence the inductor current waveform is periodic: $i(t + T_s) = i(t)$. There is no net change in inductor current over one switching period.

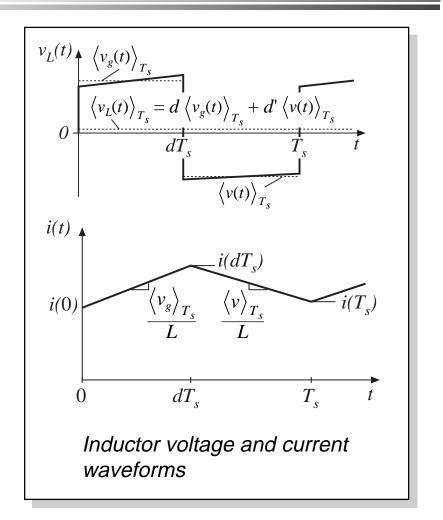During transients or ac variations, the average inductor voltage is not zero in general, and this leads to net variations in inductor current.



Net change in inductor current is correctly predicted by the average inductor voltage

Inductor equation:

$$L \frac{di(t)}{dt} = v_L(t)$$

Divide by L and integrate over one switching period:


$$\int_{t}^{t+T_{s}} di = \frac{1}{L} \int_{t}^{t+T_{s}} v_{L}(\tau) d\tau$$

Left-hand side is the change in inductor current. Right-hand side can be related to average inductor voltage by multiplying and dividing by T_s as follows:

$$i(t+T_s) - i(t) = \frac{1}{L} T_s \left\langle v_L(t) \right\rangle_{T_s}$$

So the net change in inductor current over one switching period is exactly equal to the period T_s multiplied by the average slope $\langle v_L \rangle_{T_s}/L$.

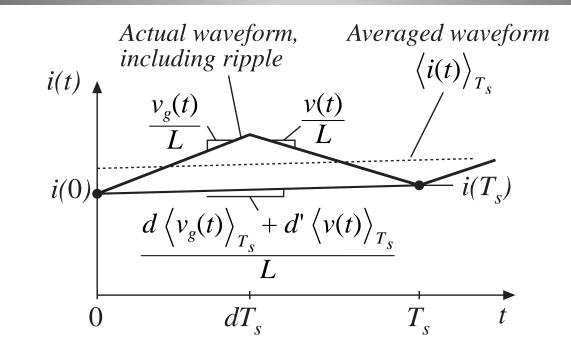Average inductor voltage correctly predicts average slope of $i_L(t)$



The net change in inductor current over one switching period is exactly equal to the period T_s multiplied by the average slope $\langle v_L \rangle_{T_s} / L$.

$$\frac{d\left\langle i(t)\right\rangle_{T_s}}{dt}$$

We have

$$i(t+T_s)-i(t)=\frac{1}{L}T_s\left\langle v_L(t)\right\rangle_{T_s}$$

Rearrange:

$$L \frac{i(t+T_s)-i(t)}{T_s} = \left\langle v_L(t) \right\rangle_{T_s}$$

Define the derivative of $\langle i \rangle_{T_s}$ as (Euler formula):

$$\frac{d\left\langle i(t)\right\rangle_{T_s}}{dt} = \frac{i(t+T_s) - i(t)}{T_s}$$


Hence,

$$L \frac{d\left\langle i(t)\right\rangle_{T_s}}{dt} = \left\langle v_L(t)\right\rangle_{T_s}$$

Fundamentals of Power Electronics

Chapter 7: AC equivalent circuit modeling

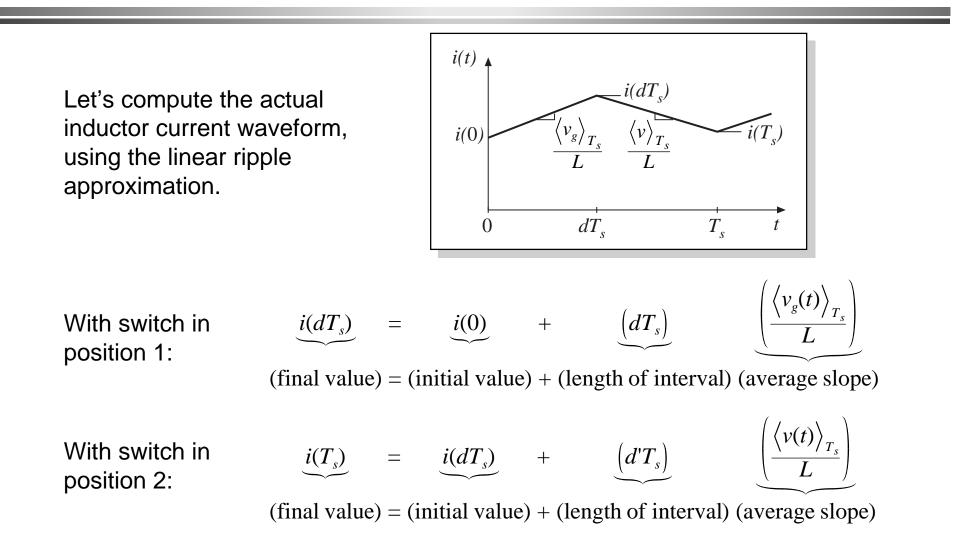Computing how the inductor current changes over one switching period



Fundamentals of Power Electronics

Chapter 7: AC equivalent circuit modeling


Net change in inductor current over one switching period

Eliminate $i(dT_s)$, to express $i(T_s)$ directly as a function of i(0):

$$i(T_{s}) = i(0) + \frac{T_{s}}{L} \underbrace{\left(d(t) \left\langle v_{g}(t) \right\rangle_{T_{s}} + d'(t) \left\langle v(t) \right\rangle_{T_{s}} \right)}_{\left\langle v_{L}(t) \right\rangle_{T_{s}}}$$

The intermediate step of computing $i(dT_s)$ is eliminated.

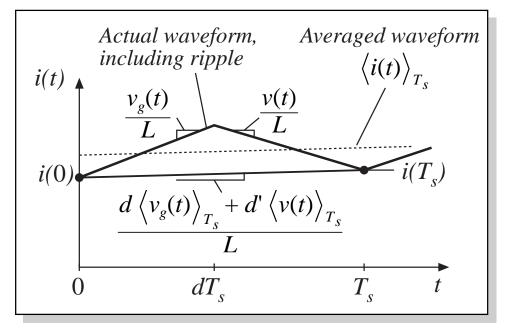The final value $i(T_s)$ is equal to the initial value i(0), plus the switching period Ts multiplied by the average slope $\langle v_L \rangle_{T_s}/L$.




7.2.3 Averaging the capacitor waveforms

Average capacitor current.

$$\left\langle i_{C}(t) \right\rangle_{T_{s}} = d(t) \left(-\frac{\left\langle v(t) \right\rangle_{T_{s}}}{R} \right) + d'(t) \left(-\left\langle i(t) \right\rangle_{T_{s}} - \frac{\left\langle v(t) \right\rangle_{T_{s}}}{R} \right)$$

Collect terms, and equate to $C d\langle v \rangle_{T_s} / dt$:
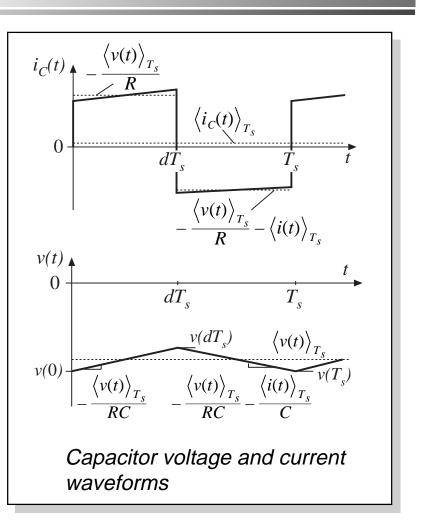
$$C \frac{d\left\langle v(t)\right\rangle_{T_s}}{dt} = -d'(t)\left\langle i(t)\right\rangle_{T_s} - \frac{\left\langle v(t)\right\rangle_{T_s}}{R}$$



7.2.4 The average input current


We found in Chapter 3 that it was sometimes necessary to write an equation for the average converter input current, to derive a complete dc equivalent circuit model. It is likewise necessary to do this for the ac model.

Buck-boost input current waveform is

$$i_g(t) = \begin{cases} \left\langle i(t) \right\rangle_{T_s} & \text{during subinterval 1} \\ 0 & \text{during subinterval 2} \end{cases}$$

Average value:
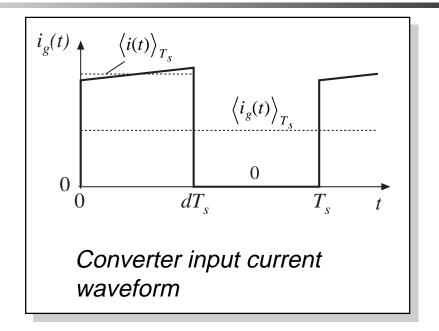
$$\left\langle i_g(t) \right\rangle_{T_s} = d(t) \left\langle i(t) \right\rangle_{T_s}$$



7.2.5. Perturbation and linearization

Converter averaged equations:

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} + d'(t) \langle v(t) \rangle_{T_s}$$
$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = -d'(t) \langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R}$$
$$\langle i_g(t) \rangle_{T_s} = d(t) \langle i(t) \rangle_{T_s}$$

—nonlinear because of multiplication of the time-varying quantity d(t) with other time-varying quantities such as i(t) and v(t).

Construct small-signal model: Linearize about quiescent operating point

If the converter is driven with some steady-state, or quiescent, inputs

$$d(t) = D$$
$$\left\langle v_g(t) \right\rangle_{T_s} = V_g$$

then, from the analysis of Chapter 2, after transients have subsided the inductor current, capacitor voltage, and input current

$$\left\langle i(t) \right\rangle_{T_s}, \left\langle v(t) \right\rangle_{T_s}, \left\langle i_g(t) \right\rangle_{T_s}$$

reach the quiescent values I, V, and I_g , given by the steady-state analysis as

$$V = -\frac{D}{D'} V_g$$
$$I = -\frac{V}{D' R}$$
$$I_g = D I$$

Perturbation

So let us assume that the input voltage and duty cycle are equal to some given (dc) quiescent values, plus superimposed small ac variations:

$$\left\langle v_g(t) \right\rangle_{T_s} = V_g + \hat{v}_g(t)$$

 $d(t) = D + \hat{d}(t)$

In response, and after any transients have subsided, the converter dependent voltages and currents will be equal to the corresponding quiescent values, plus small ac variations:

$$\left\langle i(t) \right\rangle_{T_s} = I + \hat{i}(t) \\ \left\langle v(t) \right\rangle_{T_s} = V + \hat{v}(t) \\ \left\langle i_g(t) \right\rangle_{T_s} = I_g + \hat{i}_g(t)$$

The small-signal assumption

If the ac variations are much smaller in magnitude than the respective quiescent values,

$$egin{aligned} &\hat{v}_{g}(t) \mid << \mid V_{g} \mid \ & \left| \hat{d}(t) \mid << \mid D \mid \ & \left| \hat{i}(t) \mid << \mid I \mid \ & \left| \hat{v}(t) \mid << \mid V \mid \ & \left| \hat{i}_{g}(t) \mid << \mid I_{g} \mid \end{aligned}$$

then the nonlinear converter equations can be linearized.

Perturbation of inductor equation

Insert the perturbed expressions into the inductor differential equation:

$$L\frac{d\left(I+\hat{i}(t)\right)}{dt} = \left(D+\hat{d}(t)\right)\left(V_g+\hat{v}_g(t)\right) + \left(D'-\hat{d}(t)\right)\left(V+\hat{v}(t)\right)$$

note that d'(t) is given by

$$d'(t) = (1 - d(t)) = 1 - (D + \hat{d}(t)) = D' - \hat{d}(t)$$
 with $D' = 1 - D$


Multiply out and collect terms:

$$L\left(\frac{\mathbf{A}}{dt}^{0} + \frac{d\,\hat{i}(t)}{dt}\right) = \underbrace{\left(DV_{g} + D'V\right)}_{Dc \ terms} + \underbrace{\left(D\hat{v}_{g}(t) + D'\hat{v}(t) + \left(V_{g} - V\right)\hat{d}(t)\right)}_{1^{st} \ order \ ac \ terms} + \underbrace{\hat{d}(t)\left(\hat{v}_{g}(t) - \hat{v}(t)\right)}_{2^{nd} \ order \ ac \ terms} + \underbrace{\hat{d}(t)\left(\hat{v}_{g}(t) - \hat{v}(t)\right)}_{1^{st} \ order \ ac \ terms}_{(linear)} + \underbrace{\hat{d}(t)\left(\hat{v}_{g}(t) - \hat{v}(t)\right)}_{2^{nd} \ order \ ac \ terms}_{(nonlinear)}$$

Fundamentals of Power Electronics

Chapter 7: AC equivalent circuit modeling

The perturbed inductor equation

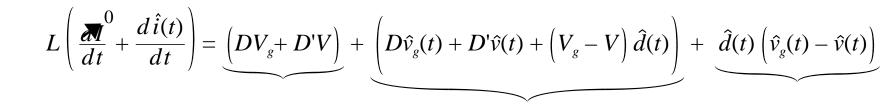

Dc terms

1st order ac terms (linear)

2nd order ac terms (nonlinear)

Since *I* is a constant (dc) term, its derivative is zero

The right-hand side contains three types of terms:

- Dc terms, containing only dc quantities
- First-order ac terms, containing a single ac quantity, usually multiplied by a constant coefficient such as a dc term. These are linear functions of the ac variations
- Second-order ac terms, containing products of ac quantities. These are nonlinear, because they involve multiplication of ac quantities

Neglect of second-order terms

$$L\left(\underbrace{\overrightarrow{at}}^{0} + \frac{d\,\widehat{i}(t)}{dt}\right) = \underbrace{\left(DV_{g} + D'V\right)}_{Dc \ terms} + \underbrace{\left(D\hat{v}_{g}(t) + D'\hat{v}(t) + \left(V_{g} - V\right)\widehat{d}(t)\right)}_{1^{st} \ order \ ac \ terms} + \underbrace{\widehat{d}(t)\left(\hat{v}_{g}(t) - \hat{v}(t)\right)}_{2^{nd} \ order \ ac \ terms}_{(nonlinear)}$$
Provided $\begin{vmatrix} \hat{v}_{g}(t) \end{vmatrix} < < \begin{vmatrix} V_{g} \end{vmatrix}$ then the second-order ac terms are much smaller than the first-order terms. For example, $\begin{vmatrix} \widehat{d}(t) \ \leqslant < |I| \end{vmatrix}$ $|\hat{v}(t)| < < |V|$ $|\hat{i}_{g}(t)| < < |I_{g}|$ So neglect second-order terms. Also, dc terms on each side of equation are equal.

Linearized inductor equation

Upon discarding second-order terms, and removing dc terms (which add to zero), we are left with

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + \left(V_g - V\right)\hat{d}(t)$$

This is the desired result: a linearized equation which describes smallsignal ac variations.

Note that the quiescent values D, D', V, V_g , are treated as given constants in the equation.

Capacitor equation

Perturbation leads to

$$C \frac{d\left(V+\hat{v}(t)\right)}{dt} = -\left(D'-\hat{d}(t)\right)\left(I+\hat{i}(t)\right) - \frac{\left(V+\hat{v}(t)\right)}{R}$$

Collect terms:

$$C\left(\frac{d\hat{v}(t)}{dt} + \frac{d\hat{v}(t)}{dt}\right) = \underbrace{\left(-D'I - \frac{V}{R}\right)}_{=} + \underbrace{\left(-D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)\right)}_{=} + \underbrace{\hat{d}(t)\hat{i}(t)}_{=}$$

Dc terms 1^{st} order ac terms 2^{nd} order ac term(linear)(nonlinear)Neglect second-order terms. Dc terms on both sides of equation are

equal. The following terms remain:

$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)$$

This is the desired small-signal linearized capacitor equation.

Average input current

Perturbation leads to

$$I_g + \hat{i}_g(t) = \left(D + \hat{d}(t)\right) \left(I + \hat{i}(t)\right)$$

Collect terms:

$$\underbrace{I_g}_{Dc \ term} + \underbrace{\hat{i}_g(t)}_{1^{st} \ order \ ac \ term} = \underbrace{(DI)}_{Dc \ term} + \underbrace{(D\hat{i}(t) + I\hat{d}(t))}_{1^{st} \ order \ ac \ terms} + \underbrace{\hat{d}(t)\hat{i}(t)}_{2^{nd} \ order \ ac \ term}$$

(linear)

Neglect second-order terms. Dc terms on both sides of equation are equal. The following first-order terms remain:

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

This is the linearized small-signal equation which described the converter input port.

(nonlinear)

7.2.6. Construction of small-signal equivalent circuit model

The linearized small-signal converter equations:

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + \left(V_g - V\right)\hat{d}(t)$$
$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)$$
$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

Reconstruct equivalent circuit corresponding to these equations, in manner similar to the process used in Chapter 3.

Inductor loop equation


$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_{g}(t) + D'\hat{v}(t) + \left(V_{g} - V\right)\hat{d}(t)$$

$$L \frac{\left(V_{g} - V\right)\hat{d}(t)}{+L\frac{d\hat{i}(t)}{dt}} - \frac{1}{+} D'\hat{v}(t)$$

$$\hat{i}(t)$$


Capacitor node equation
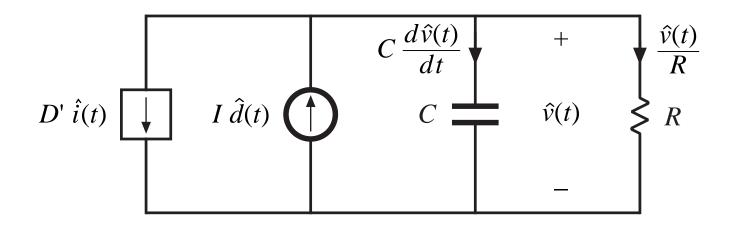
$$C\frac{d\hat{v}(t)}{dt} = -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)$$




Input port node equation

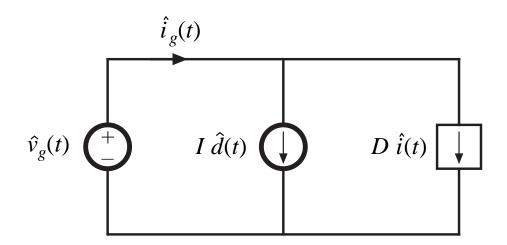 $\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$




Complete equivalent circuit

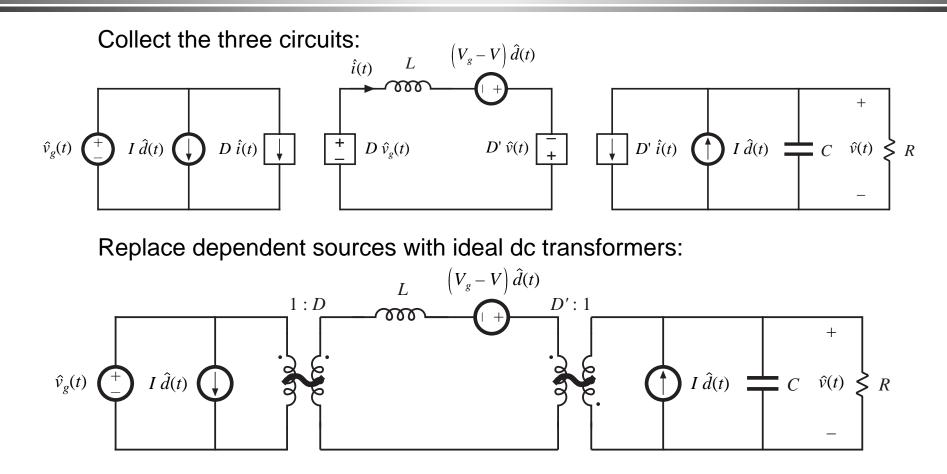


Small-signal ac equivalent circuit model of the buck-boost converter

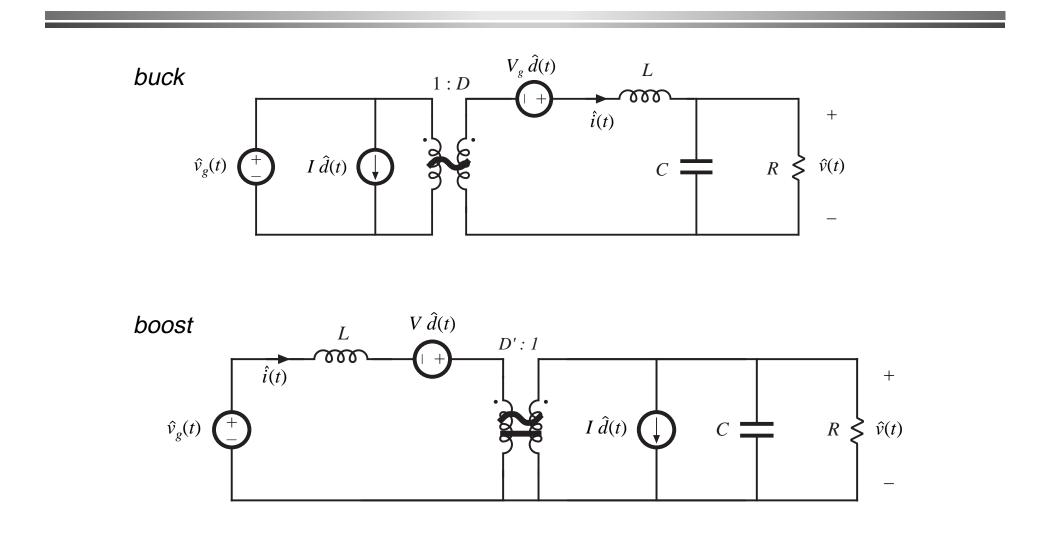7.2.7. Results for several basic converters




Results for several basic converters

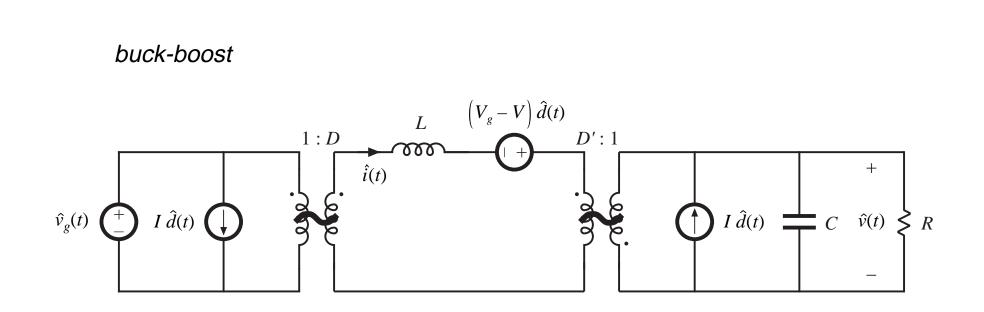


7.3. Example: a nonideal flyback converter

Flyback converter example

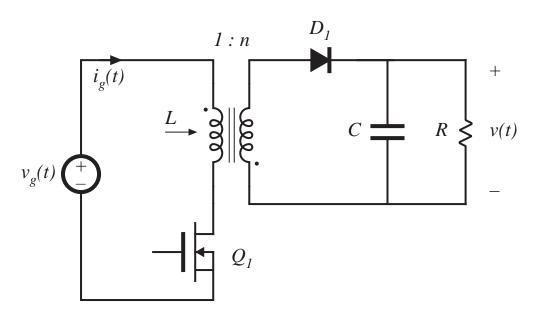

- MOSFET has onresistance R_{on}
- Flyback transformer has magnetizing inductance *L*, referred to primary

Circuits during subintervals 1 and 2

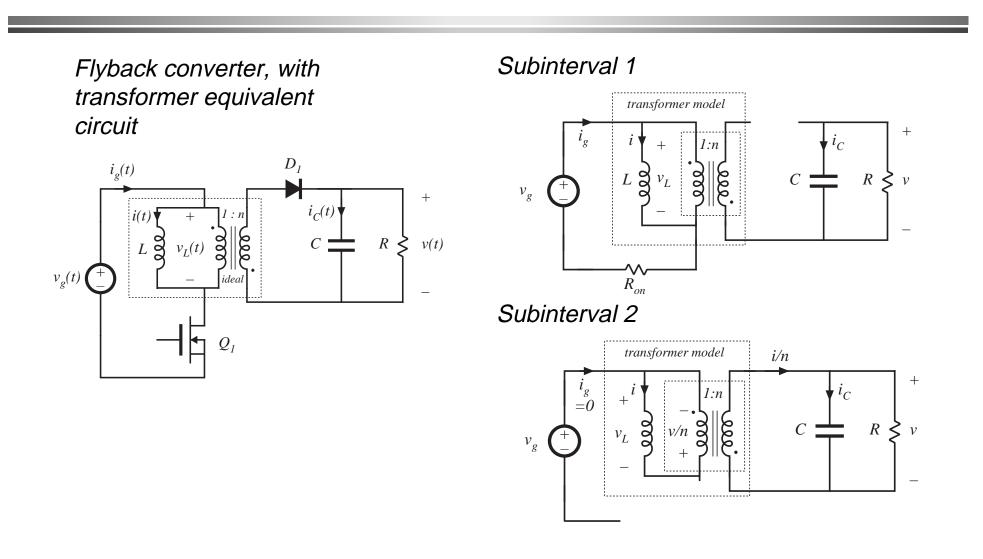

Subinterval 1

Circuit equations: transformer model $v_L(t) = v_g(t) - i(t) R_{on}$ + l_C $i_C(t) = -\frac{v(t)}{R}$ Lg v_L R v v_{g} $i_g(t) = i(t)$ Small ripple approximation: R_{on} $v_{L}(t) = \left\langle v_{g}(t) \right\rangle_{T_{s}} - \left\langle i(t) \right\rangle_{T_{s}} R_{on}$ $i_C(t) = -\frac{\left\langle v(t) \right\rangle_{T_s}}{R}$ MOSFET conducts, diode is reverse-biased $i_g(t) = \left\langle i(t) \right\rangle_{T_s}$

Subinterval 2

Circuit equations:

$$v_L(t) = -\frac{v(t)}{n}$$
$$i_C(t) = -\frac{i(t)}{n} - \frac{v(t)}{R}$$
$$i_g(t) = 0$$


 $v_{g} + v_{L} + v_{L$

Small ripple approximation:

$$v_{L}(t) = -\frac{\left\langle v(t) \right\rangle_{T_{s}}}{n}$$
$$i_{C}(t) = -\frac{\left\langle i(t) \right\rangle_{T_{s}}}{n} - \frac{\left\langle v(t) \right\rangle_{T_{s}}}{R}$$
$$i_{g}(t) = 0$$

MOSFET is off, diode conducts

Inductor waveforms

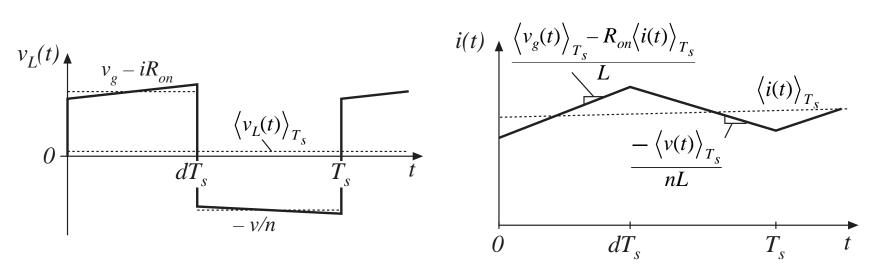

Average inductor voltage:


$$\left\langle v_{L}(t)\right\rangle_{T_{s}} = d(t)\left(\left\langle v_{g}(t)\right\rangle_{T_{s}} - \left\langle i(t)\right\rangle_{T_{s}}R_{on}\right) + d'(t)\left(\frac{-\left\langle v(t)\right\rangle_{T_{s}}}{n}\right)$$

Hence, we can write:

$$L \frac{d\left\langle i(t)\right\rangle_{T_s}}{dt} = d(t) \left\langle v_g(t)\right\rangle_{T_s} - d(t) \left\langle i(t)\right\rangle_{T_s} R_{on} - d'(t) \frac{\left\langle v(t)\right\rangle_{T_s}}{n}$$

Fundamentals of Power Electronics

Capacitor waveforms

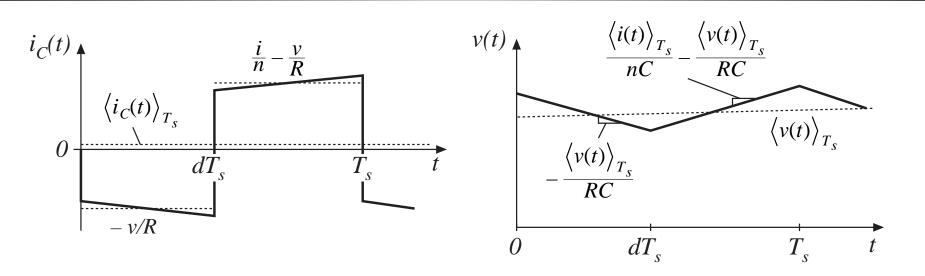

Average capacitor current:

$$\left\langle i_{C}(t)\right\rangle_{T_{s}} = d(t)\left(\frac{-\left\langle v(t)\right\rangle_{T_{s}}}{R}\right) + d'(t)\left(\frac{\left\langle i(t)\right\rangle_{T_{s}}}{n} - \frac{\left\langle v(t)\right\rangle_{T_{s}}}{R}\right)$$


Hence, we can write:

$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = d'(t) \frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R}$$

Fundamentals of Power Electronics

49

Input current waveform

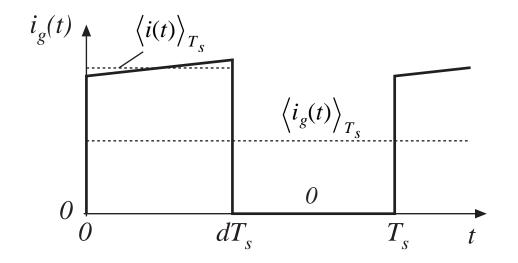

Average input current:

 $\left\langle i_{g}(t)\right\rangle _{T_{s}}=d(t)\left\langle i(t)\right\rangle _{T_{s}}$

The averaged converter equations

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} - d(t) \langle i(t) \rangle_{T_s} R_{on} - d'(t) \frac{\langle v(t) \rangle_{T_s}}{n}$$
$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = d'(t) \frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R}$$
$$\langle i_g(t) \rangle_{T_s} = d(t) \langle i(t) \rangle_{T_s}$$

— a system of nonlinear differential equations

Next step: perturbation and linearization. Let

$$\begin{split} \left\langle v_g(t) \right\rangle_{T_s} &= V_g + \hat{v}_g(t) & \left\langle i(t) \right\rangle_{T_s} = I + \hat{i}(t) \\ d(t) &= D + \hat{d}(t) & \left\langle v(t) \right\rangle_{T_s} = V + \hat{v}(t) \\ \left\langle i_g(t) \right\rangle_{T_s} &= I_g + \hat{i}_g(t) \end{split}$$

Perturbation of the averaged inductor equation

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} - d(t) \langle i(t) \rangle_{T_s} R_{on} - d'(t) \frac{\langle v(t) \rangle_{T_s}}{n}$$

$$L \frac{d(I + \hat{i}(t))}{dt} = (D + \hat{d}(t)) (V_s + \hat{v}_g(t)) - (D' - \hat{d}(t)) \frac{(V + \hat{v}(t))}{n} - (D + \hat{d}(t)) (I + \hat{i}(t)) R_{on}$$

$$L \left(\underbrace{\overrightarrow{M}}_{dt}^0 + \frac{d\hat{i}(t)}{dt} \right) = \underbrace{(DV_s - D' \frac{V}{n} - DR_{on}I)}_{Dc \ terms} + \underbrace{(D\hat{v}_g(t) - D' \frac{\hat{v}(t)}{n} + (V_g + \frac{V}{n} - IR_{on}) \hat{d}(t) - DR_{on}\hat{i}(t))}_{1^{st} \ order \ ac \ terms \ (linear)}$$

$$+ \underbrace{(\hat{d}(t)\hat{v}_g(t) + \hat{d}(t)\frac{\hat{v}(t)}{n} - \hat{d}(t)\hat{i}(t)R_{on})}_{2^{nd} \ order \ ac \ terms \ (nonlinear)}$$

Linearization of averaged inductor equation

Dc terms:

$$0 = DV_g - D'\frac{V}{n} - DR_{on}I$$

Second-order terms are small when the small-signal assumption is satisfied. The remaining first-order terms are:

$$L\frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) - D'\frac{\hat{v}(t)}{n} + \left(V_g + \frac{V}{n} - IR_{on}\right)\hat{d}(t) - DR_{on}\hat{i}(t)$$

This is the desired linearized inductor equation.

Perturbation of averaged capacitor equation

Original averaged equation:

$$C \frac{d\left\langle v(t)\right\rangle_{T_s}}{dt} = d'(t) \frac{\left\langle i(t)\right\rangle_{T_s}}{n} - \frac{\left\langle v(t)\right\rangle_{T_s}}{R}$$

Perturb about quiescent operating point:

$$C \frac{d\left(V + \hat{v}(t)\right)}{dt} = \left(D' - \hat{d}(t)\right) \frac{\left(I + \hat{i}(t)\right)}{n} - \frac{\left(V + \hat{v}(t)\right)}{R}$$

Collect terms:

$$C\left(\frac{d\hat{v}^{0}}{dt} + \frac{d\hat{v}(t)}{dt}\right) = \underbrace{\left(\frac{D'I}{n} - \frac{V}{R}\right)}_{Dc \ terms} + \underbrace{\left(\frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n}\right)}_{1^{\ st} \ order \ ac \ terms}_{(linear)} - \underbrace{\frac{\hat{d}(t)\hat{i}(t)}{n}}_{2^{\ nd} \ order \ ac \ terms}_{(nonlinear)}$$

Fundamentals of Power Electronics

Linearization of averaged capacitor equation

Dc terms:

$$0 = \left(\frac{D'I}{n} - \frac{V}{R}\right)$$

Second-order terms are small when the small-signal assumption is satisfied. The remaining first-order terms are:

$$C\frac{d\hat{v}(t)}{dt} = \frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n}$$

This is the desired linearized capacitor equation.

Perturbation of averaged input current equation

Original averaged equation:

$$\left\langle i_{g}(t)\right\rangle _{T_{s}}=d(t)\left\langle i(t)\right\rangle _{T_{s}}$$

Perturb about quiescent operating point:

$$I_g + \hat{i}_g(t) = \left(D + \hat{d}(t)\right) \left(I + \hat{i}(t)\right)$$

Collect terms:

$$\underbrace{I_g}_{g} + \underbrace{\hat{i}_g(t)}_{g} = \underbrace{(DI)}_{t} + \underbrace{(D\hat{i}(t) + I\hat{d}(t))}_{t} + \underbrace{\hat{d}(t)\hat{i}(t)}_{t}$$

$$Dc \ term \quad 1^{st} \ order \ ac \ term \quad Dc \ term \quad 1^{st} \ order \ ac \ terms \quad 2^{nd} \ order \ ac \ term \\ (nonlinear)$$

Fundamentals of Power Electronics

Linearization of averaged input current equation

Dc terms:

 $I_g = DI$

Second-order terms are small when the small-signal assumption is satisfied. The remaining first-order terms are:

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

This is the desired linearized input current equation.

Summary: dc and small-signal ac converter equations

Dc equations:

$$0 = DV_g - D'\frac{V}{n} - DR_{on}I$$
$$0 = \left(\frac{D'I}{n} - \frac{V}{R}\right)$$
$$I_g = DI$$


Small-signal ac equations:

$$L\frac{d\hat{i}(t)}{dt} = D\hat{v}_{g}(t) - D'\frac{\hat{v}(t)}{n} + \left(V_{g} + \frac{V}{n} - IR_{on}\right)\hat{d}(t) - DR_{on}\hat{i}(t)$$
$$C\frac{d\hat{v}(t)}{dt} = \frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n}$$
$$\hat{i}_{g}(t) = D\hat{i}(t) + I\hat{d}(t)$$

Next step: construct equivalent circuit models.


Small-signal ac equivalent circuit: inductor loop
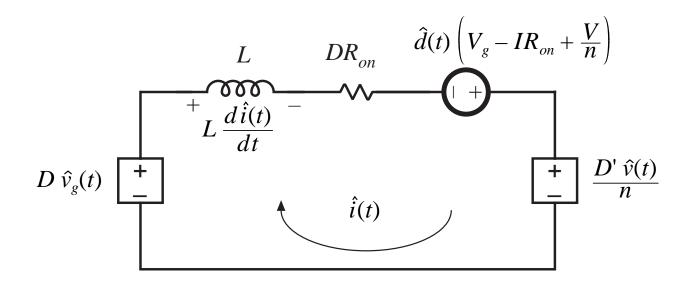
$$L\frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) - D'\frac{\hat{v}(t)}{n} + \left(V_g + \frac{V}{n} - IR_{on}\right)\hat{d}(t) - DR_{on}\hat{i}(t)$$




Small-signal ac equivalent circuit: capacitor node
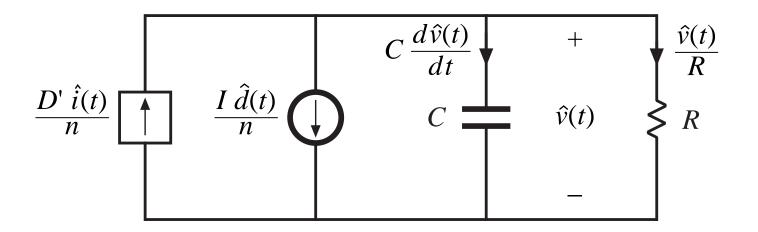
$$C \frac{d\hat{v}(t)}{dt} = \frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n}$$




Small-signal ac equivalent circuit: converter input node

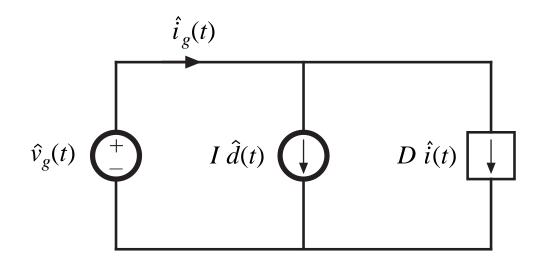
 $\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$



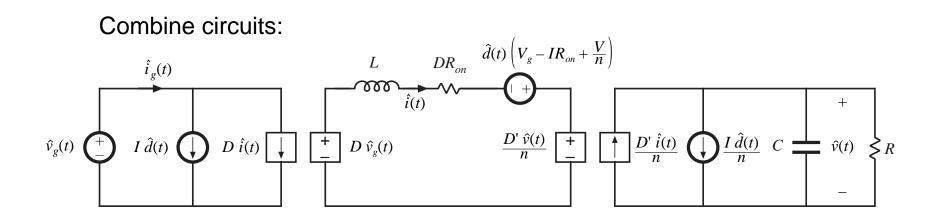Small-signal ac model, nonideal flyback converter example



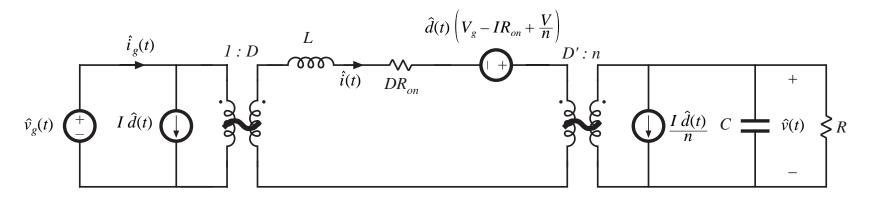Replace dependent sources with ideal transformers:



7.4. State Space Averaging

- A formal method for deriving the small-signal ac equations of a switching converter
- Equivalent to the modeling method of the previous sections
- Uses the state-space matrix description of linear circuits
- Often cited in the literature
- A general approach: if the state equations of the converter can be written for each subinterval, then the small-signal averaged model can always be derived
- Computer programs exist which utilize the state-space averaging method

7.4.1. The state equations of a network

- A canonical form for writing the differential equations of a system
- If the system is linear, then the derivatives of the *state variables* are expressed as linear combinations of the system independent inputs and state variables themselves
- The physical state variables of a system are usually associated with the storage of energy
- For a typical converter circuit, the physical state variables are the inductor currents and capacitor voltages
- Other typical physical state variables: position and velocity of a motor shaft
- At a given point in time, the values of the state variables depend on the previous history of the system, rather than the present values of the system inputs
- To solve the differential equations of a system, the initial values of the state variables must be specified

State equations of a linear system, in matrix form

A canonical matrix form:

State vector $\mathbf{x}(t)$ contains

voltages, etc.:


 $\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A} \mathbf{x}(t) + \mathbf{B} \mathbf{u}(t)$ $\mathbf{y}(t) = \mathbf{C} \mathbf{x}(t) + \mathbf{E} \mathbf{u}(t)$ $\mathbf{x}(t) = \mathbf{C} \mathbf{x}(t) + \mathbf{L} \mathbf{u}(t)$ $\mathbf{x}_{1}(t) = \begin{bmatrix} x_{1}(t) \\ x_{2}(t) \\ \vdots \end{bmatrix}, \qquad \frac{d\mathbf{x}(t)}{dt} = \begin{bmatrix} \frac{dx_{1}(t)}{dt} \\ \frac{dx_{2}(t)}{dt} \\ \vdots \end{bmatrix}$ inductor currents, capacitor

Input vector $\mathbf{u}(t)$ contains independent sources such as $v_g(t)$

Output vector $\mathbf{y}(t)$ contains other dependent quantities to be computed, such as $i_g(t)$


Matrix K contains values of capacitance, inductance, and mutual inductance, so that $\mathbf{K} \, d\mathbf{x}/dt$ is a vector containing capacitor currents and inductor winding voltages. These quantities are expressed as linear combinations of the independent inputs and state variables. The matrices A, **B**, **C**, and **E** contain the constants of proportionality.

Example

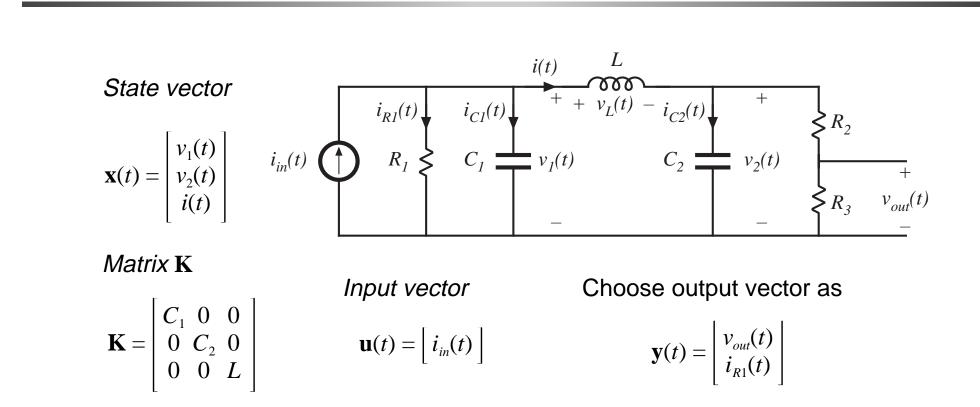

To write the state equations of this circuit, we must express the inductor voltages and capacitor currents as linear combinations of the elements of the $\mathbf{x}(t)$ and $\mathbf{u}(t)$ vectors.

Circuit equations

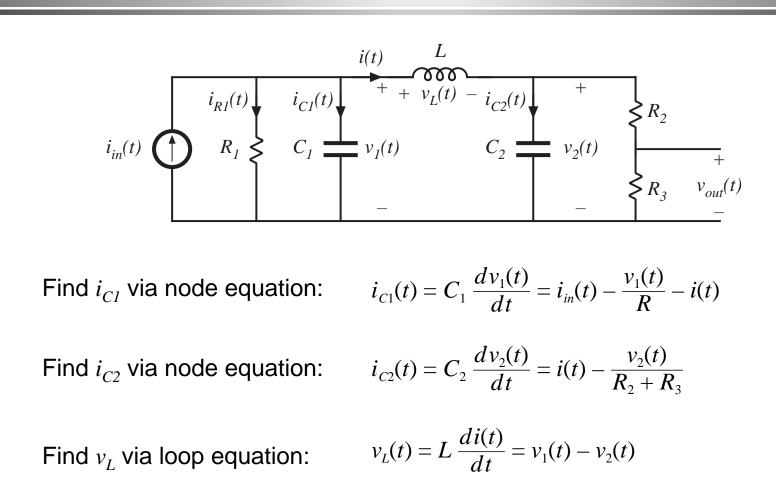

Fundamentals of Power Electronics

Equations in matrix form

The same equations:


$$i_{C1}(t) = C_1 \frac{dv_1(t)}{dt} = i_{in}(t) - \frac{v_1(t)}{R} - i(t)$$
$$i_{C2}(t) = C_2 \frac{dv_2(t)}{dt} = i(t) - \frac{v_2(t)}{R_2 + R_3}$$
$$v_L(t) = L \frac{di(t)}{dt} = v_1(t) - v_2(t)$$

Express in matrix form:

$$\begin{bmatrix} C_{1} & 0 & 0 \\ 0 & C_{2} & 0 \\ 0 & 0 & L \end{bmatrix} \underbrace{ \begin{bmatrix} \frac{dv_{1}(t)}{dt} \\ \frac{dv_{2}(t)}{dt} \\ \frac{di(t)}{dt} \end{bmatrix}}_{\mathbf{K}} = \underbrace{ \begin{bmatrix} -\frac{1}{R_{1}} & 0 & -1 \\ 0 & -\frac{1}{R_{2}+R_{3}} & 1 \\ 1 & -1 & 0 \end{bmatrix}}_{\mathbf{K}} \underbrace{ \begin{bmatrix} v_{1}(t) \\ v_{2}(t) \\ i(t) \end{bmatrix}}_{\mathbf{K}} + \underbrace{ \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{K}} \underbrace{ \begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{K}}$$

Fundamentals of Power Electronics

Output (dependent signal) equations

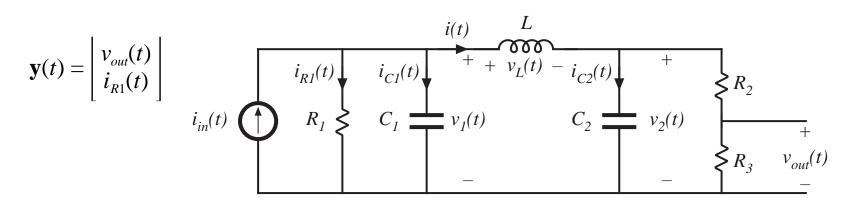

Express elements of the vector \mathbf{y} as linear combinations of elements of \mathbf{x} and \mathbf{u} :

$$v_{out}(t) = v_2(t) \frac{R_3}{R_2 + R_3}$$

 $i_{R1}(t) = \frac{v_1(t)}{R_1}$

Express in matrix form

The same equations:

$$v_{out}(t) = v_2(t) \frac{R_3}{R_2 + R_3}$$

 $i_{R1}(t) = \frac{v_1(t)}{R_1}$

Express in matrix form:

$$\underbrace{\begin{bmatrix} v_{out}(t) \\ i_{R1}(t) \end{bmatrix}}_{\mathbf{y}(t)} = \underbrace{\begin{bmatrix} 0 & \frac{R_3}{R_2 + R_3} & 0 \\ \frac{1}{R_1} & 0 & 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} v_1(t) \\ v_2(t) \\ i(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \underbrace{\begin{bmatrix} i_{in}(t) \underbrace{i_{in}(t) }\\ \underbrace{\begin{bmatrix} i_{in}(t) \underbrace{\begin{bmatrix} i_{in}(t) \underbrace{i_{in}(t) }\\ \underbrace{\begin{bmatrix} i_{in}(t) \underbrace{\begin{bmatrix} i_{in}(t) \underbrace{i_{in}(t) \\ \underbrace{\begin{bmatrix} i_{in}(t) \underbrace{i_{in}(t) \underbrace{i_{in}($$

7.4.2. The basic state-space averaged model

Given: a PWM converter, operating in continuous conduction mode, with two subintervals during each switching period.

During subinterval 1, when the switches are in position 1, the converter reduces to a linear circuit that can be described by the following state equations:

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t)$$

During subinterval 2, when the switches are in position 2, the converter reduces to another linear circuit, that can be described by the following state equations:

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_2 \mathbf{x}(t) + \mathbf{B}_2 \mathbf{u}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_2 \mathbf{x}(t) + \mathbf{E}_2 \mathbf{u}(t)$$

Equilibrium (dc) state-space averaged model

Provided that the natural frequencies of the converter, as well as the frequencies of variations of the converter inputs, are much slower than the switching frequency, then the state-space averaged model that describes the converter in equilibrium is

 $\mathbf{0} = \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}$ $\mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$

where the averaged matrices are

$$\mathbf{A} = D \mathbf{A}_{1} + D' \mathbf{A}_{2}$$
$$\mathbf{B} = D \mathbf{B}_{1} + D' \mathbf{B}_{2}$$
$$\mathbf{C} = D \mathbf{C}_{1} + D' \mathbf{C}_{2}$$
$$\mathbf{E} = D \mathbf{E}_{1} + D' \mathbf{E}_{2}$$

and the equilibrium dc components are

 $\mathbf{X} = equilibrium (dc) state vector$

 $\mathbf{U} = equilibrium (dc) input vector$

 $\mathbf{Y} = equilibrium (dc) output vector$

D = equilibrium (dc) duty cycle

Solution of equilibrium averaged model

Equilibrium state-space averaged model:

 $\mathbf{0} = \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}$ $\mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$

Solution for X and Y:

 $\mathbf{X} = -\mathbf{A}^{-1} \mathbf{B} \mathbf{U}$ $\mathbf{Y} = \left(-\mathbf{C} \mathbf{A}^{-1} \mathbf{B} + \mathbf{E}\right) \mathbf{U}$

Small-signal ac state-space averaged model

$$\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A} \,\hat{\mathbf{x}}(t) + \mathbf{B} \,\hat{\mathbf{u}}(t) + \left\{ \left(\mathbf{A}_{1} - \mathbf{A}_{2}\right) \mathbf{X} + \left(\mathbf{B}_{1} - \mathbf{B}_{2}\right) \mathbf{U} \right\} \,\hat{d}(t)$$
$$\hat{\mathbf{y}}(t) = \mathbf{C} \,\hat{\mathbf{x}}(t) + \mathbf{E} \,\hat{\mathbf{u}}(t) + \left\{ \left(\mathbf{C}_{1} - \mathbf{C}_{2}\right) \mathbf{X} + \left(\mathbf{E}_{1} - \mathbf{E}_{2}\right) \mathbf{U} \right\} \,\hat{d}(t)$$

where

 $\hat{\mathbf{x}}(t) = small - signal (ac) perturbation in state vector$ $<math display="block">\hat{\mathbf{u}}(t) = small - signal (ac) perturbation in input vector$ $\hat{\mathbf{y}}(t) = small - signal (ac) perturbation in output vector$ $\hat{d}(t) = small - signal (ac) perturbation in duty cycle$

So if we can write the converter state equations during subintervals 1 and 2, then we can always find the averaged dc and small-signal ac models

7.4.3. Discussion of the state-space averaging result

As in Sections 7.1 and 7.2, the low-frequency components of the inductor currents and capacitor voltages are modeled by averaging over an interval of length T_s . Hence, we define the average of the state vector as:

$$\left\langle \mathbf{x}(t)\right\rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} \mathbf{x}(\tau) d\tau$$

- The low-frequency components of the input and output vectors are modeled in a similar manner.
- By averaging the inductor voltages and capacitor currents, one obtains:

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

Change in state vector during first subinterval

During subinterval 1, we have

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t)$$

So the elements of $\mathbf{x}(t)$ change with the slope

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left(\mathbf{A}_{1} \mathbf{x}(t) + \mathbf{B}_{1} \mathbf{u}(t) \right)$$

Small ripple assumption: the elements of $\mathbf{x}(t)$ and $\mathbf{u}(t)$ do not change significantly during the subinterval. Hence the slopes are essentially constant and are equal to

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left(\mathbf{A}_{1} \left\langle \mathbf{x}(t) \right\rangle_{T_{s}} + \mathbf{B}_{1} \left\langle \mathbf{u}(t) \right\rangle_{T_{s}} \right)$$

Change in state vector during first subinterval

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left(\mathbf{A}_{1} \langle \mathbf{x}(t) \rangle_{T_{s}} + \mathbf{B}_{1} \langle \mathbf{u}(t) \rangle_{T_{s}} \right)$$

$$\mathbf{x}(t) \quad \mathbf{K}^{-1} \left(\mathbf{A}_{1} \langle \mathbf{x} \rangle_{T_{s}} + \mathbf{B}_{1} \langle \mathbf{u} \rangle_{T_{s}} \right)$$

$$\mathbf{x}(0)$$

$$\mathbf{x}(0)$$
Net change in state vector over first subinterval:
$$\underbrace{\mathbf{x}(dT_{s})}_{final} = \underbrace{\mathbf{x}(0)}_{value} + \underbrace{(dT_{s})}_{initial} \underbrace{\mathbf{K}^{-1} \left(\mathbf{A}_{1} \langle \mathbf{x}(t) \rangle_{T_{s}} + \mathbf{B}_{1} \langle \mathbf{u}(t) \rangle_{T_{s}} \right)}_{slope}$$

$$\underbrace{\mathbf{x}(t)}_{slope}$$

Fundamentals of Power Electronics

Change in state vector during second subinterval

Use similar arguments.

State vector now changes with the essentially constant slope

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left(\mathbf{A}_{2} \left\langle \mathbf{x}(t) \right\rangle_{T_{s}} + \mathbf{B}_{2} \left\langle \mathbf{u}(t) \right\rangle_{T_{s}} \right)$$

The value of the state vector at the end of the second subinterval is therefore

$$\underbrace{\mathbf{x}(T_{s})}_{final \ initial \ interval \ value \ length} \underbrace{\mathbf{K}^{-1}\left(\mathbf{A}_{2}\left\langle \mathbf{x}(t)\right\rangle_{T_{s}} + \mathbf{B}_{2}\left\langle \mathbf{u}(t)\right\rangle_{T_{s}}\right)}_{slope}$$

Fundamentals of Power Electronics

Net change in state vector over one switching period

We have:

$$\mathbf{x}(dT_s) = \mathbf{x}(0) + \left(dT_s\right) \mathbf{K}^{-1} \left(\mathbf{A}_1 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_1 \left\langle \mathbf{u}(t) \right\rangle_{T_s}\right)$$
$$\mathbf{x}(T_s) = \mathbf{x}(dT_s) + \left(d^T_s\right) \mathbf{K}^{-1} \left(\mathbf{A}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s}\right)$$

Eliminate $\mathbf{x}(dT_s)$, to express $\mathbf{x}(T_s)$ directly in terms of $\mathbf{x}(0)$:


$$\mathbf{x}(T_s) = \mathbf{x}(0) + dT_s \mathbf{K}^{-1} \left(\mathbf{A}_1 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_1 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right) + d'T_s \mathbf{K}^{-1} \left(\mathbf{A}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right)$$

Collect terms:

$$\mathbf{x}(T_s) = \mathbf{x}(0) + T_s \mathbf{K}^{-1} \Big(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \Big) \left\langle \mathbf{x}(t) \right\rangle_{T_s} + T_s \mathbf{K}^{-1} \Big(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \Big) \left\langle \mathbf{u}(t) \right\rangle_{T_s}$$

Fundamentals of Power Electronics

Approximate derivative of state vector

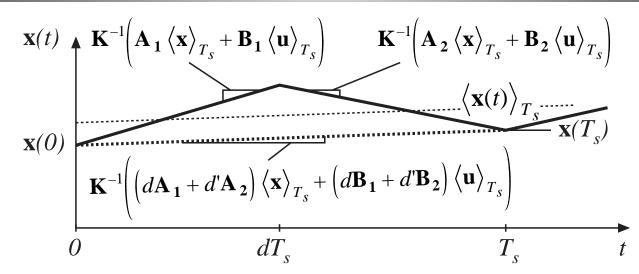

Use Euler approximation:


$$\frac{d\left\langle \mathbf{x}(t)\right\rangle_{T_s}}{dt} \approx \frac{\mathbf{x}(T_s) - \mathbf{x}(0)}{T_s}$$

We obtain:

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

Fundamentals of Power Electronics

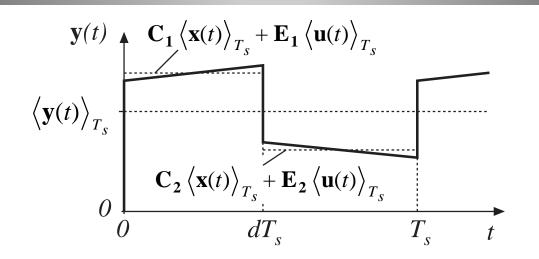Low-frequency components of output vector



Remove switching harmonics by averaging over one switching period:

$$\left\langle \mathbf{y}(t) \right\rangle_{T_s} = d(t) \left(\mathbf{C}_1 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{E}_1 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right) + d'(t) \left(\mathbf{C}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{E}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right)$$

Collect terms:

$$\left\langle \mathbf{y}(t) \right\rangle_{T_s} = \left(d(t) \mathbf{C}_1 + d'(t) \mathbf{C}_2 \right) \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \left(d(t) \mathbf{E}_1 + d'(t) \mathbf{E}_2 \right) \left\langle \mathbf{u}(t) \right\rangle_{T_s}$$

Fundamentals of Power Electronics

Averaged state equations: quiescent operating point

The averaged (nonlinear) state equations:

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s} \\ \left\langle \mathbf{y}(t) \right\rangle_{T_s} = \left(d(t) \mathbf{C}_1 + d'(t) \mathbf{C}_2 \right) \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \left(d(t) \mathbf{E}_1 + d'(t) \mathbf{E}_2 \right) \left\langle \mathbf{u}(t) \right\rangle_{T_s}$$

The converter operates in equilibrium when the derivatives of all elements of $\langle \mathbf{x}(t) \rangle_{T_s}$ are zero. Hence, the converter quiescent operating point is the solution of

$$\mathbf{0} = \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}$$
$$\mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$$

where $\mathbf{A} = D \mathbf{A}_1 + D' \mathbf{A}_2$ and $\mathbf{B} = D \mathbf{B}_1 + D' \mathbf{B}_2$ $\mathbf{C} = D \mathbf{C}_1 + D' \mathbf{C}_2$ $\mathbf{E} = D \mathbf{E}_1 + D' \mathbf{E}_2$

- $\mathbf{X} = equilibrium (dc) state vector$
- $\mathbf{U} = equilibrium (dc) input vector$
- $\mathbf{Y} = equilibrium (dc) output vector$
- D = equilibrium (dc) duty cycle

Fundamentals of Power Electronics

Averaged state equations: perturbation and linearization

Let	$\left\langle \mathbf{x}(t) \right\rangle_{T_s} = \mathbf{X} + \hat{\mathbf{x}}(t)$	with	$\left\ \mathbf{U}\right\ >> \left\ \hat{\mathbf{u}}(t)\right\ $
	$\left\langle \mathbf{u}(t) \right\rangle_{T_s} = \mathbf{U} + \hat{\mathbf{u}}(t)$		$D >> \left \hat{d}(t) \right $
	$\left\langle \mathbf{y}(t) \right\rangle_{T_s} = \mathbf{Y} + \hat{\mathbf{y}}(t)$		$\left\ \mathbf{X}\right\ >> \left\ \hat{\mathbf{x}}(t)\right\ $
	$d(t) = D + \hat{d}(t) \implies d'(t) = D' + \hat{d}(t)$	$-\hat{d}(t)$	$\left\ \mathbf{Y}\right\ >> \left\ \widehat{\mathbf{y}}(t)\right\ $


Substitute into averaged state equations:

$$\mathbf{K} \frac{d(\mathbf{X} + \hat{\mathbf{x}}(t))}{dt} = \left(\left(D + \hat{d}(t) \right) \mathbf{A}_{1} + \left(D' - \hat{d}(t) \right) \mathbf{A}_{2} \right) \left(\mathbf{X} + \hat{\mathbf{x}}(t) \right) + \left(\left(D + \hat{d}(t) \right) \mathbf{B}_{1} + \left(D' - \hat{d}(t) \right) \mathbf{B}_{2} \right) \left(\mathbf{U} + \hat{\mathbf{u}}(t) \right)$$

$$\begin{pmatrix} \mathbf{Y} + \hat{\mathbf{y}}(t) \end{pmatrix} = \left(\left(D + \hat{d}(t) \right) \mathbf{C}_{1} + \left(D' - \hat{d}(t) \right) \mathbf{C}_{2} \right) \left(\mathbf{X} + \hat{\mathbf{x}}(t) \right)$$
$$+ \left(\left(D + \hat{d}(t) \right) \mathbf{E}_{1} + \left(D' - \hat{d}(t) \right) \mathbf{E}_{2} \right) \left(\mathbf{U} + \hat{\mathbf{u}}(t) \right)$$

Fundamentals of Power Electronics

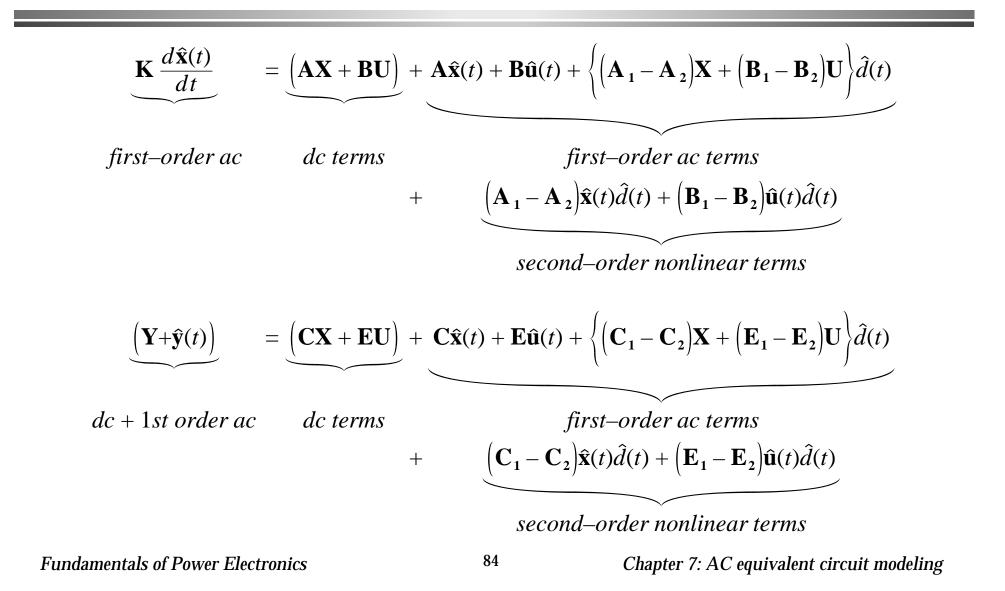Averaged state equations: perturbation and linearization




Linearized small-signal state equations

Dc terms drop out of equations. Second-order (nonlinear) terms are small when the small-signal assumption is satisfied. We are left with:


$$\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A} \,\hat{\mathbf{x}}(t) + \mathbf{B} \,\hat{\mathbf{u}}(t) + \left\{ \left(\mathbf{A}_{1} - \mathbf{A}_{2}\right) \mathbf{X} + \left(\mathbf{B}_{1} - \mathbf{B}_{2}\right) \mathbf{U} \right\} \,\hat{d}(t)$$
$$\hat{\mathbf{y}}(t) = \mathbf{C} \,\hat{\mathbf{x}}(t) + \mathbf{E} \,\hat{\mathbf{u}}(t) + \left\{ \left(\mathbf{C}_{1} - \mathbf{C}_{2}\right) \mathbf{X} + \left(\mathbf{E}_{1} - \mathbf{E}_{2}\right) \mathbf{U} \right\} \,\hat{d}(t)$$

This is the desired result.

7.4.4. Example: State-space averaging of a nonideal buck-boost converter

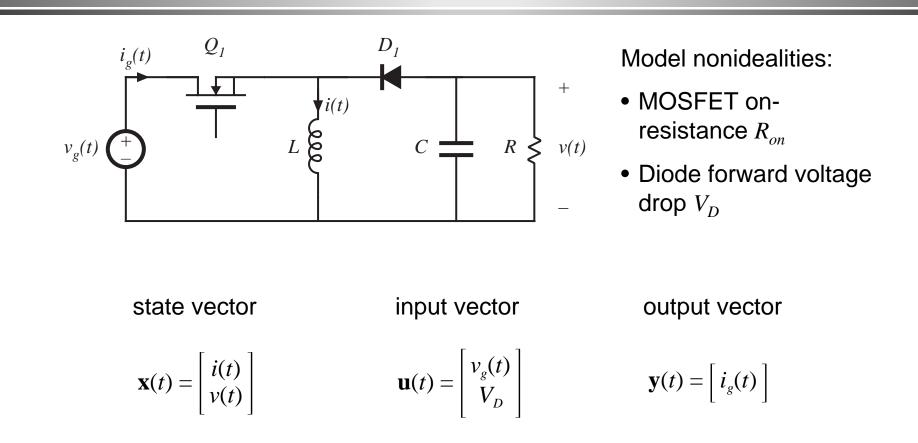


Subinterval 1

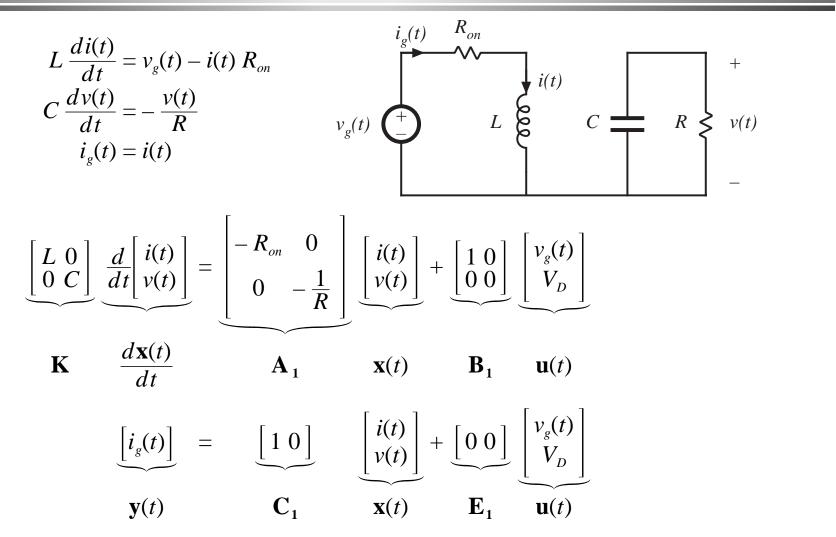

Fundamentals of Power Electronics

Subinterval 2

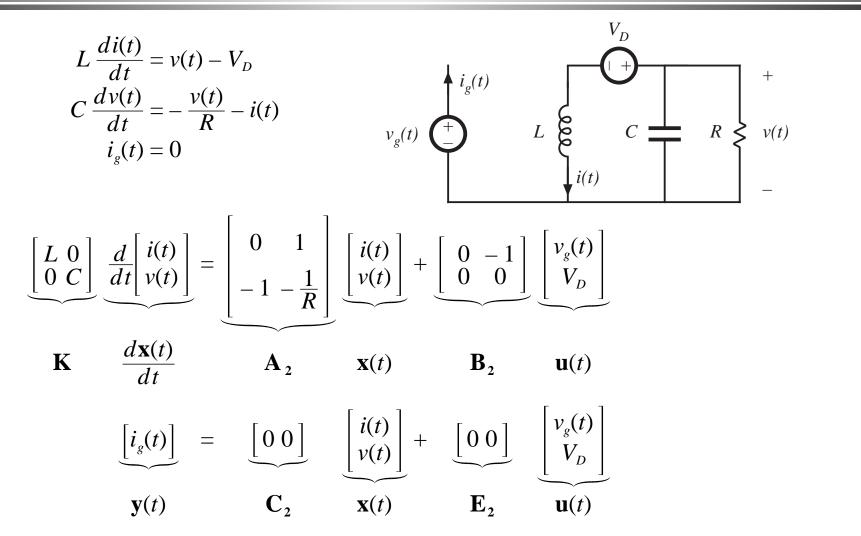

Fundamentals of Power Electronics

Evaluate averaged matrices

$$\mathbf{A} = D\mathbf{A}_{1} + D'\mathbf{A}_{2} = D \begin{bmatrix} -R_{on} & 0\\ 0 & -\frac{1}{R} \end{bmatrix} + D' \begin{bmatrix} 0 & 1\\ -1 & -\frac{1}{R} \end{bmatrix} = \begin{bmatrix} -DR_{on} & D'\\ -D' & -\frac{1}{R} \end{bmatrix}$$

In a similar manner,

$$\mathbf{B} = D\mathbf{B}_{1} + D'\mathbf{B}_{2} = \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix}$$
$$\mathbf{C} = D\mathbf{C}_{1} + D'\mathbf{C}_{2} = \begin{bmatrix} D & 0 \end{bmatrix}$$
$$\mathbf{E} = D\mathbf{E}_{1} + D'\mathbf{E}_{2} = \begin{bmatrix} 0 & 0 \end{bmatrix}$$

Fundamentals of Power Electronics

DC state equations

$$\begin{array}{l} \mathbf{0} = \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U} \\ \mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U} \end{array} \text{ or, } \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix} \\ \begin{bmatrix} I_g \end{bmatrix} = \begin{bmatrix} I \\ V \end{bmatrix} = \begin{bmatrix} D & 0 \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

DC solution:

$$\begin{bmatrix} I \\ V \end{bmatrix} = \left(\frac{1}{1 + \frac{D}{D'^2}} \frac{R_{on}}{R}\right) \begin{bmatrix} \frac{D}{D'^2 R} & \frac{1}{D' R} \\ -\frac{D}{D'} & 1 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$
$$\begin{bmatrix} I_g \end{bmatrix} = \left(\frac{1}{1 + \frac{D}{D'^2}} \frac{R_{on}}{R}\right) \begin{bmatrix} \frac{D^2}{D'^2 R} & \frac{D}{D' R} \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

Е


Fundamentals of Power Electronics

Steady-state equivalent circuit

DC state equations:

$$\begin{bmatrix} 0\\0 \end{bmatrix} = \begin{bmatrix} -DR_{on} & D'\\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} I\\V \end{bmatrix} + \begin{bmatrix} D & -D'\\0 & 0 \end{bmatrix} \begin{bmatrix} V_g\\V_D \end{bmatrix}$$
$$\begin{bmatrix} I_g \end{bmatrix} = \begin{bmatrix} D & 0 \end{bmatrix} \begin{bmatrix} I & V_g\\V_D \end{bmatrix} + \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} V_g\\V_D \end{bmatrix}$$

Corresponding equivalent circuit:

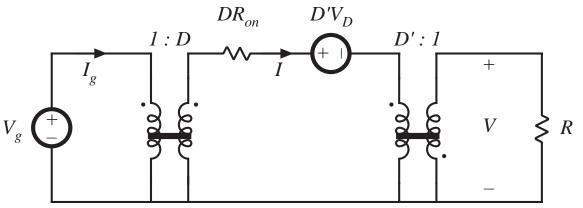

Small-signal ac model

Evaluate matrices in small-signal model:

$$\begin{pmatrix} \mathbf{A}_1 - \mathbf{A}_2 \end{pmatrix} \mathbf{X} + \begin{pmatrix} \mathbf{B}_1 - \mathbf{B}_2 \end{pmatrix} \mathbf{U} = \begin{bmatrix} -V\\I \end{bmatrix} + \begin{bmatrix} V_g - IR_{on} + V_D\\0 \end{bmatrix} = \begin{bmatrix} V_g - V - IR_{on} + V_D\\I \end{bmatrix}$$
$$\begin{pmatrix} \mathbf{C}_1 - \mathbf{C}_2 \end{pmatrix} \mathbf{X} + \begin{pmatrix} \mathbf{E}_1 - \mathbf{E}_2 \end{pmatrix} \mathbf{U} = \begin{bmatrix} I \end{bmatrix}$$

Small-signal ac state equations:

$$\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix} \frac{d}{dt} \begin{bmatrix} \hat{i}(t) \\ \hat{v}(t) \end{bmatrix} = \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} \hat{i}(t) \\ \hat{v}(t) \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{v}_{g}(t) \\ \hat{v}_{D}(t) \end{bmatrix} + \begin{bmatrix} V_{g} - V - IR_{on} + V_{D} \\ I \end{bmatrix} \hat{d}(t)$$
$$\begin{bmatrix} \hat{i}_{g}(t) \end{bmatrix} = \begin{bmatrix} D & 0 \end{bmatrix} \begin{bmatrix} \hat{i}(t) \\ \hat{v}(t) \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{v}_{g}(t) \\ \hat{v}_{D}(t) \end{bmatrix} + \begin{bmatrix} 0 \\ I \end{bmatrix} \hat{d}(t)$$

Fundamentals of Power Electronics


Construction of ac equivalent circuit

 $L \frac{di(t)}{dt} = D' \,\hat{v}(t) - DR_{on} \,\hat{i}(t) + D \,\hat{v}_g(t) + \left(V_g - V - IR_{on} + V_D\right) \hat{d}(t)$ Small-signal ac equations, in $C \frac{d\hat{v}(t)}{dt} = -D' \hat{i}(t) - \frac{\hat{v}(t)}{R} + I \hat{d}(t)$ scalar form: $\hat{i}_g(t) = D \ \hat{i}(t) + I \ \hat{d}(t)$ $\hat{i}_{g}(t)$ Corresponding equivalent circuits: input eqn inductor equation $\hat{d}(t)\left(V_g - V + V_D - IR_{on}\right)$ $D \hat{i}(t)$ $\hat{v}_{g}(t)$ $I \hat{d}(t)$ DR_{on} 200 $L \frac{d\hat{i}(t)}{dt}$ capacitor $D' \hat{v}(t)$ $D \hat{v}_o(t)$ $\hat{i}(t)$ eqn $C \, \frac{d\hat{v}(t)}{dt}$ $\frac{\hat{v}(t)}{R}$ $D' \hat{i}(t)$ $I \hat{d}(t)$ $\hat{v}(t)$ R

Fundamentals of Power Electronics

Complete small-signal ac equivalent circuit


Combine individual circuits to obtain

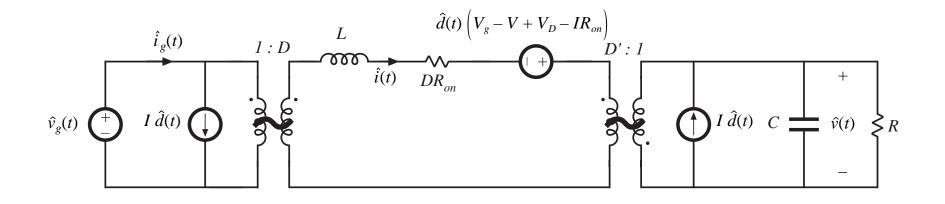

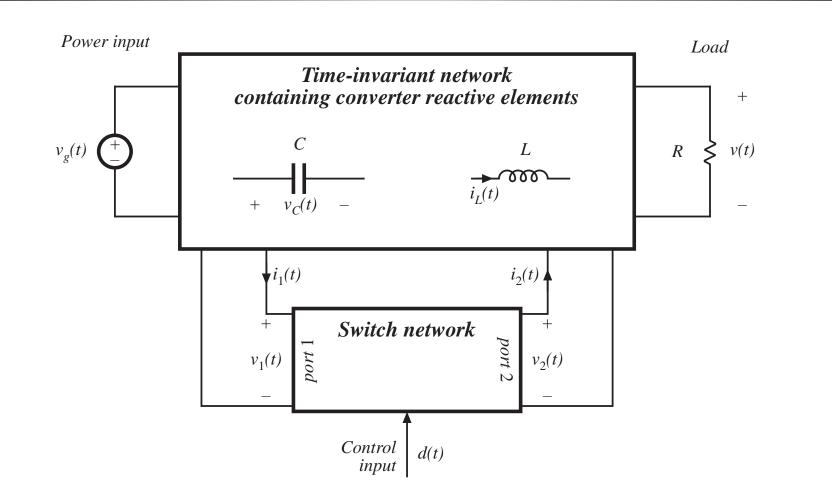7.5. Circuit Averaging and Averaged Switch Modeling


- Historically, circuit averaging was the first method known for modeling the small-signal ac behavior of CCM PWM converters
- It was originally thought to be difficult to apply in some cases
- There has been renewed interest in circuit averaging and its corrolary, averaged switch modeling, in the last decade
- Can be applied to a wide variety of converters
 - We will use it to model DCM, CPM, and resonant converters
 - Also useful for incorporating switching loss into ac model of CCM converters
 - Applicable to 3ø PWM inverters and rectifiers
 - Can be applied to phase-controlled rectifiers
- Rather than averaging and linearizing the converter state equations, the averaging and linearization operations are performed directly on the converter circuit

Separate switch network from remainder of converter



Fundamentals of Power Electronics

Boost converter example

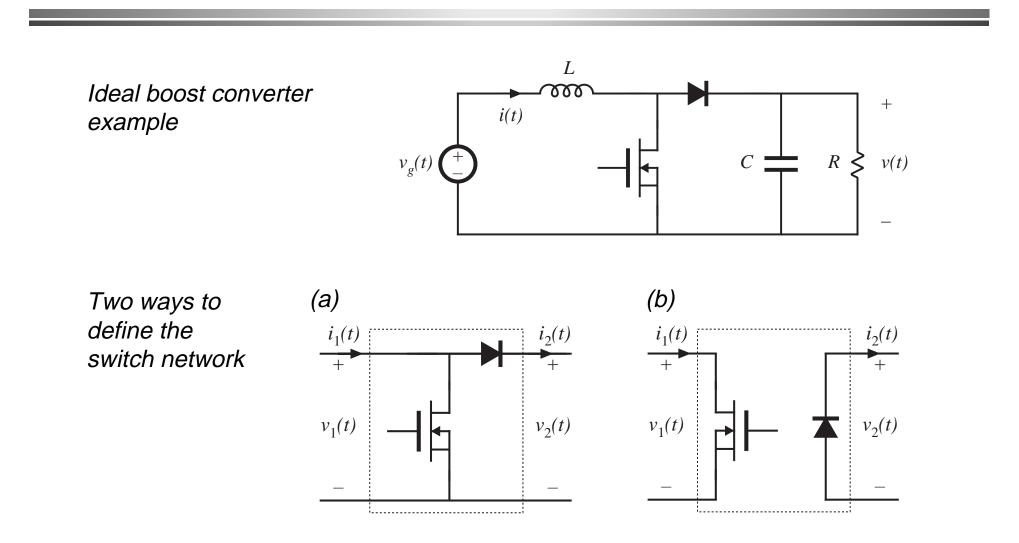

Fundamentals of Power Electronics

Discussion

- The number of ports in the switch network is less than or equal to the number of SPST switches
- Simple dc-dc case, in which converter contains two SPST switches: switch network contains two ports


The switch network terminal waveforms are then the port voltages and currents: $v_1(t)$, $i_1(t)$, $v_2(t)$, and $i_2(t)$.

Two of these waveforms can be taken as independent inputs to the switch network; the remaining two waveforms are then viewed as dependent outputs of the switch network.

 Definition of the switch network terminal quantities is not unique. Different definitions lead equivalent results having different forms

Boost converter example


Let's use definition (a):

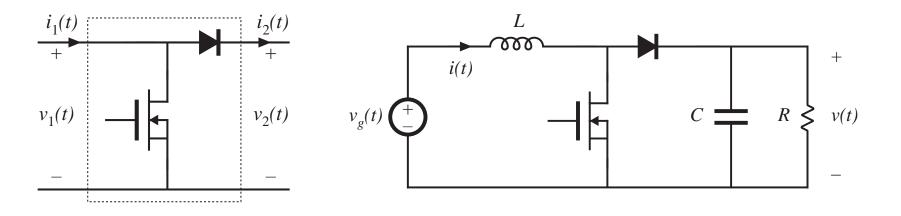

Since $i_1(t)$ and $v_2(t)$ coincide with the converter inductor current and output voltage, it is convenient to define these waveforms as the independent inputs to the switch network. The switch network dependent outputs are then $v_1(t)$ and $i_2(t)$.


Obtaining a time-invariant network: Modeling the terminal behavior of the switch network

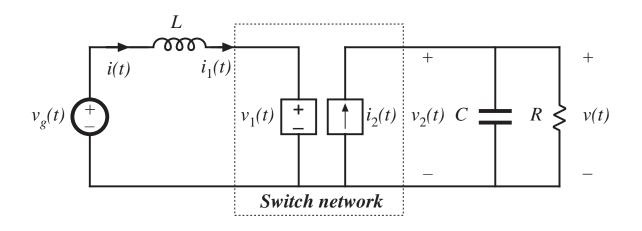
Replace the switch network with dependent sources, which correctly represent the dependent output waveforms of the switch network



Boost converter example

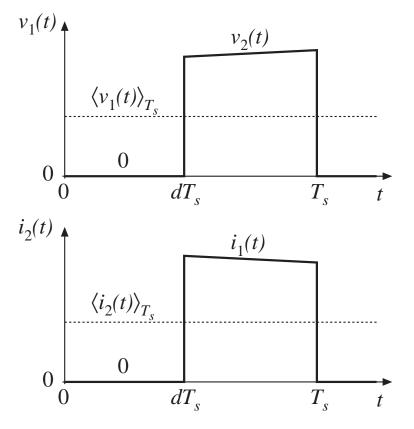Definition of dependent generator waveforms



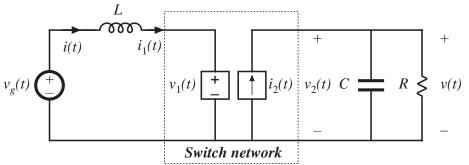


The waveforms of the dependent generators are defined to be identical to the actual terminal waveforms of the switch network.

The circuit is therefore electrical identical to the original converter.

So far, no approximations have been made.

The circuit averaging step

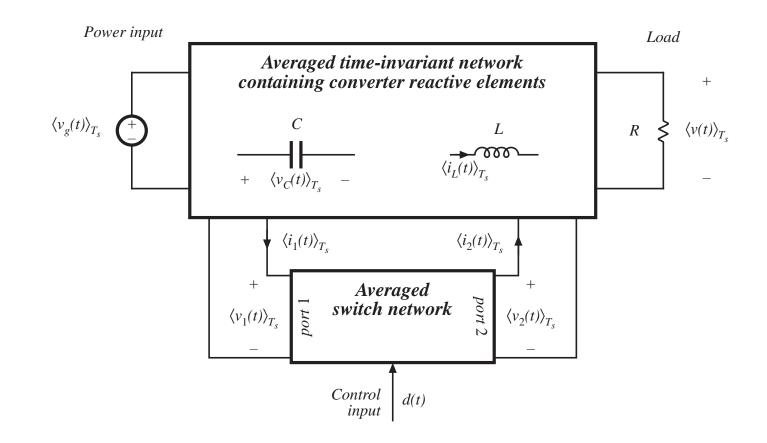Now average all waveforms over one switching period:




Fundamentals of Power Electronics

The basic assumption is made that the natural time constants of the converter are much longer than the switching period, so that the converter contains low-pass filtering of the switching harmonics. One may average the waveforms over an interval that is short compared to the system natural time constants, without significantly altering the system response. In particular, averaging over the switching period T_s removes the switching harmonics, while preserving the low-frequency components of the waveforms.


In practice, the only work needed for this step is to average the switch dependent waveforms.

Averaging step: boost converter example

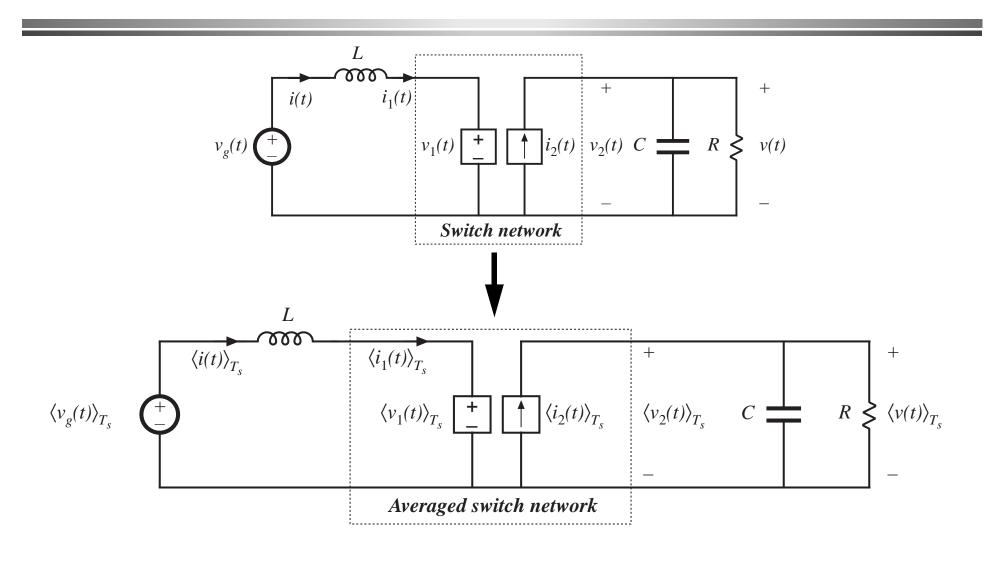


Fundamentals of Power Electronics

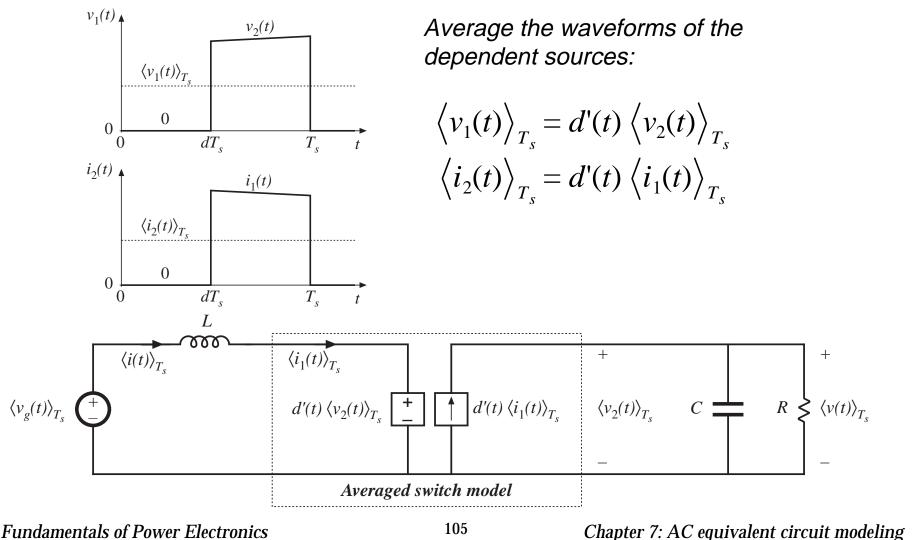Compute average values of dependent sources



Fundamentals of Power Electronics

Perturb and linearize

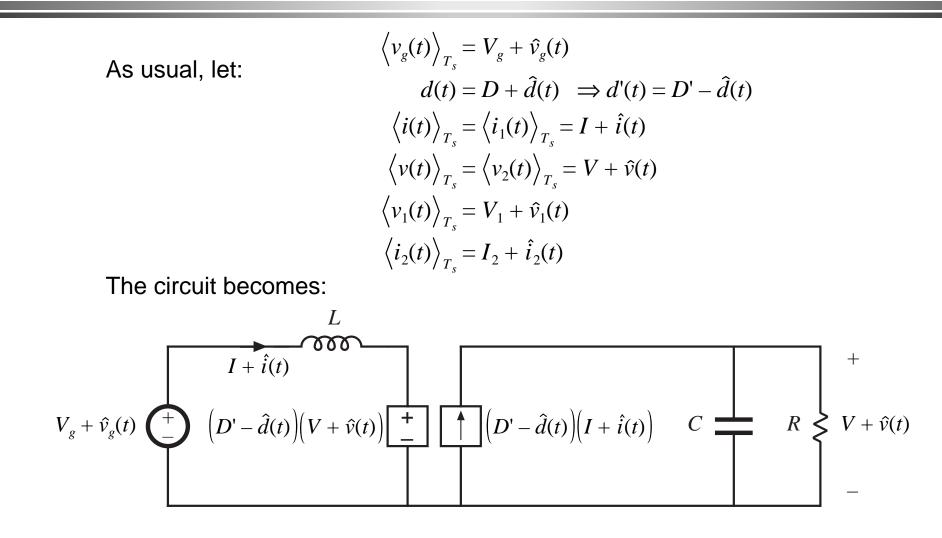


Fundamentals of Power Electronics

Dependent voltage source

$$\left(D' - \hat{d}(t)\right)\left(V + \hat{v}(t)\right) = D'\left(V + \hat{v}(t)\right) - V\hat{d}(t) - \hat{v}(t)\hat{d}(t)$$


nonlinear, 2nd order

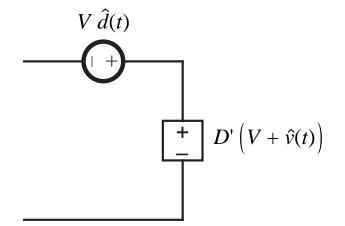


Dependent current source

$$\left(D' - \hat{d}(t)\right)\left(I + \hat{i}(t)\right) = D'\left(I + \hat{i}(t)\right) - I\hat{d}(t) - \hat{i}(t)\hat{d}(t)$$

nonlinear, 2nd order

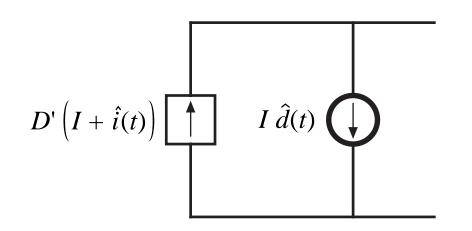

Linearized circuit-averaged model

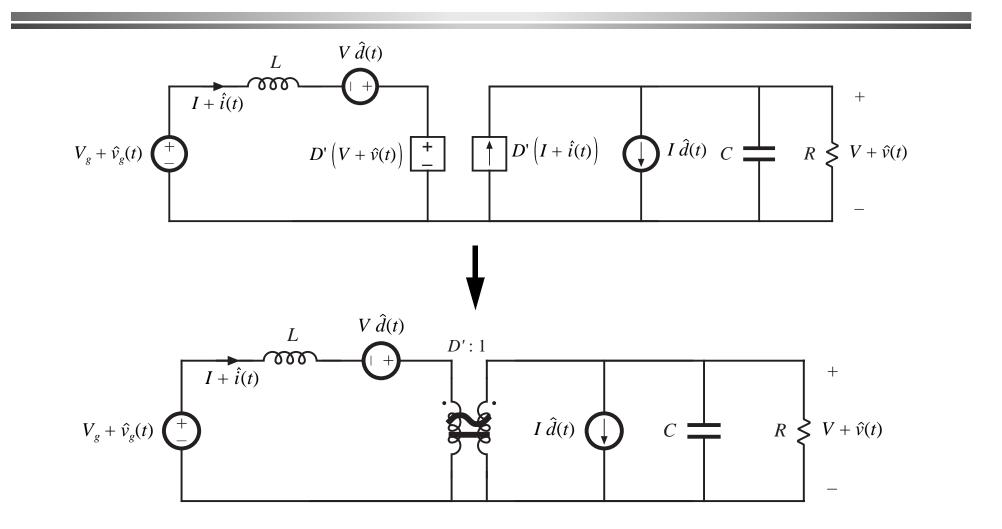

Fundamentals of Power Electronics

Summary: Circuit averaging method


Model the switch network with equivalent voltage and current sources, such that an equivalent time-invariant network is obtained

Average converter waveforms over one switching period, to remove the switching harmonics


Perturb and linearize the resulting low-frequency model, to obtain a small-signal equivalent circuit

Averaged switch modeling: CCM

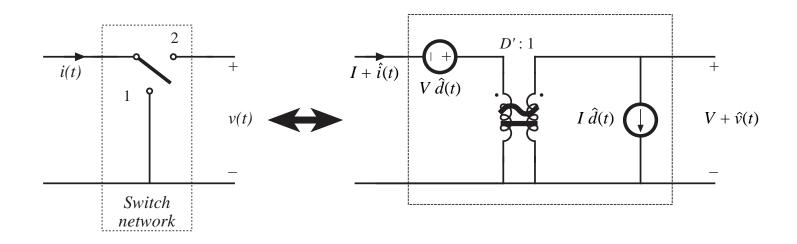Circuit averaging of the boost converter: in essence, the switch network was replaced with an effective ideal transformer and generators:



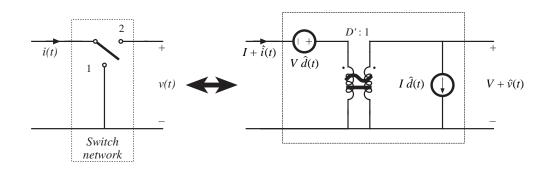Basic functions performed by switch network




For the boost example, we can conclude that the switch network performs two basic functions:

- Transformation of dc and small-signal ac voltage and current levels, according to the D':1 conversion ratio
- Introduction of ac voltage and current variations, drive by the control input duty cycle variations

Circuit averaging modifies only the switch network. Hence, to obtain a smallsignal converter model, we need only replace the switch network with its averaged model. Such a procedure is called *averaged switch modeling*.


Averaged switch modeling: Procedure

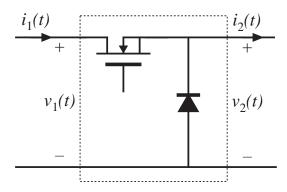1. Define a switch network and its terminal waveforms. For a simple transistor-diode switch network as in the buck, boost, etc., there are two ports and four terminal quantities: v_1 , i_1 , v_2 , i_2 . The switch network also contains a control input *d*. Buck example:




2. To derive an averaged switch model, express the average values of two of the terminal quantities, for example $\langle v_2 \rangle_{T_s}$ and $\langle i_1 \rangle_{T_s}$, as functions of the other average terminal quantities $\langle v_1 \rangle_{T_s}$ and $\langle i_1 \rangle_{T_s}$. $\langle v_2 \rangle_{T_s}$ and $\langle i_1 \rangle_{T_s}$ may also be functions of the control input *d*, but they should not be expressed in terms of other converter signals.

The basic buck-type CCM switch cell

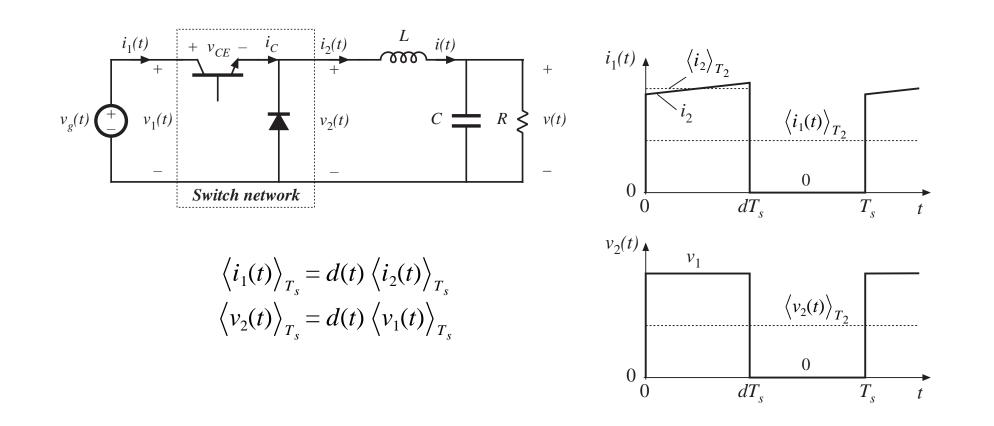


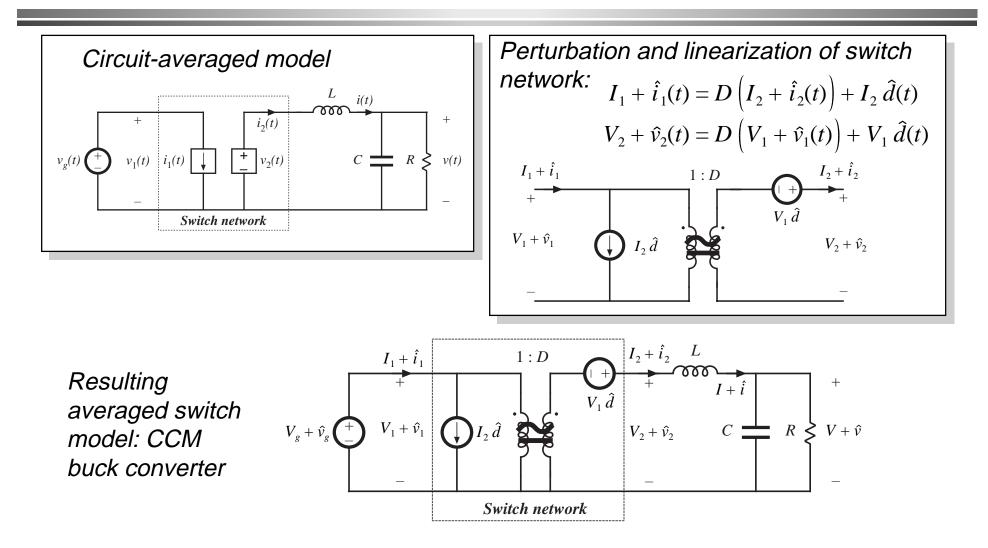Replacement of switch network by dependent sources, CCM buck example




Fundamentals of Power Electronics

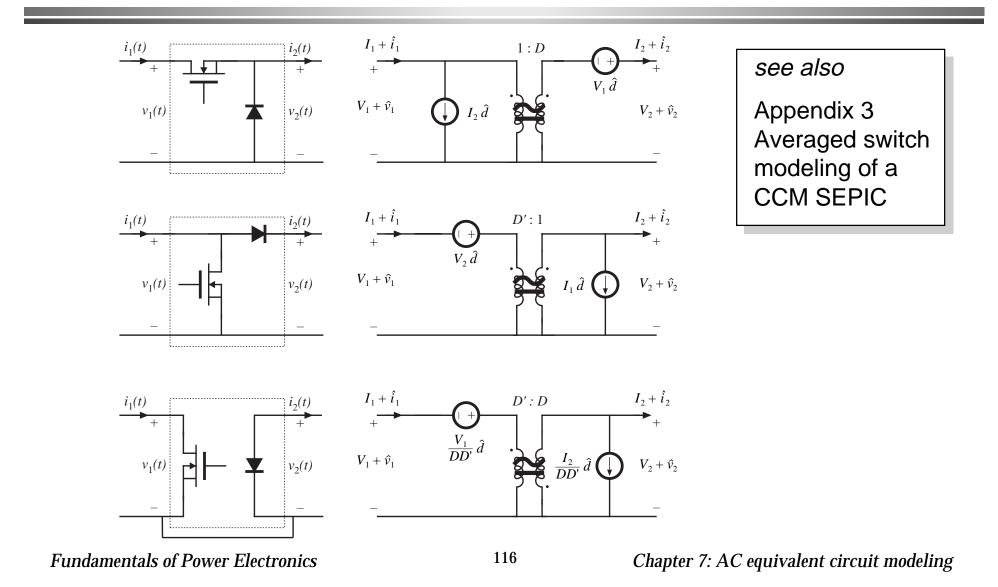Three basic switch networks, and their CCM dc and small-signal ac averaged switch models



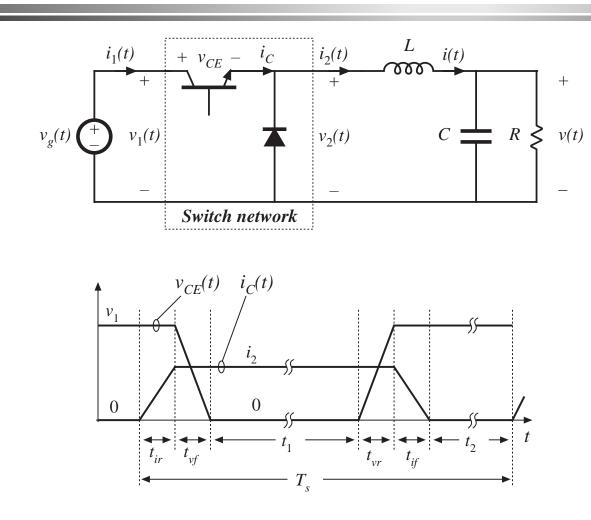Example: Averaged switch modeling of CCM buck converter, including switching loss




 $i_1(t) = i_C(t)$ $v_2(t) = v_1(t) - v_{CE}(t)$

Switch network terminal waveforms: v_1 , i_1 , v_2 , i_2 . To derive averaged switch model, express $\langle v_2 \rangle_{T_s}$ and $\langle i_1 \rangle_{T_s}$ as functions of $\langle v_1 \rangle_{T_s}$ and $\langle i_1 \rangle_{T_s} . \langle v_2 \rangle_{T_s}$ and $\langle i_1 \rangle_{T_s}$ may also be functions of the control input *d*, but they should not be expressed in terms of other converter signals.

Fundamentals of Power Electronics

Averaging $i_1(t)$

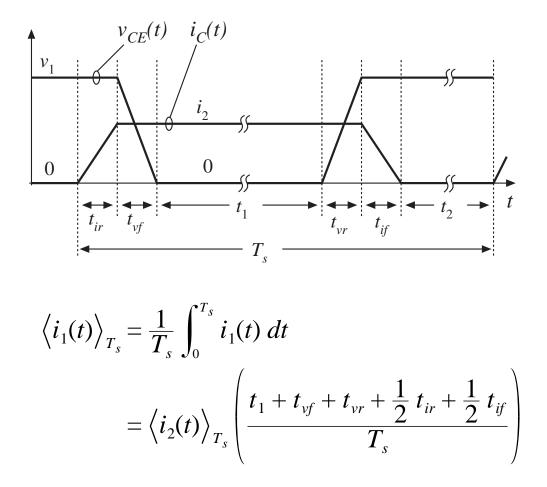

Fundamentals of Power Electronics

Expression for $\langle i_1(t) \rangle$

Given

$$\left\langle \dot{i}_{1}(t) \right\rangle_{T_{s}} = \frac{1}{T_{s}} \int_{0}^{T_{s}} \dot{i}_{1}(t) dt$$

$$= \left\langle \dot{i}_{2}(t) \right\rangle_{T_{s}} \left(\frac{t_{1} + t_{vf} + t_{vr} + \frac{1}{2} t_{ir} + \frac{1}{2} t_{if}}{T_{s}} \right)$$

Let


$$d = \left(\frac{t_1 + \frac{1}{2} t_{vf} + \frac{1}{2} t_{vr} + \frac{1}{2} t_{ir} + \frac{1}{2} t_{if}}{T_s}\right)$$
$$d_v = \left(\frac{t_{vf} + t_{vr}}{T_s}\right)$$
$$d_i = \left(\frac{t_{ir} + t_{if}}{T_s}\right)$$

Then we can write

$$\left\langle i_1(t) \right\rangle_{T_s} = \left\langle i_2(t) \right\rangle_{T_s} \left(d + \frac{1}{2} d_v \right)$$


Fundamentals of Power Electronics

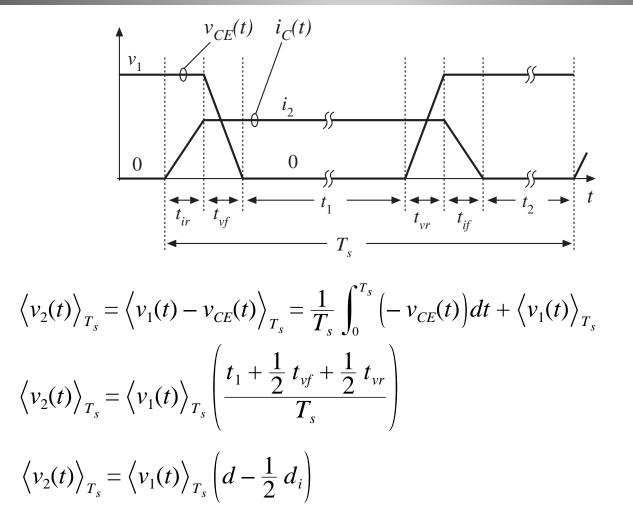Averaging the switch network output voltage $v_2(t)$




Fundamentals of Power Electronics

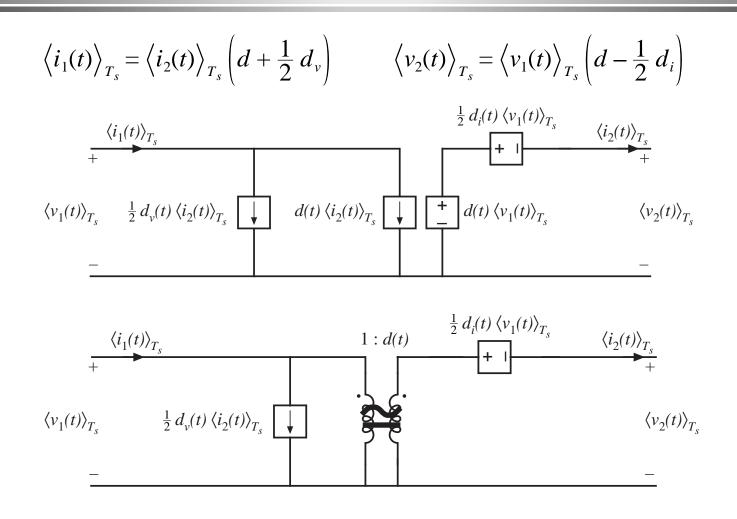Construction of large-signal averaged-switch model



Fundamentals of Power Electronics

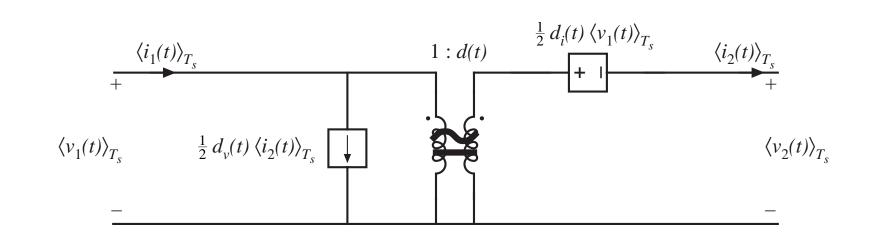
Switching loss predicted by averaged switch model



$$P_{sw} = \frac{1}{2} \left(d_v + d_i \right) \left\langle i_2(t) \right\rangle_{T_s} \left\langle v_1(t) \right\rangle_{T_s}$$

Fundamentals of Power Electronics

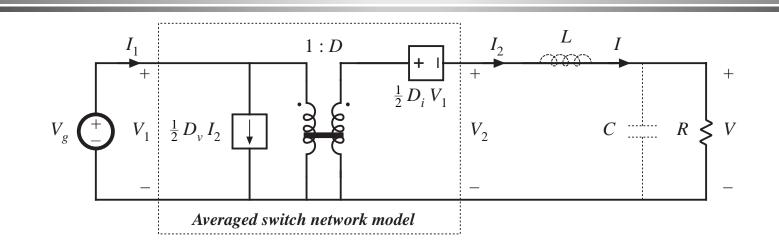Solution of averaged converter model in steady state



Output voltage:

$$V = \left(D - \frac{1}{2}D_i\right)V_g = DV_g\left(1 - \frac{D_i}{2D}\right)$$

Efficiency calcuation: $P_{in} = V_g I_1 = V_1 I_2 \left(D + \frac{1}{2} D_v \right)$ $P_{out} = V I_2 = V_1 I_2 \left(D - \frac{1}{2} D_i \right)$ $\eta = \frac{P_{out}}{P_{in}} = \frac{\left(D - \frac{1}{2} D_i \right)}{\left(D + \frac{1}{2} D_v \right)} = \frac{\left(1 - \frac{D_i}{2D} \right)}{\left(1 + \frac{D_v}{2D} \right)}$

Fundamentals of Power Electronics

7.6. The canonical circuit model

All PWM CCM dc-dc converters perform the same basic functions:

- Transformation of voltage and current levels, ideally with 100% efficiency
- Low-pass filtering of waveforms
- Control of waveforms by variation of duty cycle

Hence, we expect their equivalent circuit models to be qualitatively similar.

Canonical model:

- A standard form of equivalent circuit model, which represents the above physical properties
- Plug in parameter values for a given specific converter


7.6.1. Development of the canonical circuit model

1. Transformation of dc Converter model voltage and current 1: M(D)levels + modeled as in Chapter 3 with ideal V_{g} VR dc transformer • effective turns ratio M(D)• can refine dc model by addition of effective loss D elements, as in Power Control Load Chapter 3 input input

Fundamentals of Power Electronics

Steps in the development of the canonical circuit model

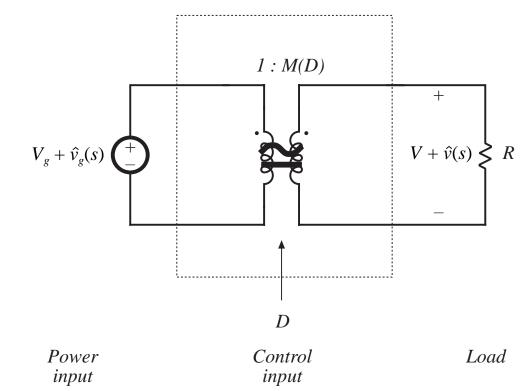- 2. Ac variations in $v_g(t)$ induce ac variations in v(t)
- these variations are also transformed by the conversion ratio M(D)




Steps in the development of the canonical circuit model

1: M(D)

 $Z_{ei}(s)$

- 3. Converter must contain an effective lowpass filter characteristic
- necessary to filter switching ripple
- also filters ac • variations
- effective filter input elements may not coincide with actual element values, but can also depend on operating point

 $V_g + \hat{v}_g(s)$

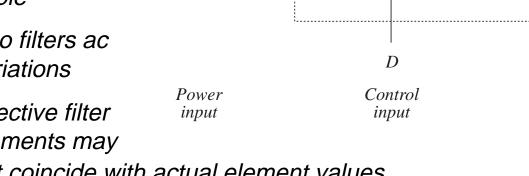

Load

+

 $V + \hat{v}(s) \leq R$

 $Z_{eo}(s)$

Fundamentals of Power Electronics


 $H_{\rho}(s)$

Effective

low-pass


filter

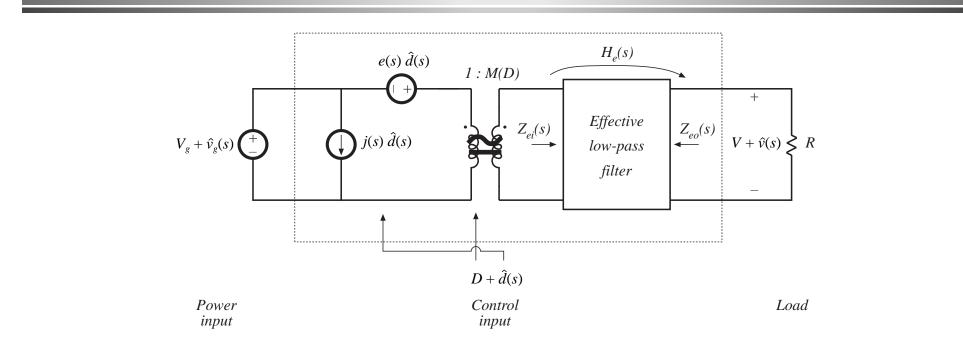Steps in the development of the canonical circuit model



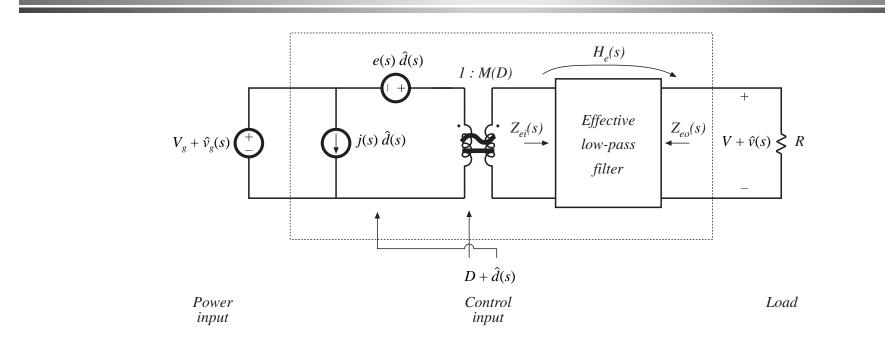- 4. Control input variations also induce ac variations in converter waveforms
- Independent sources represent effects of variations in duty cycle
- Can push all sources to input side as shown. Sources may then become frequency-dependent

Transfer functions predicted by canonical model



Line-to-output transfer function:


Control-to-output transfer function:

$$G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} = M(D) H_e(s)$$
$$G_{vd}(s) = \frac{\hat{v}(s)}{\hat{d}(s)} = e(s) M(D) H_e(s)$$

Fundamentals of Power Electronics

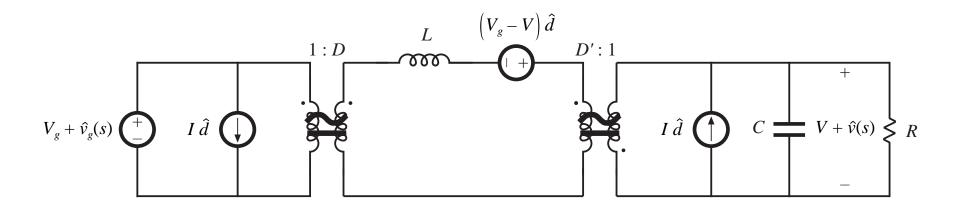
7.6.2. Example: manipulation of the buck-boost converter model into canonical form

Small-signal ac model of the buck-boost converter



- Push independent sources to input side of transformers
- Push inductor to output side of transformers
- Combine transformers

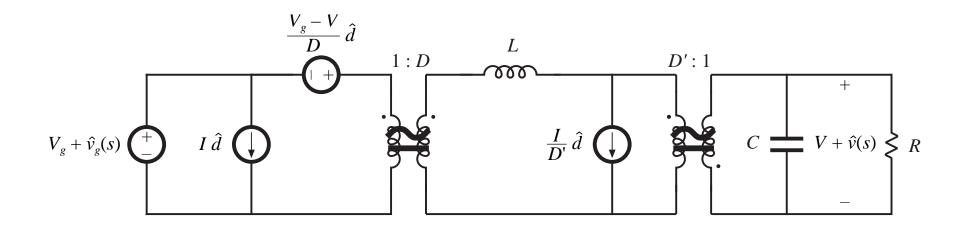
Push voltage source through 1:D transformer Move current source through D':1 transformer




How to move the current source past the inductor:

Break ground connection of current source, and connect to node A instead.

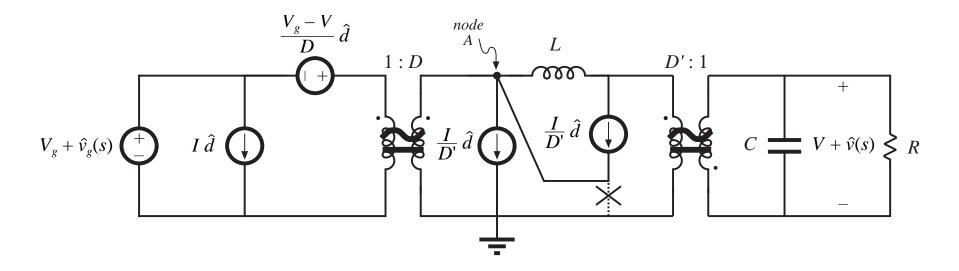Connect an identical current source from node A to ground, so that the node equations are unchanged.



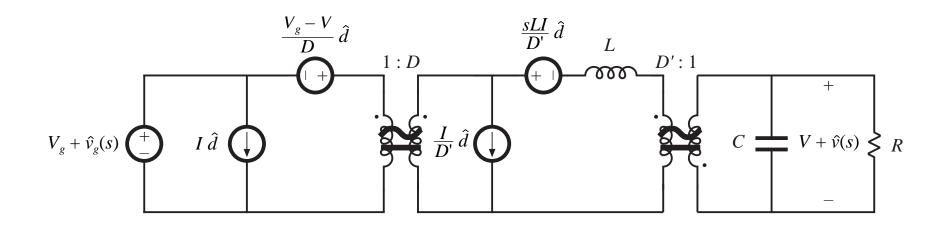The parallel-connected current source and inductor can now be replaced by a Thevenin-equivalent network:




Now push current source through 1:D transformer.

Push current source past voltage source, again by:

Breaking ground connection of current source, and connecting to node B instead.

Connecting an identical current source from node B to ground, so that the node equations are unchanged.

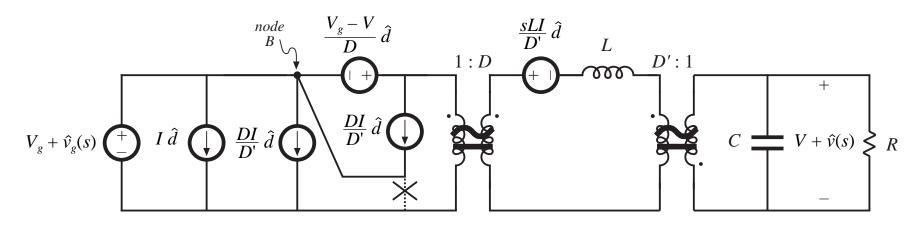Note that the resulting parallel-connected voltage and current sources are equivalent to a single voltage source.




Fundamentals of Power Electronics

Step 5: final result

Push voltage source through 1:D transformer, and combine with existing input-side transformer.

Combine series-connected transformers.

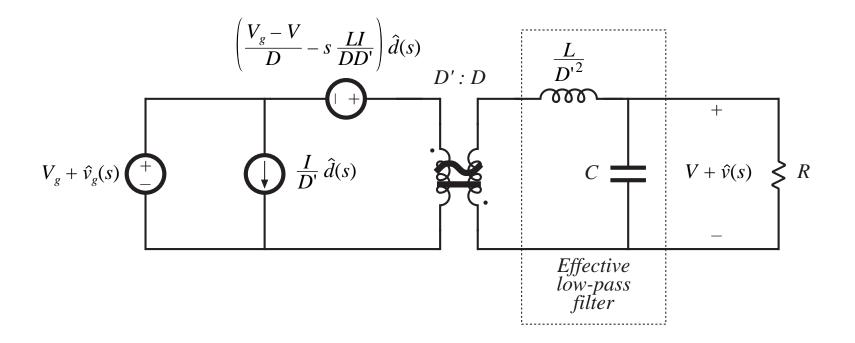

Fundamentals of Power Electronics

Coefficient of control-input voltage generator

Voltage source coefficient is:

$$e(s) = \frac{V_g + V}{D} - \frac{s LI}{D D'}$$

Simplification, using dc relations, leads to

$$e(s) = -\frac{V}{D^2} \left(1 - \frac{s DL}{D'^2 R} \right)$$

Pushing the sources past the inductor causes the generator to become frequency-dependent.

7.6.3. Canonical circuit parameters for some common converters

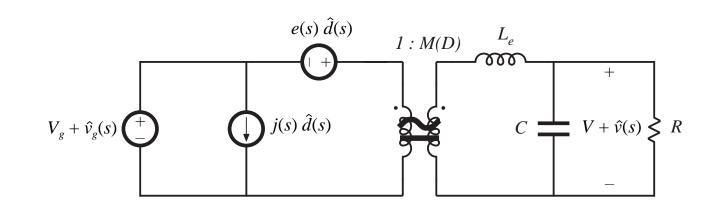


Table 7.1. Canonical model parameters for the ideal buck, boost, and buck-boost converters


Converter	M(D)	L_e	e(s)	j(s)
Buck	D	L	$\frac{V}{D^2}$	$\frac{V}{R}$
Boost	$\frac{1}{D'}$	$rac{L}{D'^2}$	$V\left(1-\frac{s\ L}{D'^2\ R}\right)$	$\frac{V}{D'^2 R}$
Buck-boost	$-\frac{D}{D'}$	$\frac{L}{D^{\prime 2}}$	$-\frac{V}{D^2}\left(1-\frac{sDL}{D'^2R}\right)$	$-\frac{V}{D^{\prime 2}R}$

Fundamentals of Power Electronics

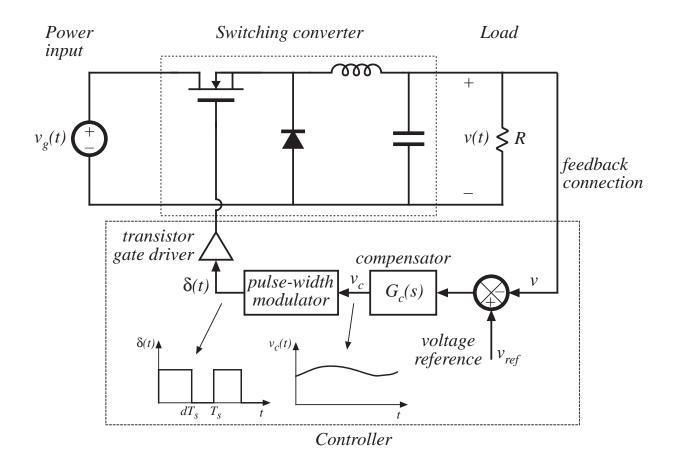
7.7. Modeling the pulse-width modulator

Pulse-width modulator converts voltage signal $v_c(t)$ into duty cycle signal d(t).

What is the relation between $v_c(t)$ and d(t)?



A simple pulse-width modulator

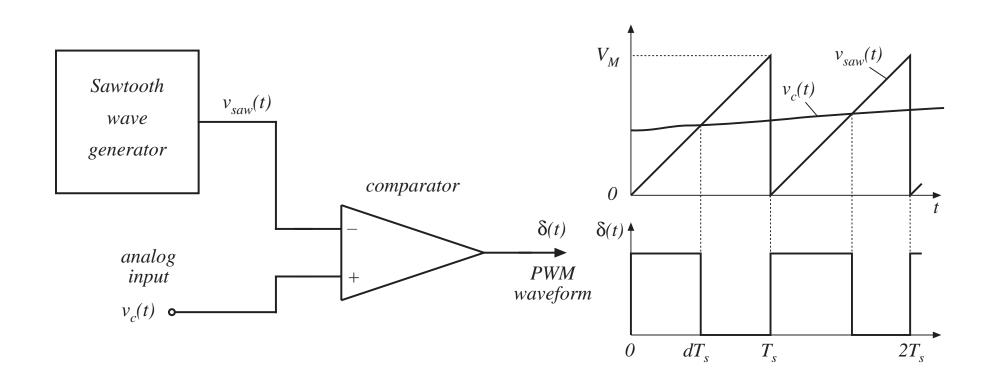


Equation of pulse-width modulator


For a linear sawtooth waveform:

$$d(t) = \frac{v_c(t)}{V_M} \quad \text{for } 0 \le v_c(t) \le V_M$$

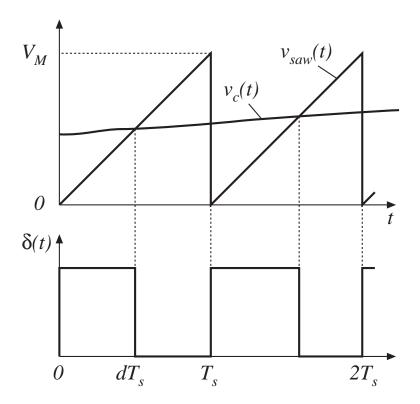So d(t) is a linear function of $v_c(t)$.



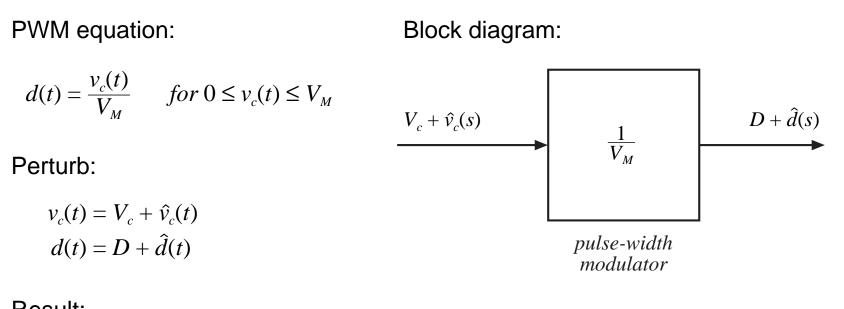Perturbed equation of pulse-width modulator



Result:

$$D + \hat{d}(t) = \frac{V_c + \hat{v}_c(t)}{V_M}$$

Dc and ac relations:

$$D = \frac{V_c}{V_M}$$
$$\hat{d}(t) = \frac{\hat{v}_c(t)}{V_M}$$

Fundamentals of Power Electronics

Sampling in the pulse-width modulator

The input voltage is a continuous function of time, but there can be only one discrete value of the duty cycle for each switching period.

Therefore, the pulse-

width modulator

 v_c $\frac{1}{V_M}$ sampler d f_s f_s

samples the control waveform, with sampling rate equal to the switching frequency.

In practice, this limits the useful frequencies of ac variations to values much less than the switching frequency. Control system bandwidth must be sufficiently less than the Nyquist rate $f_s/2$. Models that do not account for sampling are accurate only at frequencies much less than $f_s/2$.

Fundamentals of Power Electronics

7.8. Summary of key points

- The CCM converter analytical techniques of Chapters 2 and 3 can be extended to predict converter ac behavior. The key step is to average the converter waveforms over one switching period. This removes the switching harmonics, thereby exposing directly the desired dc and low-frequency ac components of the waveforms. In particular, expressions for the averaged inductor voltages, capacitor currents, and converter input current are usually found.
- 2. Since switching converters are nonlinear systems, it is desirable to construct small-signal linearized models. This is accomplished by perturbing and linearizing the averaged model about a quiescent operating point.
- 3. Ac equivalent circuits can be constructed, in the same manner used in Chapter 3 to construct dc equivalent circuits. If desired, the ac equivalent circuits may be refined to account for the effects of converter losses and other nonidealities.

Summary of key points

- 4. The state-space averaging method of section 7.4 is essentially the same as the basic approach of section 7.2, except that the formality of the state-space network description is used. The general results are listed in section 7.4.2.
- 5. The circuit averaging technique also yields equivalent results, but the derivation involves manipulation of circuits rather than equations. Switching elements are replaced by dependent voltage and current sources, whose waveforms are defined to be identical to the switch waveforms of the actual circuit. This leads to a circuit having a time-invariant topology. The waveforms are then averaged to remove the switching ripple, and perturbed and linearized about a quiescent operating point to obtain a small-signal model.

Summary of key points

6. When the switches are the only time-varying elements in the converter, then circuit averaging affects only the switch network. The converter model can then be derived by simply replacing the switch network with its averaged model. Dc and small-signal ac models of several common CCM switch networks are listed in section 7.5.4. Switching losses can also be modeled using this approach.

7. The canonical circuit describes the basic properties shared by all dc-dc PWM converters operating in the continuous conduction mode. At the heart of the model is the ideal 1:M(D) transformer, introduced in Chapter 3 to represent the basic dc-dc conversion function, and generalized here to include ac variations. The converter reactive elements introduce an effective low-pass filter into the network. The model also includes independent sources which represent the effect of duty cycle variations. The parameter values in the canonical models of several basic converters are tabulated for easy reference.

Summary of key points

8. The conventional pulse-width modulator circuit has linear gain, dependent on the slope of the sawtooth waveform, or equivalently on its peak-to-peak magnitude.

Chapter 8. Converter Transfer Functions

8.1. Review of Bode plots

- 8.1.1. Single pole response
- 8.1.2. Single zero response
- 8.1.3. Right half-plane zero
- 8.1.4. Frequency inversion
- 8.1.5. Combinations
- 8.1.6. Double pole response: resonance
- 8.1.7. The low-Q approximation
- 8.1.8. Approximate roots of an arbitrary-degree polynomial

8.2. Analysis of converter transfer functions

- 8.2.1. Example: transfer functions of the buck-boost converter
- 8.2.2. Transfer functions of some basic CCM converters
- 8.2.3. Physical origins of the right half-plane zero in converters

Converter Transfer Functions

8.3. Graphical construction of converter transfer functions

- 8.3.1. Series impedances: addition of asymptotes
- 8.3.2. Parallel impedances: inverse addition of asymptotes
- 8.3.3. Another example
- 8.3.4. Voltage divider transfer functions: division of asymptotes
- 8.4. Measurement of ac transfer functions and impedances
- 8.5. Summary of key points

Design-oriented analysis

How to approach a real (and hence, complicated) system

Problems:

Complicated derivations

Long equations

Algebra mistakes

Design objectives:

Obtain physical insight which leads engineer to synthesis of a good design

Obtain simple equations that can be inverted, so that element values can be chosen to obtain desired behavior. Equations that cannot be inverted are useless for design!

Design-oriented analysis is a structured approach to analysis, which attempts to avoid the above problems

Some elements of design-oriented analysis, discussed in this chapter

- Writing transfer functions in normalized form, to directly expose salient features
- Obtaining simple analytical expressions for asymptotes, corner frequencies, and other salient features, allows element values to be selected such that a given desired behavior is obtained
- Use of inverted poles and zeroes, to refer transfer function gains to the most important asymptote
- Analytical approximation of roots of high-order polynomials
- Graphical construction of Bode plots of transfer functions and polynomials, to

avoid algebra mistakes

approximate transfer functions

obtain insight into origins of salient features

8.1. Review of Bode plots

Decibels	Table 8.1. Expressing magnitudes in decibels		
$\left\ G \right\ _{\mathrm{dB}} = 20 \log_{10} \left(\left\ G \right\ \right)$	Actual magnitude	Magnitude in dB	
	1/2	- 6dB	
Decibels of quantities having	1	0 dB	
units (impedance example): normalize before taking log	2	6 dB	
	5 = 10/2	20 dB - 6 dB = 14 dB	
$\left\ Z \right\ _{\mathrm{dB}} = 20 \log_{10} \left(\frac{\left\ Z \right\ }{R_{base}} \right)$	10	20dB	
(base)	$1000 = 10^3$	$3 \cdot 20$ dB = 60 dB	


5Ω is equivalent to 14dB with respect to a base impedance of $R_{base} = 1\Omega$, also known as 14dBΩ.

 $60dB\mu A$ is a current 60dB greater than a base current of $1\mu A$, or 1mA.

5


Bode plot of *f*ⁿ

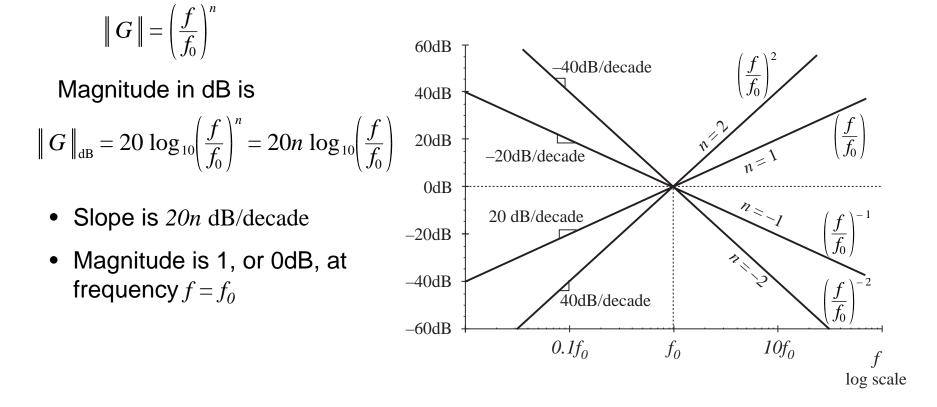Bode plots are effectively log-log plots, which cause functions which vary as f^n to become linear plots. Given:



8.1.1. Single pole response

Simple R-C example

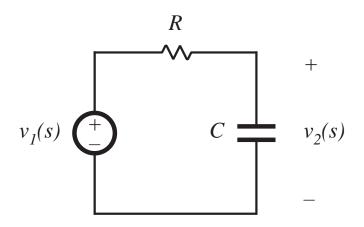

Transfer function is

$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R}$$

Express as rational fraction:

$$G(s) = \frac{1}{1 + sRC}$$

This coincides with the normalized form

$$G(s) = \frac{1}{\left(1 + \frac{s}{\omega_0}\right)}$$

with

$$\omega_0 = \frac{1}{RC}$$

Chapter 8: Converter Transfer Functions

$G(j\omega)$ and $|| G(j\omega) ||$

Let
$$s = j\omega$$
:

$$G(j\omega) = \frac{1}{\left(1 + j\frac{\omega}{\omega_0}\right)} = \frac{1 - j\frac{\omega}{\omega_0}}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$
Magnitude is


$$\|G(j\omega)\| = \sqrt{\left[\operatorname{Re}\left(G(j\omega)\right)\right]^2 + \left[\operatorname{Im}\left(G(j\omega)\right)\right]^2}$$

$$= \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$
Magnitude in dB:

$$\left\| G(j\omega) \right\|_{\rm dB} = -20 \log_{10} \left(\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2} \right) \, \rm dB$$


Fundamentals of Power Electronics

Asymptotic behavior: low frequency

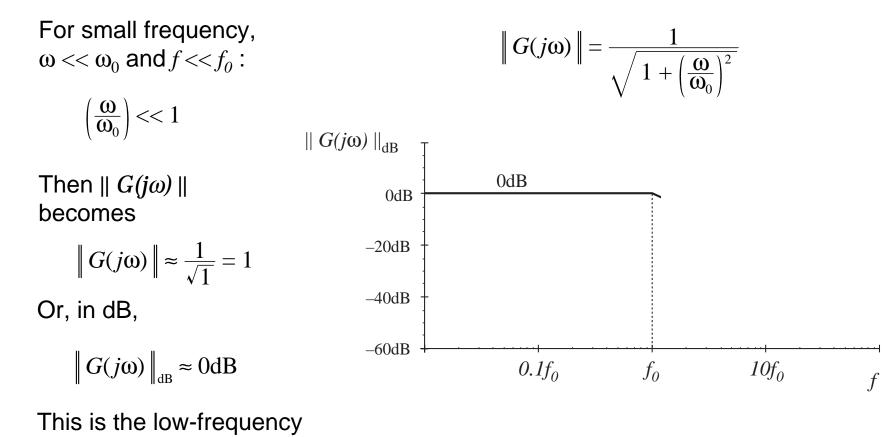

asymptote of $|| G(j\omega) ||$

Asymptotic behavior: high frequency

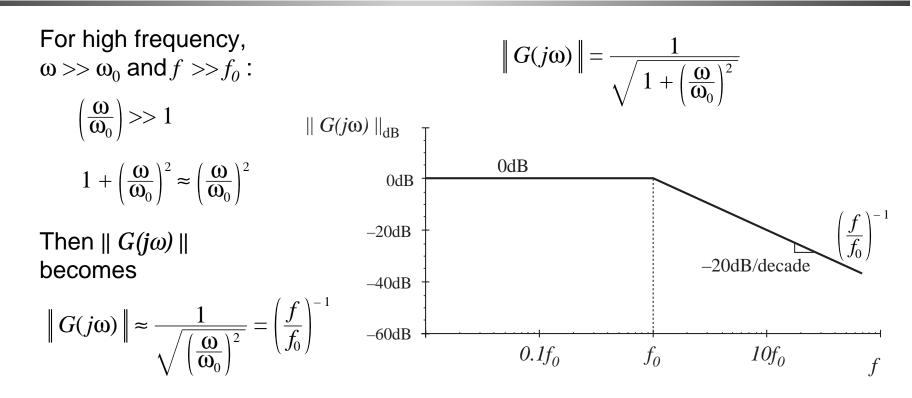

The high-frequency asymptote of $|| G(j\omega) ||$ varies as f^{-1} . Hence, n = -1, and a straight-line asymptote having a slope of -20dB/decade is obtained. The asymptote has a value of 1 at $f = f_0$.

Fundamentals of Power Electronics

Deviation of exact curve near
$$f = f_0$$

Evaluate exact magnitude:

$$at f = f_0:$$


$$\left\| G(j\omega_0) \right\| = \frac{1}{\sqrt{1 + \left(\frac{\omega_0}{\omega_0}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\left\| G(j\omega_0) \right\|_{dB} = -20 \log_{10} \left(\sqrt{1 + \left(\frac{\omega_0}{\omega_0}\right)^2} \right) \approx -3 \text{ dB}$$

at $f = 0.5 f_0$ and $2f_0$:


Similar arguments show that the exact curve lies 1dB below the asymptotes.

Summary: magnitude

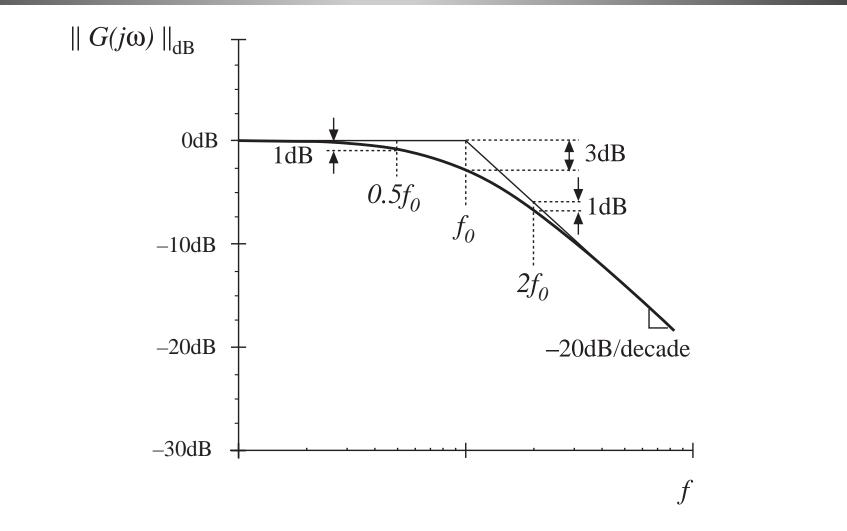

Fundamentals of Power Electronics

Phase of $G(j\omega)$

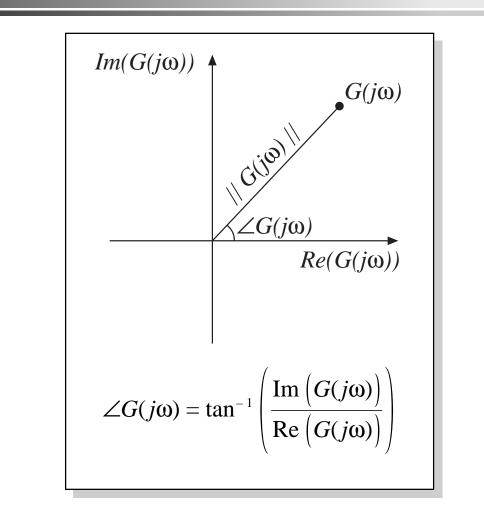


$$G(j\omega) = \frac{1}{\left(1 + j \frac{\omega}{\omega_0}\right)} = \frac{1 - j \frac{\omega}{\omega_0}}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

$$\angle G(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

Fundamentals of Power Electronics

Phase of $G(j\omega)$

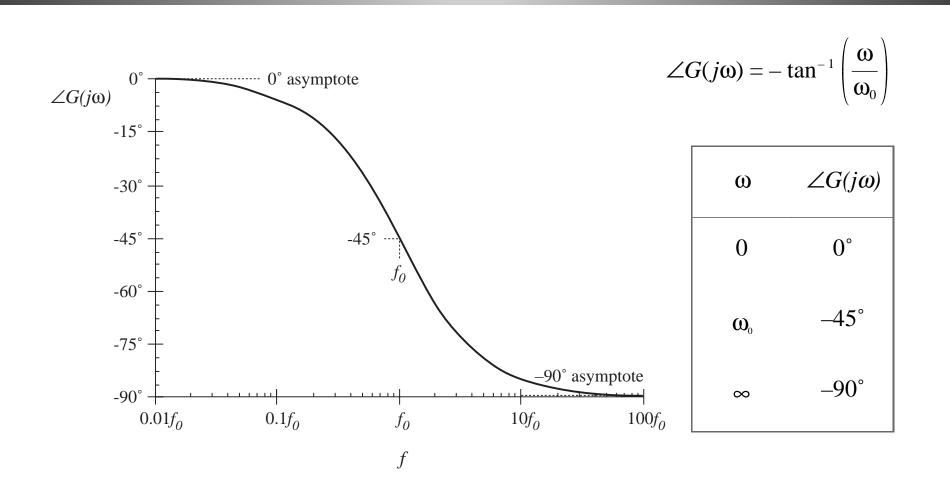

Fundamentals of Power Electronics

Phase asymptotes

Low frequency: 0°

High frequency: -90°

Low- and high-frequency asymptotes do not intersect


Hence, need a midfrequency asymptote

Try a midfrequency asymptote having slope identical to actual slope at the corner frequency f_0 . One can show that the asymptotes then intersect at the break frequencies

$$f_a = f_0 \ e^{-\pi/2} \approx f_0 / 4.81$$


 $f_b = f_0 \ e^{\pi/2} \approx 4.81 \ f_0$

Phase asymptotes

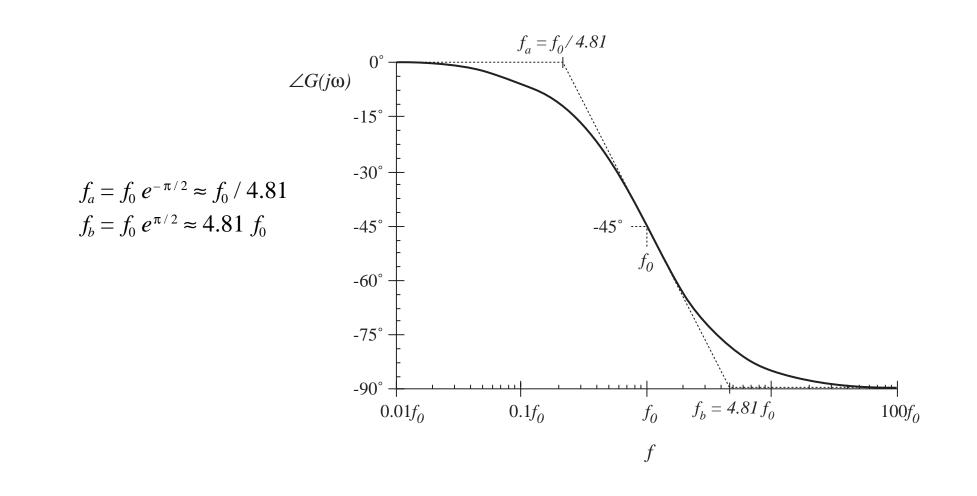


Fundamentals of Power Electronics

Phase asymptotes: a simpler choice

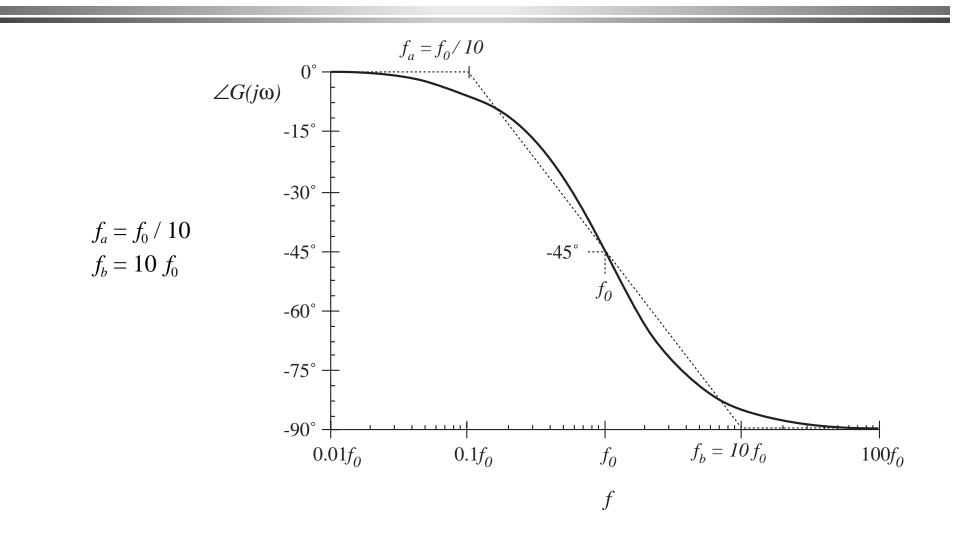

Fundamentals of Power Electronics

Summary: Bode plot of real pole

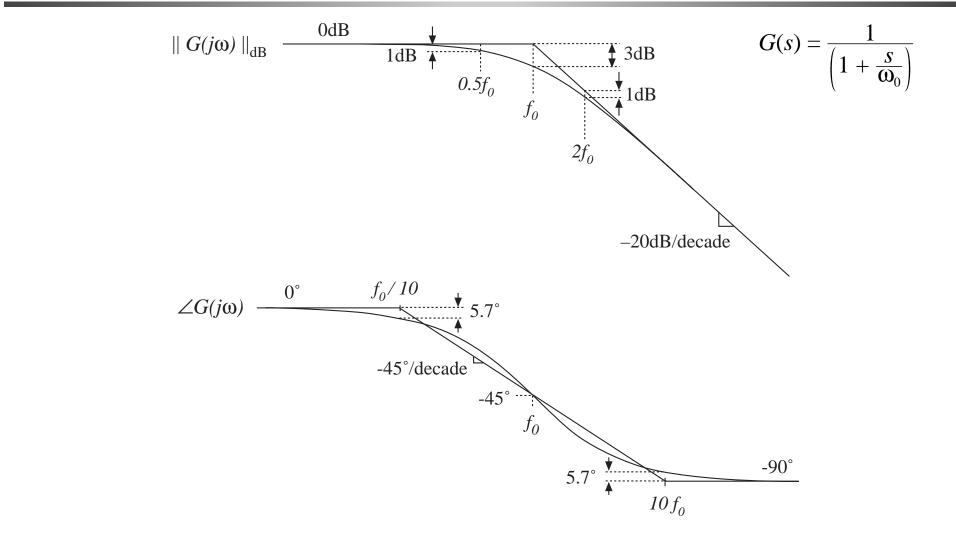

Fundamentals of Power Electronics

8.1.2. Single zero response

Normalized form:

$$G(s) = \left(1 + \frac{s}{\omega_0}\right)$$

Magnitude:

$$\left\| G(j\omega) \right\| = \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

Use arguments similar to those used for the simple pole, to derive asymptotes:

0dB at low frequency, $\omega \ll \omega_0$


+20dB/decade slope at high frequency, $\omega >> \omega_0$

Phase:

$$\angle G(j\omega) = \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

—with the exception of a missing minus sign, same as simple pole

Summary: Bode plot, real zero

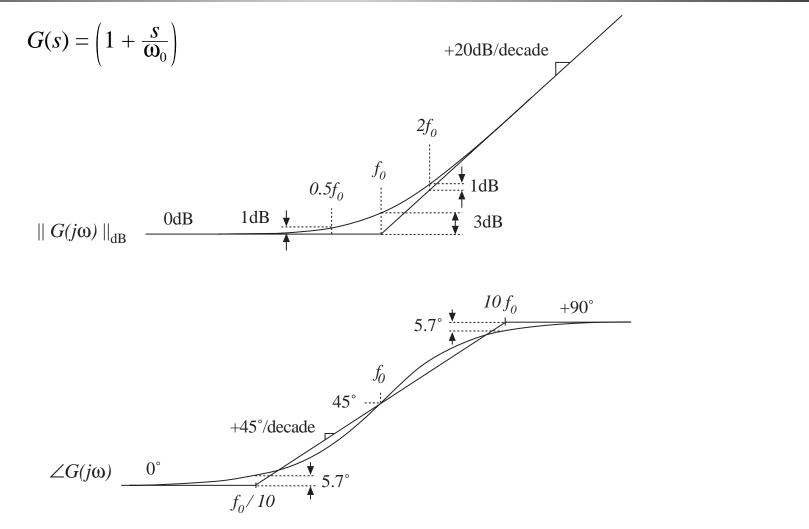

Fundamentals of Power Electronics

8.1.3. Right half-plane zero

Normalized form:

$$G(s) = \left(1 - \frac{s}{\omega_0}\right)$$

Magnitude:

$$\left\| G(j\omega) \right\| = \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

—same as conventional (left half-plane) zero. Hence, magnitude asymptotes are identical to those of LHP zero.


Phase:

$$\angle G(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

-same as real pole.

The RHP zero exhibits the magnitude asymptotes of the LHP zero, and the phase asymptotes of the pole

Summary: Bode plot, RHP zero

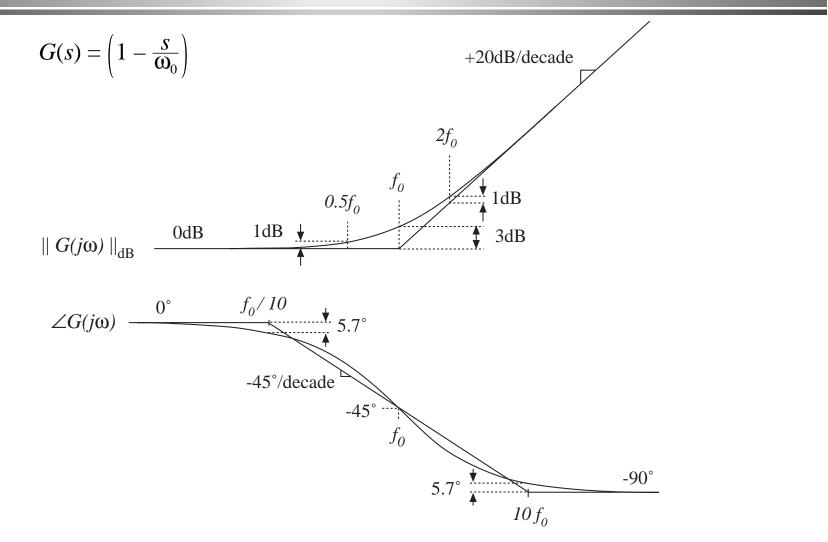

Fundamentals of Power Electronics

8.1.4. Frequency inversion

Reversal of frequency axis. A useful form when describing mid- or high-frequency flat asymptotes. Normalized form, inverted pole:


$$G(s) = \frac{1}{\left(1 + \frac{\omega_0}{s}\right)}$$

An algebraically equivalent form:

$$G(s) = \frac{\left(\frac{s}{\omega_0}\right)}{\left(1 + \frac{s}{\omega_0}\right)}$$

The inverted-pole format emphasizes the high-frequency gain.

Asymptotes, inverted pole

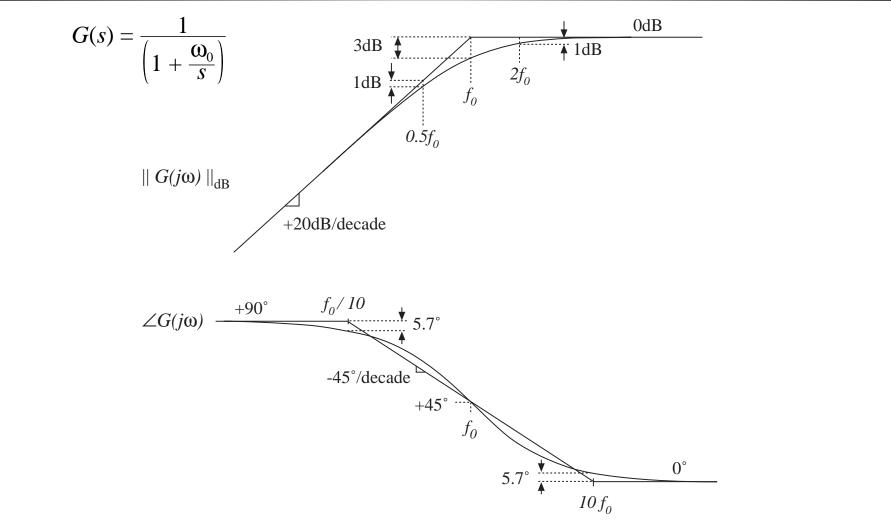

Fundamentals of Power Electronics

Inverted zero

Normalized form, inverted zero:


$$G(s) = \left(1 + \frac{\omega_0}{s}\right)$$

An algebraically equivalent form:

$$G(s) = \frac{\left(1 + \frac{s}{\omega_0}\right)}{\left(\frac{s}{\omega_0}\right)}$$

Again, the inverted-zero format emphasizes the high-frequency gain.

Asymptotes, inverted zero

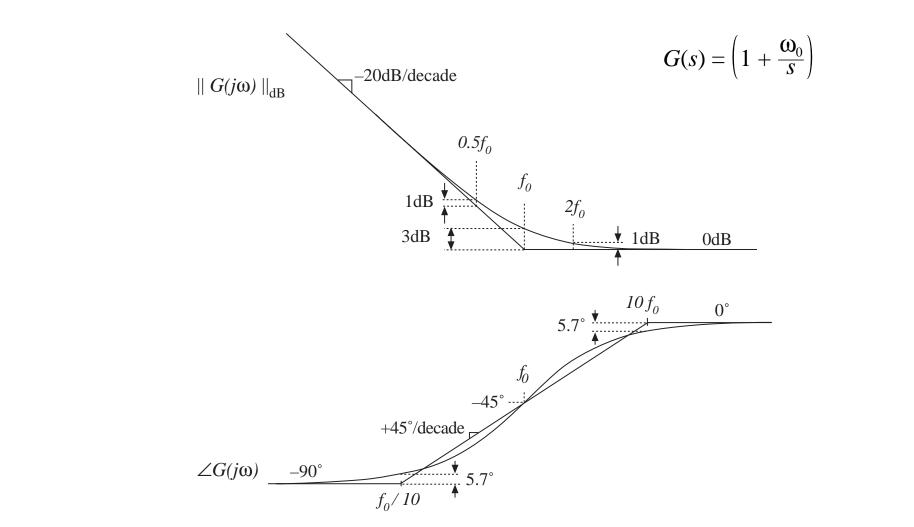

Fundamentals of Power Electronics

Suppose that we have constructed the Bode diagrams of two complex-values functions of frequency, $G_1(\omega)$ and $G_2(\omega)$. It is desired to construct the Bode diagram of the product, $G_3(\omega) = G_1(\omega) G_2(\omega)$.

Express the complex-valued functions in polar form:

 $G_{1}(\omega) = R_{1}(\omega) e^{j\theta_{1}(\omega)}$ $G_{2}(\omega) = R_{2}(\omega) e^{j\theta_{2}(\omega)}$ $G_{3}(\omega) = R_{3}(\omega) e^{j\theta_{3}(\omega)}$

The product $G_3(\omega)$ can then be written

 $G_3(\omega) = G_1(\omega) \ G_2(\omega) = R_1(\omega) \ e^{j\theta_1(\omega)} \ R_2(\omega) \ e^{j\theta_2(\omega)}$

$$G_3(\omega) = \left(R_1(\omega) \ R_2(\omega)\right) e^{j(\theta_1(\omega) + \theta_2(\omega))}$$

Fundamentals of Power Electronics

Combinations

$$G_3(\omega) = \left(R_1(\omega) \ R_2(\omega)\right) e^{j(\theta_1(\omega) + \theta_2(\omega))}$$

The composite phase is

$$\theta_3(\omega) = \theta_1(\omega) + \theta_2(\omega)$$

The composite magnitude is


$$R_{3}(\omega) = R_{1}(\omega) R_{2}(\omega)$$
$$\left| R_{3}(\omega) \right|_{dB} = \left| R_{1}(\omega) \right|_{dB} + \left| R_{2}(\omega) \right|_{dB}$$

Composite phase is sum of individual phases.

Composite magnitude, when expressed in dB, is sum of individual magnitudes.


Example 1:
$$G(s) = \frac{G_0}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

with $G_0 = 40 \Rightarrow 32 \text{ dB}, f_1 = \omega_1/2\pi = 100 \text{ Hz}, f_2 = \omega_2/2\pi = 2 \text{ kHz}$

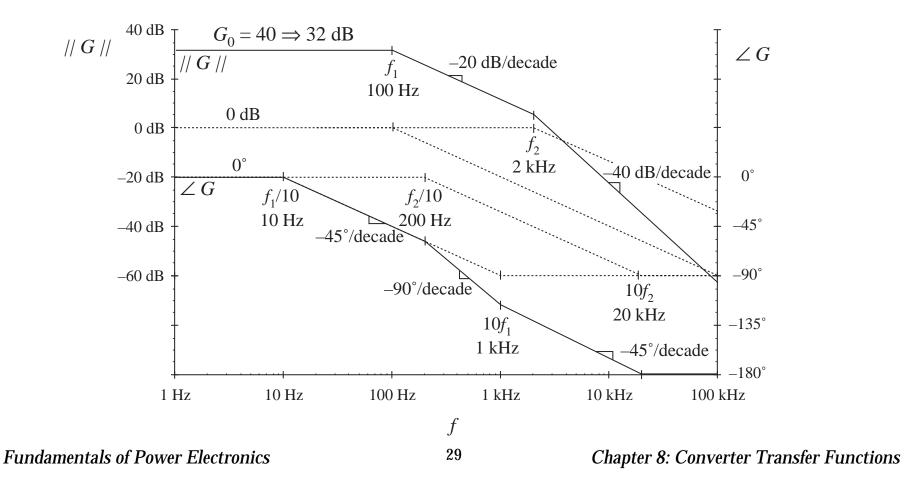

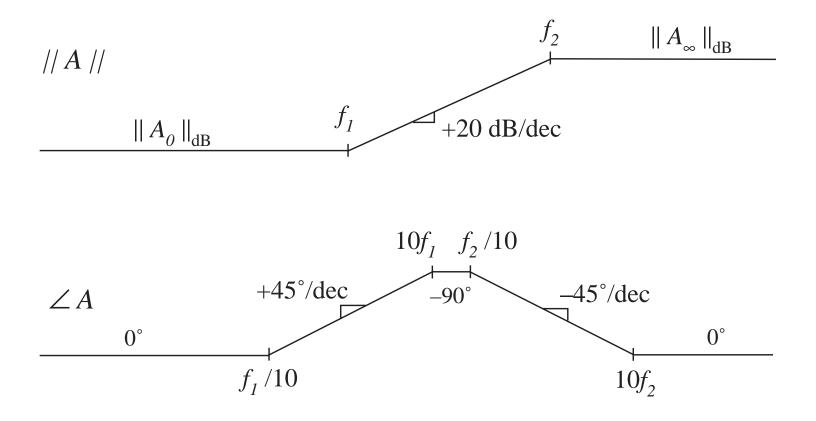Example 2

Determine the transfer function A(s) corresponding to the following asymptotes:



Fundamentals of Power Electronics

30

Example 2, continued

One solution:

$$A(s) = A_0 \frac{\left(1 + \frac{s}{\omega_1}\right)}{\left(1 + \frac{s}{\omega_2}\right)}$$

Analytical expressions for asymptotes:

For
$$f < f_1$$


$$\left\| A_0 \frac{\left(1 + \frac{c}{\delta f_1} \right)}{\left(1 + \frac{c}{\delta f_2} \right)} \right\|_{s = j\omega} = A_0 \frac{1}{1} = A_0$$

For
$$f_1 < f < f_2$$

$$\left\| A_0 \frac{\left(\mathbf{T} + \frac{s}{\omega_1} \right)}{\left(1 + \frac{s}{\omega_2} \right)} \right\|_{s = j\omega} = A_0 \frac{\left\| \frac{s}{\omega_1} \right\|_{s = j\omega}}{1} = A_0 \frac{\omega}{\omega_1} = A_0 \frac{f_1}{f_1}$$

Fundamentals of Power Electronics

Example 2, continued

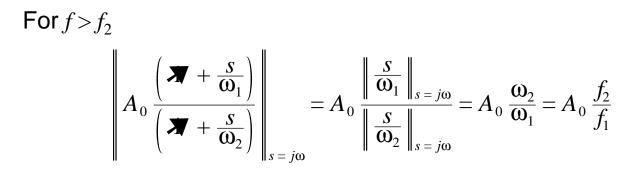

So the high-frequency asymptote is


$$A_{\infty} = A_0 \frac{f_2}{f_1}$$

Another way to express A(s): use inverted poles and zeroes, and express A(s) directly in terms of A_{∞}

$$A(s) = A_{\infty} \frac{\left(1 + \frac{\omega_1}{s}\right)}{\left(1 + \frac{\omega_2}{s}\right)}$$

Fundamentals of Power Electronics

8.1.6 Quadratic pole response: resonance

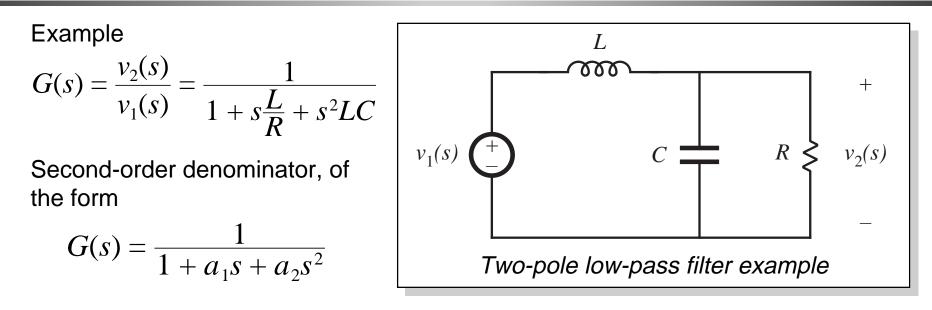

with $a_1 = L/R$ and $a_2 = LC$

How should we construct the Bode diagram?

Approach 1: factor denominator

$$G(s) = \frac{1}{1 + a_1 s + a_2 s^2}$$

We might factor the denominator using the quadratic formula, then construct Bode diagram as the combination of two real poles:

$$G(s) = \frac{1}{\left(1 - \frac{s}{s_1}\right)\left(1 - \frac{s}{s_2}\right)} \quad \text{with} \quad s_1 = -\frac{a_1}{2a_2} \left[1 - \sqrt{1 - \frac{4a_2}{a_1^2}}\right]$$
$$s_2 = -\frac{a_1}{2a_2} \left[1 + \sqrt{1 - \frac{4a_2}{a_1^2}}\right]$$

- If $4a_2 \le a_1^2$, then the roots s_1 and s_2 are real. We can construct Bode diagram as the combination of two real poles.
- If $4a_2 > a_1^2$, then the roots are complex. In Section 8.1.1, the assumption was made that ω_0 is real; hence, the results of that section cannot be applied and we need to do some additional work.

Fundamentals of Power Electronics

٦

Approach 2: Define a standard normalized form for the quadratic case

$$G(s) = \frac{1}{1 + 2\zeta \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2} \quad \text{or} \quad G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

- When the coefficients of s are real and positive, then the parameters ζ, ω₀, and Q are also real and positive
- The parameters ζ , ω_0 , and Q are found by equating the coefficients of s
- The parameter ω_0 is the angular corner frequency, and we can define $f_0 = \omega_0/2\pi$
- The parameter ζ is called the *damping factor*. ζ controls the shape of the exact curve in the vicinity of $f = f_0$. The roots are complex when $\zeta < 1$.
- In the alternative form, the parameter Q is called the *quality factor*. Q also controls the shape of the exact curve in the vicinity of $f = f_0$. The roots are complex when Q > 0.5.

The *Q*-factor

In a second-order system, ζ and Q are related according to

$$Q = \frac{1}{2\zeta}$$

Q is a measure of the dissipation in the system. A more general definition of Q, for sinusoidal excitation of a passive element or system is

$$Q = 2\pi \frac{\text{(peak stored energy)}}{\text{(energy dissipated per cycle)}}$$

For a second-order passive system, the two equations above are equivalent. We will see that Q has a simple interpretation in the Bode diagrams of second-order transfer functions.

Analytical expressions for f_0 and Q

Two-pole low-pass filter example: we found that

$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{1}{1 + s\frac{L}{R} + s^2 LC}$$

Equate coefficients of like powers of s with the standard form

$$G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Result:

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$
$$Q = R\sqrt{\frac{C}{L}}$$

Fundamentals of Power Electronics

Magnitude asymptotes, quadratic form

In the form
$$G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

let $s = j\omega$ and find magnitude: $\|G(j\omega)\| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2}\left(\frac{\omega}{\omega_0}\right)^2}}$
Asymptotes are $\|G(j\omega)\|_{dB}$
 $\|G\| \to 1$ for $\omega << \omega_0$ $0 \, dB$
 $\|G\| \to \left(\frac{f}{f_0}\right)^{-2}$ for $\omega >> \omega_0$ $-20 \, dB$
 $-40 \, dB$
 $-60 \, dB$
 $-60 \, dB$
 $-40 \, dB$
 $-40 \, dB/dccade$
 $-40 \, dB/dccade$

Fundamentals of Power Electronics

Deviation of exact curve from magnitude asymptotes


$$G(j\omega) \| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0}\right)^2}}$$

At $\omega = \omega_0$, the exact magnitude is


$$\|G(j\omega_0)\| = Q$$
 or, in dB:

$$\left\| G(j\omega_0) \right\|_{\rm dB} = \left| Q \right|_{\rm dB}$$

The exact curve has magnitude Q at $f = f_0$. The deviation of the exact curve from the asymptotes is $|Q|_{dB}$

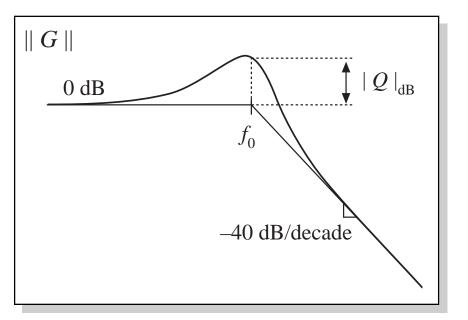

Two-pole response: exact curves

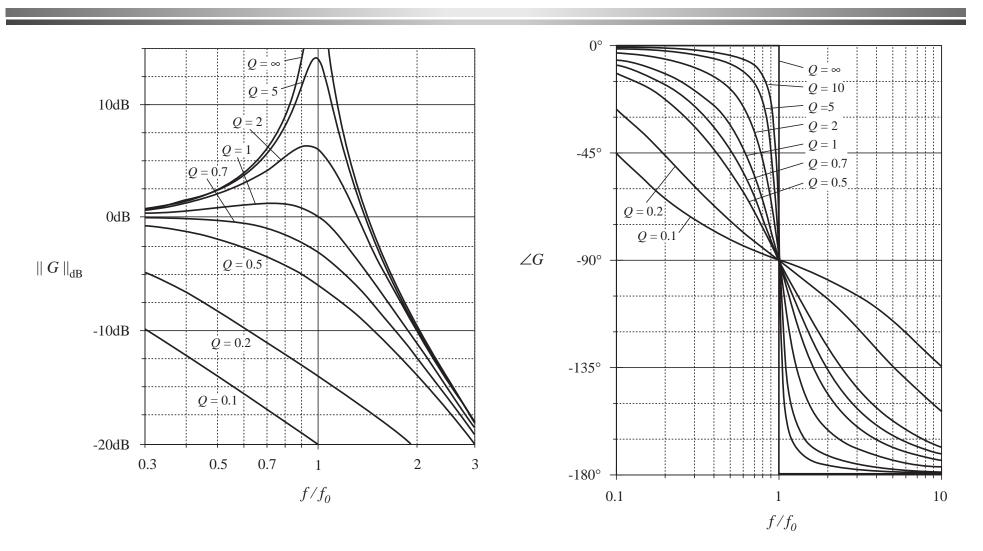

Fundamentals of Power Electronics

8.1.7. The low-*Q* approximation

Given a second-order denominator polynomial, of the form

$$G(s) = \frac{1}{1 + a_1 s + a_2 s^2}$$
 or $G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$

When the roots are real, i.e., when Q < 0.5, then we can factor the denominator, and construct the Bode diagram using the asymptotes for real poles. We would then use the following normalized form:


$$G(s) = \frac{1}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

This is a particularly desirable approach when Q << 0.5, i.e., when the corner frequencies ω_1 and ω_2 are well separated.

An example

A problem with this procedure is the complexity of the quadratic formula used to find the corner frequencies.

R-L-C network example:

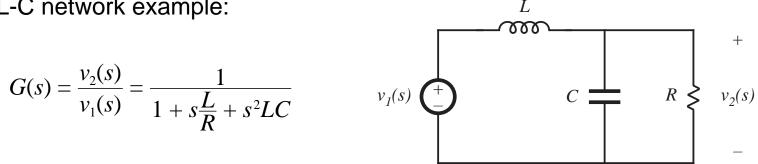

Use quadratic formula to factor denominator. Corner frequencies are:

$$\omega_1, \omega_2 = \frac{L/R \pm \sqrt{(L/R)^2 - 4LC}}{2LC}$$

Fundamentals of Power Electronics

Factoring the denominator

$$\omega_1, \, \omega_2 = \frac{L / R \pm \sqrt{\left(L / R\right)^2 - 4 LC}}{2 LC}$$

This complicated expression yields little insight into how the corner frequencies ω_1 and ω_2 depend on *R*, *L*, and *C*.

When the corner frequencies are well separated in value, it can be shown that they are given by the much simpler (approximate) expressions

$$\omega_1 \approx \frac{R}{L}, \qquad \omega_2 \approx \frac{1}{RC}$$

 ω_1 is then independent of *C*, and ω_2 is independent of *L*.

These simpler expressions can be derived via the Low-Q Approximation.

Derivation of the Low-*Q* Approximation

Given

$$G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Use quadratic formula to express corner frequencies ω_1 and ω_2 in terms of Q and ω_0 as:

$$\omega_1 = \frac{\omega_0}{Q} \frac{1 - \sqrt{1 - 4Q^2}}{2} \qquad \qquad \omega_2 = \frac{\omega_0}{Q} \frac{1 + \sqrt{1 - 4Q^2}}{2}$$

Corner frequency ω_2

$$\omega_2 = \frac{\omega_0}{Q} \frac{1 + \sqrt{1 - 4Q^2}}{2}$$

can be written in the form


$$\omega_2 = \frac{\omega_0}{Q} F(Q)$$

where

$$F(Q) = \frac{1}{2} \left(1 + \sqrt{1 - 4Q^2} \right)$$

For small Q, F(Q) tends to 1. We then obtain
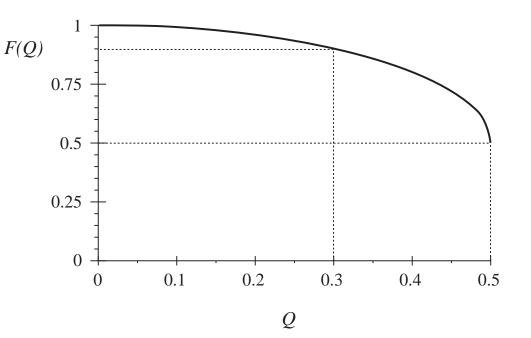
$$\omega_2 \approx \frac{\omega_0}{Q}$$
 for $Q \ll \frac{1}{2}$



For Q < 0.3, the approximation F(Q) = 1 is within 10% of the exact value.

Corner frequency ω_1

$$\omega_1 = \frac{\omega_0}{Q} \frac{1 - \sqrt{1 - 4Q^2}}{2}$$

can be written in the form


$$\omega_1 = \frac{Q \,\omega_0}{F(Q)}$$

where

$$F(Q) = \frac{1}{2} \left(1 + \sqrt{1 - 4Q^2} \right)$$


For small Q, F(Q) tends to 1. We then obtain
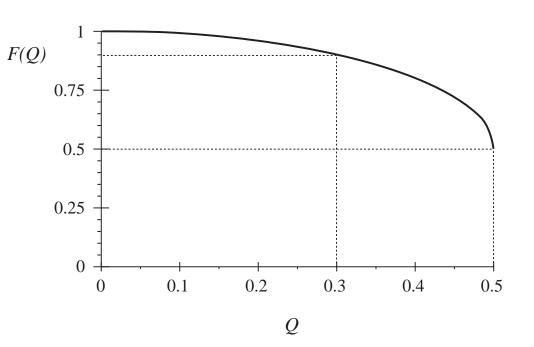
$$\omega_1 \approx Q \,\omega_0 \quad \text{for } Q \ll \frac{1}{2}$$



For Q < 0.3, the approximation F(Q) = 1 is within 10% of the exact value.

The Low-*Q* Approximation

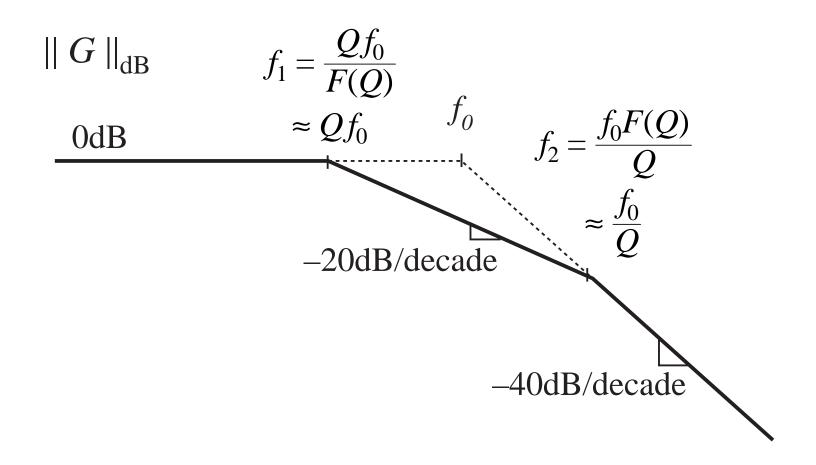

R-L-C Example

For the previous example:

$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{1}{1 + s\frac{L}{R} + s^2 LC} \qquad f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} \qquad Q = R\sqrt{\frac{C}{L}}$$

Use of the Low-Q Approximation leads to

$$\omega_1 \approx Q \ \omega_0 = R \ \sqrt{\frac{C}{L}} \ \frac{1}{\sqrt{LC}} = \frac{R}{L}$$
$$\omega_2 \approx \frac{\omega_0}{Q} = \frac{1}{\sqrt{LC}} \ \frac{1}{R \ \sqrt{\frac{C}{L}}} = \frac{1}{RC}$$

8.2. Analysis of converter transfer functions

- 8.2.1. Example: transfer functions of the buck-boost converter
- 8.2.2. Transfer functions of some basic CCM converters
- 8.2.3. Physical origins of the right half-plane zero in converters

8.2.1. Example: transfer functions of the buck-boost converter

Small-signal ac equations of the buck-boost converter, derived in section 7.2:

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + \left(V_g - V\right)\hat{d}(t)$$
$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)$$
$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

Definition of transfer functions

The converter contains two inputs, $\hat{d}(s)$ and $\hat{v}_{g}(s)$ and one output, $\hat{v}(s)$

Hence, the ac output voltage variations can be expressed as the superposition of terms arising from the two inputs:

$$\hat{v}(s) = G_{vd}(s) \ \hat{d}(s) + G_{vg}(s) \ \hat{v}_g(s)$$

The control-to-output and line-to-output transfer functions can be defined as

$$G_{vd}(s) = \frac{\hat{v}(s)}{\hat{d}(s)} \bigg|_{\hat{v}_g(s) = 0} \quad \text{and} \quad G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} \bigg|_{\hat{d}(s) = 0}$$

Derivation of transfer functions

Algebraic approach

Take Laplace transform of converter equations, letting initial conditions be zero:

$$sL\hat{i}(s) = D\hat{v}_g(s) + D'\hat{v}(s) + \left(V_g - V\right)\hat{d}(s)$$
$$sC\hat{v}(s) = -D'\hat{i}(s) - \frac{\hat{v}(s)}{R} + I\hat{d}(s)$$

Eliminate $\hat{i}(s)$, and solve for $\hat{v}(s)$

$$\hat{i}(s) = \frac{D\hat{v}_g(s) + D'\hat{v}(s) + \left(V_g - V\right)\hat{d}(s)}{sL}$$

Derivation of transfer functions

$$sC\hat{v}(s) = -\frac{D'}{sL} \left(D\hat{v}_g(s) + D'\hat{v}(s) + \left(V_g - V\right)\hat{d}(s) \right) - \frac{\hat{v}(s)}{R} + I\hat{d}(s)$$
$$\hat{v}(s) = \frac{-DD'}{D'^2 + s\frac{L}{R} + s^2 LC} \,\hat{v}_g(s) - \frac{V_g - V - s LI}{D'^2 + s\frac{L}{R} + s^2 LC} \,\hat{d}(s)$$

write in normalized form:

$$\hat{v}(s) = \left(-\frac{D}{D'}\right) \frac{1}{1 + s \frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2}} \,\hat{v}_g(s) - \left(\frac{V_g - V}{D'^2}\right) \frac{\left(1 - s \frac{LI}{V_g - V}\right)}{1 + s \frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2}} \,\hat{d}(s)$$

Derivation of transfer functions

Hence, the line-to-output transfer function is

$$G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} \bigg|_{\hat{d}(s)=0} = \left(-\frac{D}{D'}\right) \frac{1}{1 + s \frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2}}$$

which is of the following standard form:

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Salient features of the line-to-output transfer function

Equate standard form to derived transfer function, to determine expressions for the salient features:

Control-to-output transfer function

$$G_{vd}(s) = \frac{\hat{v}(s)}{\hat{d}(s)}\Big|_{\hat{v}_{g}(s)=0} = \left(-\frac{V_{g}-V}{D'^{2}}\right) \frac{\left(1-s \frac{LI}{V_{g}-V}\right)}{\left(1+s \frac{L}{D'^{2}R}+s^{2} \frac{LC}{D'^{2}}\right)}$$

Standard form:

$$G_{vd}(s) = G_{d0} \frac{\left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2\right)}$$

Salient features of control-to-output transfer function

$$G_{d0} = -\frac{V_g - V}{D'^2} = -\frac{V_g}{D'^3} = \frac{V}{D D'^2}$$
$$\omega_z = \frac{V_g - V}{L I} = \frac{D' R}{D L} \qquad \text{(RHP)}$$
$$\omega_0 = \frac{D'}{\sqrt{LC}}$$
$$Q = D'R \sqrt{\frac{C}{L}}$$

— Simplified using the dc relations:

$$V = -\frac{D}{D'} V_g$$
$$I = -\frac{V}{D' R}$$

Fundamentals of Power Electronics

Chapter 8: Converter Transfer Functions

Plug in numerical values

Suppose we are given the following numerical values:

$$D = 0.6$$

$$R = 10\Omega$$

$$V_g = 30V$$

$$L = 160\mu H$$

$$C = 160\mu F$$

Then the salient features have the following numerical values:

$$G_{g0} = \frac{D}{D'} = 1.5 \Rightarrow 3.5 \text{dB}$$


$$G_{d0} = \frac{|V|}{D D'^2} = 469 \text{V} \Rightarrow 53.4 \text{dBV}$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{D'}{2\pi\sqrt{LC}} = 400 \text{Hz}$$


$$Q = D' R \sqrt{\frac{C}{L}} = 4 \Rightarrow 12 \text{dB}$$

$$f_z = \frac{\omega_z}{2\pi} = \frac{D' R}{2\pi DL} = 6.6 \text{kHz}$$

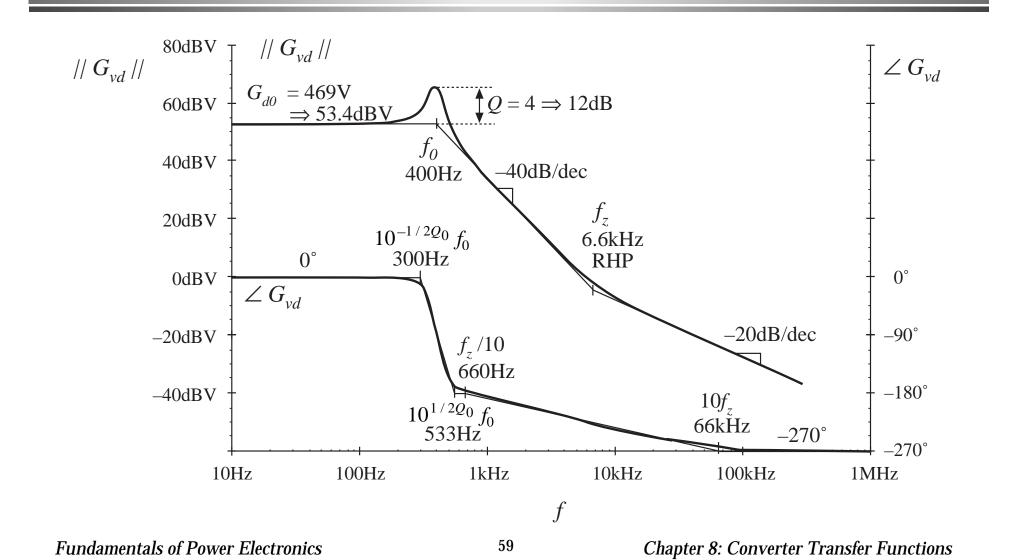Bode plot: control-to-output transfer function



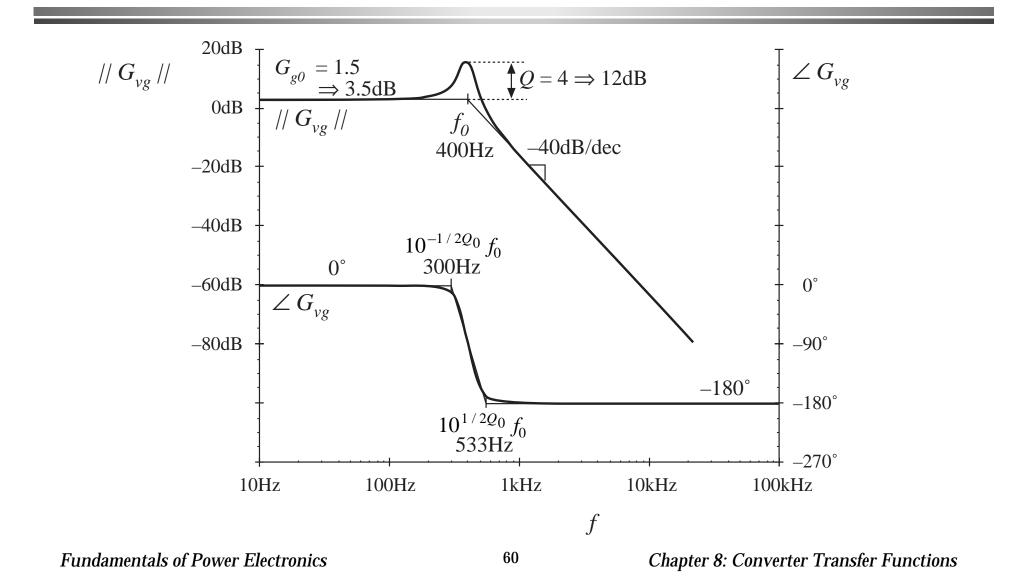Bode plot: line-to-output transfer function



8.2.2. Transfer functions of some basic CCM converters

Table 8.2. Salient features of the small-signal CCM transfer functions of some basic dc-dc converters


Converter	G_{g0}	G_{d0}	ω_0	Q	ω _z
buck	D	$\frac{V}{D}$	$\frac{1}{\sqrt{LC}}$	$R\sqrt{\frac{C}{L}}$	∞
boost	$\frac{1}{D'}$	$\frac{V}{D'}$	$rac{D'}{\sqrt{LC}}$	$D'R \sqrt{\frac{C}{L}}$	$\frac{D'^2 R}{L}$
buck-boost	$-\frac{D}{D'}$	$\frac{V}{D D'^2}$	$rac{D'}{\sqrt{LC}}$	$D'R \sqrt{rac{C}{L}}$	$\frac{D^{\prime 2}R}{DL}$

where the transfer functions are written in the standard forms

Fundamentals of Power Electronics


Chapter 8: Converter Transfer Functions

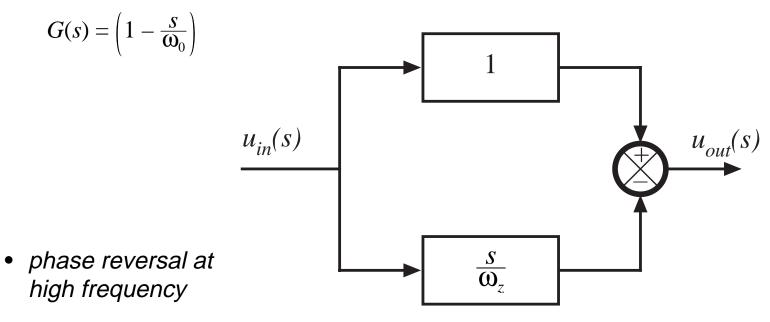8.2.3. Physical origins of the right half-plane zero



 transient response: output initially tends in wrong direction

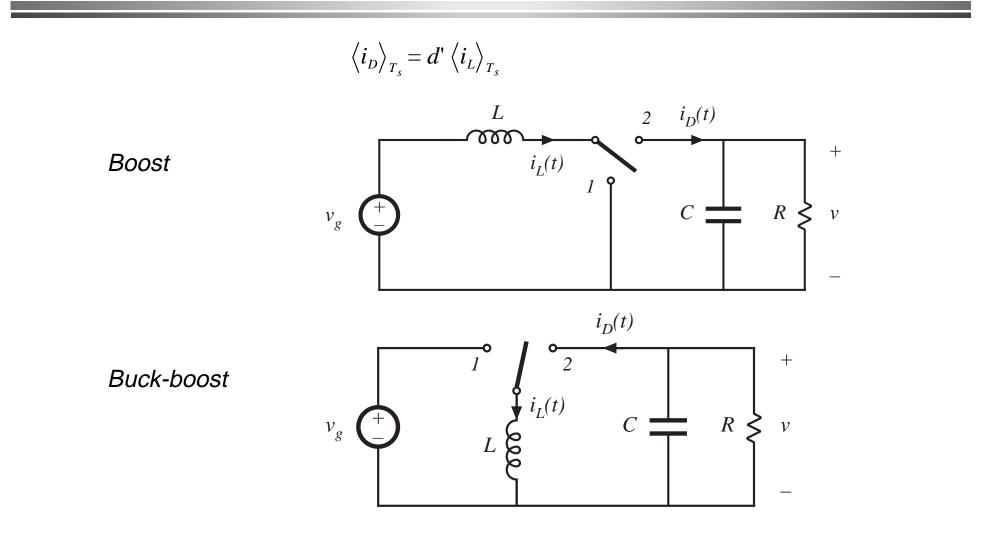
Two converters whose CCM control-to-output transfer functions exhibit RHP zeroes




Waveforms, step increase in duty cycle

 $\left\langle i_{D}\right\rangle _{T_{s}}=d'\left\langle i_{L}\right\rangle _{T_{s}}$

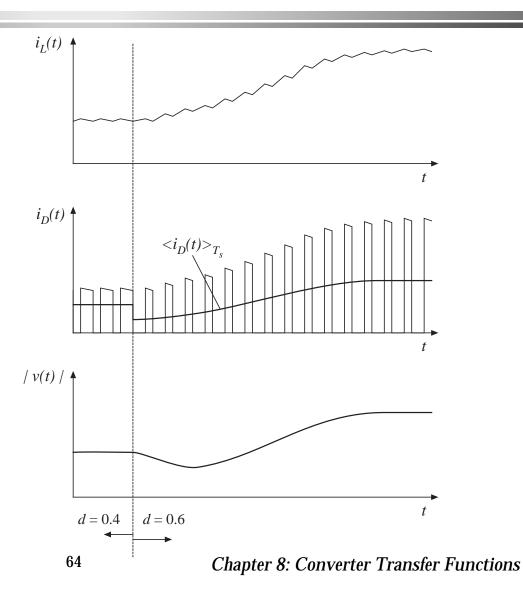- Increasing d(t) causes the average diode current to initially decrease
- As inductor current increases to its new equilibrium value, average diode current eventually increases




Impedance graph paper

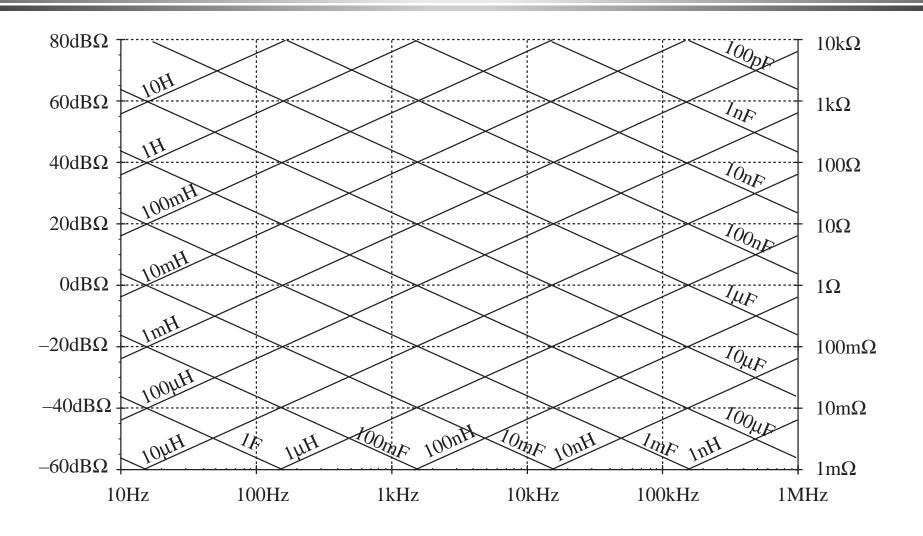


Fundamentals of Power Electronics

Chapter 8: Converter Transfer Functions

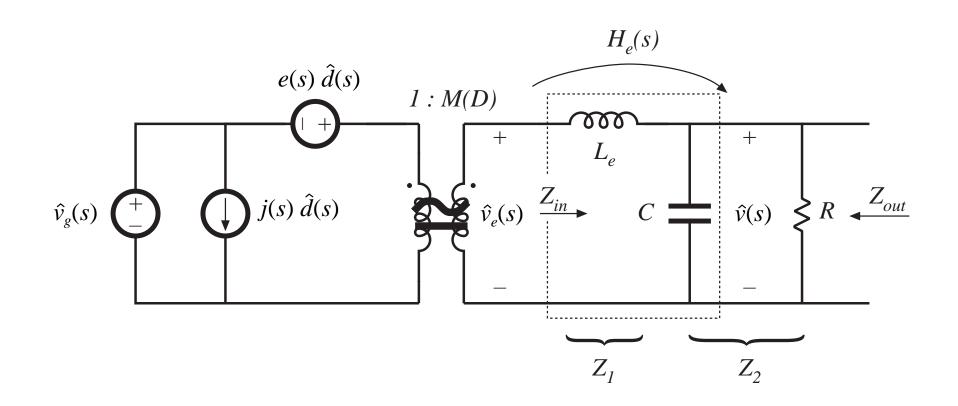Transfer functions predicted by canonical model




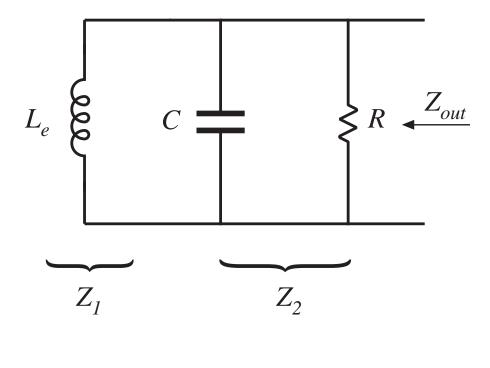Output impedance Z_{out} : set sources to zero




 $Z_{out} = Z_1 \parallel Z_2$

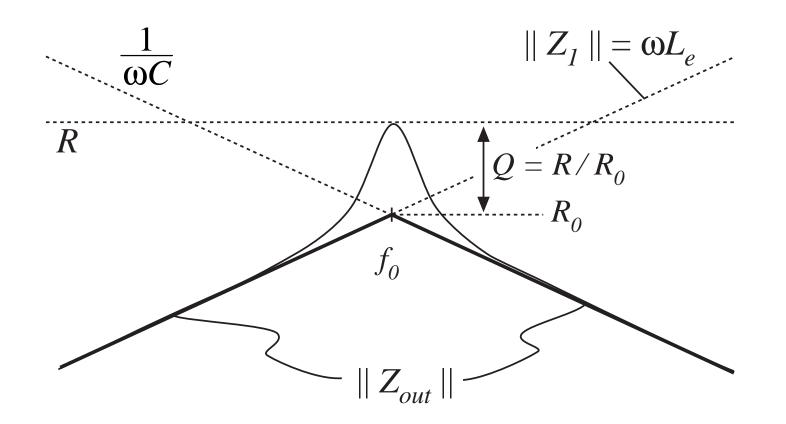
Graphical construction of output impedance



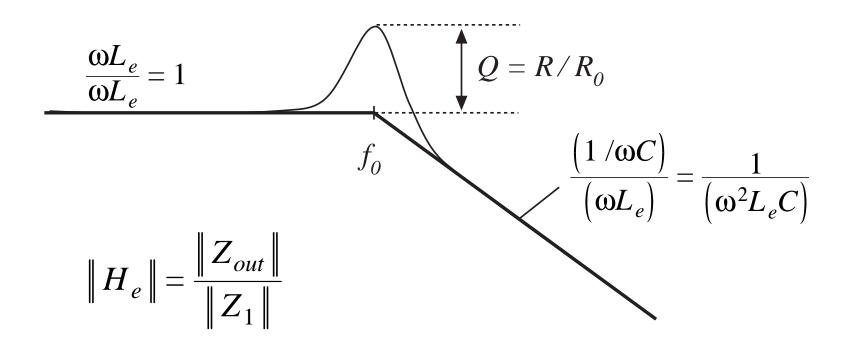
Graphical construction of filter effective transfer function



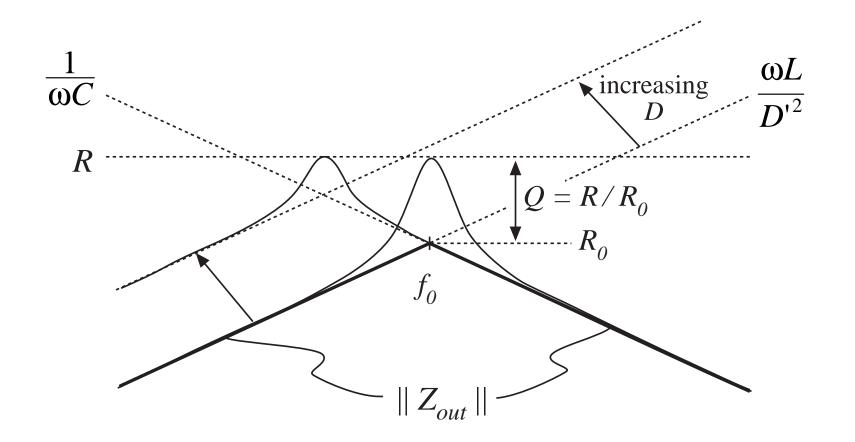Boost and buck-boost converters: $L_e = L / D'^2$



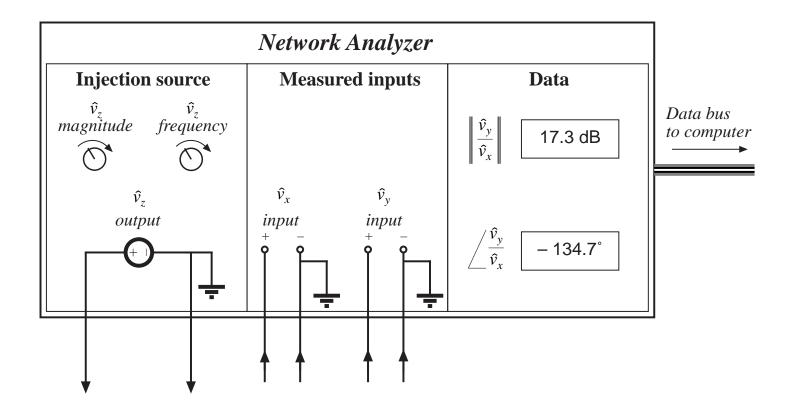8.4. Measurement of ac transfer functions and impedances



Swept sinusoidal measurements

- Injection source produces sinusoid \hat{v}_z of controllable amplitude and frequency
- Signal inputs \hat{v}_x and \hat{v}_y perform function of narrowband tracking voltmeter:


Component of input at injection source frequency is measured

Narrowband function is essential: switching harmonics and other noise components are removed

• Network analyzer measures


$$\left| \frac{\hat{v}_{y}}{\hat{v}_{x}} \right|$$
 and $\angle \frac{\hat{v}_{y}}{\hat{v}_{x}}$

Measurement of an ac transfer function

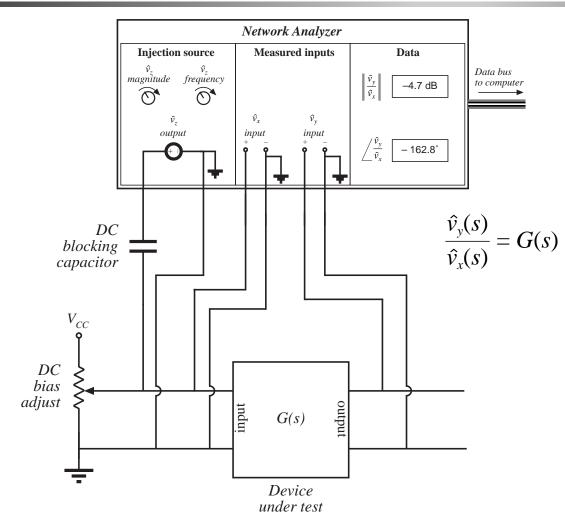

- Potentiometer establishes correct quiescent operating point
- Injection sinusoid coupled to device input via dc blocking capacitor
- Actual device input and output voltages are measured as \hat{v}_x and \hat{v}_y
- Dynamics of blocking capacitor are irrelevant

Measurement of an output impedance

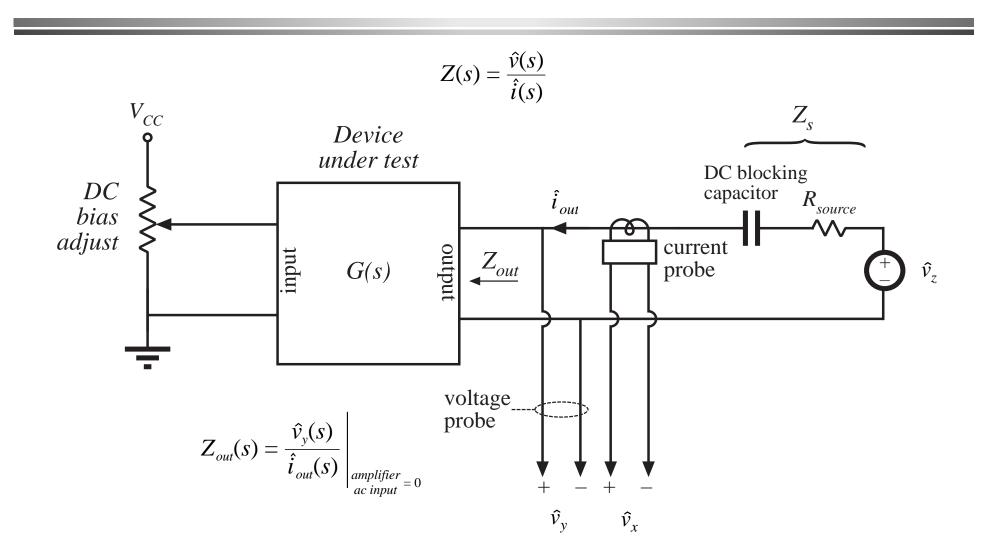

Fundamentals of Power Electronics

Chapter 8: Converter Transfer Functions

Measurement of output impedance

• Treat output impedance as transfer function from output current to output voltage:

$$Z(s) = \frac{\hat{v}(s)}{\hat{i}(s)} \qquad \qquad Z_{out}(s) = \frac{\hat{v}_{y}(s)}{\hat{i}_{out}(s)} \bigg|_{\substack{\text{amplifier} \\ ac \text{ input}} = 0}$$

- Potentiometer at device input port establishes correct quiescent operating point
- Current probe produces voltage proportional to current; this voltage is connected to network analyzer channel \hat{v}_x
- Network analyzer result must be multiplied by appropriate factor, to account for scale factors of current and voltage probes

Measurement of small impedances

Grounding problems cause measurement to fail:


Injection current can return to analyzer via two paths. Injection current which returns via voltage probe ground induces voltage drop in voltage probe, corrupting the measurement. Network analyzer measures

$$Z + (1 - k) Z_{probe} = Z + Z_{probe} \parallel Z_{rz}$$

For an accurate measurement, require


$$\left\| Z \right\| >> \left\| \left(Z_{probe} \mid\mid Z_{rz} \right) \right.$$

Fundamentals of Power Electronics

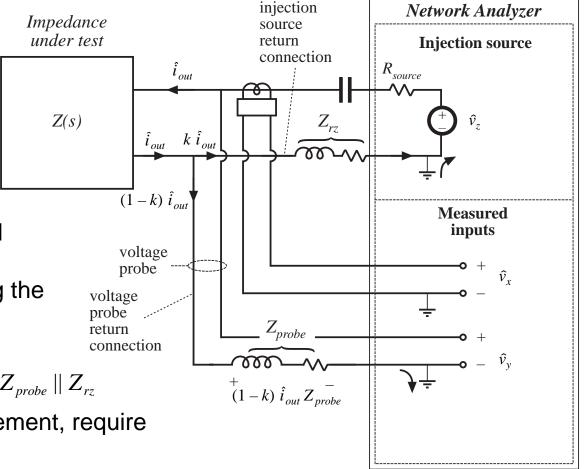

Chapter 8: Converter Transfer Functions

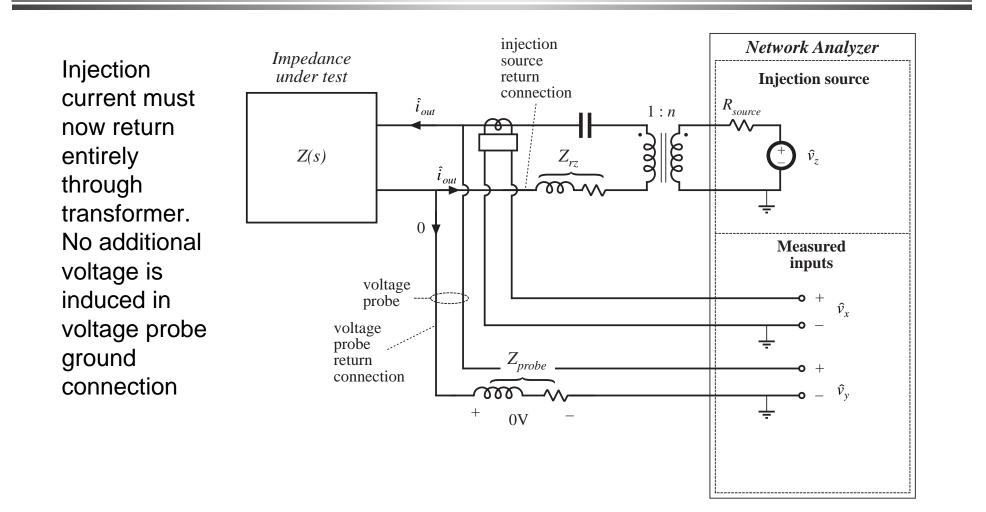Improved measurement: add isolation transformer



8.5. Summary of key points

- 1. The magnitude Bode diagrams of functions which vary as $(f/f_0)n$ have slopes equal to 20n dB per decade, and pass through 0dB at $f = f_0$.
- 2. It is good practice to express transfer functions in normalized polezero form; this form directly exposes expressions for the salient features of the response, i.e., the corner frequencies, reference gain, etc.
- 3. The right half-plane zero exhibits the magnitude response of the left half-plane zero, but the phase response of the pole.
- 4. Poles and zeroes can be expressed in frequency-inverted form, when it is desirable to refer the gain to a high-frequency asymptote.

Summary of key points

- 5. A two-pole response can be written in the standard normalized form of Eq. (8-53). When Q > 0.5, the poles are complex conjugates. The magnitude response then exhibits peaking in the vicinity of the corner frequency, with an exact value of Q at $f = f_0$. High Q also causes the phase to change sharply near the corner frequency.
- 6. When the *Q* is less than 0.5, the two pole response can be plotted as two real poles. The low- *Q* approximation predicts that the two poles occur at frequencies f_0 / Q and Qf_0 . These frequencies are within 10% of the exact values for $Q \le 0.3$.
- 7. The low- *Q* approximation can be extended to find approximate roots of an arbitrary degree polynomial. Approximate analytical expressions for the salient features can be derived. Numerical values are used to justify the approximations.

Summary of key points

- 8. Salient features of the transfer functions of the buck, boost, and buckboost converters are tabulated in section 8.2.2. The line-to-output transfer functions of these converters contain two poles. Their controlto-output transfer functions contain two poles, and may additionally contain a right half-pland zero.
- 9. Approximate magnitude asymptotes of impedances and transfer functions can be easily derived by graphical construction. This approach is a useful supplement to conventional analysis, because it yields physical insight into the circuit behavior, and because it exposes suitable approximations. Several examples, including the impedances of basic series and parallel resonant circuits and the transfer function $H_e(s)$ of the boost and buck-boost converters, are worked in section 8.3.
- 10. Measurement of transfer functions and impedances using a network analyzer is discussed in section 8.4. Careful attention to ground connections is important when measuring small impedances.

- 9.1. Introduction
- 9.2. Effect of negative feedback on the network transfer functions
 - 9.2.1. Feedback reduces the transfer function from disturbances to the output
 - 9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop
- 9.3. Construction of the important quantities 1/(1+T) and T/(1+T) and the closed-loop transfer functions

Controller design

9.4. Stability

- 9.4.1. The phase margin test
- 9.4.2. The relation between phase margin and closed-loop damping factor
- 9.4.3. Transient response vs. damping factor

9.5. Regulator design


- 9.5.1. Lead (PD) compensator
- 9.5.2. Lag (PI) compensator
- 9.5.3. Combined (PID) compensator
- 9.5.4. Design example

Controller design

9.6. Measurement of loop gains

- 9.6.1. Voltage injection
- 9.6.2. Current injection
- 9.6.3. Measurement of unstable systems
- 9.7. Summary of key points


9.1. Introduction

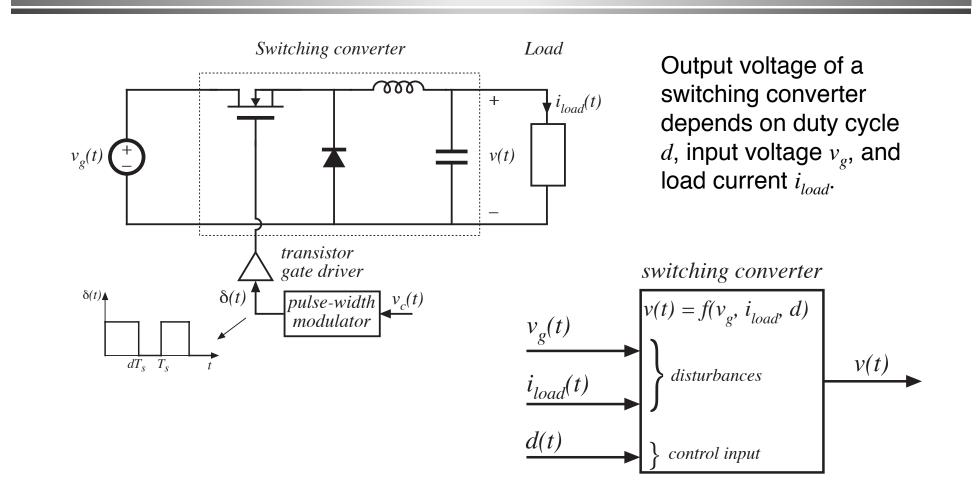

The dc regulator application

Objective: maintain constant output voltage v(t) = V, in spite of disturbances in $v_g(t)$ and $i_{load}(t)$.

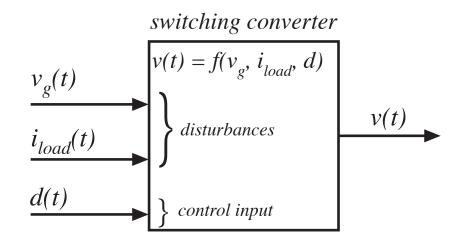Typical variation in $v_g(t)$: 100Hz or 120Hz ripple, produced by rectifier circuit.



Load current variations: a significant step-change in load current, such as from 50% to 100% of rated value, may be applied.

A typical output voltage regulation specification: $5V \pm 0.1V$.


Circuit elements are constructed to some specified tolerance. In high volume manufacturing of converters, all output voltages must meet specifications.

The dc regulator application


So we cannot expect to set the duty cycle to a single value, and obtain a given constant output voltage under all conditions.

Negative feedback: build a circuit that automatically adjusts the duty cycle as necessary, to obtain the specified output voltage with high accuracy, regardless of disturbances or component tolerances.

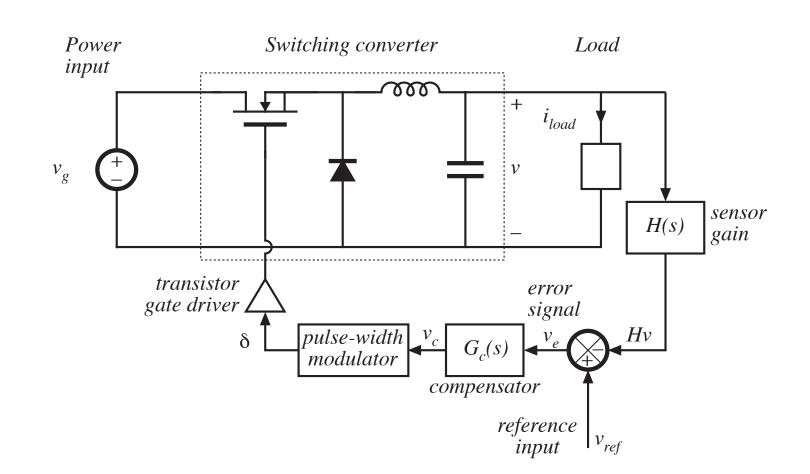Negative feedback: a switching regulator system




Negative feedback

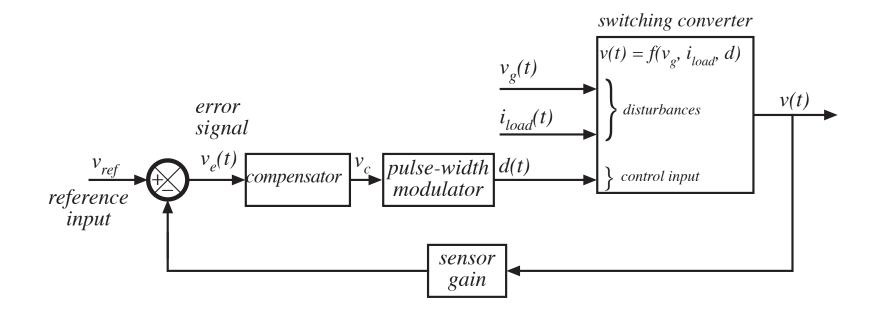

9.2. Effect of negative feedback on the network transfer functions

Small signal model: open-loop converter

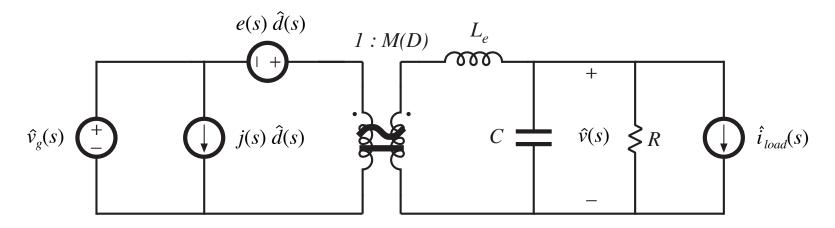

Output voltage can be expressed as

$$\hat{v}(s) = G_{vd}(s) \ \hat{d}(s) + G_{vg}(s) \ \hat{v}_g(s) \pm Z_{out}(s) \ \hat{i}_{load}(s)$$

where

$$G_{vd}(s) = \frac{\hat{v}(s)}{\hat{d}(s)} \bigg|_{\substack{\hat{v}_g = 0 \\ \hat{i}_{load} = 0}} \qquad G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} \bigg|_{\substack{\hat{d} = 0 \\ \hat{i}_{load} = 0}} \qquad Z_{out}(s) = \pm \frac{\hat{v}(s)}{\hat{i}_{load}(s)} \bigg|_{\substack{\hat{d} = 0 \\ \hat{v}_g = 0}}$$


Fundamentals of Power Electronics

Voltage regulator system small-signal model

- Use small-signal converter model
- Perturb and linearize remainder of feedback loop:


$$v_{ref}(t) = V_{ref} + \hat{v}_{ref}(t)$$
$$v_e(t) = V_e + \hat{v}_e(t)$$

etc.

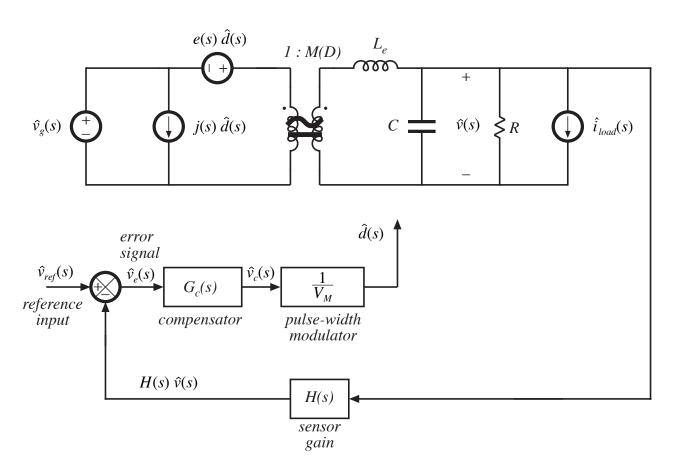

Fundamentals of Power Electronics

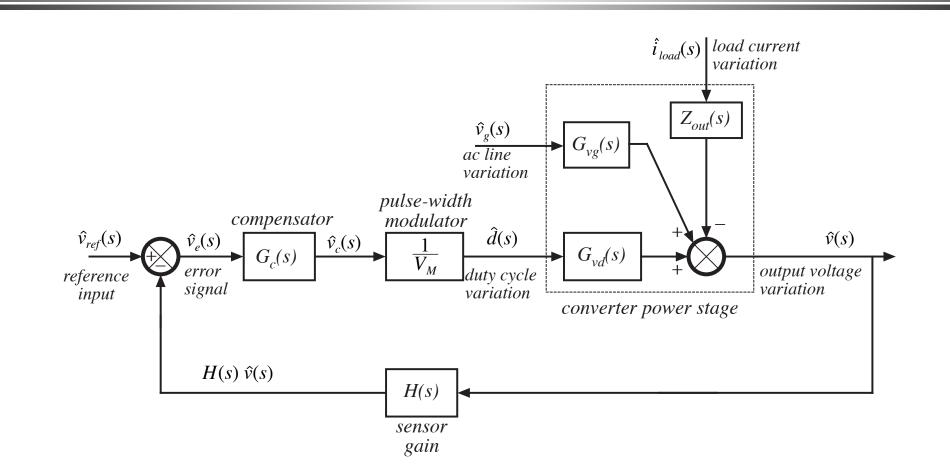Regulator system small-signal block diagram



11

Solution of block diagram

Manipulate block diagram to solve for $\hat{v}(s)$. Result is

$$\hat{v} = \hat{v}_{ref} \frac{G_c G_{vd} / V_M}{1 + H G_c G_{vd} / V_M} + \hat{v}_g \frac{G_{vg}}{1 + H G_c G_{vd} / V_M} \pm \hat{i}_{load} \frac{Z_{out}}{1 + H G_c G_{vd} / V_M}$$

which is of the form

$$\hat{v} = \hat{v}_{ref} \frac{1}{H} \frac{T}{1+T} + \hat{v}_g \frac{G_{vg}}{1+T} \pm \hat{i}_{load} \frac{Z_{out}}{1+T}$$

with $T(s) = H(s) G_c(s) G_{vd}(s) / V_M = "loop gain"$

Loop gain T(s) = products of the gains around the negative feedback loop.

9.2.1. Feedback reduces the transfer functions from disturbances to the output

Original (open-loop) line-to-output transfer function:

$$G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} \bigg|_{\substack{\hat{d} = 0 \\ \hat{i}_{load} = 0}}$$

With addition of negative feedback, the line-to-output transfer function becomes:

$$\frac{\hat{v}(s)}{\hat{v}_g(s)} \bigg|_{\substack{\hat{v}_{ref} = 0\\\hat{i}_{load} = 0}} = \frac{G_{vg}(s)}{1 + T(s)}$$

Feedback reduces the line-to-output transfer function by a factor of

$$\frac{1}{1+T(s)}$$

If T(s) is large in magnitude, then the line-to-output transfer function becomes small.

Closed-loop output impedance

Original (open-loop) output impedance:

$$Z_{out}(s) = \pm \left. \frac{\hat{v}(s)}{\hat{i}_{load}(s)} \right|_{\substack{\hat{d} = 0\\ \hat{v}_g = 0}}$$

With addition of negative feedback, the output impedance becomes:

$$\frac{\hat{v}(s)}{\pm \hat{i}_{load}(s)} \bigg|_{\substack{\hat{v}_{ref} = 0\\ \hat{v}_g = 0}} = \frac{Z_{out}(s)}{1 + T(s)}$$

Feedback reduces the output impedance by a factor of

$$\frac{1}{1+T(s)}$$

If T(s) is large in magnitude, then the output impedance is greatly reduced in magnitude.

9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop

Closed-loop transfer function from \hat{v}_{ref} to $\hat{v}(s)$ is:

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)}\Big|_{\substack{\hat{v}_g=0\\\hat{i}_{load}=0}} = \frac{1}{H(s)} \frac{T(s)}{1+T(s)}$$

If the loop gain is large in magnitude, i.e., ||T|| >> 1, then $(1+T) \approx T$ and $T/(1+T) \approx T/T = 1$. The transfer function then becomes

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \approx \frac{1}{H(s)}$$


which is independent of the gains in the forward path of the loop.

This result applies equally well to dc values:

$$\frac{V}{V_{ref}} = \frac{1}{H(0)} \frac{T(0)}{1 + T(0)} \approx \frac{1}{H(0)}$$


Fundamentals of Power Electronics

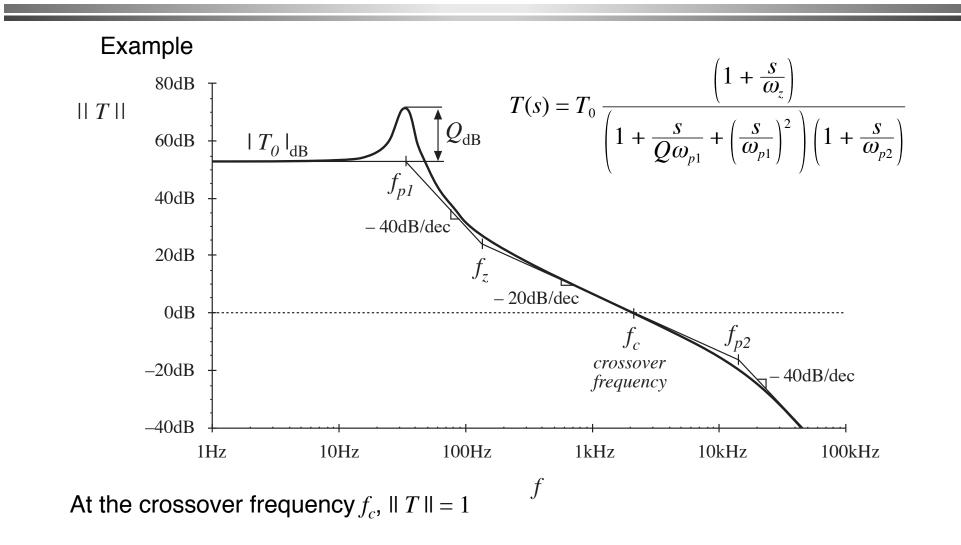9.3. Construction of the important quantities 1/(1+T) and T/(1+T)




Fundamentals of Power Electronics

Approximating 1/(1+T) and T/(1+T)

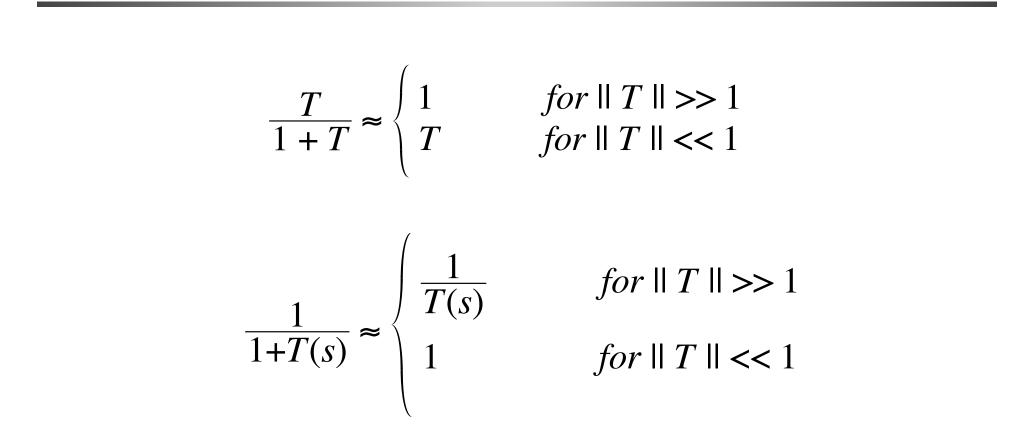

Example: construction of T/(1+T)

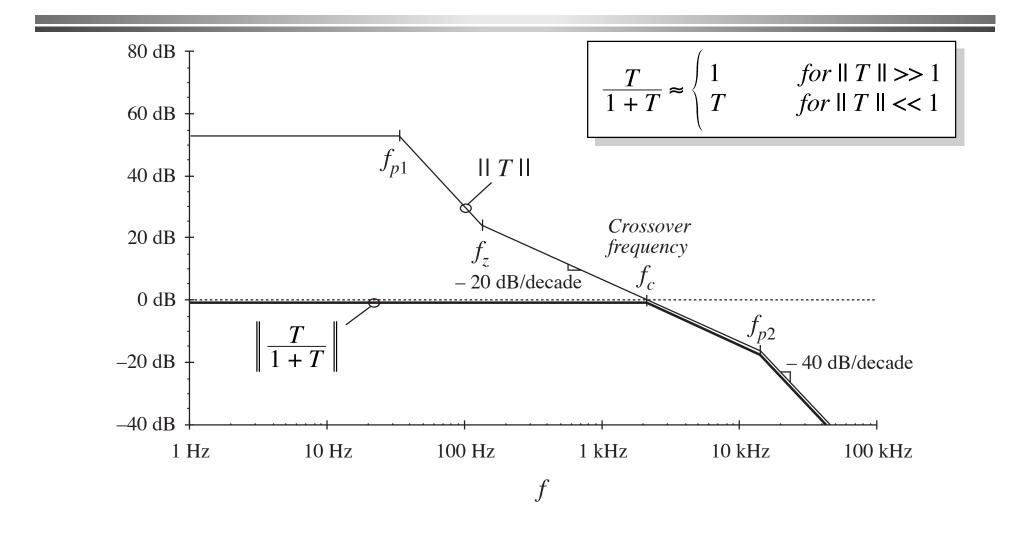

Fundamentals of Power Electronics

Example: analytical expressions for approximate reference to output transfer function

At frequencies sufficiently less that the crossover frequency, the loop gain T(s) has large magnitude. The transfer function from the reference to the output becomes

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)} \approx \frac{1}{H(s)}$$

This is the desired behavior: the output follows the reference according to the ideal gain 1/H(s). The feedback loop works well at frequencies where the loop gain T(s) has large magnitude.


At frequencies above the crossover frequency, || T || < 1. The quantity T/(1+T) then has magnitude approximately equal to 1, and we obtain

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} = \frac{1}{H(s)} \frac{T(s)}{1+T(s)} \approx \frac{T(s)}{H(s)} = \frac{G_c(s)G_{vd}(s)}{V_M}$$

This coincides with the open-loop transfer function from the reference to the output. At frequencies where || T || < 1, the loop has essentially no effect on the transfer function from the reference to the output.

Fundamentals of Power Electronics

Same example: construction of 1/(1+T)

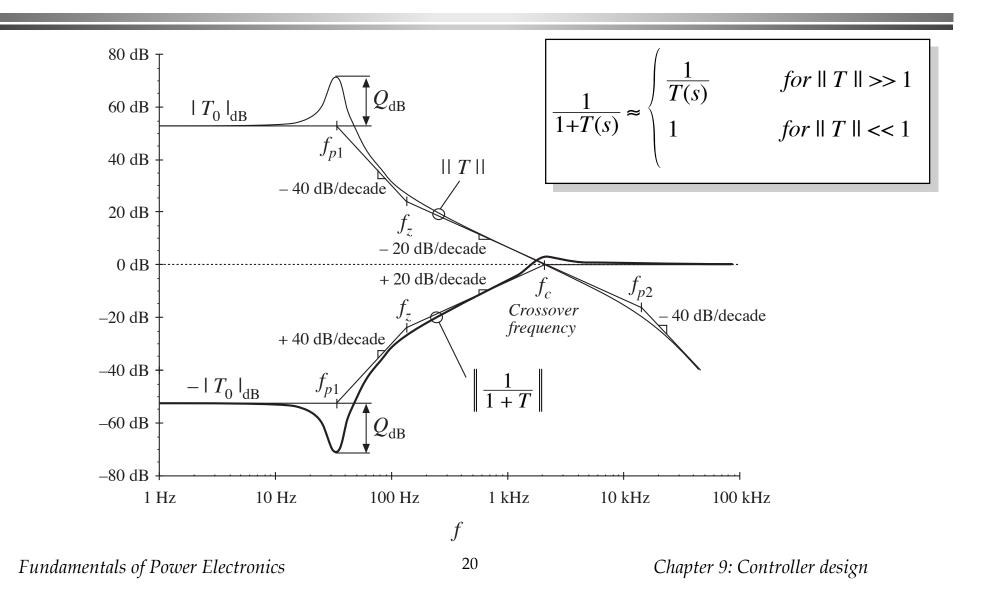


Interpretation: how the loop rejects disturbances

```
Below the crossover frequency: f < f_c and ||T|| > 1
```

Then $1/(1+T) \approx 1/T$, and disturbances are reduced in magnitude by 1/|| T ||

Above the crossover frequency: $f > f_c$ and || T || < 1

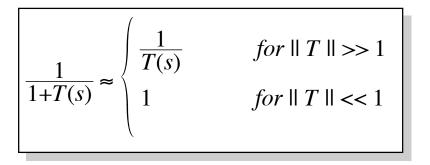Then $1/(1+T) \approx 1$, and the feedback loop has essentially no effect on disturbances



Terminology: open-loop vs. closed-loop

Original transfer functions, before introduction of feedback ("open-loop transfer functions"):

 $G_{vd}(s)$ $G_{vg}(s)$ $Z_{out}(s)$

Upon introduction of feedback, these transfer functions become ("closed-loop transfer functions"):

1	T(s)	$G_{vg}(s)$	$Z_{out}(s)$
$\overline{H(s)}$	$\overline{1+T(s)}$	$\overline{1+T(s)}$	$\overline{1+T(s)}$

The loop gain:

T(s)

9.4. Stability

Even though the original open-loop system is stable, the closed-loop transfer functions can be unstable and contain right half-plane poles. Even when the closed-loop system is stable, the transient response can exhibit undesirable ringing and overshoot, due to the high Q -factor of the closed-loop poles in the vicinity of the crossover frequency.

When feedback destabilizes the system, the denominator (1+T(s)) terms in the closed-loop transfer functions contain roots in the right half-plane (i.e., with positive real parts). If T(s) is a rational fraction of the form N(s) / D(s), where N(s) and D(s) are polynomials, then we can write

$$\frac{T(s)}{1+T(s)} = \frac{\frac{N(s)}{D(s)}}{1+\frac{N(s)}{D(s)}} = \frac{N(s)}{N(s)+D(s)}$$
$$\frac{1}{1+T(s)} = \frac{1}{1+\frac{N(s)}{D(s)}} = \frac{D(s)}{N(s)+D(s)}$$

 Could evaluate stability by evaluating N(s) + D(s), then factoring to evaluate roots. This is a lot of work, and is not very illuminating.

Fundamentals of Power Electronics

Determination of stability directly from T(s)

- Nyquist stability theorem: general result.
- A special case of the Nyquist stability theorem: the phase margin test

Allows determination of closed-loop stability (i.e., whether 1/(1+T(s)) contains RHP poles) directly from the magnitude and phase of T(s).

A good design tool: yields insight into how T(s) should be shaped, to obtain good performance in transfer functions containing 1/(1+T(s)) terms.

9.4.1. The phase margin test

A test on T(s), to determine whether 1/(1+T(s)) contains RHP poles.

The crossover frequency f_c is defined as the frequency where

 $|| T(j2\pi f_c) || = 1 \Rightarrow 0 dB$


The phase margin φ_m is determined from the phase of T(s) at f_c , as follows:

 $\varphi_m = 180^\circ + \angle T(j2\pi f_c)$

If there is exactly one crossover frequency, and if T(s) contains no RHP poles, then


the quantities T(s)/(1+T(s)) and 1/(1+T(s)) contain no RHP poles whenever the phase margin φ_m is positive.

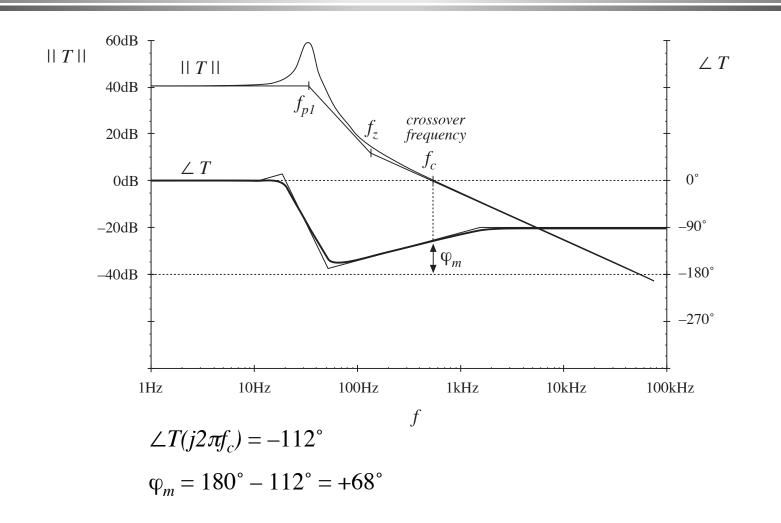Example: a loop gain leading to a stable closed-loop system



Fundamentals of Power Electronics

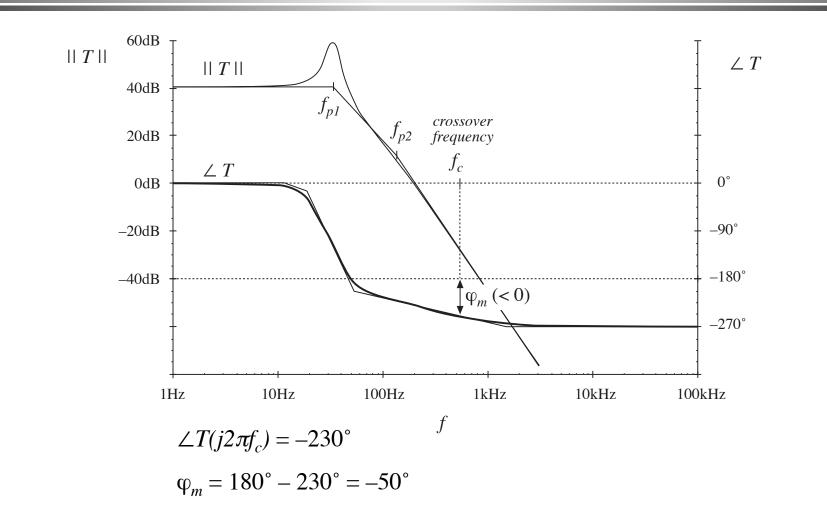Example: a loop gain leading to an unstable closed-loop system



Fundamentals of Power Electronics

9.4.2. The relation between phase margin and closed-loop damping factor


How much phase margin is required?

A small positive phase margin leads to a stable closed-loop system having complex poles near the crossover frequency with high Q. The transient response exhibits overshoot and ringing.

Increasing the phase margin reduces the Q. Obtaining real poles, with no overshoot and ringing, requires a large phase margin.

The relation between phase margin and closed-loop Q is quantified in this section.

A simple second-order system

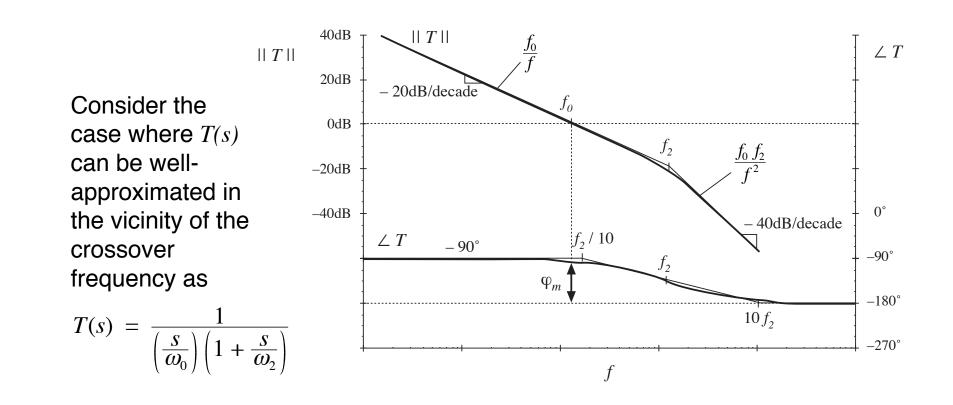

Closed-loop response

lf

$$T(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

Then

$$\frac{T(s)}{1+T(s)} = \frac{1}{1+\frac{1}{T(s)}} = \frac{1}{1+\frac{s}{\omega_0} + \frac{s^2}{\omega_0\omega_2}}$$

or,


$$\frac{T(s)}{1+T(s)} = \frac{1}{1+\frac{s}{Q\omega_c} + \left(\frac{s}{\omega_c}\right)^2}$$

where

$$\omega_c = \sqrt{\omega_0 \omega_2} = 2\pi f_c$$
 $Q = \frac{\omega_0}{\omega_c} = \sqrt{\frac{\omega_0}{\omega_2}}$


Fundamentals of Power Electronics

Low-Q case

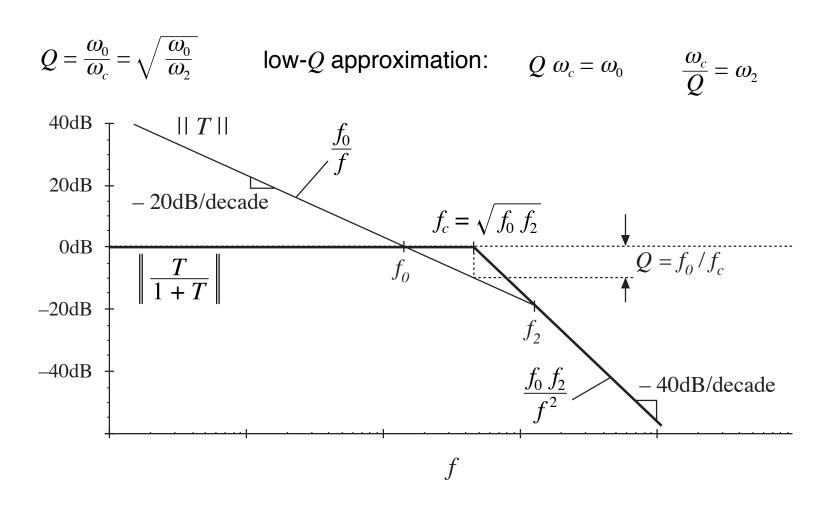

Fundamentals of Power Electronics

High-*Q* case

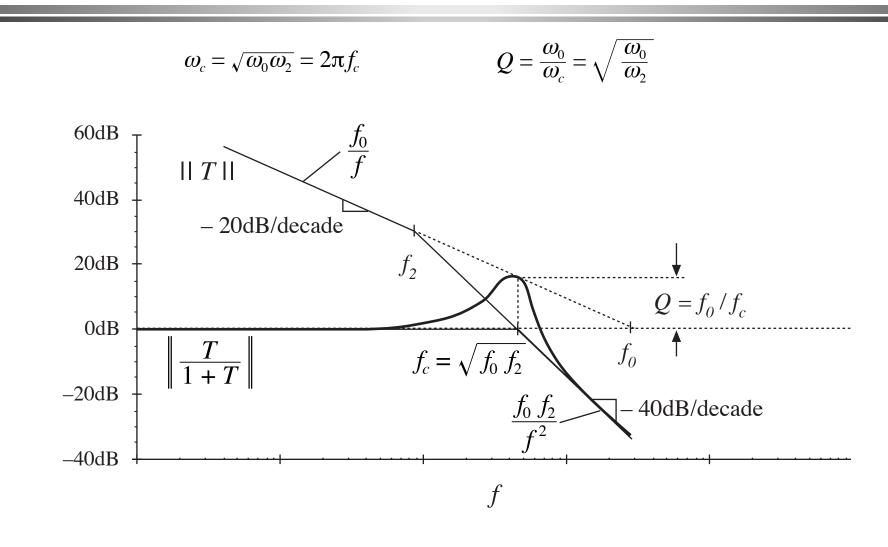


Fundamentals of Power Electronics

$$Q$$
 vs. φ_m

Solve for exact crossover frequency, evaluate phase margin, express as function of ϕ_m . Result is:

$$Q = \frac{\sqrt{\cos \varphi_m}}{\sin \varphi_m}$$
$$\varphi_m = \tan^{-1} \sqrt{\frac{1 + \sqrt{1 + 4Q^4}}{2Q^4}}$$

$$Q$$
 vs. φ_m

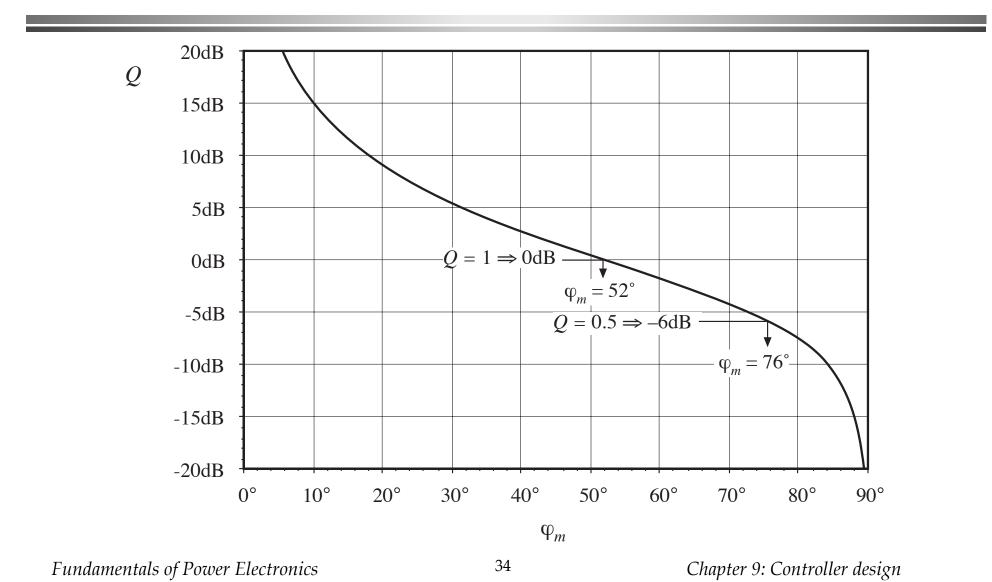

9.4.3. Transient response vs. damping factor

Unit-step response of second-order system T(s)/(1+T(s))

$$\hat{v}(t) = 1 + \frac{2Q \ e^{-\omega_c t/2Q}}{\sqrt{4Q^2 \pm 1}} \sin \left[\frac{\sqrt{4Q^2 \pm 1}}{2Q} \ \omega_c \ t + \tan^{-1} \left(\sqrt{4Q^2 \pm 1} \right) \right] \qquad Q > 0.5$$

$$\omega_1, \, \omega_2 = \frac{\omega_c}{2Q} \left(1 \pm \sqrt{1 \pm 4Q^2}\right)$$


For Q > 0.5, the peak value is

peak
$$\hat{v}(t) = 1 + e^{\pm \pi / \sqrt{4Q^2 \pm 1}}$$

Fundamentals of Power Electronics

т

Transient response vs. damping factor

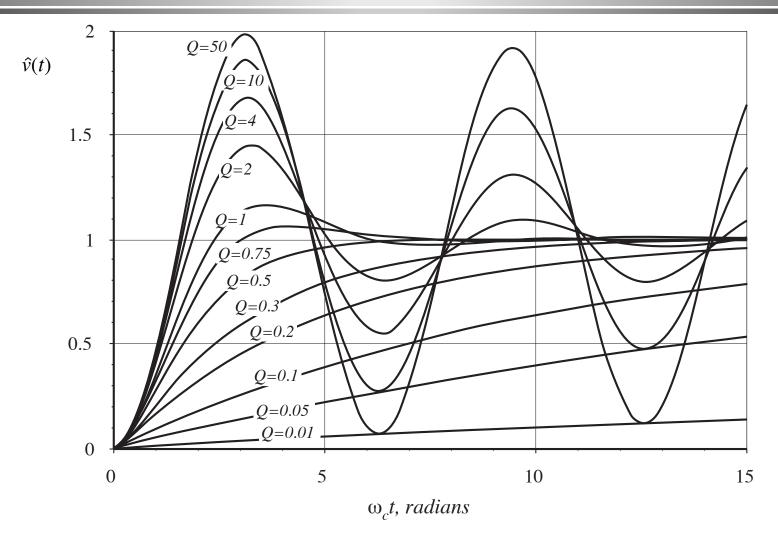

Fundamentals of Power Electronics

9.5. Regulator design

Typical specifications:

- Effect of load current variations on output voltage regulation This is a limit on the maximum allowable output impedance
- Effect of input voltage variations on the output voltage regulation

This limits the maximum allowable line-to-output transfer function

Transient response time


This requires a sufficiently high crossover frequency

Overshoot and ringing


An adequate phase margin must be obtained

The regulator design problem: add compensator network $G_c(s)$ to modify T(s) such that all specifications are met.

9.5.1. Lead (PD) compensator

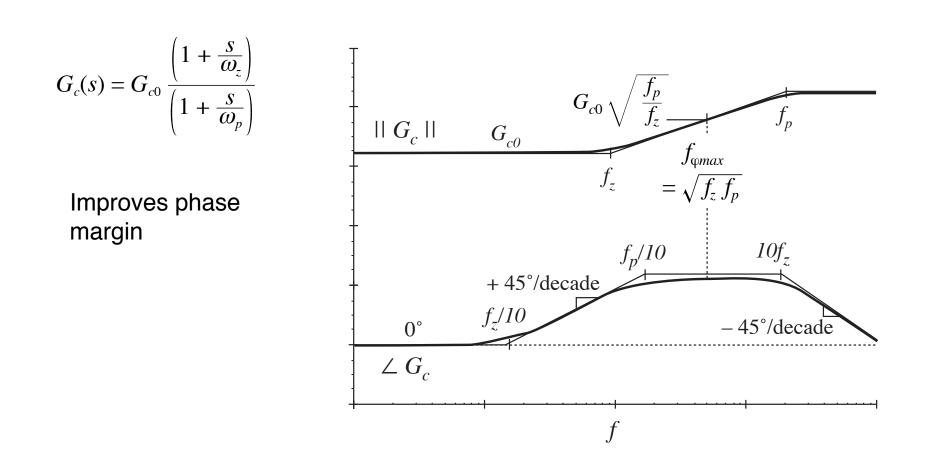

Lead compensator: maximum phase lead

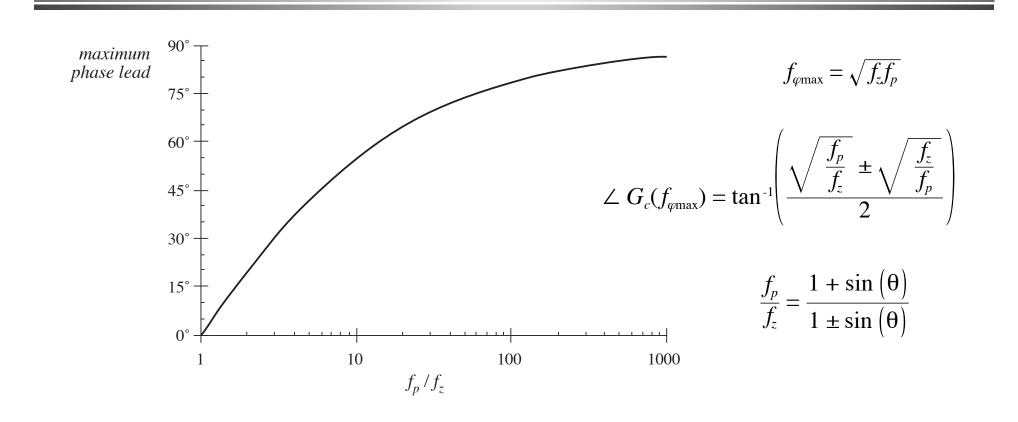


Lead compensator design

To optimally obtain a compensator phase lead of θ at frequency f_c , the pole and zero frequencies should be chosen as follows:


$$f_{z} = f_{c} \sqrt{\frac{1 \pm \sin(\theta)}{1 + \sin(\theta)}}$$
$$f_{p} = f_{c} \sqrt{\frac{1 + \sin(\theta)}{1 \pm \sin(\theta)}}$$

If it is desired that the magnitude of the compensator gain at f_c be unity, then G_{c0} should be chosen as


$$G_{c0} = \sqrt{\frac{f_z}{f_p}}$$

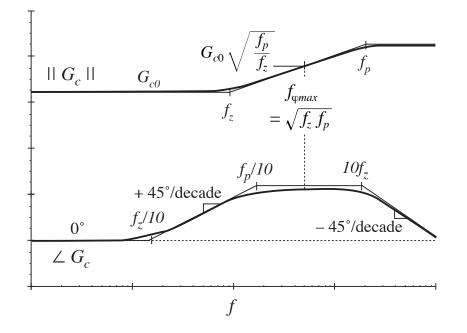


Example: lead compensation

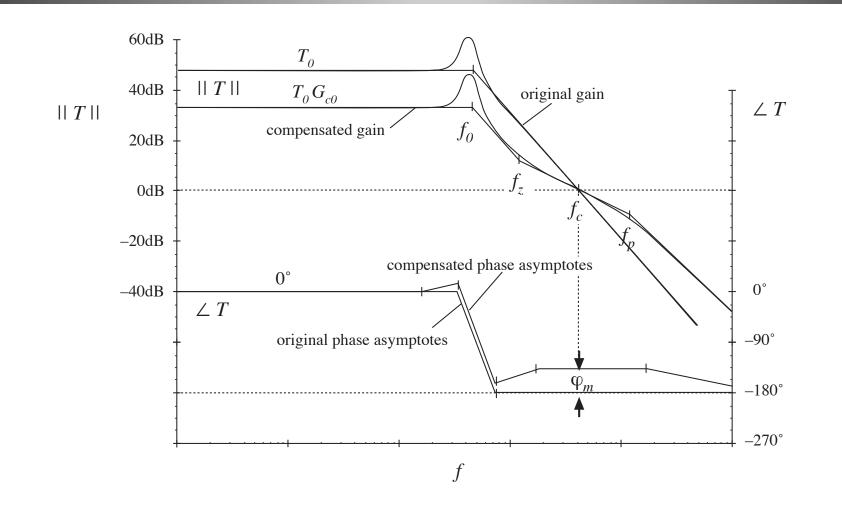

9.5.2. Lag (PI) compensation

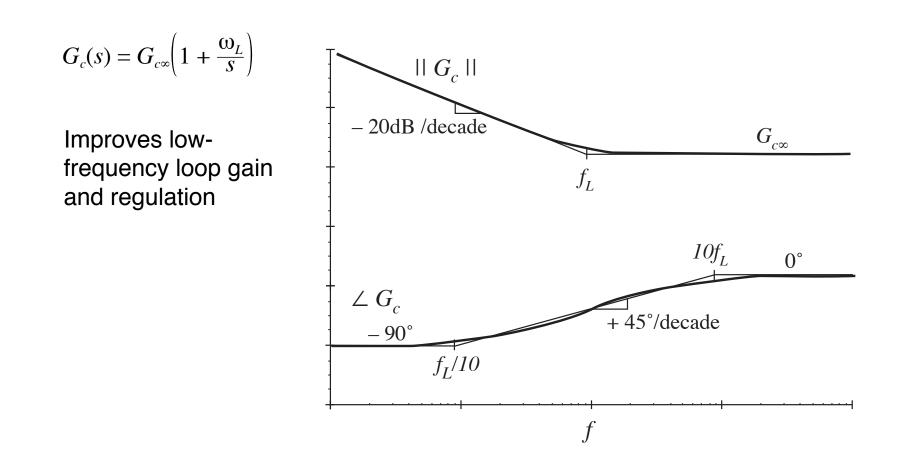


Example: lag compensation

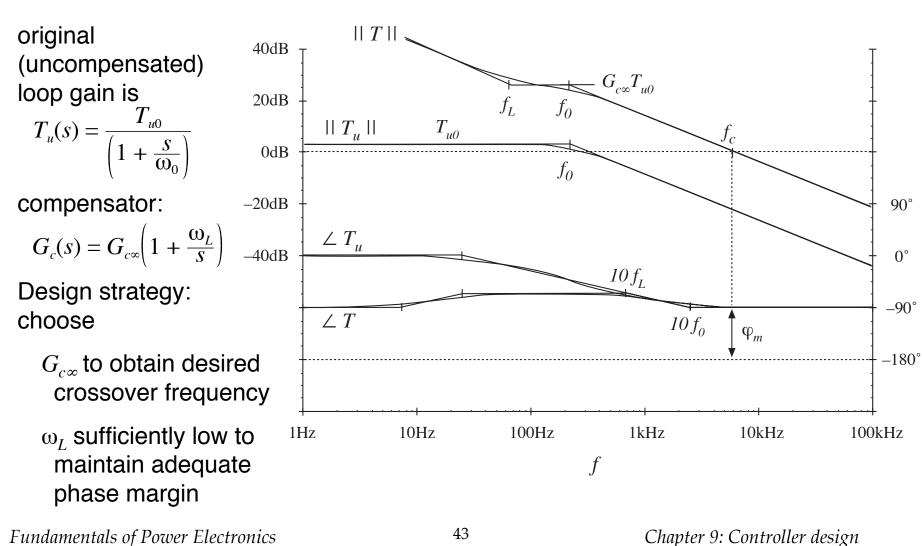

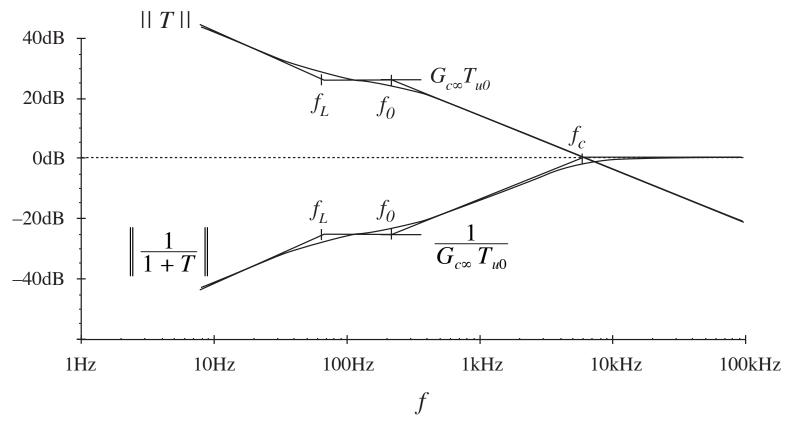
Example, continued

Construction of 1/(1+T), lag compensator example:




Fundamentals of Power Electronics

9.5.3. Combined (PID) compensator

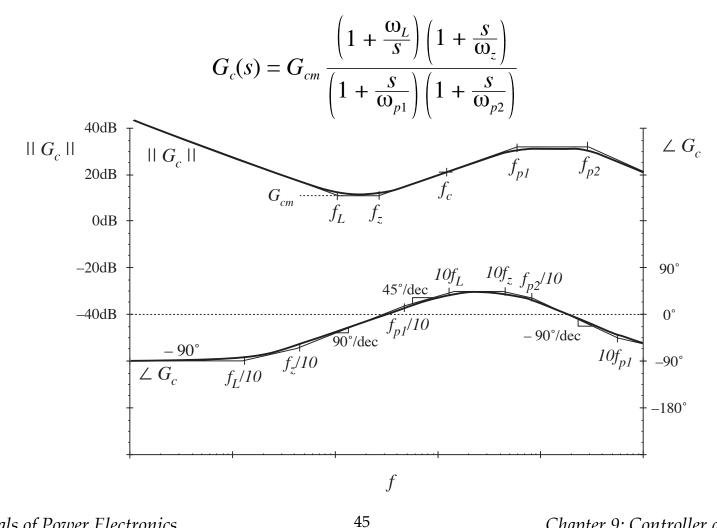

Fundamentals of Power Electronics


9.5.4. Design example

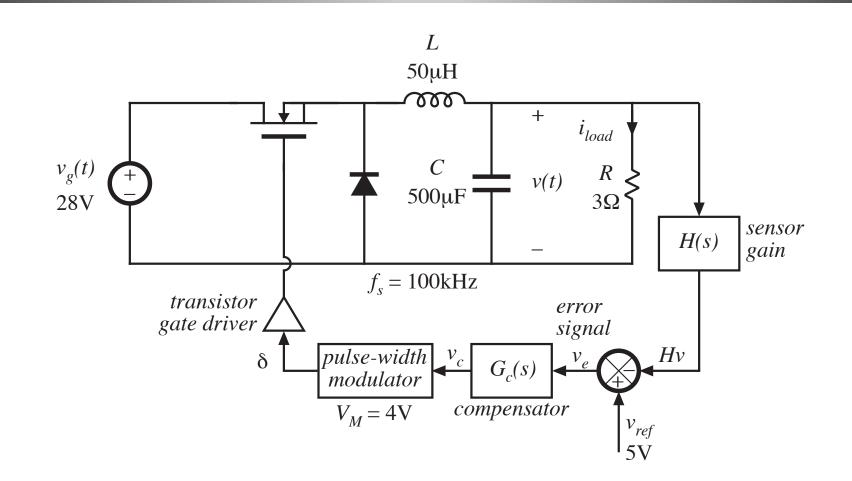

Quiescent operating point


Input voltage	$V_g = 28$ V
Output	$V = 15$ V, $I_{load} = 5$ A, $R = 3\Omega$
Quiescent duty cycle	D = 15/28 = 0.536
Reference voltage	$V_{ref} = 5 \mathrm{V}$
Quiescent value of control voltage	$V_c = DV_M = 2.14$ V
Gain H(s)	$H = V_{ref}/V = 5/15 = 1/3$

Small-signal model

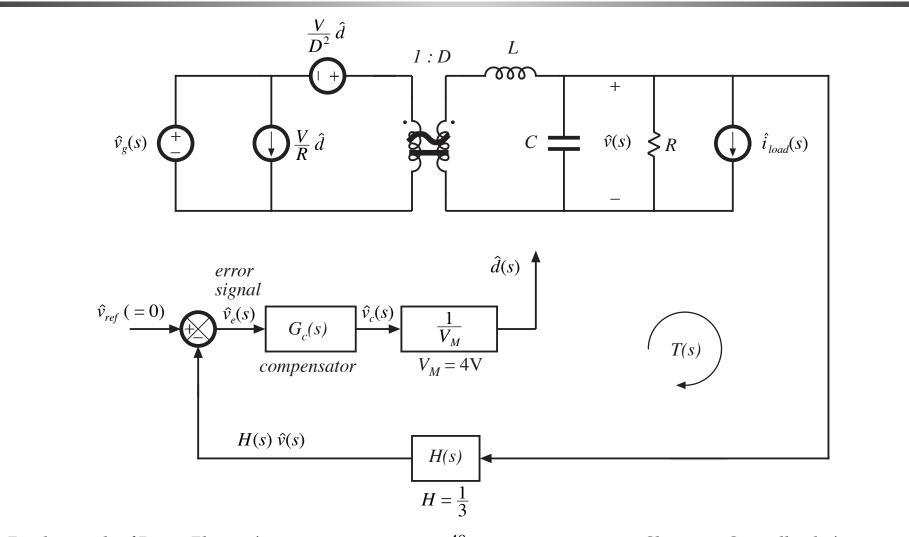

Fundamentals of Power Electronics

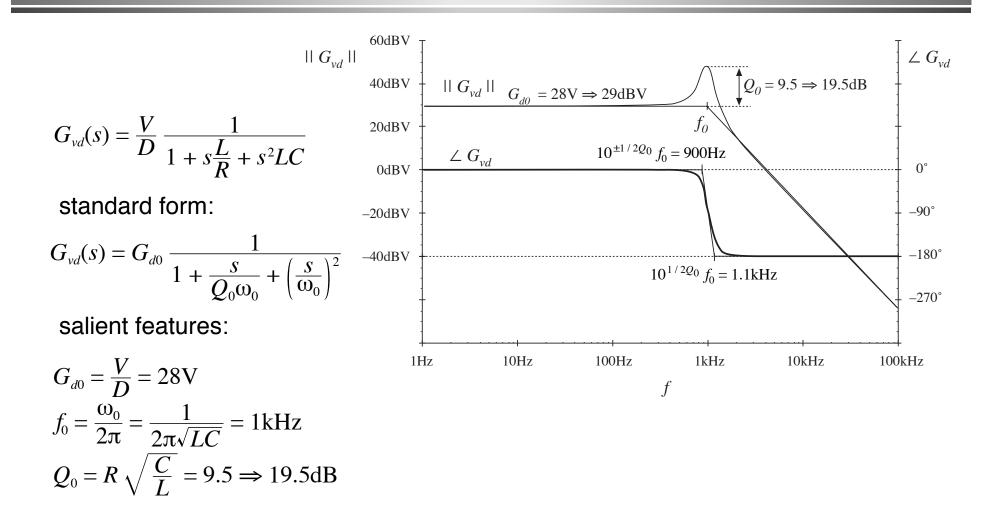Open-loop control-to-output transfer function $G_{vd}(s)$



Open-loop line-to-output transfer function and output impedance

$$G_{vg}(s) = D \frac{1}{1 + s\frac{L}{R} + s^2 LC}$$


—same poles as control-to-output transfer function standard form:

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$


Output impedance:

$$Z_{out}(s) = R \parallel \frac{1}{sC} \parallel sL = \frac{sL}{1 + s\frac{L}{R} + s^2LC}$$

System block diagram

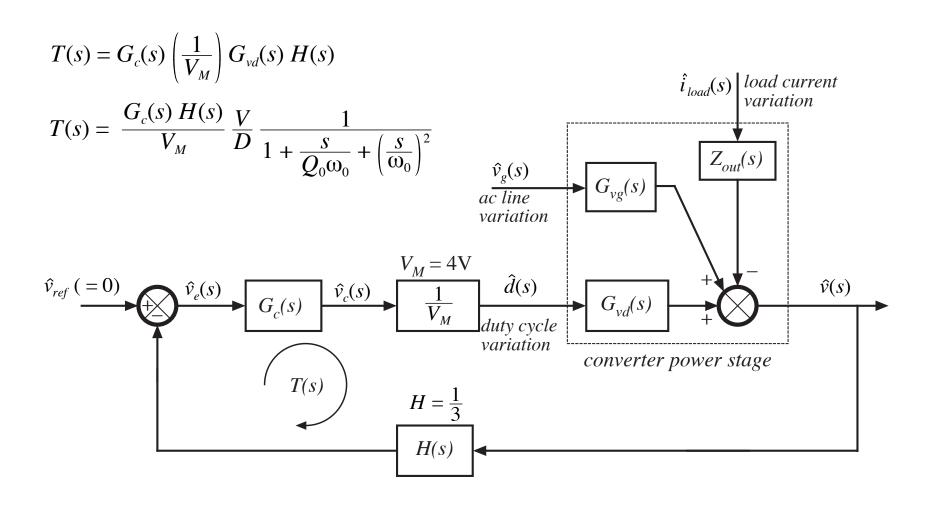

Uncompensated loop gain (with $G_c = 1$)

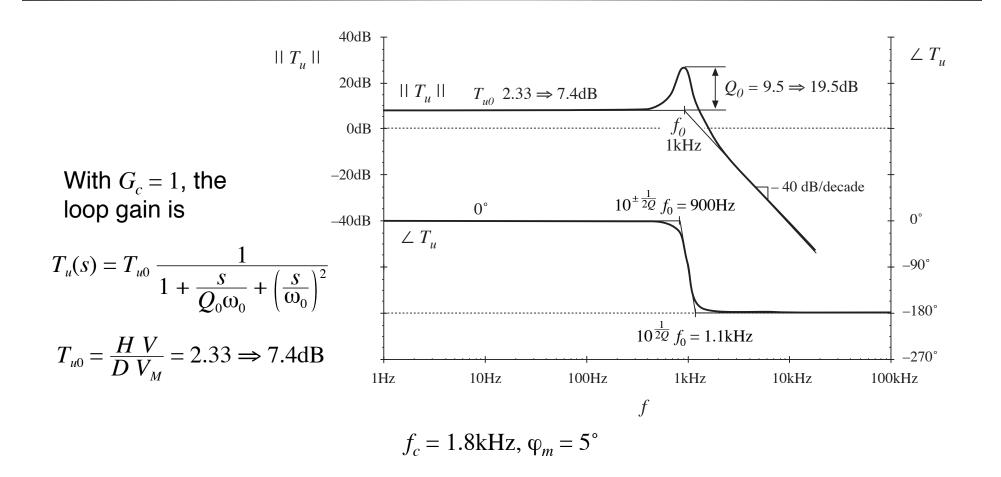


Lead compensator design

- Obtain a crossover frequency of 5kHz, with phase margin of 52°
- T_u has phase of approximately -180° at 5kHz, hence lead (PD) compensator is needed to increase phase margin.
- Lead compensator should have phase of +52° at 5kHz
- T_u has magnitude of -20.6dB at 5kHz
- Lead compensator gain should have magnitude of +20.6dB at 5kHz
- Lead compensator pole and zero frequencies should be

$$f_z = (5\text{kHz}) \sqrt{\frac{1 \pm \sin(52^\circ)}{1 + \sin(52^\circ)}} = 1.7\text{kHz}$$
$$f_p = (5\text{kHz}) \sqrt{\frac{1 + \sin(52^\circ)}{1 \pm \sin(52^\circ)}} = 14.5\text{kHz}$$


• Compensator dc gain should be $G_{c0} = \left(\frac{f_c}{f_0}\right)^2 \frac{1}{T_{u0}} \sqrt{\frac{f_z}{f_p}} = 3.7 \Rightarrow 11.3 \text{dB}$

Lead compensator Bode plot

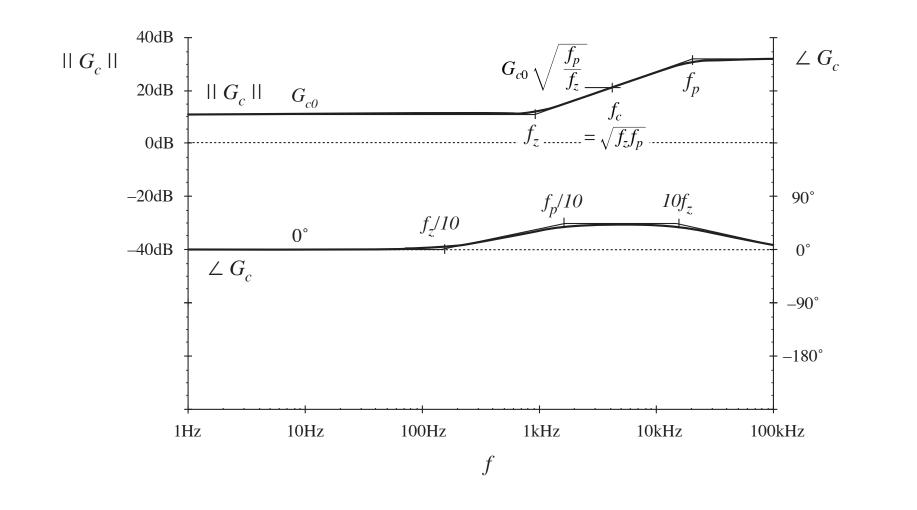


Fundamentals of Power Electronics

Loop gain, with lead compensator

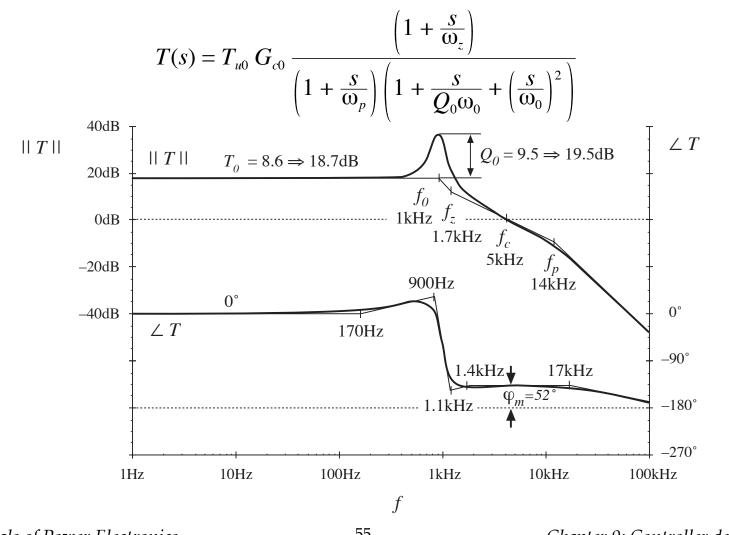


Fundamentals of Power Electronics

1/(1+T), with lead compensator

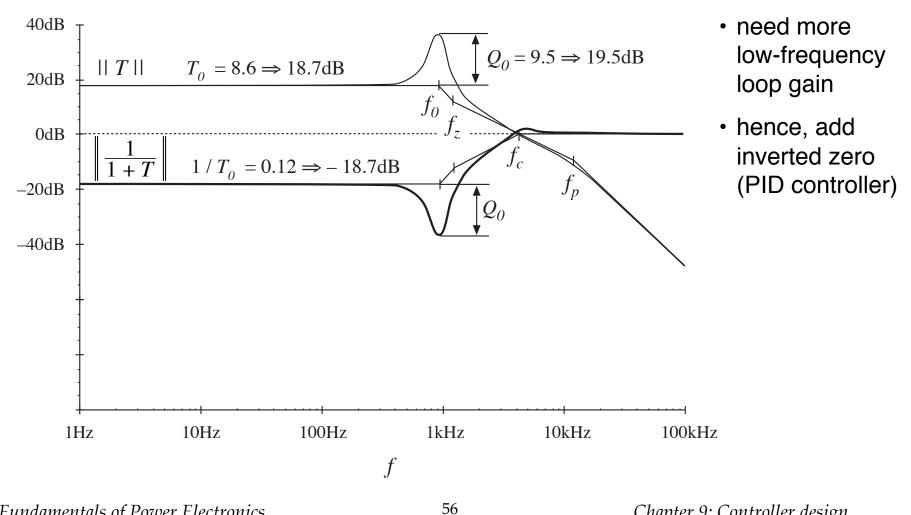


Improved compensator (PID)

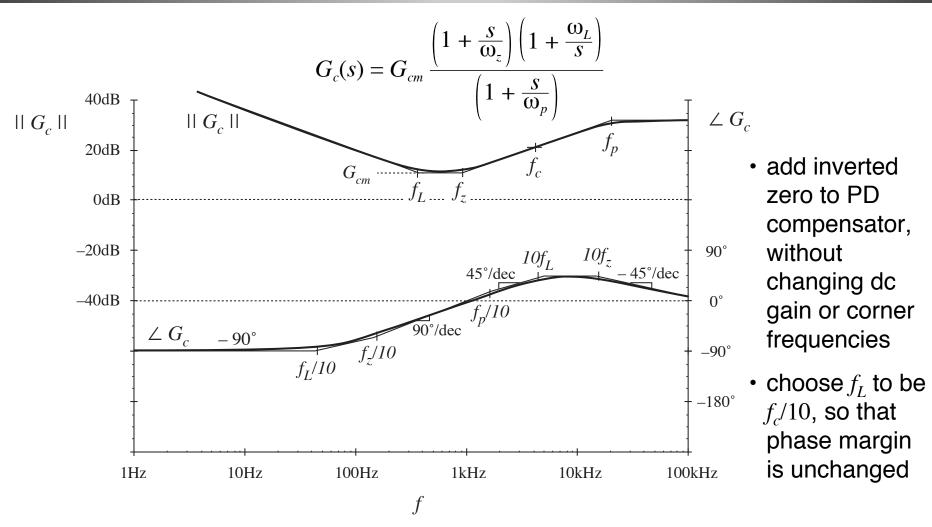


Fundamentals of Power Electronics

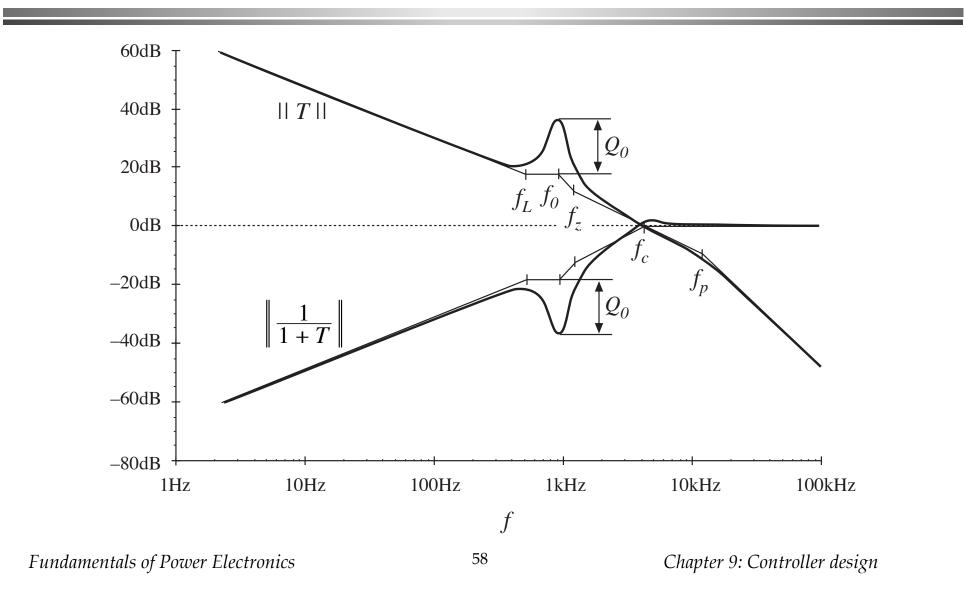T(s) and 1/(1+T(s)), with PID compensator




Line-to-output transfer function

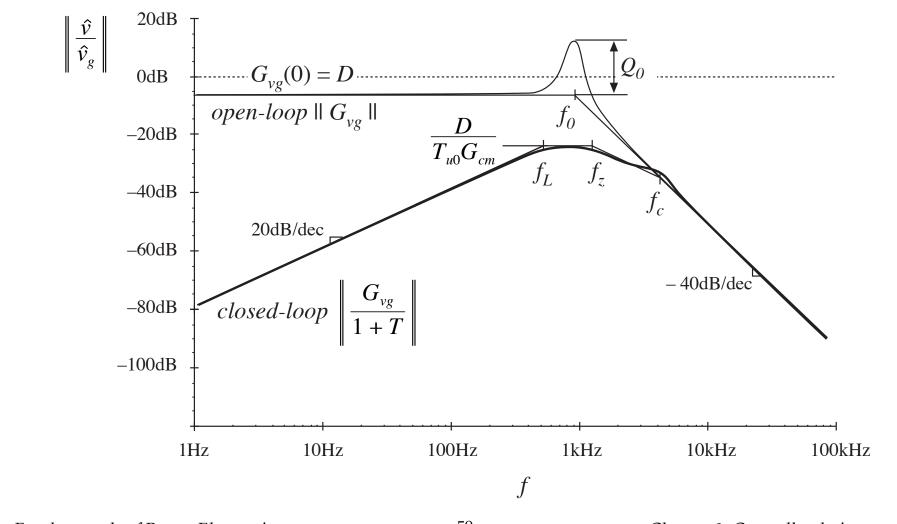


Fundamentals of Power Electronics

9.6. Measurement of loop gains

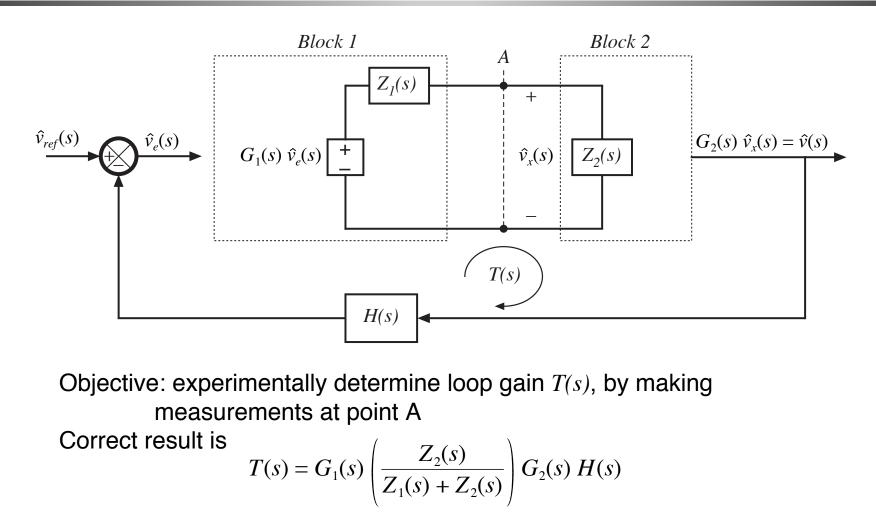

Fundamentals of Power Electronics

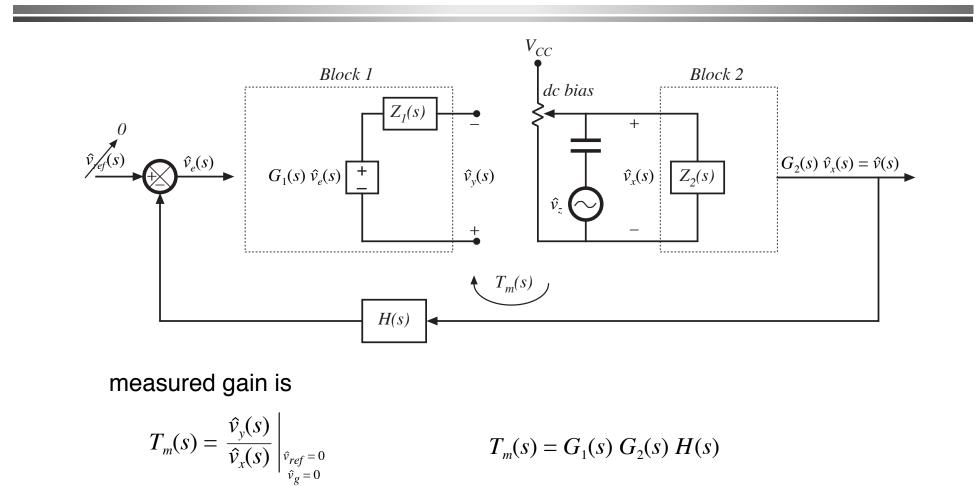Conventional approach: break loop, measure T(s) as conventional transfer function



Measured vs. actual loop gain

Actual loop gain:

$$T(s) = G_1(s) \left(\frac{Z_2(s)}{Z_1(s) + Z_2(s)} \right) G_2(s) H(s)$$

Measured loop gain:

 $T_m(s) = G_1(s) \ G_2(s) \ H(s)$

Express T_m as function of T:


$$T_m(s) = T(s) \left(1 + \frac{Z_1(s)}{Z_2(s)}\right)$$

 $T_m(s) \approx T(s)$ provided that $||Z_2|| >> ||Z_1||$

Discussion


- Breaking the loop disrupts the loading of block 2 on block 1.
 - A suitable injection point must be found, where loading is not significant.
- Breaking the loop disrupts the dc biasing and quiescent operating point.
 - A potentiometer must be used, to correctly bias the input to block 2.
 - In the common case where the dc loop gain is large, it is very difficult to correctly set the dc bias.
- It would be desirable to avoid breaking the loop, such that the biasing circuits of the system itself set the quiescent operating point.

9.6.1. Voltage injection

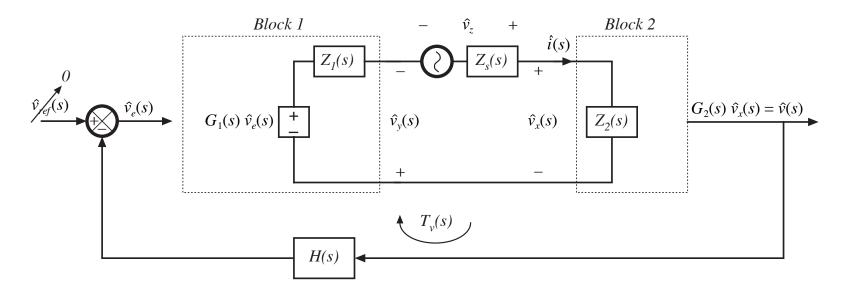

- Ac injection source v_z is connected between blocks 1 and 2
- · Dc bias is determined by biasing circuits of the system itself
- Injection source does modify loading of block 2 on block 1

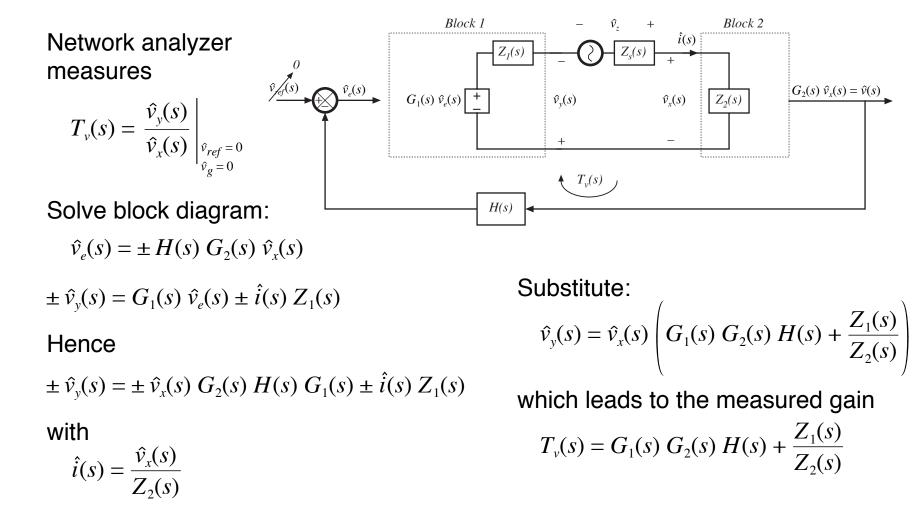Voltage injection: measured transfer function $T_v(s)$



Fundamentals of Power Electronics

Comparison of $T_v(s)$ with T(s)

Actual loop gain is

Gain measured via voltage injection:

 $T_{v}(s) = G_{1}(s) \ G_{2}(s) \ H(s) + \frac{Z_{1}(s)}{Z_{2}(s)}$

$$T(s) = G_1(s) \left(\frac{Z_2(s)}{Z_1(s) + Z_2(s)} \right) G_2(s) H(s)$$


Express Tv(s) in terms of T(s):

$$T_{\nu}(s) = T(s) \left(1 + \frac{Z_1(s)}{Z_2(s)}\right) + \frac{Z_1(s)}{Z_2(s)}$$


Condition for accurate measurement:

$$T_{\nu}(s) \approx T(s)$$
 provided (i) $||Z_1(s)|| \ll ||Z_2(s)||$, and
(ii) $||T(s)|| \gg ||\frac{Z_1(s)}{Z_2(s)}||$

Example: voltage injection

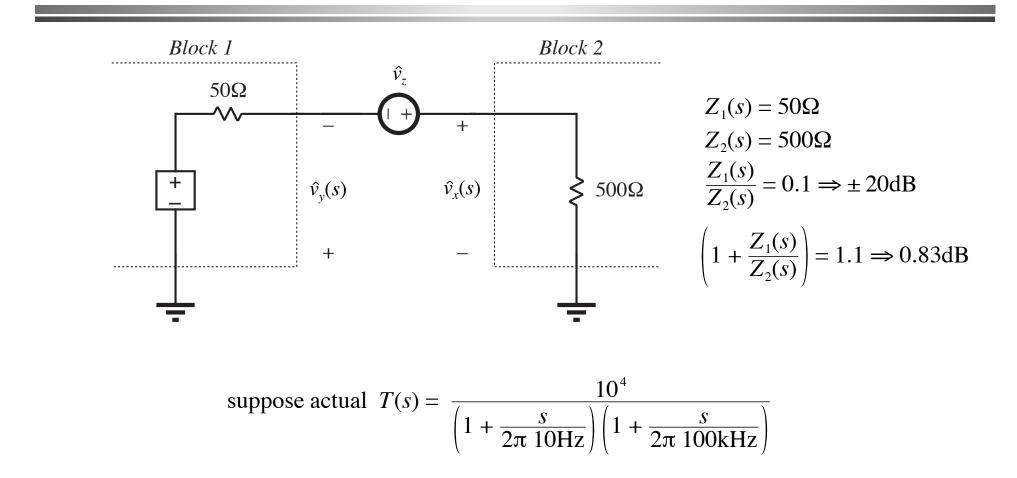


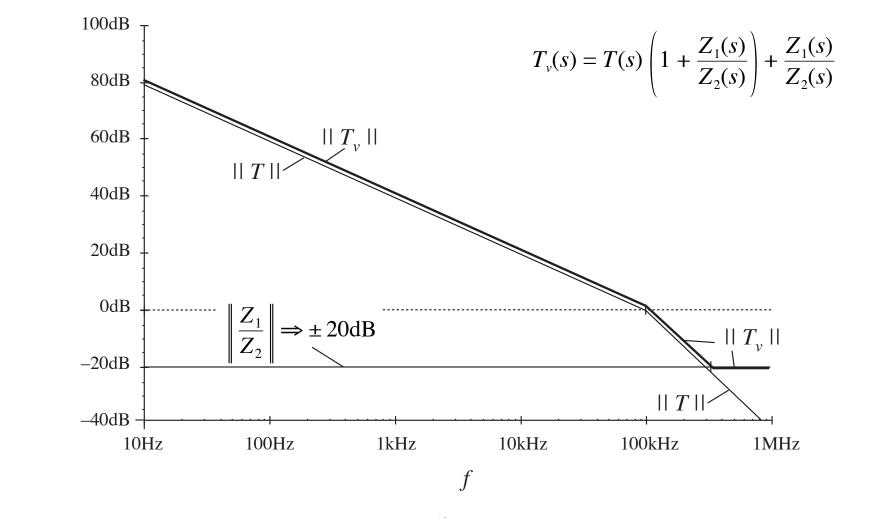
Example: measured $T_v(s)$ and actual T(s)



Fundamentals of Power Electronics

9.6.2. Current injection

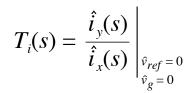

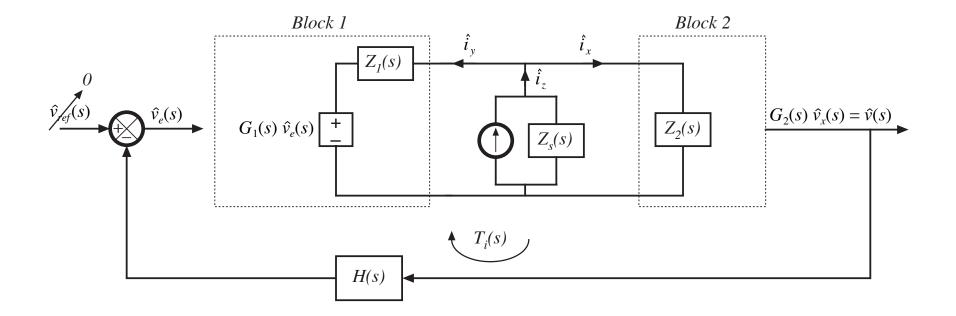


Current injection

It can be shown that

$$T_i(s) = T(s) \left(1 + \frac{Z_2(s)}{Z_1(s)}\right) + \frac{Z_2(s)}{Z_1(s)}$$

Conditions for obtaining accurate measurement:


(*i*) $||Z_2(s)|| << ||Z_1(s)||$, and (*ii*) $||T(s)|| >> ||\frac{Z_2(s)}{Z_1(s)}||$ Injection source impedance Z_s is irrelevant. We could inject using a Thevenin-equivalent voltage source:

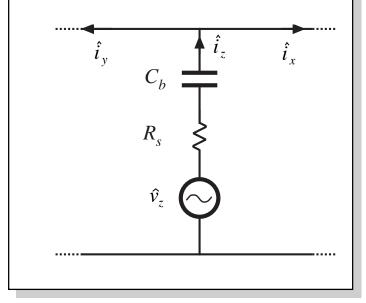

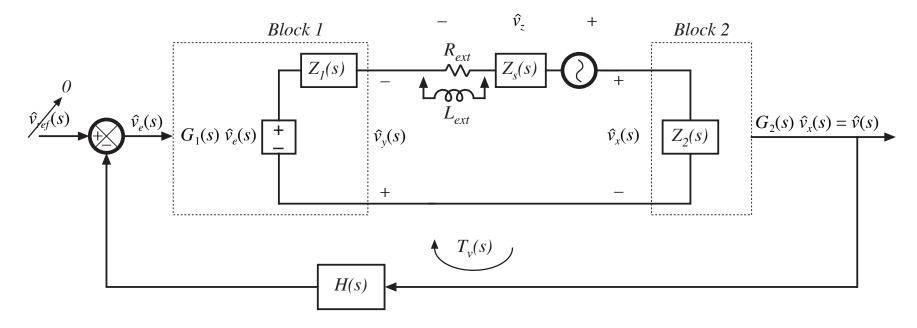9.6.3. Measurement of unstable systems

- Injection source impedance Z_s does not affect measurement
- Increasing Z_s reduces loop gain of circuit, tending to stabilize system

 Original (unstable) loop gain is measured (not including Z_s), while circuit operates stabily



9.7. Summary of key points

- 1. Negative feedback causes the system output to closely follow the reference input, according to the gain 1 / H(s). The influence on the output of disturbances and variation of gains in the forward path is reduced.
- 2. The loop gain T(s) is equal to the products of the gains in the forward and feedback paths. The loop gain is a measure of how well the feedback system works: a large loop gain leads to better regulation of the output. The crossover frequency f_c is the frequency at which the loop gain T has unity magnitude, and is a measure of the bandwidth of the control system.

Summary of key points

- 3. The introduction of feedback causes the transfer functions from disturbances to the output to be multiplied by the factor 1/(1+T(s)). At frequencies where *T* is large in magnitude (i.e., below the crossover frequency), this factor is approximately equal to 1/T(s). Hence, the influence of low-frequency disturbances on the output is reduced by a factor of 1/T(s). At frequencies where *T* is small in magnitude (i.e., above the crossover frequency), the factor is approximately equal to 1. The feedback loop then has no effect. Closed-loop disturbance-to-output transfer functions, such as the line-to-output transfer function or the output impedance, can easily be constructed using the algebra-on-the-graph method.
- 4. Stability can be assessed using the phase margin test. The phase of *T* is evaluated at the crossover frequency, and the stability of the important closed-loop quantities T/(1+T) and 1/(1+T) is then deduced. Inadequate phase margin leads to ringing and overshoot in the system transient response, and peaking in the closed-loop transfer functions.

Summary of key points


- 5. Compensators are added in the forward paths of feedback loops to shape the loop gain, such that desired performance is obtained. Lead compensators, or PD controllers, are added to improve the phase margin and extend the control system bandwidth. PI controllers are used to increase the low-frequency loop gain, to improve the rejection of low-frequency disturbances and reduce the steady-state error.
- 6. Loop gains can be experimentally measured by use of voltage or current injection. This approach avoids the problem of establishing the correct quiescent operating conditions in the system, a common difficulty in systems having a large dc loop gain. An injection point must be found where interstage loading is not significant. Unstable loop gains can also be measured.

Chapter 10 Ac and Dc Equivalent Circuit Modeling of the Discontinuous Conduction Mode

Introduction

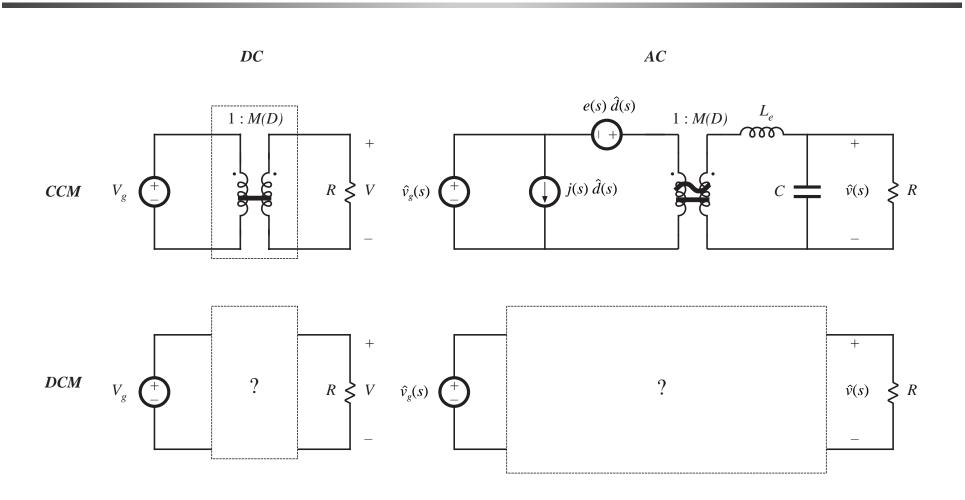- 10.1. DCM Averaged Switch Model
- 10.2. Small-Signal AC Modeling of the DCM Switch Network
- 10.3. Generalized Averaged Switch Modeling
- 10.4. Summary of Key Points

We are missing ac and dc equivalent circuit models for the discontinuous conduction mode




Change in characteristics at the CCM/DCM boundary

- Steady-state output voltage becomes strongly load-dependent
- Simpler dynamics: one pole and the RHP zero are moved to very high frequency, and can normally be ignored
- Traditionally, boost and buck-boost converters are designed to operate in DCM at full load
- All converters may operate in DCM at light load


So we need equivalent circuits that model the steady-state and smallsignal ac models of converters operating in DCM The averaged switch approach will be employed

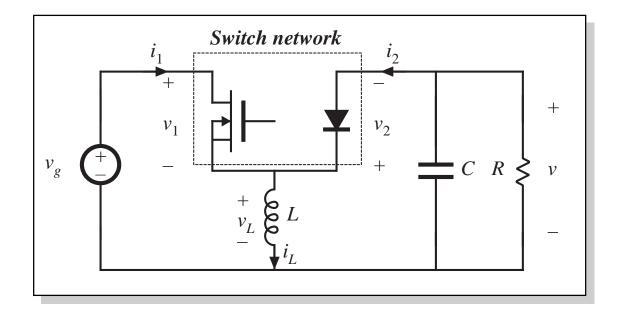10.1 Derivation of DCM averaged switch model: buck-boost example

- Define switch terminal quantities v₁, i₁, v₂, i₂, as shown
- Let us find the averaged quantities (v₁), (i₁), (v₂), (i₂), for operation in DCM, and determine the relations between them



DCM waveforms

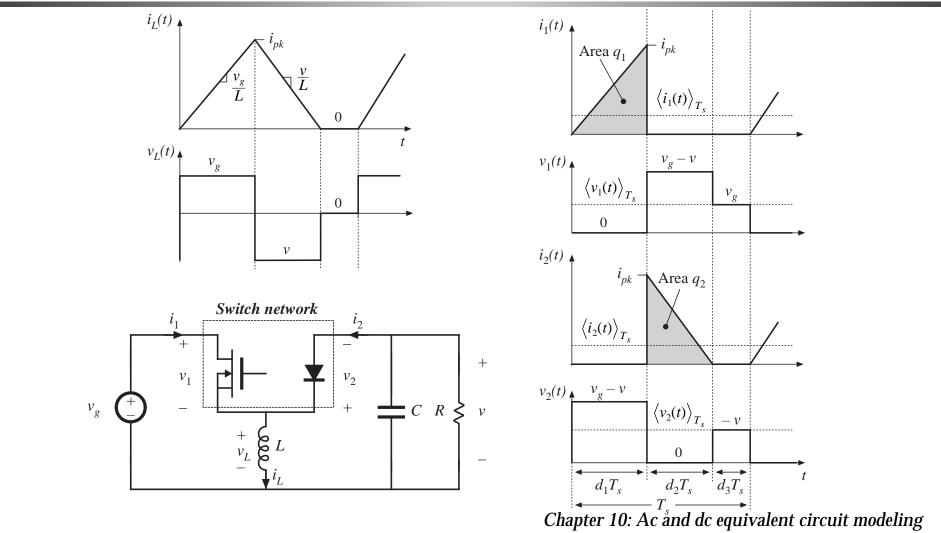

Fundamentals of Power Electronics

Basic DCM equations

Peak inductor current:

$$i_{pk} = \frac{v_g}{L} d_1 T_s$$

Average inductor voltage:


$$\left\langle v_{L}(t)\right\rangle_{T_{s}} = d_{1}\left\langle v_{g}(t)\right\rangle_{T_{s}} + d_{2}\left\langle v(t)\right\rangle_{T_{s}} + d_{3}\cdot 0$$

In DCM, the diode switches off when the inductor current reaches zero. Hence, $i(0) = i(T_s) = 0$, and the average inductor voltage is zero. This is true even during transients.

$$\left\langle v_{L}(t)\right\rangle_{T_{s}} = d_{1}(t)\left\langle v_{g}(t)\right\rangle_{T_{s}} + d_{2}(t)\left\langle v(t)\right\rangle_{T_{s}} = 0$$


Solve for d_2 :

$$d_{2}(t) = -d_{1}(t) \frac{\left\langle v_{g}(t) \right\rangle_{T_{s}}}{\left\langle v(t) \right\rangle_{T_{s}}}$$

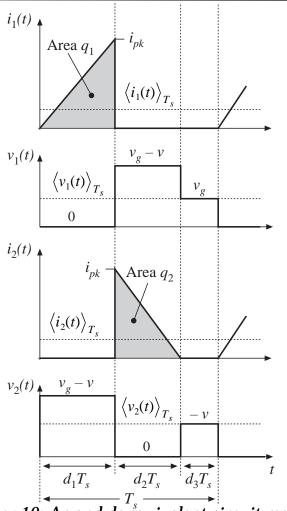

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Average switch network terminal voltages

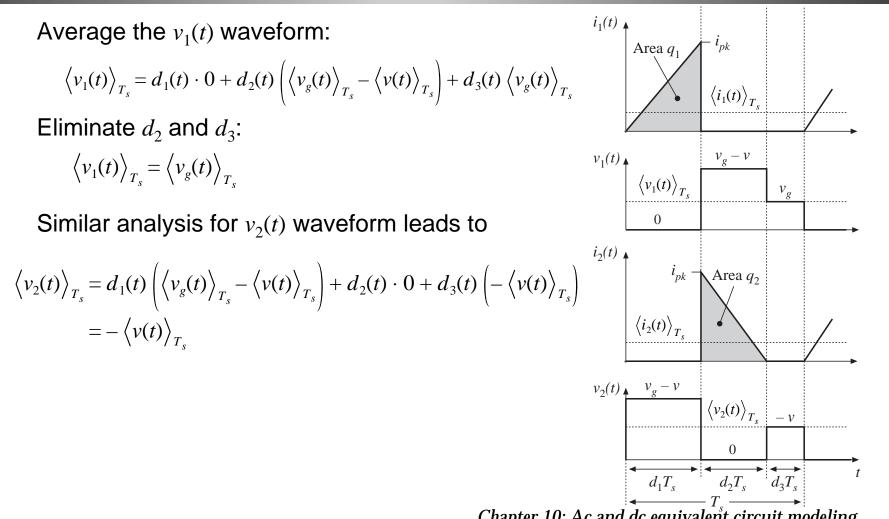

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Average switch network terminal currents

Average the $i_1(t)$ waveform:

$$\left\langle i_1(t) \right\rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_1(t) dt = \frac{q_1}{T_s}$$

The integral q_1 is the area under the $i_1(t)$ waveform during first subinterval. Use triangle area formula:

$$q_{1} = \int_{t}^{t+T_{s}} i_{1}(t) dt = \frac{1}{2} \left(d_{1}T_{s} \right) \left(i_{pk} \right)$$


Eliminate i_{pk} :


$$\left\langle i_1(t) \right\rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \left\langle v_1(t) \right\rangle_{T_s}$$

Note $\langle i_1(t) \rangle_{T_s}$ is not equal to $d \langle i_L(t) \rangle_{T_s}$!

Similar analysis for $i_2(t)$ waveform leads to

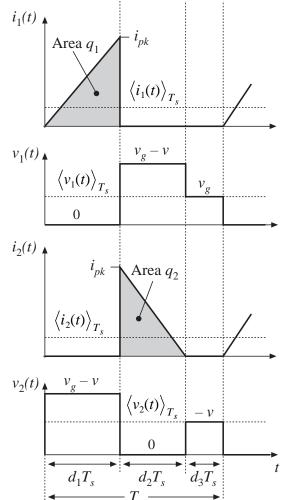
$$\left\langle i_{2}(t)\right\rangle_{T_{s}} = \frac{d_{1}^{2}(t) T_{s}}{2L} \frac{\left\langle v_{1}(t)\right\rangle_{T_{s}}^{2}}{\left\langle v_{2}(t)\right\rangle_{T_{s}}}$$



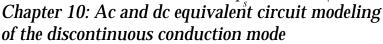


Input port: Averaged equivalent circuit
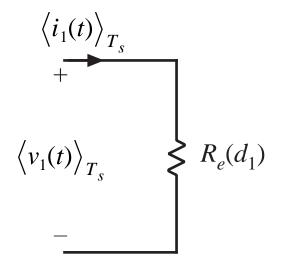
$$\left\langle i_{1}(t)\right\rangle_{T_{s}} = \frac{d_{1}^{2}(t) T_{s}}{2L} \left\langle v_{1}(t)\right\rangle_{T_{s}}$$
$$\left\langle i_{1}(t)\right\rangle_{T_{s}} = \frac{\left\langle v_{1}(t)\right\rangle_{T_{s}}}{R_{e}(d_{1})}$$
$$R_{e}(d_{1}) = \frac{2L}{d_{1}^{2} T_{s}}$$




9 Chapter 10: Ac and dc equivalent circuit modeling 9 of the discontinuous conduction mode

Output port: Averaged equivalent circuit

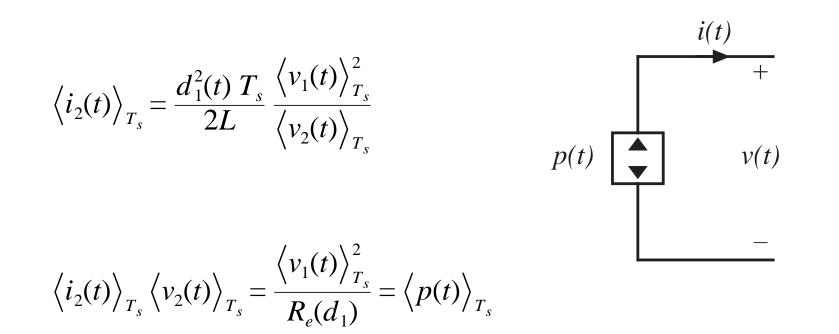

Fundamentals of Power Electronics

The dependent power source

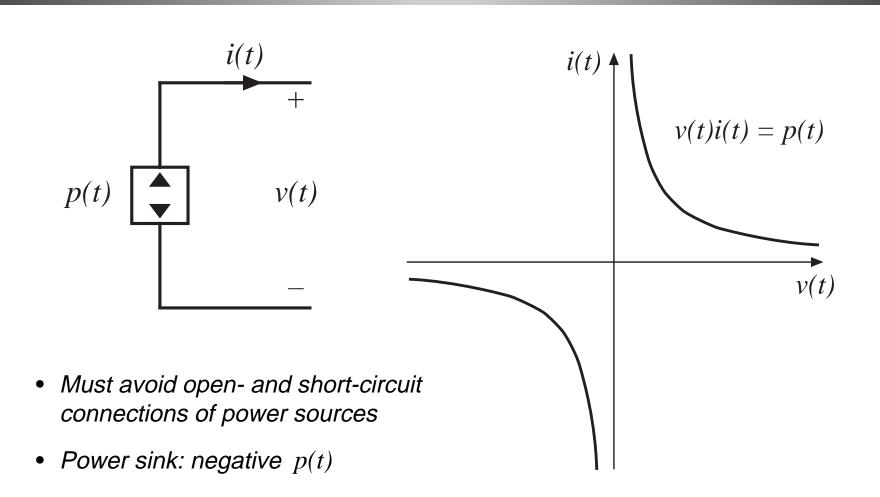

How the power source arises in lossless two-port networks


In a lossless two-port network without internal energy storage: instantaneous input power is equal to instantaneous output power

In all but a small number of special cases, the instantaneous power throughput is dependent on the applied external source and load


If the instantaneous power depends only on the external elements connected to one port, then the power is not dependent on the characteristics of the elements connected to the other port. The other port becomes a source of power, equal to the power flowing through the first port

A power source (or power sink) element is obtained

Properties of power sources

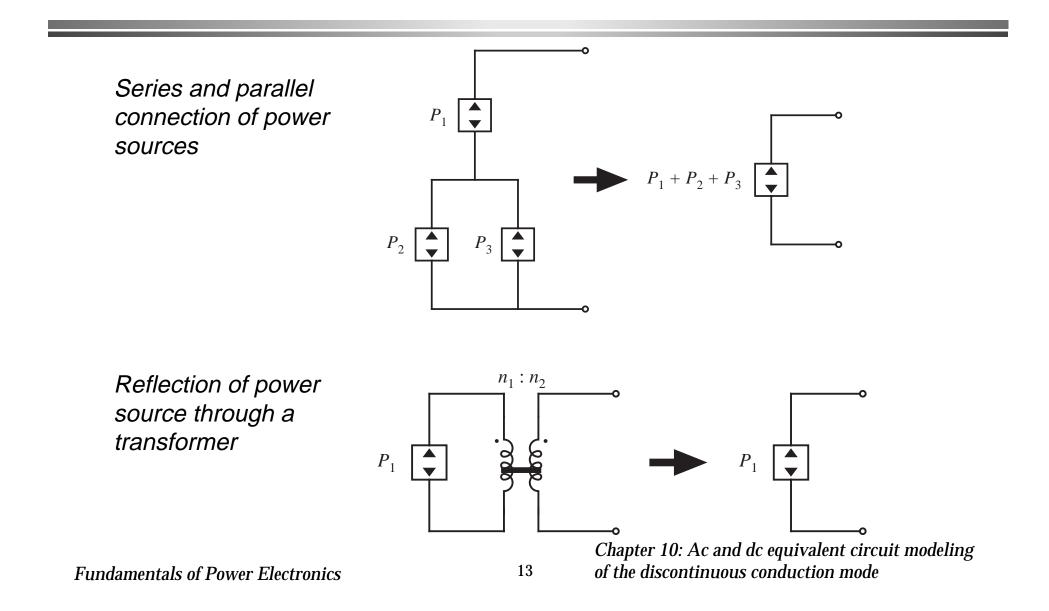

The loss-free resistor (LFR)

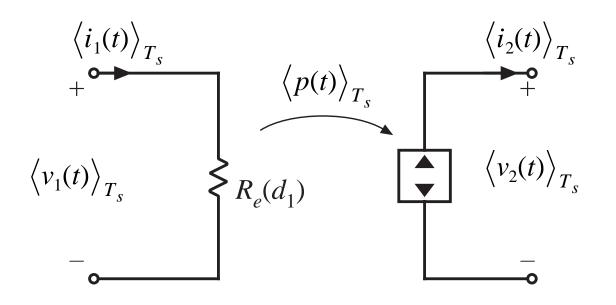


A two-port lossless network

Input port obeys Ohm's Law

Power entering input port is transferred to output port


Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

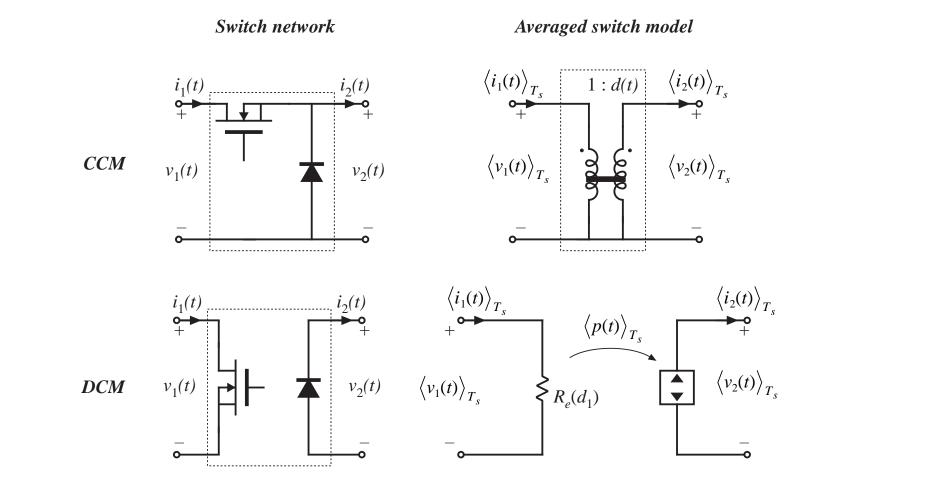Averaged modeling of CCM and DCM switch networks



Fundamentals of Power Electronics

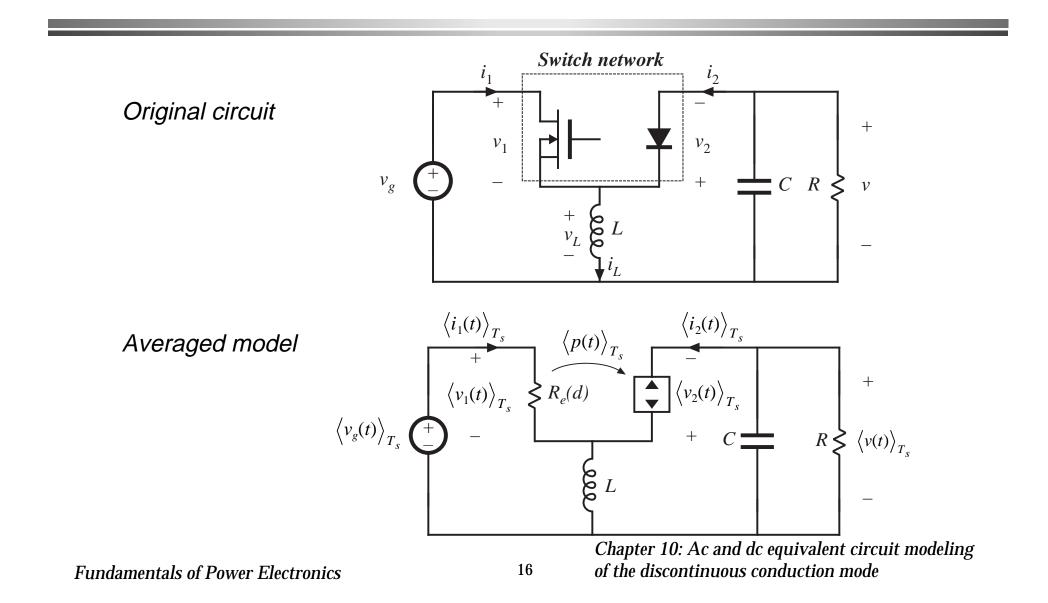Averaged switch model: buck-boost example




Solution of averaged model: steady state

Let

 $L \rightarrow$ short circuit

 $C \rightarrow \text{open circuit}$

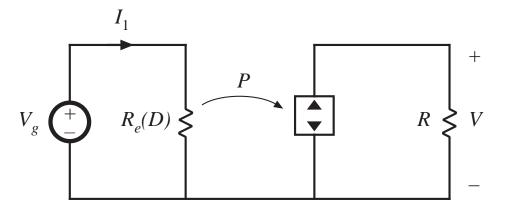

Converter input power:

$$P = \frac{V_g^2}{R_e}$$

Converter output power:

$$P = \frac{V^2}{R}$$

Fundamentals of Power Electronics

Equate and solve:

$$P = \frac{V_g^2}{R_e} = \frac{V^2}{R}$$

$$\frac{V}{V_g} = \pm \sqrt{\frac{R}{R_e}}$$

Steady-state LFR solution

$$\frac{V}{V_g} = \pm \sqrt{\frac{R}{R_e}}$$

is a general result, for any system that can be modeled as an LFR.

For the buck-boost converter, we have

$$R_e(D) = \frac{2L}{D^2 T_s}$$


Eliminate R_e :

$$\frac{V}{V_g} = -\sqrt{\frac{D^2 T_s R}{2L}} = -\frac{D}{\sqrt{K}}$$

which agrees with the previous steady-state solution of Chapter 5.

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

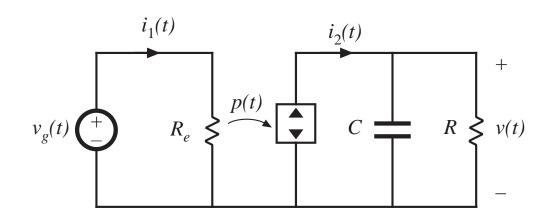Steady-state LFR solution with ac terminal waveforms



Converter average input power: $P_{av} = \frac{V_{g,rms}^2}{R_e}$

Converter average output power:

$$P_{av} = \frac{V_{rms}^2}{R}$$

Fundamentals of Power Electronics


Note that no average power flows into capacitor

Equate and solve:

$$\frac{V_{rms}}{V_{g,rms}} = \sqrt{\frac{R}{R_e}}$$


Averaged models of other DCM converters

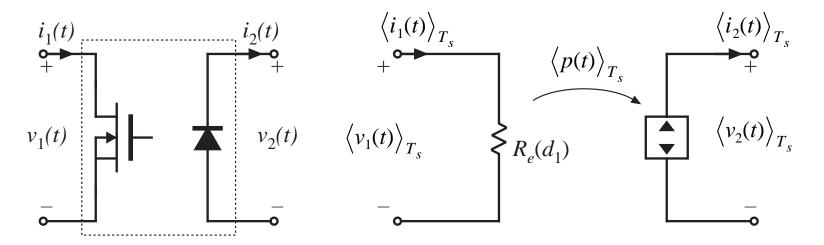- Determine averaged terminal waveforms of switch network
- In each case, averaged transistor waveforms obey Ohm's law, while averaged diode waveforms behave as dependent power source
- Can simply replace transistor and diode with the averaged model as follows:




Fundamentals of Power Electronics

DCM buck, boost

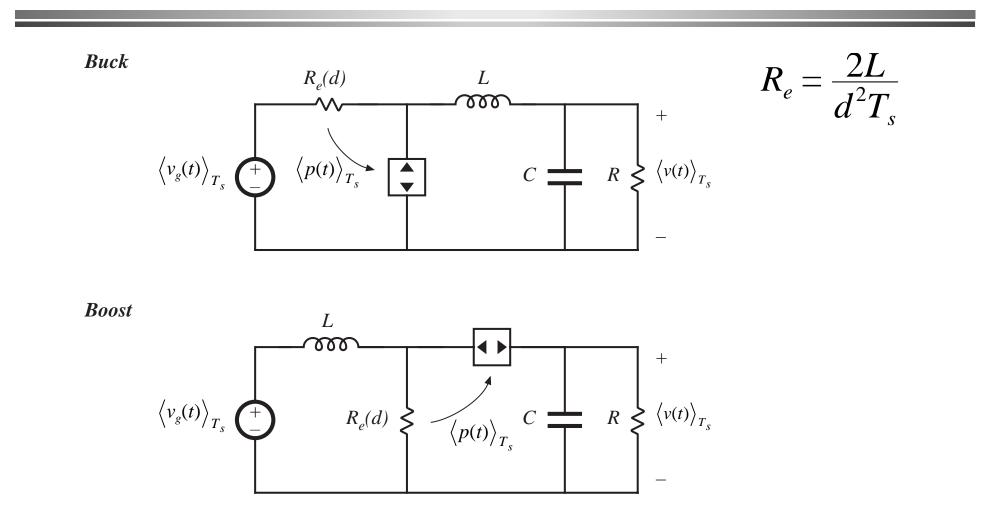


Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

DCM Cuk, SEPIC

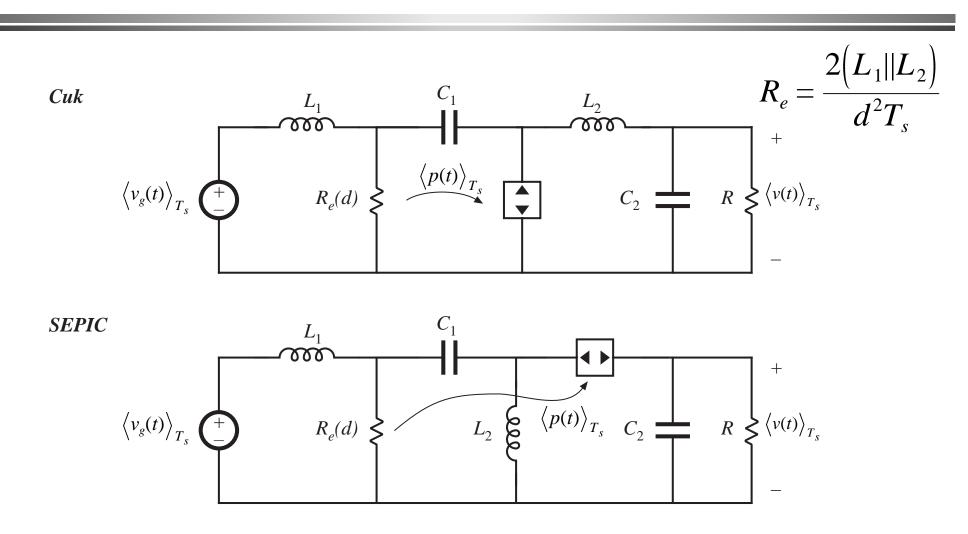

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Steady-state solution: DCM buck, boost

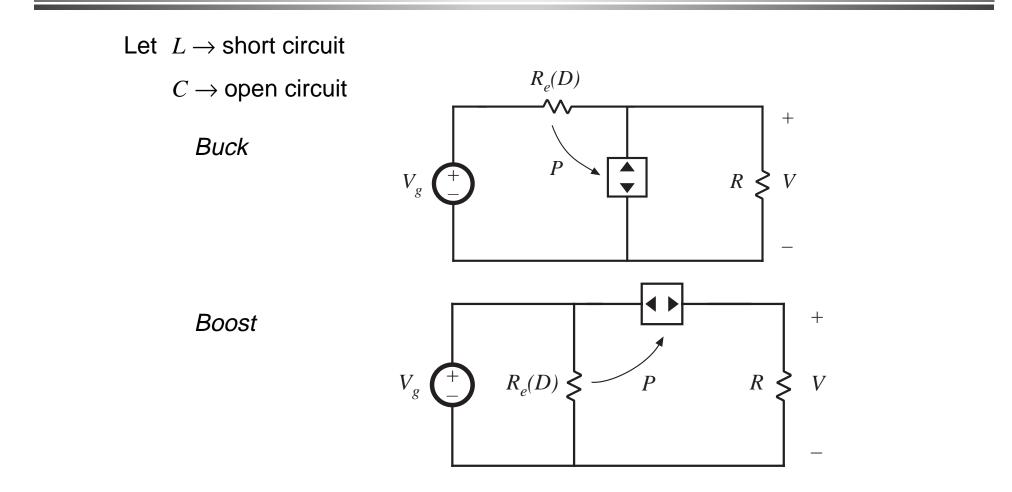

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode


Steady-state solution of DCM/LFR models

Converter	M, CCM	M, DCM
Buck	D	$\frac{2}{1 + \sqrt{1 + 4R_e/R}}$
Boost	$\frac{1}{1-D}$	$\frac{1+\sqrt{1+4R/R_e}}{2}$
Buck-boost, Cuk	$\frac{-D}{1-D}$	$-\sqrt{\frac{R}{R_e}}$
SEPIC	$\frac{D}{1-D}$	$\sqrt{rac{R}{R_e}}$
$I > I_{crit}$ for CCM $I < I_{crit}$ for DCM	$I_{crit} = \frac{1 - L}{D}$	$\frac{D}{R_e(D)}$

Table 10.1. CCM and DCM conversion ratios of basic converters

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

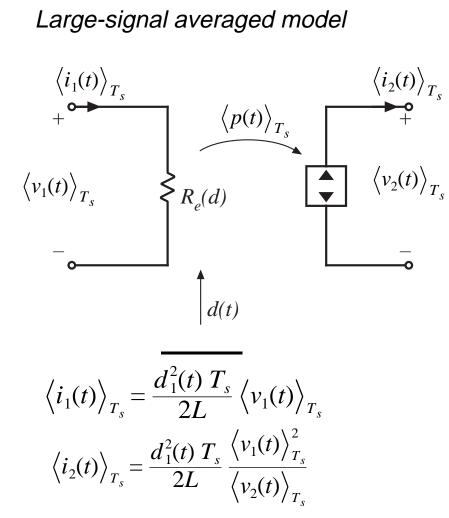10.2 Small-signal ac modeling of the DCM switch network



Fundamentals of Power Electronics

Perturb and linearize: let

$$d(t) = D + \hat{d}(t)$$

$$\left\langle v_{1}(t) \right\rangle_{T_{s}} = V_{1} + \hat{v}_{1}(t)$$

$$\left\langle i_{1}(t) \right\rangle_{T_{s}} = I_{1} + \hat{i}_{1}(t)$$

$$\left\langle v_{2}(t) \right\rangle_{T_{s}} = V_{2} + \hat{v}_{2}(t)$$

$$\left\langle i_{2}(t) \right\rangle_{T_{s}} = I_{2} + \hat{i}_{2}(t)$$

$$\hat{i}_{1} = \frac{\hat{v}_{1}}{r_{1}} + j_{1}\hat{d} + g_{1}\hat{v}_{2}$$

$$\hat{i}_{2} = -\frac{\hat{v}_{2}}{r_{2}} + j_{2}\hat{d} + g_{2}\hat{v}_{1}$$

Linearization via Taylor series

Given the nonlinear equation

$$\left\langle i_1(t) \right\rangle_{T_s} = \frac{\left\langle v_1(t) \right\rangle_{T_s}}{R_e(d(t))} = f_1\left(\left\langle v_1(t) \right\rangle_{T_s}, \left\langle v_2(t) \right\rangle_{T_s}, d(t)\right)$$

Expand in three-dimensional Taylor series about the quiescent operating point:

$$I_1 + \hat{i}_1(t) = f_1(V_1, V_2, D) + \hat{v}_1(t) \left. \frac{df_1(v_1, V_2, D)}{dv_1} \right|_{v_1 = V_1}$$


(for simple notation, drop angle brackets)

$$+ \hat{v}_{2}(t) \left. \frac{df_{1}(V_{1}, v_{2}, D)}{dv_{2}} \right|_{v_{2}} = V_{2}} + \hat{d}(t) \left. \frac{df_{1}(V_{1}, V_{2}, d)}{dd} \right|_{d} = D$$



Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Equate dc and first-order ac terms

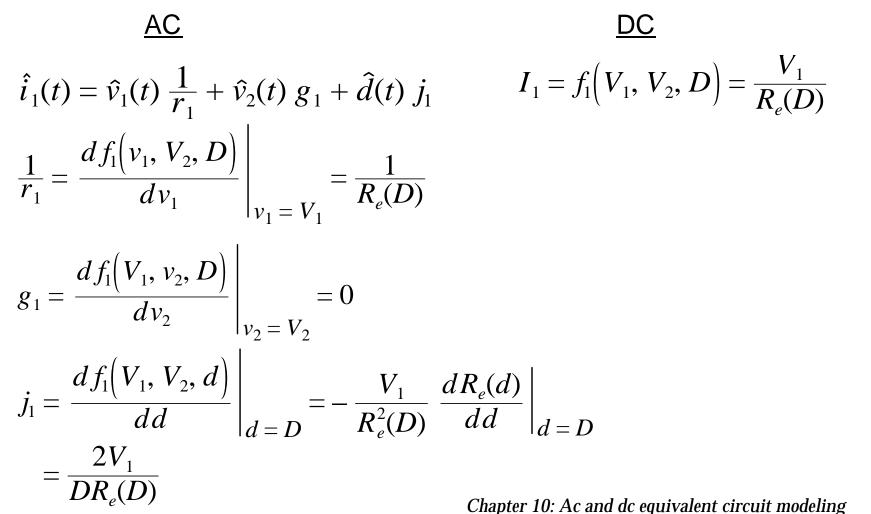

Fundamentals of Power Electronics

Output port same approach

$$\left\langle i_{2}(t)\right\rangle_{T_{s}} = \frac{\left\langle v_{1}(t)\right\rangle_{T_{s}}^{2}}{R_{e}(d(t))\left\langle v_{2}(t)\right\rangle_{T_{s}}} = f_{2}\left(\left\langle v_{1}(t)\right\rangle_{T_{s}},\left\langle v_{2}(t)\right\rangle_{T_{s}},d(t)\right)$$

$$I_2 = f_2(V_1, V_2, D) = \frac{V_1^2}{R_e(D) V_2}$$
 DC terms

$$\hat{i}_2(t) = \hat{v}_2(t) \left(-\frac{1}{r_2}\right) + \hat{v}_1(t)g_2 + \hat{d}(t)j_2 \qquad \text{Small-signal ac}$$
linearization

Fundamentals of Power Electronics

Output resistance parameter r_2

$$\frac{1}{r_2} = -\frac{df_2(V_1, v_2, D)}{dv_2} \bigg|_{v_2 = V_2} = \frac{1}{R} = \frac{1}{M^2 R_e(D)}$$

$$\langle i_2(t) \rangle_{T_s} \left(\begin{array}{c} Power \ source \\ characteristic \\ operating \\ point \\ \hline R \\ \hline \\ Interview \\ \hline \\ V_2(t) \rangle_{T_s} \end{array} \right)$$

Fundamentals of Power Electronics

Small-signal DCM switch model parameters

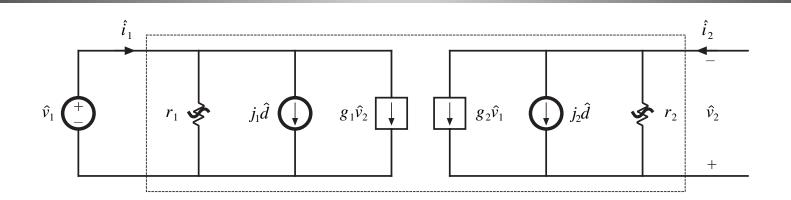



Table 10.2. Small-signal DCM switch model parameters

Switch type	g_1	j_1	r_1	g_2	j_2	r_2
Buck, Fig. 10.16(a)	$\frac{1}{R_e}$	$\frac{2(1-M)V_1}{DR_e}$	R_e	$\frac{2-M}{MR_e}$	$\frac{2(1-M)V_1}{DMR_e}$	$M^2 R_e$
Boost, Fig. 10.16(b)	$\frac{1}{\left(M-1\right)^2 R_e}$	$\frac{2MV_1}{D(M-1)R_e}$	$\frac{(M-1)^2}{M} R_e$	$\frac{2M-1}{\left(M-1\right)^2 R_e}$	$\frac{2V_1}{D(M-1)R_e}$	$(M-1)^2 R_e$
Buck-boost, Fig. 10.7(b)	0	$rac{2V_1}{DR_e}$	R_{e}	$\frac{2M}{R_e}$	$\frac{2V_1}{DMR_e}$	$M^2 R_e$


30

Fundamentals of Power Electronics

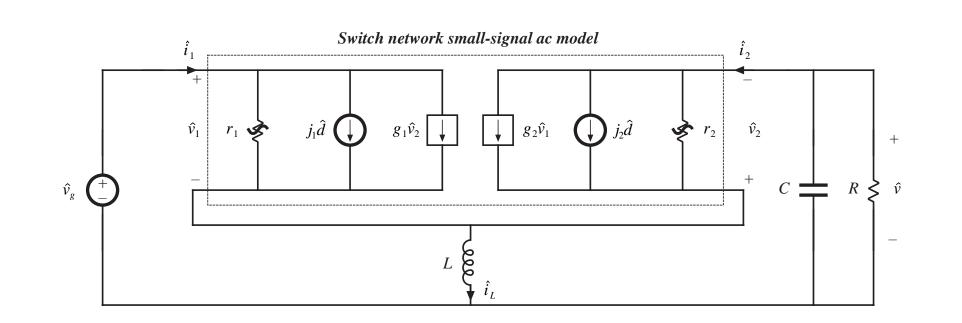Small-signal ac model, DCM buck-boost example




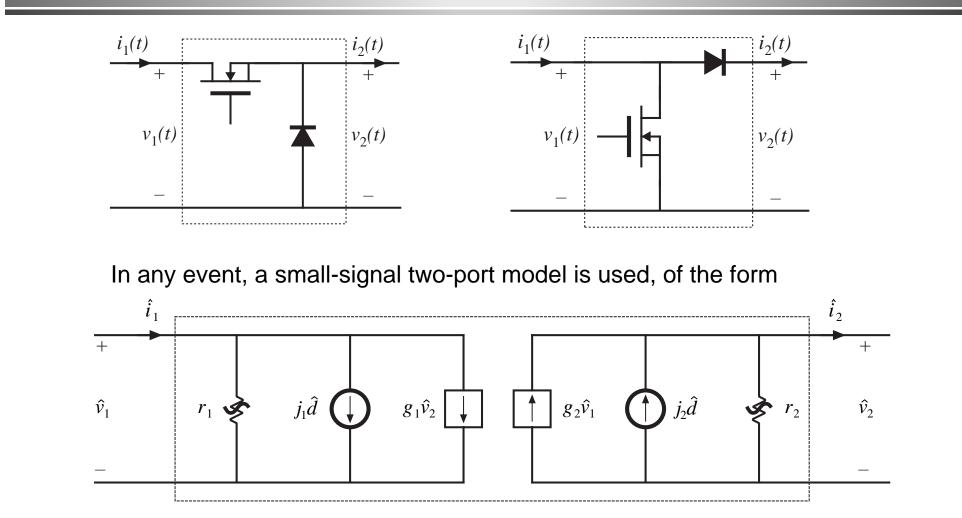A more convenient way to model the buck and boost small-signal DCM switch networks



Fundamentals of Power Electronics

Small-signal ac models of the DCM buck and boost converters (more convenient forms)

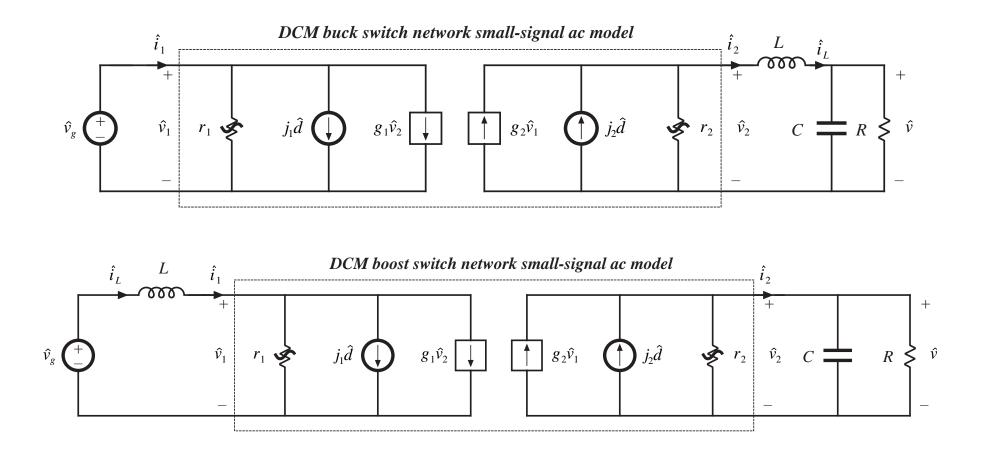


Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

- When expressed in terms of *R*, *L*, *C*, and *M* (not *D*), the small-signal transfer functions are the same in DCM as in CCM
- Hence, DCM boost and buck-boost converters exhibit two poles and one RHP zero in control-to-output transfer functions
- *But*, value of *L* is small in DCM. Hence
 - RHP zero appears at high frequency, usually greater than switching frequency
 - Pole due to inductor dynamics appears at high frequency, near to or greater than switching frequency
 - So DCM buck, boost, and buck-boost converters exhibit essentially a single-pole response
- A simple approximation: let $L \rightarrow 0$

The simple approximation $L \rightarrow 0$

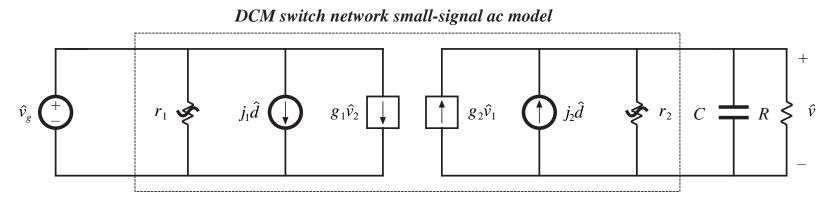Buck, boost, and buck-boost converter models all reduce to



Transfer functions

$$\begin{array}{ll} \textit{control-to-output} & G_{vd}(s) = \frac{\hat{v}}{\hat{d}} \bigg|_{\hat{v}_g = 0} = \frac{G_{d0}}{1 + \frac{S}{\Theta_p}} & \textit{with} & G_{d0} = j_2 \left(R \parallel r_2 \right) \\ \omega_p = \frac{1}{\left(R \parallel r_2 \right) C} \\ \textit{line-to-output} & G_{vg}(s) = \frac{\hat{v}}{\hat{v}_g} \bigg|_{\hat{d} = 0} = \frac{G_{g0}}{1 + \frac{S}{\Theta_p}} & G_{g0} = g_2 \left(R \parallel r_2 \right) = M \end{array}$$

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Transfer function salient features

Converter	G_{d0}	G_{g0}	ω_p
Buck	$\frac{2V}{D} \frac{1-M}{2-M}$	М	$\frac{2-M}{(1-M)RC}$
Boost	$\frac{2V}{D} \frac{M-1}{2M-1}$	M	$\frac{2M-1}{(M-1)RC}$
Buck-boost	$rac{V}{D}$	M	$\frac{2}{RC}$

 Table 10.3.
 Salient features of DCM converter small-signal transfer functions

DCM boost example

 $R = 12 \Omega$ $L = 5 \mu H$ $C = 470 \mu F$ $f_s = 100 \text{ kHz}$

The output voltage is regulated to be V = 36 V. It is desired to determine $G_{vd}(s)$ at the

operating point where the load current is I = 3 A and the dc input voltage is $V_g = 24$ V.

Fundamentals of Power Electronics


Evaluate simple model parameters

$$\begin{split} P &= I \Big(V - V_g \Big) = \Big(3 \text{ A} \Big) \Big(36 \text{ V} - 24 \text{ V} \Big) = 36 \text{ W} \\ R_e &= \frac{V_g^2}{P} = \frac{(24 \text{ V})^2}{36 \text{ W}} = 16 \Omega \\ D &= \sqrt{\frac{2L}{R_e T_s}} = \sqrt{\frac{2(5 \text{ \mu H})}{(16 \Omega)(10 \text{ \mu s})}} = 0.25 \\ G_{d0} &= \frac{2V}{D} \frac{M - 1}{2M - 1} = \frac{2(36 \text{ V})}{(0.25)} \frac{\left(\frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)}{\left(2 \frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)} = 72 \text{ V} \Rightarrow 37 \text{ dBV} \\ f_p &= \frac{\omega_p}{2\pi} = \frac{2M - 1}{2\pi (M - 1)RC} = \frac{\left(2 \frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)}{2\pi \left(\frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)} = 112 \text{ Hz} \\ Expression (12 \text{ G})(470 \text{ \mu F}) \\ Expression (12 \text{ G})$$

Fundamentals of Power Electronics

of the discontinuous conduction mode

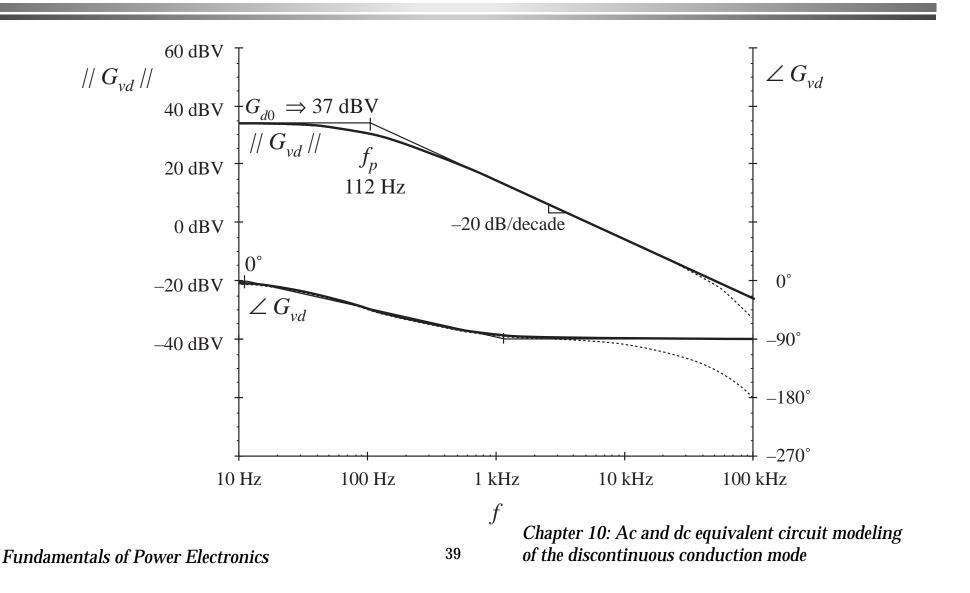Control-to-output transfer function, boost example



10.3 Generalized Switch Averaging

An approach that directly relates the transfer functions of converters

operating in DCM, and/or

with current programmed control, and/or


with resonant switches, and/or

with other control schemes or switch implementations,


to the transfer functions of the parent CCM converter, derived in Chapter 7.

The models for these other modes, control schemes, and switch implementations are shown to be equivalent to the CCM models of Chapter 7, plus additional effective feedback loops that describe the switch behavior

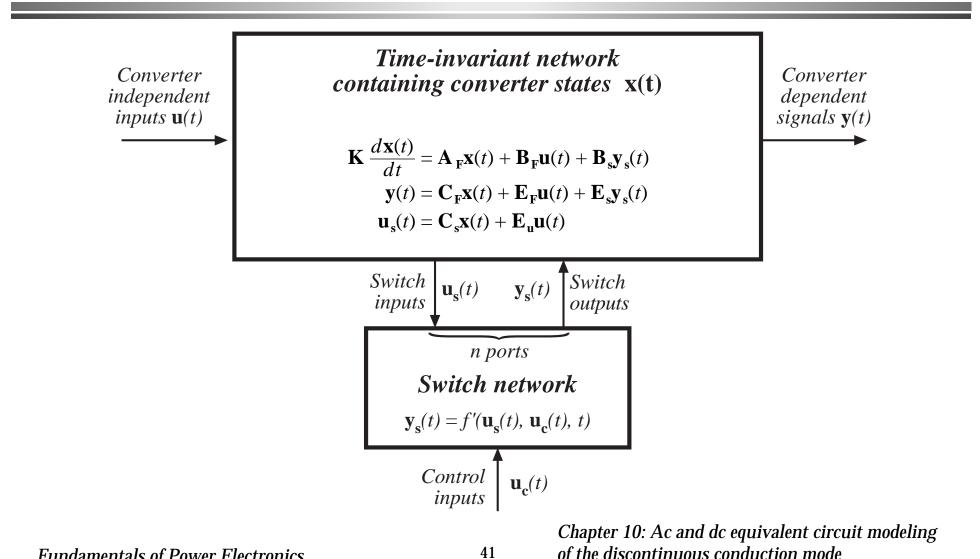Converter and switch network state equations



Averaged system equations

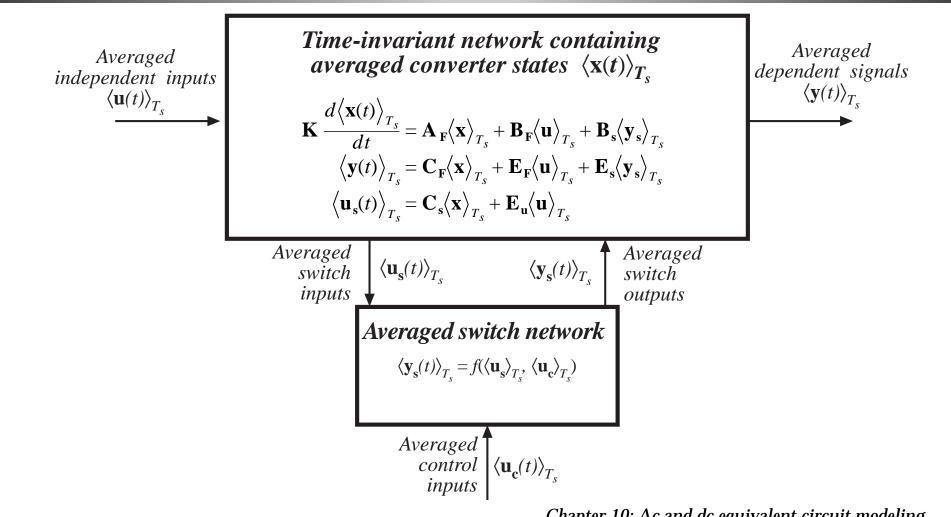

Fundamentals of Power Electronics

Averaging the switch network dependent quantities

Place switch network dependent outputs in vector $y_s(t)$, then average over one switching period, to obtain an equation of the form

$$\left\langle \mathbf{y}_{\mathbf{s}}(t) \right\rangle_{T_{s}} = \boldsymbol{f}\left(\left\langle \mathbf{u}_{\mathbf{s}}(t) \right\rangle_{T_{s}}, \left\langle \mathbf{u}_{\mathbf{c}}(t) \right\rangle_{T_{s}}\right)$$

Now attempt to write the converter state equations in the same form used for CCM state-space averaging in Chapter 7. This can be done provided that the above equation can be manipulated into the form

$$\langle \mathbf{y}_{\mathbf{s}}(t) \rangle_{T_s} = \mu(t) \mathbf{y}_{\mathbf{s}\mathbf{1}}(t) + \mu'(t) \mathbf{y}_{\mathbf{s}\mathbf{2}}(t)$$

where $y_{s1}(t)$ is the value of $y_s(t)$ in the CCM converter during subinterval 1 $y_{s2}(t)$ is the value of $y_s(t)$ in the CCM converter during subinterval 2 μ is called the switch conversion ratio $\mu' = 1 - \mu$

Fundamentals of Power Electronics

Switch conversion ratio μ

If it is true that

$$\left\langle \mathbf{y}_{s}(t) \right\rangle_{T_{s}} = \mu(t) \mathbf{y}_{s1}(t) + \mu'(t) \mathbf{y}_{s2}(t)$$

then CCM equations can be used directly, simply by replacing the duty cycle d(t) with the switch conversion ratio $\mu(t)$:


Steady-state relations are found by replacing D with μ_0

Small-signal transfer functions are found by replacing $\hat{d}(t)$ with $\hat{\mu}(t)$

The switch conversion ratio μ is a generalization of the CCM duty cycle *d*. In general, μ may depend on the switch independent inputs, that is, converter voltages and currents. So feedback may be built into the switch network.

A proof follows later.

10.3.1 Buck converter example

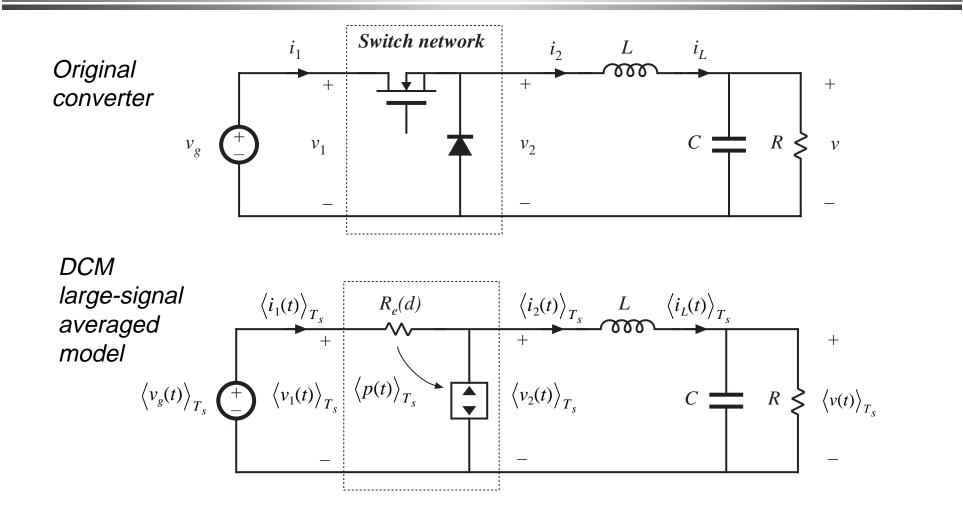

Fundamentals of Power Electronics

Defining the switch network inputs and outputs


Switch input vector $\mathbf{u}_{\mathbf{s}}(t) = \begin{bmatrix} v_1(t) \\ i_2(t) \end{bmatrix}$

Switch control input


 $\mathbf{u}_{\mathbf{c}}(t) = \left[d(t)\right]$

Switch output vector
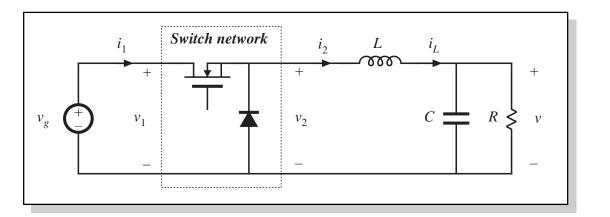
$$\mathbf{y}_{\mathbf{s}}(t) = \begin{bmatrix} v_2(t) \\ i_1(t) \end{bmatrix}$$



Switch output waveforms, CCM operation

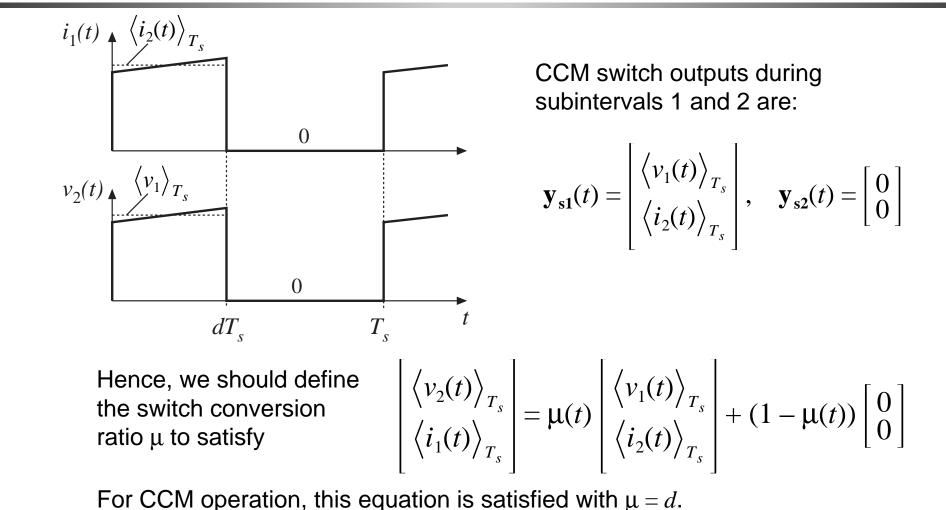


Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Solve for μ , in general

$$\left\langle \mathbf{y}_{s}(t) \right\rangle_{T_{s}} = \boldsymbol{\mu}(t) \ \mathbf{y}_{s1}(t) + \boldsymbol{\mu}'(t) \ \mathbf{y}_{s2}(t) \qquad \Rightarrow \\ \left| \left\langle v_{2}(t) \right\rangle_{T_{s}} \right| = \boldsymbol{\mu}(t) \left| \left\langle v_{1}(t) \right\rangle_{T_{s}} \right| + (1 - \boldsymbol{\mu}(t)) \left[\begin{array}{c} 0 \\ 0 \end{array} \right] \qquad \Rightarrow \\ \boldsymbol{\mu}(t) = \frac{\left\langle v_{2}(t) \right\rangle_{T_{s}}}{\left\langle v_{1}(t) \right\rangle_{T_{s}}} = \frac{\left\langle i_{1}(t) \right\rangle_{T_{s}}}{\left\langle i_{2}(t) \right\rangle_{T_{s}}}$$

This is a general definition of μ , for the switch network as defined previously for the buck converter. It is valid not only in CCM, but also in DCM and ...

Evaluation of μ

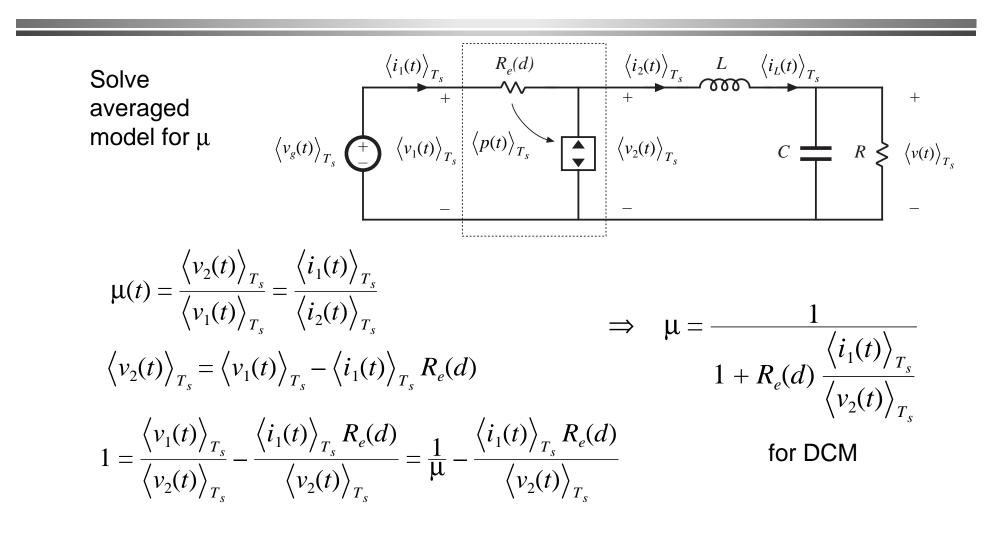

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Elimination of dependent quantities

we found that $\mu = \frac{1}{1 + R_e(d) \frac{\left\langle i_1(t) \right\rangle_{T_s}}{\left\langle v_2(t) \right\rangle_{T_s}}}$

Lossless switch network:

$$\left\langle i_{1}(t)\right\rangle_{T_{s}}\left\langle v_{1}(t)\right\rangle_{T_{s}} = \left\langle i_{2}(t)\right\rangle_{T_{s}}\left\langle v_{2}(t)\right\rangle_{T_{s}} \implies \frac{\left\langle i_{1}(t)\right\rangle_{T_{s}}}{\left\langle v_{2}(t)\right\rangle_{T_{s}}} = \frac{\left\langle i_{2}(t)\right\rangle_{T_{s}}}{\left\langle v_{1}(t)\right\rangle_{T_{s}}}$$

Hence

$$\mu\left(\left\langle v_{1}(t)\right\rangle_{T_{s}},\left\langle i_{2}(t)\right\rangle_{T_{s}},d\right) = \frac{1}{1+R_{e}(d)\frac{\left\langle i_{2}(t)\right\rangle_{T_{s}}}{\left\langle v_{1}(t)\right\rangle_{T_{s}}}}$$

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

1

DCM switch conversion ratio μ

$$\mu\left(\left\langle v_{1}(t)\right\rangle_{T_{s}},\left\langle i_{2}(t)\right\rangle_{T_{s}},d\right) = \frac{1}{1+R_{e}(d)}\frac{\left\langle i_{2}(t)\right\rangle_{T_{s}}}{\left\langle v_{1}(t)\right\rangle_{T_{s}}}$$

- A general result for DCM
- Replace d of CCM expression with μ to obtain a valid DCM expression
- In DCM, switch conversion ratio is a function of not only the transistor duty cycle *d*, but also the switch independent terminal waveforms *i*₂ and *v*₁. The switch network contains built-in feedback.

Perturbation and linearization

$$\mu(t) = \mu_0 + \hat{\mu}(t)$$
$$\left\langle \mathbf{u}_{\mathbf{s}}(t) \right\rangle_{T_s} = \mathbf{U}_{\mathbf{s}} + \hat{\mathbf{u}}_{\mathbf{s}}(t)$$
$$\mathbf{u}_{\mathbf{c}}(t) = \mathbf{U}_{\mathbf{c}} + \hat{\mathbf{u}}_{\mathbf{c}}(t)$$

Steady-state components:

$$\boldsymbol{\mu}_0 = \boldsymbol{\mu}(\mathbf{U}_{\mathbf{s}}, \mathbf{U}_{\mathbf{c}}, D)$$

Buck example:

$$\mu_0 = \frac{1}{1 + R_e(D) \frac{I_2}{V_1}}$$

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Buck example: steady-state solution

In CCM, we know that

$$\frac{V}{V_g} = M(D) = D$$
$$I_L = \frac{V}{R}$$

DCM: replace *D* with μ_0 :

T T

$$\frac{V}{V_g} = M(\mu_0) = \mu_0$$

$$I_2 = \frac{V}{R}$$
with
$$\mu_0 = \frac{1}{1 + R_e(D) \frac{I_2}{V_1}}$$

Can now solve for V to obtain the usual DCM expression for V/V_g .

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

DCM buck example: small-signal equations

Express linearized conversion ratio as a function of switch control input and independent terminal inputs:


$$\hat{\mu}(t) = \frac{\hat{v}_1(t)}{V_s} - \frac{\hat{i}_2(t)}{I_s} + k_s \,\hat{d}(t)$$

The gains are found by evaluation of derivatives at the quiescent operating point

$$\frac{1}{V_s} = \frac{d\mu(v_1, I_2, D)}{dv_1} \bigg|_{v_1 = V_1} = \frac{\mu_0^2 I_2 R_e(D)}{V_1^2}$$
$$\frac{1}{I_s} = -\frac{d\mu(V_1, i_2, D)}{di_2} \bigg|_{i_2 = I_2} = \frac{\mu_0^2 R_e(D)}{V_1}$$
$$k_s = \frac{d\mu(V_1, I_2, d)}{dd} \bigg|_{d = D} = \frac{2\mu_0^2 I_2 R_e(D)}{DV_1}$$


Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Result: small-signal model of DCM buck

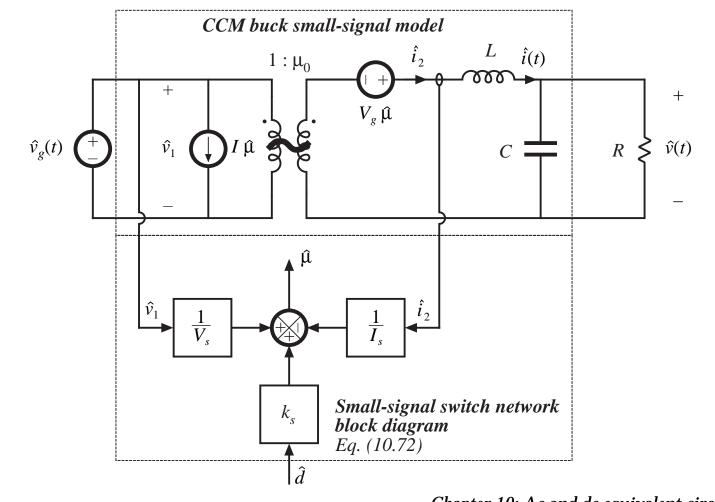


Fundamentals of Power Electronics

Control-to-output transfer function

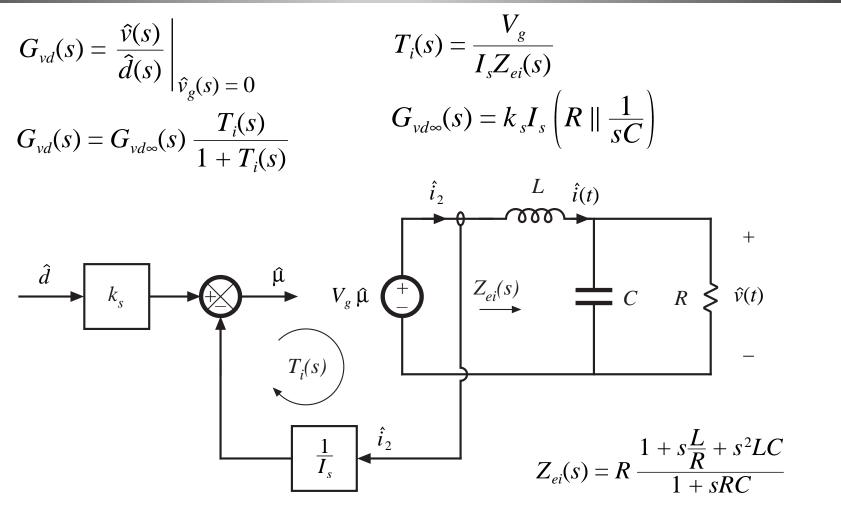


Magnitude of the loop gain $T_i(s)$

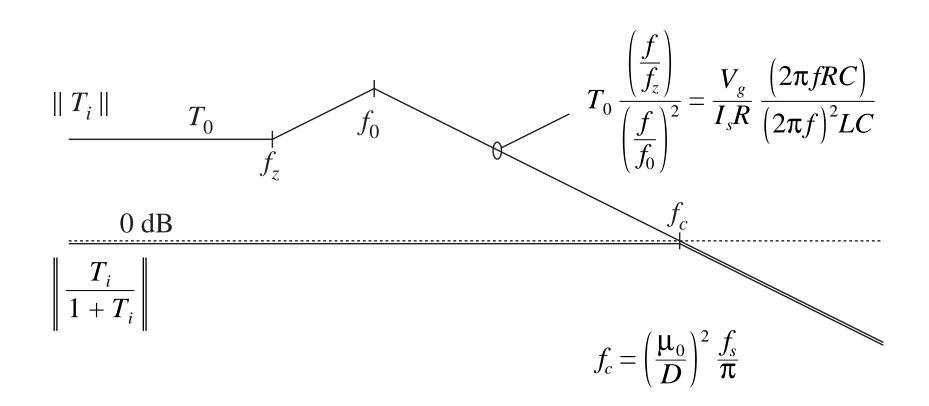

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

10.3.2 Proof of Generalized Averaged Switch Modeling

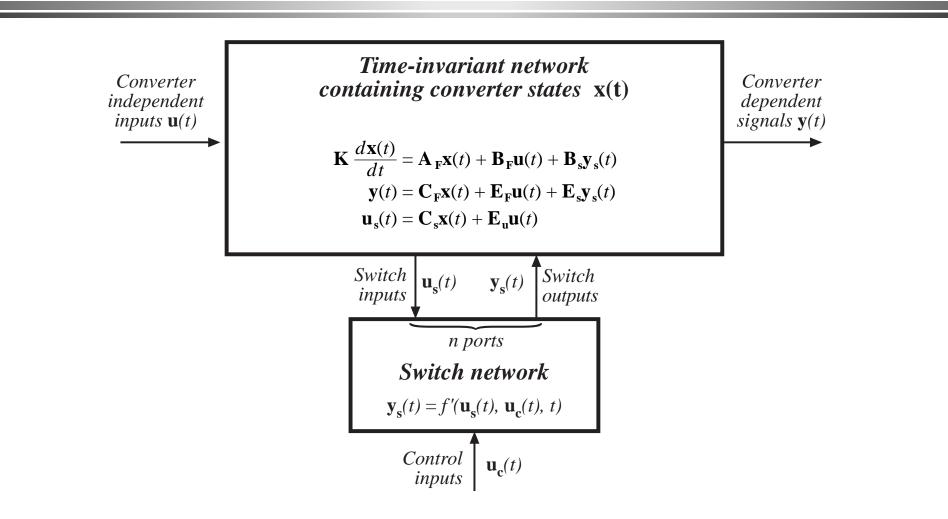

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

System state equations

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_{\mathbf{F}}\mathbf{x}(t) + \mathbf{B}_{\mathbf{F}}\mathbf{u}(t) + \mathbf{B}_{\mathbf{s}}\mathbf{y}_{\mathbf{s}}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_{\mathbf{F}}\mathbf{x}(t) + \mathbf{E}_{\mathbf{F}}\mathbf{u}(t) + \mathbf{E}_{\mathbf{s}}\mathbf{y}_{\mathbf{s}}(t)$$
$$\mathbf{u}_{\mathbf{s}}(t) = \mathbf{C}_{\mathbf{s}}\mathbf{x}(t) + \mathbf{E}_{\mathbf{u}}\mathbf{u}(t)$$
$$\mathbf{y}_{\mathbf{s}}(t) = \mathbf{f'}\left(\mathbf{u}_{\mathbf{s}}(t), \mathbf{u}_{\mathbf{c}}(t), t\right)$$

Average:

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \mathbf{A}_{\mathbf{F}} \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_{\mathbf{F}} \langle \mathbf{u}(t) \rangle_{T_s} + \mathbf{B}_{\mathbf{s}} \langle \mathbf{y}_{\mathbf{s}}(t) \rangle_{T_s} \langle \mathbf{y}(t) \rangle_{T_s} = \mathbf{C}_{\mathbf{F}} \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_{\mathbf{F}} \langle \mathbf{u}(t) \rangle_{T_s} + \mathbf{E}_{\mathbf{s}} \langle \mathbf{y}_{\mathbf{s}}(t) \rangle_{T_s} \langle \mathbf{u}_{\mathbf{s}}(t) \rangle_{T_s} = \mathbf{C}_{\mathbf{s}} \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_{\mathbf{u}} \langle \mathbf{u}(t) \rangle_{T_s} \langle \mathbf{y}_{\mathbf{s}}(t) \rangle_{T_s} = \mathbf{f} \Big[\langle \mathbf{u}_{\mathbf{s}}(t) \rangle_{T_s}, \langle \mathbf{u}_{\mathbf{c}}(t) \rangle_{T_s} \Big]$$

Also suppose that we can write

$$\langle \mathbf{y}_{s}(t) \rangle_{T_{s}} = \mu(t) \mathbf{y}_{s1}(t) + \mu'(t) \mathbf{y}_{s2}(t)$$

Values of $y_s(t)$ during subintervals 1 and 2 are defined as $y_{s1}(t)$ and $y_{s2}(t)$

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

System averaged state equations

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \mathbf{A}_{\mathbf{F}} \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_{\mathbf{F}} \langle \mathbf{u}(t) \rangle_{T_s} + \mu \mathbf{B}_{\mathbf{s}} \mathbf{y}_{\mathbf{s}\mathbf{1}}(t) + \mu' \mathbf{B}_{\mathbf{s}} \mathbf{y}_{\mathbf{s}\mathbf{2}}(t)$$
$$\langle \mathbf{y}(t) \rangle_{T_s} = \mathbf{C}_{\mathbf{F}} \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_{\mathbf{F}} \langle \mathbf{u}(t) \rangle_{T_s} + \mu \mathbf{E}_{\mathbf{s}} \mathbf{y}_{\mathbf{s}\mathbf{1}}(t) + \mu' \mathbf{E}_{\mathbf{s}} \mathbf{y}_{\mathbf{s}\mathbf{2}}(t)$$

It is desired to relate this to the result of the state-space averaging method, in which the converter state equations for subinterval 1 are written as

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_{1}\mathbf{x}(t) + \mathbf{B}_{1}\mathbf{u}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_{1}\mathbf{x}(t) + \mathbf{E}_{1}\mathbf{u}(t)$$

with similar expressions for subinterval 2

But the time-invariant network equations predict that the converter state equations for the first subinterval are

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_{\mathbf{F}} \mathbf{x}(t) + \mathbf{B}_{\mathbf{F}} \mathbf{u}(t) + \mathbf{B}_{\mathbf{s}} \mathbf{y}_{\mathbf{s}\mathbf{1}}(t)$$

Now equate the two
$$\mathbf{y}(t) = \mathbf{C}_{\mathbf{F}} \mathbf{x}(t) + \mathbf{E}_{\mathbf{F}} \mathbf{u}(t) + \mathbf{E}_{\mathbf{s}} \mathbf{y}_{\mathbf{s}\mathbf{1}}(t)$$

expressions

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Fundamentals of Power Electronics

Equate the state equation expressions derived via the two methods

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_{1}\mathbf{x}(t) + \mathbf{B}_{1}\mathbf{u}(t) = \mathbf{A}_{F}\mathbf{x}(t) + \mathbf{B}_{F}\mathbf{u}(t) + \mathbf{B}_{s}\mathbf{y}_{s1}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_{1}\mathbf{x}(t) + \mathbf{E}_{1}\mathbf{u}(t) = \mathbf{C}_{F}\mathbf{x}(t) + \mathbf{E}_{F}\mathbf{u}(t) + \mathbf{E}_{s}\mathbf{y}_{s1}(t)$$

Solve for $\mathbf{B}_{s}\mathbf{y}_{s1}$ and $\mathbf{E}_{s}\mathbf{y}_{s1}$:

$$\mathbf{B}_{s}\mathbf{y}_{s1}(t) = \left(\mathbf{A}_{1} - \mathbf{A}_{F}\right)\mathbf{x}(t) + \left(\mathbf{B}_{1} - \mathbf{B}_{F}\right)\mathbf{u}(t)$$
$$\mathbf{E}_{s}\mathbf{y}_{s1}(t) = \left(\mathbf{C}_{1} - \mathbf{C}_{F}\right)\mathbf{x}(t) + \left(\mathbf{E}_{1} - \mathbf{E}_{F}\right)\mathbf{u}(t)$$

Result for subinterval 2:

$$\mathbf{B}_{s}\mathbf{y}_{s2}(t) = \left(\mathbf{A}_{2} - \mathbf{A}_{F}\right)\mathbf{x}(t) + \left(\mathbf{B}_{2} - \mathbf{B}_{F}\right)\mathbf{u}(t)$$
$$\mathbf{E}_{s}\mathbf{y}_{s2}(t) = \left(\mathbf{C}_{2} - \mathbf{C}_{F}\right)\mathbf{x}(t) + \left(\mathbf{E}_{2} - \mathbf{E}_{F}\right)\mathbf{u}(t)$$

Now plug these results back into averaged state equations

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Averaged state equations

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \mathbf{A}_{\mathbf{F}} \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_{\mathbf{F}} \langle \mathbf{u}(t) \rangle_{T_s}$$

$$+ \mu \left(\left(\mathbf{A}_1 - \mathbf{A}_{\mathbf{F}} \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mathbf{B}_1 - \mathbf{B}_{\mathbf{F}} \right) \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

$$+ \mu' \left(\left(\mathbf{A}_2 - \mathbf{A}_{\mathbf{F}} \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mathbf{B}_2 - \mathbf{B}_{\mathbf{F}} \right) \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

$$\langle \mathbf{y}(t) \rangle_{T_s} = \mathbf{C}_{\mathbf{F}} \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_{\mathbf{F}} \langle \mathbf{u}(t) \rangle_{T_s}$$

$$+ \mu \left(\left(\mathbf{C}_1 - \mathbf{C}_{\mathbf{F}} \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mathbf{E}_1 - \mathbf{E}_{\mathbf{F}} \right) \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

$$+ \mu' \left(\left(\mathbf{C}_2 - \mathbf{C}_{\mathbf{F}} \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mathbf{E}_2 - \mathbf{E}_{\mathbf{F}} \right) \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Collect terms

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(\mu \mathbf{A}_1 + \mu' \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mu \mathbf{B}_1 + \mu' \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s} \\ \left\langle \mathbf{y}(t) \right\rangle_{T_s} = \left(\mu \mathbf{C}_1 + \mu' \mathbf{C}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mu \mathbf{E}_1 + \mu' \mathbf{E}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

- This is the desired result. It is identical to the large-signal result of the state-space averaging method, except that the duty cycle d has been replaced with the conversion ratio µ.
- Hence, we can use any result derived via state-space averaging, by simply replacing d with μ.

Perturb and linearize

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(\mu \mathbf{A}_1 + \mu' \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mu \mathbf{B}_1 + \mu' \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s} \\ \left\langle \mathbf{y}(t) \right\rangle_{T_s} = \left(\mu \mathbf{C}_1 + \mu' \mathbf{C}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(\mu \mathbf{E}_1 + \mu' \mathbf{E}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

Let

.

$$\left\langle \mathbf{x}(t) \right\rangle_{T_s} = \mathbf{X} + \hat{\mathbf{x}}(t) \left\langle \mathbf{u}(t) \right\rangle_{T_s} = \mathbf{U} + \hat{\mathbf{u}}(t) \left\langle \mathbf{y}(t) \right\rangle_{T_s} = \mathbf{Y} + \hat{\mathbf{y}}(t) \mu(t) = \mu_0 + \hat{\mu}(t) \left\langle \mathbf{u}_{\mathbf{s}}(t) \right\rangle_{T_s} = \mathbf{U}_{\mathbf{s}} + \hat{\mathbf{u}}_{\mathbf{s}}(t) \left\langle \mathbf{u}_{\mathbf{c}}(t) \right\rangle_{T_s} = \mathbf{U}_{\mathbf{c}} + \hat{\mathbf{u}}_{\mathbf{c}}(t)$$

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Result


DC model $0 = \mathbf{AX} + \mathbf{BU}$ $\mathbf{Y} = \mathbf{CX} + \mathbf{EU}$	\mathbf{where} $\mathbf{A} = \left(\mu_0 \mathbf{A}_1 + \mu_0' \mathbf{A}_2\right)$ $\mathbf{B} = \left(\mu_0 \mathbf{B}_1 + \mu_0' \mathbf{B}_2\right)$	$\mathbf{k}_{s}^{T} = \frac{\mathrm{d}\mu \left(\left\langle \mathbf{u}_{s}(t) \right\rangle_{T_{s}}, \left\langle \mathbf{u}_{c}(t) \right\rangle_{T_{s}} \right)}{\mathrm{d} \left\langle \mathbf{u}_{s}(t) \right\rangle_{T_{s}}}$	$\left \begin{array}{c} \left\langle \mathbf{u}_{s}(t) \right\rangle_{T_{s}} = \mathbf{U}_{s} \\ \left\langle \mathbf{u}_{c}(t) \right\rangle_{T_{s}} = \mathbf{U}_{c} \end{array} \right $	
Small-signal	$\mathbf{D} = (\boldsymbol{\mu}_0 \mathbf{D}_1 + \boldsymbol{\mu}_0 \mathbf{D}_2)$ $\mathbf{C} = (\boldsymbol{\mu}_0 \mathbf{C}_1 + \boldsymbol{\mu}_0' \mathbf{C}_2)$ $\mathbf{E} = (\boldsymbol{\mu}_0 \mathbf{E}_1 + \boldsymbol{\mu}_0' \mathbf{E}_2)$	$\mathbf{k}_{\mathbf{c}}^{T} = \frac{\mathrm{d}\mu \left(\left\langle \mathbf{u}_{s}(t) \right\rangle_{T_{s}}, \left\langle \mathbf{u}_{c}(t) \right\rangle_{T_{s}} \right)}{\mathrm{d} \left\langle \mathbf{u}_{c}(t) \right\rangle_{T_{s}}}$		
ac model $\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{d\hat{\mathbf{x}}(t)} = \mathbf{A}\hat{\mathbf{x}}(t) + \mathbf{B}\hat{\mathbf{x}}(t) + \int_{0}^{\infty} (\mathbf{x}) d\mathbf{x}(t) d\mathbf{x}(t)$			$\begin{vmatrix} \langle \mathbf{u}_{s}(t) \rangle_{T_{s}} = \mathbf{U}_{s} \\ \langle \mathbf{u}_{c}(t) \rangle_{T_{s}} = \mathbf{U}_{c} \end{vmatrix}$	
$\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A}\hat{\mathbf{x}}(t) + \mathbf{B}\hat{\mathbf{u}}(t) + \left(\left(\mathbf{A}_{1} - \mathbf{A}_{2}\right)\mathbf{X} + \left(\mathbf{B}_{1} - \mathbf{B}_{2}\right)\mathbf{U}\right)\hat{\boldsymbol{\mu}}(t)$ $\hat{\mathbf{y}}(t) = \mathbf{C}\hat{\mathbf{x}}(t) + \mathbf{E}\hat{\mathbf{u}}(t) + \left(\left(\mathbf{C}_{1} - \mathbf{C}_{2}\right)\mathbf{X} + \left(\mathbf{E}_{1} - \mathbf{E}_{2}\right)\mathbf{U}\right)\hat{\boldsymbol{\mu}}(t)$				
with the linearized switch gains	$\hat{\boldsymbol{\mu}}(t) = \mathbf{k}_{\mathbf{s}}^{T} \hat{\mathbf{u}}_{\mathbf{s}}(t) + \mathbf{k}_{\mathbf{c}}^{T} \hat{\mathbf{u}}_{\mathbf{c}}(t)$)		

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

Fundamentals of Power Electronics

65

A generalized canonical model

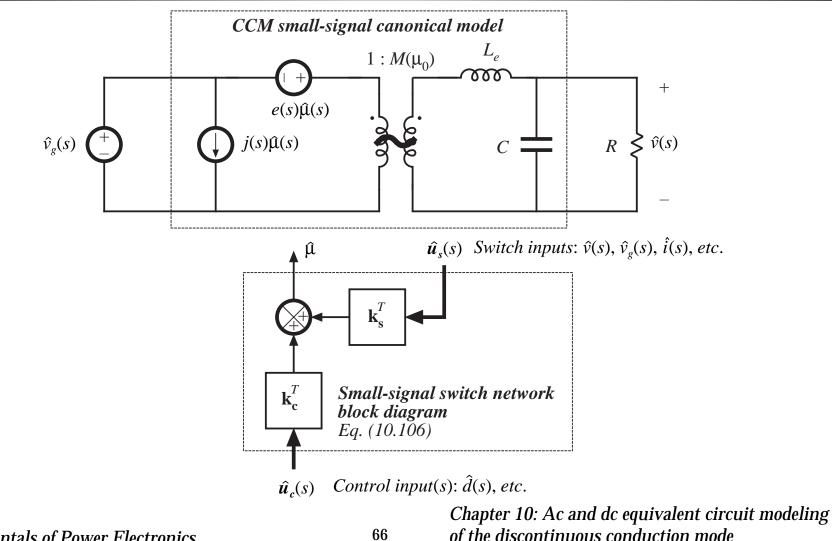

- 1. In the discontinuous conduction mode, the average transistor voltage and current are proportional, and hence obey Ohm's law. An averaged equivalent circuit can be obtained by replacing the transistor with an effective resistor $R_e(d)$. The average diode voltage and current obey a power source characteristic, with power equal to the power effectively dissipated by R_e . In the averaged equivalent circuit, the diode is replaced with a dependent power source.
- 2. The two-port lossless network consisting of an effective resistor and power source, which results from averaging the transistor and diode waveforms of DCM converters, is called a loss-free resistor. This network models the basic power-processing functions of DCM converters, much in the same way that the ideal dc transformer models the basic functions of CCM converters.
- 3. The large-signal averaged model can be solved under equilibrium conditions to determine the quiescent values of the converter currents and voltages. Average power arguments can often be used.

Key points

- 4. A small-signal ac model for the DCM switch network can be derived by perturbing and linearizing the loss-free resistor network. The result has the form of a two-port *y*-parameter model. The model describes the small-signal variations in the transistor and diode currents, as functions of variations in the duty cycle and in the transistor and diode ac voltage variations. This model is most convenient for ac analysis of the buck-boost converter.
- To simplify the ac analysis of the DCM buck and boost converters, it is convenient to define two other forms of the small-signal switch model, corresponding to the switch networks of Figs. 10.16(a) and 10.16(b). These models are also *y*-parameter twoport models, but have different parameter values.


Key points

- 6. Since the inductor value is small when the converter operates in the discontinuous conduction mode, the inductor dynamics of the DCM buck, boost, and buck-boost converters occur at high frequency, above or just below the switching frequency. Hence, in most cases the inductor dynamics can be ignored. In the small-signal ac model, the inductance *L* is set to zero, and the remaining model is solved relatively easily for the low-frequency converter dynamics. The DCM buck, boost, and buck-boost converters exhibit transfer functions containing a single low-frequency dominant pole.
- 7. It is also possible to adapt the CCM models developed in Chapter 7 to treat converters with switches that operate in DCM, as well as other switches discussed in later chapters. The switch conversion ratio μ is a generalization of the duty cycle *d* of CCM switch networks; this quantity can be substituted in place of *d* in any CCM model. The result is a model that is valid for DCM operation. Hence, existing CCM models can be adapted directly.

Key points

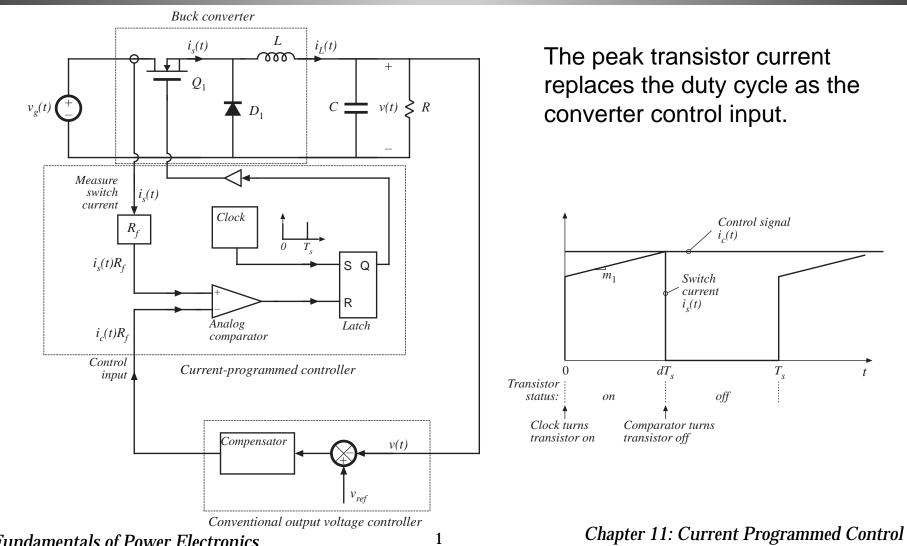8. The conversion ratio µ of DCM switch networks is a function of the applied voltage and current. As a result, the switch network contains effective feedback. So the small-signal model of a DCM converter can be expressed as the CCM converter model, plus effective feedback representing the behavior of the DCM switch network. Two effects of this feedback are increase of the converter output impedance via current feedback, and decrease of the *Q*-factor of the transfer function poles. The pole arising from the inductor dynamics occurs at the crossover frequency of the effective current feedback loop.

Chapter 11 **Current Programmed Control**



Current programmed control vs. duty cycle control

Advantages of current programmed control:

- Simpler dynamics —inductor pole is moved to high frequency
- Simple robust output voltage control, with large phase margin, can be obtained without use of compensator lead networks
- It is always necessary to sense the transistor current, to protect against overcurrent failures. We may as well use the information during normal operation, to obtain better control
- Transistor failures due to excessive current can be prevented simply by limiting $i_c(t)$
- Transformer saturation problems in bridge or push-pull converters can be mitigated

A disadvantage: susceptibility to noise

Chapter 11: Outline

- 11.1 Oscillation for D > 0.5
- 11.2 A simple first-order modelSimple model via algebraic approachAveraged switch modeling
- 11.3 A more accurate model

Current programmed controller model: block diagram

CPM buck converter example

- 11.4 Discontinuous conduction mode
- 11.5 Summary


11.1 Oscillation for D > 0.5

- The current programmed controller is inherently unstable for D > 0.5, regardless of the converter topology
- Controller can be stabilized by addition of an artificial ramp


Objectives of this section:

- Stability analysis
- Describe artificial ramp scheme

Inductor current waveform, CCM

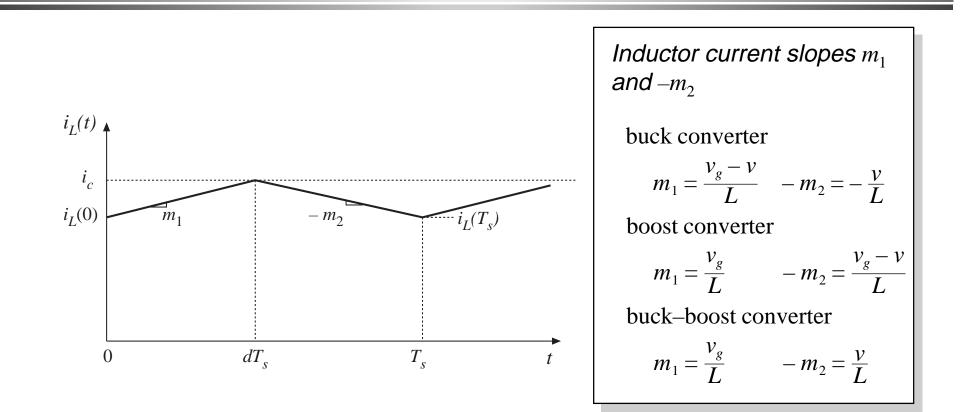

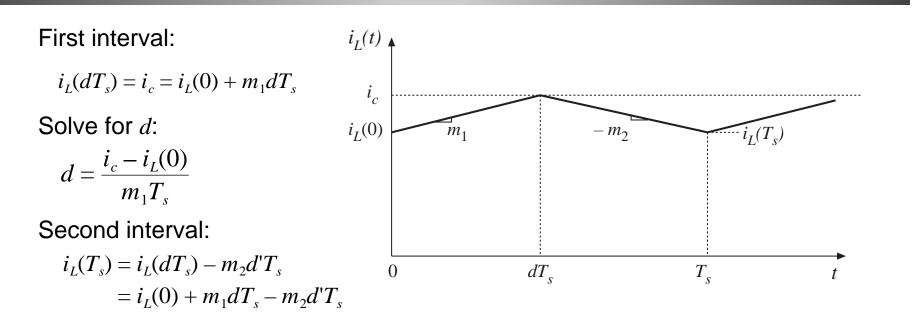
Steady-state inductor current waveform, CPM




In steady state:

$$0 = M_1 DT_s - M_2 D'T_s$$
$$\frac{M_2}{M_1} = \frac{D}{D'}$$

Perturbed inductor current waveform

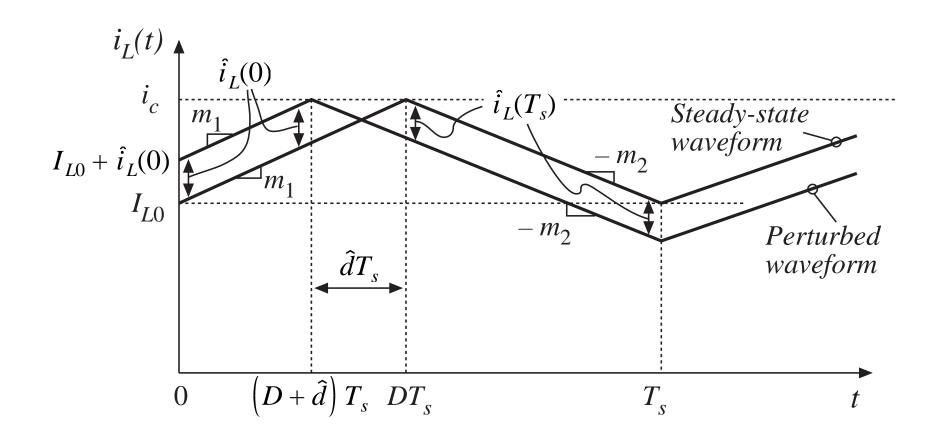

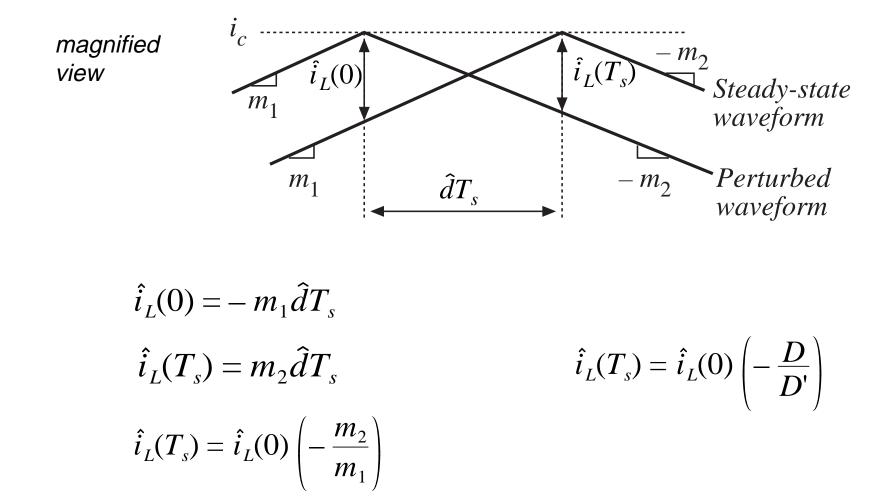Change in inductor current perturbation over one switching period



Fundamentals of Power Electronics

Change in inductor current perturbation over many switching periods

$$\hat{i}_{L}(T_{s}) = \hat{i}_{L}(0) \left(-\frac{D}{D'}\right)$$


$$\hat{i}_{L}(2T_{s}) = \hat{i}_{L}(T_{s}) \left(-\frac{D}{D'}\right) = \hat{i}_{L}(0) \left(-\frac{D}{D'}\right)^{2}$$

$$\hat{i}_{L}(nT_{s}) = \hat{i}_{L}((n-1)T_{s}) \left(-\frac{D}{D'}\right) = \hat{i}_{L}(0) \left(-\frac{D}{D'}\right)^{n}$$


$$\left|\hat{i}_{L}(nT_{s})\right| \rightarrow \begin{cases} 0 \quad \text{when } \left|-\frac{D}{D'}\right| < 1 \\ \infty \quad \text{when } \left|-\frac{D}{D'}\right| > 1 \end{cases}$$

For stability: D < 0.5


Example: unstable operation for D = 0.6

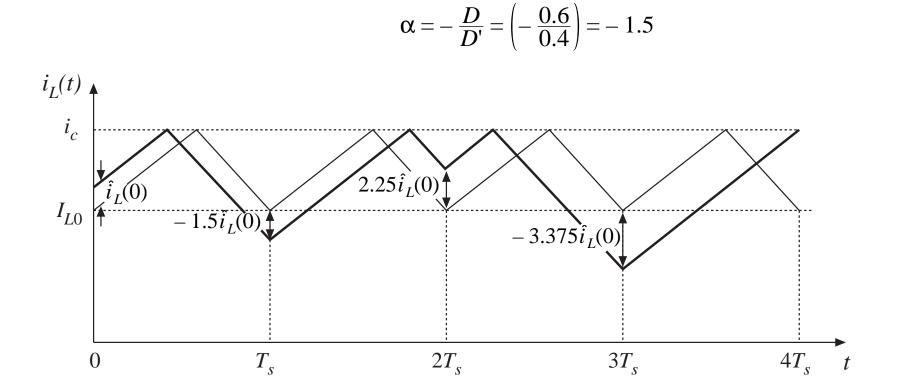

Example: stable operation for D = 1/3

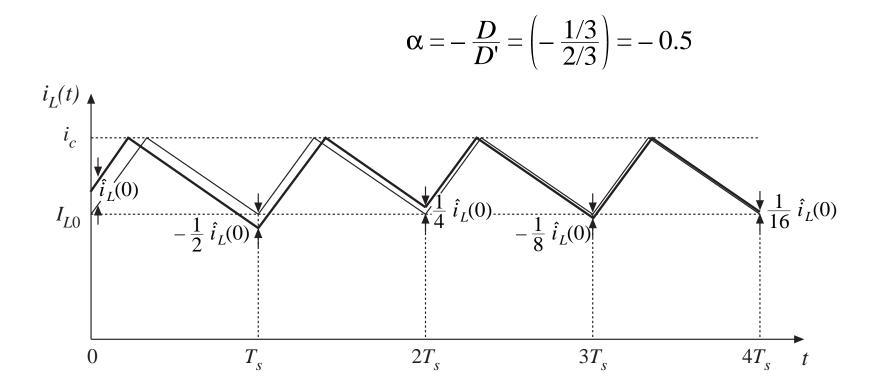

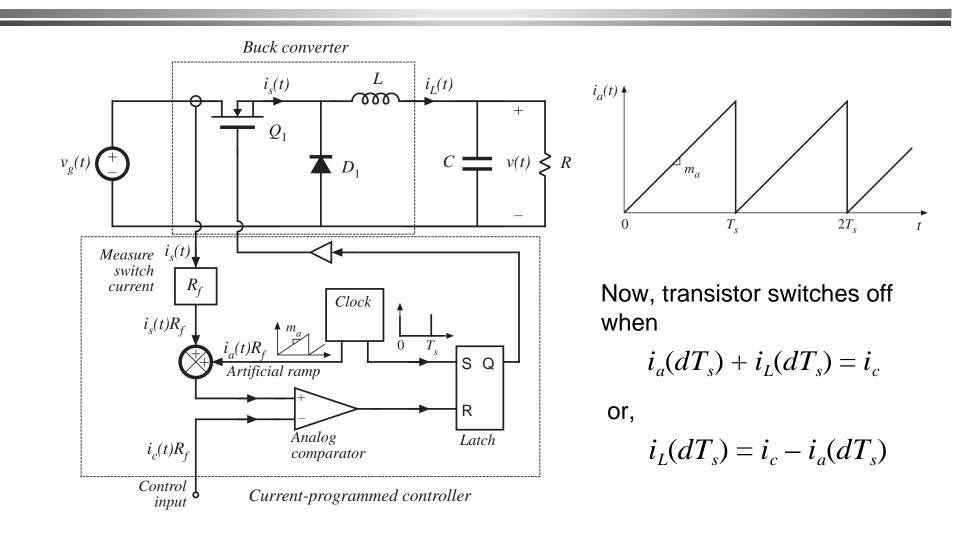
Stabilization via addition of an artificial ramp to the measured switch current waveform




Fundamentals of Power Electronics

Steady state waveforms with artificial ramp

 $i_L(dT_s) = i_c - i_a(dT_s)$

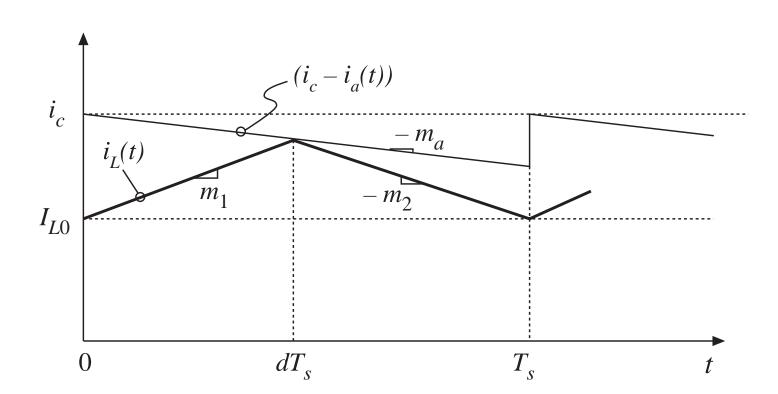

Stability analysis: perturbed waveform

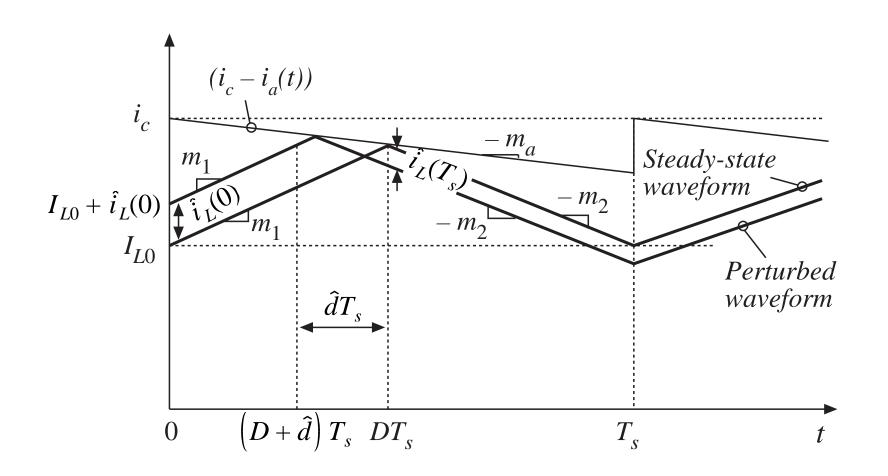

Fundamentals of Power Electronics

Stability analysis: change in perturbation over complete switching periods

First subinterval:

$$\hat{i}_L(0) = -\hat{d}T_s \left(m_1 + m_a\right)$$

Second subinterval:

$$\hat{i}_L(T_s) = -\hat{d}T_s\left(m_a - m_2\right)$$

Net change over one switching period:

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{m_2 - m_a}{m_1 + m_a}\right)$$

After *n* switching periods:

$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left(-\frac{m_2 - m_a}{m_1 + m_a}\right) = \hat{i}_L(0) \left(-\frac{m_2 - m_a}{m_1 + m_a}\right)^n = \hat{i}_L(0) \alpha^n$$

1

Characteristic value:

$$\alpha = -\frac{m_2 - m_a}{m_1 + m_a} \qquad \left| \hat{i}_L(nT_s) \right| \rightarrow \begin{cases} 0 & \text{when } |\alpha| < 1\\ \infty & \text{when } |\alpha| > 1 \end{cases}$$

Fundamentals of Power Electronics

The characteristic value $\boldsymbol{\alpha}$

α = -	1 –	$\frac{m_a}{m_2}$
	$\frac{\overline{D'}}{\overline{D}}$ -	$+\frac{m_a}{m_2}$

- For stability, require $|\alpha| < 1$
- Buck and buck-boost converters: $m_2 = -v/L$

So if v is well-regulated, then m_2 is also well-regulated

• A common choice:
$$m_a = 0.5 m_2$$

This leads to $\alpha = -1$ at D = 1, and $|\alpha| < 1$ for $0 \le D < 1$.


The minimum α that leads to stability for all *D*.

• Another common choice: $m_a = m_2$

This leads to $\alpha = 0$ for $0 \le D < 1$.

Deadbeat control, finite settling time

11.2 A Simple First-Order Model

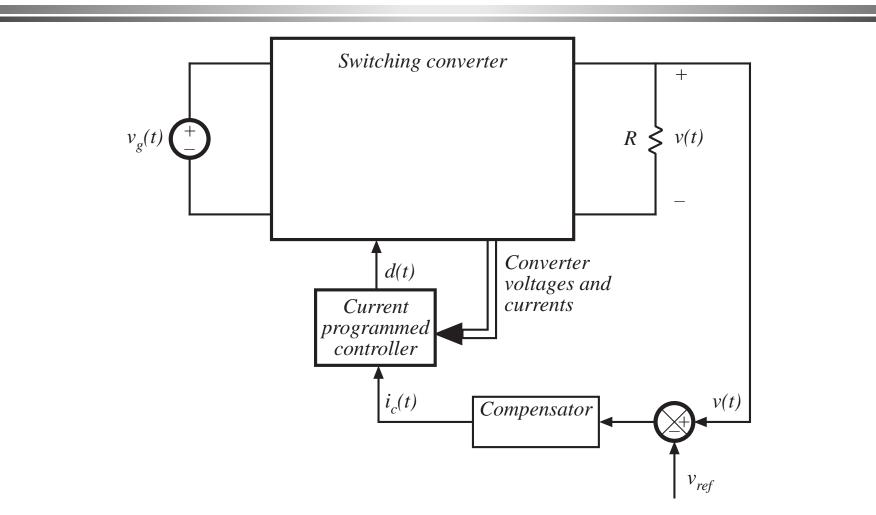

Fundamentals of Power Electronics


The first-order approximation

$$\left\langle i_L(t) \right\rangle_{T_s} = i_c(t)$$

- Neglects switching ripple and artificial ramp
- Yields physical insight and simple first-order model
- Accurate when converter operates well into CCM (so that switching ripple is small) and when the magnitude of the artificial ramp is not too large
- Resulting small-signal relation:

$$\hat{i}_L(s) \approx \hat{i}_c(s)$$

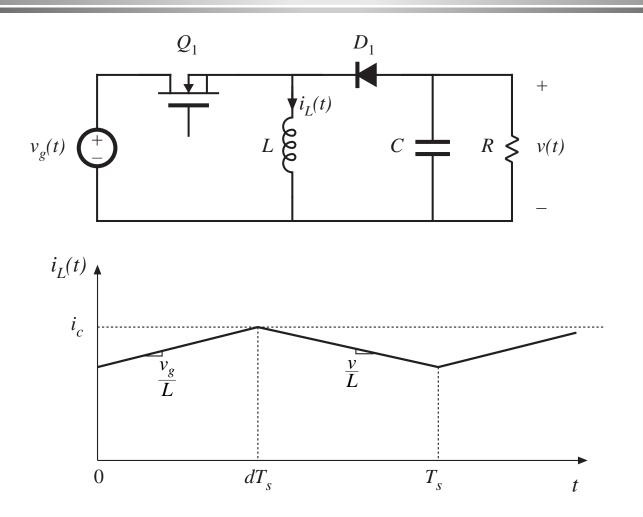11.2.1 Simple model via algebraic approach: CCM buck-boost example



Fundamentals of Power Electronics

19

Small-signal equations of CCM buck-boost, duty cycle control

$$L \frac{d\hat{i}_L(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + \left(V_g - V\right)\hat{d}(t)$$
$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}_L - \frac{\hat{v}(t)}{R} + I_L\hat{d}(t)$$
$$\hat{i}_g(t) = D\hat{i}_L + I_L\hat{d}(t)$$

Derived in Chapter 7

Transformed equations

Take Laplace transform, letting initial conditions be zero:

$$sL\hat{i}_{L}(s) = D\hat{v}_{g}(s) + D'\hat{v}(s) + \left(V_{g} - V\right)\hat{d}(s)$$
$$sC\hat{v}(s) = -D'\hat{i}_{L}(s) - \frac{\hat{v}(s)}{R} + I_{L}\hat{d}(s)$$
$$\hat{i}_{g}(s) = D\hat{i}_{L}(s) + I_{L}\hat{d}(s)$$

The simple approximation

Now let

$$\hat{i}_L(s) \approx \hat{i}_c(s)$$

Eliminate the duty cycle (now an intermediate variable), to express the equations using the new control input i_L . The inductor equation becomes:

$$sL\hat{i}_c(s) \approx D\hat{v}_g(s) + D'\hat{v}(s) + (V_g - V)\hat{d}(s)$$

Solve for the duty cycle variations:

$$\hat{d}(s) = \frac{sL\hat{i}_c(s) - D\hat{v}_g(s) - D'\hat{v}(s)}{\left(V_g - V\right)}$$

The simple approximation, continued

Substitute this expression to eliminate the duty cycle from the remaining equations:

$$sC\hat{v}(s) = -D'\hat{i}_{c}(s) - \frac{\hat{v}(s)}{R} + I_{L} \frac{sL\hat{i}_{c}(s) - D\hat{v}_{g}(s) - D'\hat{v}(s)}{\left(V_{g} - V\right)}$$
$$\hat{i}_{g}(s) = D\hat{i}_{c}(s) + I_{L} \frac{sL\hat{i}_{c}(s) - D\hat{v}_{g}(s) - D'\hat{v}(s)}{\left(V_{g} - V\right)}$$


Collect terms, simplify using steady-state relations:

$$sC\hat{v}(s) = \left(\frac{sLD}{D'R} - D'\right)\hat{i}_{c}(s) - \left(\frac{D}{R} + \frac{1}{R}\right)\hat{v}(s) - \left(\frac{D^{2}}{D'R}\right)\hat{v}_{g}(s)$$
$$\hat{i}_{g}(s) = \left(\frac{sLD}{D'R} + D\right)\hat{i}_{c}(s) - \left(\frac{D}{R}\right)\hat{v}(s) - \left(\frac{D^{2}}{D'R}\right)\hat{v}_{g}(s)$$

Fundamentals of Power Electronics


Construct equivalent circuit: input port
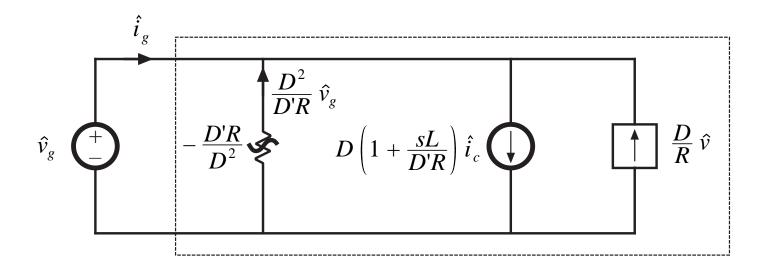
$$\hat{i}_g(s) = \left(\frac{sLD}{D'R} + D\right) \hat{i}_c(s) - \left(\frac{D}{R}\right) \hat{v}(s) - \left(\frac{D^2}{D'R}\right) \hat{v}_g(s)$$



Construct equivalent circuit: output port
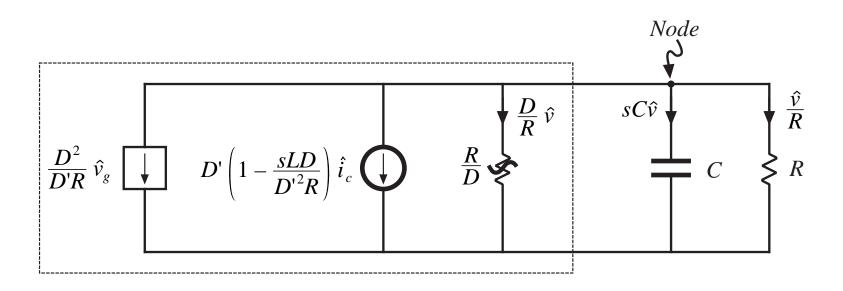
$$sC\hat{v}(s) = \left(\frac{sLD}{D'R} - D'\right)\hat{i}_c(s) - \left(\frac{D}{R} + \frac{1}{R}\right)\hat{v}(s) - \left(\frac{D^2}{D'R}\right)\hat{v}_g(s)$$



CPM Canonical Model, Simple Approximation


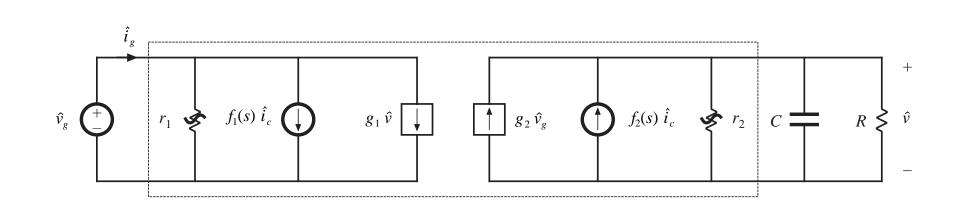


Table of results for basic converters

Table 11.1	Curren	Current programmed mode small-signal equivalent circuit parameters, simple model						
Converter	g_1	f_1	r_1	g_2	f_2	<i>r</i> ₂		
Buck	$\frac{D}{R}$	$D\left(1+\frac{sL}{R}\right)$	$-\frac{R}{D^2}$	0	1	∞		
Boost	0	1	∞	$\frac{1}{D'R}$	$D'\left(1-\frac{sL}{D'^2R}\right)$	R		
Buck-boost	$-\frac{D}{R}$	$D\left(1+\frac{sL}{D'R}\right)$	$-\frac{D'R}{D^2}$	$-\frac{D^2}{D'R}$	$-D'\left(1-\frac{sDL}{D'^2R}\right)$	$\frac{R}{D}$		

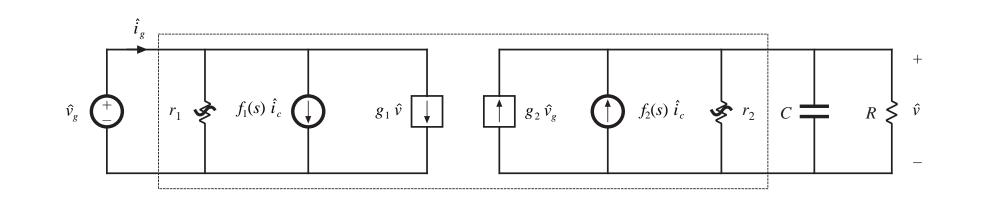Transfer functions predicted by simple model



Control-to-output transfer function


 $G_{vc}(s) = \frac{\hat{v}(s)}{\hat{i}_c(s)} \bigg|_{\hat{v}_g=0} = f_2 \left(r_2 \parallel R \parallel \frac{1}{sC} \right)$ $G_{vc}(s) = -R \frac{D'}{1+D} \frac{\left(1 - s \frac{DL}{D'^2 R} \right)}{\left(1 + s \frac{RC}{1+D} \right)}$

Result for buck-boost example

Chapter 11: Current Programmed Control

28

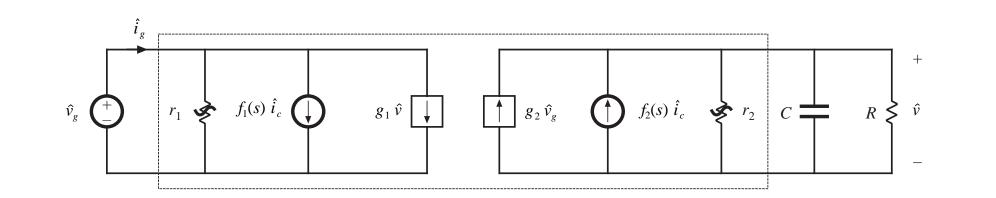Transfer functions predicted by simple model



Line-to-output transfer function


$$G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} \bigg|_{\hat{i}_c = 0} = g_2 \left(r_2 \parallel R \parallel \frac{1}{sC} \right)$$

Result for buck-boost example

$$G_{vg}(s) = -\frac{D^2}{1 - D^2} \frac{1}{\left(1 + s \frac{RC}{1 + D}\right)}$$

Fundamentals of Power Electronics

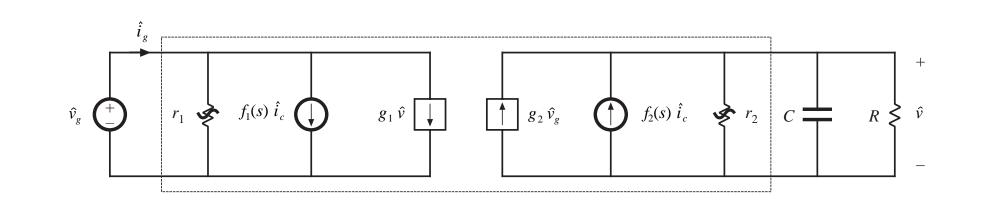Transfer functions predicted by simple model



Output impedance


$$Z_{out}(s) = r_2 \parallel R \parallel \frac{1}{sC}$$

Result for buck-boost example

$$Z_{out}(s) = \frac{R}{1+D} \frac{1}{\left(1+s \frac{RC}{1+D}\right)}$$

Chapter 11: Current Programmed Control

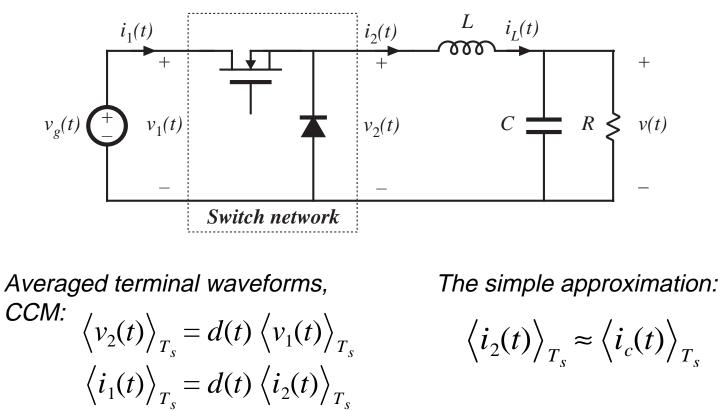11.2.2 Averaged switch modeling with the simple approximation



$$\left\langle i_2(t) \right\rangle_{T_s} \approx \left\langle i_c(t) \right\rangle_{T_s}$$

Fundamentals of Power Electronics

31

CPM averaged switch equations

$$\left\langle v_2(t) \right\rangle_{T_s} = d(t) \left\langle v_1(t) \right\rangle_{T_s} \\ \left\langle i_1(t) \right\rangle_{T_s} = d(t) \left\langle i_2(t) \right\rangle_{T_s}$$

$$\left\langle i_2(t) \right\rangle_{T_s} \approx \left\langle i_c(t) \right\rangle_{T_s}$$

Eliminate duty cycle:

$$\left\langle i_{1}(t) \right\rangle_{T_{s}} = d(t) \left\langle i_{c}(t) \right\rangle_{T_{s}} = \frac{\left\langle v_{2}(t) \right\rangle_{T_{s}}}{\left\langle v_{1}(t) \right\rangle_{T_{s}}} \left\langle i_{c}(t) \right\rangle_{T_{s}}$$

$$\left\langle i_{1}(t) \right\rangle_{T_{s}} \left\langle v_{1}(t) \right\rangle_{T_{s}} = \left\langle i_{c}(t) \right\rangle_{T_{s}} \left\langle v_{2}(t) \right\rangle_{T_{s}} = \left\langle p(t) \right\rangle_{T_{s}}$$


1

١


So:

- Output port is a current source
- Input port is a dependent current sink

CPM averaged switch model

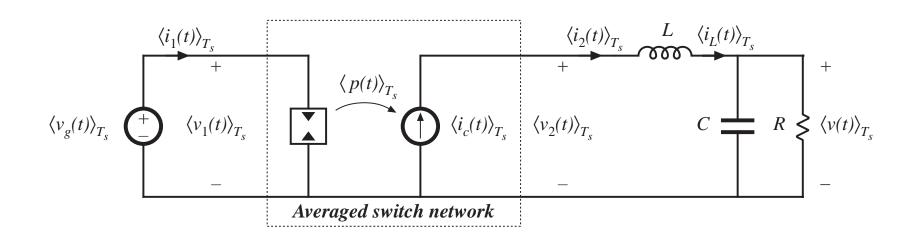

Results for other converters

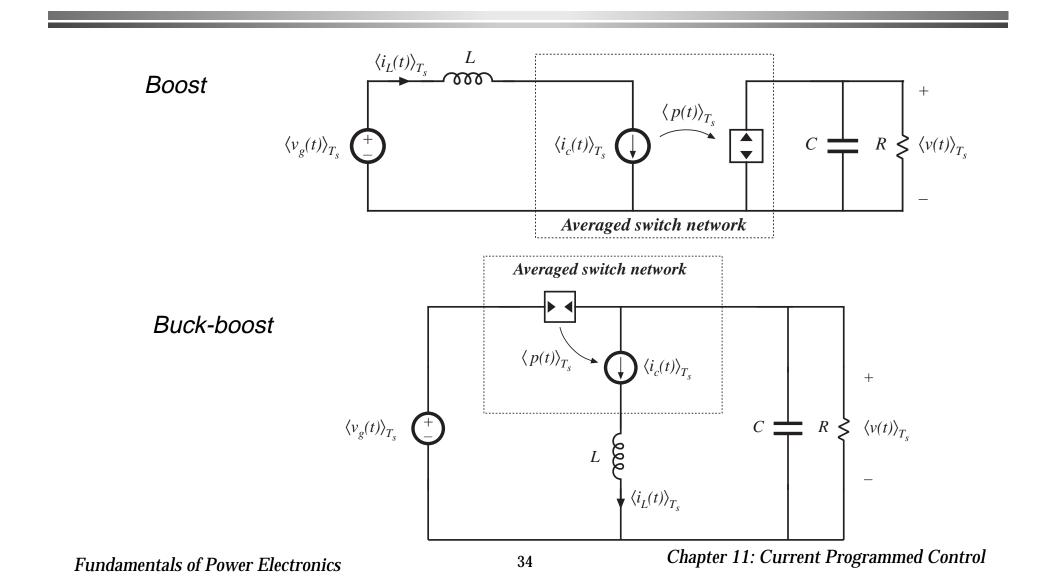

Perturbation and linearization to construct small-signal model

Let

$$\left\langle v_{1}(t) \right\rangle_{T_{s}} = V_{1} + \hat{v}_{1}(t)$$

$$\left\langle \dot{i}_{1}(t) \right\rangle_{T_{s}} = I_{1} + \hat{i}_{1}(t)$$

$$\left\langle v_{2}(t) \right\rangle_{T_{s}} = V_{2} + \hat{v}_{2}(t)$$

$$\left\langle \dot{i}_{2}(t) \right\rangle_{T_{s}} = I_{2} + \hat{i}_{2}(t)$$

$$\left\langle \dot{i}_{c}(t) \right\rangle_{T_{s}} = I_{c} + \hat{i}_{c}(t)$$

Resulting input port equation:

$$V_1 + \hat{v}_1(t) \left(I_1 + \hat{i}_1(t) \right) = \left(I_c + \hat{i}_c(t) \right) \left(V_2 + \hat{v}_2(t) \right)$$


Small-signal result:

$$\hat{i}_1(t) = \hat{i}_c(t) \frac{V_2}{V_1} + \hat{v}_2(t) \frac{I_c}{V_1} - \hat{v}_1(t) \frac{I_1}{V_1}$$

Output port equation:


$$\hat{i}_2 = \hat{i}_c$$

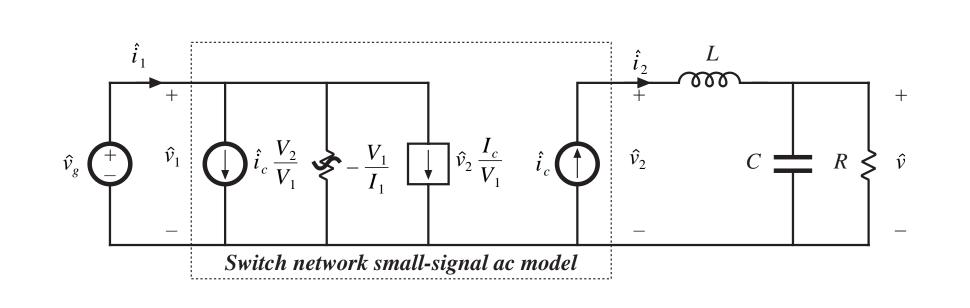Resulting small-signal model Buck example




$$\hat{i}_1(t) = \hat{i}_c(t) \frac{V_2}{V_1} + \hat{v}_2(t) \frac{I_c}{V_1} - \hat{v}_1(t) \frac{I_1}{V_1}$$

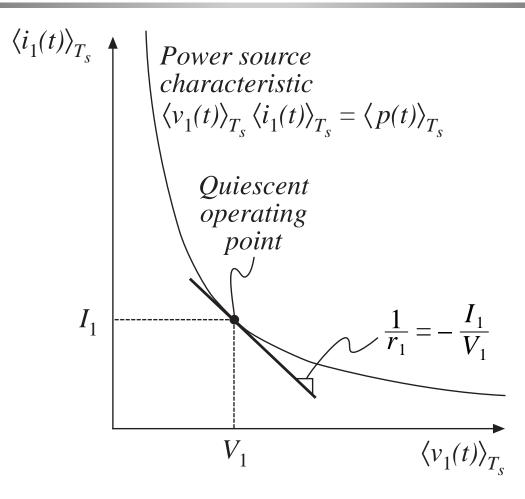Origin of input port negative incremental resistance



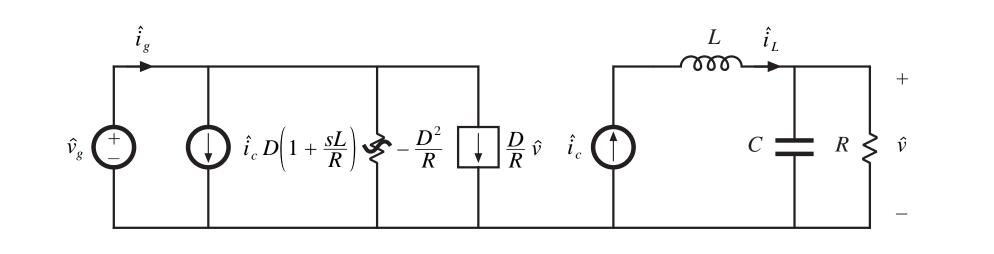
Expressing the equivalent circuit in terms of the converter input and output voltages



$$\hat{i}_1(s) = D\left(1 + s \frac{L}{R}\right)\hat{i}_c(s) + \frac{D}{R}\hat{v}(s) - \frac{D^2}{R}\hat{v}_g(s)$$

Fundamentals of Power Electronics

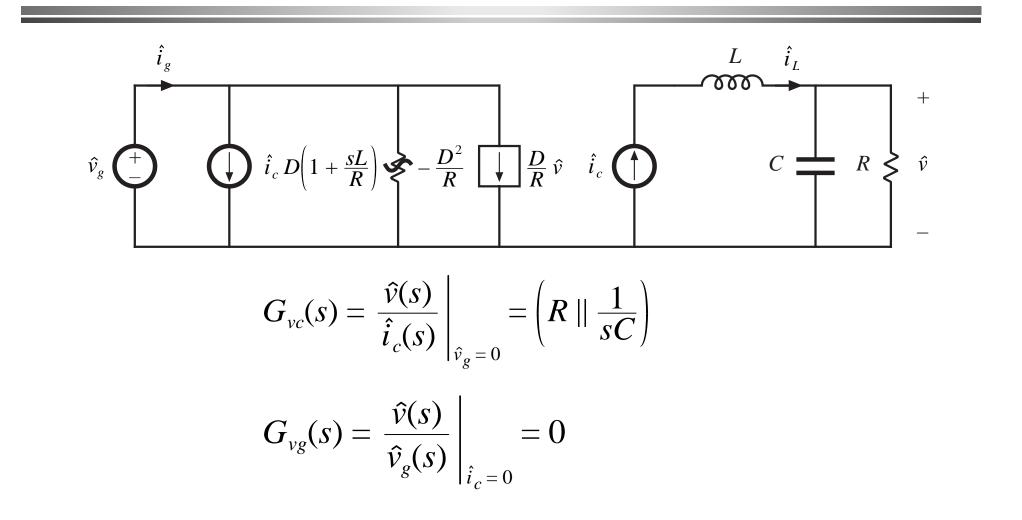Predicted transfer functions of the CPM buck converter



11.3 A More Accurate Model


- The simple models of the previous section yield insight into the lowfrequency behavior of CPM converters
- Unfortunately, they do not always predict everything that we need to know:

Line-to-output transfer function of the buck converter

Dynamics at frequencies approaching f_s

- More accurate model accounts for nonideal operation of current mode controller built-in feedback loop
- Converter duty-cycle-controlled model, plus block diagram that accurately models equations of current mode controller

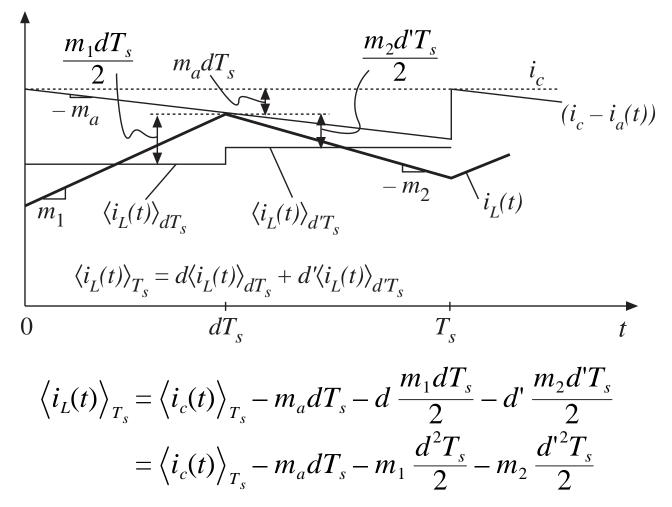11.3.1 Current programmed controller model



Fundamentals of Power Electronics

41

Perturb

Let

$$\langle i_L(t) \rangle_{T_s} = I_L + \hat{i}_L(t) \langle i_c(t) \rangle_{T_s} = I_c + \hat{i}_c(t) d(t) = D + \hat{d}(t) m_1(t) = M_1 + \hat{m}_1(t) m_2(t) = M_2 + \hat{m}_2(t)$$

It is assumed that the artificial ramp slope does not vary.

Note that it is necessary to perturb the slopes, since these depend on the applied inductor voltage. For basic converters,

buck converter

$$\hat{m}_1 = \frac{\hat{v}_g - \hat{v}}{L} \quad \hat{m}_2 = \frac{\hat{v}}{L}$$

boost converter

$$\hat{m}_1 = \frac{\hat{v}_g}{L} \qquad \hat{m}_2 = \frac{\hat{v} - \hat{v}_g}{L}$$

buck-boost converter

$$\hat{m}_1 = \frac{\hat{v}_g}{L} \qquad \hat{m}_2 = -\frac{\hat{v}}{L}$$

Fundamentals of Power Electronics

Linearize

$$(I_L + \hat{i}_L(t)) = (I_c + \hat{i}_c(t)) - M_a T_s (D + \hat{d}(t)) - (M_1 + \hat{m}_1(t)) (D + \hat{d}(t))^2 \frac{T_s}{2} - (M_2 + \hat{m}_2(t)) (D' - \hat{d}(t))^2 \frac{T_s}{2}$$

The first-order ac terms are

$$\hat{i}_{L}(t) = \hat{i}_{c}(t) - \left(M_{a}T_{s} + DM_{1}T_{s} - D'M_{2}T_{s}\right)\hat{d}(t) - \frac{D^{2}T_{s}}{2}\hat{m}_{1}(t) - \frac{D'^{2}T_{s}}{2}\hat{m}_{2}(t)$$

Simplify using dc relationships:

$$\hat{i}_L(t) = \hat{i}_c(t) - M_a T_s \hat{d}(t) - \frac{D^2 T_s}{2} \hat{m}_1(t) - \frac{D'^2 T_s}{2} \hat{m}_2(t)$$

Solve for duty cycle variations:

$$\hat{d}(t) = \frac{1}{M_a T_s} \left| \hat{i}_c(t) - \hat{i}_L(t) - \frac{D^2 T_s}{2} \,\hat{m}_1(t) - \frac{D'^2 T_s}{2} \,\hat{m}_2(t) \right|$$

Fundamentals of Power Electronics

Equation of the current programmed controller

The expression for the duty cycle is of the general form

$$\hat{d}(t) = F_m \left[\hat{i}_c(t) - \hat{i}_L(t) - F_g \hat{v}_g(t) - F_v \hat{v}(t) \right]$$
$$F_m = 1/M_a T_s$$


Table 11.2. Current programmed controller gains for basic converters

Converter	F_{g}	F_{v}
Buck	$rac{D^2T_s}{2L}$	$\frac{\left(1-2D\right)T_s}{2L}$
Boost	$\frac{\left(2D-1\right)T_s}{2L}$	$\frac{D'^2T_s}{2L}$
Buck-boost	$rac{D^2T_s}{2L}$	$-rac{D'^2T_s}{2L}$

Fundamentals of Power Electronics


Block diagram of the current programmed controller
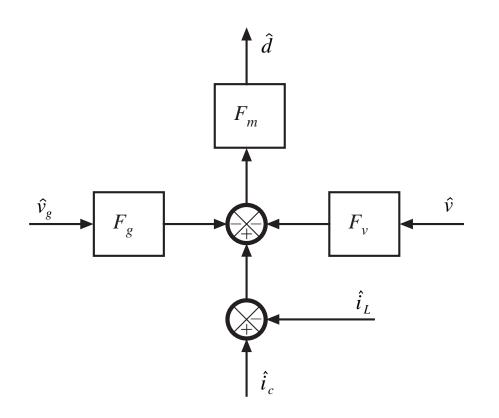
$$\hat{d}(t) = F_m \left[\hat{i}_c(t) - \hat{i}_L(t) - F_g \hat{v}_g(t) - F_v \hat{v}(t) \right]$$



- Describes the duty cycle chosen by the CPM controller
- Append this block diagram to the duty cycle controlled converter model, to obtain a complete CPM system model


CPM buck converter model

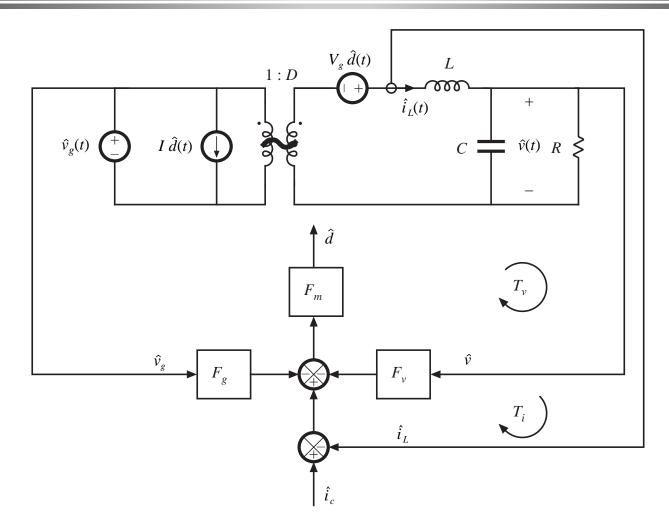


Fundamentals of Power Electronics

46

CPM boost converter model

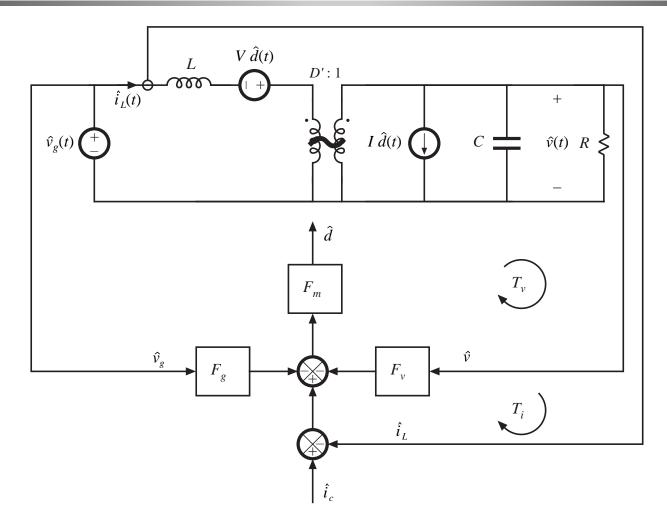


CPM buck-boost converter model

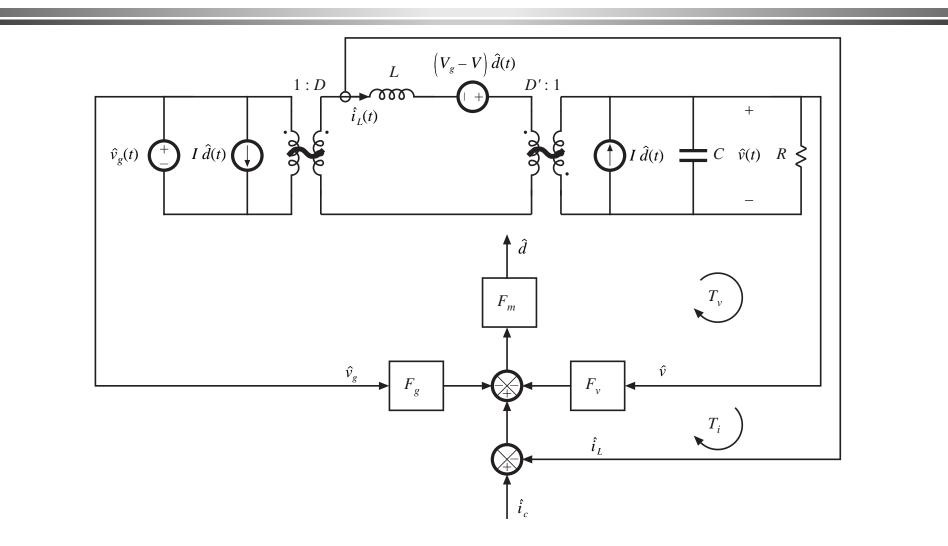


Fundamentals of Power Electronics

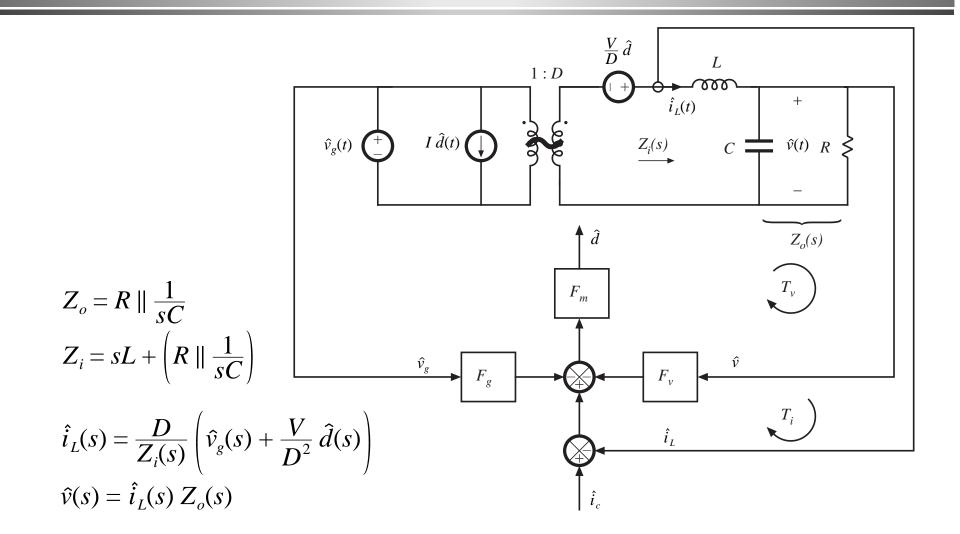11.3.2 Example: analysis of CPM buck converter



Fundamentals of Power Electronics

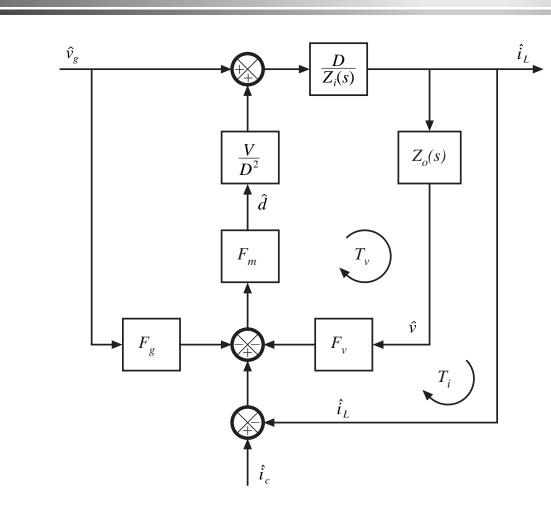Block diagram of entire CPM buck converter



Fundamentals of Power Electronics

Voltage loop gain: $T_v(s) = F_m \frac{V}{D^2} \frac{D}{Z_i(s)} Z_o(s) F_v$

Current loop gain:

$$T_{i}(s) = \frac{1}{Z_{o}(s)} \frac{T_{v}(s)}{1 + T_{v}(s)}$$
$$T_{i}(s) = \frac{F_{m} \frac{V}{D^{2}} \frac{D}{Z_{i}(s)}}{1 + F_{m} \frac{V}{D^{2}} \frac{D}{Z_{i}(s)} Z_{o}(s) F_{v}}$$

Transfer function from \hat{i}_c to \hat{i}_L :

 $\frac{\hat{i}_L(s)}{\hat{i}_c(s)} = \frac{T_i(s)}{1 + T_i(s)}$

Discussion: Transfer function from \hat{i}_c to \hat{i}_L

- When the loop gain Ti(s) is large in magnitude, then \hat{i}_L is approximately equal to \hat{i}_c . The results then coincide with the simple approximation.
- $\frac{\hat{i}_L(s)}{\hat{i}_c(s)} = \frac{T_i(s)}{1 + T_i(s)}$
- The control-to-output transfer function can be written as

$$G_{vc}(s) = \frac{\hat{v}(s)}{\hat{i}_{c}(s)} = Z_{o}(s) \frac{T_{i}(s)}{1 + T_{i}(s)}$$

which is the simple approximation result, multiplied by the factor $T_i/(1 + T_i)$.

Loop gain $T_i(s)$

Result for the buck converter:


$$T_i(s) = \left(K \frac{1-\alpha}{1+\alpha}\right) \frac{\left(1+sRC\right)}{1+s\left(\frac{L}{R} \frac{2DM_a}{M_2} \frac{1-\alpha}{1+\alpha}\right) + s^2 \left(LC \frac{2DM_a}{M_2} \frac{1-\alpha}{1+\alpha}\right)}$$

Characteristic value
$$\alpha = -\frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}}$$

Controller stable for $\mid \alpha \mid < 1$

 $K = 2L/RT_s$ CCM for K > D'

Loop gain

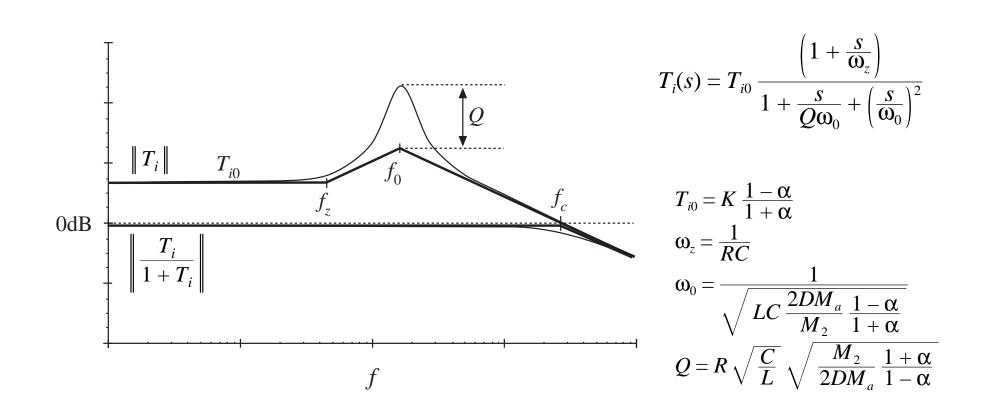

Crossover frequency f_c

High frequency asymptote of T_i is

$$T_i(s) \approx T_{i0} \frac{\left(\frac{s}{\omega_z}\right)}{\left(\frac{s}{\omega_0}\right)^2} = T_{i0} \frac{\omega_0^2}{s\omega_z}$$

Equate magnitude to one at crossover frequency:

$$\|T_i(j2\pi f_c)\| \approx T_{i0} \frac{f_0^2}{2\pi f_c f_z} = 1$$

Solve for crossover frequency:

$$f_c = \frac{M_2}{M_a} \frac{f_s}{2\pi D}$$

Fundamentals of Power Electronics

Construction of transfer functions

$$\frac{\hat{i}_L(s)}{\hat{i}_c(s)} = \frac{T_i(s)}{1 + T_i(s)} \approx \frac{1}{\left(1 + \frac{s}{\omega_c}\right)}$$
$$G_{vc}(s) = Z_o(s) \frac{T_i(s)}{1 + T_i(s)} \approx R \frac{1}{\left(1 + sRC\right)\left(1 + \frac{s}{\omega_c}\right)}$$

—the result of the simple first-order model, with an added pole at the loop crossover frequency

Exact analysis

$$G_{vc}(s) = R\left(\frac{T_{i0}}{1+T_{i0}}\right) \frac{1}{1+s\left(\frac{T_{i0}}{1+T_{i0}}\frac{1}{\omega_{z}} + \frac{1}{\left(1+T_{i0}\right)}Q\omega_{0}\right) + \frac{1}{1+T_{i0}}\left(\frac{s}{\omega_{0}}\right)^{2}}$$

for
$$|T_{i0}| >> 1$$
,

$$G_{vc}(s) \approx R \frac{1}{1 + \frac{s}{\omega_z} + \frac{s^2}{T_{i0} \omega_0^2}}$$

Low *Q* approximation:

$$G_{vc}(s) \approx R \, \frac{1}{\left(1 + \frac{s}{\omega_z}\right) \left(1 + \frac{s\omega_z}{T_{i0}\omega_0^2}\right)}$$

which agrees with the previous slide

Line-to-output transfer function

Solution of complete block diagram leads to

$$\hat{v}(s) = \hat{i}_{c}(s) Z_{o}(s) \frac{T_{i}(s)}{1 + T_{i}(s)} + \hat{v}_{g}(s) \frac{G_{g0}(s)}{1 + T_{i}(s)}$$
with
$$G_{g0}(s) = Z_{o}(s) \frac{D}{Z_{i}(s)} \frac{\left(1 - \frac{V}{D^{2}} F_{m}F_{g}\right)}{\left(1 + \frac{V}{D^{2}} F_{m}F_{v}Z_{o}(s) \frac{D}{Z_{i}(s)}\right)}$$

Fundamentals of Power Electronics

Line-to-output transfer function

$$G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_{g}(s)} \bigg|_{\hat{i}_{c}(s) = 0} = \frac{G_{g0}(s)}{1 + T_{i}(s)}$$

$$G_{vg}(s) = \frac{\left(\frac{1}{1 + T_{i0}}\right) \frac{(1 - \alpha)}{(1 + \alpha)} 2D^{2} \left(\frac{M_{a}}{M_{2}} - \frac{1}{2}\right)}{1 + s \left(\frac{T_{i0}}{1 + T_{i0}} \frac{1}{\omega_{z}} + \frac{1}{(1 + T_{i0})} Q\omega_{0}\right) + \frac{1}{1 + T_{i0}} \left(\frac{s}{\omega_{0}}\right)^{2}}$$

Poles are identical to control-to-output transfer function, and can be factored the same way:

$$G_{vg}(s) \approx \frac{G_{vg}(0)}{\left(1 + \frac{s}{\omega_z}\right) \left(1 + \frac{s}{\omega_c}\right)}$$

Fundamentals of Power Electronics

Line-to-output transfer function: dc gain

$$G_{vg}(0) \approx \frac{2D^2}{K} \left(\frac{M_a}{M_2} - \frac{1}{2} \right)$$
 for large T_{i0}


For any T_{i0} , the dc gain goes to zero when $M_a/M_2 = 0.5$

Effective feedforward of input voltage variations in CPM controller then effectively cancels out the v_g variations in the direct forward path of the converter.

11.4 Discontinuous conduction mode


- Again, use averaged switch modeling approach
- Result: simply replace
 - Transistor by power sink
 - Diode by power source
- Inductor dynamics appear at high frequency, near to or greater than the switching frequency
- Small-signal transfer functions contain a single low frequency pole
- DCM CPM boost and buck-boost are stable without artificial ramp
- DCM CPM buck without artificial ramp is stable for D < 2/3. A small artificial ramp $m_a \ge 0.086m_2$ leads to stability for all D.

DCM CPM buck-boost example

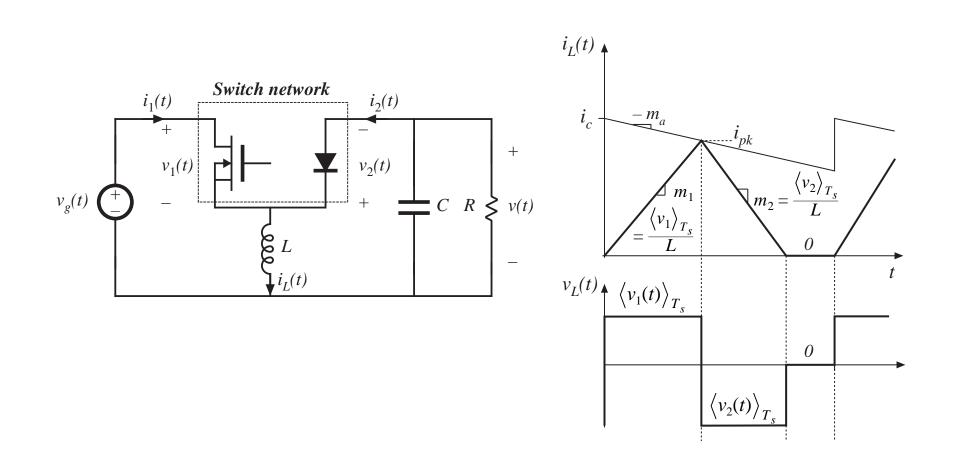


Analysis

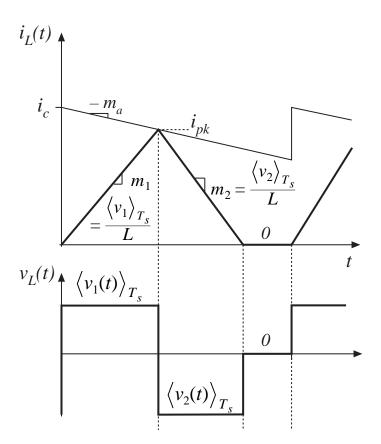 $i_{pk} = m_1 d_1 T_s$ $m_1 = \frac{\left\langle v_1(t) \right\rangle_{T_s}}{L}$ $i_c = i_{pk} + m_a d_1 T_s$ $= \left(m_1 + m_a \right) d_1 T_s$ $d_1(t) = \frac{i_c(t)}{\left(m_1 + m_a \right) T_s}$



Averaged switch input port equation

 $\left\langle i_1(t) \right\rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_1(\tau) \mathrm{d}\tau = \frac{q_1}{T_s}$ $\left\langle i_1(t) \right\rangle_T = \frac{1}{2} i_{pk}(t) d_1(t)$ $\langle i_1(t) \rangle_{T_1} = \frac{1}{2} m_1 d_1^2(t) T_s$ $\left\langle i_{1}(t)\right\rangle_{T_{s}} = \frac{\frac{1}{2}Li_{c}^{2}f_{s}}{\left\langle v_{1}(t)\right\rangle_{T_{s}}\left(1+\frac{m_{a}}{m_{1}}\right)^{2}}$ $\left\langle i_{1}(t)\right\rangle_{T_{s}}\left\langle v_{1}(t)\right\rangle_{T_{s}} = \frac{\frac{1}{2}Li_{c}^{2}f_{s}}{\left(1+\frac{m_{a}}{m_{1}}\right)^{2}} = \left\langle p(t)\right\rangle_{T_{s}}$

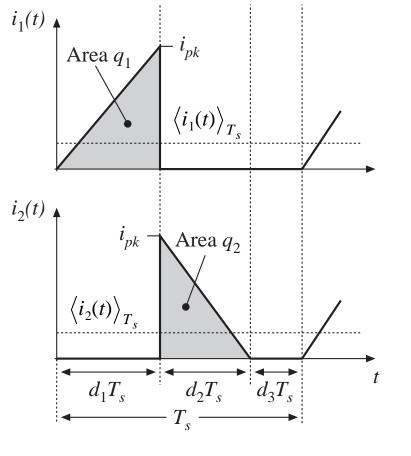

Fundamentals of Power Electronics

Discussion: switch network input port

- Averaged transistor waveforms obey a power sink characteristic
- During first subinterval, energy is transferred from input voltage source, through transistor, to inductor, equal to

$$W = \frac{1}{2} L i_{pk}^2$$


This energy transfer process accounts for power flow equal to

$$\left\langle p(t) \right\rangle_{T_s} = W f_s = \frac{1}{2} L i_{pk}^2 f_s$$

which is equal to the power sink expression of the previous slide.

Averaged switch output port equation

 $\left\langle i_2(t) \right\rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_2(\tau) \mathrm{d}\tau = \frac{q_2}{T_s}$ $q_2 = \frac{1}{2} i_{pk} d_2 T_s$ $d_{2}(t) = d_{1}(t) \frac{\left\langle v_{1}(t) \right\rangle_{T_{s}}}{\left\langle v_{2}(t) \right\rangle_{T}}$ $\left\langle i_2(t) \right\rangle_{T_s} = \frac{\left\langle p(t) \right\rangle_{T_s}}{\left\langle v_2(t) \right\rangle}$

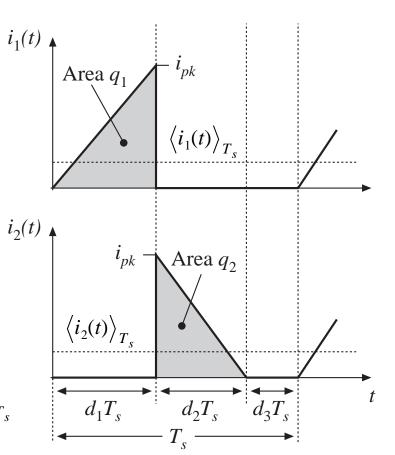


Chapter 11: Current Programmed Control

Fundamentals of Power Electronics


Discussion: switch network output port

- Averaged diode waveforms obey a power sink characteristic
- During second subinterval, all stored energy in inductor is transferred, through diode, to load
- Hence, in averaged model, diode becomes a power source, having value equal to the power consumed by the transistor power sink element

Averaged equivalent circuit

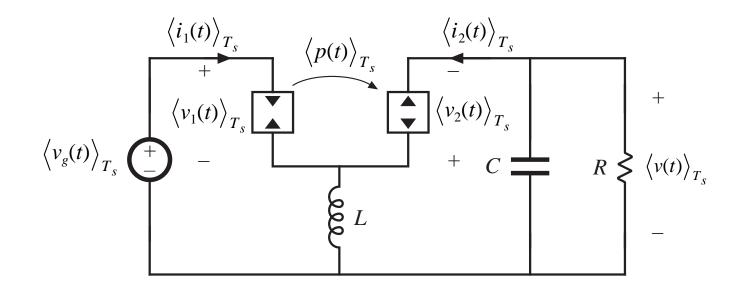

Steady state model: DCM CPM buck-boost

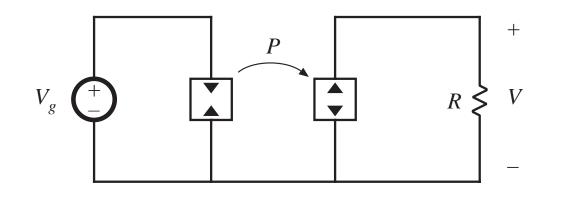

Solution


Fundamentals of Power Electronics

$$\frac{V^2}{R} = P$$
$$P = \frac{\frac{1}{2}LI_c^2(t)f_s}{\left(1 + \frac{M_a}{M_1}\right)^2}$$

$$V = \sqrt{PR} = I_c \qquad \sqrt{\frac{RLf_s}{2\left(1 + \frac{M_a}{M_1}\right)^2}}$$

for a resistive load

Models of buck and boost

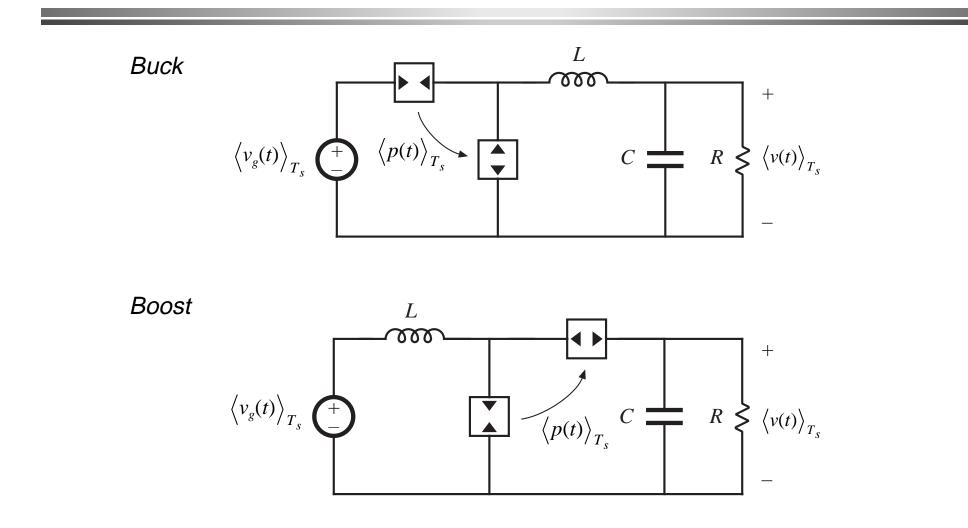


Summary of steady-state DCM CPM characteristics

Stability range Converter М I_{crit} when $m_a = 0$ $\frac{P_{load} - P}{P_{load}}$ $0 \le M < \frac{2}{3}$ $\frac{1}{2} \left(I_c - M m_a T \right)$ Buck $\frac{P_{load}}{P_{load} - P}$ $\frac{\left(I_c - \frac{M-1}{M} m_a T_s\right)}{2 M}$ Boost $0 \le D \le 1$ $\frac{\left(I_c - \frac{M}{M-1} m_a T_s\right)}{2\left(M-1\right)}$ **Buck-boost** Depends on load characteristic: $0 \le D \le 1$ $P_{load} = P$ $|I| > |I_{crit}|$ for CCM $|I| < |I_{crit}|$ for DCM

Table 11.3. Steady-state DCM CPM characteristics of basic converters

Fundamentals of Power Electronics

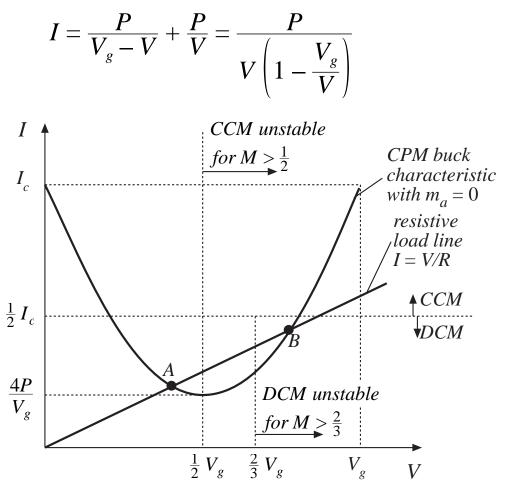
Buck converter: output characteristic with $m_a = 0$




- with a resistive load, there can be two operating points
- the operating point having $V > 0.67 V_g$ can be shown to be unstable

Fundamentals of Power Electronics


Linearized small-signal models: Buck

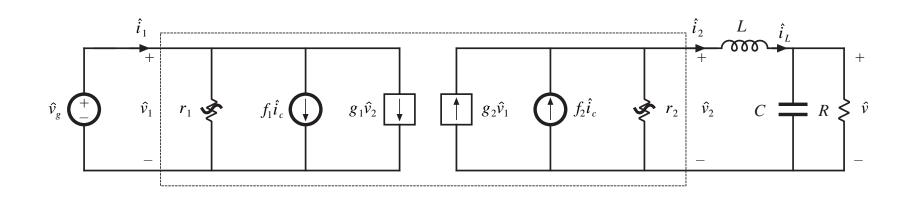

Linearized small-signal models: Boost

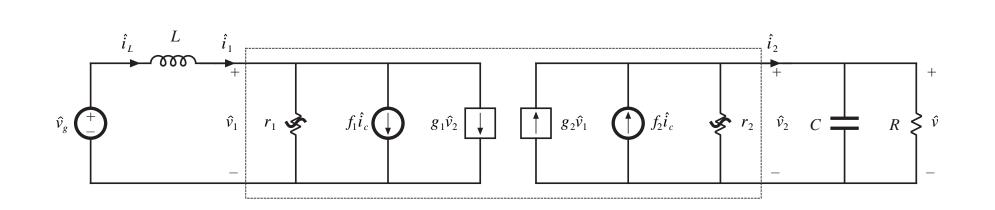

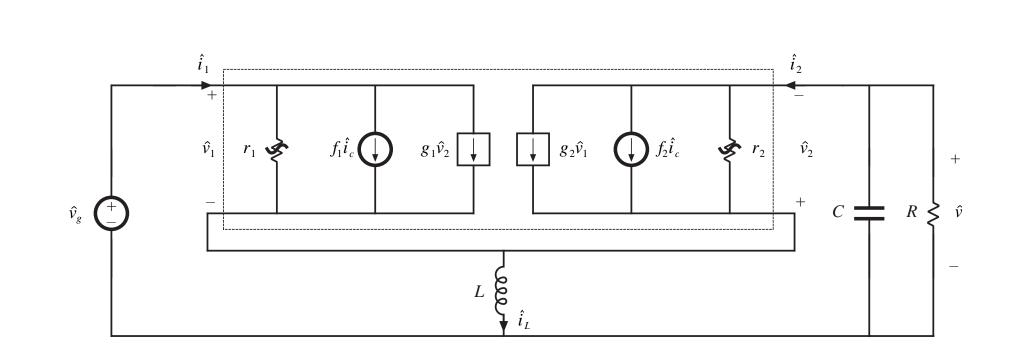Linearized small-signal models: Buck-boost



DCM CPM small-signal parameters: input port

Converter	g_1	f_1	<i>r</i> ₁
Buck	$rac{1}{R}\left(rac{M^2}{1-M} ight)rac{\left(1-rac{m_a}{m_1} ight)}{\left(1+rac{m_a}{m_1} ight)}$	$2 \frac{I_1}{I_c}$	$-R\left(rac{1-M}{M^2} ight)rac{\left(1+rac{m_a}{m_1} ight)}{\left(1-rac{m_a}{m_1} ight)}$
Boost	$-rac{1}{R}\left(rac{M}{M-1} ight)$	$2 \frac{I}{I_c}$	$\frac{R}{M^2 \left(\frac{2-M}{M-1} + \frac{2\frac{m_a}{m_1}}{1+\frac{m_a}{m_1}}\right)}$
Buck-boost	0	$2 \frac{I_1}{I_c}$	$rac{-R}{M^2} rac{\left(1+rac{m_a}{m_1} ight)}{\left(1-rac{m_a}{m_1} ight)}$

umant and anomened DCM amoult signal activations singuit a super- T_{11} 11 1 1 0


Chapter 11: Current Programmed Control

DCM CPM small-signal parameters: output port

Table 11.5. Current programmed DCM small-signal equivalent circuit parameters: output port						
Converter	g_2	f_2	r_2			
Buck	$\frac{1}{R} \left(\frac{M}{1-M} \right) \frac{\left(\frac{m_a}{m_1} \left(2 - M \right) - M \right)}{\left(1 + \frac{m_a}{m_1} \right)}$	$2 \frac{I}{I_c}$	$R rac{ig(1-Mig)ig(1+rac{m_a}{m_1}ig)}{ig(1-2M+rac{m_a}{m_1}ig)}$			
Boost	$rac{1}{R}\left(rac{M}{M-1} ight)$	$2 \frac{I_2}{I_c}$	$R\left(rac{M-1}{M} ight)$			
Buck-boost	$rac{2M}{R} rac{\left(rac{m_a}{m_1} ight)}{\left(1+rac{m_a}{m_1} ight)}$	$2 \frac{I_2}{I_c}$	R			

Simplified DCM CPM model, with L = 0

Buck, boost, buck-boost all become

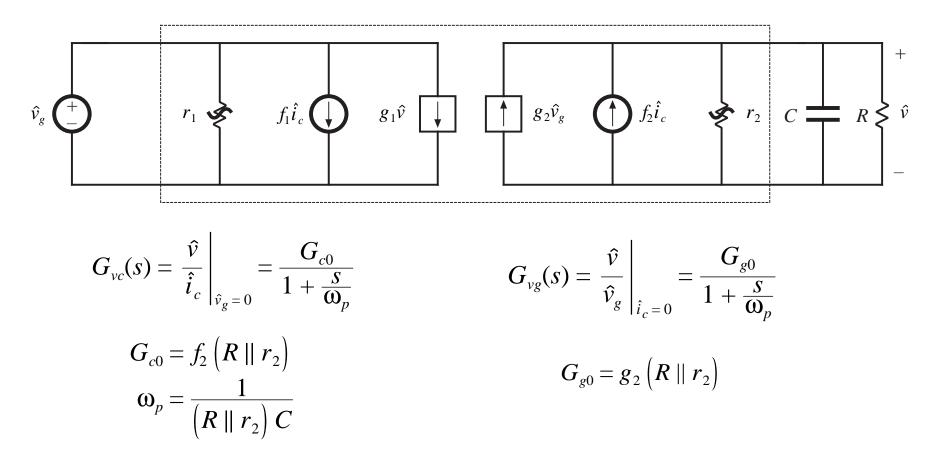

Fundamentals of Power Electronics

Chapter 11: Current Programmed Control

Buck ω_p

Plug in parameters:

$$\omega_{p} = \frac{1}{RC} \frac{\left(2 - 3M\right)\left(1 - M\right) + \frac{m_{a}}{m_{2}}M\left(2 - M\right)}{\left(1 - M\right)\left(1 - M + M\frac{m_{a}}{m_{2}}\right)}$$

- For $m_a = 0$, numerator is negative when M > 2/3.
- ω_p then constitutes a RHP pole. Converter is unstable.
- Addition of small artificial ramp stabilizes system.
- $m_a > 0.086$ leads to stability for all $M \le 1$.
- Output voltage feedback can also stabilize system, without an artificial ramp

11.5 Summary of key points

- 1. In current-programmed control, the peak switch current $i_s(t)$ follows the control input $i_c(t)$. This widely used control scheme has the advantage of a simpler control-to-output transfer function. The line-to-output transfer functions of current-programmed buck converters are also reduced.
- 2. The basic current-programmed controller is unstable when D > 0.5, regardless of the converter topology. The controller can be stabilized by addition of an artificial ramp having slope ma. When $m_a \ge 0.5 m_2$, then the controller is stable for all duty cycle.
- 3. The behavior of current-programmed converters can be modeled in a simple and intuitive manner by the first-order approximation $\langle i_L(t) \rangle_{T_s} \approx i_c(t)$. The averaged terminal waveforms of the switch network can then be modeled simply by a current source of value i_c , in conjunction with a power sink or power source element. Perturbation and linearization of these elements leads to the small-signal model. Alternatively, the small-signal converter equations derived in Chapter 7 can be adapted to cover the current programmed mode, using the simple approximation $i_L(t) \approx i_c(t)$.

Fundamentals of Power Electronics

Chapter 11: Current Programmed Control

Summary of key points

- 4. The simple model predicts that one pole is eliminated from the converter line-to-output and control-to-output transfer functions. Current programming does not alter the transfer function zeroes. The dc gains become load-dependent.
- 5. The more accurate model of Section 11.3 correctly accounts for the difference between the average inductor current $\langle i_L(t) \rangle_{T_s}$ and the control input $i_c(t)$. This model predicts the nonzero line-to-output transfer function $G_{vg}(s)$ of the buck converter. The current-programmed controller behavior is modeled by a block diagram, which is appended to the small-signal converter models derived in Chapter 7. Analysis of the resulting multiloop feedback system then leads to the relevant transfer functions.
- 6. The more accurate model predicts that the inductor pole occurs at the crossover frequency fc of the effective current feedback loop gain $T_i(s)$. The frequency f_c typically occurs in the vicinity of the converter switching frequency f_s . The more accurate model also predicts that the line-to-output transfer function $G_{vg}(s)$ of the buck converter is nulled when $m_a = 0.5 m_2$.

Fundamentals of Power Electronics

Chapter 11: Current Programmed Control

Summary of key points

7. Current programmed converters operating in the discontinuous conduction mode are modeled in Section 11.4. The averaged transistor waveforms can be modeled by a power sink, while the averaged diode waveforms are modeled by a power source. The power is controlled by $i_c(t)$. Perturbation and linearization of these averaged models, as usual, leads to small-signal equivalent circuits.

Part III. Magnetics


- 12. Basic Magnetics Theory
- 13. Filter Inductor Design
- 14. Transformer Design

Chapter 12. Basic Magnetics Theory


12.1. Review of basic magnetics							
12.1.1. Basic relations	12.1.2. Magnetic circuits						
12.2. Transformer modeling							
12.2.1. The ideal transformer	12.2.3. Leakage inductances						
12.2.2. The magnetizing inductance							
12.3. Loss mechanisms in magnetic devices							
12.3.1. Core loss	12.3.2. Low-frequency copper loss						
12.4. Eddy currents in winding conductors							
12.4.1. The skin effect	12.4.4. Power loss in a layer						
12.4.2. The proximity effect	12.4.5. Example: power loss in a transformer winding						
12.4.3. MMF diagrams	12.4.6. PWM waveform harmonics						

Chapter 12: Basic Magnetics Theory

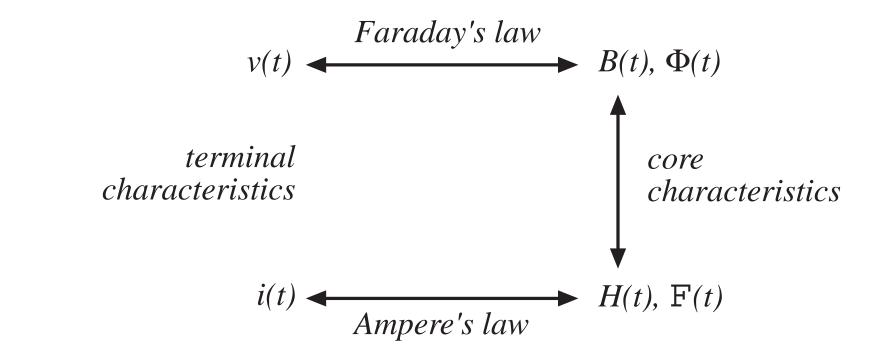12.1. Review of basic magnetics12.1.1. Basic relations




Basic quantities

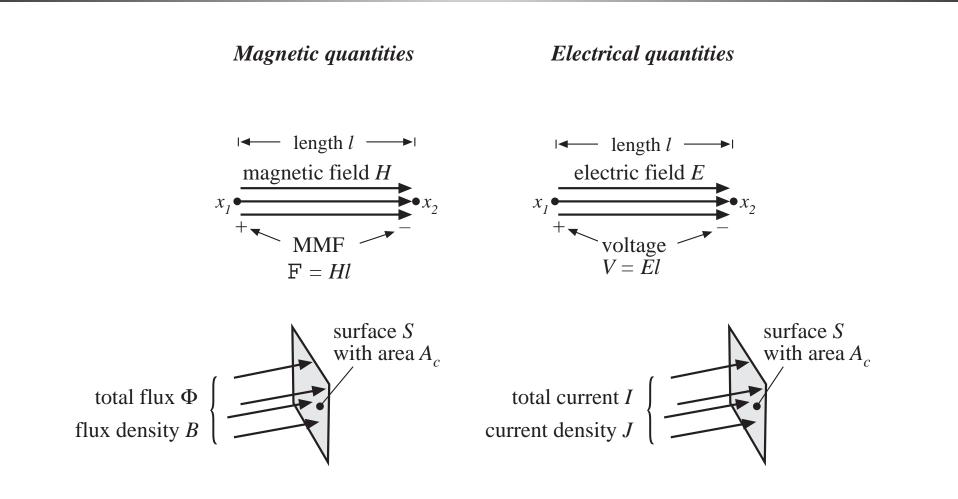


Magnetic field *H* and magnetomotive force F

Magnetomotive force (MMF) F between points x_1 and x_2 is related to the magnetic field *H* according to

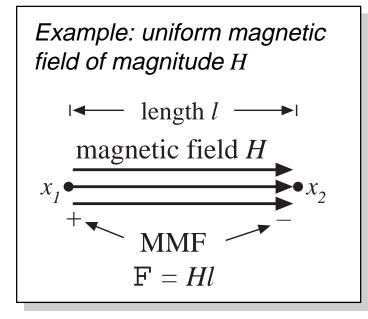
$$\mathbf{F} = \int_{x_1}^{x_2} \boldsymbol{H} \cdot \boldsymbol{dl}$$



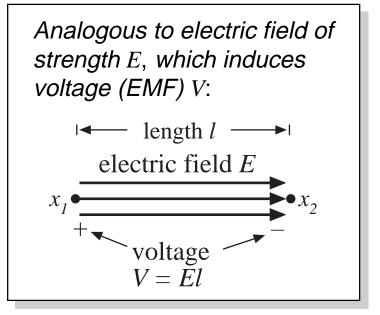

Fundamentals of Power Electronics

Flux density *B* and total flux Φ

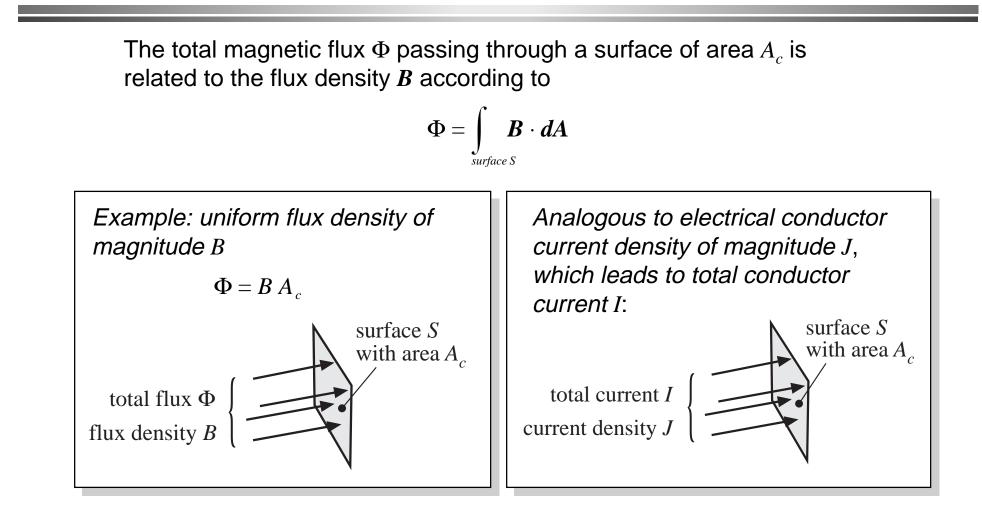

Faraday's law


Voltage v(t) is induced in a loop of wire by change in the total flux $\Phi(t)$ passing through the interior of the loop, according to

$$v(t) = \frac{d\Phi(t)}{dt}$$

flux $\Phi(t)$


For uniform flux distribution, $\Phi(t) = B(t)A_c$ and hence

$$v(t) = A_c \frac{dB(t)}{dt}$$

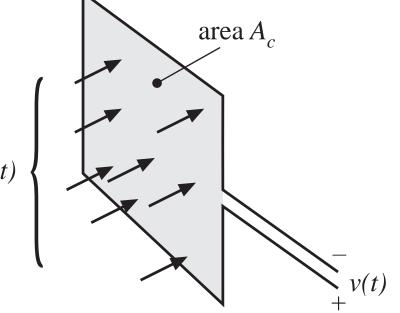

Lenz's law

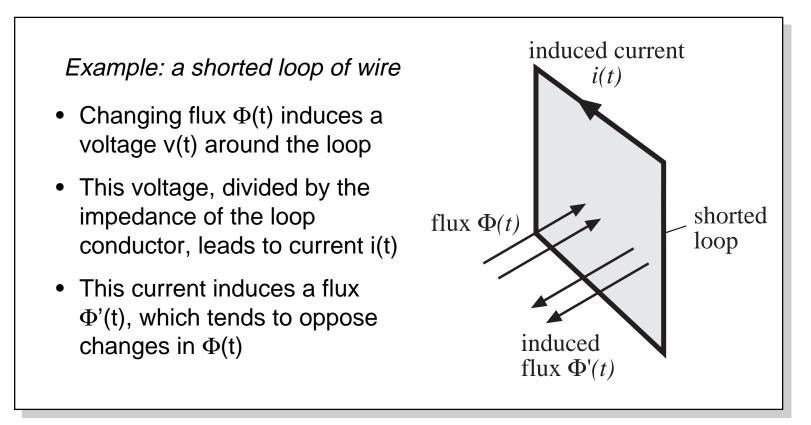
The voltage v(t) induced by the changing flux $\Phi(t)$ is of the polarity that tends to drive a current through the loop to counteract the flux change.



Ampere's law

The net MMF around a closed path is equal to the total current passing through the interior of the path:

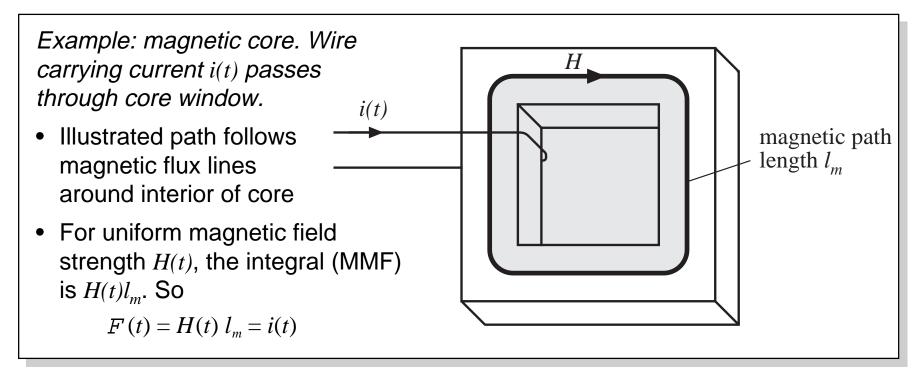
$$\oint_{closed path} \boldsymbol{H} \cdot \boldsymbol{dl} = total \ current \ passing \ through \ interior \ of \ path$$



Ampere's law: discussion

- Relates magnetic field strength H(t) to winding current i(t)
- We can view winding currents as sources of MMF
- Previous example: total MMF around core, $F(t) = H(t)l_m$, is equal to the winding current MMF i(t)
- The total MMF around a closed loop, accounting for winding current MMF's, is zero

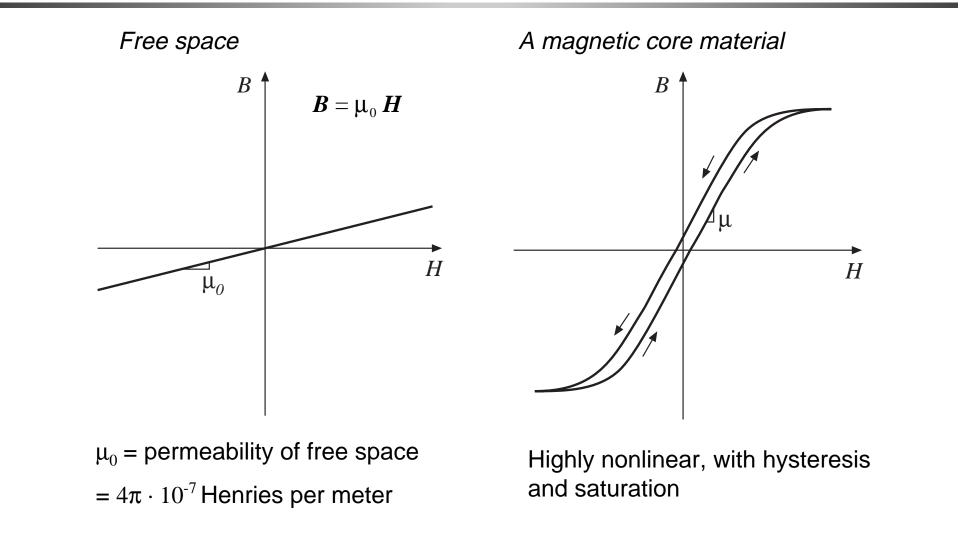
Core material characteristics: the relation between *B* and *H*



Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory

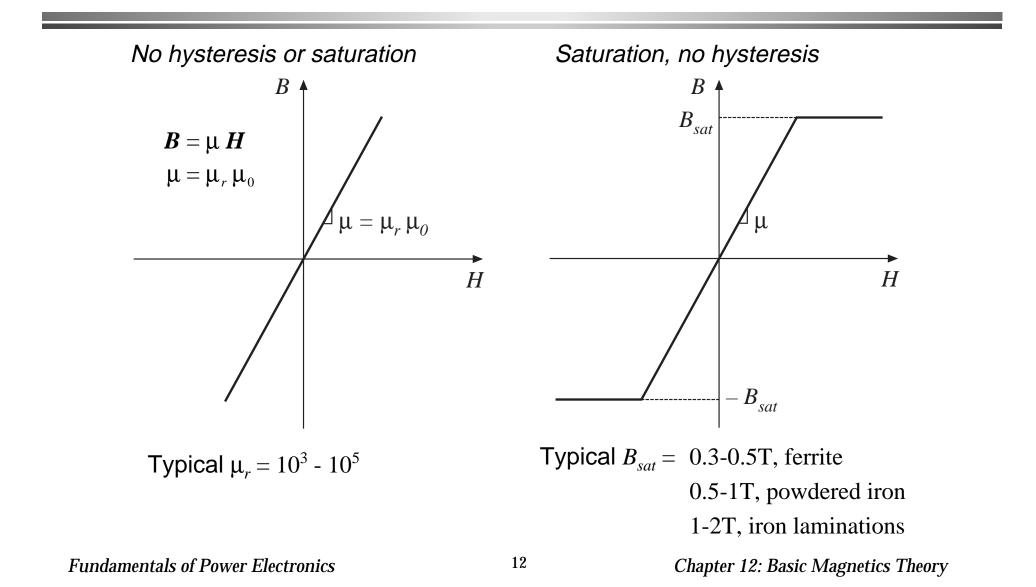Piecewise-linear modeling of core material characteristics




Units

Table 12.1. Units for magnetic quantities

quantity	MKS	unrationalized cgs	conversions	
core material equation	$B=\mu_0\;\mu_{ m r}\;H$	$B = \mu_{ m r} H$		
В	Tesla	Gauss	$1T = 10^{4}G$	
Н	Ampere / meter	Oersted	$1A/m = 4\pi \cdot 10^{-3}$ Oe	
Φ	Weber	Maxwell	$1Wb = 10^8 Mx$ $1T = 1Wb / m^2$	

Example: a simple inductor

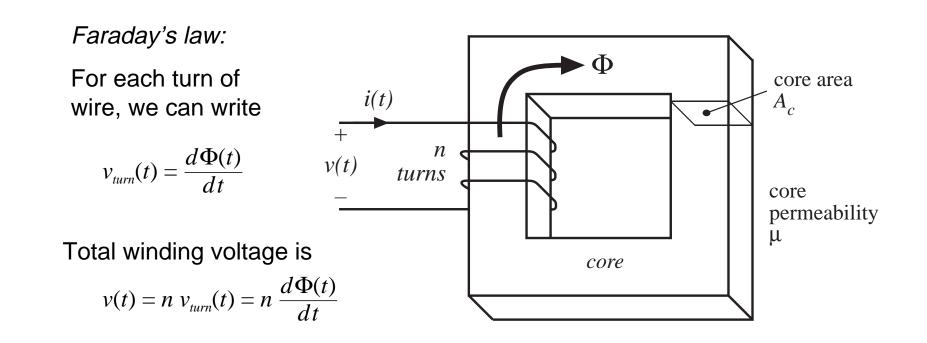

Express in terms of the average flux density $B(t) = \Phi(t)/A_c$


$$v(t) = n A_c \frac{dB(t)}{dt}$$

Fundamentals of Power Electronics

Inductor example: Ampere's law

Choose a closed path which follows the average magnetic field line around the interior of the core. Length of this path is called the *mean magnetic path length* l_m .

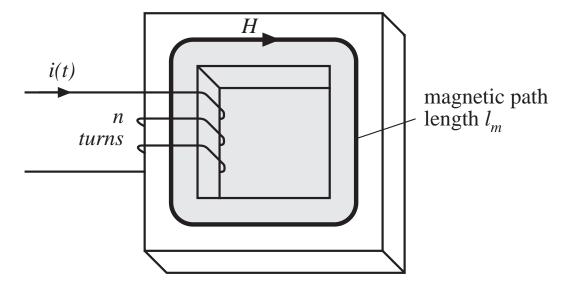For uniform field strength H(t), the core MMF around the path is $H l_m$.




Winding contains n turns of wire, each carrying current i(t). The net current passing through the path interior (i.e., through the core window) is ni(t).

From Ampere's law, we have

$$H(t) l_m = n i(t)$$

Inductor example: core material model

$$B = \begin{cases} B_{sat} & \text{for } H \ge B_{sat} / \mu \\ \mu H & \text{for } |H| < B_{sat} / \mu \\ -B_{sat} & \text{for } H \le B_{sat} / \mu \end{cases}$$

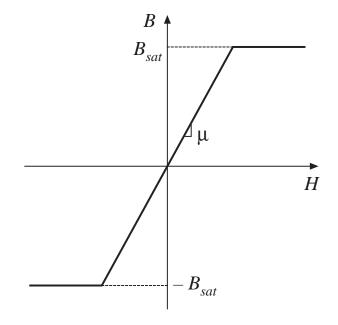

Find winding current at onset of saturation: substitute $i = I_{sat}$ and $H = B_{sat}/\mu$ into equation previously derived via Ampere's law. Result is

$$I_{sat} = \frac{B_{sat} l_m}{\mu n}$$

Electrical terminal characteristics

We have:

$$v(t) = n A_c \frac{dB(t)}{dt} \qquad H(t) l_m = n i(t) \qquad B = \begin{cases} B_{sat} & \text{for } H \ge B_{sat} / \mu \\ \mu H & \text{for } |H| < B_{sat} / \mu \\ -B_{sat} & \text{for } H \le B_{sat} / \mu \end{cases}$$

Eliminate *B* and *H*, and solve for relation between *v* and *i*. For $|i| < I_{sat}$,

$$v(t) = \mu n A_c \frac{dH(t)}{dt} \qquad \longrightarrow \qquad v(t) = \frac{\mu n^2 A_c}{l_m} \frac{di(t)}{dt}$$

which is of the form

$$v(t) = L \frac{di(t)}{dt}$$
 with $L = \frac{\mu n^2 A_c}{l_m}$

-an inductor


For $|i| > I_{sat}$ the flux density is constant and equal to B_{sat} . Faraday's law then predicts

$$v(t) = n A_c \frac{dB_{sat}}{dt} = 0$$
 —saturation leads to short circuit

Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory

12.1.2. Magnetic circuits

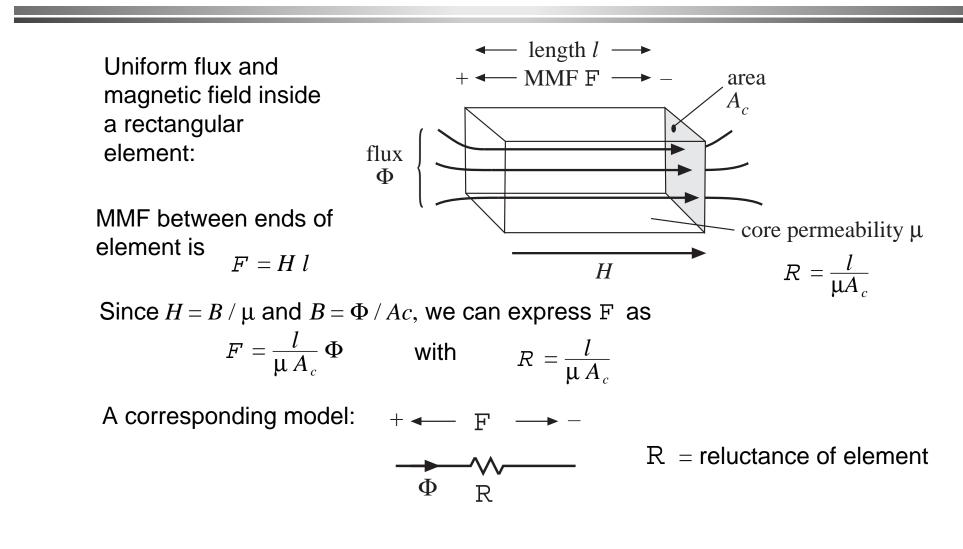


Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory

Magnetic circuits: magnetic structures composed of multiple windings and heterogeneous elements

- Represent each element with reluctance
- Windings are sources of MMF
- MMF \rightarrow voltage, flux \rightarrow current
- Solve magnetic circuit using Kirchoff's laws, etc.

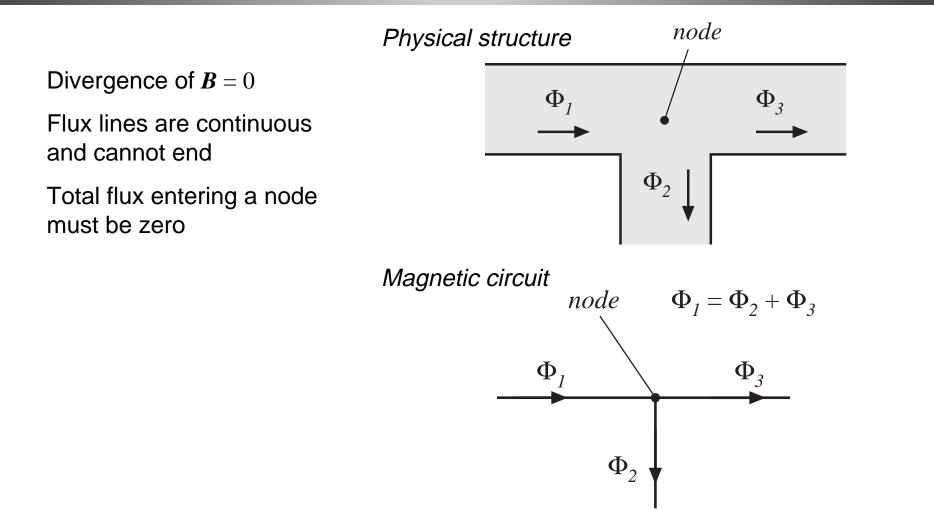Magnetic analog of Kirchoff's current law



Fundamentals of Power Electronics

Magnetic analog of Kirchoff's voltage law

Follows from Ampere's law:


$$\oint_{closed path} \boldsymbol{H} \cdot \boldsymbol{dl} = total \ current \ passing \ through \ interior \ of \ path$$

Left-hand side: sum of MMF's across the reluctances around the closed path


Right-hand side: currents in windings are sources of MMF's. An *n*-turn winding carrying current i(t) is modeled as an MMF (voltage) source, of value ni(t).


Total MMF's around the closed path add up to zero.

Example: inductor with air gap

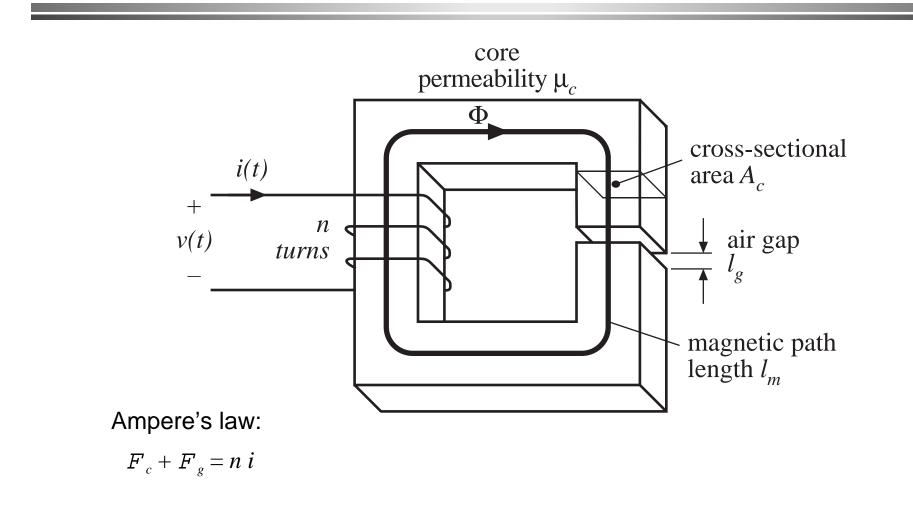

Magnetic circuit model

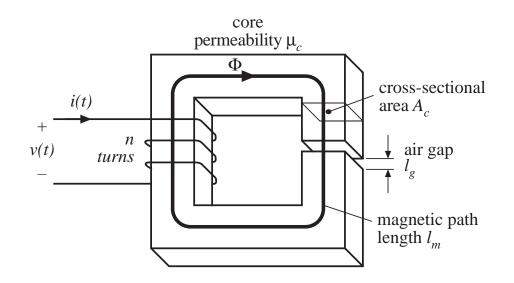

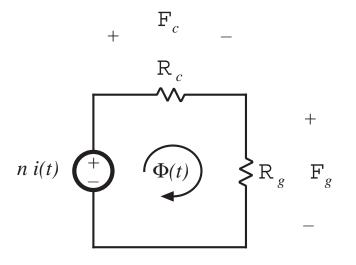


$$F_{c} + F_{g} = n i \qquad \qquad R_{c} = \frac{l_{c}}{\mu A_{c}}$$
$$n i = \Phi \left(R_{c} + R_{g} \right) \qquad \qquad R_{g} = \frac{l_{g}}{\mu_{0} A_{c}}$$

Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory


Solution of model

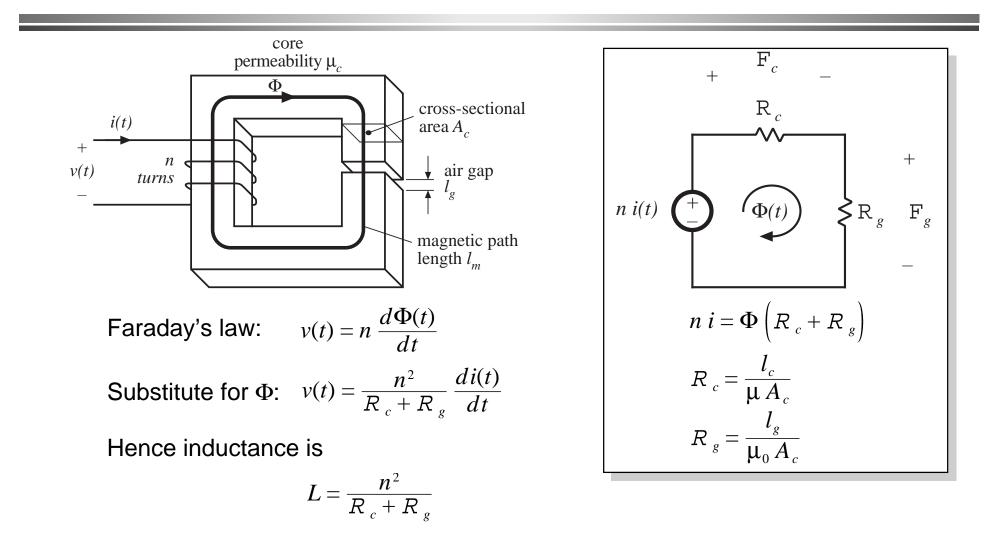

Fundamentals of Power Electronics


Chapter 12: Basic Magnetics Theory

Effect of air gap

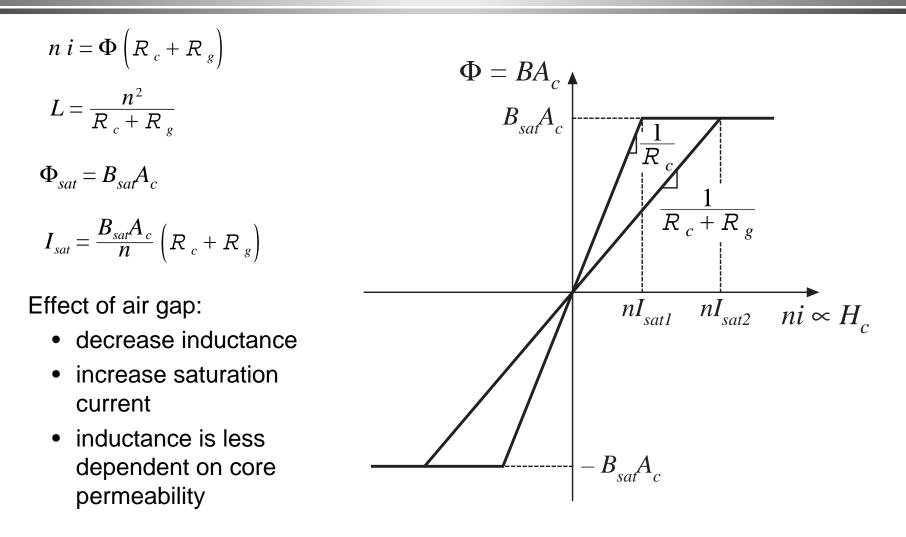

Fundamentals of Power Electronics

12.2. Transformer modeling

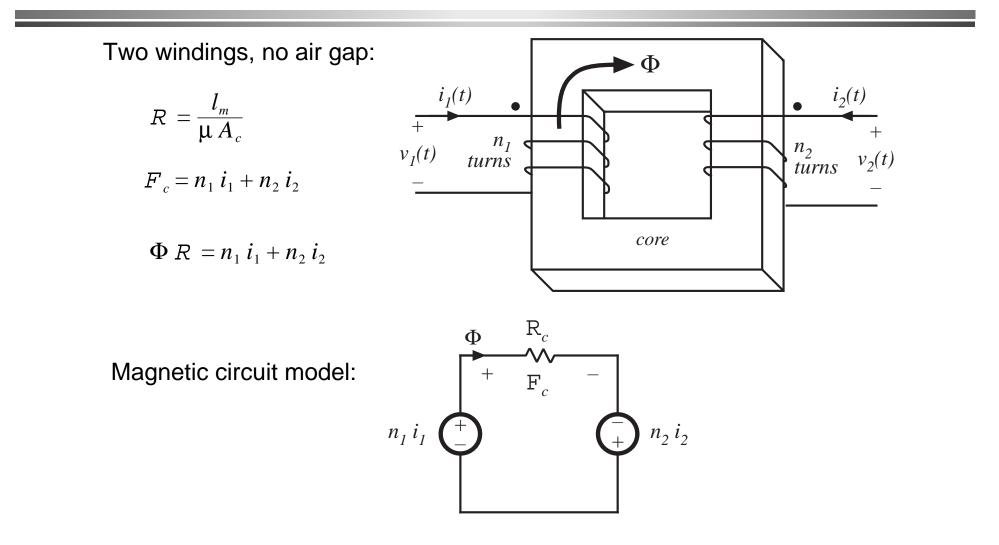

Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory

12.2.1. The ideal transformer

In the ideal transformer, the core reluctance R approaches zero.

MMF $F_c = \Phi R$ also approaches zero. We then obtain

$$0 = n_1 i_1 + n_2 i_2$$

Also, by Faraday's law,

$$v_1 = n_1 \frac{d\Phi}{dt}$$
$$v_2 = n_2 \frac{d\Phi}{dt}$$


Eliminate Φ :

$$\frac{d\Phi}{dt} = \frac{v_1}{n_1} = \frac{v_2}{n_2}$$

Ideal transformer equations:


$$\frac{v_1}{n_1} = \frac{v_2}{n_2}$$
 and $n_1 i_1 + n_2 i_2 = 0$

Fundamentals of Power Electronics

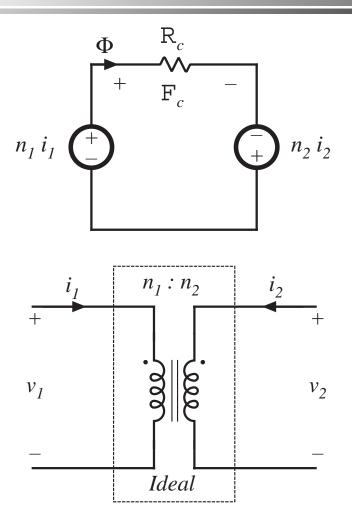



12.2.2. The magnetizing inductance

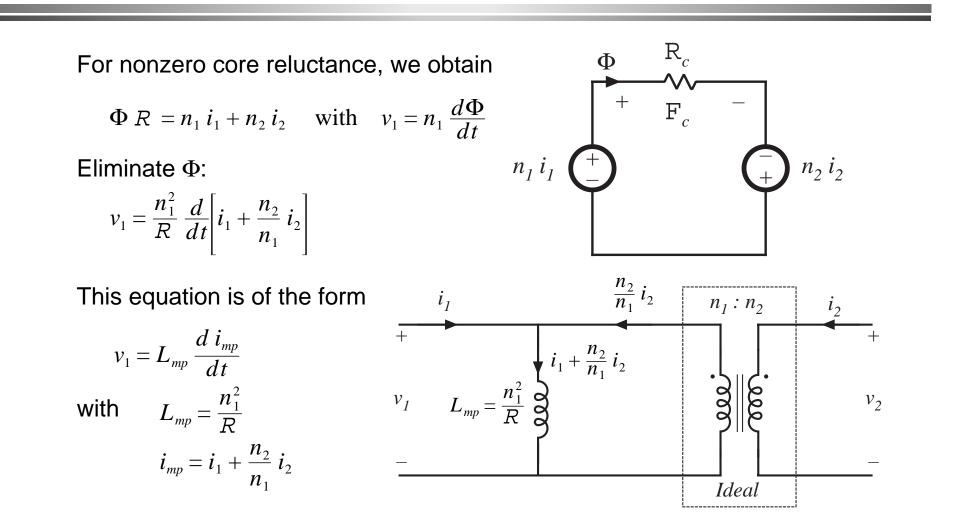

Magnetizing inductance: discussion

- Models magnetization of core material
- A real, physical inductor, that exhibits saturation and hysteresis
- If the secondary winding is disconnected:

we are left with the primary winding on the core

primary winding then behaves as an inductor

the resulting inductor is the magnetizing inductance, referred to the primary winding

• Magnetizing current causes the ratio of winding currents to differ from the turns ratio

Transformer saturation

- Saturation occurs when core flux density B(t) exceeds saturation flux density B_{sat} .
- When core saturates, the magnetizing current becomes large, the impedance of the magnetizing inductance becomes small, and the windings are effectively shorted out.
- Large winding currents $i_1(t)$ and $i_2(t)$ **do not** necessarily lead to saturation. If

$$0 = n_1 i_1 + n_2 i_2$$

then the magnetizing current is zero, and there is no net magnetization of the core.

• Saturation is caused by excessive applied volt-seconds

Saturation vs. applied volt-seconds

Magnetizing current depends on the integral of the applied winding voltage:

$$i_{mp}(t) = \frac{1}{L_{mp}} \int v_1(t) dt$$

Flux density is proportional:

$$B(t) = \frac{1}{n_1 A_c} \int v_1(t) dt$$


 $i_{1} \qquad \frac{n_{2}}{n_{1}} i_{2} \qquad n_{1} : n_{2} \qquad i_{2} \\ + \\ v_{1} \qquad L_{mp} = \frac{n_{1}^{2}}{R} \qquad i_{1} + \frac{n_{2}}{n_{1}} i_{2} \\ - \\ Ideal \qquad Ideal$

Flux density befcomes large, and core saturates, when the applied volt-seconds λ_1 are too large, where


$$\lambda_1 = \int_{t_1}^{t_2} v_1(t) dt$$

limits of integration chosen to coincide with positive portion of applied voltage waveform

12.2.3. Leakage inductances

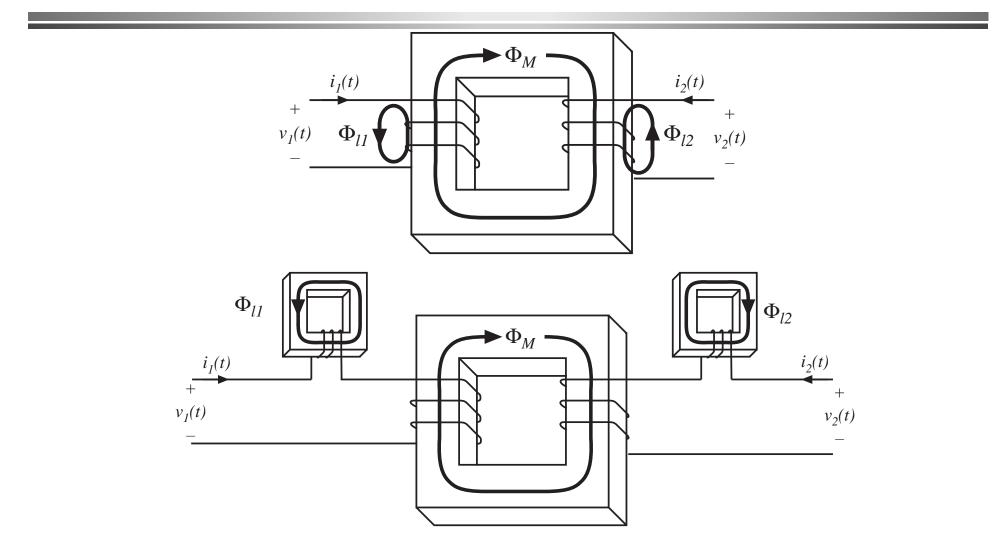

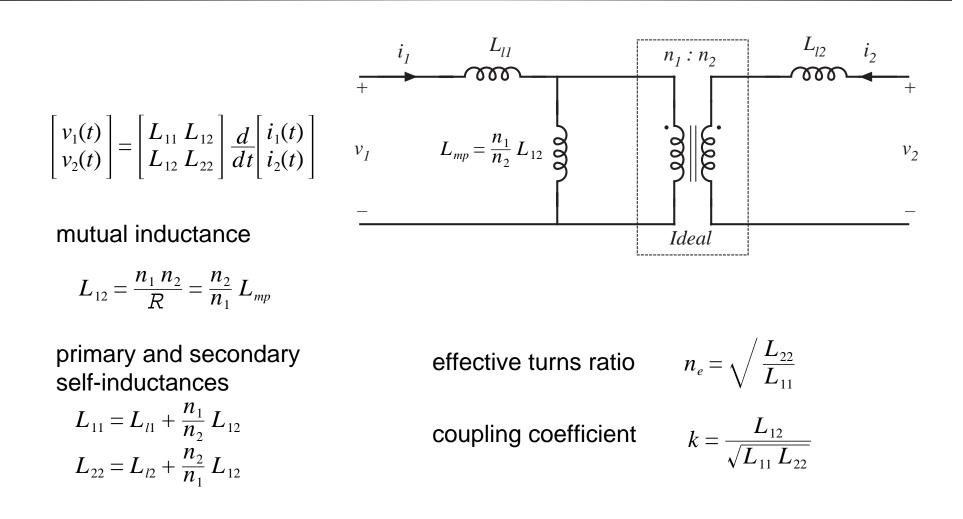Transformer model, including leakage inductance



Fundamentals of Power Electronics

12.3. Loss mechanisms in magnetic devices

Low-frequency losses:

Dc copper loss

Core loss: hysteresis loss

High-frequency losses: the skin effect

Core loss: classical eddy current losses

Eddy current losses in ferrite cores

High frequency copper loss: the proximity effect

Proximity effect: high frequency limit


MMF diagrams, losses in a layer, and losses in basic multilayer windings

Effect of PWM waveform harmonics

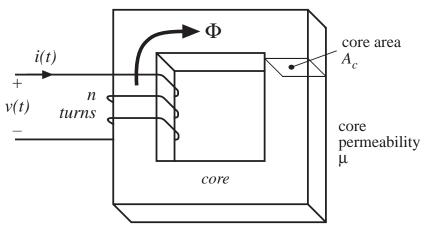12.3.1. Core loss

Energy per cycle *W* flowing into *n*turn winding of an inductor, excited by periodic waveforms of frequency *f*:

$$W = \int_{\text{one cycle}} v(t)i(t)dt$$



Relate winding voltage and current to core B and H via Faraday's law and Ampere's law:


$$v(t) = n A_c \frac{dB(t)}{dt} \qquad \qquad H(t) l_m = n i(t)$$

Substitute into integral:

$$W = \int_{\text{one cycle}} \left(nA_c \frac{dB(t)}{dt} \right) \left(\frac{H(t)l_m}{n} \right) dt$$
$$= \left(A_c l_m \right) \int_{\text{one cycle}} H dB$$

Fundamentals of Power Electronics

Core loss: Hysteresis loss

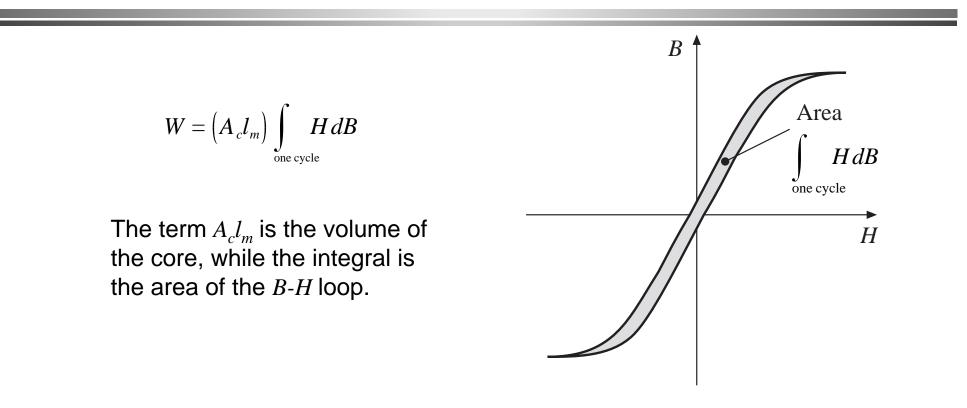

(energy lost per cycle) = (core volume) (area of *B*-*H* loop)

$$P_{H} = (f)(A_{c}l_{m})\int_{\text{one cycle}} H dB$$

Hysteresis loss is directly proportional to applied frequency

Modeling hysteresis loss

- Hysteresis loss varies directly with applied frequency
- Dependence on maximum flux density: how does area of *B-H* loop depend on maximum flux density (and on applied waveforms)?
 Emperical equation (Steinmetz equation):


 $P_{H} = K_{H} f B^{\alpha}_{\max}(core \ volume)$

The parameters K_H and α are determined experimentally.

Dependence of P_H on B_{max} is predicted by the theory of magnetic domains.

Core loss: eddy current loss

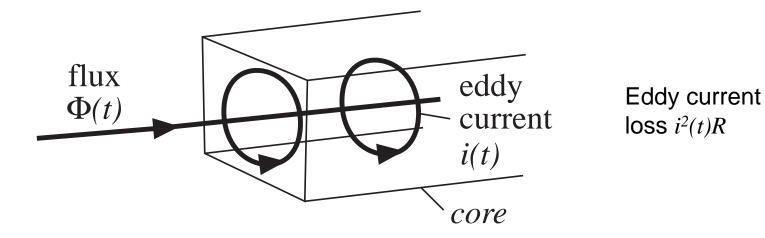Magnetic core materials are reasonably good conductors of electric current. Hence, according to Lenz's law, magnetic fields within the core induce currents ("eddy currents") to flow within the core. The eddy currents flow such that they tend to generate a flux which opposes changes in the core flux $\Phi(t)$. The eddy currents tend to prevent flux from penetrating the core.




Modeling eddy current loss

- Ac flux $\Phi(t)$ induces voltage v(t) in core, according to Faraday's law. Induced voltage is proportional to derivative of $\Phi(t)$. In consequence, magnitude of induced voltage is directly proportional to excitation frequency *f*.
- If core material impedance Z is purely resistive and independent of frequency, Z = R, then eddy current magnitude is proportional to voltage: i(t) = v(t)/R. Hence magnitude of i(t) is directly proportional to excitation frequency f.
- Eddy current power loss *i*²(*t*)*R* then varies with square of excitation frequency *f*.
- Classical Steinmetz equation for eddy current loss:

 $P_E = K_E f^2 B_{\text{max}}^2$ (core volume)

• Ferrite core material impedance is capacitive. This causes eddy current power loss to increase as f^4 .

Total core loss: manufacturer's data

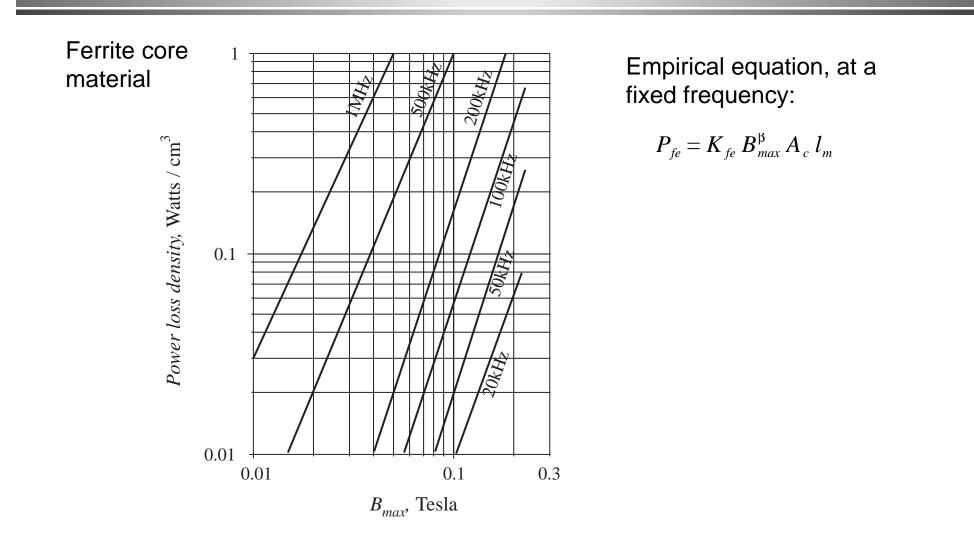

Fundamentals of Power Electronics

Core materials

Core type	B_{sat}	Relative core loss	Applications
Laminations iron, silicon steel	1.5 - 2.0 T	high	50-60 Hz transformers, inductors
Powdered cores powdered iron, molypermalloy	0.6 - 0.8 T	medium	1 kHz transformers, 100 kHz filter inductors
Ferrite Manganese-zinc, Nickel-zinc	0.25 - 0.5 T	low	20 kHz - 1 MHz transformers, ac inductors

12.3.2. Low-frequency copper loss


DC resistance of wire

$$R = \rho \, \frac{l_b}{A_w}$$


where A_w is the wire bare cross-sectional area, and l_b is the length of the wire. The resistivity ρ is equal to $1.724 \cdot 10^{-6} \Omega$ cm for soft-annealed copper at room temperature. This resistivity increases to $2.3 \cdot 10^{-6} \Omega$ cm at 100° C.

The wire resistance leads to a power loss of

$$P_{cu} = I_{rms}^2 R$$

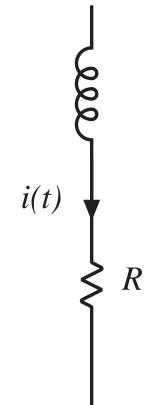


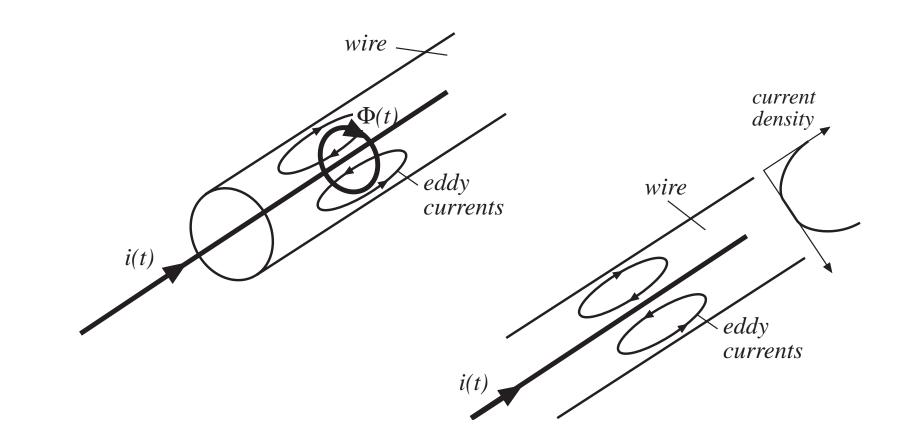12.4. Eddy currents in winding conductors12.4.1. The skin effect



Penetration depth δ

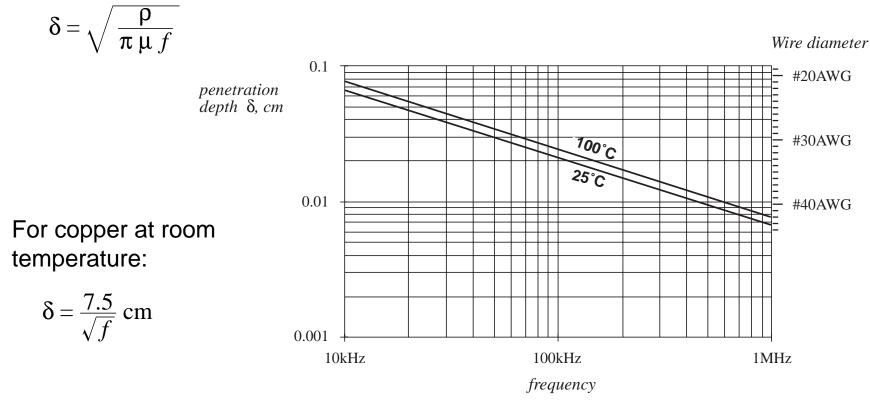For sinusoidal currents: current density is an exponentially decaying function of distance into the conductor, with characteristic length δ known as the *penetration depth* or *skin depth*.




Fundamentals of Power Electronics

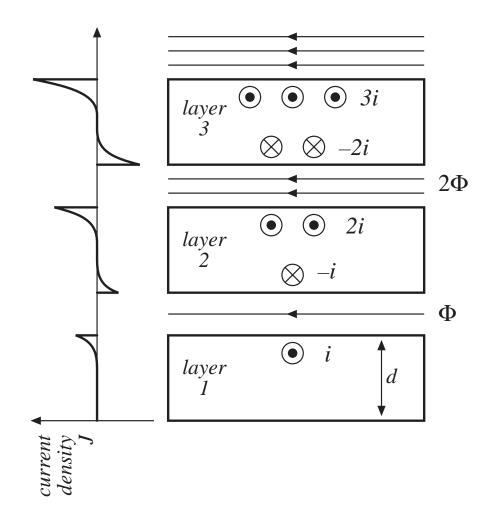12.4.2. The proximity effect

Ac current in a conductor induces eddy currents in adjacent conductors by a process called the *proximity effect*. This causes significant power loss in the windings of high-frequency transformers and ac inductors.

A multi-layer foil winding, with $d \gg \delta$. Each layer carries net current i(t).



Estimating proximity loss: high-frequency limit

Let P_1 be power loss in layer 1:

$$P_1 = I_{rms}^2 \left(R_{dc} \frac{d}{\delta} \right)$$

Power loss P_2 in layer 2 is:

$$P_{2} = I_{rms}^{2} \left(R_{dc} \frac{d}{\delta} \right) + \left(2I_{rms} \right)^{2} \left(R_{dc} \frac{d}{\delta} \right)$$
$$= 5P_{1}$$

Power loss P_3 in layer 3 is: $P_3 = \left(2I_{rms}\right)^2 \left(R_{dc} \frac{d}{\delta}\right) + \left(3I_{rms}\right)^2 \left(R_{dc} \frac{d}{\delta}\right)$ $= 13P_1$

 $\int_{\sigma}^{2} \left(R_{dc} \frac{d}{\delta} \right)$ $\int_{\sigma}^{1} \frac{1}{1}$ $\int_{\sigma}^{1} \frac{1}{1}$

 $ayer \quad \textcircled{\bullet}_{3}$

layer

• *3i*

-2i

2i

d

2Φ

Φ

 \bigcirc

-i

 (\bullet)

Power loss P_m in layer m is:

$$P_m = ((m-1)^2 + m^2) P_1$$

Total loss in *M*-layer winding: high-frequency limit

Add up losses in each layer:

$$P_{w}\Big|_{d \gg \delta} = \sum_{j=1}^{M} P_{j} = \frac{M}{3} \left(2M^{2} + 1 \right) P_{1}$$

Compare with dc copper loss:

If foil thickness were $d = \delta$, then at dc each layer would produce copper loss P_1 . The copper loss of the *M*-layer winding would be

$$P_{w,dc}\Big|_{d=\delta} = M P_1$$

For foil thicknesses other than $d = \delta$, the dc resistance and power loss are changed by a factor of d/δ . The total winding dc copper loss is


$$P_{w,dc} = M P_1 \frac{\delta}{d}$$

So the proximity effect increases the copper loss by a factor of

$$F_{R}\Big|_{d \gg \delta} = \frac{P_{w}\Big|_{d \gg \delta}}{P_{w,dc}} = \frac{1}{3} \frac{d}{\delta} \left(2M^{2} + 1\right)$$

Fundamentals of Power Electronics

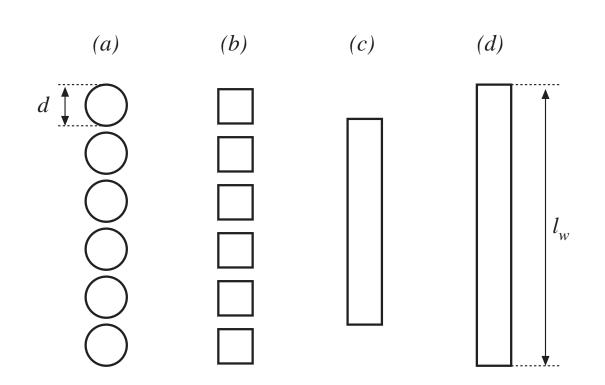Approximating a layer of round conductors as an effective foil conductor



Conductor spacing factor:


$$\eta = \sqrt{\frac{\pi}{4}} d \frac{n_l}{l_w}$$

Effective ratio of conductor thickness to skin depth:


$$\phi = \sqrt{\eta} \ \frac{d}{\delta}$$

12.4.3. Magnetic fields in the vicinity of winding conductors: MMF diagrams

Two-winding transformer example

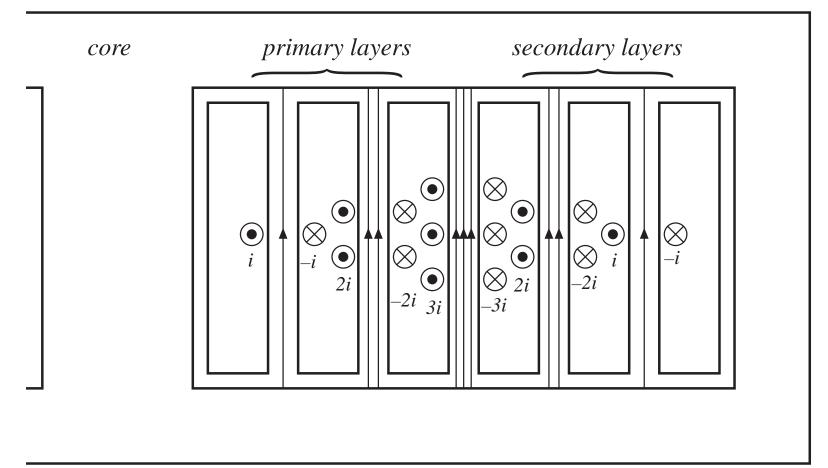


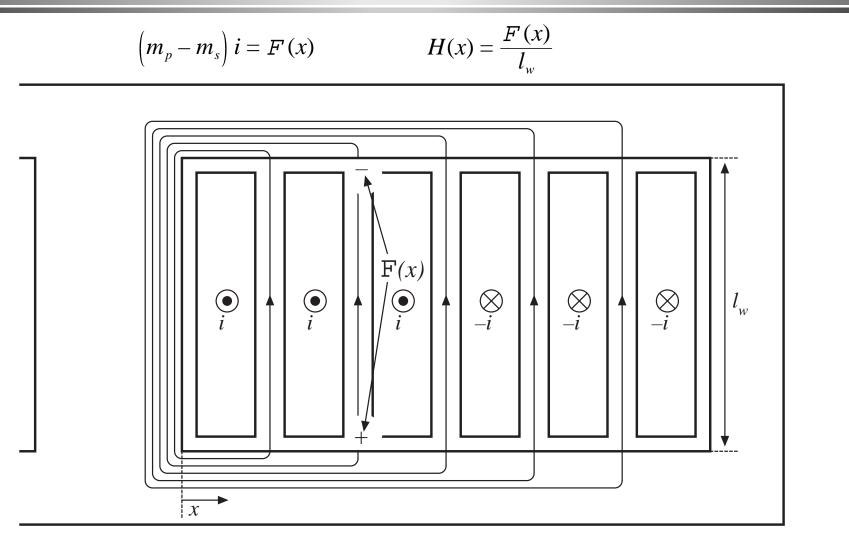Transformer example: magnetic field lines




Fundamentals of Power Electronics

Ampere's law and MMF diagram

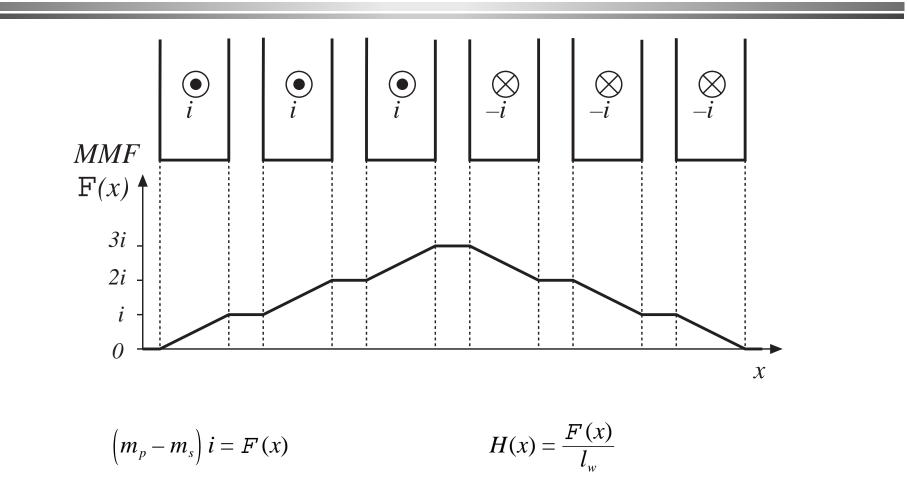


Fundamentals of Power Electronics


MMF diagram for $d >> \delta$

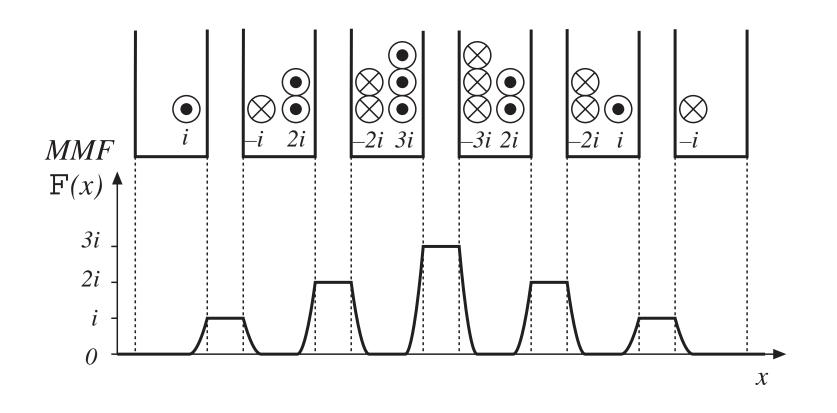

Interleaved windings

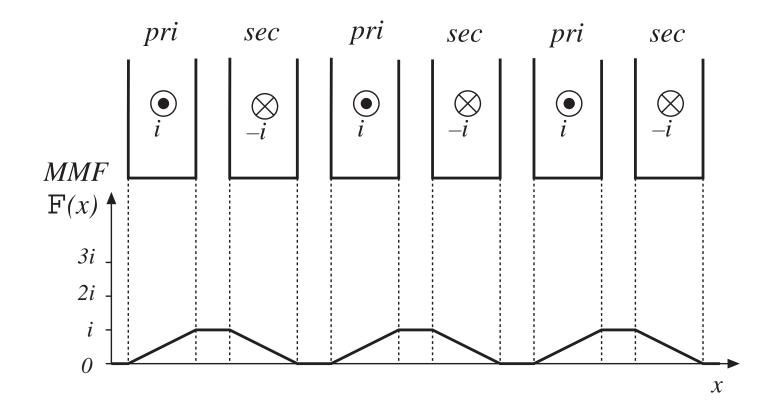

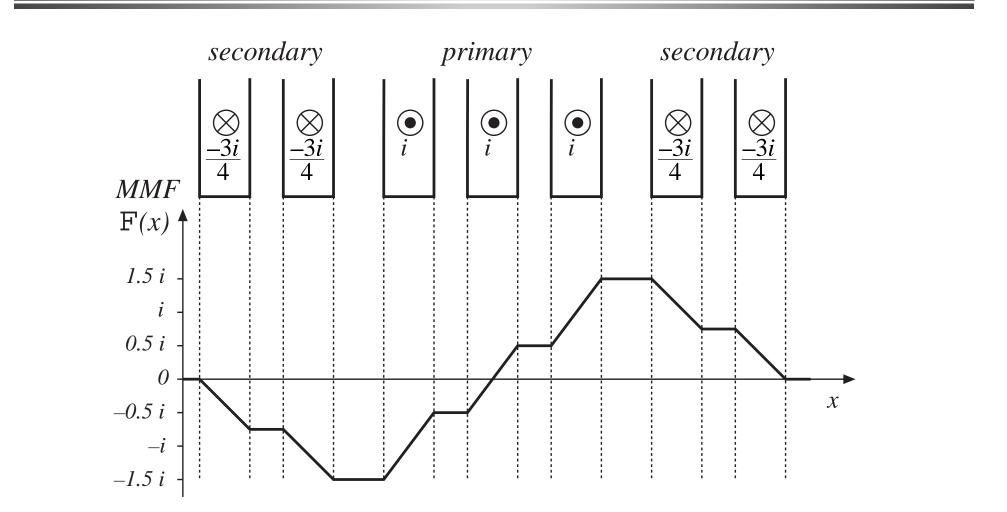Partially-interleaved windings: fractional layers




12.4.4. Power loss in a layer

Approximate computation of copper loss in one layer

Assume uniform magnetic fields at surfaces of layer, of strengths H(0) and H(d). Assume that these fields are parallel to layer surface (i.e., neglect fringing and assume field normal component is zero).

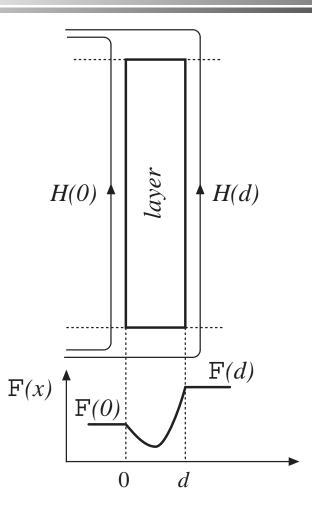The magnetic fields H(0) and H(d) are driven by the MMFs F(0) and F(d). Sinusoidal waveforms are assumed, and rms values are used. It is assumed that H(0) and H(d) are in phase.



Solution for layer copper loss *P*

Solve Maxwell's equations to find current density distribution within layer. Then integrate to find total copper loss *P* in layer. Result is

$$P = R_{dc} \frac{\Phi}{n_l^2} \left[\left(F^2(d) + F^2(0) \right) G_1(\phi) - 4 F(d)F(0) G_2(\phi) \right]$$

where

$$R_{dc} = \rho \; \frac{(MLT) \; n_l^2}{l_w \, \eta \; d}$$

$$G_1(\varphi) = \frac{\sinh(2\varphi) + \sin(2\varphi)}{\cosh(2\varphi) - \cos(2\varphi)}$$

 n_l = number of turns in layer, R_{dc} = dc resistance of layer,

(MLT) = mean-length-per-turn, or circumference, of layer.

$$G_{2}(\varphi) = \frac{\sinh(\varphi)\cos(\varphi) + \cosh(\varphi)\sin(\varphi)}{\cosh(2\varphi) - \cos(2\varphi)}$$
$$\varphi = \sqrt{\eta} \frac{d}{\delta} \qquad \eta = \sqrt{\frac{\pi}{4}} d\frac{n_{l}}{l_{w}}$$

Winding carrying current I, with n_l turns per layer

If winding carries current of rms magnitude *I*, then

 $F(d) - F(0) = n_l I$

Express F(d) in terms of the winding current *I*, as


$$\mathbf{F}(d) = m n_l I$$

The quantity *m* is the ratio of the MMF F(d) to the layer ampere-turns $n_l I$. Then,

$$\frac{\mathrm{F}(0)}{\mathrm{F}(d)} = \frac{m-1}{m}$$


Power dissipated in the layer can now be written
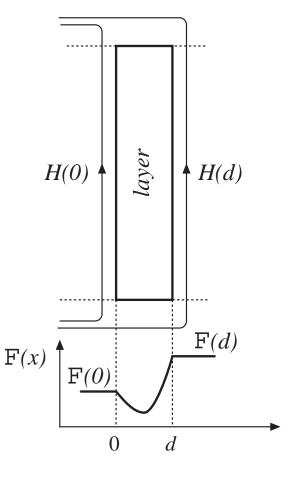
$$P = I^2 R_{dc} \varphi Q'(\varphi, m)$$
$$Q'(\varphi, m) = \left(2m^2 - 2m + 1\right) G_1(\varphi) - 4m \left(m - 1\right) G_2(\varphi)$$




Fundamentals of Power Electronics

Increased copper loss in layer

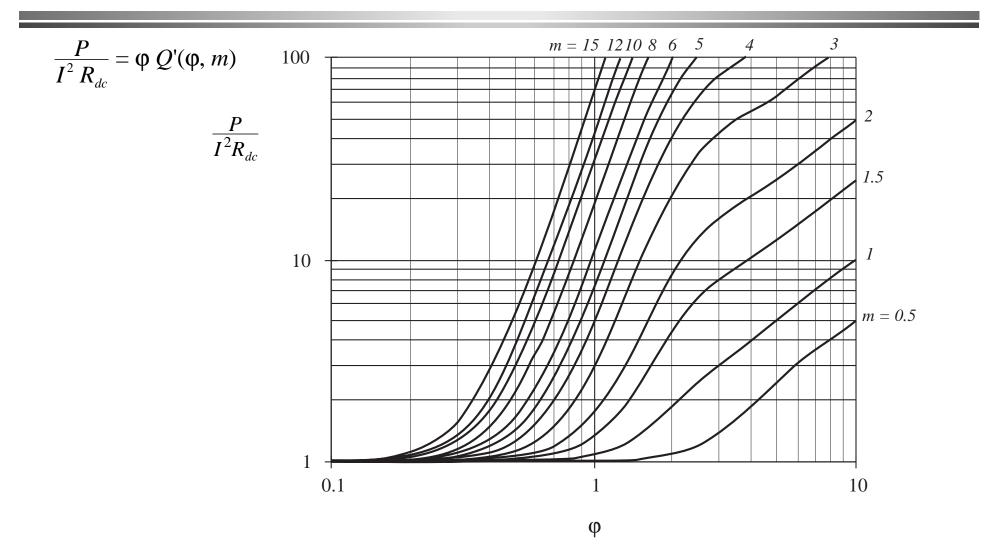


Fundamentals of Power Electronics

Layer copper loss vs. layer thickness

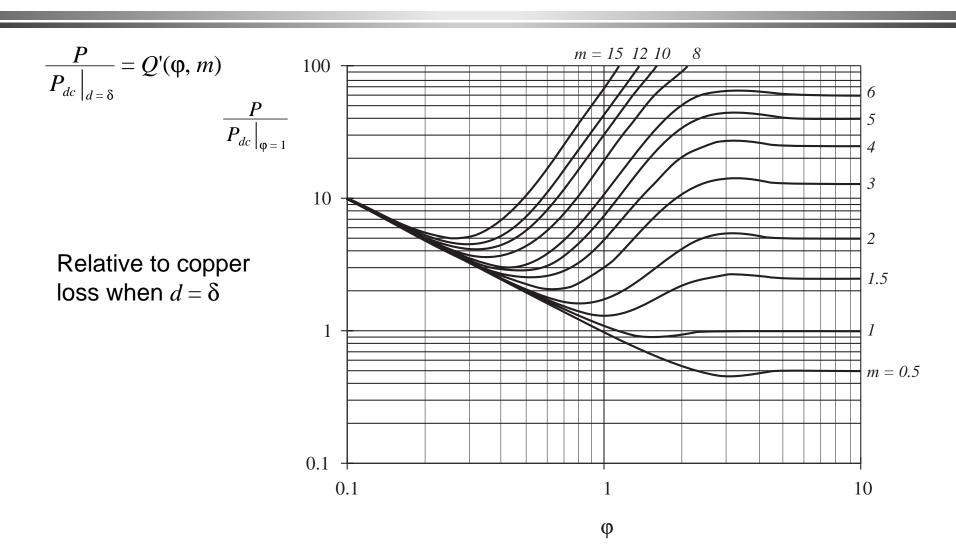


Fundamentals of Power Electronics

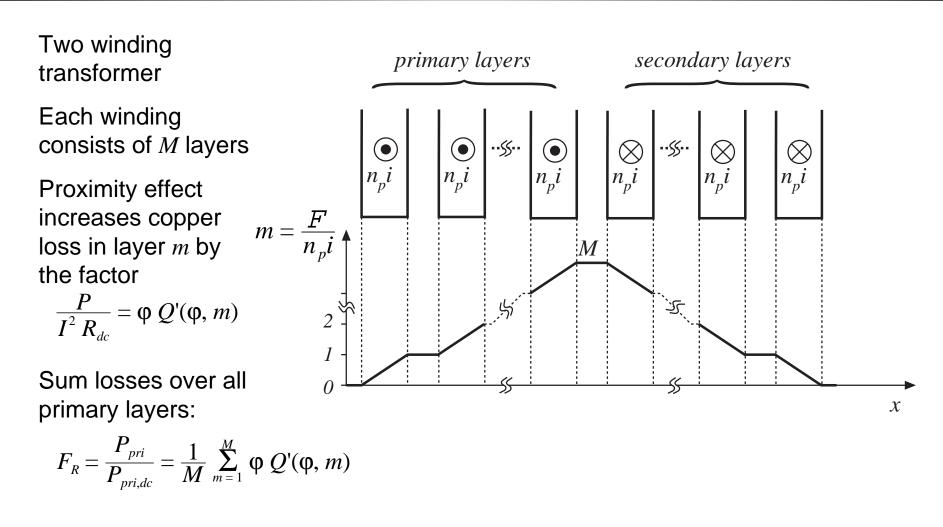12.4.5. Example: Power loss in a transformer winding




Increased total winding loss

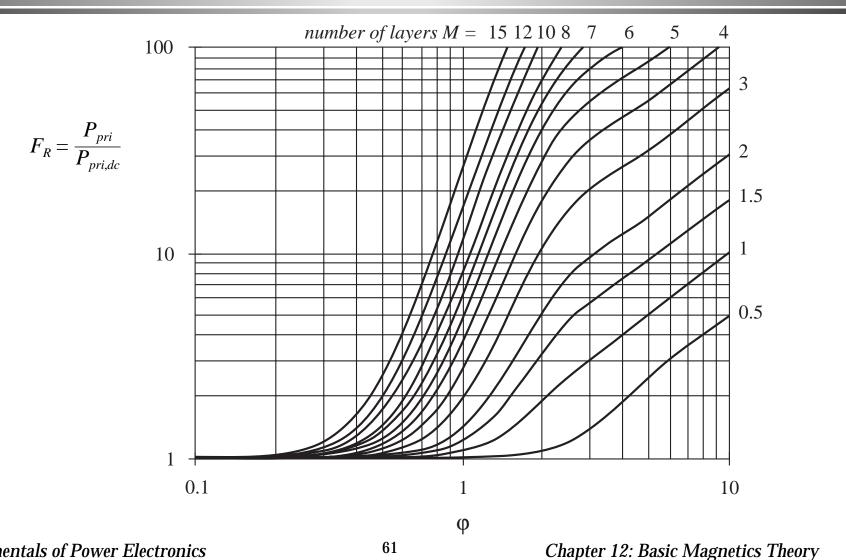 $F_{R} = \varphi \left[G_{1}(\varphi) + \frac{2}{3} \left(M^{2} - 1 \right) \left(G_{1}(\varphi) - 2G_{2}(\varphi) \right) \right]$ Express summation in closed form:




Total winding loss

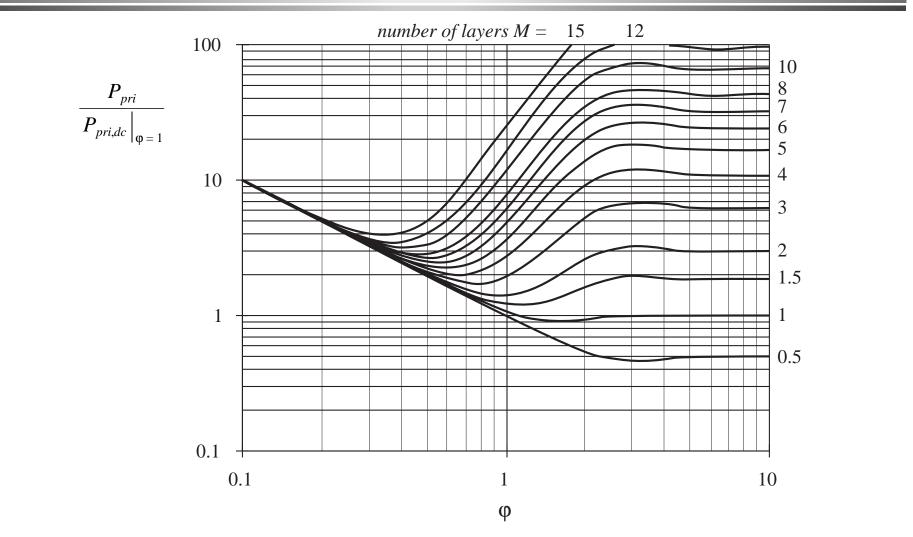

Fundamentals of Power Electronics

12.4.6. PWM waveform harmonics

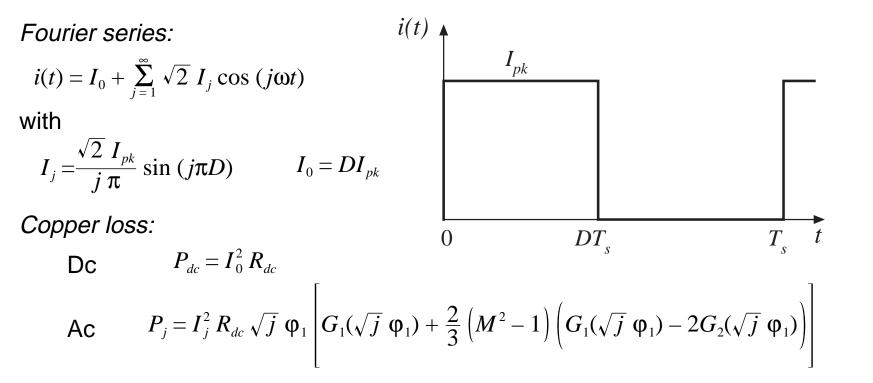

Total, relative to value predicted by low-frequency analysis:

$$\frac{P_{cu}}{D I_{pk}^2 R_{dc}} = D + \frac{2\varphi_1}{D\pi^2} \sum_{j=1}^{\infty} \frac{\sin^2 (j\pi D)}{j \sqrt{j}} \left[G_1(\sqrt{j} \varphi_1) + \frac{2}{3} \left(M^2 - 1 \right) \left(G_1(\sqrt{j} \varphi_1) - 2G_2(\sqrt{j} \varphi_1) \right) \right]$$

Fundamentals of Power Electronics

Harmonic loss factor F_H


Effect of harmonics: F_H = ratio of total ac copper loss to fundamental copper loss

$$F_H = \frac{\sum_{j=1}^{\infty} P_j}{P_1}$$

The total winding copper loss can then be written

$$P_{cu} = I_0^2 R_{dc} + F_H F_R I_1^2 R_{dc}$$

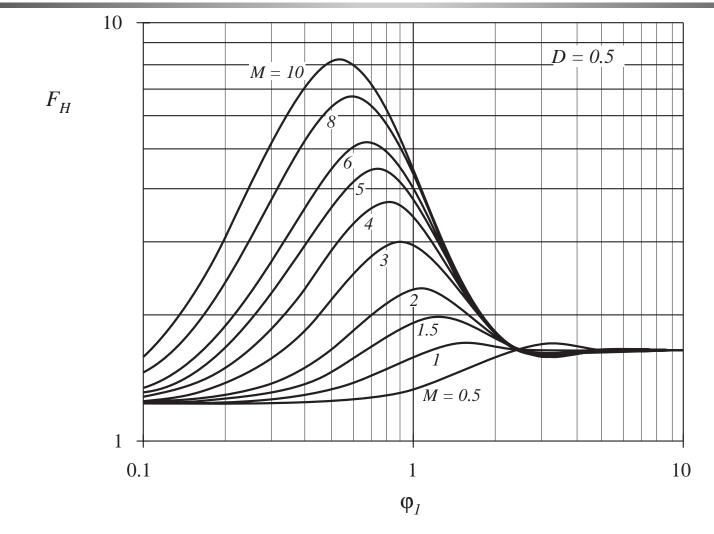
Increased proximity losses induced by PWM waveform harmonics: D = 0.5



Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory

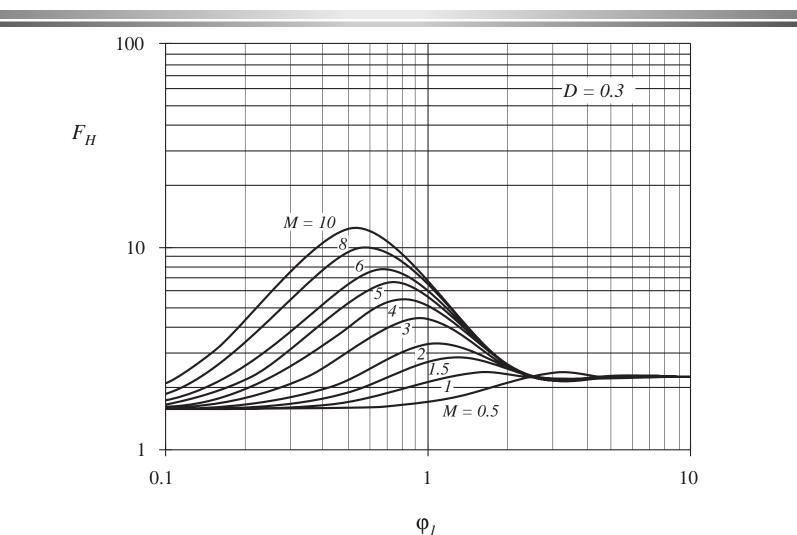
Increased proximity losses induced by PWM waveform harmonics: D = 0.3



Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory

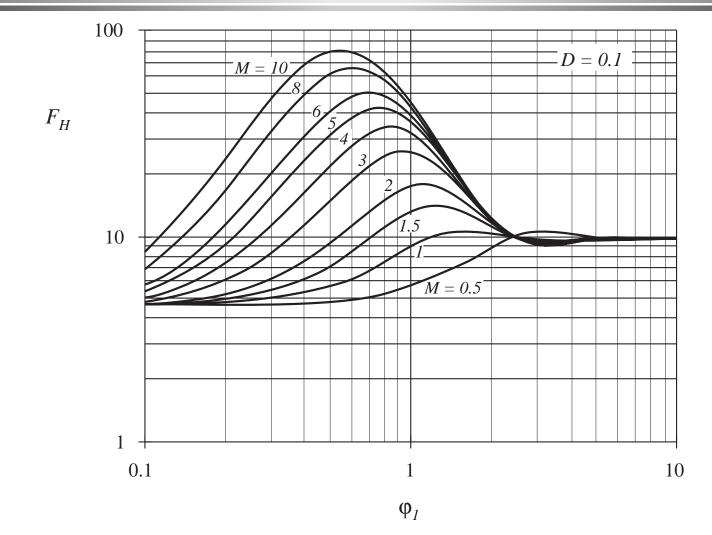Increased proximity losses induced by PWM waveform harmonics: D = 0.1



Fundamentals of Power Electronics

Chapter 12: Basic Magnetics Theory

- 1. Magnetic devices can be modeled using lumped-element magnetic circuits, in a manner similar to that commonly used to model electrical circuits. The magnetic analogs of electrical voltage *V*, current *I*, and resistance *R*, are magnetomotive force (MMF) F, flux Φ , and reluctance R respectively.
- 2. Faraday's law relates the voltage induced in a loop of wire to the derivative of flux passing through the interior of the loop.
- 3. Ampere's law relates the total MMF around a loop to the total current passing through the center of the loop. Ampere's law implies that winding currents are sources of MMF, and that when these sources are included, then the net MMF around a closed path is equal to zero.
- 4. Magnetic core materials exhibit hysteresis and saturation. A core material saturates when the flux density *B* reaches the saturation flux density B_{sat} .

Summary of key points

- 5. Air gaps are employed in inductors to prevent saturation when a given maximum current flows in the winding, and to stabilize the value of inductance. The inductor with air gap can be analyzed using a simple magnetic equivalent circuit, containing core and air gap reluctances and a source representing the winding MMF.
- 6. Conventional transformers can be modeled using sources representing the MMFs of each winding, and the core MMF. The core reluctance approaches zero in an ideal transformer. Nonzero core reluctance leads to an electrical transformer model containing a magnetizing inductance, effectively in parallel with the ideal transformer. Flux that does not link both windings, or "leakage flux," can be modeled using series inductors.
- 7. The conventional transformer saturates when the applied winding voltseconds are too large. Addition of an air gap has no effect on saturation. Saturation can be prevented by increasing the core cross-sectional area, or by increasing the number of primary turns.

Summary of key points

- 8. Magnetic materials exhibit core loss, due to hysteresis of the *B*-*H* loop and to induced eddy currents flowing in the core material. In available core materials, there is a tradeoff between high saturation flux density B_{sat} and high core loss P_{fe} . Laminated iron alloy cores exhibit the highest B_{sat} but also the highest P_{fe} , while ferrite cores exhibit the lowest P_{fe} but also the lowest B_{sat} . Between these two extremes are powdered iron alloy and amorphous alloy materials.
- 9. The skin and proximity effects lead to eddy currents in winding conductors, which increase the copper loss P_{cu} in high-current high-frequency magnetic devices. When a conductor has thickness approaching or larger than the penetration depth δ , magnetic fields in the vicinity of the conductor induce eddy currents in the conductor. According to Lenz's law, these eddy currents flow in paths that tend to oppose the applied magnetic fields.

Summary of key points

- 10. The magnetic field strengths in the vicinity of the winding conductors can be determined by use of MMF diagrams. These diagrams are constructed by application of Ampere's law, following the closed paths of the magnetic field lines which pass near the winding conductors. Multiple-layer noninterleaved windings can exhibit high maximum MMFs, with resulting high eddy currents and high copper loss.
- 11. An expression for the copper loss in a layer, as a function of the magnetic field strengths or MMFs surrounding the layer, is given in Section 12.4.4. This expression can be used in conjunction with the MMF diagram, to compute the copper loss in each layer of a winding. The results can then be summed, yielding the total winding copper loss. When the effective layer thickness is near to or greater than one skin depth, the copper losses of multiple-layer noninterleaved windings are greatly increased.

12. Pulse-width-modulated winding currents of contain significant total harmonic distortion, which can lead to a further increase of copper loss. The increase in proximity loss caused by current harmonics is most pronounced in multiple-layer non-interleaved windings, with an effective layer thickness near one skin depth.

- 13.1. Several types of magnetic devices, their *B*-*H* loops, and core vs. copper loss
- 13.2. Filter inductor design constraints
- 13.3. The core geometrical constant K_g
- 13.4. A step-by-step design procedure
- 13.5. Summary of key points

13.1. Several types of magnetic devices, their *B*-*H* loops, and core vs. copper loss

A key design decision: the choice of maximum operating flux density B_{max}


- Choose B_{max} to avoid saturation of core, or
- Further reduce B_{max} , to reduce core losses

Different design procedures are employed in the two cases.

Types of magnetic devices:

Filter inductor	Ac inductor
Conventional transformer	Coupled inductor
Flyback transformer	SEPIC transformer
Magnetic amplifier	Saturable reactor

Filter inductor

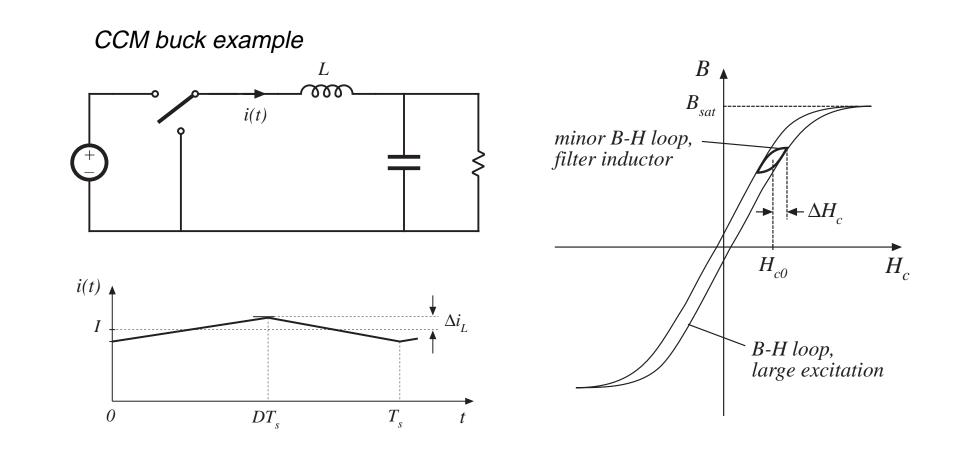


Fundamentals of Power Electronics


Chapter 13: Filter inductor design

Filter inductor, cont.

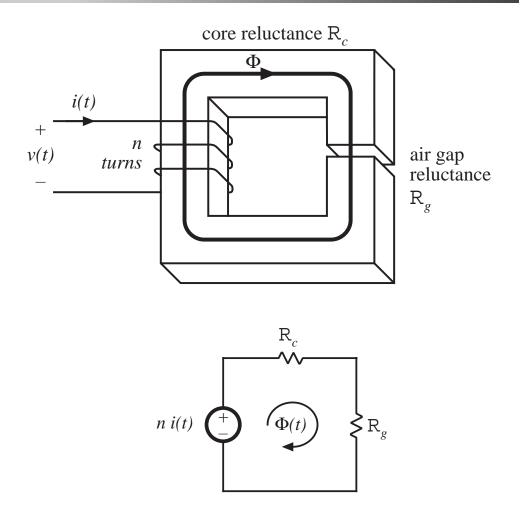- Negligible core loss, negligible proximity loss
- Loss dominated by dc copper loss
- Flux density chosen simply to avoid saturation
- Air gap is employed
- Could use core materials having high saturation flux density (and relatively high core loss), even though converter switching frequency is high




Ac inductor

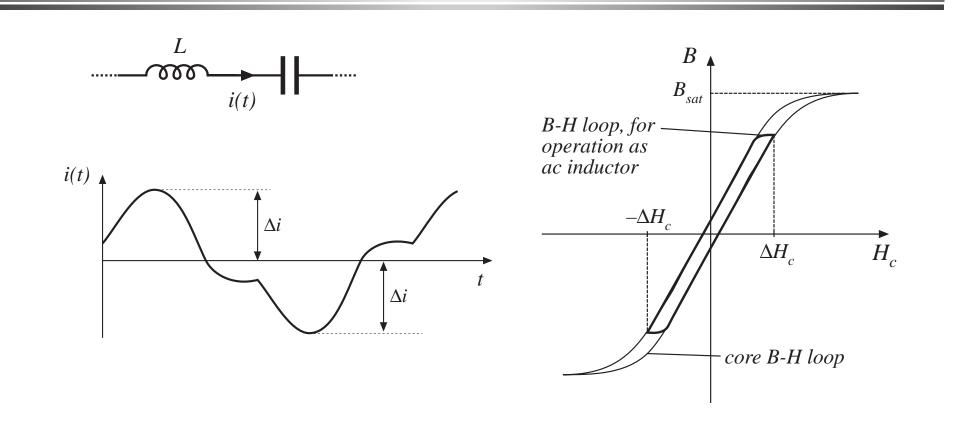

Ac inductor, cont.

- Core loss, copper loss, proximity loss are all significant
- An air gap is employed
- Flux density is chosen to reduce core loss
- A high-frequency material (ferrite) must be employed

Conventional transformer

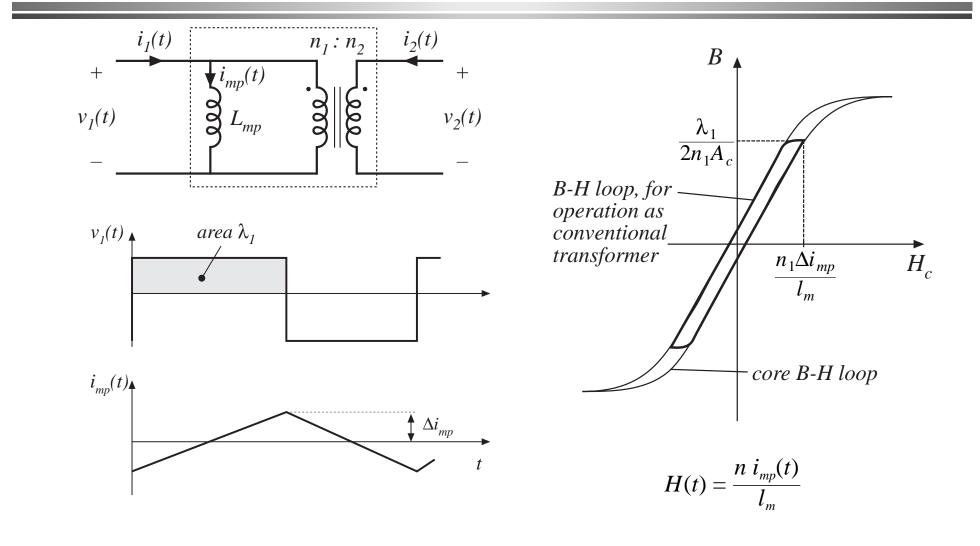


Fundamentals of Power Electronics

Chapter 13: Filter inductor design

Conventional transformer, cont.

- Core loss, copper loss, and proximity loss are usually significant
- No air gap is employed
- Flux density is chosen to reduce core loss
- A high frequency material (ferrite) must be employed

Coupled inductor

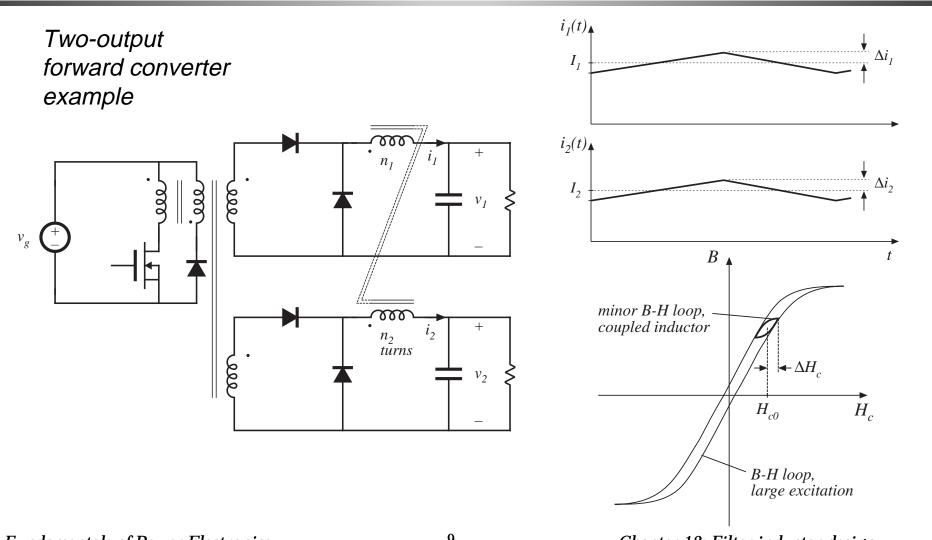


Fundamentals of Power Electronics

Chapter 13: Filter inductor design

Coupled inductor, cont.

- A filter inductor having multiple windings
- Air gap is employed
- Core loss and proximity loss usually not significant
- Flux density chosen to avoid saturation
- Low-frequency core material can be employed

DCM Flyback transformer

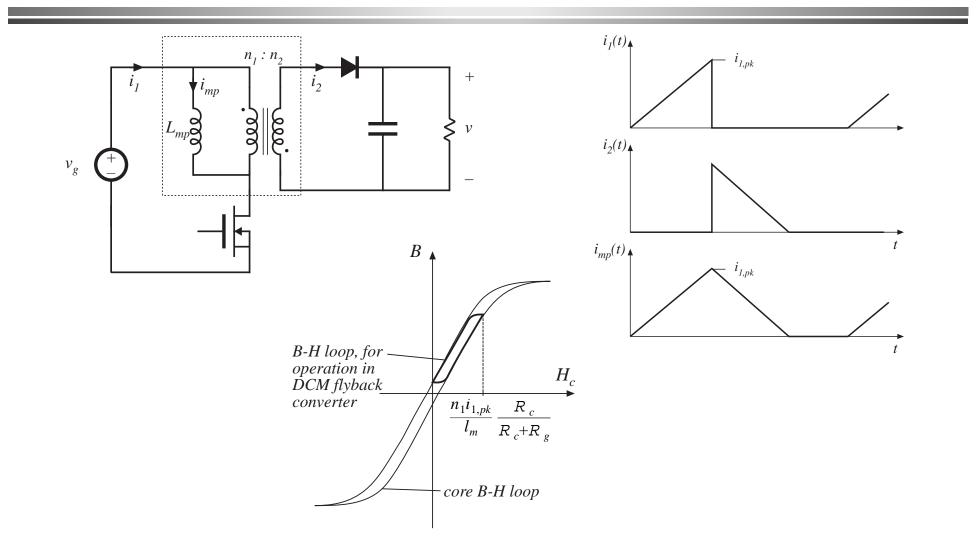

Fundamentals of Power Electronics

Chapter 13: Filter inductor design

DCM flyback transformer, cont.

- Core loss, copper loss, proximity loss are significant
- Flux density is chosen to reduce core loss
- Air gap is employed
- A high-frequency core material (ferrite) must be used

13.2. Filter inductor design constraints

Objective:


Design inductor having a given inductance *L*,

which carries worst-case current I_{max} without saturating,

and which has a given winding resistance R, or, equivalently, exhibits a worst-case copper loss of

$$P_{cu} = I_{rms}^{2} R$$

13

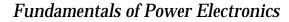


000

R

i(t)



Assumed filter inductor geometry

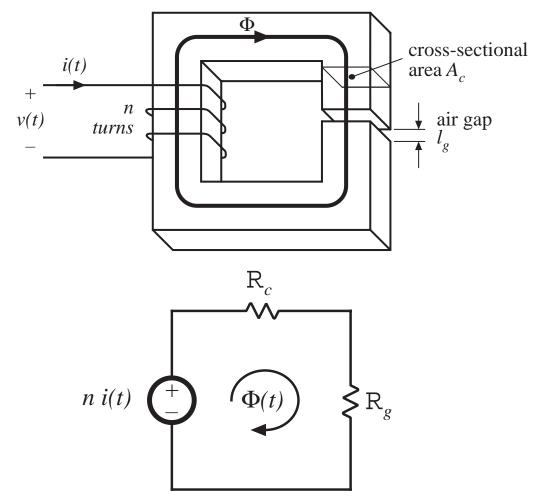

$$R_{c} = \frac{l_{c}}{\mu_{c} A_{c}}$$
$$R_{g} = \frac{l_{g}}{\mu_{0} A_{c}}$$

Solve magnetic circuit:

$$ni = \Phi\left(R_{c} + R_{g}\right)$$

For
$$\mathbb{R}_{c} \gg \mathbb{R}_{g}$$
: $ni \approx \Phi \mathbb{R}_{g}$

Chapter 13: Filter inductor design

Given a peak winding current I_{max} , it is desired to operate the core flux density at a peak value B_{max} . The value of B_{max} is chosen to be less than the worst-case saturation flux density of the core material.

From solution of magnetic circuit:

$$ni = BA_c R_g$$

Let $I = I_{max}$ and $B = B_{max}$:

$$nI_{max} = B_{max}A_c \mathbb{R}_g = B_{max}\frac{l_g}{\mu_0}$$

This is constraint #1. The turns ratio n and air gap length l_g are unknown.

13.3.2. Constraint: Inductance


Must obtain specified inductance *L*. We know that the inductance is

$$L = \frac{n^2}{R_g} = \frac{\mu_0 A_c n^2}{l_g}$$

This is constraint #2. The turns ratio n, core area A_c , and air gap length l_g are unknown.

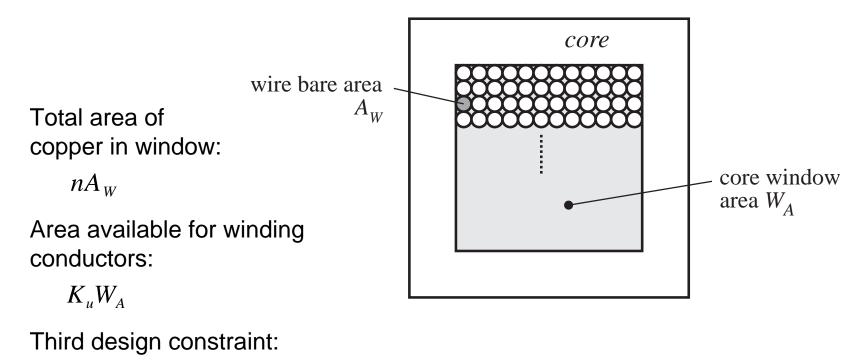13.3.3. Constraint: Winding area

Wire must fit through core window (i.e., hole in center of core)



$$K_u W_A \ge nA_W$$

The window utilization factor K_u also called the "fill factor"

 K_u is the fraction of the core window area that is filled by copper Mechanisms that cause K_u to be less than 1:

- Round wire does not pack perfectly, which reduces K_u by a factor of 0.7 to 0.55 depending on winding technique
- Insulation reduces K_u by a factor of 0.95 to 0.65, depending on wire size and type of insulation
- Bobbin uses some window area
- Additional insulation may be required between windings

Typical values of K_u :

0.5 for simple low-voltage inductor

0.25 to 0.3 for off-line transformer

0.05 to 0.2 for high-voltage transformer (multiple kV)

0.65 for low-voltage foil-winding inductor

13.2.4 Winding resistance

The resistance of the winding is

$$R = \rho \, \frac{l_b}{A_W}$$

where ρ is the resistivity of the conductor material, l_b is the length of the wire, and A_W is the wire bare area. The resistivity of copper at room temperature is $1.724 \cdot 10^{-6} \Omega$ -cm. The length of the wire comprising an *n*-turn winding can be expressed as

$$l_b = n (MLT)$$

where (MLT) is the mean-length-per-turn of the winding. The meanlength-per-turn is a function of the core geometry. The above equations can be combined to obtain the fourth constraint:

$$R = \rho \, \frac{n \, (MLT)}{A_W}$$

Fundamentals of Power Electronics

13.3 The core geometrical constant K_g

2

The four constraints:

$$nI_{max} = B_{max} \frac{l_g}{\mu_0} \qquad \qquad L = \frac{\mu_0 A_c n^2}{l_g}$$
$$K_u W_A \ge nA_W \qquad \qquad R = \rho \frac{n (MLT)}{A_W}$$

These equations involve the quantities

 A_c , W_A , and *MLT*, which are functions of the core geometry,

 I_{max} , B_{max} , μ_0 , L, K_u , R, and ρ , which are given specifications or other known quantities, and

n, l_g , and A_W , which are unknowns.

Eliminate the three unknowns, leading to a single equation involving the remaining quantities.

Core geometrical constant K_g

Elimination of n, l_g , and A_W leads to

$$\frac{A_c^2 W_A}{(MLT)} \ge \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u}$$

- Right-hand side: specifications or other known quantities
- Left-hand side: function of only core geometry

So we must choose a core whose geometry satisfies the above equation.

The core geometrical constant K_g is defined as

$$K_g = \frac{A_c^2 W_A}{(MLT)}$$

Discussion

$$K_g = \frac{A_c^2 W_A}{(MLT)} \ge \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u}$$

 K_g is a figure-of-merit that describes the effective electrical size of magnetic cores, in applications where the following quantities are specified:

- Copper loss
- Maximum flux density

How specifications affect the core size:

A smaller core can be used by increasing

 $B_{max} \Rightarrow$ use core material having higher B_{sat}

 $R \Rightarrow$ allow more copper loss

How the core geometry affects electrical capabilities:

A larger K_g can be obtained by increase of

 $A_c \Rightarrow$ more iron core material, or

 $W_A \Rightarrow$ larger window and more copper

Fundamentals of Power Electronics

Chapter 13: Filter inductor design

13.4 A step-by-step procedure

The following quantities are specified, using the units noted:

Wire resistivity	ρ	$(\Omega$ -cm)
Peak winding current	I _{max}	(A)
Inductance	L	(H)
Winding resistance	R	(Ω)
Winding fill factor	K_{u}	
Core maximum flux density	B_{max}	(T)

The core dimensions are expressed in cm:

Core cross-sectional area	A_{c}	(cm^2)
Core window area	W_A	(cm^2)
Mean length per turn	MLT	(cm)

The use of centimeters rather than meters requires that appropriate factors be added to the design equations.

Determine core size

$$K_g \ge \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u} 10^8 \qquad (\text{cm}^5)$$

Choose a core which is large enough to satisfy this inequality (see Appendix 2 for magnetics design tables).

Note the values of A_c , W_A , and *MLT* for this core.

Determine air gap length

$$l_{g} = \frac{\mu_{0} L I_{max}^{2}}{B_{max}^{2} A_{c}} 10^{4} \qquad (m)$$

with A_c expressed in cm². $\mu_0 = 4\pi 10^{-7}$ H/m.

The air gap length is given in meters.

The value expressed above is approximate, and neglects fringing flux and other nonidealities.

A_L

Core manufacturers sell gapped cores. Rather than specifying the air gap length, the equivalent quantity A_L is used.

- A_L is equal to the inductance, in mH, obtained with a winding of 1000 turns.
- When A_L is specified, it is the core manufacturer's responsibility to obtain the correct gap length.

The required A_L is given by:

$$A_{L} = \frac{10B_{max}^{2}A_{c}^{2}}{LI_{max}^{2}} \qquad (\text{mH/1000 turns}) \qquad \begin{array}{l} \text{Units:} \\ A_{c} & \text{cm}^{2}, \\ L & \text{Henries,} \\ B_{max} & \text{Tesla.} \end{array}$$

 $L = A_L n^2 10^{-9}$ (Henries)

Fundamentals of Power Electronics

Determine number of turns *n*

$$n = \frac{LI_{max}}{B_{max}A_c} \quad 10^4$$

Evaluate wire size

$$A_W \le \frac{K_u W_A}{n} \quad (\mathrm{cm}^2)$$

Select wire with bare copper area A_W less than or equal to this value. An American Wire Gauge table is included in Appendix 2.

As a check, the winding resistance can be computed:


$$R = \frac{\rho n \, (MLT)}{A_w} \qquad (\Omega)$$

- 1. A variety of magnetic devices are commonly used in switching converters. These devices differ in their core flux density variations, as well as in the magnitudes of the ac winding currents. When the flux density variations are small, core loss can be neglected. Alternatively, a low-frequency material can be used, having higher saturation flux density.
- 2. The core geometrical constant K_g is a measure of the magnetic size of a core, for applications in which copper loss is dominant. In the K_g design method, flux density and total copper loss are specified.

Chapter 14. Transformer Design

Some more advanced design issues, not considered in previous chapter:


- Inclusion of core loss
- Selection of operating flux density to optimize total loss
- Multiple winding design: how to allocate the available window area among several windings
- A transformer design procedure
- How switching frequency
 affects transformer size

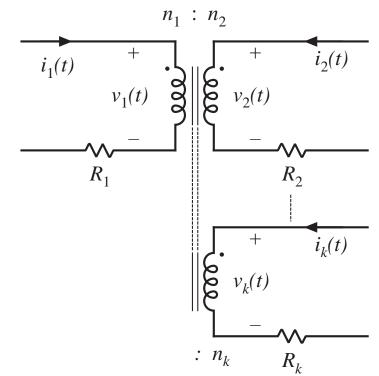


Chapter 14. Transformer Design

- 14.1. Winding area optimization
- 14.2. Transformer design: Basic constraints
- 14.3. A step-by-step transformer design procedure
- 14.4. Examples
- 14.5. Ac inductor design
- 14.6. Summary

14.1. Winding area optimization

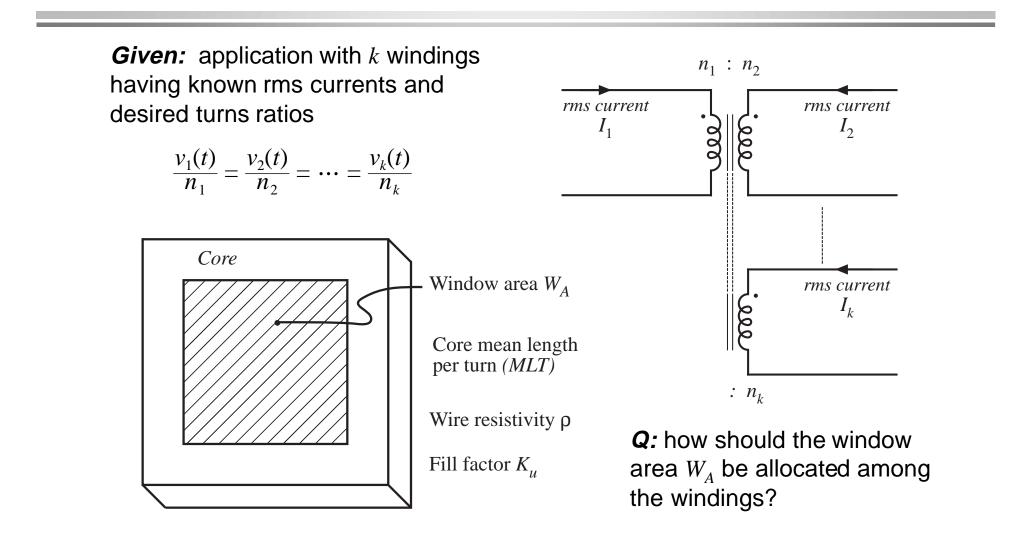

Allocation of winding area

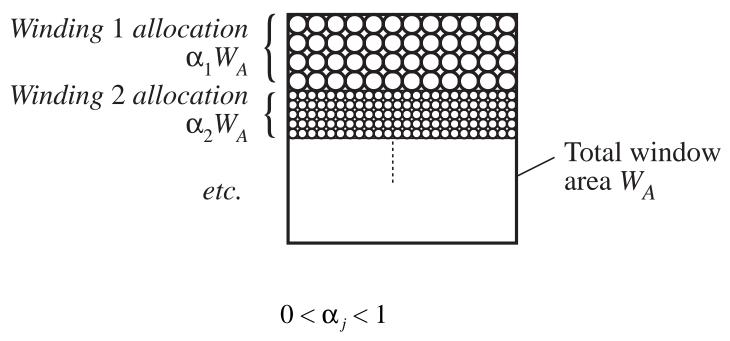

$$\alpha_1 + \alpha_2 + \cdots + \alpha_k = 1$$

Copper loss in winding *j*

Copper loss (not accounting for proximity loss) is

$$P_{cu,j} = I_j^2 R_j$$

Resistance of winding j is

$$R_j = \rho \, \frac{l_j}{A_{W,j}}$$

with

$$l_{j} = n_{j} (MLT)$$
$$A_{W,j} = \frac{W_{A}K_{u}\alpha_{j}}{n_{j}}$$

length of wire, winding j

wire area, winding *j*

Hence

$$P_{cu,j} = \frac{n_j^2 i_j^2 \rho (MLT)}{W_A K_u \alpha_j}$$

 \mathbf{a}


Total copper loss of transformer

Sum previous expression over all windings:

$$P_{cu,tot} = P_{cu,1} + P_{cu,2} + \dots + P_{cu,k} = \frac{\rho (MLT)}{W_A K_u} \sum_{j=1}^k \left(\frac{n_j^2 I_j^2}{\alpha_j} \right)$$

Need to select values for $\alpha_1, \alpha_2, ..., \alpha_k$ such that the total copper loss is minimized

Variation of copper losses with α_1

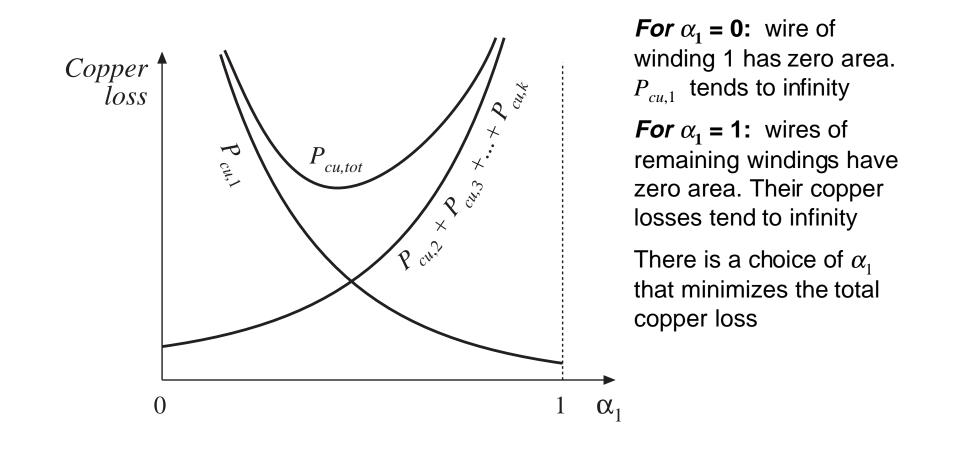

Method of Lagrange multipliers to minimize total copper loss

Minimize the function

$$P_{cu,tot} = P_{cu,1} + P_{cu,2} + \dots + P_{cu,k} = \frac{\rho (MLT)}{W_A K_u} \sum_{j=1}^k \left(\frac{n_j^2 I_j^2}{\alpha_j} \right)$$

subject to the constraint

$$\alpha_1 + \alpha_2 + \cdots + \alpha_k = 1$$

Define the function

$$f(\alpha_1, \alpha_2, \cdots, \alpha_k, \xi) = P_{cu,tot}(\alpha_1, \alpha_2, \cdots, \alpha_k) + \xi g(\alpha_1, \alpha_2, \cdots, \alpha_k)$$

where

$$g(\boldsymbol{\alpha}_1, \boldsymbol{\alpha}_2, \cdots, \boldsymbol{\alpha}_k) = 1 - \sum_{j=1}^k \boldsymbol{\alpha}_j$$

is the constraint that must equal zero and ξ is the Lagrange multiplier

Lagrange multipliers continued

Optimum point is solution of the system of equations

$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \alpha_1} = 0$$
$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \alpha_2} = 0$$
$$\vdots$$
$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \alpha_k} = 0$$
$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \xi} = 0$$

Result:

$$\xi = \frac{\rho (MLT)}{W_A K_u} \left(\sum_{j=1}^k n_j I_j \right)^2 = P_{cu,tot}$$
$$\alpha_m = \frac{n_m I_m}{\sum_{n=1}^\infty n_j I_j}$$

An alternate form:

$$\alpha_m = \frac{V_m I_m}{\sum_{n=1}^{\infty} V_j I_j}$$

Interpretation of result


$$\alpha_m = \frac{V_m I_m}{\sum_{n=1}^{\infty} V_j I_j}$$

Apparent power in winding j is

```
V_j I_j
where V_j is the rms or peak applied voltage I_j is the rms current
```

Window area should be allocated according to the apparent powers of the windings

Example PWM full-bridge transformer

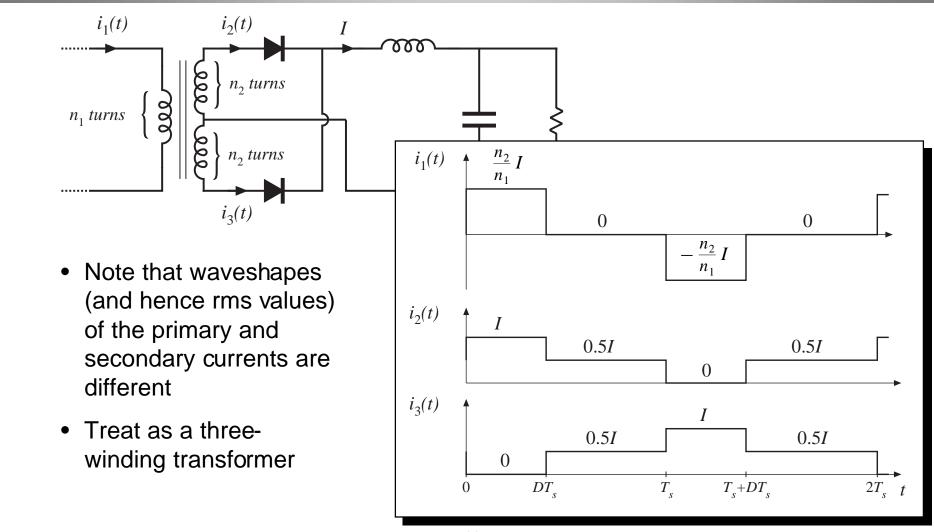

Expressions for RMS winding currents

$$I_{1} = \sqrt{\frac{1}{2T_{s}} \int_{0}^{2T_{s}} i_{1}^{2}(t) dt} = \frac{n_{2}}{n_{1}} I \sqrt{D}$$

$$I_{2} = I_{3} = \sqrt{\frac{1}{2T_{s}} \int_{0}^{2T_{s}} i_{2}^{2}(t) dt} = \frac{1}{2} I \sqrt{1 + D}$$

$$i_{2}(t)$$

$$I_{2} = I_{3} = \sqrt{\frac{1}{2T_{s}} \int_{0}^{2T_{s}} i_{2}^{2}(t) dt} = \frac{1}{2} I \sqrt{1 + D}$$

$$i_{2}(t)$$

$$I_{3}(t)$$

Allocation of window area:

$$\alpha_m = \frac{V_m I_m}{\sum_{n=1}^{\infty} V_j I_j}$$

Plug in rms current expressions. Result:

$$\alpha_1 = \frac{1}{\left(1 + \sqrt{\frac{1+D}{D}}\right)}$$

$$\alpha_2 = \alpha_3 = \frac{1}{2} \frac{1}{\left(1 + \sqrt{\frac{D}{1+D}}\right)}$$

Fraction of window area allocated to primary winding

Fraction of window area allocated to each secondary winding

Numerical example

Suppose that we decide to optimize the transformer design at the worst-case operating point D = 0.75. Then we obtain

 $\alpha_1 = 0.396$ $\alpha_2 = 0.302$ $\alpha_3 = 0.302$

The total copper loss is then given by

$$P_{cu,tot} = \frac{\rho(MLT)}{W_A K_u} \left(\sum_{j=1}^3 n_j I_j\right)^2 \\ = \frac{\rho(MLT) n_2^2 I^2}{W_A K_u} \left(1 + 2D + 2\sqrt{D(1+D)}\right)^2$$

14.2 Transformer design: Basic constraints

Core loss

$$P_{fe} = K_{fe} B^{\beta}_{max} A_c l_m$$

Typical value of β for ferrite materials: 2.6 or 2.7

 B_{max} is the peak value of the ac component of B(t)

So increasing B_{max} causes core loss to increase rapidly

This is the first constraint


Flux density Constraint #2

Flux density B(t) is related to the applied winding voltage according to Faraday's Law. Denote the voltseconds applied to the primary winding during the positive portion of $v_1(t)$ as λ_1 :

$$\lambda_1 = \int_{t_1}^{t_2} v_1(t) dt$$

This causes the flux to change from its negative peak to its positive peak. From Faraday's law, the peak value of the ac component of flux density is

$$B_{max} = \frac{\lambda_1}{2n_1 A_c}$$

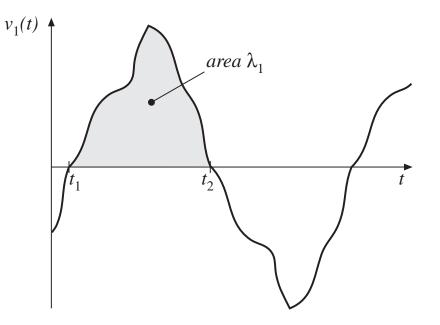

To attain a given flux density, the primary turns should be chosen according to

$$n_1 = \frac{\lambda_1}{2B_{max}A_c}$$

Fundamentals of Power Electronics

Chapter 14: Transformer design

Copper loss Constraint #3

- Allocate window area between windings in optimum manner, as described in previous section
- Total copper loss is then equal to

$$P_{cu} = \frac{\rho(MLT)n_1^2 I_{tot}^2}{W_A K_u}$$

with


$$I_{tot} = \sum_{j=1}^{k} \frac{n_j}{n_1} I_j$$

Eliminate n_1 , using result of previous slide:

$$P_{cu} = \left(\frac{\rho \ \lambda_1^2 \ I_{tot}^2}{K_u}\right) \left(\frac{(MLT)}{W_A A_c^2}\right) \left(\frac{1}{B_{max}^2}\right)$$

Note that copper loss decreases rapidly as B_{max} is increased

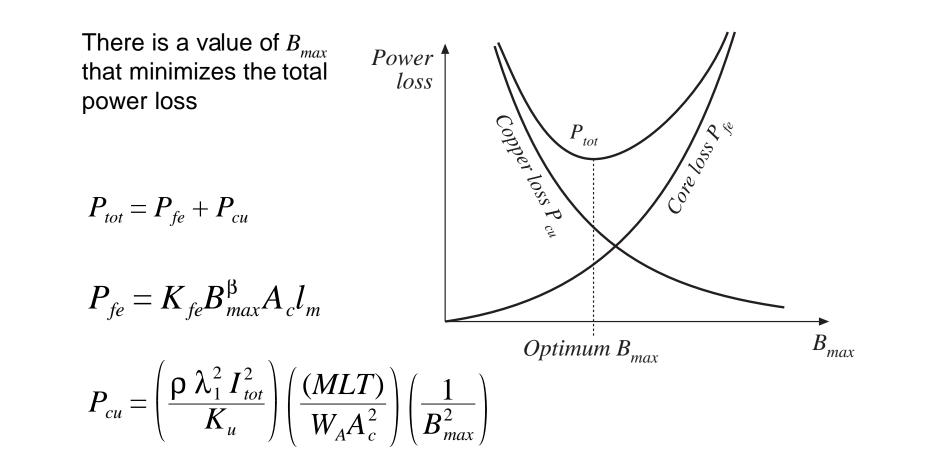Total power loss 4. $P_{tot} = P_{cu} + P_{fe}$



5. Find optimum flux density B_{max}

Given that

$$P_{tot} = P_{fe} + P_{cu}$$

Then, at the B_{max} that minimizes P_{tot} , we can write

$$\frac{dP_{tot}}{dB_{max}} = \frac{dP_{fe}}{dB_{max}} + \frac{dP_{cu}}{dB_{max}} = 0$$

Note: optimum does not necessarily occur where $P_{fe} = P_{cu}$. Rather, it occurs where

$$\frac{dP_{fe}}{dB_{max}} = -\frac{dP_{cu}}{dB_{max}}$$

Take derivatives of core and copper loss

$$P_{fe} = K_{fe} B^{\beta}_{max} A_c l_m \qquad P_{cu} = \left(\frac{\rho \lambda_1^2 I_{tot}^2}{K_u}\right) \left(\frac{(MLT)}{W_A A_c^2}\right) \left(\frac{1}{B_{max}^2}\right)$$
$$\frac{dP_{fe}}{dB_{max}} = \beta K_{fe} B^{(\beta-1)}_{max} A_c l_m \qquad \frac{dP_{cu}}{dB_{max}} = -2 \left(\frac{\rho \lambda_1^2 I_{tot}^2}{4K_u}\right) \left(\frac{(MLT)}{W_A A_c^2}\right) B_{max}^{-3}$$
Now, substitute into $\frac{dP_{fe}}{dB_{max}} = -\frac{dP_{cu}}{dB_{max}}$ and solve for B_{max} :
$$B_{max} = \left[\frac{\rho \lambda_1^2 I_{tot}^2}{2K_u} \frac{(MLT)}{W_A A_c^2 l_m} \frac{1}{\beta K_{fe}}\right]^{\left(\frac{1}{\beta+2}\right)} \qquad \text{Optimum } B_{max} \text{ for a given core and application}$$

Total loss

Substitute optimum B_{max} into expressions for P_{cu} and P_{fe} . The total loss is:

$$P_{tot} = \left[A_c l_m K_{fe}\right]^{\left(\frac{2}{\beta+2}\right)} \left[\frac{\rho \lambda_1^2 I_{tot}^2}{4K_u} \frac{(MLT)}{W_A A_c^2}\right]^{\left(\frac{\beta}{\beta+2}\right)} \left[\left(\frac{\beta}{2}\right)^{-\left(\frac{\beta}{\beta+2}\right)} + \left(\frac{\beta}{2}\right)^{\left(\frac{2}{\beta+2}\right)}\right]$$

Rearrange as follows:

$$\frac{W_A \left(A_c\right)^{\left(2(\beta-1)/\beta\right)}}{\left(MLT\right) l_m^{\left(2/\beta\right)}} \left[\left(\frac{\beta}{2}\right)^{-\left(\frac{\beta}{\beta+2}\right)} + \left(\frac{\beta}{2}\right)^{\left(\frac{2}{\beta+2}\right)} \right]^{-\left(\frac{\beta+2}{\beta}\right)} = \frac{\rho \lambda_1^2 I_{tot}^2 K_{fe}^{\left(2/\beta\right)}}{4K_u \left(P_{tot}\right)^{\left((\beta+2)/\beta\right)}}$$

Left side: terms depend on core geometry

Right side: terms depend on specifications of the application

The core geometrical constant K_{gfe}

Define
$$K_{gfe} = \frac{W_A \left(A_c\right)^{\left(2(\beta-1)/\beta\right)}}{(MLT) \ l_m^{\left(2/\beta\right)}} \left[\left(\frac{\beta}{2}\right)^{-\left(\frac{\beta}{\beta+2}\right)} + \left(\frac{\beta}{2}\right)^{\left(\frac{2}{\beta+2}\right)} \right]^{-\left(\frac{\beta+2}{\beta}\right)}$$

Design procedure: select a core that satisfies

$$K_{gfe} \geq \frac{\rho \lambda_1^2 I_{tot}^2 K_{fe}^{(2/\beta)}}{4K_u \left(P_{tot}\right)^{\left(\left(\beta+2\right)/\beta\right)}}$$

Appendix 2 lists the values of K_{gfe} for common ferrite cores

 K_{gfe} is similar to the K_g geometrical constant used in Chapter 13:

- K_g is used when B_{max} is specified
- K_{gfe} is used when B_{max} is to be chosen to minimize total loss

14.3 Step-by-step transformer design procedure

The following quantities are specified, using the units noted:		
Wire effective resistivity	ρ	$(\Omega-cm)$
Total rms winding current, ref to pri	I_{tot}	(A)
Desired turns ratios	$n_2/n_1, n_3/n_1,$ etc.	
Applied pri volt-sec	λ_1^2	(V-sec)
Allowed total power dissipation	P_{tot}	(W)
Winding fill factor	K_{u}^{ior}	
Core loss exponent	β	
Core loss coefficient	K_{fe}	(W/cm^3T^β)
Other quantities and their dimension	ons:	
Core cross-sectional area	A_{c}	(cm^2)
Core window area	Ŵ _A	(cm^2)
Mean length per turn	MLT	(cm)
Magnetic path length	l_e	(cm)
Wire areas	$A_{w1},$	(cm^2)
Peak ac flux density	B_{max}	(T)

Fundamentals of Power Electronics

Chapter 14: Transformer design

Procedure Determine core size

$$K_{gfe} \geq \frac{\rho \lambda_1^2 I_{tot}^2 K_{fe}^{(2/\beta)}}{4K_u \left(P_{tot}\right)^{\left(\left(\beta+2\right)/\beta\right)}} \ 10^8$$

Select a core from Appendix 2 that satisfies this inequality.

It may be possible to reduce the core size by choosing a core material that has lower loss, i.e., lower K_{fe} .

2. Evaluate peak ac flux density

$$B_{max} = \left[10^8 \ \frac{\rho \lambda_1^2 I_{tot}^2}{2K_u} \ \frac{(MLT)}{W_A A_c^3 l_m} \ \frac{1}{\beta K_{fe}} \right]^{\left(\frac{1}{\beta+2}\right)}$$

At this point, one should check whether the saturation flux density is exceeded. If the core operates with a flux dc bias B_{dc} , then $B_{max} + B_{dc}$ should be less than the saturation flux density.

If the core will saturate, then there are two choices:

- Specify B_{max} using the K_g method of Chapter 13, or
- Choose a core material having greater core loss, then repeat steps 1 and 2

3. and 4. Evaluate turns

Primary turns:

$$n_1 = \frac{\lambda_1}{2B_{max}A_c} \quad 10^4$$

Choose secondary turns according to desired turns ratios:

$$n_2 = n_1 \left(\frac{n_2}{n_1}\right)$$
$$n_3 = n_1 \left(\frac{n_3}{n_1}\right)$$
$$\vdots$$

5. and 6. Choose wire sizes

Fraction of window area assigned to each winding:

$$\alpha_1 = \frac{n_1 I_1}{n_1 I_{tot}}$$
$$\alpha_2 = \frac{n_2 I_2}{n_1 I_{tot}}$$
$$\vdots$$
$$\alpha_k = \frac{n_k I_k}{n_1 I_{tot}}$$

Choose wire sizes according to:

$$A_{w1} \leq \frac{\alpha_1 K_u W_A}{n_1}$$
$$A_{w2} \leq \frac{\alpha_2 K_u W_A}{n_2}$$
$$\vdots$$

Check: computed transformer model

Predicted magnetizing inductance, referred to primary:


$$L_M = \frac{\mu n_1^2 A_c}{l_m}$$

Peak magnetizing current:


$$i_{M, pk} = \frac{\lambda_1}{2L_M}$$

Predicted winding resistances:
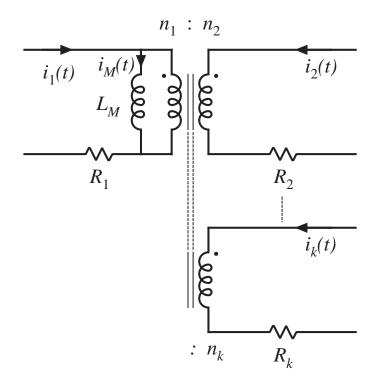
$$R_{1} = \frac{\rho n_{1}(MLT)}{A_{w1}}$$
$$R_{2} = \frac{\rho n_{2}(MLT)}{A_{w2}}$$
$$\vdots$$



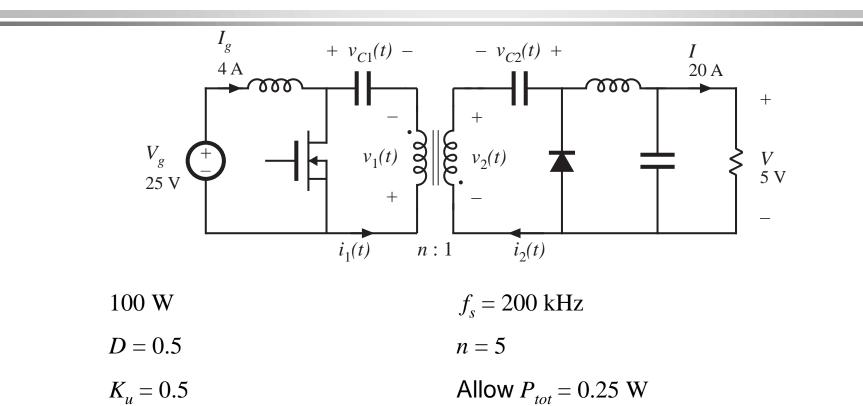
14.4.1 Example 1: Single-output isolated Cuk converter



Use a ferrite pot core, with Magnetics Inc. P material. Loss parameters at 200 kHz are

$$K_{fe} = 24.7 \qquad \qquad \beta = 2.6$$

Waveforms

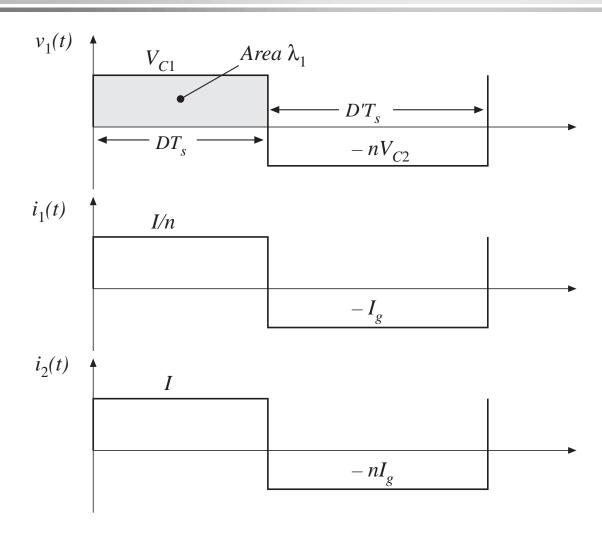

Fundamentals of Power Electronics

Applied primary voltseconds:

$$λ_1 = DT_s V_{c1} = (0.5) (5 \, \mu \text{sec}) (25 \, \text{V})$$

= 62.5 V-μsec

Applied primary rms current:

$$I_1 = \sqrt{D\left(\frac{I}{n}\right)^2 + D'\left(I_g\right)^2} = 4 \text{ A}$$

Applied secondary rms current:

 $I_2 = nI_1 = 20 \text{ A}$

Total rms winding current:

$$I_{tot} = I_1 + \frac{1}{n} I_2 = 8 \text{ A}$$

Chapter 14: Transformer design

Choose core size

$$K_{gfe} \ge \frac{(1.724 \cdot 10^{-6})(62.5 \cdot 10^{-6})^2 (8)^2 (24.7)^{(2/2.6)}}{4 (0.5) (0.25)^{(4.6/2.6)}} \quad 10^8$$
$$= 0.00295$$

Pot core data of Appendix 2 lists 2213 pot core with

$$K_{gfe} = 0.0049$$

Next smaller pot core is not large enough.

Evaluate peak ac flux density

$$B_{max} = \left[10^8 \frac{(1.724 \cdot 10^{-6})(62.5 \cdot 10^{-6})^2(8)^2}{2 (0.5)} \frac{(4.42)}{(0.297)(0.635)^3(3.15)} \frac{1}{(2.6)(24.7)}\right]^{(1/4.6)}$$

= 0.0858 Tesla

This is much less than the saturation flux density of approximately 0.35 T. Values of Bmax in the vicinity of 0.1 T are typical for ferrite designs that operate at frequencies in the vicinity of 100 kHz.

Evaluate turns

 $n_1 = 10^4 \frac{(62.5 \cdot 10^{-6})}{2(0.0858)(0.635)}$ = 5.74 turns

$$n_2 = \frac{n_1}{n} = 1.15$$
 turns

In practice, we might select

 $n_1 = 5$ and $n_2 = 1$

This would lead to a slightly higher flux density and slightly higher loss.

Determine wire sizes

Fraction of window area allocated to each winding:

$$\alpha_1 = \frac{\left(4 \text{ A}\right)}{\left(8 \text{ A}\right)} = 0.5$$
$$\alpha_2 = \frac{\left(\frac{1}{5}\right)\left(20 \text{ A}\right)}{\left(8 \text{ A}\right)} = 0.5$$

(Since, in this example, the ratio of winding rms currents is equal to the turns ratio, equal areas are allocated to each winding)

From wire table,

Appendix 2:

Wire areas:

$$A_{w1} = \frac{(0.5)(0.5)(0.297)}{(5)} = 14.8 \cdot 10^{-3} \text{ cm}^2 \qquad \text{AWG \#16}$$
$$A_{w2} = \frac{(0.5)(0.5)(0.297)}{(1)} = 74.2 \cdot 10^{-3} \text{ cm}^2 \qquad \text{AWG \#9}$$

Wire sizes: discussion

Primary

5 turns #16 AWG

Secondary


1 turn #9 AWG

- Very large conductors!
- One turn of #9 AWG is not a practical solution

Some alternatives


- Use foil windings
- Use Litz wire or parallel strands of wire

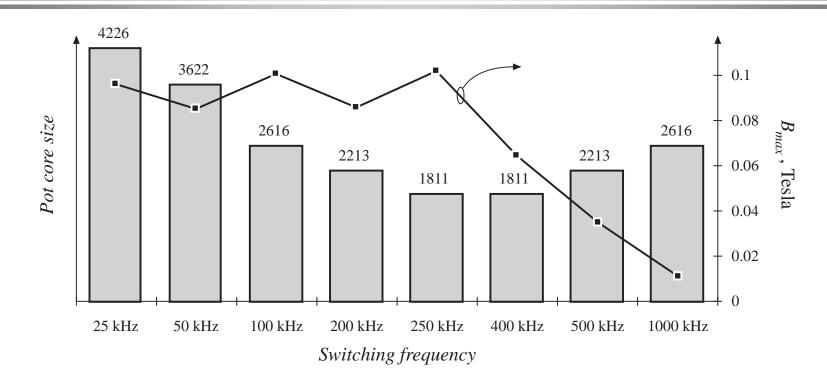Effect of switching frequency on transformer size for this P-material Cuk converter example



 As switching frequency is increased from 25 kHz to 250 kHz, core size is dramatically reduced As switching frequency is increased from 400 kHz to 1 MHz, core size increases

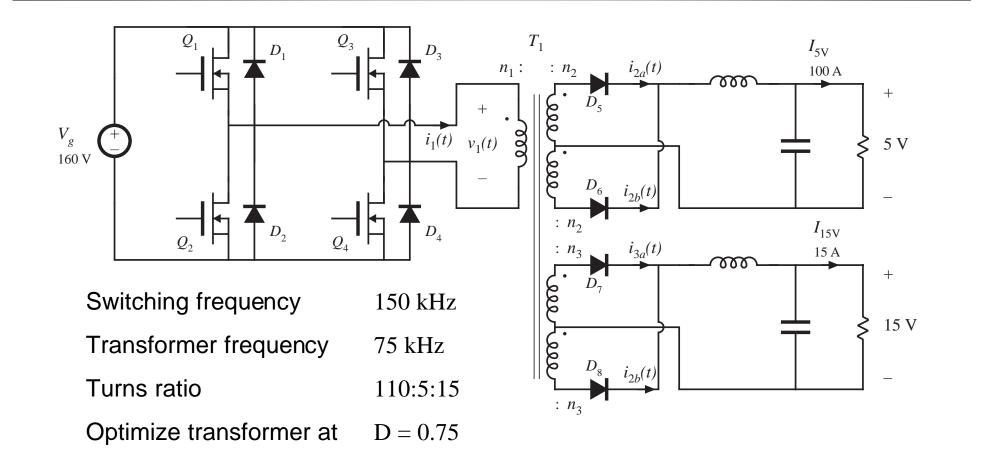14.4.2 Example 2 Multiple-Output Full-Bridge Buck Converter



Other transformer design details

Use Magnetics, Inc. ferrite P material. Loss parameters at 75 kHz:

 $K_{fe} = 7.6 \text{ W/T}^{\beta} \text{cm}^{3}$ $\beta = 2.6$

Use E-E core shape

Assume fill factor of

 $K_u = 0.25$ (reduced fill factor accounts for added insulation required in multiple-output off-line application)


Allow transformer total power loss of

 $P_{tot} = 4 \text{ W}$ (approximately 0.5% of total output power)

Use copper wire, with

 $\rho = 1.724 \cdot 10^{-6} \ \Omega$ -cm


Applied transformer waveforms

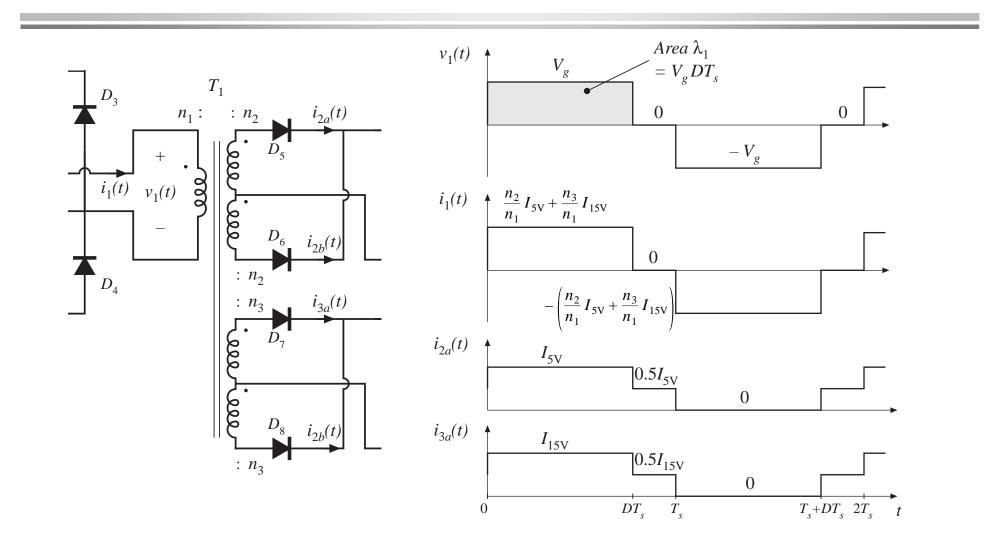

Fundamentals of Power Electronics

Chapter 14: Transformer design

Applied primary volt-seconds

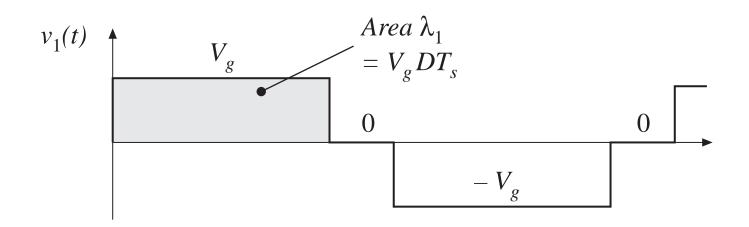

 $\lambda_1 = DT_s V_g = (0.75) (6.67 \,\mu sec) (160 \,V) = 800 \,V - \mu sec$


Fundamentals of Power Electronics

Chapter 14: Transformer design

Applied primary rms current

$$i_{1}(t) \qquad \frac{n_{2}}{n_{1}}I_{5V} + \frac{n_{3}}{n_{1}}I_{15V} \\ 0 \\ -\left(\frac{n_{2}}{n_{1}}I_{5V} + \frac{n_{3}}{n_{1}}I_{15V}\right) \\ I_{1} = \left(\frac{n_{2}}{n_{1}}I_{5V} + \frac{n_{3}}{n_{1}}I_{15V}\right)\sqrt{D} = 5.7 \text{ A}$$

Applied rms current, secondary windings

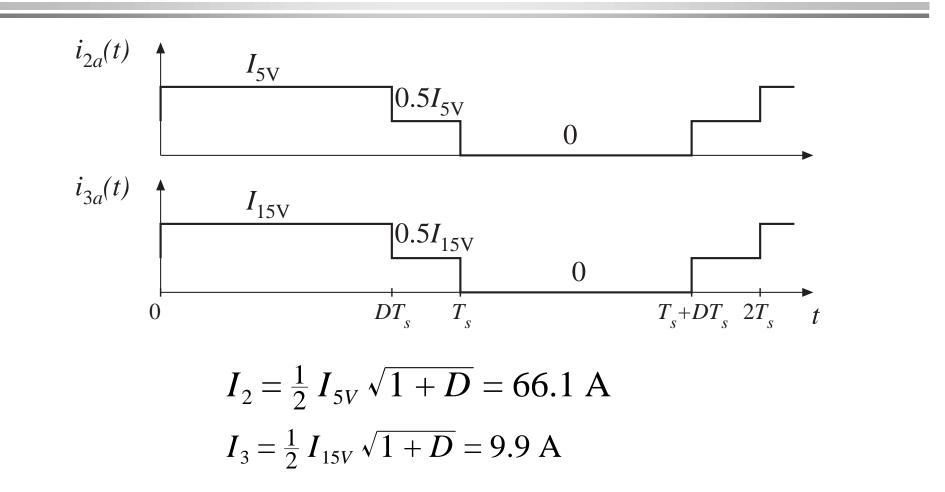


I_{tot}

RMS currents, summed over all windings and referred to primary


$$I_{tot} = \sum_{\substack{all \ 5 \\ windings}} \frac{n_j}{n_1} I_j = I_1 + 2 \frac{n_2}{n_1} I_2 + 2 \frac{n_3}{n_1} I_3$$
$$= (5.7 \text{ A}) + \frac{5}{110} (66.1 \text{ A}) + \frac{15}{110} (9.9 \text{ A})$$
$$= 14.4 \text{ A}$$

Select core size
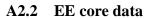
$$K_{gfe} \ge \frac{(1.724 \cdot 10^{-6})(800 \cdot 10^{-6})^2 (14.4)^2 (7.6)^{(2/2.6)}}{4 (0.25) (4)^{(4.6/2.6)}} \quad 10^8$$
$$= 0.00937$$



From Appendix 2

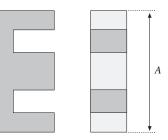

Core	Geometrical	Geometrical	Cross-	Bobbin	Mean	Magnetic	Core
type	constant	constant	sectional	winding	length	path	weight
			area	area	per turn	length	
(A)	$K_{g_{5}}$	K_{gfe}	A_{c_2}	W_A	MLT	l_m	
(mm)	cm ^o	cm ^x	(cm^2)	(cm^2)	(cm)	(cm)	(g)
EE22	8.26.10-3	$1.8 \cdot 10^{-3}$	0.41	0.196	3.99	3.96	8.81
EE30	85.7·10 ⁻³	6.7·10 ⁻³	1.09	0.476	6.60	5.77	32.4
 EE40	0.209	11.8.10-3	1.27	1.10	8.50	7.70	50.3
EE50	0.909	28.4·10 ⁻³	2.26	1.78	10.0	9.58	116

Evaluate ac flux density B_{max}

Eq. (14.41):

$$B_{max} = \left[10^8 \frac{\rho \lambda_1^2 I_{tot}^2}{2K_u} \frac{(MLT)}{W_A A_c^3 l_m} \frac{1}{\beta K_{fe}} \right]^{\left(\frac{1}{\beta+2}\right)}$$

Plug in values:

$$B_{max} = \left[10^8 \frac{(1.724 \cdot 10^{-6})(800 \cdot 10^{-6})^2 (14.4)^2}{2 (0.25)} \frac{(8.5)}{(1.1)(1.27)^3 (7.7)} \frac{1}{(2.6)(7.6)} \right]^{(1/4.6)}$$

= 0.23 Tesla

This is less than the saturation flux density of approximately 0.35 T

Evaluate turns

Choose n_1 according to Eq. (14.42):

$$n_1 = \frac{\lambda_1}{2B_{max}A_c} \quad 10^4$$

$$n_1 = 10^4 \frac{(800 \cdot 10^{-6})}{2(0.23)(1.27)}$$

= 13.7 turns

Choose secondary turns according to desired turns ratios:

$$n_2 = \frac{5}{110} n_1 = 0.62 \text{ turns}$$
$$n_3 = \frac{15}{110} n_1 = 1.87 \text{ turns}$$

Rounding the number of turns

To obtain desired turns ratio of

110:5:15

we might round the actual turns to

22:1:3

Increased n_1 would lead to

- Less core loss
- More copper loss
- Increased total loss

Loss calculation with rounded turns

With $n_1 = 22$, the flux density will be reduced to

$$B_{max} = \frac{(800 \cdot 10^{-6})}{2 (22) (1.27)} \ 10^4 = 0.143 \ \text{Tesla}$$

The resulting losses will be

$$P_{fe} = (7.6)(0.143)^{2.6}(1.27)(7.7) = 0.47 \text{ W}$$

$$P_{cu} = \frac{(1.724 \cdot 10^{-6})(800 \cdot 10^{-6})^2(14.4)^2}{4 (0.25)} \frac{(8.5)}{(1.1)(1.27)^2} \frac{1}{(0.143)^2} 10^8$$

$$= 5.4 \text{ W}$$

$$P_{tot} = P_{fe} + P_{cu} = 5.9 \text{ W}$$

Which exceeds design goal of 4 W by 50%. So use next larger core size: EE50.

Calculations with EE50

Repeat previous calculations for EE50 core size. Results:


$$B_{max} = 0.14 \text{ T}, n_1 = 12, P_{tot} = 2.3 \text{ W}$$

Again round n_1 to 22. Then

$$B_{max} = 0.08 \text{ T}, P_{cu} = 3.89 \text{ W}, P_{fe} = 0.23 \text{ W}, P_{tot} = 4.12 \text{ W}$$

Which is close enough to 4 W.

Wire sizes for EE50 design

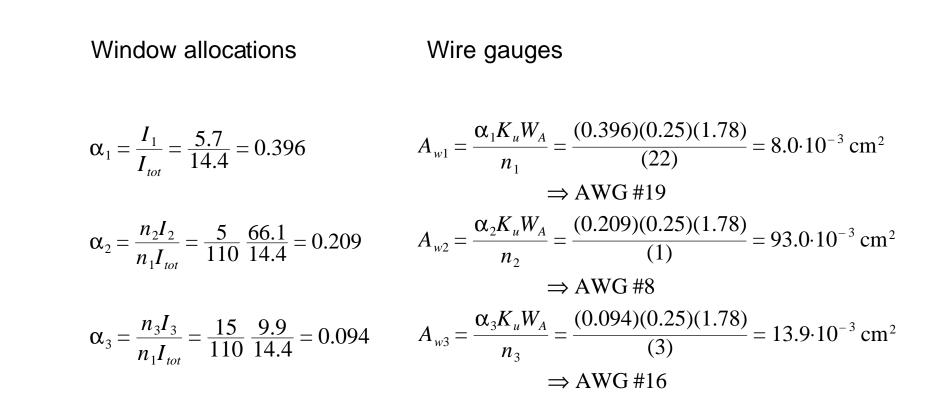

Might actually use foil or Litz wire for secondary windings

Part IV Modern Rectifiers and Power System Harmonics

Chapter 15	Power and Harmonics in Nonsinusoidal Systems
Chapter 16	Line-Commutated Rectifiers
Chapter 17	The Ideal Rectifier

Low Harmonic Rectifier Modeling and Control

Chapter 18

 ~ 1


Chapter 15 Power And Harmonics in Nonsinusoidal Systems

15.1. Average power in terms of Fourier series 15.2. RMS value of a waveform 15.3. Power factor THD Distortion and Displacement factors 15.4. Power phasors in sinusoidal systems

- 15.5. Harmonic currents in three-phase systems
- 15.6. AC line current harmonic standards

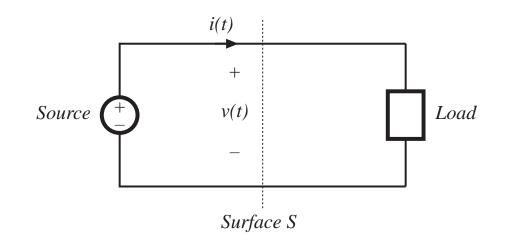15.1. Average power

Observe transmission of energy through surface S



Express voltage and current as Fourier series:

$$v(t) = V_0 + \sum_{n=1}^{\infty} V_n \cos\left(n\omega t - \varphi_n\right)$$
$$i(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos\left(n\omega t - \Theta_n\right)$$

relate energy transmission to harmonics

Fundamentals of Power Electronics

Energy transmitted to load, per cycle

$$W_{cycle} = \int_0^T v(t)i(t)dt$$

This is related to average power as follows:

$$P_{av} = \frac{W_{cycle}}{T} = \frac{1}{T} \int_0^T v(t)i(t)dt$$

Investigate influence of harmonics on average power: substitute Fourier series

$$P_{av} = \frac{1}{T} \int_0^T \left(V_0 + \sum_{n=1}^\infty V_n \cos\left(n\omega t - \varphi_n\right) \right) \left(I_0 + \sum_{n=1}^\infty I_n \cos\left(n\omega t - \Theta_n\right) \right) dt$$

Fundamentals of Power Electronics

Evaluation of integral

Orthogonality of harmonics: Integrals of cross-product terms are zero

$$\int_{0}^{T} \left(V_{n} \cos \left(n \omega t - \varphi_{n} \right) \right) \left(I_{m} \cos \left(m \omega t - \Theta_{m} \right) \right) dt = \begin{cases} 0 & \text{if } n \neq m \\ \frac{V_{n} I_{n}}{2} \cos \left(\varphi_{n} - \Theta_{n} \right) & \text{if } n = m \end{cases}$$


Expression for average power becomes

$$P_{av} = V_0 I_0 + \sum_{n=1}^{\infty} \frac{V_n I_n}{2} \cos\left(\varphi_n - \Theta_n\right)$$


So net energy is transmitted to the load only when the Fourier series of v(t) and i(t) contain terms at the same frequency. For example, if the voltage and current both contain third harmonic, then they lead to the average power $V_{i}L_{i}$

$$\frac{V_3I_3}{2}\cos\left(\varphi_3-\theta_3\right)$$

Fundamentals of Power Electronics

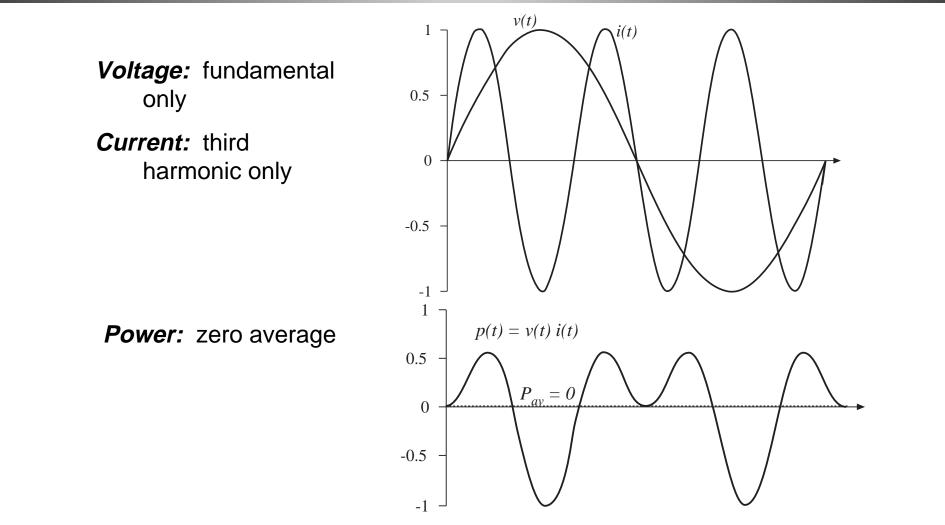

Fundamentals of Power Electronics

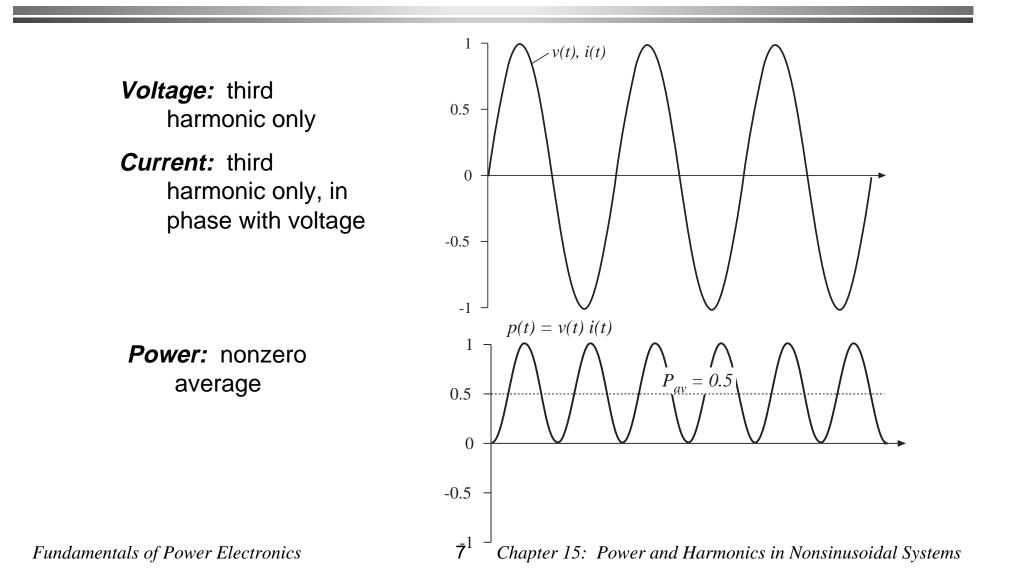


Fourier series:

$$v(t) = 1.2 \cos(\omega t) + 0.33 \cos(3\omega t) + 0.2 \cos(5\omega t)$$

$$i(t) = 0.6 \cos(\omega t + 30^{\circ}) + 0.1 \cos(5\omega t + 45^{\circ}) + 0.1 \cos(7\omega t + 60^{\circ})$$

Average power calculation:
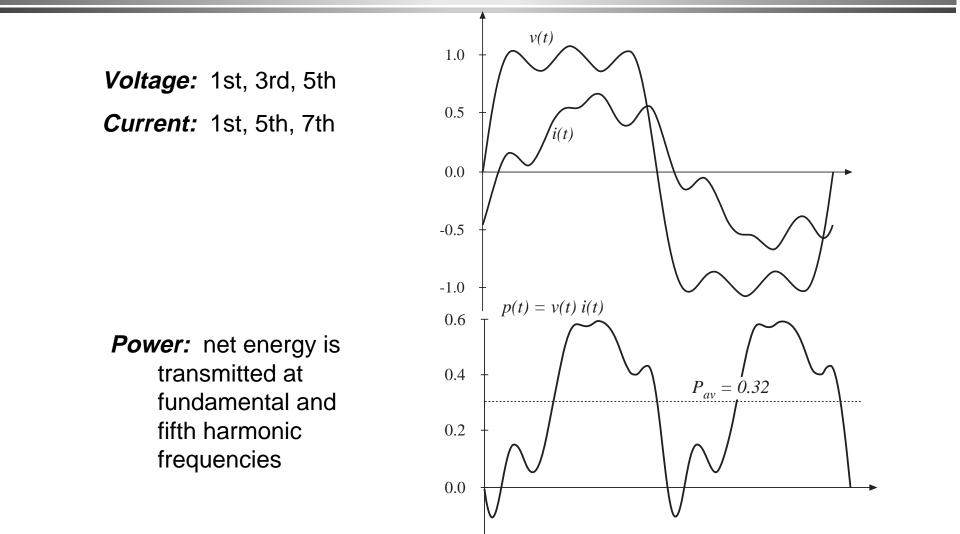
$$P_{av} = \frac{(1.2)(0.6)}{2}\cos(30^\circ) + \frac{(0.2)(0.1)}{2}\cos(45^\circ) = 0.32$$



9.2 Chapter 15: Power and Harmonics in Nonsinusoidal Systems

15.2. Root-mean-square (RMS) value of a waveform, in terms of Fourier series

(rms value) =
$$\sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Insert Fourier series. Again, cross-multiplication terms have zero average. Result is

(rms value) =
$$\sqrt{V_0^2 + \sum_{n=1}^{\infty} \frac{V_n^2}{2}}$$

- Similar expression for current
- Harmonics always increase rms value
- Harmonics do not necessarily increase average power
- Increased rms values mean increased losses

For efficient transmission of energy from a source to a load, it is desired to maximize average power, while minimizing rms current and voltage (and hence minimizing losses).

Power factor is a figure of merit that measures how efficiently energy is transmitted. It is defined as

power factor = $\frac{(average power)}{(rms voltage) (rms current)}$

Power factor always lies between zero and one.

15.3.1. Linear resistive load, nonsinusoidal voltage

Then current harmonics are in phase with, and proportional to, voltage harmonics. All harmonics result in transmission of energy to load, and unity power factor occurs.

Fundamentals of Power Electronics

15.3.2. Nonlinear dynamical load, sinusoidal voltage

With a sinusoidal voltage, current harmonics do not lead to average power. However, current harmonics do increase the rms current, and hence they decrease the power factor.

$$P_{av} = \frac{V_1 I_1}{2} \cos \left(\varphi_1 - \theta_1\right)$$

(rms current) = $\sqrt{I_0^2 + \sum_{n=1}^{\infty} \frac{I_n^2}{2}}$
(power factor) = $\left(\frac{\frac{I_1}{\sqrt{2}}}{\sqrt{I_0^2 + \sum_{n=1}^{\infty} \frac{I_n^2}{2}}}\right) \left(\cos \left(\varphi_1 - \theta_1\right)\right)$

= (distortion factor) (displacement factor)

Fundamentals of Power Electronics

Distortion factor

Defined only for sinusoidal voltage.

(distortion factor) =
$$\left(\frac{\frac{I_1}{\sqrt{2}}}{\sqrt{I_0^2 + \sum_{n=1}^{\infty} \frac{I_n^2}{2}}}\right) = \frac{\text{(rms fundamental current)}}{\text{(rms current)}}$$


Related to Total Harmonic Distortion (THD):

(THD) =
$$\frac{\sqrt{\sum_{n=2}^{\infty} I_n^2}}{I_1}$$

(distortion factor) = $\frac{1}{\sqrt{1 + (\text{THD})^2}}$


Fundamentals of Power Electronics

Distortion factor vs. THD

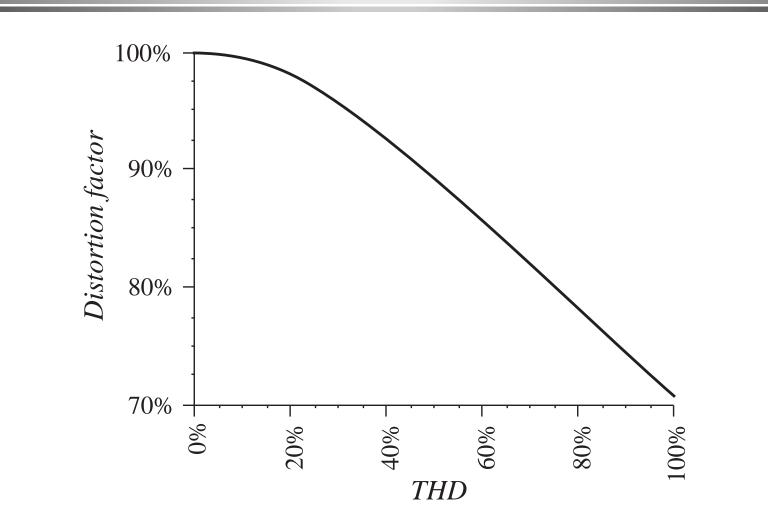

15 Chapter 15: Power and Harmonics in Nonsinusoidal Systems

Peak detection rectifier example

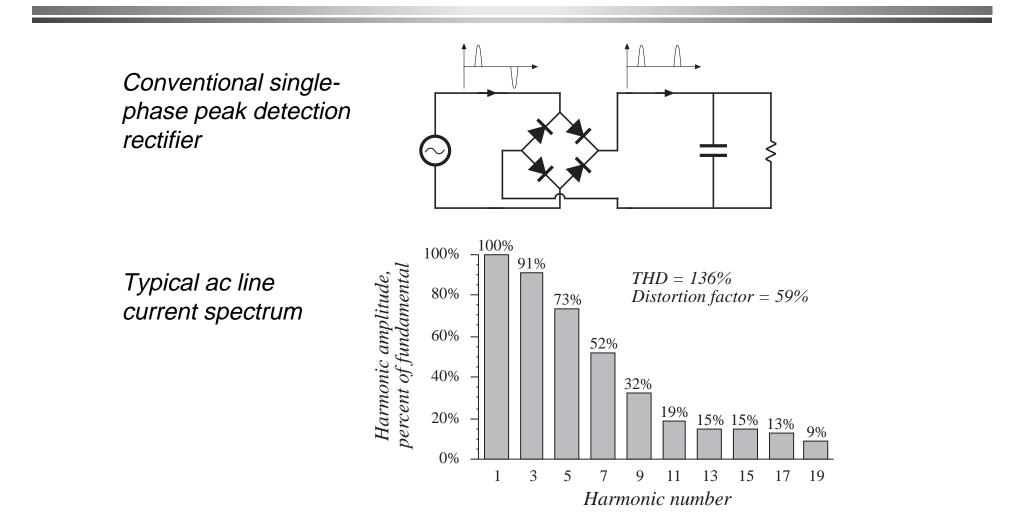

Fundamentals of Power Electronics

Maximum power obtainable from 120V 15A wall outlet

with peak detection rectifier

(ac voltage) (derated breaker current) (power factor) (rectifier efficiency) = (120 V) (80% of 15 A) (0.55) (0.98) = 776 W

at unity power factor

(ac voltage) (derated breaker current) (power factor) (rectifier efficiency) = (120 V) (80% of 15 A) (0.99) (0.93) = 1325 W

15.4. Power phasors in sinusoidal systems

Apparent power is the product of the rms voltage and rms current

It is easily measured —simply the product of voltmeter and ammeter readings

Unit of apparent power is the volt-ampere, or VA

Many elements, such as transformers, are rated according to the VA that they can supply

So power factor is the ratio of average power to apparent power

With sinusoidal waveforms (no harmonics), we can also define the

real power Preactive power Qcomplex power SIf the voltage and current are represented by phasors V and I, then

 $S = VI^* = P + jQ$


with I^* = complex conjugate of I, j = square root of -1. The magnitude of S is the apparent power (VA). The real part of S is the average power P (watts). The imaginary part of S is the reactive power Q (reactive volt-amperes, or VARs).

Example: power phasor diagram

The phase angle between the voltage and current, or $(\phi_1 - \theta_1)$, coincides with the angle of *S*. The power factor is

power factor =
$$\frac{P}{\|S\|} = \cos(\varphi_1 - \theta_1)$$

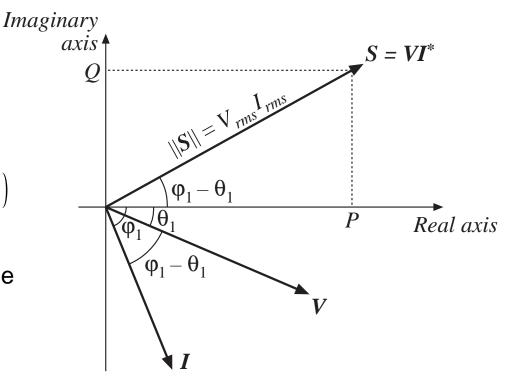In this purely sinusoidal case, the distortion factor is unity, and the power factor coincides with the displacement factor.



The reactive power Q does not lead to net transmission of energy between the source and load. When $Q \neq 0$, the rms current and apparent power are greater than the minimum amount necessary to transmit the average power P.

Inductor: current lags voltage by 90°, hence displacement factor is zero.

The alternate storing and releasing of energy in an inductor leads to current flow and nonzero apparent power, but P = 0.

Just as resistors consume real (average) power P, inductors can be viewed as consumers of reactive power Q.

Capacitor: current leads voltage by 90°, hence displacement factor is zero.

Capacitors supply reactive power Q.

They are often placed in the utility power distribution system near inductive loads. If Q supplied by capacitor is equal to Q consumed by inductor, then the net current (flowing from the source into the capacitor-inductive-load combination) is phase with the voltage, leading to unity power factor and minimum rms current magnitude.

Fundamentals of Power Electronics

Lagging fundamental current of phasecontrolled rectifiers

It will be seen in the next chapter that phase-controlled rectifiers produce a nonsinusoidal current waveform whose fundamental component lags the voltage.

This lagging current does not arise from energy storage, but it does nonetheless lead to a reduced displacement factor, and to rms current and apparent power that are greater than the minimum amount necessary to transmit the average power.


At the fundamental frequency, phase-controlled rectifiers can be viewed as consumers of reactive power Q, similar to inductive loads.

15.5. Harmonic currents in three phase systems

The presence of harmonic currents can also lead to some special problems in three-phase systems:

- In a four-wire three-phase system, harmonic currents can lead to large currents in the neutral conductors, which may easily exceed the conductor rms current rating
- Power factor correction capacitors may experience significantly increased rms currents, causing them to fail
- In this section, these problems are examined, and the properties of harmonic current flow in three-phase systems are derived:
 - Harmonic neutral currents in 3ø four-wire networks
 - Harmonic neutral voltages in 3ø three-wire wye-connected loads

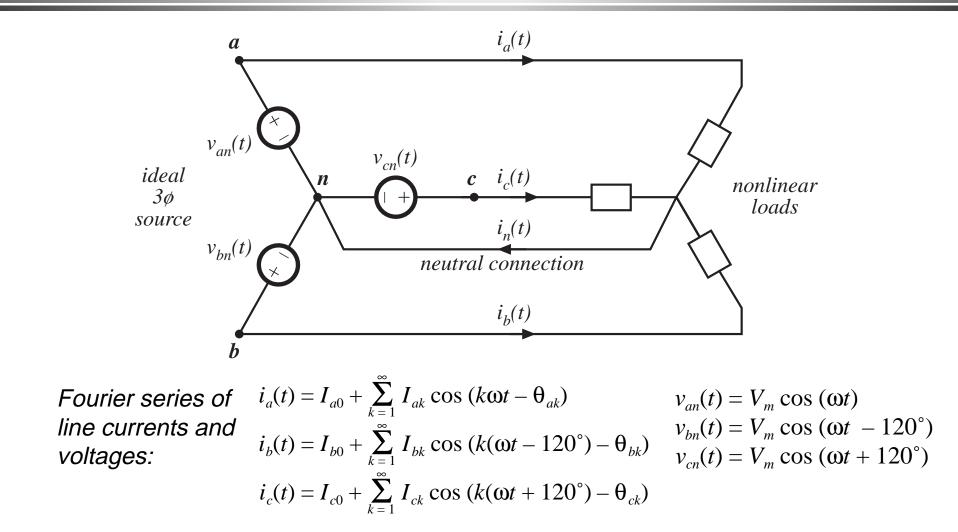15.5.1. Harmonic currents in three-phase four-wire networks



Fundamentals of Power Electronics

23 Chapter 15: Power and Harmonics in Nonsinusoidal Systems

Neutral current

$$i_{n}(t) = I_{a0} + I_{b0} + I_{c0} + \sum_{k=1}^{\infty} \left[I_{ak} \cos (k\omega t - \theta_{ak}) + I_{bk} \cos (k(\omega t - 120^{\circ}) - \theta_{bk}) + I_{ck} \cos (k(\omega t + 120^{\circ}) - \theta_{ck}) \right]$$

If the load is unbalanced, then there is nothing more to say. The neutral connection may contain currents having spectrum similar to the line currents.

In the balanced case, $I_{ak} = I_{bk} = I_{ck} = I_k$ and $\theta_{ak} = \theta_{bk} = \theta_{ck} = \theta_k$, for all *k*; i.e., the harmonics of the three phases all have equal amplitudes and phase shifts. The neutral current is then

$$i_n(t) = 3I_0 + \sum_{k=3,6,9,\cdots}^{\infty} 3I_k \cos(k\omega t - \theta_k)$$

Fundamentals of Power Electronics

24 Chapter 15: Power and Harmonics in Nonsinusoidal Systems

Neutral currents

$$i_n(t) = 3I_0 + \sum_{k=3,6,9,\cdots}^{\infty} 3I_k \cos(k\omega t - \theta_k)$$

- Fundamental and most harmonics cancel out
- Triplen (triple-n, or 0, 3, 6, 9, ...) harmonics do not cancel out, but add. Dc components also add.
- Rms neutral current is

$$i_{n, rms} = 3 \sqrt{I_0^2 + \sum_{k=3,6,9,\cdots}^{\infty} \frac{I_k^2}{2}}$$

Example

A balanced nonlinear load produces line currents containing fundamental and 20% third harmonic: $i_{an}(t) = I_1 \cos(\omega t - \theta_1) + 0.2 I_1 \cos(3\omega t - \theta_3)$. Find the rms neutral current, and compare its amplitude to the rms line current amplitude.

Solution


$$i_{n, rms} = 3 \sqrt{\frac{(0.2I_1)^2}{2}} = \frac{0.6 I_1}{\sqrt{2}}$$

$$i_{1, rms} = \sqrt{\frac{I_1^2 + (0.2I_1)^2}{2}} = \frac{I_1}{\sqrt{2}} \sqrt{1 + 0.04} \approx \frac{I_1}{\sqrt{2}}$$

- The neutral current magnitude is 60% of the line current magnitude!
- The triplen harmonics in the three phases add, such that 20% third harmonic leads to 60% third harmonic neutral current.
- Yet the presence of the third harmonic has very little effect on the rms value of the line current. Significant unexpected neutral current flows.

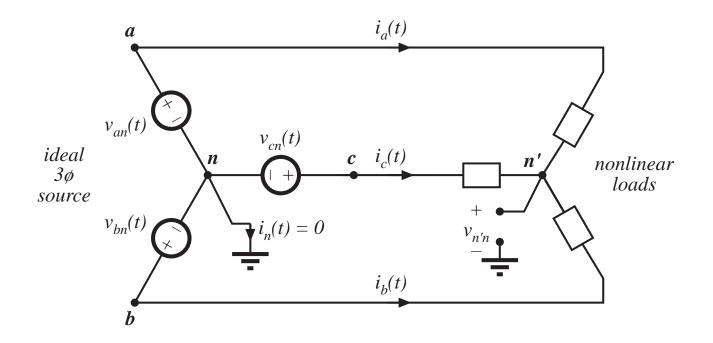15.5.2. Harmonic currents in three-phase three-wire networks

Wye-connected nonlinear load, no neutral connection:



27 Chapter 15: Power and Harmonics in Nonsinusoidal Systems

No neutral connection

If the load is balanced, then it is still true that

$$i_n(t) = 3I_0 + \sum_{k=3,6,9,\cdots}^{\infty} 3I_k \cos(k\omega t - \theta_k)$$

But $i_n(t) = 0$, since there is no neutral connection.

So the ac line currents cannot contain dc or triplen harmonics.


What happens:

A voltage is induced at the load neutral point, that causes the line current dc and triplen harmonics to become zero.

The load neutral point voltage contains dc and triplen harmonics.

With an unbalanced load, the line currents can still contain dc and triplen harmonics.

Delta-connected load

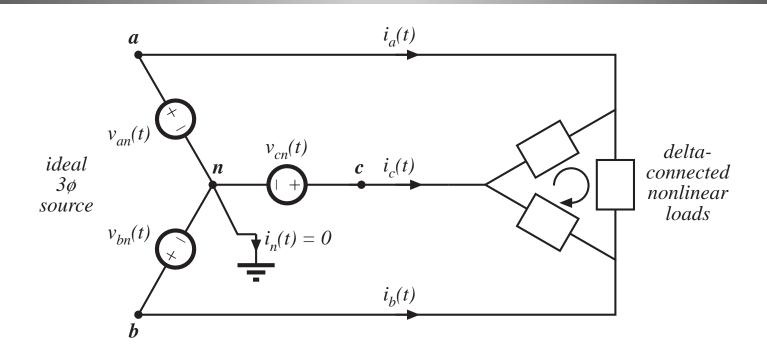

- There is again no neutral connection, so the ac line currents contain no dc or triplen harmonics
- The load currents may contain dc and triplen harmonics: with a balanced nonlinear load, these circulate around the delta.


Harmonic currents in power factor correction capacitors

PFC capacitors are usually not intended to conduct significant harmonic currents.

Heating in capacitors is a function of capacitor equivalent series resistance (esr) and rms current. The maximum allowable rms current then leads to the capacitor rating:

rated rms voltage
$$V_{rms} = \frac{I_{rms}}{2\pi fC}$$

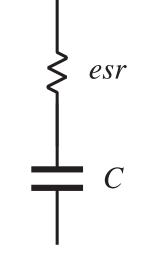rated reactive power $= \frac{I_{rms}^2}{2\pi fC}$



15.6. AC line current harmonic standards

15.6.1. US MIL-STD-461B

- 15.6.2. International Electrotechnical Commission Standard 555
- 15.6.3. IEEE/ANSI Standard 519

15.6.1. US MIL-STD-461B

- For loads of 1kW or greater, no current harmonic magnitude may be greater than 3% of the fundamental magnitude.
- For the nth harmonic with n > 33, the harmonic magnitude may not exceed (1/n) times the fundamental magnitude.
- Harmonic limits are now employed by all of the US armed forces. The specific limits are often tailored to the specific application.
- The shipboard application is a good example of the problems faced in a relatively small stand-alone power system having a large fraction of electronic loads.

15.6.2. International Electrotechnical Commission Standard 555

- First draft of their IEC-555 standard:1982. It has since undergone a number of revisions.
- Enforcement of IEC-555 is the prerogative of each individual country, and hence it has been sometimes difficult to predict whether and where this standard will actually be given the force of law.
- Nonetheless, IEC-555 is now enforced in Europe, making it a de facto standard for commercial equipment intended to be sold worldwide.
- IEC-555 covers a number of different types of low power equipment, with differing harmonic limits. Harmonics for equipment having an input current of up to 16A, connected to 50 or 60 Hz, 220V to 240V single phase circuits (two or three wire), as well as 380V to 415V three phase (three or four wire) circuits, are limited.

Low-power harmonic limits

- In a city environment such as a large building, a large fraction of the total power system load can be nonlinear
- Example: a major portion of the electrical load in a building is comprised of fluorescent lights, which present a very nonlinear characteristic to the utility system.
- A modern office may also contain a large number of personal computers, printers, copiers, etc., each of which may employ peak detection rectifiers.
- Although each individual load is a negligible fraction of the total local load, these loads can collectively become significant.

Class A: Balanced three-phase equipment, and any equipment which does not fit into the other categories. This class includes low harmonic rectifiers for computer and other office equipment. These limits are given in Table 15.1, and are absolute ampere limits.

Class B: Portable tools, and similar devices. The limits are equal to the Table 15.1 limits, multiplied by 1.5.

Class A limits

Odd ha	rmonics	Even harmonics		
Harmonic number	Maximum current	Harmonic number	Maximum curre	
3	2.30A	2	1.08A	
5	1.14A	4	0.43A	
7	0.77A	6	0.30A	
9	0.40A	$8 \le n \le 40$	$0.23 \mathrm{A} \cdot (8/n)$	
11	0.33A			
13	0.21A			
$15 \le n \le 39$	$0.15 \mathrm{A} \cdot (15/n)$			

Table 15.1. IEC-555 Harmonic current limits, Class A and certain Class C

IEC-555: Class C

Class C: Lighting equipment, including dimmers and gas discharge lamps. The input current harmonics of ballasted lamps with an input power of more than 25W must meet the limits of Table 15.2, expressed as a percent of the fundamental current. If the input power is less than 25W, then Table 15.3 applies. Incandescent lamp fixtures containing phase-control dimmers, rated at greater than 600W, must meet the limits of Table 15.1. When testing for compliance, the dimmer must drive a rated-power lamp, with the phase control set to a firing angle of 90°±5°. Incandescent lamp dimmers rated at less than 600W are not covered by the standard. Discharge lamps containing dimmers must meet the limits of both Tables 15.2 and 15.3 at maximum load. Harmonic currents at any dimming position may not exceed the maximum load harmonic currents.

Class C limits


Table 15.2. IEC-555 Harmonic current limits, certain Class C

Harmonic number	Maximum current, percent of fundamental
2	2%
3	$(30\%) \cdot (\text{power factor})$
5	10%
7	7%
9	5%
$11 \le n \le 39$	3%

IEC-555: Class D

Class D: Equipment not covered by Class B or C, which has a special waveshape as defined below. This class is directed at diode-capacitor peak-detection rectifiers. Equipment is placed in class D if the ac input current waveshape lies within the shaded area for at least 95% of the duration of each half-cycle. The center line of the shaded area is set to

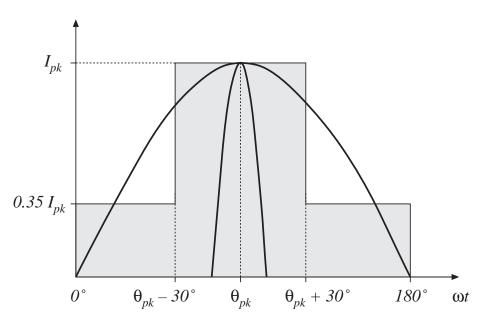coincide with the peak of the current waveform. A sinusoid, and a typical peak detection rectifier waveform, are shown for reference; the sinusoid is not Class D but the peak detection rectifier waveform is. The limits for Class D equipment are given in Table 15.3.



9 Chapter 15: Power and Harmonics in Nonsinusoidal Systems

Class D limits

Odd harmonics			Even harmonics		
Harmonic number	Relative limit (mA/W)	Absolute limit (A)	Harmonic number	Relative limit (mA/W)	Absolute limit (A)
3	3.6	2.30A	2	1.0	0.3A
5	2.0	1.14A	4	0.5	0.15A
7	1.5	0.77A			
9	1.0	0.40A			
$11 \le n \le 39$	$0.6 \cdot (11/n)$	0.33A			

- In 1993, the IEEE published a revised draft standard limiting the amplitudes of current harmonics, IEEE Guide for Harmonic Control and Reactive Compensation of Static Power Converters.
- Harmonic limits are based on the ratio of the fundamental component of the load current IL to the short circuit current at the point of common (PCC) coupling at the utility I_{sc}.
- Stricter limits are imposed on large loads than on small loads. The limits are similar in magnitude to IEC-555, and cover high voltage loads (of much higher power) not addressed by IEC-555. Enforcement of this standard is presently up to the local utility company.
- The odd harmonic limits are listed in Tables 15.4 and 15.5. The limits for even harmonics are 25% of the odd harmonic limits. Dc current components and half-wave rectifiers are not allowed.

IEEE-519 current limits, low voltage systems

Tabl	Table 15.4. IEEE-519 Maximum odd harmonic current limits for general distribution systems, 120V through 69kV					
I _{SC} /I _L	<i>n</i> < 11	11≤ <i>n</i> <17	17≤ <i>n</i> <23	23≤ <i>n</i> <35	35≤ <i>n</i>	THD
<20	4.0%	2.0%	1.5%	0.6%	0.3%	5.0%
20–50	7.0%	3.5%	2.5%	1.0%	0.5%	8.0%
50-100	10.0%	4.5%	4.0%	1.5%	0.7%	12.0%
100-1000	12.0%	5.5%	5.0%	2.0%	1.0%	15.0%
>1000	15.0%	7.0%	6.0%	2.5%	1.4%	20.0%

IEEE-519 current limits, high voltage systems

69.001kV through 101kV						
I _{SC} /IL	<i>n</i> < 11	11≤ <i>n</i> <17	17≤ <i>n</i> <23	23≤ <i>n</i> <35	35≤ <i>n</i>	THD
<20	2.0%	1.0%	0.75%	0.3%	0.15%	2.5%
20–50	3.5%	1.75%	1.25%	0.5%	0.25%	4.0%
50-100	5.0%	2.25%	2.0%	0.75%	0.35%	6.0%
100-1000	6.0%	2.75%	2.5%	1.0%	0.5%	7.5%
>1000	7.5%	3.5%	3.0%	1.25%	0.7%	10.0%

Table 15.5. IEEE-519 Maximum odd harmonic current limits for general distribution systems,69.001kV through 161kV

IEEE-519 voltage limits

Table 15.6. IEEE-519 voltage distortion limits				
Bus voltage at PCC	Individual harmonics	THD		
69kV and below	3.0%	5.0%		
69.001kV-161kV	1.5%	2.5%		
above 161kV	1.0%	1.5%		

It is the responsibility of the utility to meet these limits.

Chapter 16 Line-Commutated Rectifiers

16.1 The single-phase full-wave rectifier

- 16.1.1 Continuous conduction mode
- 16.1.2 Discontinuous conduction mode
- 16.1.3 Behavior when *C* is large
- 16.1.4 Minimizing *THD* when *C* is small
- 16.2 The three-phase bridge rectifier
 - 16.2.1 Continuous conduction mode
 - 16.2.2 Discontinuous conduction mode

Fundamentals of Power Electronics


16.3 Phase control

- 16.3.1 Inverter mode
- 16.3.2 Harmonics and power factor
- 16.3.3 Commutation
- 16.4 Harmonic trap filters
- 16.5 Transformer connections
- 16.6 Summary

Chapter 16: Line-commutated rectifiers

1

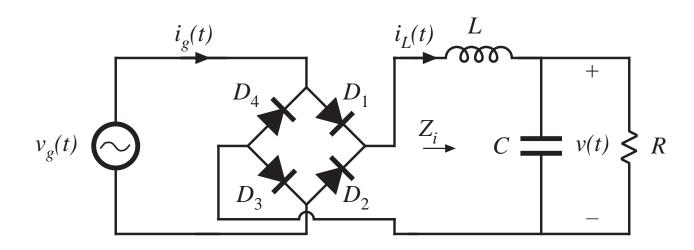16.1 The single-phase full-wave rectifier




Full-wave rectifier with dc-side *L*-*C* filter

Two common reasons for including the dc-side L-C filter:

- Obtain good dc output voltage (large *C*) and acceptable ac line current waveform (large *L*)
- Filter conducted EMI generated by dc load (small *L* and *C*)


16.1.1 Continuous conduction mode

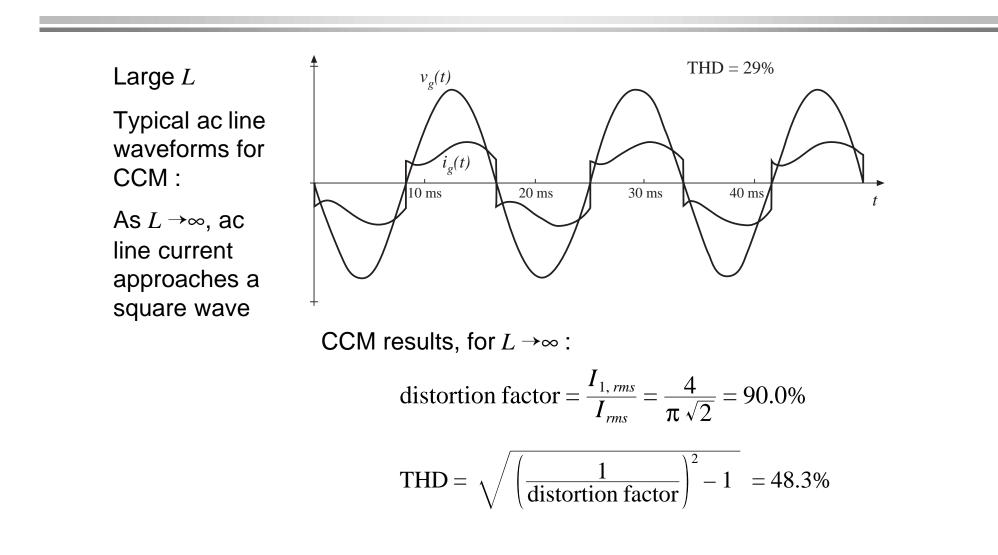

Fundamentals of Power Electronics


Chapter 16: Line-commutated rectifiers

16.1.2 Discontinuous conduction mode

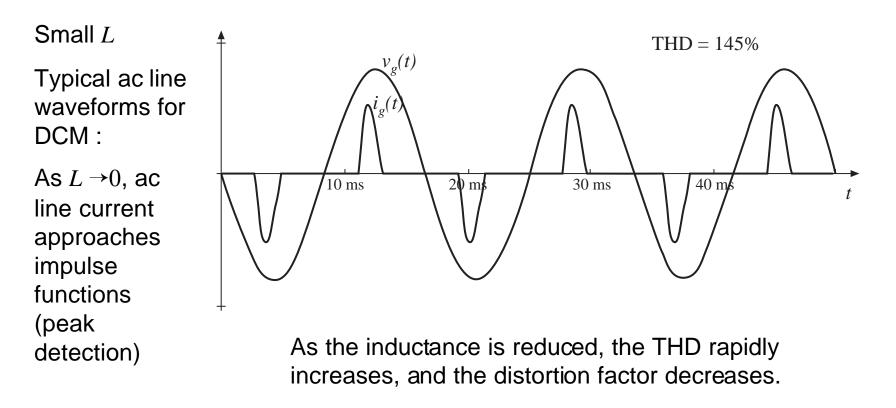

Typical distortion factor of a full-wave rectifier with no inductor is in the range 55% to 65%, and is governed by ac system inductance.

16.1.3 Behavior when *C* is large

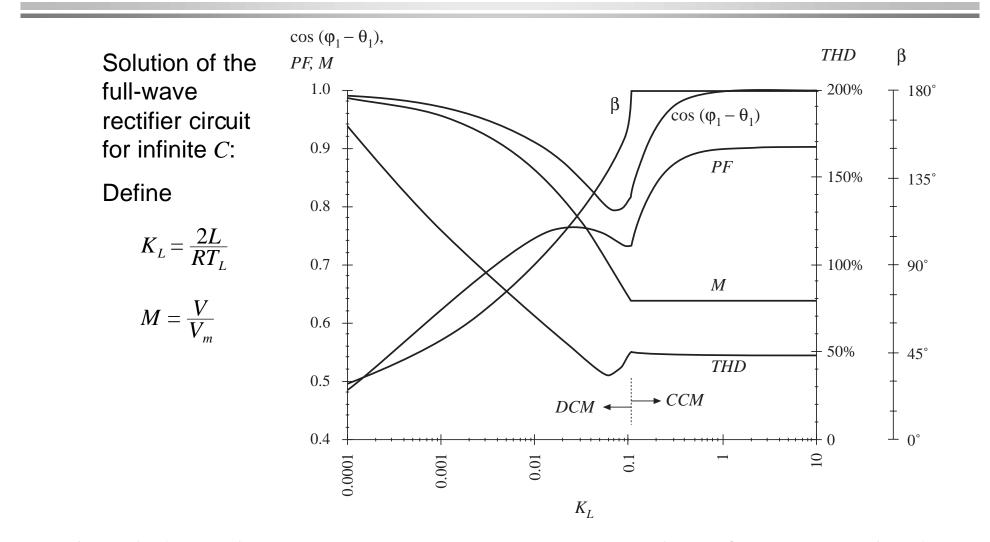


Fundamentals of Power Electronics


Chapter 16: Line-commutated rectifiers

Sometimes the L-C filter is present only to remove high-frequency conducted EMI generated by the dc load, and is not intended to modify the ac line current waveform. If L and C are both zero, then the load resistor is connected directly to the output of the diode bridge, and the ac line current waveform is purely sinusoidal.

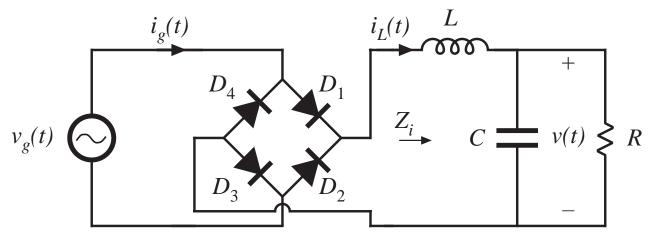
An approximate argument: the *L*-*C* filter has negligible effect on the ac line current waveform provided that the filter input impedance Z_i has zero phase shift at the second harmonic of the ac line frequency, $2f_L$.



Approximate THD

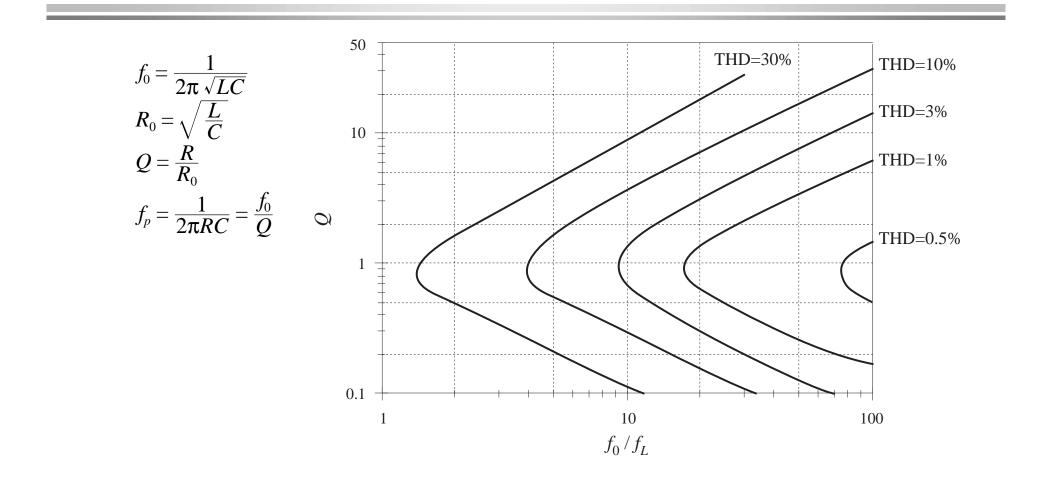

Example

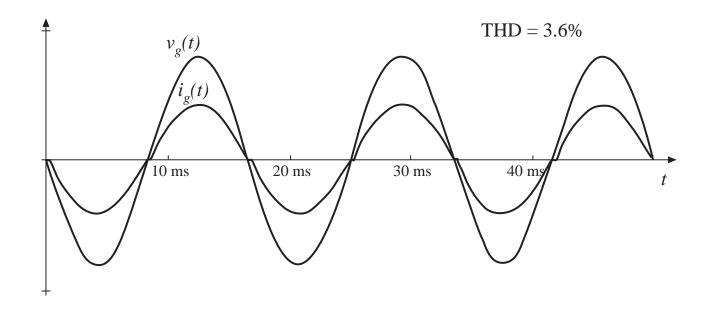


Typical ac line current and voltage waveforms, near the boundary between continuous and discontinuous modes and with small dc filter capacitor. $f_0/f_L = 10$, Q = 1

Fundamentals of Power Electronics

Chapter 16: Line-commutated rectifiers

16.2 The Three-Phase Bridge Rectifier

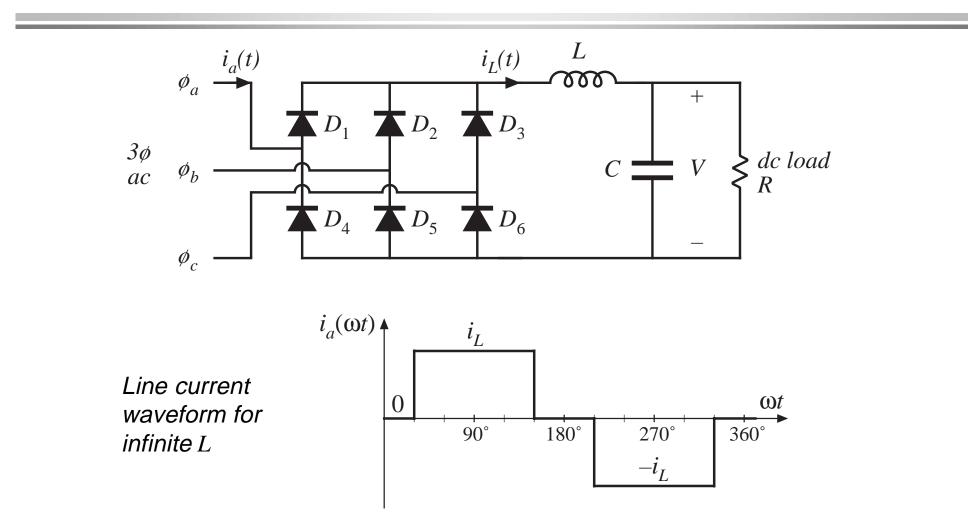


16.2.1 Continuous conduction mode

Fourier series:


$$i_a(t) = \sum_{n=1,5,7,11,\dots}^{\infty} \frac{4}{n\pi} I_L \sin\left(\frac{n\pi}{2}\right) \sin\left(\frac{n\pi}{3}\right) \sin\left(n\omega t\right)$$

- Similar to square wave, but missing triplen harmonics
- THD = 31%
- Distortion factor = $3/\pi = 95.5\%$
- In comparison with single phase case:

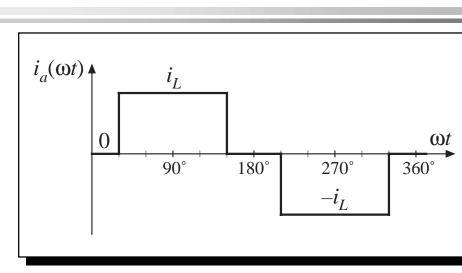the missing 60° of current improves the distortion factor from 90% to 95%, because the triplen harmonics are removed




A typical CCM waveform

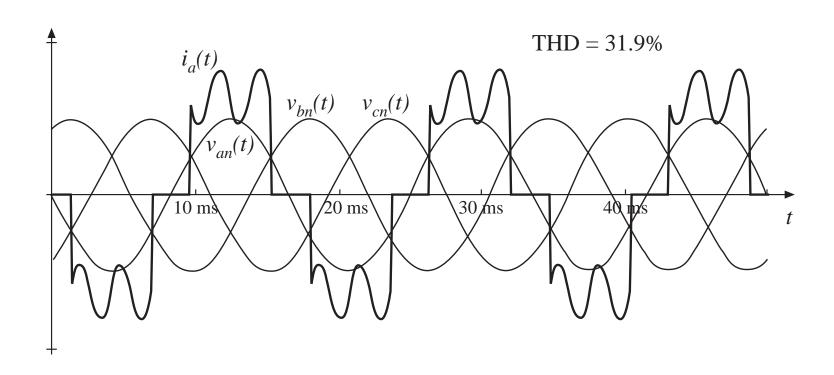

Inductor current contains sixth harmonic ripple (360 Hz for a 60 Hz ac system). This ripple is superimposed on the ac line current waveform, and influences the fifth and seventh harmonic content of $i_a(t)$.

16.2.2 Discontinuous conduction mode

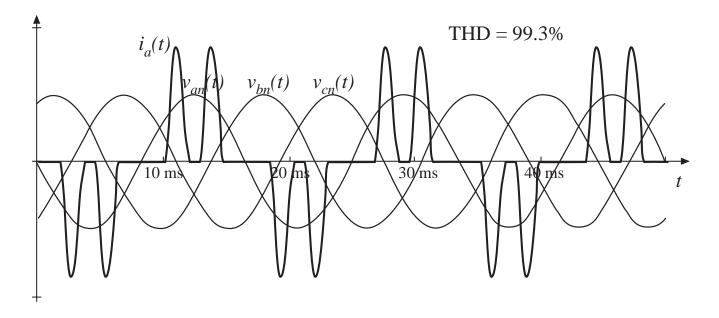


Phase *a* current contains pulses at the positive and negative peaks of the line-to-line voltages $v_{ab}(t)$ and $v_{ac}(t)$. Distortion factor and THD are increased. Distortion factor of the typical waveform illustrated above is 71%.

16.3 Phase control

Replace diodes with SCRs:


Phase control waveforms:

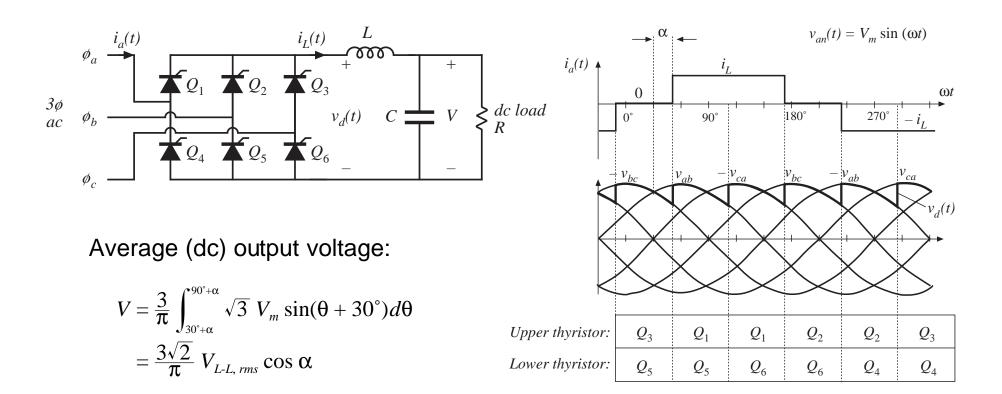

Fundamentals of Power Electronics


Chapter 16: Line-commutated rectifiers

Dc output voltage vs. delay angle α

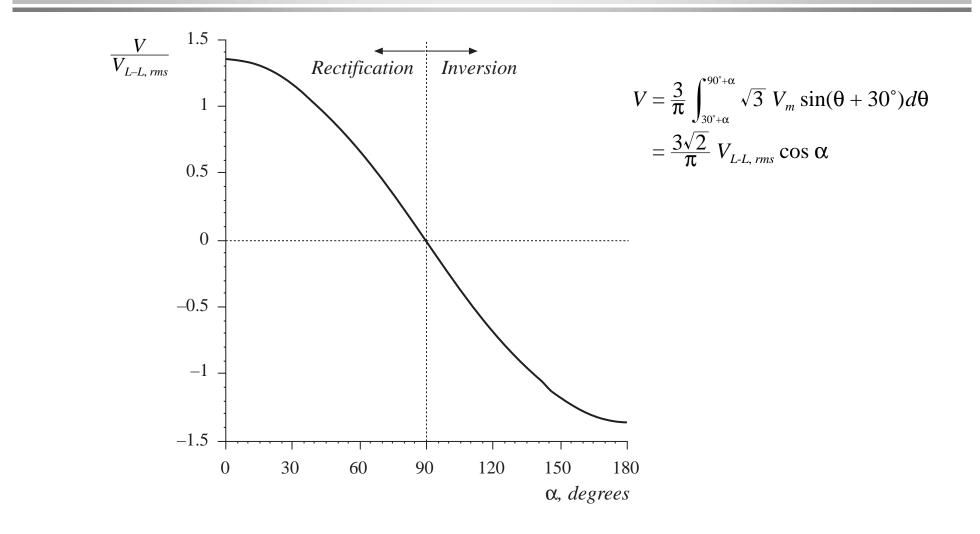

Fundamentals of Power Electronics

16.3.1 Inverter mode

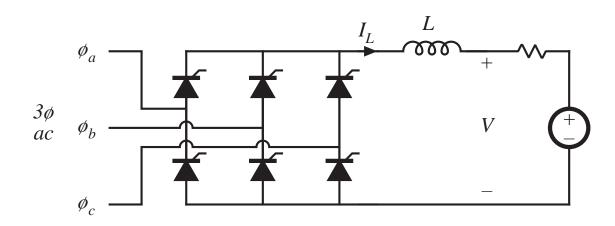

If the load is capable of supplying power, then the direction of power flow can be reversed by reversal of the dc output voltage *V*. The delay angle α must be greater than 90°. The current direction is unchanged.

16.3.2 Harmonics and power factor

Fourier series of ac line current waveform, for large dc-side inductance:

$$i_a(t) = \sum_{n=1,5,7,11,\dots}^{\infty} \frac{4}{n\pi} I_L \sin\left(\frac{n\pi}{2}\right) \sin\left(\frac{n\pi}{3}\right) \sin\left(n\omega t - n\alpha\right)$$

Same as uncontrolled rectifier case, except that waveform is delayed by the angle α . This causes the current to lag, and decreases the displacement factor. The power factor becomes:


power factor =
$$0.955 \left| \cos \left(\alpha \right) \right|$$

When the dc output voltage is small, then the delay angle α is close to 90° and the power factor becomes quite small. The rectifier apparently consumes reactive power, as follows:

$$Q = \sqrt{3} I_{a, rms} V_{L-L, rms} \sin \alpha = I_L \frac{3\sqrt{2}}{\pi} V_{L-L, rms} \sin \alpha$$

Fundamentals of Power Electronics

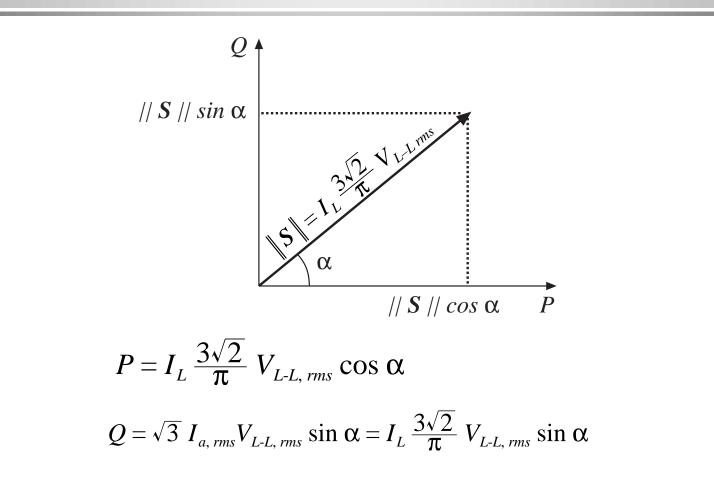
Real and reactive power in controlled rectifier at fundamental frequency



Fundamentals of Power Electronics

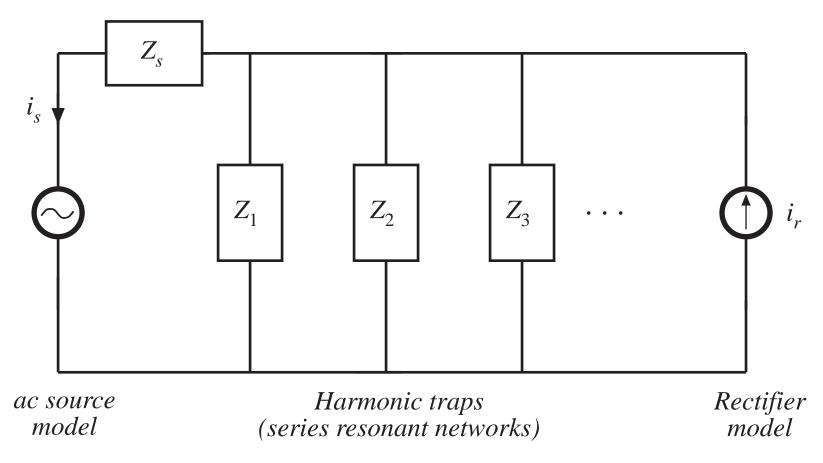
16.4 Harmonic trap filters

A passive filter, having resonant zeroes tuned to the harmonic frequencies




Fundamentals of Power Electronics

Harmonic trap

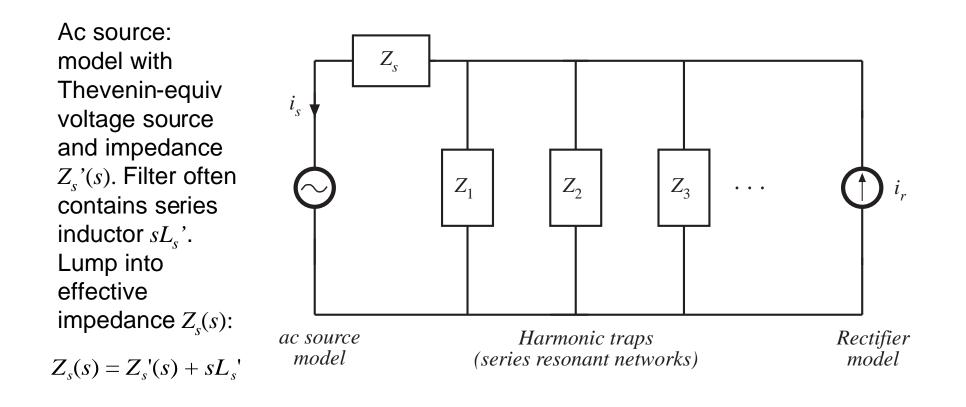


Filter transfer function

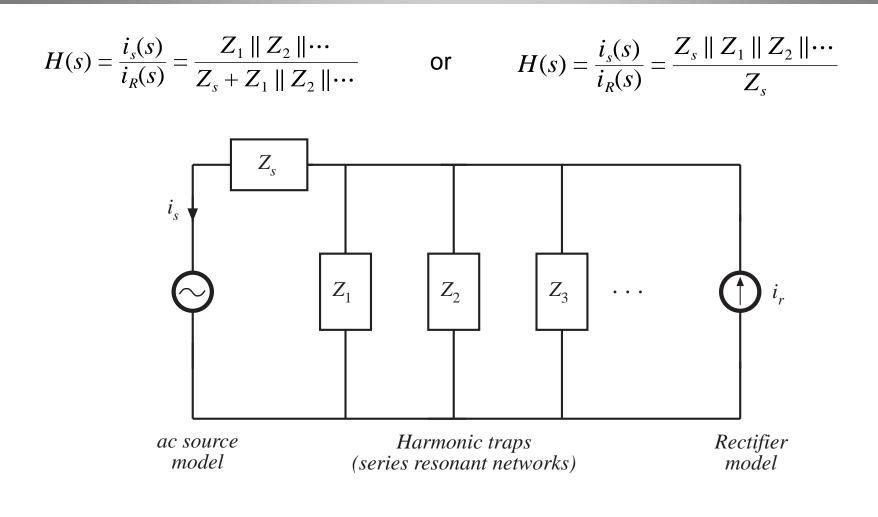


Fundamentals of Power Electronics

Simple example

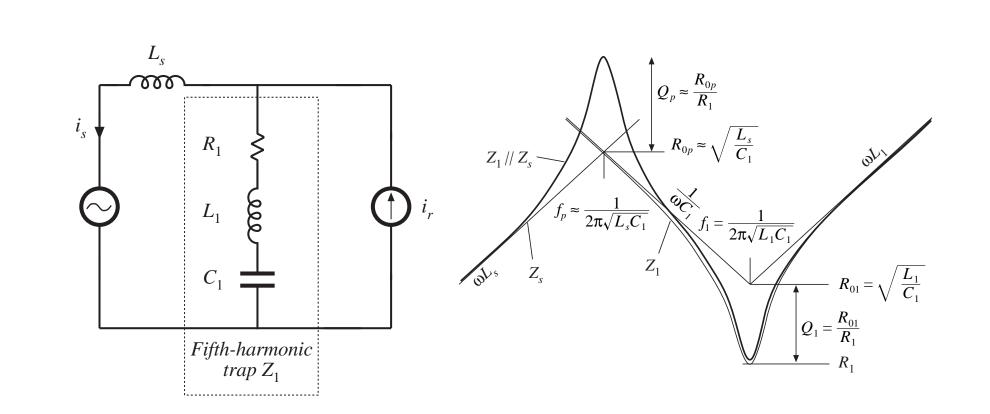


Simple example: transfer function

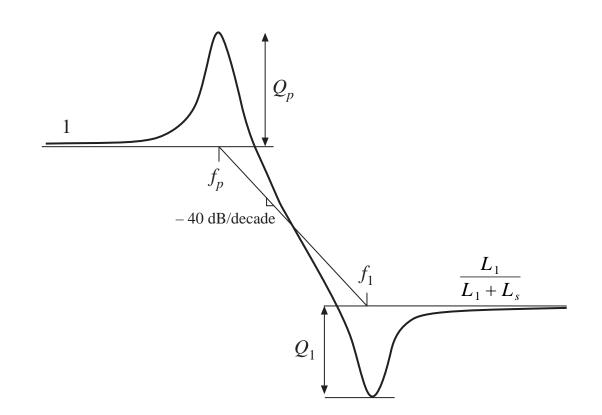


- Series resonance: fifth harmonic trap
- Parallel resonance: C_1 and L_s
- Parallel resonance tends to increase amplitude of third harmonic
- Q of parallel resonance is larger than Q of series resonance


Example 2

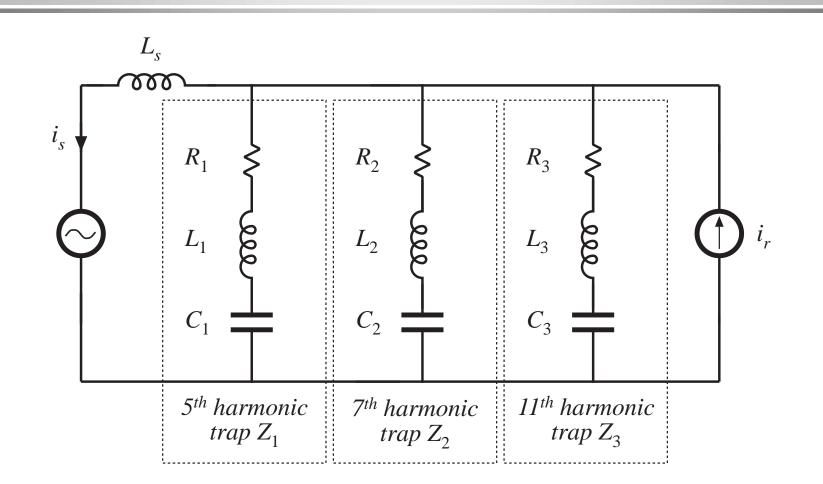


Approximate impedance asymptotes

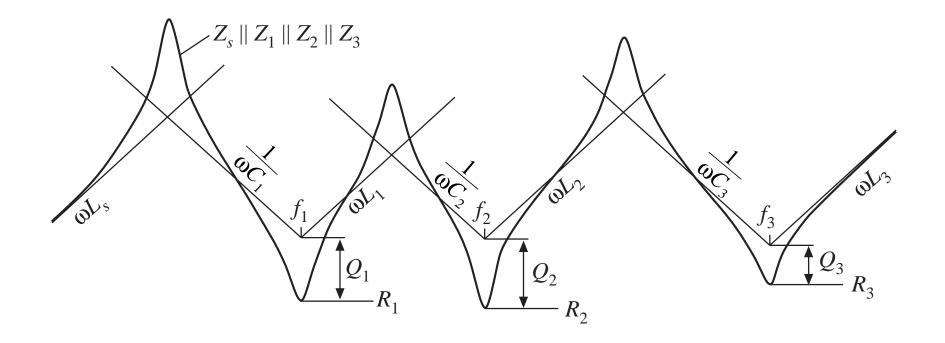


Transfer function asymptotes

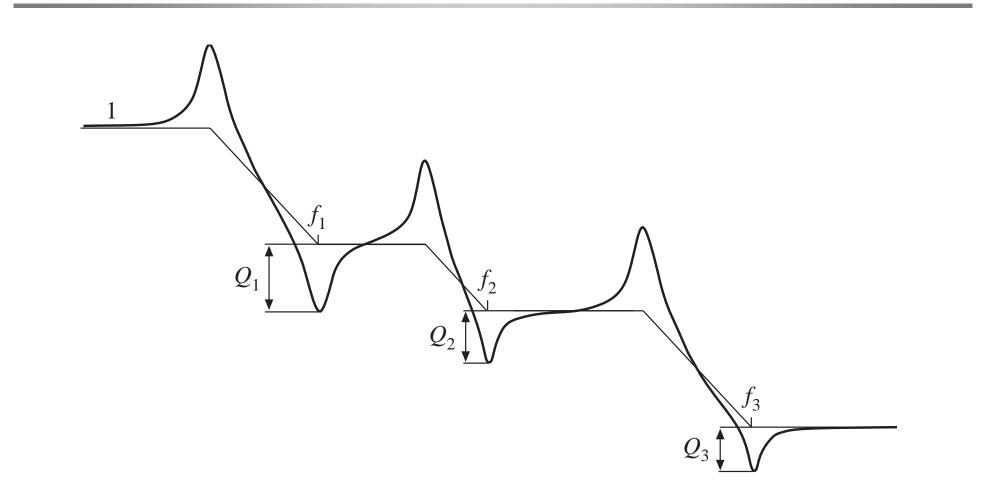

Bypass resistor

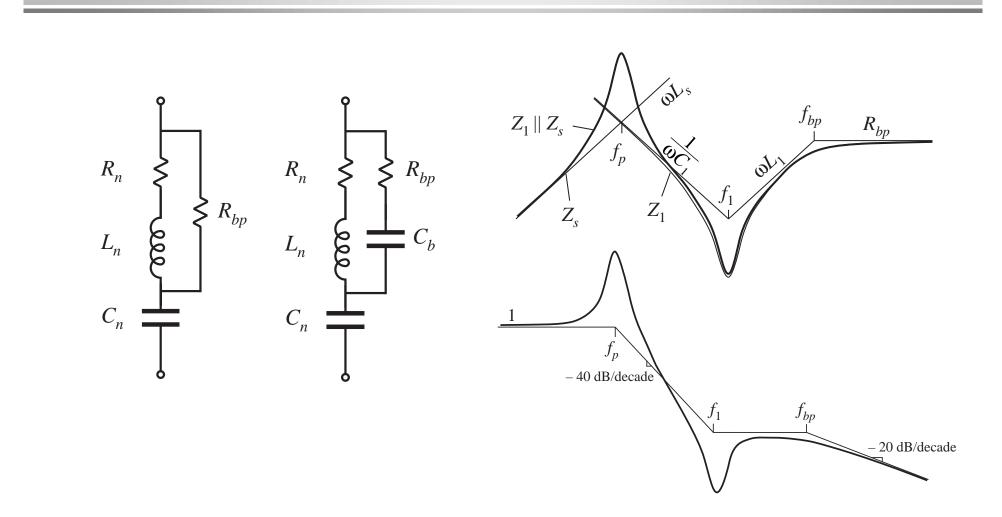

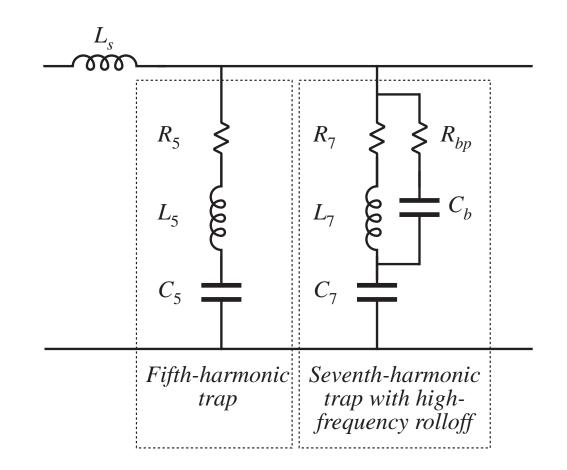
Harmonic trap filter with high-frequency roll-off



Fundamentals of Power Electronics

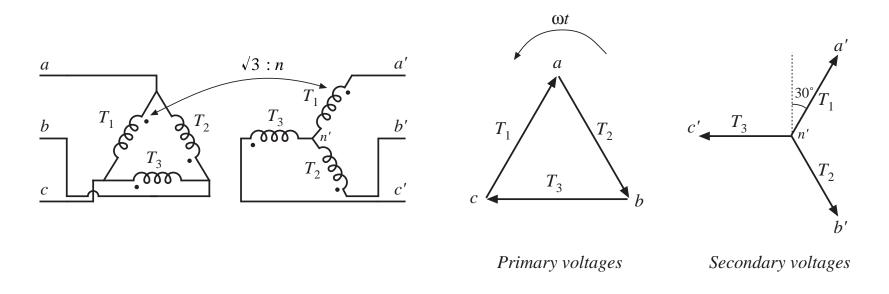
16.5 Transformer connections

Three-phase transformer connections can be used to shift the phase of the voltages and currents
This shifted phase can be used to cancel out the low-order harmonics
Three-phase delta-wye transformer connection shifts phase by 30°:




Fundamentals of Power Electronics

Twelve-pulse rectifier

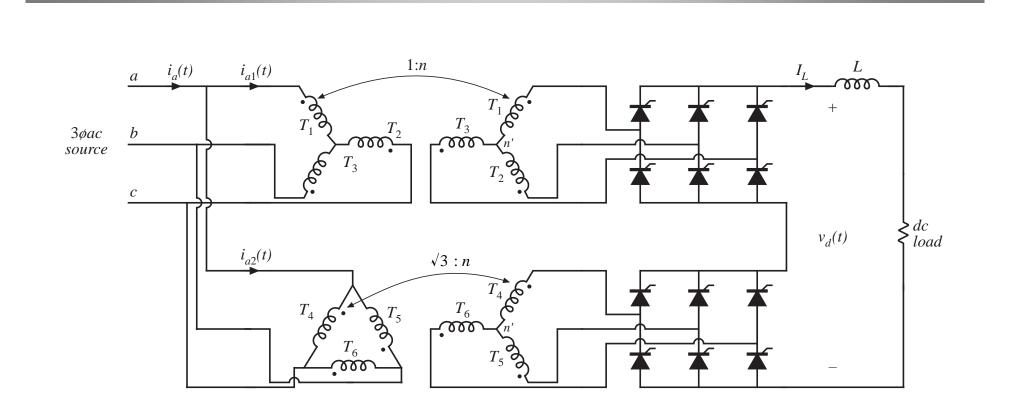

Waveforms of 12 pulse rectifier

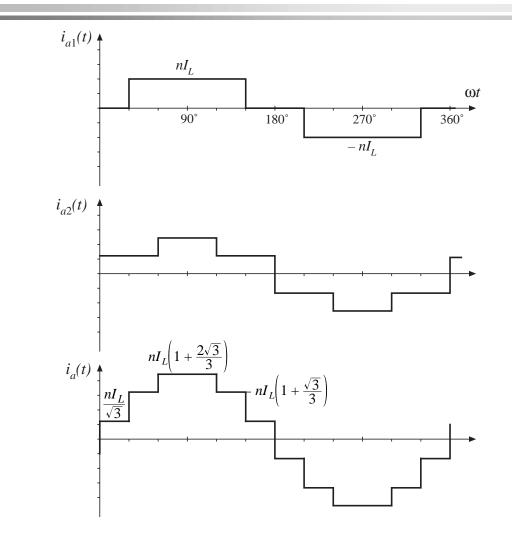

- Ac line current contains 1st, 11th, 13th, 23rd, 25th, etc. These harmonic amplitudes vary as 1/n
- 5th, 7th, 17th, 19th, etc. harmonics are eliminated

Fundamentals of Power Electronics

Rectifiers with high pulse number

Eighteen-pulse rectifier:

- Use three six-pulse rectifiers
- Transformer connections shift phase by 0°, +20°, and -20°
- No 5th, 7th, 11th, 13th harmonics

Twenty-four-pulse rectifier

- Use four six-pulse rectifiers
- Transformer connections shift phase by 0°, 15°, -15°, and 30°
- No 5th, 7th, 11th, 13th, 17th, or 19th harmonics

If *p* is pulse number, then rectifier produces line current harmonics of number $n = pk \pm 1$, with k = 0, 1, 2, ...

Chapter 17 The Ideal Rectifier

- 17.1 Properties of the ideal rectifier
- 17.2 Realization of a near-ideal rectifier
- 17.3 Single-phase converter systems employing ideal rectifiers
- 17.4 RMS values of rectifier waveforms
- 17.5 Ideal three-phase rectifiers

1

17.1 Properties of the ideal rectifier

It is desired that the rectifier present a resistive load to the ac power system. This leads to

- unity power factor
- ac line current has same waveshape as voltage

$$i_{ac}(t) = \frac{v_{ac}(t)}{R_e}$$

$$R_e \text{ is called the emulated resistance}$$


$$i_{ac}(t)$$

$$R_e$$

Control of power throughput


$$P_{av} = \frac{V_{ac,rms}^2}{R_e(v_{control})}$$

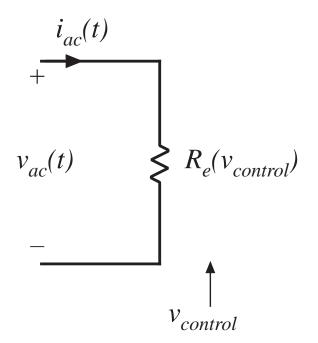Power apparently "consumed" by R_e is actually transferred to rectifier dc output port. To control the amount of output power, it must be possible to adjust the value of R_e .




Output port model

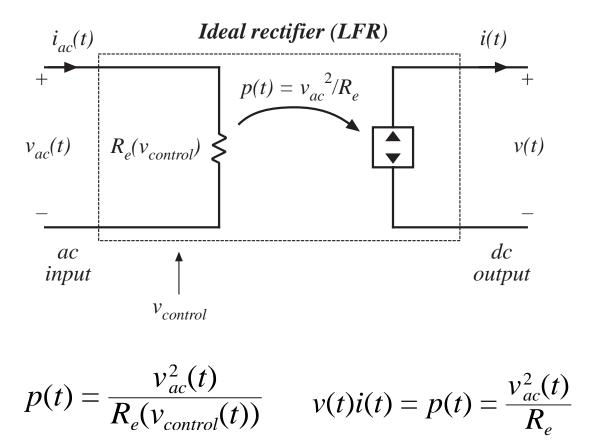The ideal rectifier is lossless and contains no internal energy storage. Hence, the instantaneous input power equals the instantaneous output power. Since the instantaneous power is independent of the dc load characteristics, the output port obeys a power source characteristic.



The dependent power source

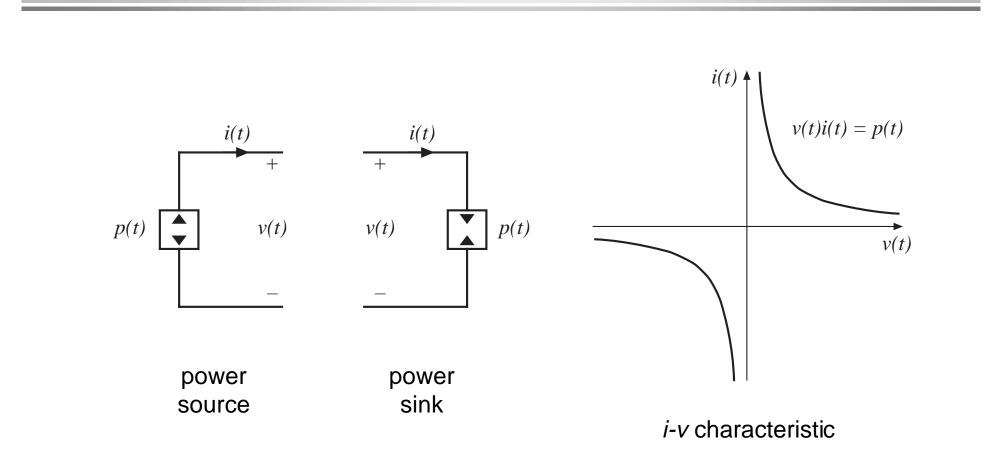

Equations of the ideal rectifier / LFR

Defining equations of the ideal rectifier:

$$i_{ac}(t) = rac{v_{ac}(t)}{R_e(v_{control})}$$

$$v(t)i(t) = p(t)$$


$$p(t) = \frac{v_{ac}^2(t)}{R_e(v_{control}(t))}$$

When connected to a resistive load of value *R*, the input and output rms voltages and currents are related as follows:

$$\frac{V_{rms}}{V_{ac,rms}} = \sqrt{\frac{R}{R_e}}$$


$$\frac{I_{ac,rms}}{I_{rms}} = \sqrt{\frac{R}{R_e}}$$

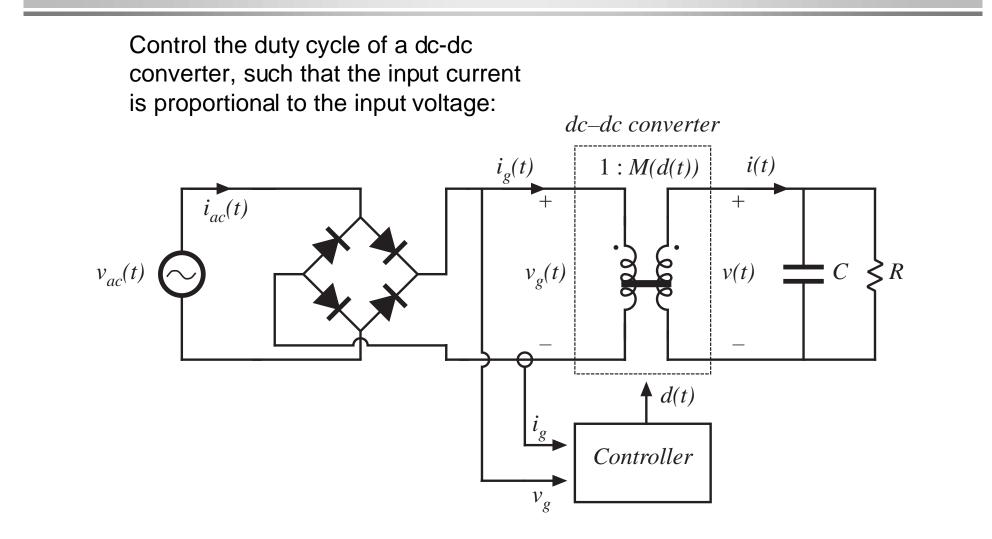17.2 Realization of a near-ideal rectifier



Fundamentals of Power Electronics

Waveforms

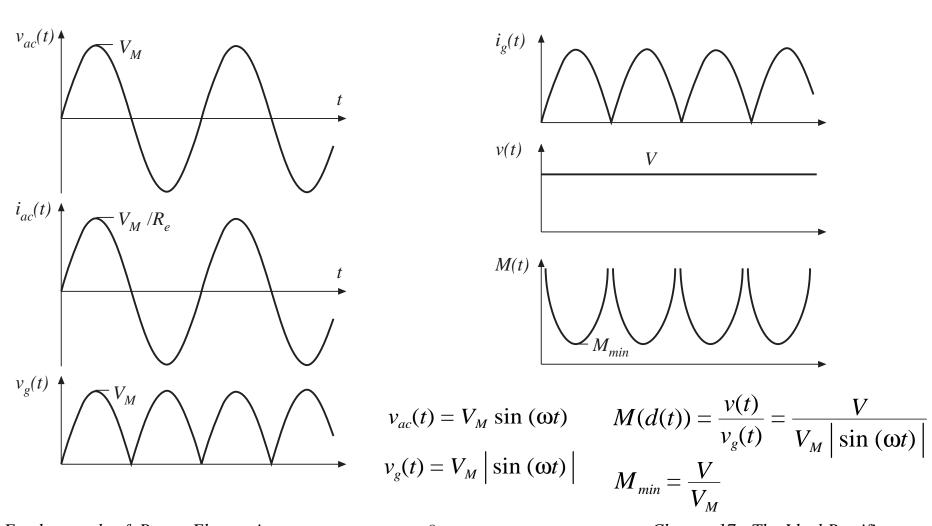

Fundamentals of Power Electronics


Choice of converter

$$M(d(t)) = \frac{v(t)}{v_g(t)} = \frac{V}{V_M \left| \sin(\omega t) \right|} \qquad M(t) \qquad \qquad M($$

- To avoid distortion near line voltage zero crossings, converter should be capable of producing M(d(t)) approaching infinity
- Above expression neglects converter dynamics
- Boost, buck-boost, Cuk, SEPIC, and other converters with similar conversion ratios are suitable
- We will see that the boost converter exhibits lowest transistor stresses. For this reason, it is most often chosen

Boost converter

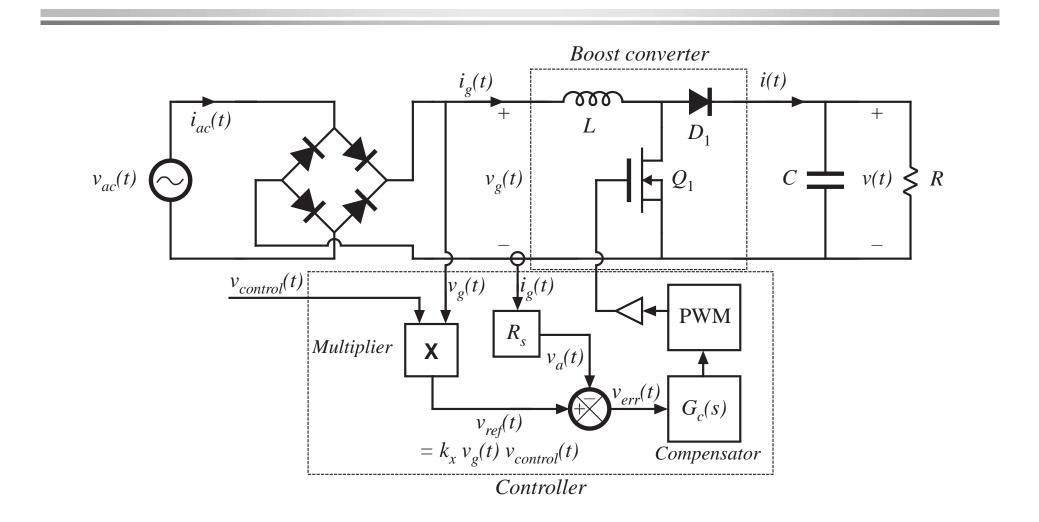with controller to cause input current to follow input voltage



Variation of duty cycle in boost rectifier

$$M(d(t)) = \frac{v(t)}{v_g(t)} = \frac{V}{V_M \left| \sin \left(\omega t \right) \right|}$$

Since $M \ge 1$ in the boost converter, it is required that $V \ge V_M$ If the converter operates in CCM, then

$$M(d(t)) = \frac{1}{1 - d(t)}$$

The duty ratio should therefore follow

$$d(t) = 1 - \frac{v_g(t)}{V}$$
 in CCM

Fundamentals of Power Electronics

CCM/DCM boundary, boost rectifier

Inductor current ripple is

$$\Delta i_g(t) = \frac{v_g(t)d(t)T_s}{2L}$$

Low-frequency (average) component of inductor current waveform is

$$\left\langle i_g(t) \right\rangle_{T_s} = \frac{v_g(t)}{R_e}$$

The converter operates in CCM when

$$\left\langle i_g(t) \right\rangle_{T_s} > \Delta i_g(t) \implies d(t) < \frac{2L}{R_e T_s}$$

Substitute CCM expression for d(t):

$$R_e < rac{2L}{T_s \left(1 - rac{v_g(t)}{V}
ight)}$$
 for CCM

Fundamentals of Power Electronics

CCM/DCM boundary

$$R_e < rac{2L}{T_s \left(1 - rac{v_g(t)}{V}
ight)}$$
 for CCM

Note that $v_g(t)$ varies with time, between 0 and V_M . Hence, this equation may be satisfied at some points on the ac line cycle, and not at others. The converter always operates in CCM provided that

$$R_e < \frac{2L}{T_s}$$

The converter always operates in DCM provided that

$$R_e > \frac{2L}{T_s \left(1 - \frac{V_M}{V}\right)}$$

For R_e between these limits, the converter operates in DCM when $v_g(t)$ is near zero, and in CCM when $v_g(t)$ approaches V_M .


Fundamentals of Power Electronics

Static input characteristics of the boost converter

A plot of input current $i_g(t)$ vs input voltage $v_g(t)$, for various duty cycles d(t). In CCM, the boost converter equilibrium equation is

$$\frac{v_g(t)}{V} = 1 - d(t)$$

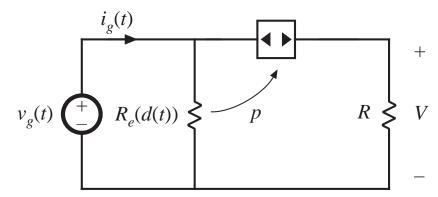The input characteristic in DCM is found by solution of the averaged DCM model (Fig. 10.12(b)):



Beware! This DCM $R_e(d)$ from Chapter 10 is not the same as the rectifier emulated resistance $R_e = v_g/i_g$

Fundamentals of Power Electronics

Solve for input current:

$$i_g(t) = \frac{v_g(t)}{R_e(d(t))} + \frac{p(t)}{V - v_g(t)}$$

with $p(t) = \frac{v_g^2(t)}{R_e(d(t))}$
 $R_e(d(t)) = \frac{2L}{d^2(t)T_s}$

Static input characteristics of the boost converter


Now simplify DCM current expression, to obtain

$$\frac{2L}{VT_s} i_g(t) \left(1 - \frac{v_g(t)}{V}\right) = d^2(t) \frac{v_g(t)}{V}$$

CCM/DCM mode boundary, in terms of $v_g(t)$ and $i_g(t)$:

$$\frac{2L}{VT_s} i_g(t) > \left(\frac{v_g(t)}{V}\right) \left(1 - \frac{v_g(t)}{V}\right)$$

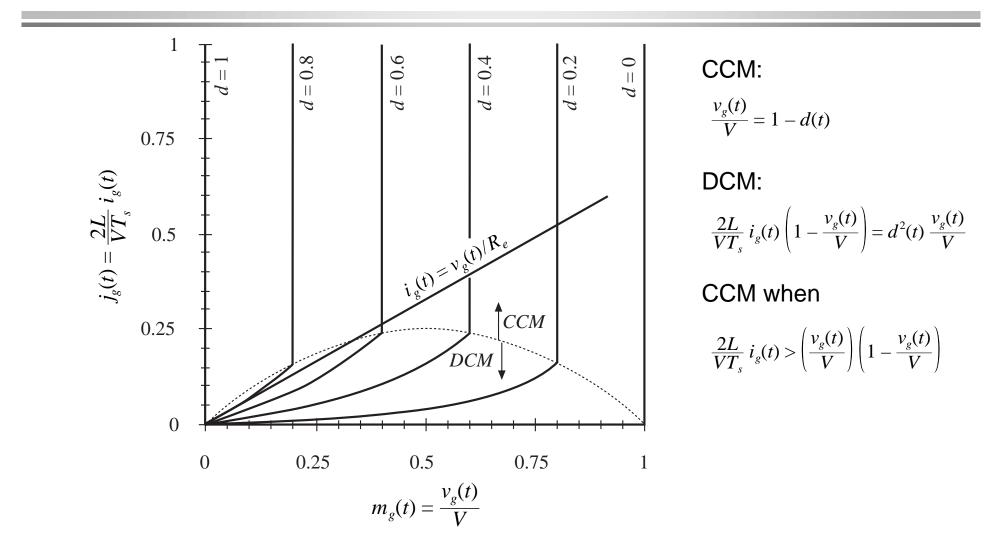Boost input characteristics with superimposed resistive characteristic



Fundamentals of Power Electronics

R_e of the multiplying (average current) controller

Boost converter $i_g(t)$ i(t)200 + + $i_{ac}(t)$ L D_1 v(t) $v_{ac}(t)$ $v_{g}(t)$ C Q_1 $v_g(t)$ $v_{control}(t)$ (t)PWM R_{s} Multiplier v(t $G_c(s)$ $v_{ref}(t)$ $= k_x v_g(t) v_{control}(t)$ **Compensator** Controller

Solve circuit to find R_e :

Current sensor gain

$$v_a(t) = i_g(t)R_s$$

when the error signal is small,

$$v_a(t) \approx v_{ref}(t)$$

multiplier equation

$$v_{ref}(t) = k_x v_g(t) v_{control}(t)$$

then
$$R_e$$
 is


$$R_e = \frac{v_g(t)}{i_g(t)} = \frac{\left(\frac{v_{ref}(t)}{k_x v_{control}(t)}\right)}{\left(\frac{v_a(t)}{R_s}\right)}$$

simplify:

 $\leq R$

$$R_e(v_{control}(t)) = \frac{R_s}{k_x v_{control}(t)}$$

Low frequency system model

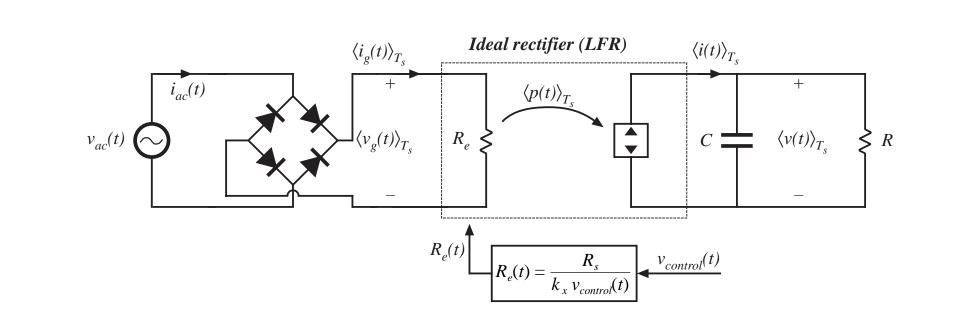

$$R_e(v_{control}(t)) = \frac{R_s}{k_x v_{control}(t)}$$

This model also applies to other converters that are controlled in the same manner, including buck-boost, Cuk, and SEPIC.

Open-loop DCM approach

We found in Chapter 10 that the buck-boost, SEPIC, and Cuk converters, when operated open-loop in DCM, inherently behave as loss-free resistors. This suggests that they could also be used as near-ideal rectifiers, without need for a multiplying controller.

Advantage: simple control

Disadvantages: higher peak currents, larger input current EMI

Like other DCM applications, this approach is usually restricted to low power (< 200W).

The boost converter can also be operated in DCM as a low harmonic rectifier. Input characteristic is

$$\left\langle i_g(t) \right\rangle_{T_s} = \frac{v_g(t)}{R_e} + \frac{v_g^2(t)}{R_e \left(v(t) - v_g(t) \right)}$$

Input current contains harmonics. If v is sufficiently greater than v_g , then harmonics are small.

Fundamentals of Power Electronics

17.3 Single-phase converter systems containing ideal rectifiers

- It is usually desired that the output voltage v(t) be regulated with high accuracy, using a wide-bandwidth feedback loop
- For a given constant load characteristic, the instantaneous load current and power are then also constant:

$$p_{load}(t) = v(t)i(t) = VI$$

 The instantaneous input power of a single-phase ideal rectifier is not constant:

$$p_{ac}(t) = v_g(t)i_g(t)$$

with

$$v_g(t) = V_M \left| \sin (\omega t) \right| \qquad \qquad i_g(t) = \frac{v_g(t)}{R_e}$$

so
$$p_{ac}(t) = \frac{V_M^2}{R_e} \sin^2\left(\omega t\right) = \frac{V_M^2}{2R_e} \left(1 - \cos\left(2\omega t\right)\right)$$

Fundamentals of Power Electronics


Power flow in single-phase ideal rectifier system

- Ideal rectifier is lossless, and contains no internal energy storage.
- Hence instantaneous input and output powers must be equal
- An energy storage element must be added
- Capacitor energy storage: instantaneous power flowing into capacitor is equal to difference between input and output powers:


$$p_{C}(t) = \frac{dE_{C}(t)}{dt} = \frac{d\left(\frac{1}{2}Cv_{C}^{2}(t)\right)}{dt} = p_{ac}(t) - p_{load}(t)$$

Energy storage capacitor voltage must be allowed to vary, in accordance with this equation

Capacitor energy storage in 1ø system

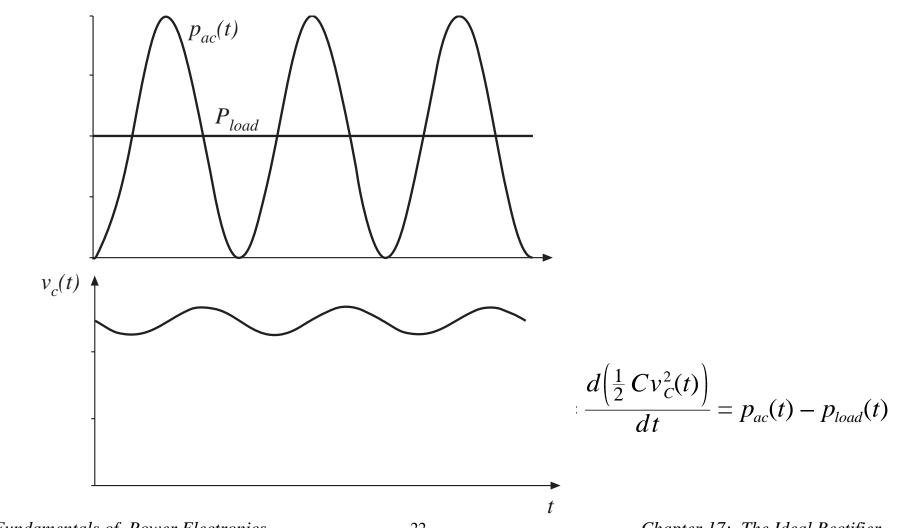

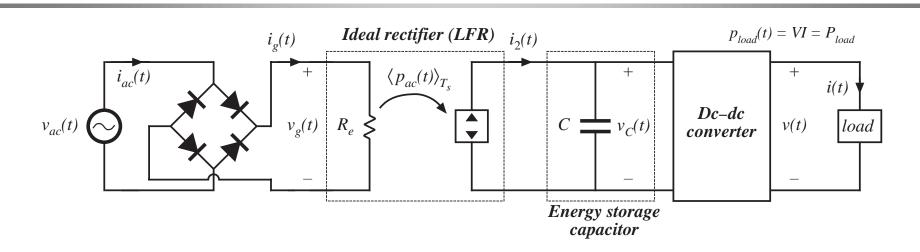Single-phase system with internal energy storage



Energy storage capacitor voltage $v_C(t)$ must be independent of input and output voltage waveforms, so that it can vary according to

$$\frac{d\left(\frac{1}{2}Cv_{c}^{2}(t)\right)}{dt} = p_{ac}(t) - p_{load}(t)$$

Fundamentals of Power Electronics

This system is capable of

- Wide-bandwidth control of output voltage
- Wide-bandwidth control of input current waveform
- Internal independent energy storage

Hold up time

Internal energy storage allows the system to function in other situations where the instantaneous input and output powers differ.

A common example: continue to supply load power in spite of failure of ac line for short periods of time.

Hold up time: the duration which the dc output voltage v(t) remains regulated after $v_{ac}(t)$ has become zero

A typical hold-up time requirement: supply load for one complete missing ac line cycle, or 20msec in a 50Hz system

During the hold-up time, the load power is supplied entirely by the energy storage capacitor

Energy storage element

Instead of a capacitor, and inductor or higher-order LC network could store the necessary energy.

But, inductors are not good energy-storage elements

Example

100V 100µF capacitor

100A 100 μ H inductor

each store 1 Joule of energy

But the capacitor is considerably smaller, lighter, and less expensive

So a single big capacitor is the best solution

Inrush current

A problem caused by the large energy storage capacitor: the large inrush current observed during system startup, necessary to charge the capacitor to its equilibrium value.

Boost converter is not capable of controlling this inrush current.

Even with d = 0, a large current flows through the boost converter diode to the capacitor, as long as $v(t) < v_g(t)$.

Additional circuitry is needed to limit the magnitude of this inrush current.

Converters having buck-boost characteristics are capable of controlling the inrush current. Unfortunately, these converters exhibit higher transistor stresses.

Universal input

The capability to operate from the ac line voltages and frequencies found everywhere in the world:

50Hz and 60Hz

Nominal rms line voltages of 100V to 260V:

100V, 110V, 115V, 120V, 132V, 200V, 220V, 230V, 240V, 260V

Regardless of the input voltage and frequency, the near-ideal rectifier produces a constant nominal dc output voltage. With a boost converter, this voltage is 380 or 400V.

Low-frequency model of dc-dc converter


Dc-dc converter produces well-regulated dc load voltage V.

Load therefore draws constant current *I*.


Load power is therefore the constant value $P_{load} = VI$.

To the extent that dc-dc converter losses can be neglected, then dc-dc converter input power is P_{load} , regardless of capacitor voltage $v_c(t)$.

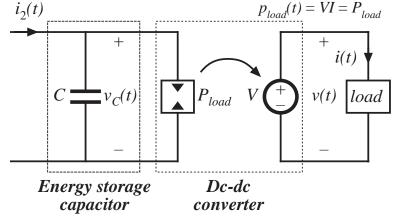Dc-dc converter input port behaves as a power sink. A low frequency converter model is i(t) = VI = P




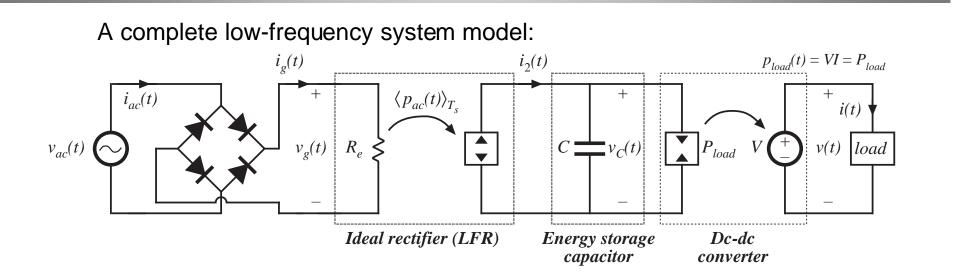Low-frequency energy storage process, 1ø system



- Difference between rectifier output power and dc-dc converter input power flows into capacitor
- In equilibrium, average rectifier and load powers must be equal
- But the system contains no mechanism to accomplish this
- An additional feeback loop is necessary, to adjust R_e such that the rectifier average power is equal to the load power

Obtaining average power balance

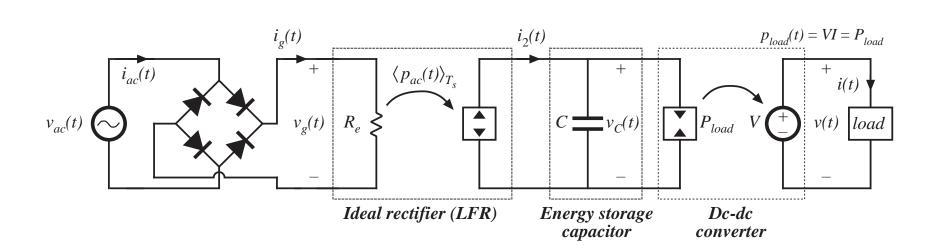


If the load power exceeds the average rectifier power, then there is a net discharge in capacitor energy and voltage over one ac line cycle.

There is a net increase in capacitor charge when the reverse is true.

This suggests that rectifier and load powers can be balanced by regulating the energy storage capacitor voltage.

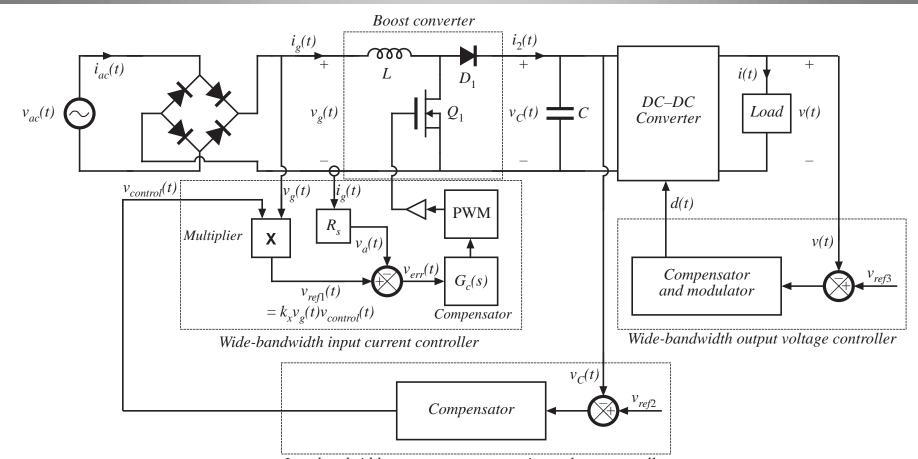A complete 1ø system containing three feedback loops




Low-bandwidth energy-storage capacitor voltage controller

Bandwidth of capacitor voltage loop

- The energy-storage-capacitor voltage feedback loop causes the dc component of $v_c(t)$ to be equal to some reference value
- Average rectifier power is controlled by variation of R_e .
- R_e must not vary too quickly; otherwise, ac line current harmonics are generated
- Extreme limit: loop has infinite bandwidth, and $v_c(t)$ is perfectly regulated to be equal to a constant reference value
 - Energy storage capacitor voltage then does not change, and this capacitor does not store or release energy
 - Instantaneous load and ac line powers are then equal
 - Input current becomes


$$\dot{i}_{ac}(t) = \frac{p_{ac}(t)}{v_{ac}(t)} = \frac{p_{load}(t)}{v_{ac}(t)} = \frac{P_{load}}{V_M \sin\left(\omega t\right)}$$

Input current waveform, extreme limit

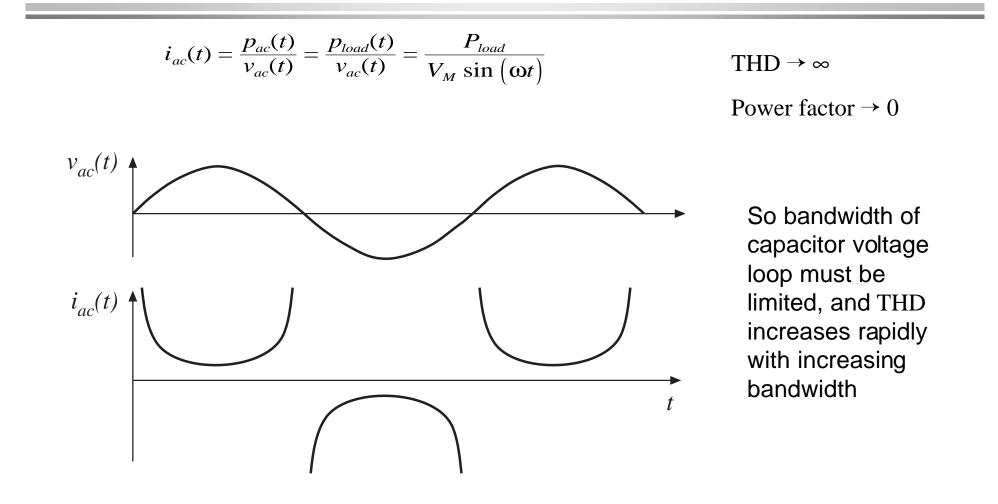

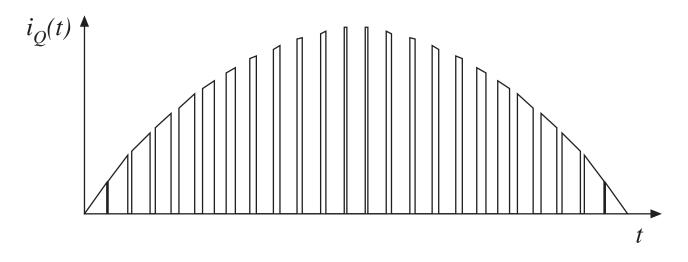17.4 RMS values of rectifier waveforms

Doubly-modulated transistor current waveform, boost rectifier:




Computation of rms value of this waveform is complex and tedious

Approximate here using double integral

Generate tables of component rms and average currents for various rectifier converter topologies, and compare

RMS transistor current

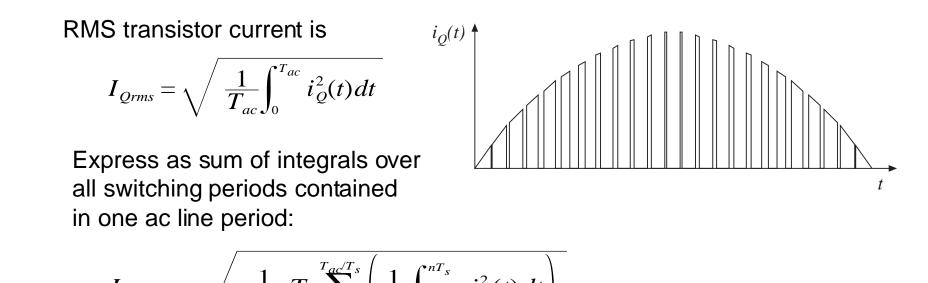

$$I_{Qrms} = \sqrt{\frac{1}{T_{ac}} T_s \sum_{n=1}^{T_{ac}/T_s} \left(\frac{1}{T_s} \int_{(n-1)T_s}^{n_s} i_Q^2(t) dt\right)}$$

Quantity in parentheses is the value of i_Q^2 , averaged over the n^{th} switching period.

Approximation of RMS expression

$$I_{Qrms} = \sqrt{\frac{1}{T_{ac}} T_s \sum_{n=1}^{T_{ac}/T_s} \left(\frac{1}{T_s} \int_{(n-1)T_s}^{nT_s} i_Q^2(t) dt\right)}$$

When $T_s \ll T_{ac}$, then the summation can be approximated by an integral, which leads to the double-average:

$$I_{Qrms} \approx \sqrt{\frac{1}{T_{ac}} \lim_{T_s \to 0} \left[T_s \sum_{n=1}^{T_{ac}/T_s} \left(\frac{1}{T_s} \int_{(n-1)T_s}^{nT_s} i_Q^2(\tau) d\tau \right) \right]}$$
$$= \sqrt{\frac{1}{T_{ac}} \int_{0}^{T_{ac}} \frac{1}{T_s} \int_{t}^{t+T_s} i_Q^2(\tau) d\tau dt}$$
$$= \sqrt{\left\langle \left\langle i_Q^2(t) \right\rangle_{T_s} \right\rangle_{T_{ac}}}$$

Fundamentals of Power Electronics

17.4.1 Boost rectifier example

For the boost converter, the transistor current $i_Q(t)$ is equal to the input current when the transistor conducts, and is zero when the transistor is off. The average over one switching period of $i_Q^2(t)$ is therefore

$$\left\langle i_{Q}^{2} \right\rangle_{T_{s}} = \frac{1}{T_{s}} \int_{t}^{t+T_{s}} i_{Q}^{2}(t) dt$$

= $d(t) i_{ac}^{2}(t)$

If the input voltage is

$$v_{ac}(t) = V_M \left| \sin \omega t \right|$$

then the input current will be given by

$$i_{ac}(t) = \frac{V_M}{R_e} \left| \sin \omega t \right|$$

and the duty cycle will ideally be

$$\frac{V}{v_{ac}(t)} = \frac{1}{1 - d(t)}$$

(this neglects converter dynamics)

Fundamentals of Power Electronics

Boost rectifier example

Duty cycle is therefore

$$d(t) = 1 - \frac{V_M}{V} \left| \sin \omega t \right|$$

Evaluate the first integral:

$$\left\langle i_{Q}^{2} \right\rangle_{T_{s}} = \frac{V_{M}^{2}}{R_{e}^{2}} \left(1 - \frac{V_{M}}{V} \left| \sin \omega t \right| \right) \sin^{2} \left(\omega t \right)$$

Now plug this into the RMS formula:

$$I_{Qrms} = \sqrt{\frac{1}{T_{ac}} \int_{0}^{T_{ac}} \left\langle i_{Q}^{2} \right\rangle_{T_{s}} dt}$$
$$= \sqrt{\frac{1}{T_{ac}} \int_{0}^{T_{ac}} \frac{V_{M}^{2}}{R_{e}^{2}} \left(1 - \frac{V_{M}}{V} \left|\sin \omega t\right|\right) \sin^{2} (\omega t) dt}$$
$$I_{Qrms} = \sqrt{\frac{2}{T_{ac}} \frac{V_{M}^{2}}{R_{e}^{2}} \int_{0}^{T_{ac}/2} \left(\sin^{2} (\omega t) - \frac{V_{M}}{V} \sin^{3} (\omega t)\right) dt}$$

Fundamentals of Power Electronics

Integration of powers of $\sin \theta$ over complete half-cycle

	n	$\frac{1}{\pi}\int_0^{\pi} \sin^n\left(\theta\right)d\theta$
(1	$\frac{2}{\pi}$
$\frac{1}{\pi} \int_0^{\pi} \sin^n(\theta) d\theta = \begin{cases} \frac{2}{\pi} \frac{2 \cdot 4 \cdot 6 \cdots (n-1)}{1 \cdot 3 \cdot 5 \cdots n} & \text{if } n \text{ is odd} \\ \frac{1 \cdot 3 \cdot 5 \cdots (n-1)}{2 \cdot 4 \cdot 6 \cdots n} & \text{if } n \text{ is even} \end{cases}$	2	$\frac{1}{2}$
	3	$\frac{4}{3\pi}$
	4	$\frac{3}{8}$
	5	$\frac{16}{15\pi}$
	6	$\frac{15}{48}$

Boost example: Transistor RMS current

$$I_{Qrms} = \frac{V_M}{\sqrt{2}R_e} \sqrt{1 - \frac{8}{3\pi} \frac{V_M}{V}} = I_{ac rms} \sqrt{1 - \frac{8}{3\pi} \frac{V_M}{V}}$$

Transistor RMS current is minimized by choosing V as small as possible: $V = V_M$. This leads to

$$I_{Qrms} = 0.39 I_{ac rms}$$

When the dc output voltage is not too much greater than the peak ac input voltage, the boost rectifier exhibits very low transistor current. Efficiency of the boost rectifier is then quite high, and 95% is typical in a 1kW application.

Table of rectifier current stresses for various topologies

	ms	Average	Peak	
CCM boost				
Transistor	$I_{acrms}\sqrt{1-rac{8}{3\pi}rac{V_M}{V}}$	$I_{acrms}rac{2\sqrt{2}}{\pi}\left(1-rac{\pi}{8}rac{V_M}{V} ight)$	$I_{acrms}\sqrt{2}$	
Diode	$I_{dc} \sqrt{rac{16}{3\pi} rac{V}{V_M}}$	I_{dc}	$2 \ I_{dc} rac{V}{V_M}$	
Inductor	I _{ac rms}	$I_{ac rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac rms} \sqrt{2}$	
CCM flyback, with <i>n</i> :1	isolation transformer and input	filter		
Transistor, xfmr primary	$I_{ac\ rms}\sqrt{1+rac{8}{3\pi}rac{V_M}{nV}}$	$I_{ac rms} \frac{2\sqrt{2}}{\pi}$	$I_{acrms}\sqrt{2}\left(1+\frac{1}{2}\right)$	
L_1	I _{ac rms}	$I_{ac rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac rms} \sqrt{2}$	
C_1	$I_{ac\ rms}\sqrt{rac{8}{3\pi}rac{V_M}{nV}}$	0	$I_{acrms}\sqrt{2}\max\left(1,\frac{V}{n}\right)$	
Diode, xfmr secondary	$I_{dc} \sqrt{rac{3}{2} + rac{16}{3\pi} rac{nV}{V_M}}$	I_{dc}	$2I_{dc}\left(1+rac{nV}{V_M} ight)$	

 Table 17.2
 Summary of rectifier current stresses for several converter topologies

Table of rectifier current stresses continued

CCM SEPIC, nonisolat		$2\sqrt{2}$	
Transistor	$I_{ac\ rms} \sqrt{1+rac{8}{3\pi}rac{V_M}{V}}$	$I_{ac rms} \frac{2\sqrt{2}}{\pi}$	$I_{acrms}\sqrt{2}\left(1+rac{V_l}{V}\right)$
L_1	I _{ac rms}	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac rms} \sqrt{2}$
C_1	$I_{ac\ rms}\sqrt{rac{8}{3\pi}rac{V_M}{V}}$	0	$I_{acrms} \max\left(1, \frac{V_l}{V}\right)$
L_2	$I_{ac rms} \frac{V_M}{V} \frac{\sqrt{3}}{2}$	$rac{I_{ac\ rms}}{\sqrt{2}}rac{V_M}{V}$	$I_{ac\ rms} rac{V_M}{V} \sqrt{2}$
Diode	$I_{dc} \sqrt{\frac{3}{2} + \frac{16}{3\pi} \frac{V}{V_M}}$	I_{dc}	$2I_{dc}\left(1+rac{V}{V_M} ight)$
CCM SEPIC, with <i>n</i> :1	isolation transformer		
transistor	$I_{ac\ rms}\sqrt{1+rac{8}{3\pi}rac{V_M}{nV}}$	$I_{acrms} \frac{2\sqrt{2}}{\pi}$	$I_{acrms}\sqrt{2}\left(1+\frac{V_l}{nV}\right)$
L_1	I _{ac rms}	$I_{ac rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac rms} \sqrt{2}$
<i>C</i> ₁ , xfmr primary	$I_{acrms}\sqrt{rac{8}{3\pi}rac{V_M}{nV}}$	0	$I_{acrms}\sqrt{2}\max\left(1,\frac{1}{2}\right)$
Diode, xfmr secondary	$I_{dc} \sqrt{\frac{3}{2} + \frac{16}{3\pi} \frac{nV}{V_M}}$	I_{dc}	$2I_{dc}\left(1+rac{nV}{V_M} ight)$
•	es, $\frac{I_{acrms}}{I_{dc}} = \sqrt{2} \frac{V}{V_M}$, ac input volt	$tage = V_M \sin(\omega t)$	
dc output volta	-ac M		

Comparison of rectifier topologies

Boost converter

- Lowest transistor rms current, highest efficiency
- Isolated topologies are possible, with higher transistor stress
- No limiting of inrush current
- Output voltage must be greater than peak input voltage

Buck-boost, SEPIC, and Cuk converters

- Higher transistor rms current, lower efficiency
- Isolated topologies are possible, without increased transistor stress
- Inrush current limiting is possible
- Output voltage can be greater than or less than peak input voltage

Comparison of rectifier topologies


1kW, 240Vrms example. Output voltage: 380Vdc. Input current: 4.2Arms

Converter	Transistor rms current	Transistor voltage	Diode rms current	Transistor rms current, 120V	Diode rms current, 120V
Boost	2 A	380 V	3.6 A	6.6 A	5.1 A
Nonisolated SEPIC	5.5 A	719 V	4.85 A	9.8 A	6.1 A
Isolated SEPIC	5.5 A	719 V	36.4 A	11.4 A	42.5 A

Isolated SEPIC example has 4:1 turns ratio, with 42V 23.8A dc load

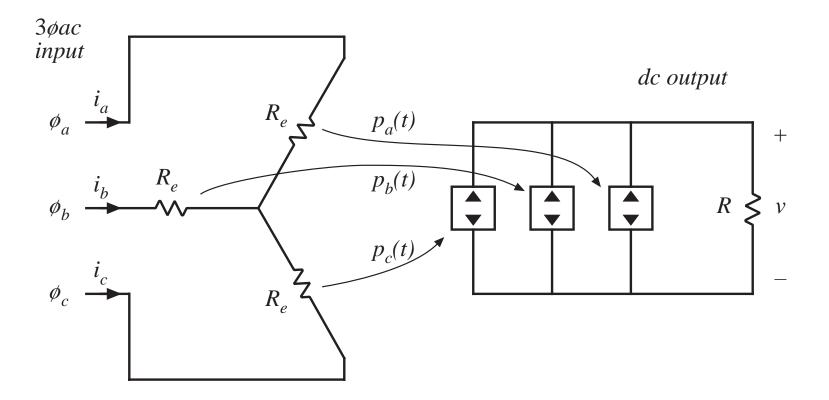
17.5 Ideal three-phase rectifiers

Ideal 3ø rectifier, modeled as three 1ø ideal rectifiers:



Ideal 3ø rectifier model

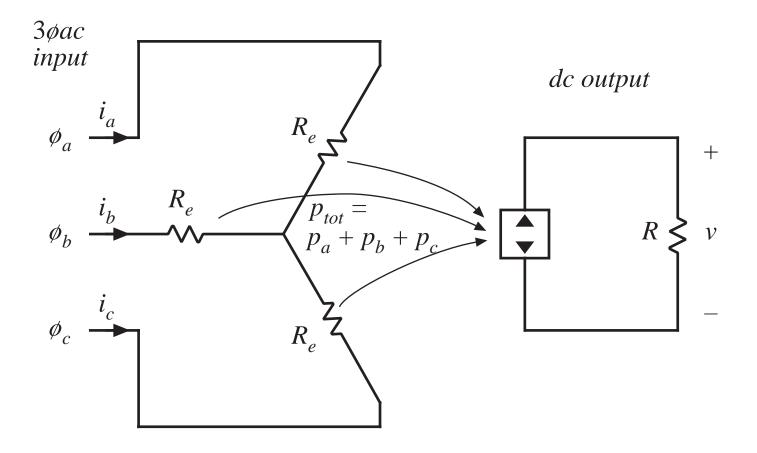Combine parallel-connected power sources into a single source $p_{tot}(t)$:



Fundamentals of Power Electronics

Value of $p_{tot}(t)$

Ac input voltages:


$$v_{an}(t) = V_M \sin(\omega t)$$
$$v_{bn}(t) = V_M \sin(\omega t - 120^\circ)$$
$$v_{cn}(t) = V_M \sin(\omega t - 240^\circ)$$

Instantaneous phase powers:

$$p_{a}(t) = \frac{v_{an}^{2}(t)}{R_{e}} = \frac{V_{M}^{2}}{2R_{e}} \left(1 - \cos\left(2\omega t\right)\right)$$

$$p_{b}(t) = \frac{v_{bn}^{2}(t)}{R_{e}} = \frac{V_{M}^{2}}{2R_{e}} \left(1 - \cos\left(2\omega t - 240^{\circ}\right)\right)$$
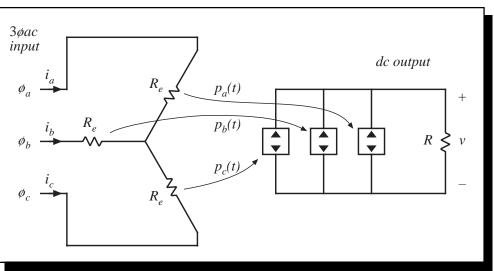
$$p_{c}(t) = \frac{v_{cn}^{2}(t)}{R_{e}} = \frac{V_{M}^{2}}{2R_{e}} \left(1 - \cos\left(2\omega t - 120^{\circ}\right)\right)$$



Total 3ø instantaneous power:

$$p_{tot}(t) = p_a(t) + p_b(t) + p_c(t) = \frac{3}{2} \frac{V_M^2}{R_e}$$


- 2nd harmonic terms add to zero
- total 3ø power $p_{tot}(t)$ is constant

Fundamentals of Power Electronics


Instantaneous power in ideal 3ø rectifier

$$p_{tot}(t) = p_a(t) + p_b(t) + p_c(t) = \frac{3}{2} \frac{V_M^2}{R_e}$$

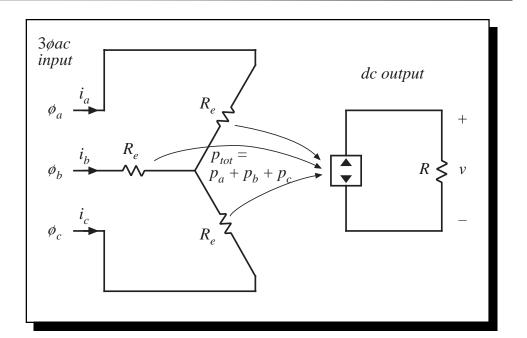- In a balanced system, the ideal 3ø rectifier supplies constant power to its dc output
- a constant power load can be supplied, without need for lowfrequency internal energy storage



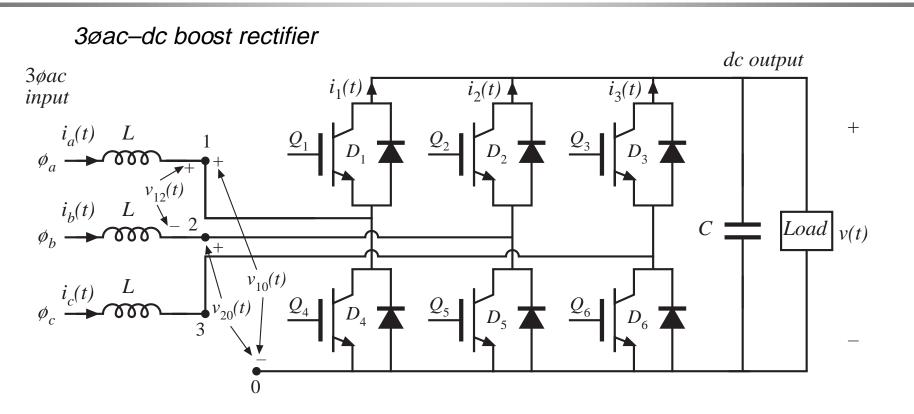17.5.1 Three-phase rectifiers operating in CCM



- Uses six current-bidirectional switches
- Operation of each individual phase is similar to the 1ø boost rectifier


The 3øac–dc boost rectifier

- Voltage-source inverter, operated backwards as a rectifier
- Converter is capable of bidirectional power flow
- Dc output voltage V must be greater than peak ac line-line voltage $V_{L,pk}$.
- Ac input currents are nonpulsating. In CCM, input EMI filtering is relatively easy
- Very low RMS transistor currents and conduction loss
- The leading candidate to replace uncontrolled 3ø rectifiers
- Requires six active devices
- Cannot regulate output voltage down to zero:
 - no current limiting
 - cannot replace traditional buck-type controlled rectifiers


Control of switches in CCM 3øac-dc boost rectifier

Pulse-width modulation:

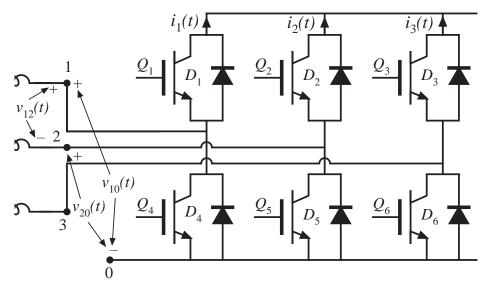Drive lower transistors $(Q_4 - Q_6)$ with complements of duty cycles of respective upper transistors $(Q_1 - Q_3)$. Each phase operates independently, with its own duty cycle.



Fundamentals of Power Electronics

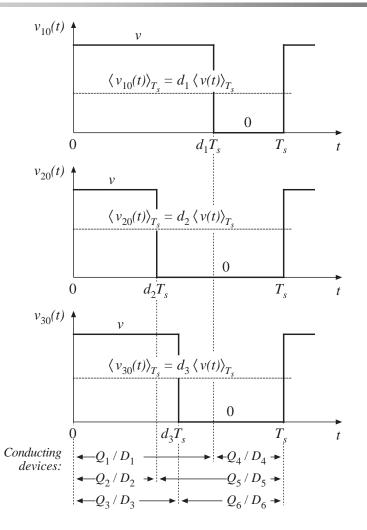

Average switch waveforms

Average the switch voltages:

 $\left\langle v_{10}(t) \right\rangle_{T_s} = d_1(t) \left\langle v(t) \right\rangle_{T_s}$ $\left\langle v_{20}(t) \right\rangle_{T_s} = d_2(t) \left\langle v(t) \right\rangle_{T_s}$ $\left\langle v_{30}(t) \right\rangle_{T_s} = d_3(t) \left\langle v(t) \right\rangle_{T_s}$

Average line-line voltages:


$$\left\langle v_{12}(t) \right\rangle_{T_s} = \left\langle v_{10}(t) \right\rangle_{T_s} - \left\langle v_{20}(t) \right\rangle_{T_s} = \left(d_1(t) - d_2(t) \right) \left\langle v(t) \right\rangle_{T_s}$$

$$\left\langle v_{23}(t) \right\rangle_{T_s} = \left\langle v_{20}(t) \right\rangle_{T_s} - \left\langle v_{30}(t) \right\rangle_{T_s} = \left(d_2(t) - d_3(t) \right) \left\langle v(t) \right\rangle_{T_s}$$


$$\left\langle v_{31}(t) \right\rangle_{T_s} = \left\langle v_{30}(t) \right\rangle_{T_s} - \left\langle v_{10}(t) \right\rangle_{T_s} = \left(d_3(t) - d_1(t) \right) \left\langle v(t) \right\rangle_{T_s}$$

Average switch output-side currents:

Fundamentals of Power Electronics

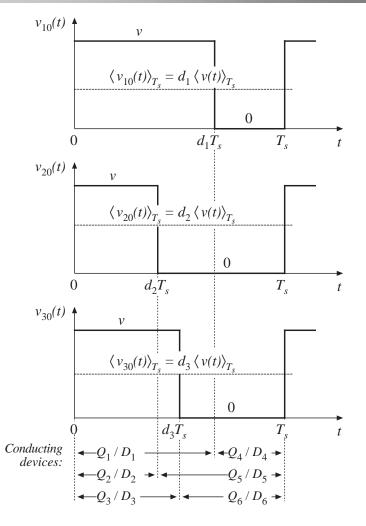

Averaged circuit model

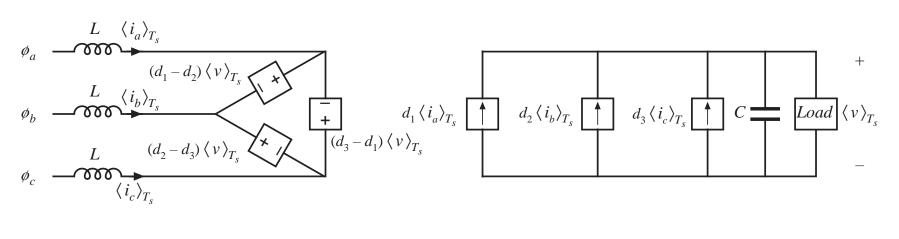

Q: How to vary *d*(*t*) such that the desired ac and dc waveforms are obtained?

Solution is not unique.

Sinusoidal PWM

A simple modulation scheme: Sinusoidal PWM

Vary duty cycles sinusoidally, in synchronism with ac line $d_1(t) = D_0 + \frac{1}{2} D_m \sin(\omega t - \varphi)$ $d_2(t) = D_0 + \frac{1}{2} D_m \sin(\omega t - \varphi - 120^\circ)$ $d_3(t) = D_0 + \frac{1}{2} D_m \sin(\omega t - \varphi - 240^\circ)$

where

 $\boldsymbol{\omega}$ is the ac line frequency

 D_0 is a dc bias

 D_m is the modulation index

For $D_0 = 0.5$, D_m in the above equations must be less than 1.

The modulation index is defined as one-half of the peak amplitude of the fundamental component of the duty cycle modulation. In some other modulation schemes, it is possible that $D_m > 1$.

Solution, linear sinusoidal PWM

If the switching frequency is high, then the inductors can be small and have negligible effect at the ac line frequency. The averaged switch voltage and ac line voltage are then equal:

$$\left\langle v_{12}(t) \right\rangle_{T_s} = \left(d_1(t) - d_2(t) \right) \left\langle v(t) \right\rangle_{T_s} \approx v_{ab}(t)$$

Substitute expressions for duty cycle and ac line voltage variations:

$$\frac{1}{2}D_{m}\left[\sin\left(\omega t-\varphi\right)-\sin\left(\omega t-\varphi-120^{\circ}\right)\right]\left\langle v(t)\right\rangle_{T_{s}}=V_{M}\left[\sin\left(\omega t\right)-\sin\left(\omega t-120^{\circ}\right)\right]$$

For small *L*, ϕ tends to zero. The expression then becomes

$$\frac{1}{2} D_m V = V_M$$

Solve for the output voltage:

$$V = \frac{2V_{M}}{D_{m}} \qquad V = \frac{2}{\sqrt{3}} \frac{V_{L,pk}}{D_{m}} = 1.15 \frac{V_{L,pk}}{D_{m}}$$

Fundamentals of Power Electronics

Chapter 17: The Ideal Rectifier


Boost rectifier with sinusoidal PWM

$$V = \frac{2}{\sqrt{3}} \frac{V_{L,pk}}{D_m} = 1.15 \frac{V_{L,pk}}{D_m}$$

With sinusoidal PWM, the dc output voltage must be greater than 1.15 times the peak line-line input voltage. Hence, the boost rectifier increases the voltage magnitude.


Nonlinear modulation

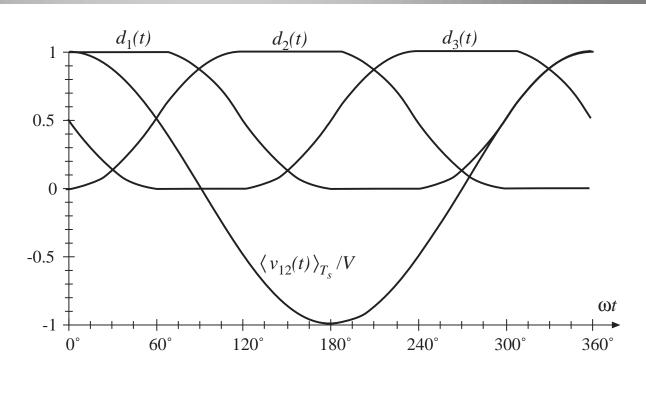- Triplen harmonics can be added to the duty ratio modulation, without appearing in the line-line voltages.
- Overmodulation, in which the modulation index D_m is increased beyond 1, also



leads to undistorted line-line voltages provided that $D_m \leq 1.15$. The pulse width modulator saturates, but the duty ratio variations contain only triplen harmonics. $V = V_{L,pk}$ is obtained at $D_m = 1.15$. Further increases in D_m cause distorted ac line waveforms.

Buck-type 3øac–dc rectifier

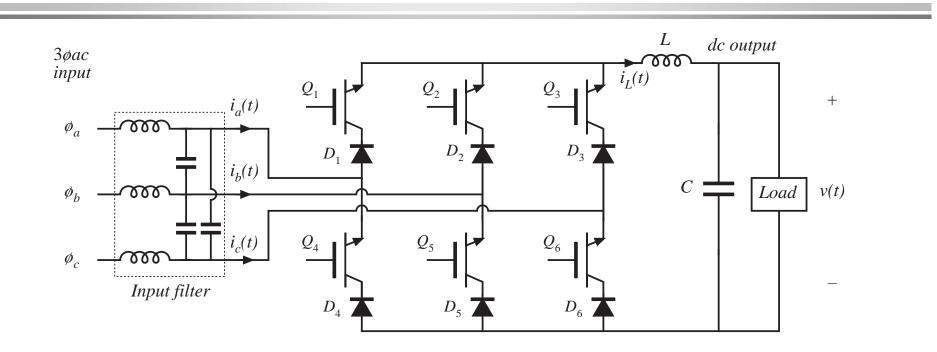


- Can produce controlled dc output voltages in the range $0 \le V \le V_{L,pk}$
- Requires two-quadrant voltage-bidirectional switches
- Exhibits greater active semiconductor stress than boost topology
- Can operate in inverter mode by reversal of output voltage polarity


Fundamentals of Power Electronics

Chapter 17: The Ideal Rectifier


Buck-boost topology

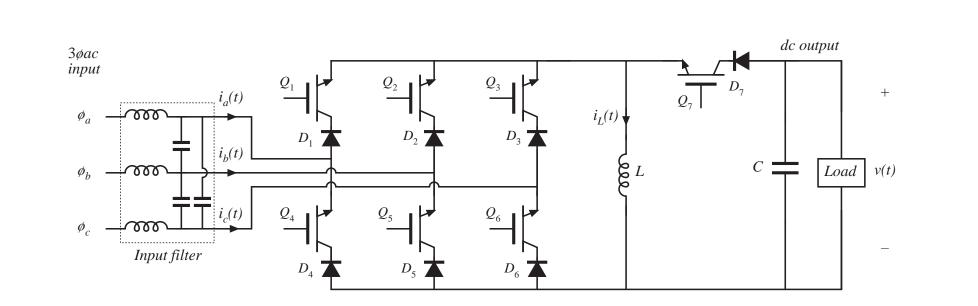

Cuk topology

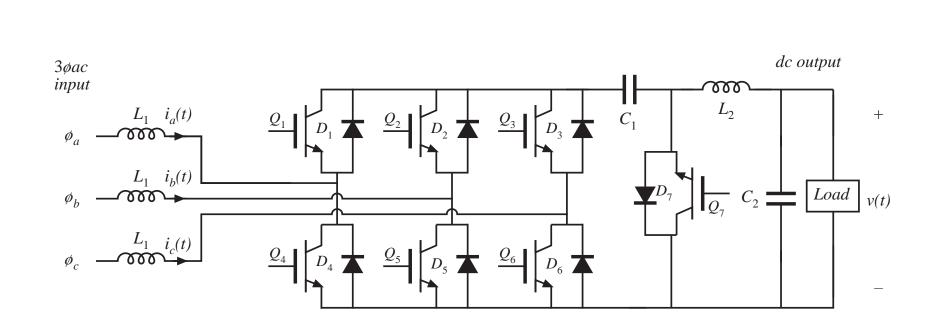

Use of three single-phase rectifiers

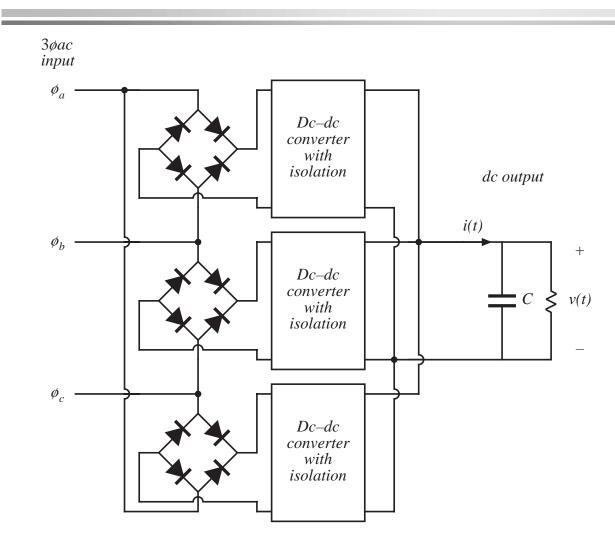

- Each rectifier must include isolation between input and output
- Isolation transformers must be rated to carry the pulsating single-phase ac power $p_{ac}(t)$
- Outputs can be connected in series or parallel
- Because of the isolation requirement, semiconductor stresses are greater than in 3ø boost rectifier

17.5.2 Some other approaches to three-phase rectification


Low-harmonic rectification requires active semiconductor devices that are much more expensive than simple peak-detection diode rectifiers.

What is the minimum active silicon required to perform the function of 3ø low-harmonic rectification?

- No active devices are needed: diodes and harmonic traps will do the job, but these require low-frequency reactive elements
- When control of the output voltage is needed, then there must be at least one active device
- To avoid low-frequency reactive elements, at least one highfrequency switch is needed


So let's search for approaches that use just one active switch, and only high-frequency reactive elements

The single-switch DCM boost 3ø rectifier

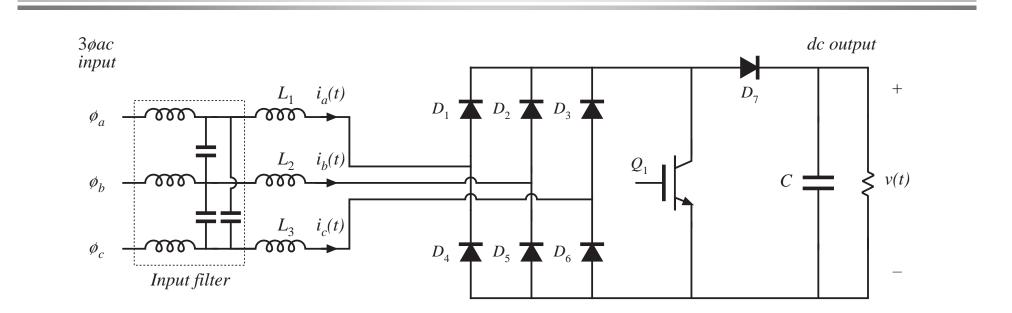


Inductors L_1 to L_3 operate in discontinuous conduction mode, in conjunction with diodes D_1 to D_6 . Average input currents $\langle i_a(t) \rangle_{T_s}$, $\langle i_b(t) \rangle_{T_s}$, and $\langle i_c(t) \rangle_{T_s}$ are approximately proportional to the instantaneous input line-neutral voltages. Transistor is operated with constant duty cycle; slow variation of the duty cycle allows control of output power.

The single-switch DCM boost 3ø rectifier

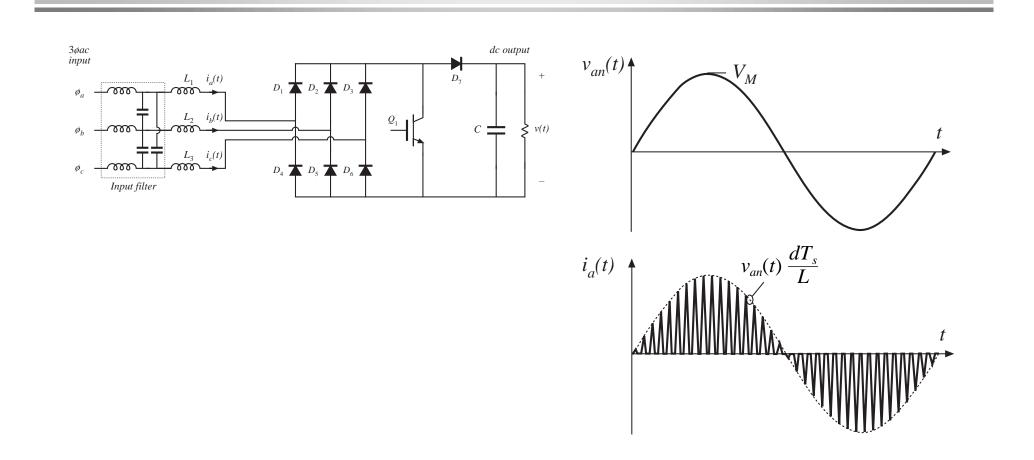

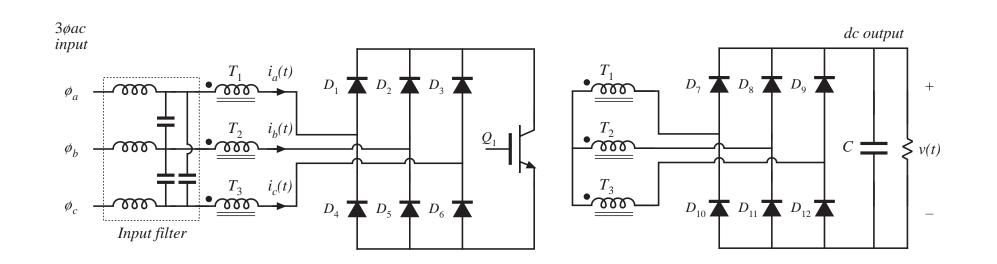The single-switch 3ø DCM flyback rectifier



The single-switch 3ø DCM flyback rectifier


This converter is effectively three independent single-phase DCM flyback converters that share a common switch.

Since the open-loop DCM flyback converter can be modeled as a Loss-Free Resistor, three-phase low-harmonic rectification is obtained naturally.

Basic converter has a boost characteristic, but buck-boost characteristic is possible (next slide).


Inrush current limiting and isolation are obtained easily.

High peak currents, needs an input EMI filter

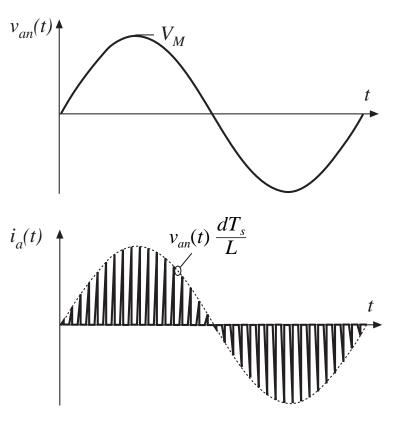


Chapter 17: The Ideal Rectifier

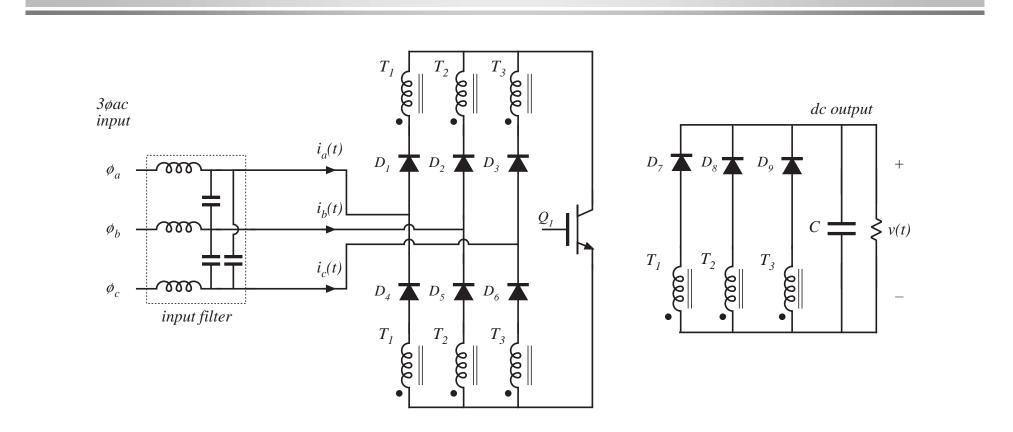3ø Flyback rectifier with buck-boost conversion ratio



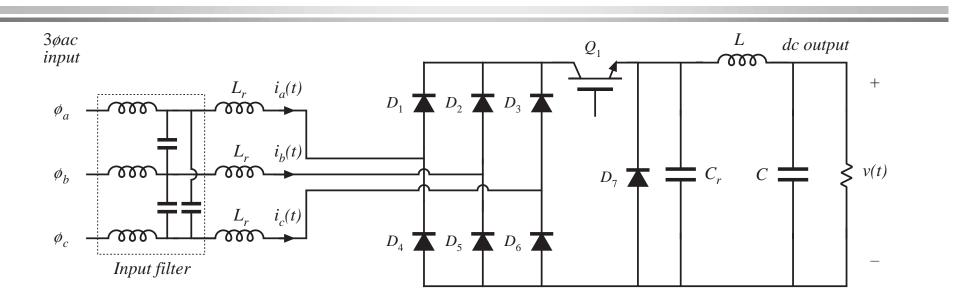Single-switch three-phase zero-currentswitching quasi-resonant buck rectifier




Inductors L_r and capacitor C_r form resonant tank circuits, having resonant frequency slightly greater than the switching frequency.

Turning on Q_1 initiates resonant current pulses, whose amplitudes depend on the instantaneous input line-neutral voltages.

When the resonant current pulses return to zero, diodes D_1 to D_6 are reverse-biased. Transistor Q_1 can then be turned off at zero current.

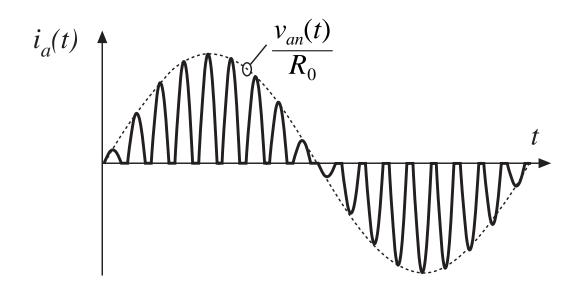Single-switch three-phase zero-currentswitching quasi-resonant buck rectifier




Input line currents are approximately sinusoidal pulses, whose amplitudes follow the input line-neutral voltages.

Lowest total active semiconductor stress of all buck-type 3ø low harmonic rectifiers

Fundamentals of Power Electronics

Chapter 17: The Ideal Rectifier

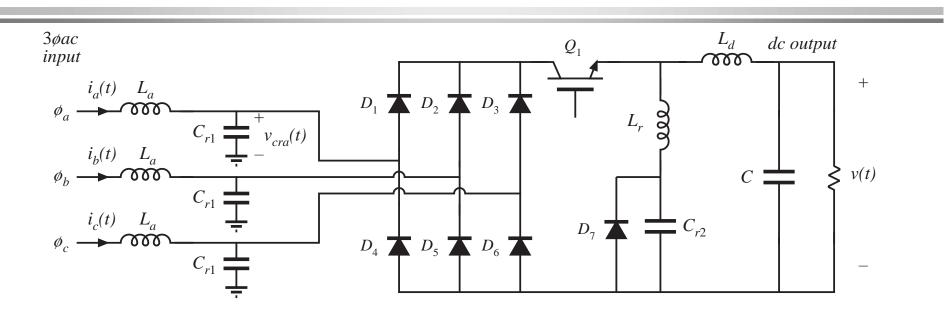Multiresonant single-switch zero-current switching 3ø buck rectifier




Inductors L_r and capacitors C_{r1} and C_{r2} form resonant tank circuits, having resonant frequency slightly greater than the switching frequency.

Turning on Q_1 initiates resonant voltage pulses in $v_{cra}(t)$, whose amplitudes depend on the instantaneous input line-neutral currents $i_a(t)$ to $i_c(t)$.

All diodes switch off when their respective tank voltages reach zero. Transistor Q_1 is turned off at zero current.

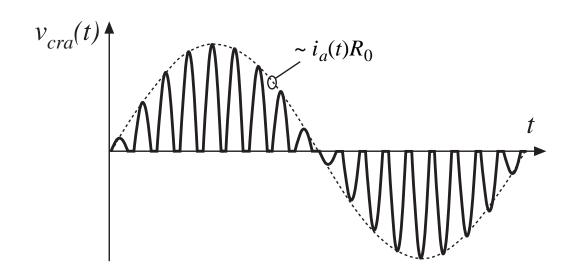
Multiresonant single-switch zero-current switching 3ø buck rectifier



Input-side resonant voltages are approximately sinusoidal pulses, whose amplitudes follow the input currents. Input filter inductors operate in CCM.

Higher total active semiconductor stress than previous approach, but less EMI filtering is needed. Low THD: < 4% THD can be obtained.

Harmonic correction

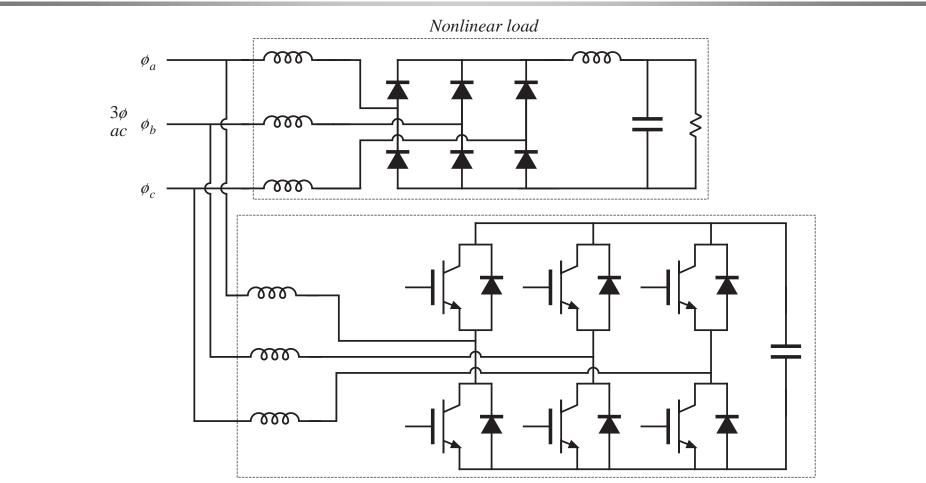

Harmonic corrector

Fundamentals of Power Electronics

Chapter 17: The Ideal Rectifier

Harmonic correction

- An active filter that is controlled to cancel the harmonic currents created by a nonlinear load.
- Does not need to conduct the average load power.
- Total active semiconductor stress is high when the nonlinear load generates large harmonic currents having high THD.
- In the majority of applications, this approach exhibits greater total active semiconductor stress than the simple 3ø CCM boost rectifier.

17.6 Summary of key points

- 1. The ideal rectifier presents an effective resistive load, the emulated resistance R_e , to the ac power system. The power apparently "consumed" by R_e is transferred to the dc output port. In a three-phase ideal rectifier, input resistor emulation is obtained in each phase. In both the single-phase and three-phase cases, the output port follows a power source characteristic, dependent on the instantaneous ac input power. Ideal rectifiers can perform the function of low-harmonic rectification, without need for low-frequency reactive elements.
- 2. The dc-dc boost converter, as well as other converters capable of increasing the voltage, can be adapted to the ideal rectifier application. A control system causes the input current to be proportional to the input voltage. The converter may operate in CCM, DCM, or in both modes. The mode boundary is expressed as a function of R_e , $2L/T_s$, and the instantaneous voltage ratio $v_g(t)/V$. A well-designed average current controller leads to resistor emulation regardless of the operating mode; however, other schemes discussed in the next chapter may lead to distorted current waveforms when the mode boundary is crossed.

Fundamentals of Power Electronics

74

Chapter 17: The Ideal Rectifier

Summary of key points

- 3. In a single-phase system, the instantaneous ac input power is pulsating, while the dc load power is constant. Whenever the instantaneous input and output powers are not equal, the ideal rectifier system must contain energy storage. A large capacitor is commonly employed; the voltage of this capacitor must be allowed to vary independently, as necessary to store and release energy. A slow feedback loop regulates the dc component of the capacitor voltage, to ensure that the average ac input power and dc load power are balanced.
- 4. RMS values of rectifiers waveforms can be computed by double integration. In the case of the boost converter, the rms transistor current can be as low as 39% of the rms ac input current, when *V* is close in value to V_M . Other converter topologies such as the buck-boost, SEPIC, and Cuk converters exhibit significantly higher rms transistor currents but are capable of limiting the converter inrush current.

Summary of key points

- 5. In the three-phase case, a boost-type rectifier based on the PWM voltagesource inverter also exhibits low rms transistor currents. This approach requires six active switching elements, and its dc output voltage must be greater than the peak input line-to-line voltage. Average current control can be used to obtain input resistor emulation. An equivalent circuit can be derived by averaging the switch waveforms. The converter operation can be understood by assuming that the switch duty cycles vary sinusoidally; expressions for the average converter waveforms can then be derived.
- Other three-phase rectifier topologies are known, including six-switch rectifiers having buck and buck-boost characteristics. In addition, threephase low-harmonic rectifiers having a reduced number of active switches, as few as one, are discussed here.

Chapter 18 Low Harmonic Rectifier Modeling and Control

18.1 Modeling losses and efficiency in CCM high-quality rectifiers

Expression for controller duty cycle d(t)Expression for the dc load current Solution for converter efficiency η Design example

18.2 Controller schemes

Average current control
Feedforward
Current programmed control
Hysteretic control
Nonlinear carrier control

18.3 Control system modeling

Modeling the outer low-bandwidth control system Modeling the inner wide-bandwidth average current controller


ECEN5807 Power Electronics 2

18.1 Modeling losses and efficiency in CCM high-quality rectifiers

Objective: extend procedure of Chapter 3, to predict the output voltage, duty cycle variations, and efficiency, of PWM CCM low harmonic rectifiers.


Approach: Use the models developed in Chapter 3. Integrate over one ac line cycle to determine steady-state waveforms and average power.

Boost example

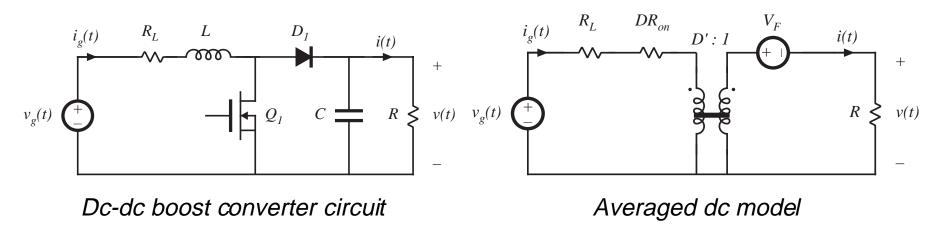


ECEN5807 Power Electronics 2

Modeling the ac-dc boost rectifier

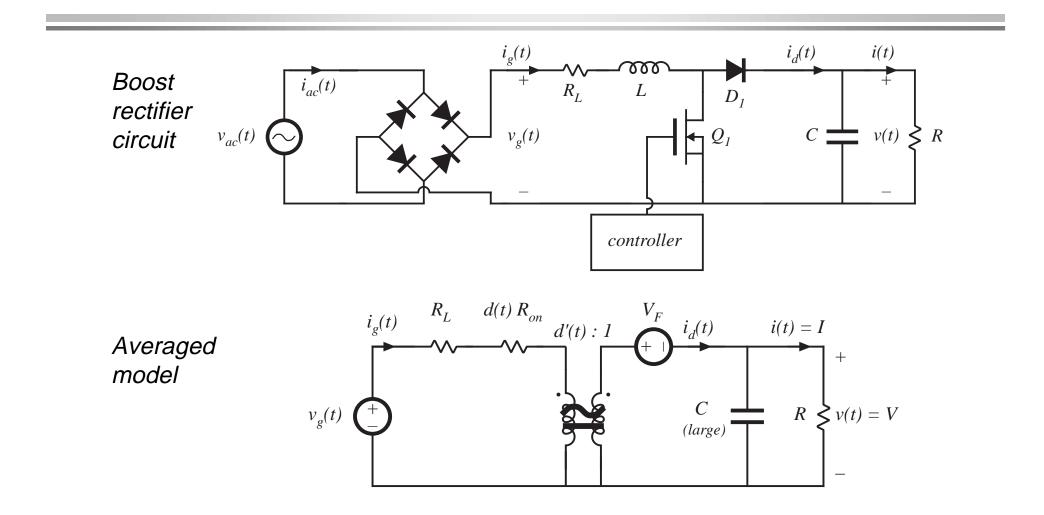

ECEN5807 Power Electronics 2

Boost rectifier waveforms

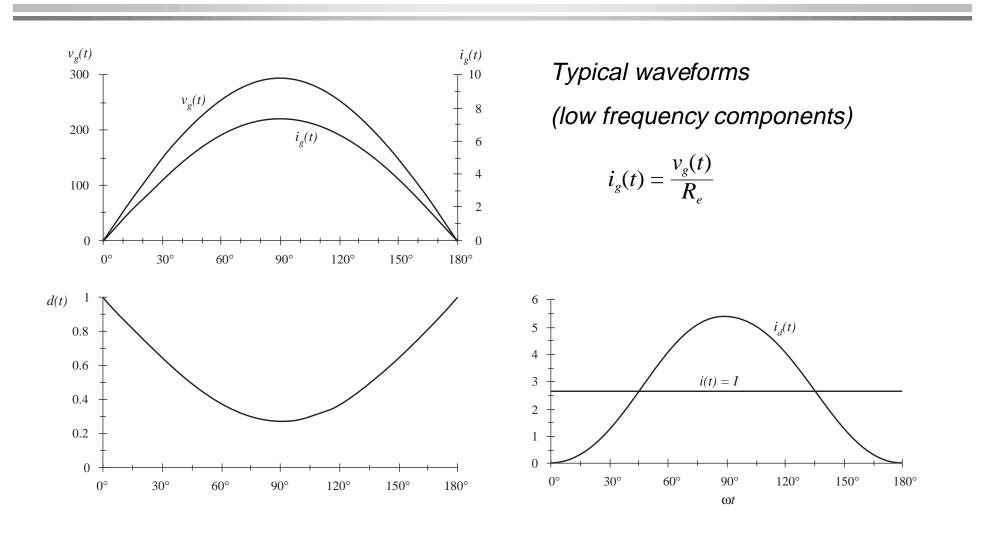


4

ECEN5807 Power Electronics 2

Chapter 18: Low harmonic rectifier modeling and control

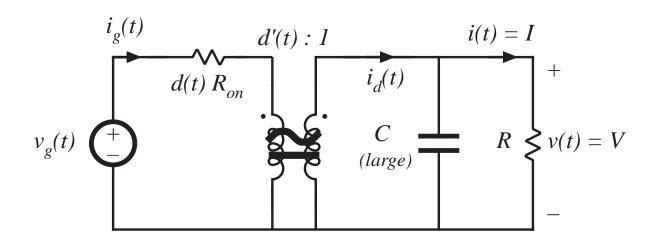Example: boost rectifier with MOSFET on-resistance



Averaged model


Inductor dynamics are neglected, a good approximation when the ac line variations are slow compared to the converter natural frequencies

18.1.1 Expression for controller duty cycle d(t)

Solve input side of model:

 $i_g(t)d(t)R_{on} = v_g(t) - d'(t)v$

with $i_g(t) = \frac{v_g(t)}{R_e}$ $v_g(t) = V_M | \sin \omega t |$

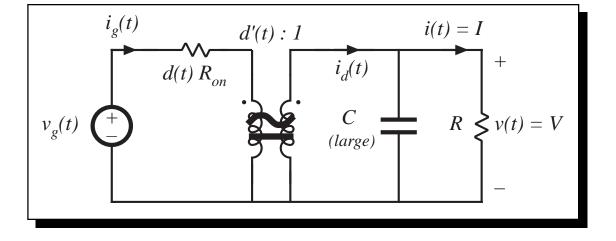

eliminate $i_g(t)$:

 $\frac{v_g(t)}{R_e} d(t)R_{on} = v_g(t) - d'(t)v$

solve for d(t):

$$d(t) = \frac{v - v_g(t)}{v - v_g(t) \frac{R_{on}}{R_e}}$$

Again, these expressions neglect converter dynamics, and assume that the converter always operates in CCM.

ECEN5807 Power Electronics 2


18.1.2 Expression for the dc load current

Solve output side of model, using charge balance on capacitor *C*:

$$i_d(t) = d'(t)i_g(t) = d'(t)\frac{r_g(t)}{R_e}$$

But*d*'(*t*) is:
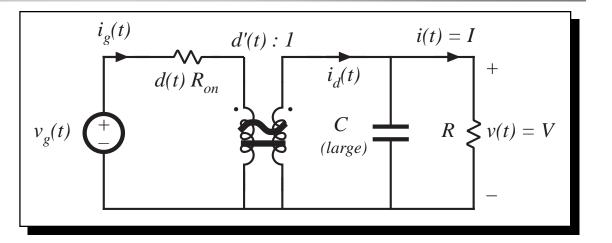
$$d'(t) = \frac{v_g(t) \left(1 - \frac{R_{on}}{R_e}\right)}{v - v_g(t) \frac{R_{on}}{R_e}}$$



hence $i_d(t)$ can be expressed as

$$i_d(t) = \frac{v_g^2(t)}{R_e} \frac{\left(1 - \frac{R_{on}}{R_e}\right)}{v - v_g(t) \frac{R_{on}}{R_e}}$$

Next, average $i_d(t)$ over an ac line period, to find the dc load current *I*.

ECEN5807 Power Electronics 2

Dc load current *I*

Now substitute $v_g(t) = V_M \sin \omega t$, and integrate to find $\langle i_d(t) \rangle_{T_{ac}}$:

$$I = \left\langle i_d \right\rangle_{T_{ac}} = \frac{2}{T_{ac}} \int_0^{T_{ac}/2} \left(\frac{V_M^2}{R_e} \right) \frac{\left(1 - \frac{R_{on}}{R_e} \right) \sin^2 \left(\omega t \right)}{\left(v - \frac{V_M R_{on}}{R_e} \sin \left(\omega t \right) \right)} dt$$

This can be written in the normalized form

$$I = \frac{2}{T_{ac}} \frac{V_M^2}{VR_e} \left(1 - \frac{R_{on}}{R_e}\right) \int_0^{T_{ac}/2} \frac{\sin^2(\omega t)}{1 - a\sin(\omega t)} dt$$

with $a = \left(\frac{V_M}{V}\right) \left(\frac{R_{on}}{R_e}\right)$

ECEN5807 Power Electronics 2

Chapter 18: Low harmonic rectifier modeling and control

8

Integration

By waveform symmetry, we need only integrate from 0 to $T_{ac}/4$. Also, make the substitution $\theta = \omega t$:

$$I = \frac{V_M^2}{VR_e} \left(1 - \frac{R_{on}}{R_e}\right) \frac{2}{\pi} \int_0^{\pi/2} \frac{\sin^2\left(\theta\right)}{1 - a\sin\left(\theta\right)} d\theta$$

This integral is obtained not only in the boost rectifier, but also in the buck-boost and other rectifier topologies. The solution is

$$\frac{4}{\pi} \int_{0}^{\pi/2} \frac{\sin^{2}\left(\theta\right)}{1 - a\,\sin\left(\theta\right)} \, d\theta = F(a) = \frac{2}{a^{2}\pi} \left(-2a - \pi + \frac{4\,\sin^{-1}\left(a\right) + 2\,\cos^{-1}\left(a\right)}{\sqrt{1 - a^{2}}}\right)$$


9

- Result is in closed form
- *a* is a measure of the loss resistance relative to *R*_e

• *a* is typically much smaller than unity

ECEN5807 Power Electronics 2

The integral *F*(*a*)

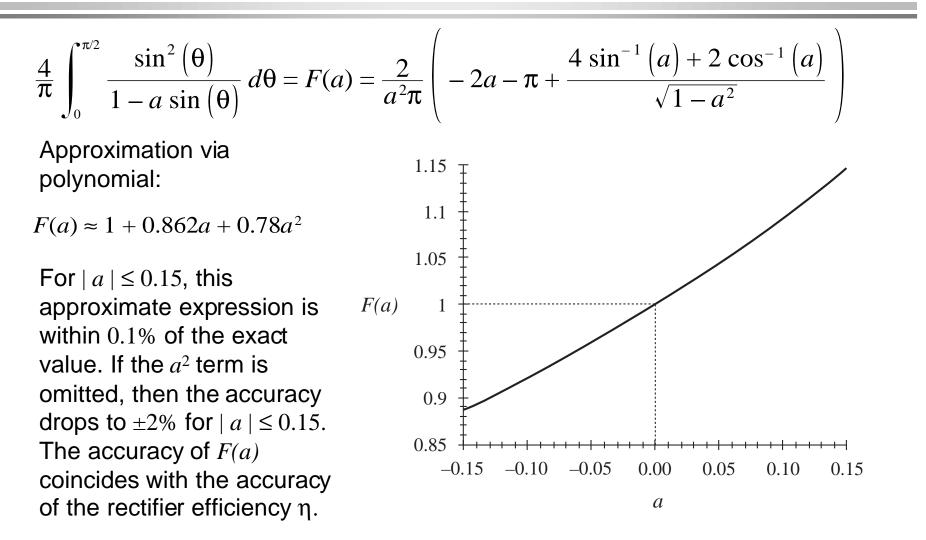

ECEN5807 Power Electronics 2

18.1.4 Solution for converter efficiency η

Converter average input power is

$$P_{in} = \left\langle p_{in}(t) \right\rangle_{T_{ac}} = \frac{V_M^2}{2R_e}$$

Average load power is

$$P_{out} = VI = \left(V\right) \left(\frac{V_M^2}{VR_e} \left(1 - \frac{R_{on}}{R_e}\right) \frac{F(a)}{2}\right) \quad \text{with} \quad a = \left(\frac{V_M}{V}\right) \left(\frac{R_{on}}{R_e}\right)$$

So the efficiency is


$$\eta = \frac{P_{out}}{P_{in}} = \left(1 - \frac{R_{on}}{R_e}\right)F(a)$$

Polynomial approximation:

$$\eta \approx \left(1 - \frac{R_{on}}{R_e}\right) \left(1 + 0.862 \frac{V_M}{V} \frac{R_{on}}{R_e} + 0.78 \left(\frac{V_M}{V} \frac{R_{on}}{R_e}\right)^2\right)$$

ECEN5807 Power Electronics 2

Boost rectifier efficiency

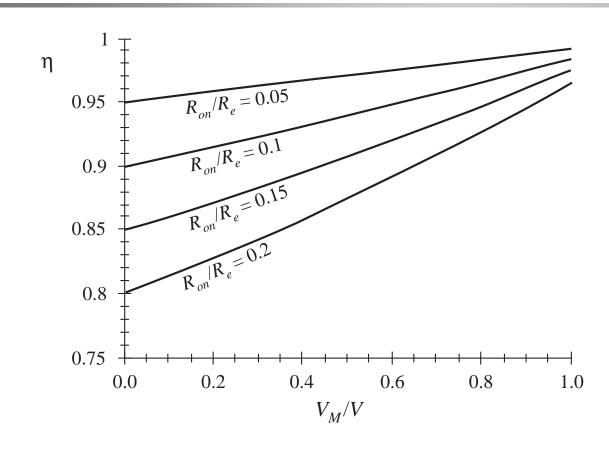

$$\eta = \frac{P_{out}}{P_{in}} = \left(1 - \frac{R_{on}}{R_e}\right)F(a)$$

- To obtain high efficiency, choose V slightly larger than V_M
- Efficiencies in the range 90% to 95% can then be obtained, even with R_{on} as high as 0.2R_e
- Losses other than MOSFET on-resistance are not included here

18.1.5 Design example

Let us design for a given efficiency. Consider the following specifications:

Output voltage	390 V
Output power	500 W
rms input voltage	120 V
Efficiency	95%

Assume that losses other than the MOSFET conduction loss are negligible.

Average input power is


$$P_{in} = \frac{P_{out}}{\eta} = \frac{500 \text{ W}}{0.95} = 526 \text{ W}$$

Then the emulated resistance is

$$R_e = \frac{V_{g, rms}^2}{P_{in}} = \frac{(120 \text{ V})^2}{526 \text{ W}} = 27.4 \text{ }\Omega$$

ECEN5807 Power Electronics 2

Design example

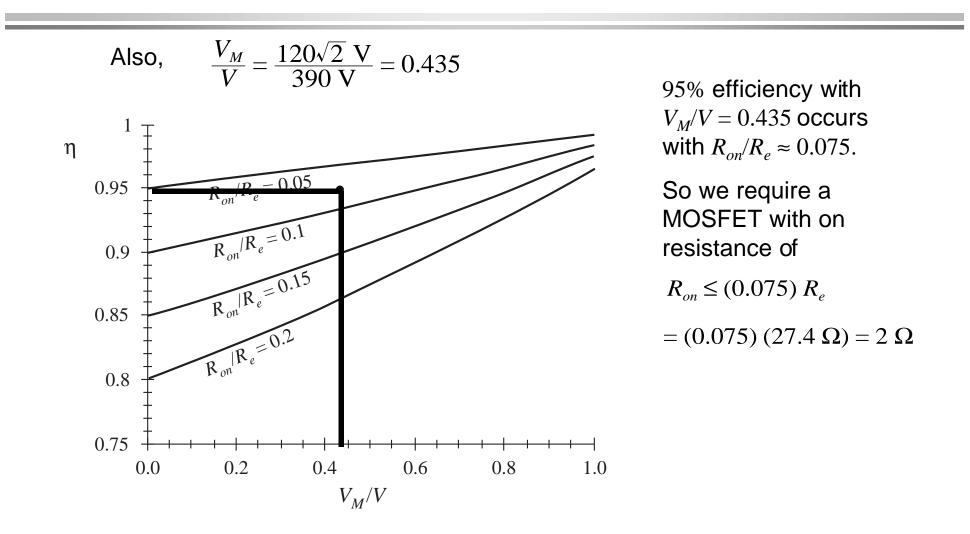


ECEN5807 Power Electronics 2

18.2 Controller schemes

Average current control Feedforward Current programmed control Hysteretic control Nonlinear carrier control

18.2.1 Average current control

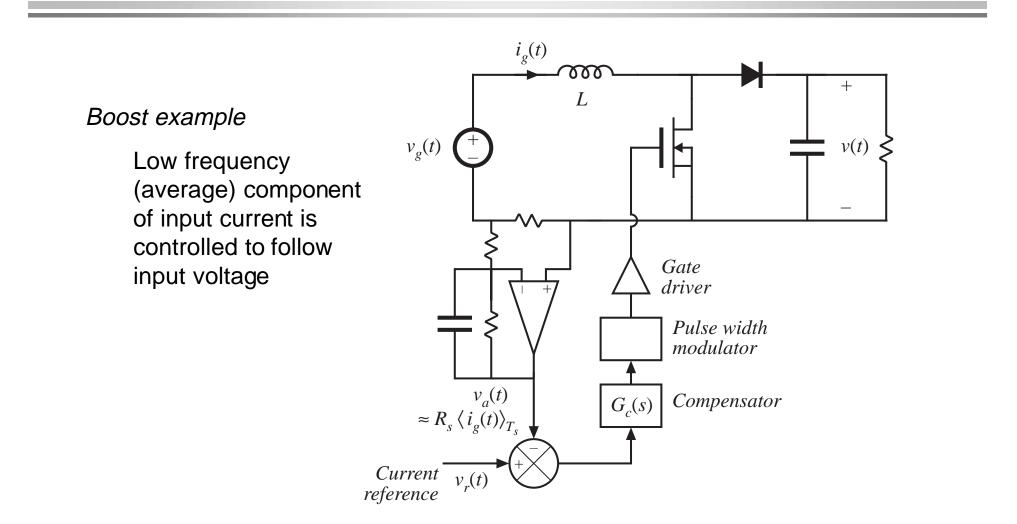

ECEN5807 Power Electronics 2


16 *Chapter 18: Low harmonic rectifier modeling and control*

Use of multiplier to control average power

As discussed in Chapter 17, an output voltage feedback loop adjusts the emulated resistance R_e such that the rectifier power equals the dc load power:


$$P_{av} = \frac{V_{g,rms}^2}{R_e} = P_{load}$$

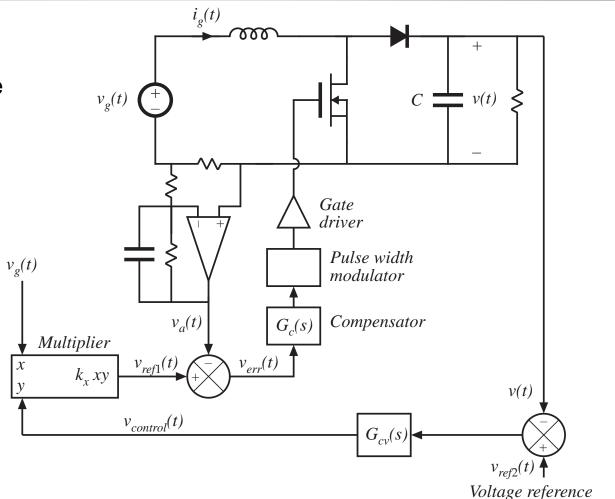An analog multiplier introduces the dependence of R_e on v(t).




17 Chapter 18: Low harmonic rectifier modeling and control

18.2.2 Feedforward

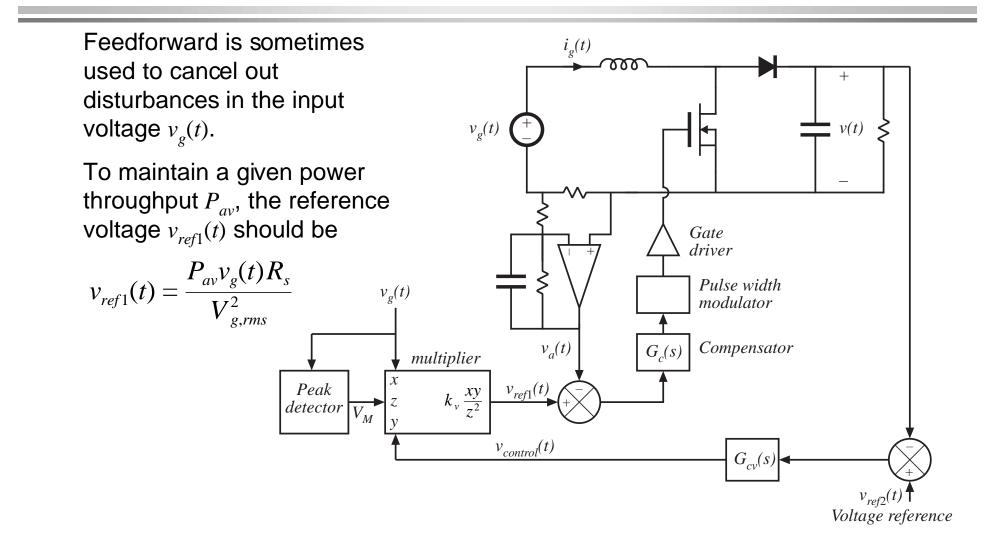

18 Chapter 18: Low harmonic rectifier modeling and control

Feedforward, continued

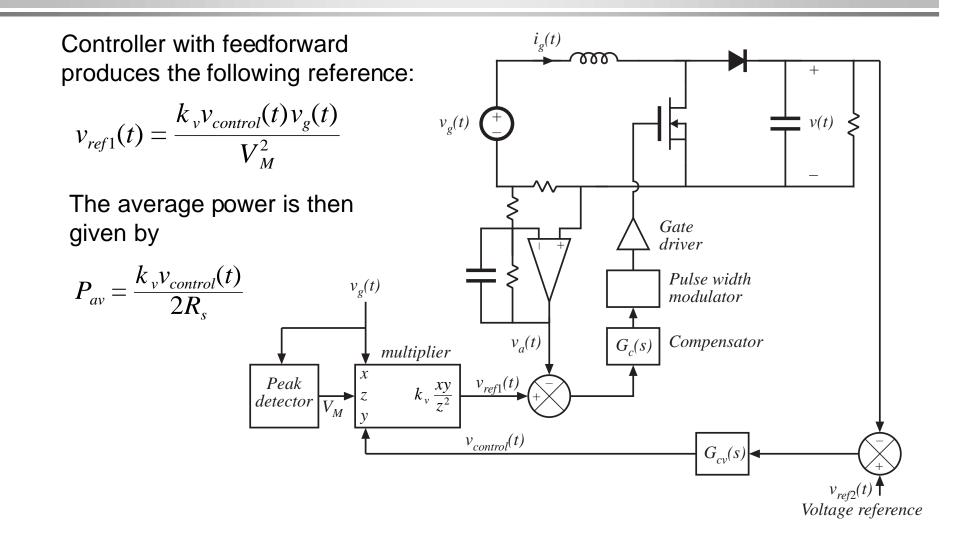


19 Chapter 18: Low harmonic rectifier modeling and control

18.2.3 Current programmed control

Current programmed control is a natural approach to obtain input resistor emulation:

Peak transistor current is programmed to follow input voltage.

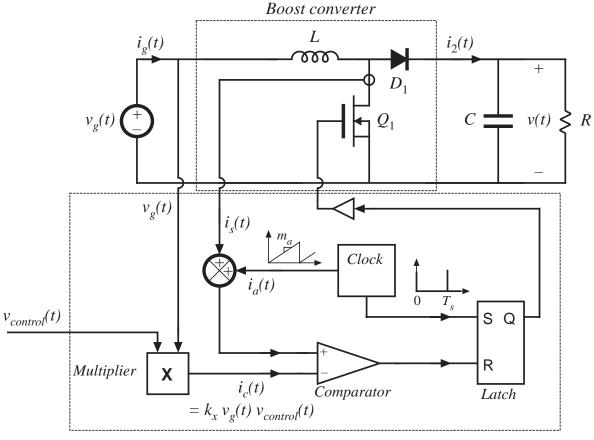Peak transistor current differs from average inductor current, because of inductor current ripple and artificial ramp. This leads to significant input current waveform distortion.




Current-programmed controller

ECEN5807 Power Electronics 2


20 Chapter 18: Low harmonic rectifier modeling and control

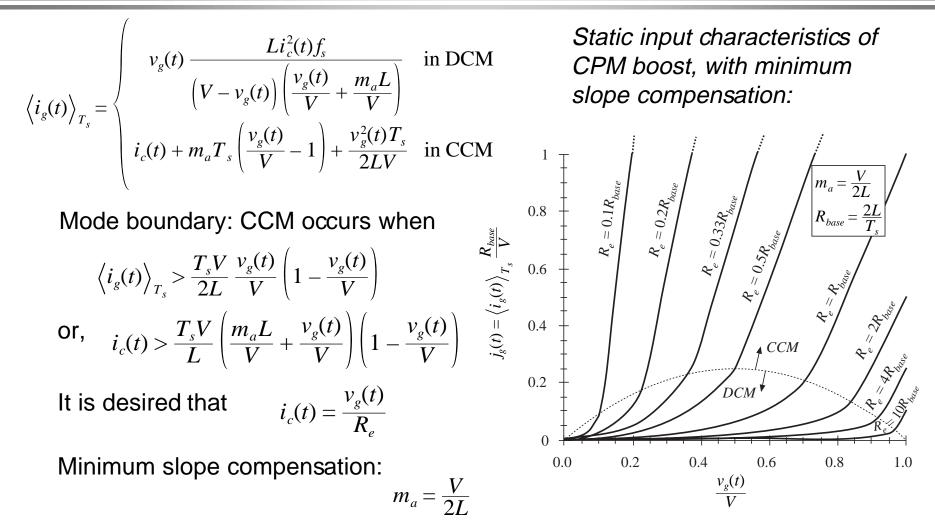CPM boost converter: Static input characteristics



21 Chapter 18: Low harmonic rectifier modeling and control

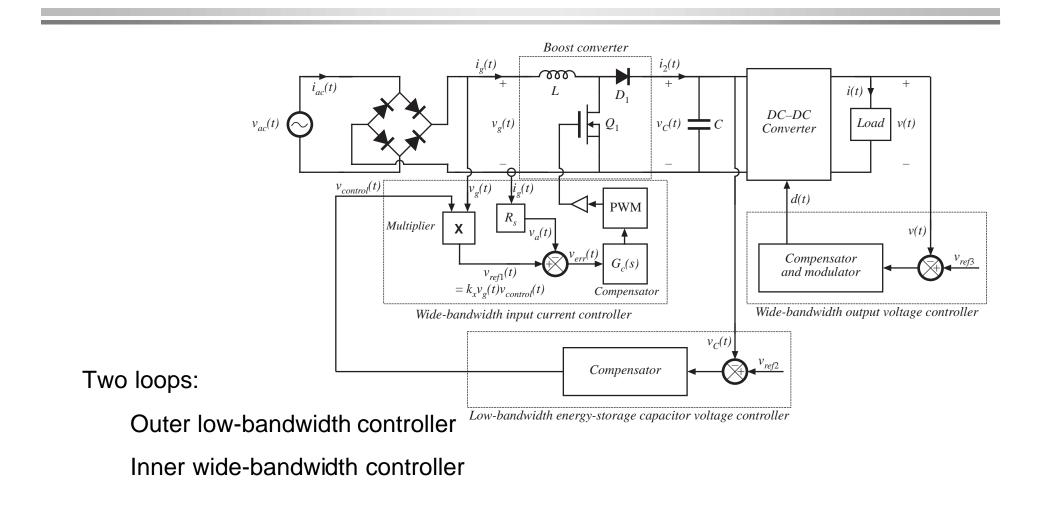18.3 Control system modeling of high quality rectifiers




18.3.1 Modeling the outer low-bandwidth control system

This loop maintains power balance, stabilizing the rectifier output voltage against variations in load power, ac line voltage, and component values

The loop must be slow, to avoid introducing variations in R_e at the harmonics of the ac line frequency

Objective of our modeling efforts: low-frequency small-signal model that predicts transfer functions at frequencies below the ac line frequency

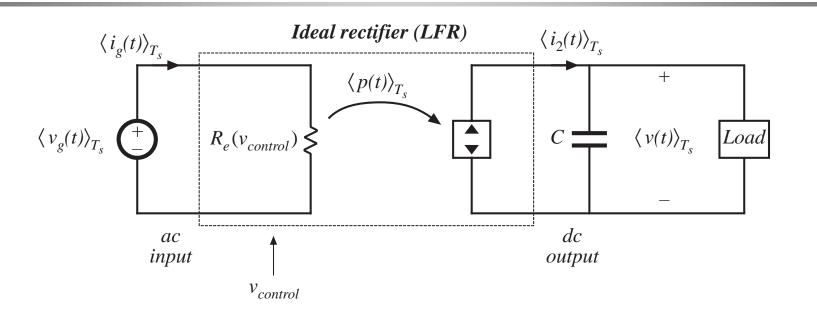Large signal model averaged over switching period T_s




Ideal rectifier model, assuming that inner wide-bandwidth loop operates ideally

High-frequency switching harmonics are removed via averaging

Ac line-frequency harmonics are included in model

Nonlinear and time-varying


Predictions of large-signal model

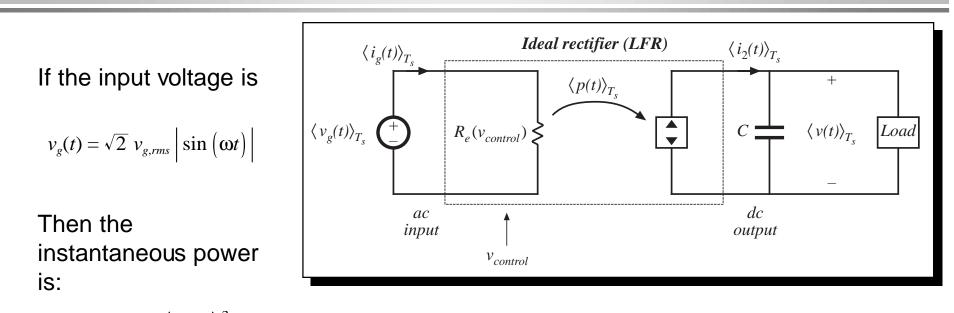

$$\left\langle p(t) \right\rangle_{T_s} = \frac{\left\langle v_g(t) \right\rangle_{T_s}^2}{R_e(v_{control}(t))} = \frac{v_{g,rms}^2}{R_e(v_{control}(t))} \left(1 - \cos\left(2\omega t\right) \right)$$

which contains a constant term plus a secondharmonic term

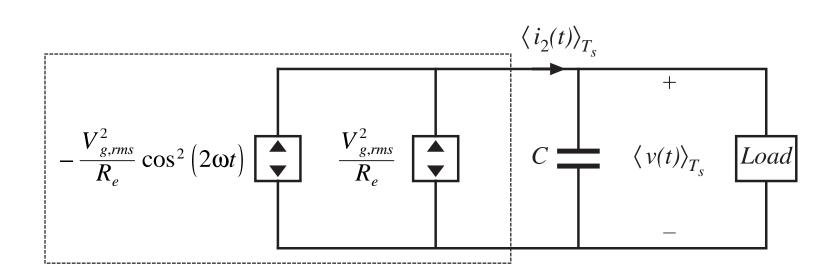
Separation of power source into its constant and time-varying components



Rectifier output port

The second-harmonic variation in power leads to second-harmonic variations in the output voltage and current

Removal of even harmonics via averaging

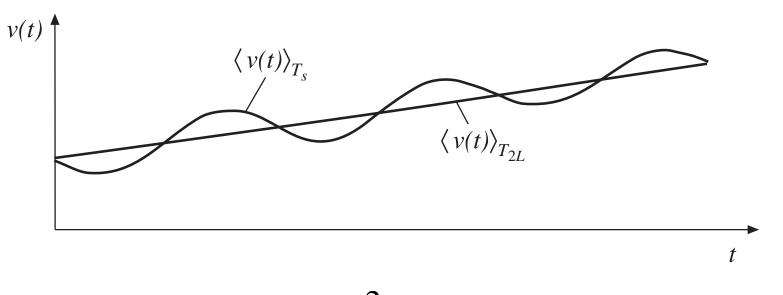


$$T_{2L} = \frac{1}{2} \frac{2\pi}{\omega} = \frac{\pi}{\omega}$$

ECEN5807 Power Electronics 2

27 Chapter 18: Low harmonic rectifier modeling and control

Resulting averaged model

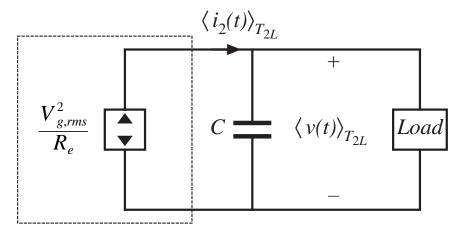

Rectifier output port

Time invariant model

Power source is nonlinear

Perturbation and linearization

The averaged model predicts that the rectifier output current is

$$\left\langle i_{2}(t) \right\rangle_{T_{2L}} = \frac{\left\langle p(t) \right\rangle_{T_{2L}}}{\left\langle v(t) \right\rangle_{T_{2L}}} = \frac{v_{g,rms}^{2}(t)}{R_{e}(v_{control}(t)) \left\langle v(t) \right\rangle_{T_{2L}}}$$
$$= f \left(v_{g,rms}(t), \left\langle v(t) \right\rangle_{T_{2L}}, v_{control}(t)) \right)$$

Let

with

$$\left\langle v(t) \right\rangle_{T_{2L}} = V + \hat{v}(t)$$

$$\left\langle \dot{i}_{2}(t) \right\rangle_{T_{2L}} = I_{2} + \hat{i}_{2}(t)$$

$$v_{g,rms} = V_{g,rms} + \hat{v}_{g,rms}(t)$$

$$v_{control}(t) = V_{control} + \hat{v}_{control}(t)$$

$$V_{g,rms} = V_{g,rms} + \hat{v}_{g,rms}(t)$$

$$V_{g,rms} = V_{g,rms} + \hat{v}_{g,rms}(t)$$

$$V >> | \hat{v}(t) |$$

$$I_{2} >> | \hat{i}_{2}(t) |$$

$$V_{g,rms} >> | \hat{v}_{g,rms}(t) |$$

$$V_{control} >> | \hat{v}_{control}(t) |$$


ECEN5807 Power Electronics 2

29

Linearized result

$$I_{2} + \hat{i}_{2}(t) = g_{2}\hat{v}_{g,rms}(t) + j_{2}\hat{v}(t) - \frac{\hat{v}_{control}(t)}{r_{2}}$$


where

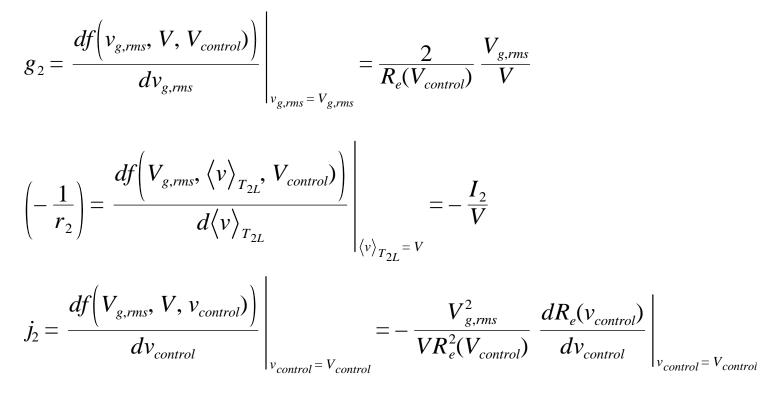

ECEN5807 Power Electronics 2

30 Chapter 18: Low harmonic rectifier modeling and control

Small-signal equivalent circuit

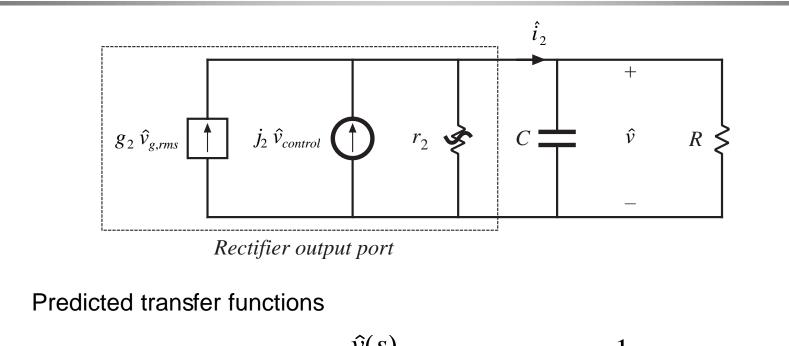

Control-to-output $\frac{\hat{v}(s)}{\hat{v}_{control}(s)} = j_2 R ||r_2 \frac{1}{1 + sC R||r_2}$ Line-to-output $\frac{\hat{v}(s)}{\hat{v}_{g,rms}(s)} = g_2 R ||r_2 \frac{1}{1 + sC R||r_2}$

ECEN5807 Power Electronics 2


31 *Chapter 18: Low harmonic rectifier modeling and control*

Model parameters

 Table 18.1
 Small-signal model parameters for several types of rectifier control schemes

Controller type	g_2	j_2	r_2
Average current control with feedforward, Fig. 18.9	0	$rac{P_{av}}{VV_{control}}$	$rac{V^2}{P_{av}}$
Current-programmed control, Fig. 18.10	$\frac{2P_{av}}{VV_{g,rms}}$	$rac{P_{av}}{VV_{control}}$	$\frac{V^2}{P_{av}}$
Nonlinear-carrier charge control of boost rectifier, Fig. 18.14	$\frac{2P_{av}}{VV_{g,rms}}$	$rac{P_{av}}{VV_{control}}$	$\frac{V^2}{2P_{av}}$
Boost with hysteretic control, Fig. 18.13(b)	$rac{2P_{av}}{VV_{g,rms}}$	$rac{P_{av}}{VT_{on}}$	$rac{V^2}{P_{av}}$
DCM buck-boost, flyback, SEPIC, or Cuk converters	$rac{2P_{av}}{VV_{g,rms}}$	$rac{2P_{av}}{VD}$	$rac{V^2}{P_{av}}$

Constant power load

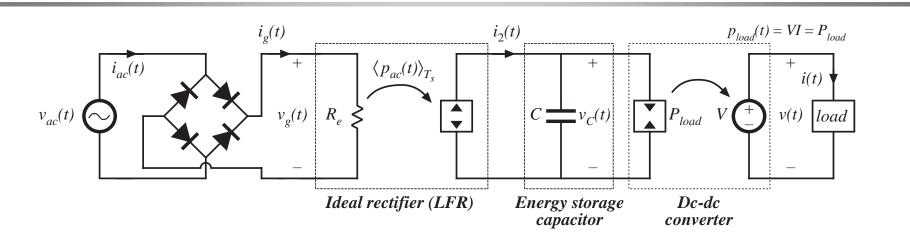

Rectifier and dc-dc converter operate with same average power

Incremental resistance R of constant power load is negative, and is

$$R = -\frac{V^2}{P_{av}}$$

which is equal in magnitude and opposite in polarity to rectifier incremental output resistance r_2 for all controllers except NLC

Transfer functions with constant power load


When $r_2 = -R$, the parallel combination $r_2 \parallel R$ becomes equal to zero. The small-signal transfer functions then reduce to

$$\frac{\hat{v}(s)}{\hat{v}_{control}(s)} = \frac{\dot{j}_2}{sC}$$

$$\frac{\hat{v}(s)}{\hat{v}_{g,rms}(s)} = \frac{g_2}{sC}$$

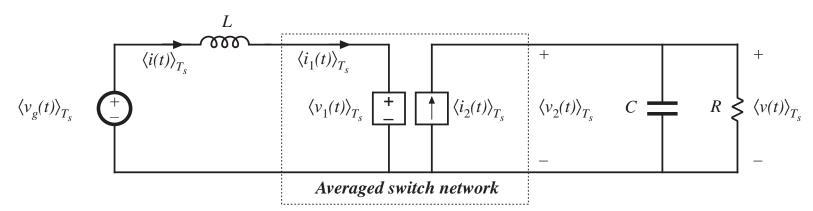18.3.2 Modeling the inner wide-bandwidth average current controller

Averaged (but not linearized) boost converter model, Fig. 7.42:



In Chapter 7, we perturbed and linearized using the assumptions

 $\left\langle v_g(t) \right\rangle_{T_s} = V_g + \hat{v}_g(t)$ $d(t) = D + \hat{d}(t) \implies d'(t) = D' - \hat{d}(t)$ $\left\langle i(t) \right\rangle_{T_{1}} = \left\langle i_{1}(t) \right\rangle_{T_{2}} = I + \hat{i}(t)$ $\left\langle v(t) \right\rangle_{T_{c}} = \left\langle v_{2}(t) \right\rangle_{T_{c}} = V + \hat{v}(t)$ $\left\langle v_1(t) \right\rangle_{T_s} = V_1 + \hat{v}_1(t)$ $\left\langle i_2(t) \right\rangle_{T_c} = I_2 + \hat{i}_2(t)$

Problem: variations in v_{g} , i_1 , and d are not small.

So we are faced with the design of a control system that exhibits significant nonlinear time-varying behavior.

ECEN5807 Power Electronics 2

35

Linearizing the equations of the boost rectifier

When the rectifier operates near steady-state, it is true that

$$\left\langle v(t) \right\rangle_{T_s} = V + \hat{v}(t)$$

with

$$\left| \hat{v}(t) \right| << \left| V \right|$$

In the special case of the boost rectifier, this is sufficient to linearize the equations of the average current controller.

The boost converter average inductor voltage is

$$L \frac{d\left\langle i_g(t)\right\rangle_{T_s}}{dt} = \left\langle v_g(t)\right\rangle_{T_s} - d'(t)V - d'(t)\hat{v}(t)$$

substitute:

$$L \frac{d\left\langle i_g(t)\right\rangle_{T_s}}{dt} = \left\langle v_g(t)\right\rangle_{T_s} - d'(t)V - d'(t)\hat{v}(t)$$

ECEN5807 Power Electronics 2


36 *Chapter 18: Low harmonic rectifier modeling and control*

Linearized boost rectifier model

$$L \frac{d\left\langle i_g(t)\right\rangle_{T_s}}{dt} = \left\langle v_g(t)\right\rangle_{T_s} - d'(t)V - d'(t)\hat{v}(t)$$

The nonlinear term is much smaller than the linear ac term. Hence, it can be discarded to obtain
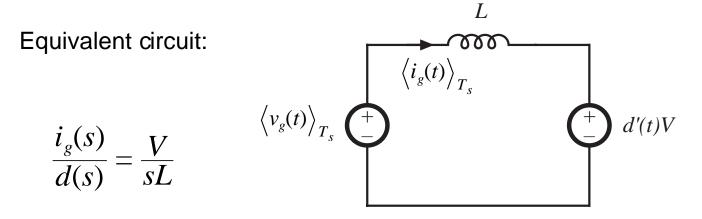
$$L \frac{d\left\langle i_g(t)\right\rangle_{T_s}}{dt} = \left\langle v_g(t)\right\rangle_{T_s} - d'(t)V$$



³⁷ *Chapter 18: Low harmonic rectifier modeling and control*

The above approach is not sufficient to linearize the equations needed to design the rectifier averaged current controllers of buck-boost, Cuk, SEPIC, and other converter topologies. These are truly nonlinear time-varying systems.

An approximate approach that is sometimes used in these cases: the *quasi-static approximation*

Assume that the ac line variations are much slower than the converter dynamics, so that the rectifier always operates near equilibrium. The quiescent operating point changes slowly along the input sinusoid, and we can find the slowly-varying "equilibrium" duty ratio as in Section 18.1.

The converter small-signal transfer functions derived in Chapters 7 and 8 are evaluated, using the time-varying operating point. The poles, zeroes, and gains vary slowly as the operating point varies. An average current controller is designed, that has a positive phase margin at each operating point.

Quasi-static approximation: discussion

In the literature, several authors have reported success using this method

Should be valid provided that the converter dynamics are sufficiently fast, such that the converter always operates near the assumed operating points

No good condition on system parameters, which can justify the approximation, is presently known for the basic converter topologies

It is well-understood in the field of control systems that, when the converter dynamics are not sufficiently fast, then the quasi-static approximation yields neither necessary nor sufficient conditions for stability. Such behavior can be observed in rectifier systems. Worst-case analysis to prove stability should employ simulations.

Chapter 19 Resonant Conversion

Introduction

19.1 Sinusoidal analysis of resonant converters

19.2 Examples

Series resonant converter Parallel resonant converter

19.3 Exact characteristics of the series and parallel resonant converters

19.4 Soft switching

Zero current switching Zero voltage switching The zero voltage transition converter

19.5 Load-dependent properties of resonant converters

1


Introduction to Resonant Conversion

Resonant power converters contain resonant L-C networks whose voltage and current waveforms vary sinusoidally during one or more subintervals of each switching period. These sinusoidal variations are large in magnitude, and the small ripple approximation does not apply.

Some types of resonant converters:


- Dc-to-high-frequency-ac inverters
- Resonant dc-dc converters
- Resonant inverters or rectifiers producing line-frequency ac

A basic class of resonant inverters

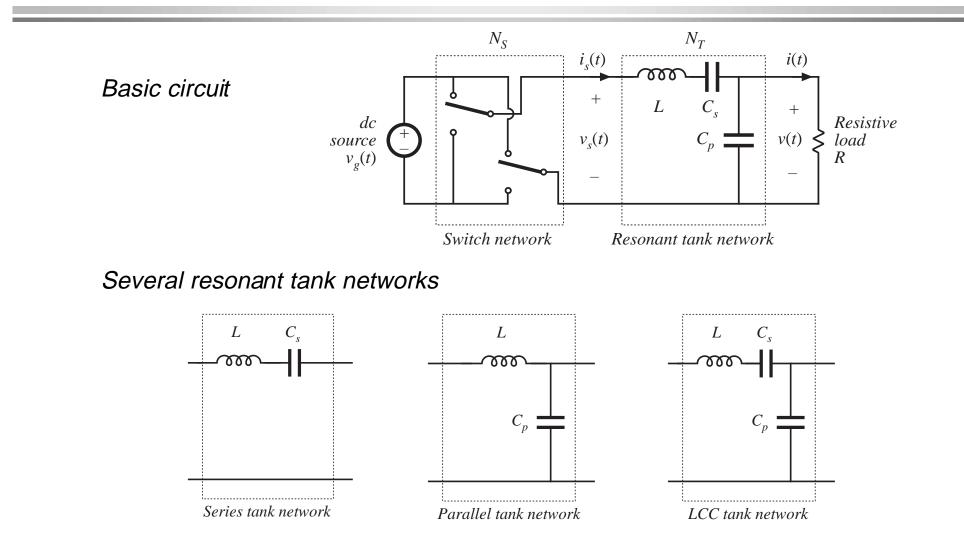

Fundamentals of Power Electronics

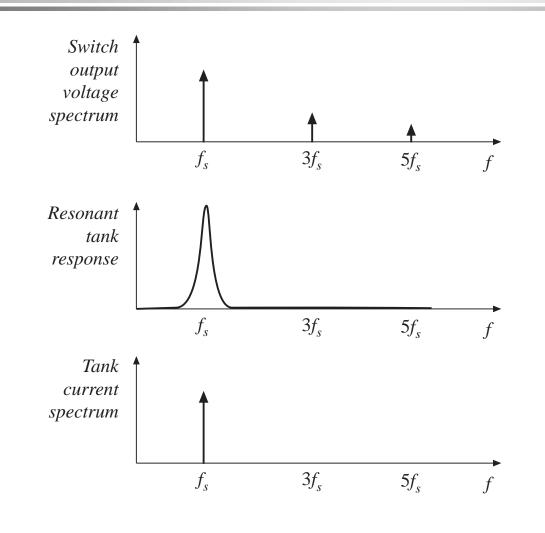Tank network responds only to fundamental component of switched waveforms




Tank current and output voltage are essentially sinusoids at the switching frequency f_s .

Output can be controlled by variation of switching frequency, closer to or away from the tank resonant frequency

Fundamentals of Power Electronics

Derivation of a resonant dc-dc converter

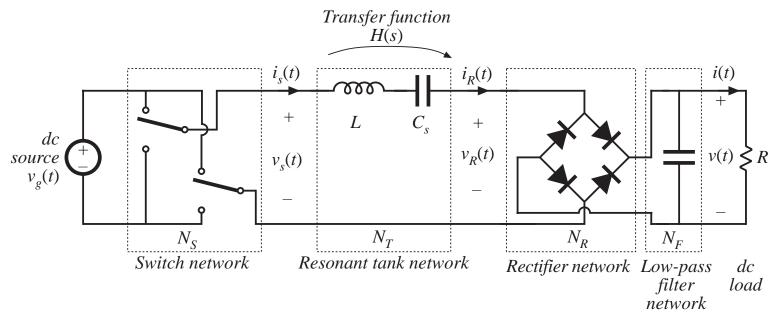
Rectify and filter the output of a dc-high-frequency-ac inverter




The series resonant dc-dc converter

A series resonant link inverter

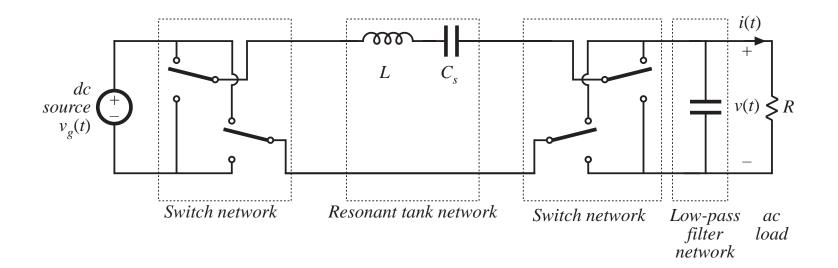Same as dc-dc series resonant converter, except output rectifiers are replaced with four-quadrant switches:



Quasi-resonant converters

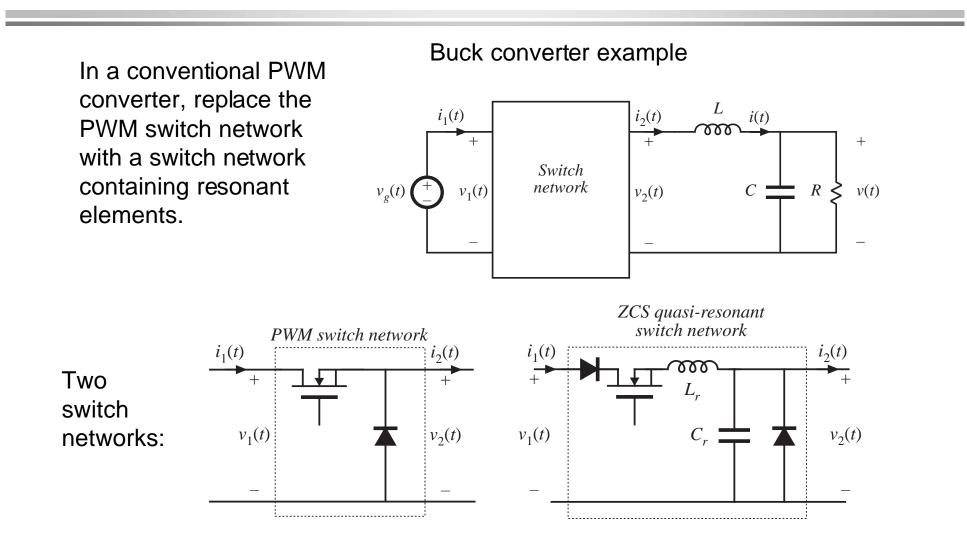

Fundamentals of Power Electronics

Chapter 19: Resonant Conversion

Resonant conversion: advantages

The chief advantage of resonant converters: reduced switching loss

Zero-current switching

Zero-voltage switching

Turn-on or turn-off transitions of semiconductor devices can occur at zero crossings of tank voltage or current waveforms, thereby reducing or eliminating some of the switching loss mechanisms. Hence resonant converters can operate at higher switching frequencies than comparable PWM converters

Zero-voltage switching also reduces converter-generated EMI

Zero-current switching can be used to commutate SCRs

In specialized applications, resonant networks may be unavoidable

High voltage converters: significant transformer leakage inductance and winding capacitance leads to resonant network

Resonant conversion: disadvantages

Can optimize performance at one operating point, but not with wide range of input voltage and load power variations

Significant currents may circulate through the tank elements, even when the load is disconnected, leading to poor efficiency at light load

Quasi-sinusoidal waveforms exhibit higher peak values than equivalent rectangular waveforms

These considerations lead to increased conduction losses, which can offset the reduction in switching loss


Resonant converters are usually controlled by variation of switching frequency. In some schemes, the range of switching frequencies can be very large

Complexity of analysis

Resonant conversion: Outline of discussion

- Simple steady-state analysis via sinusoidal approximation
- Simple and exact results for the series and parallel resonant converters
- Mechanisms of soft switching
- Circulating currents, and the dependence (or lack thereof) of conduction loss on load power
- Quasi-resonant converter topologies
- Steady-state analysis of quasi-resonant converters
- Ac modeling of quasi-resonant converters via averaged switch modeling

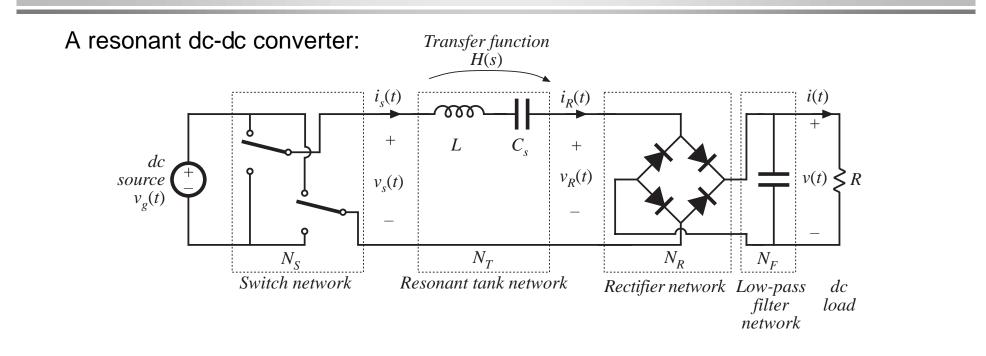
19.1 Sinusoidal analysis of resonant converters



If tank responds primarily to fundamental component of switch network output voltage waveform, then harmonics can be neglected.

Let us model all ac waveforms by their fundamental components.

The sinusoidal approximation

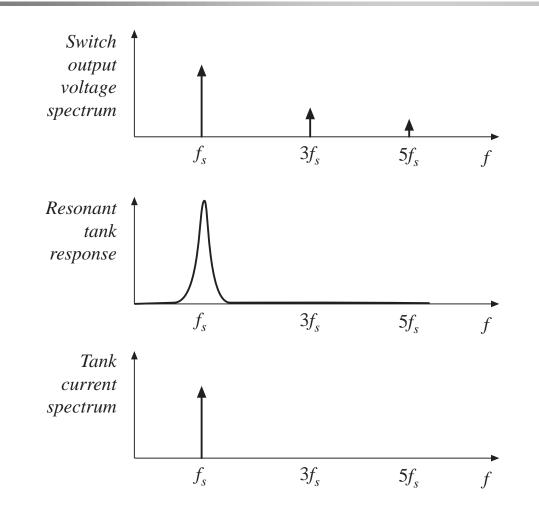


Tank current and output voltage are essentially sinusoids at the switching frequency f_s .

Neglect harmonics of switch output voltage waveform, and model only the fundamental component.

Remaining ac waveforms can be found via phasor analysis.

Fundamentals of Power Electronics


19.1.1 Controlled switch network model

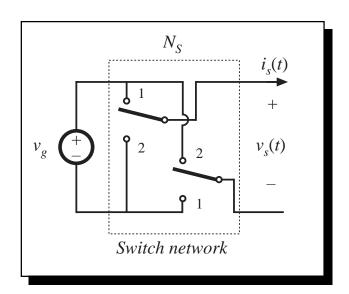

If the switch network produces a square wave, then its output voltage has the following Fourier series:

$$v_s(t) = \frac{4V_g}{\pi} \sum_{n=1, 3, 5, \dots} \frac{1}{n} \sin(n\omega_s t)$$

Fundamentals of Power Electronics

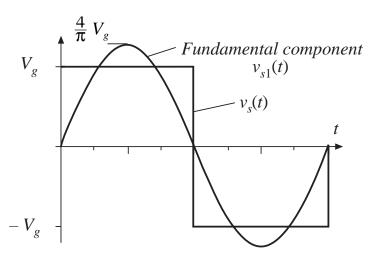


The fundamental component is

$$v_{s1}(t) = \frac{4V_g}{\pi} \sin(\omega_s t) = V_{s1} \sin(\omega_s t)$$

So model switch network output port with voltage source of value $v_{s1}(t)$

Model of switch network input port

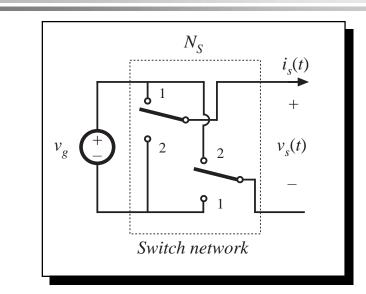

Assume that switch network output current is

 $i_s(t) \approx I_{s1} \sin (\omega_s t - \varphi_s)$

It is desired to model the dc component (average value) of the switch network input current.

Fundamentals of Power Electronics

$$f_{s1}$$


 $i_g(t)$
 ϕ_s
 ϕ_s

$$\left\langle i_g(t) \right\rangle_{T_s} = \frac{2}{T_s} \int_0^{T_s/2} i_g(\tau) d\tau$$

$$\approx \frac{2}{T_s} \int_0^{T_s/2} I_{s1} \sin\left(\omega_s \tau - \varphi_s\right) d\tau$$


$$= \frac{2}{\pi} I_{s1} \cos\left(\varphi_s\right)$$

Switch network: equivalent circuit

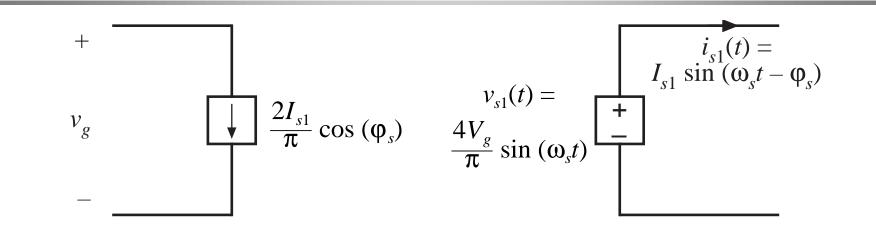

- Switch network converts dc to ac
- Dc components of input port waveforms are modeled
- Fundamental ac components of output port waveforms are modeled
- Model is power conservative: predicted average input and output powers are equal

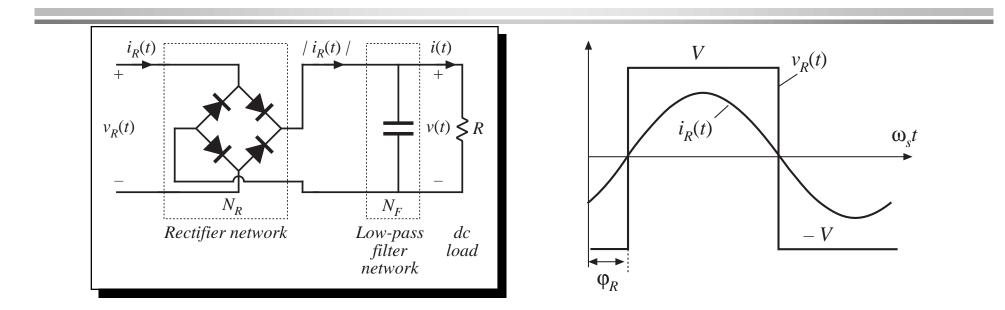19.1.2 Modeling the rectifier and capacitive filter networks



Assume large output filter capacitor, having small ripple.

 $v_R(t)$ is a square wave, having zero crossings in phase with tank output current $i_R(t)$. If $i_R(t)$ is a sinusoid: $i_R(t) = I_{R1} \sin (\omega_s t - \varphi_R)$

Then $v_R(t)$ has the following Fourier series:

$$v_R(t) = \frac{4V}{\pi} \sum_{n=1,3,5,\cdots}^{\infty} \frac{1}{n} \sin(n\omega_s t - \varphi_R)$$

Fundamentals of Power Electronics


Sinusoidal approximation: rectifier


Again, since tank responds only to fundamental components of applied waveforms, harmonics in $v_R(t)$ can be neglected. $v_R(t)$ becomes

$$v_{R1}(t) = \frac{4V}{\pi} \sin (\omega_s t - \varphi_R) = V_{R1} \sin (\omega_s t - \varphi_R)$$

Actual waveforms


with harmonics ignored

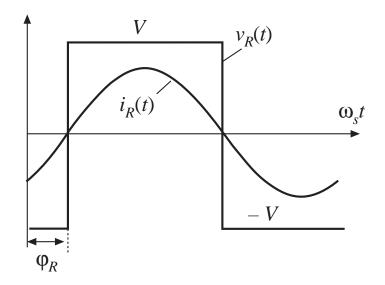

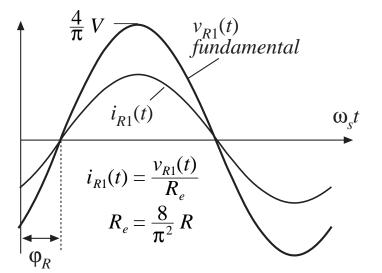

Fundamentals of Power Electronics

Rectifier dc output port model

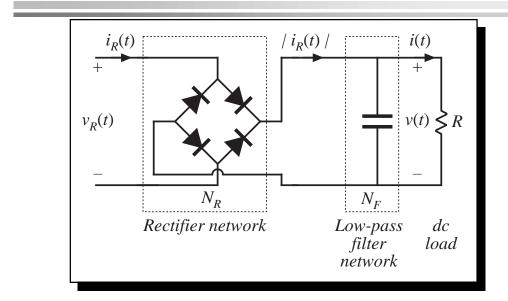

V $v_R(t)$ $w_R(t)$ $w_S t$ -V Output capacitor charge balance: dc load current is equal to average rectified tank output current

$$\left\langle \left| i_{R}(t) \right| \right\rangle_{T_{s}} = I$$

Hence

$$I = \frac{2}{T_s} \int_0^{T_s/2} I_{R1} \left| \sin \left(\omega_s t - \varphi_R \right) \right| dt$$
$$= \frac{2}{\pi} I_{R1}$$

Equivalent circuit of rectifier

Rectifier input port:

Fundamental components of current and voltage are sinusoids that are in phase

Hence rectifier presents a resistive load to tank network

Effective resistance R_e is


$$R_e = \frac{v_{R1}(t)}{i_R(t)} = \frac{8}{\pi^2} \frac{V}{I}$$

 $i_{R1}(t)$ + $v_{R1}(t)$ $R_{e} \neq \frac{2}{\pi} I_{R1}$ - $R_{e} = \frac{8}{\pi^{2}} R$ Rectifier equivalent circuit

With a resistive load R, this becomes

$$R_e = \frac{8}{\pi^2} R = 0.8106R$$

19.1.3 Resonant tank network

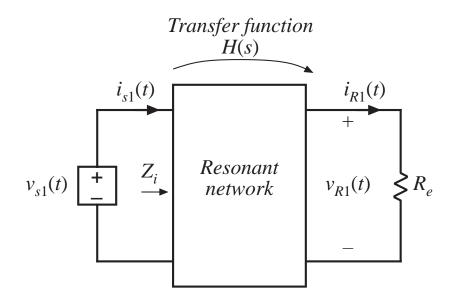

Model of ac waveforms is now reduced to a linear circuit. Tank network is excited by effective sinusoidal voltage (switch network output port), and is load by effective resistive load (rectifier input port).

Can solve for transfer function via conventional linear circuit analysis.

Solution of tank network waveforms

Transfer function:

$$\frac{v_{R1}(s)}{v_{s1}(s)} = H(s)$$

Ratio of peak values of input and output voltages:


$$\frac{V_{R1}}{V_{s1}} = \left\| H(s) \right\|_{s = j\omega_s}$$

Solution for tank output current:


$$i_R(s) = \frac{v_{R1}(s)}{R_e} = \frac{H(s)}{R_e} v_{s1}(s)$$

which has peak magnitude

$$I_{R1} = \frac{\left\| H(s) \right\|_{s=j\omega_s}}{R_e} V_{s1}$$

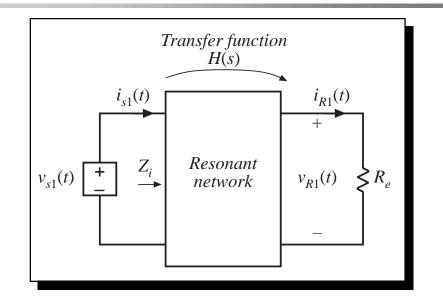

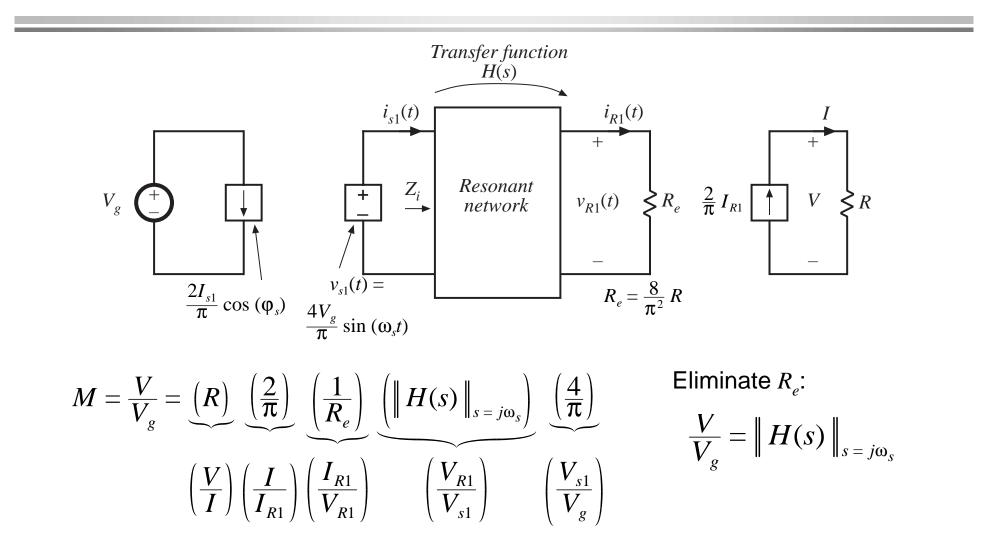19.1.4 Solution of converter voltage conversion ratio $M = V/V_g$




Fundamentals of Power Electronics

Conversion ratio *M*


$$\frac{V}{V_g} = \left\| H(s) \right\|_{s = j\omega_s}$$

So we have shown that the conversion ratio of a resonant converter, having switch and rectifier networks as in previous slides, is equal to the magnitude of the tank network transfer function. This transfer function is evaluated with the tank loaded by the effective rectifier input resistance R_{e} .

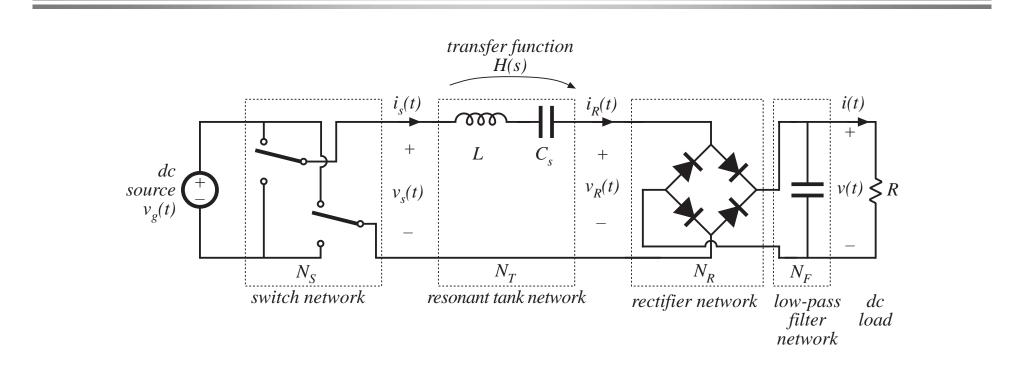
19.2 Examples19.2.1 Series resonant converter




Model: series resonant converter

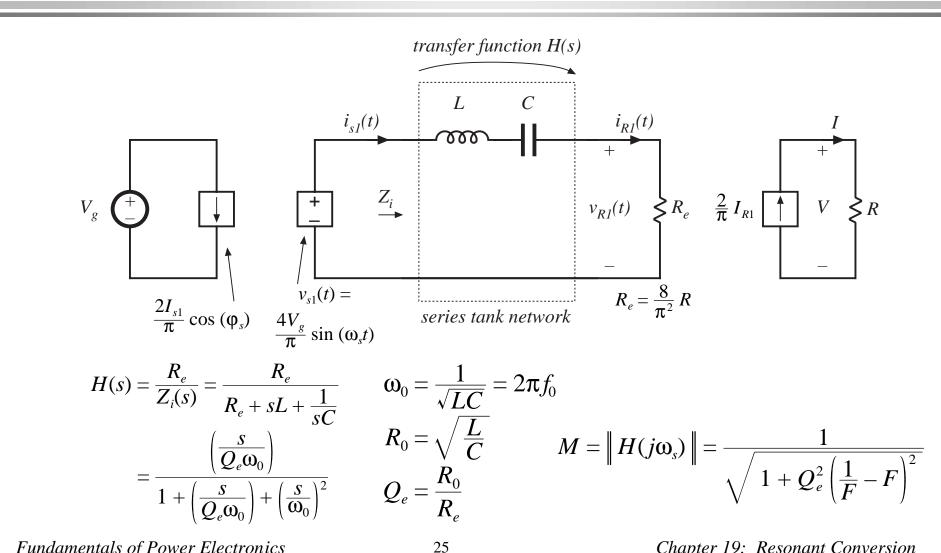


Construction of Z_i

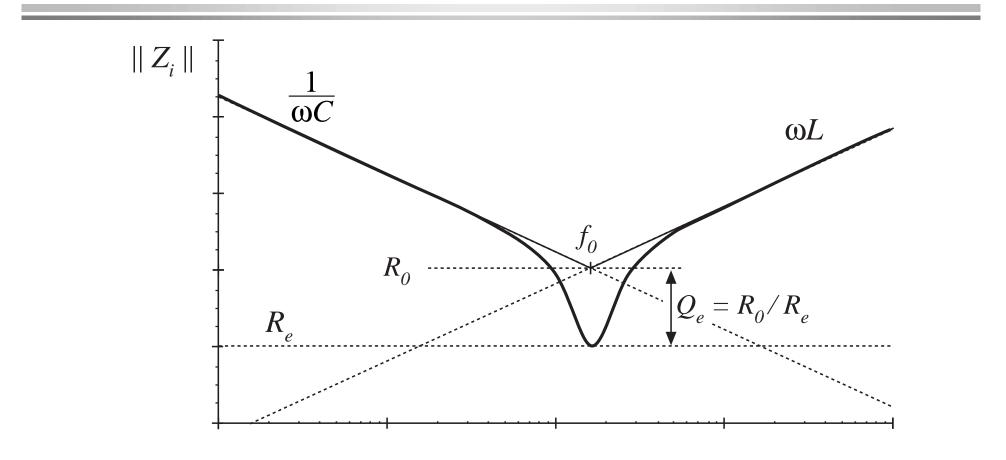

Construction of *H*

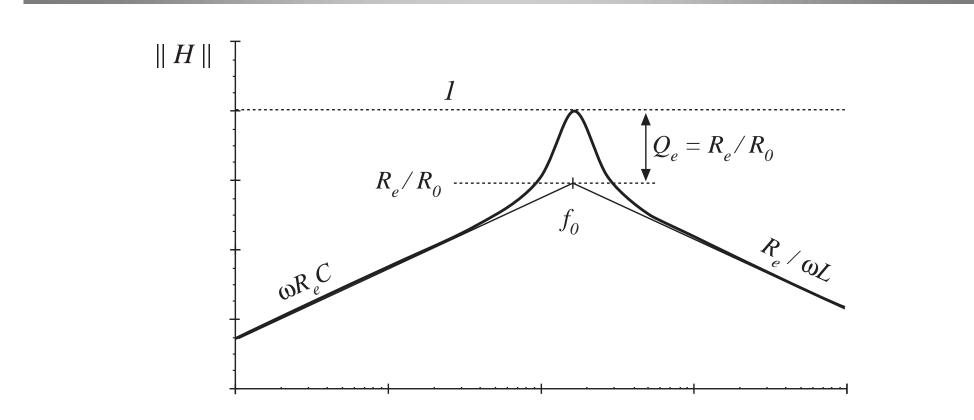

19.2.2 Subharmonic modes of the SRC

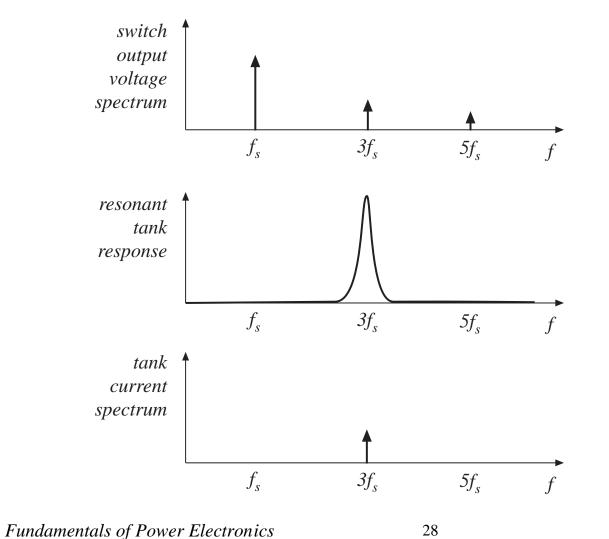

Example: excitation of tank by third harmonic of switching frequency


Can now approximate $v_s(t)$ by its third harmonic:

$$v_s(t) \approx v_{sn}(t) = \frac{4V_g}{n\pi} \sin(n\omega_s t)$$


Result of analysis:

$$M = \frac{V}{V_g} = \frac{\left\| H(jn\omega_s) \right\|}{n}$$

Subharmonic modes of SRC

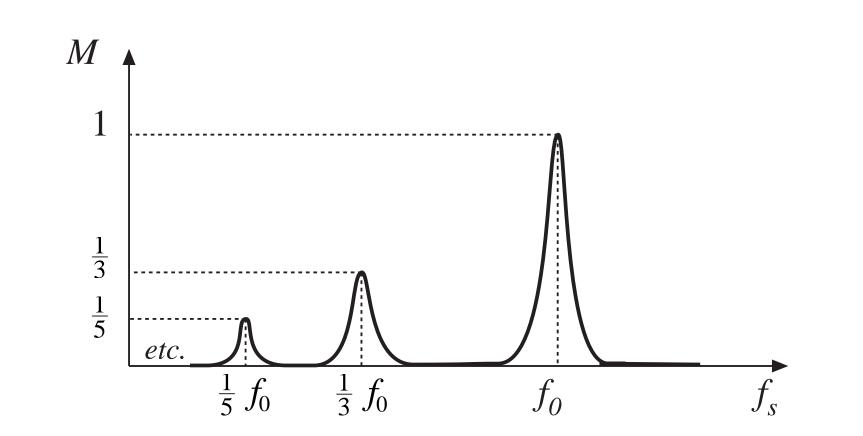

19.2.3 Parallel resonant dc-dc converter

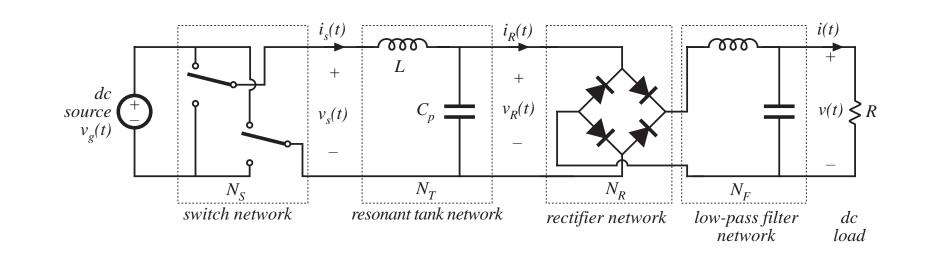


Differs from series resonant converter as follows:

Different tank network

Rectifier is driven by sinusoidal voltage, and is connected to inductive-input low-pass filter

Need a new model for rectifier and filter networks

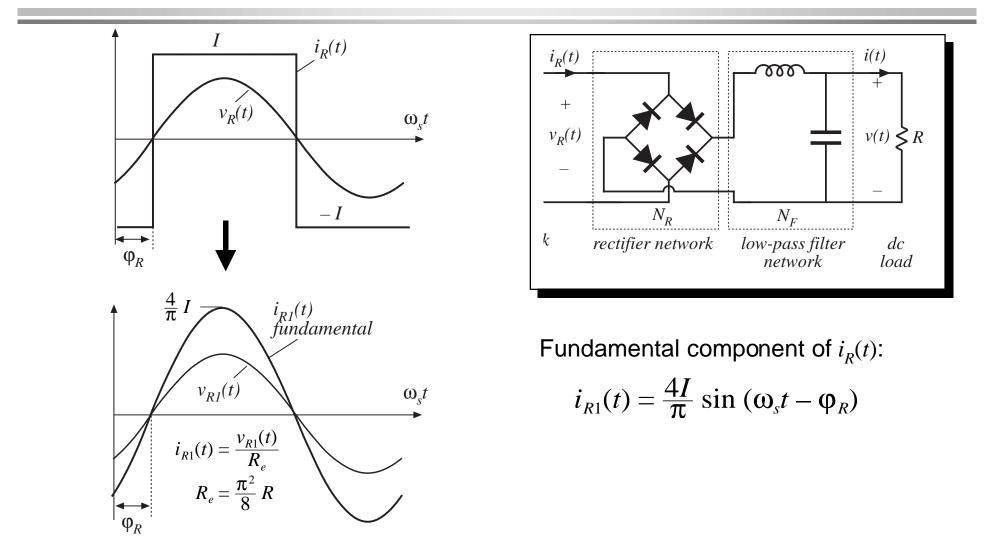Model of uncontrolled rectifier with inductive filter network



Fundamentals of Power Electronics

Effective resistance R_e

Again define

$$R_e = \frac{v_{R1}(t)}{i_{R1}(t)} = \frac{\pi V_{R1}}{4I}$$


In steady state, the dc output voltage V is equal to the average value of $|v_R|$:

$$V = \frac{2}{T_s} \int_0^{T_s/2} V_{R1} \left| \sin \left(\omega_s t - \varphi_R \right) \right| dt = \frac{2}{\pi} V_{R1}$$


For a resistive load, V = IR. The effective resistance R_e can then be expressed

$$R_e = \frac{\pi^2}{8} R = 1.2337R$$

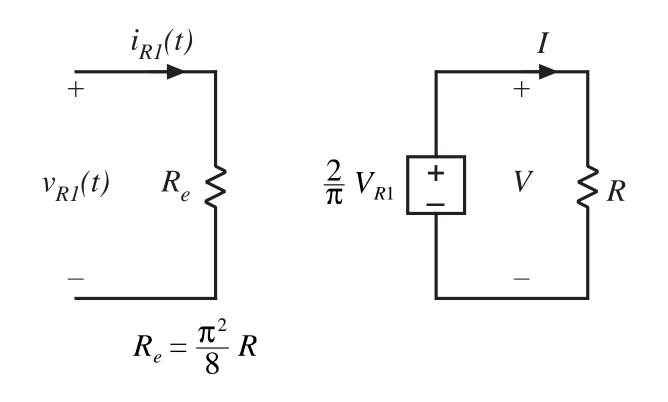Equivalent circuit model of uncontrolled rectifier with inductive filter network




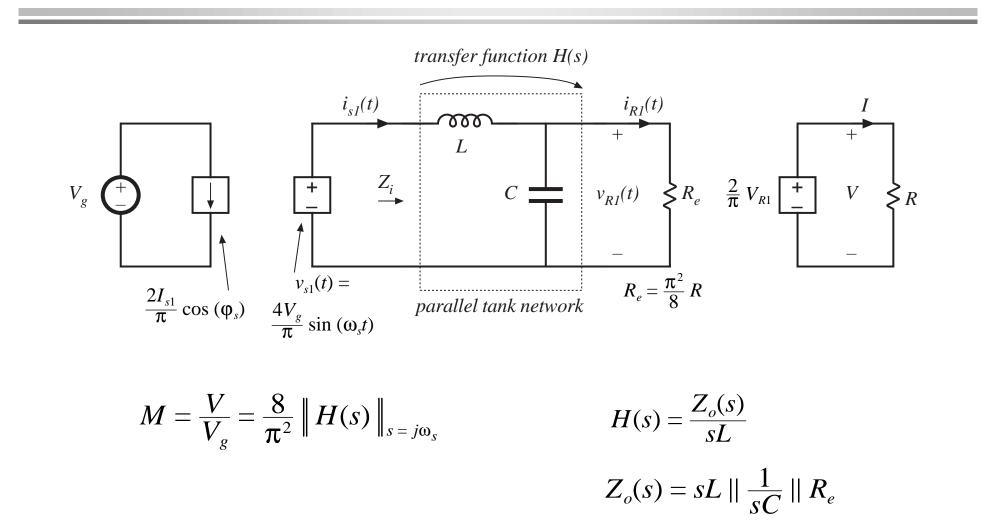Equivalent circuit model Parallel resonant dc-dc converter




Fundamentals of Power Electronics

Construction of Z_o

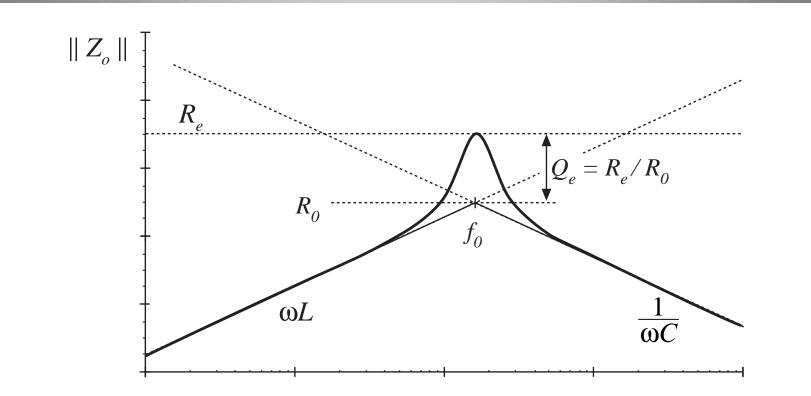

Construction of H

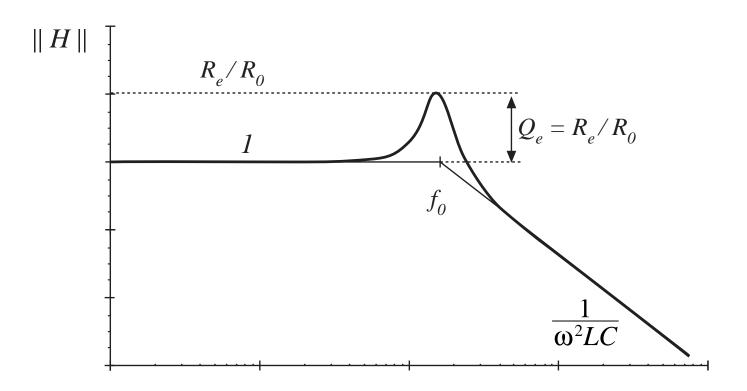

Dc conversion ratio of the PRC

$$M = \frac{8}{\pi^2} \left\| \frac{Z_o(s)}{sL} \right\|_{s=j\omega_s} = \frac{8}{\pi^2} \left\| \frac{1}{1 + \frac{s}{Q_e \omega_0} + \left(\frac{s}{\omega_0}\right)^2} \right\|_{s=j\omega_s}$$
$$= \frac{8}{\pi^2} \frac{1}{\sqrt{\left(1 - F^2\right)^2 + \left(\frac{F}{Q_e}\right)^2}}$$


At resonance, this becomes

$$M = \frac{8}{\pi^2} \frac{R_e}{R_0} = \frac{R}{R_0}$$


- PRC can step up the voltage, provided $R > R_0$
- PRC can produce *M* approaching infinity, provided output current is limited to value less than V_g / R_0

19.3 Exact characteristics of the series and parallel resonant dc-dc converters

Define

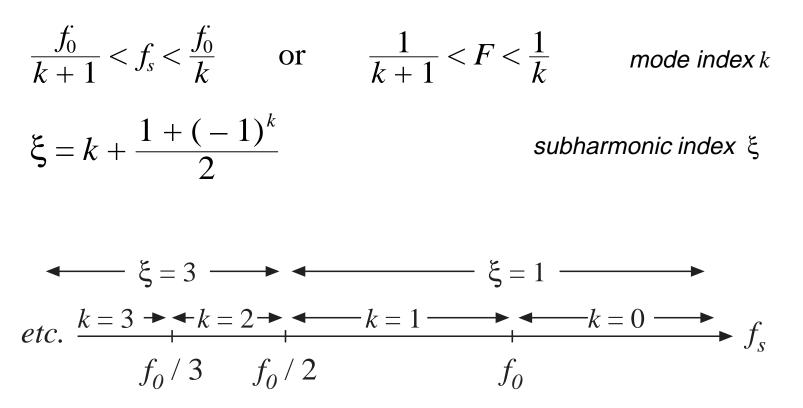

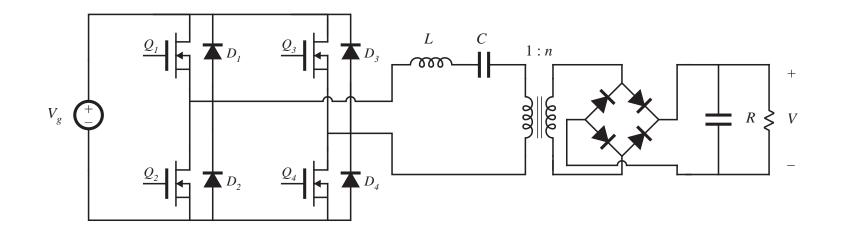19.3.1 Exact characteristics of the series resonant converter




Normalized load voltage and current:

$$M = \frac{V}{nV_g} \qquad \qquad J = \frac{InR_0}{V_g}$$

Continuous conduction mode, SRC

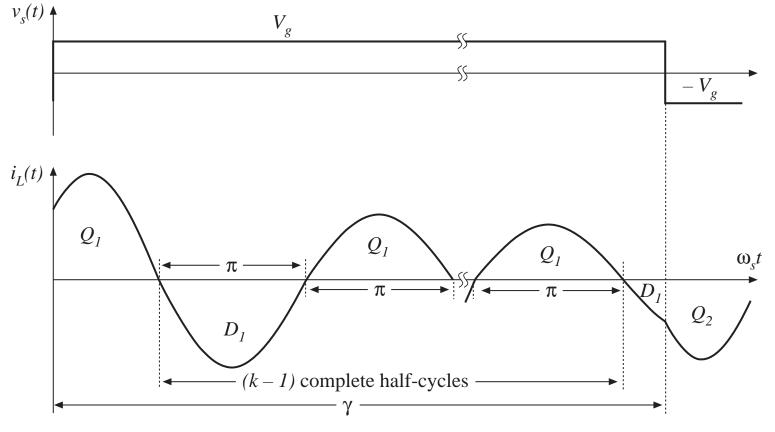Tank current rings continuously for entire length of switching period Waveforms for type k CCM, odd k:




Fundamentals of Power Electronics

40

Series resonant converter

Waveforms for type k CCM, even k:

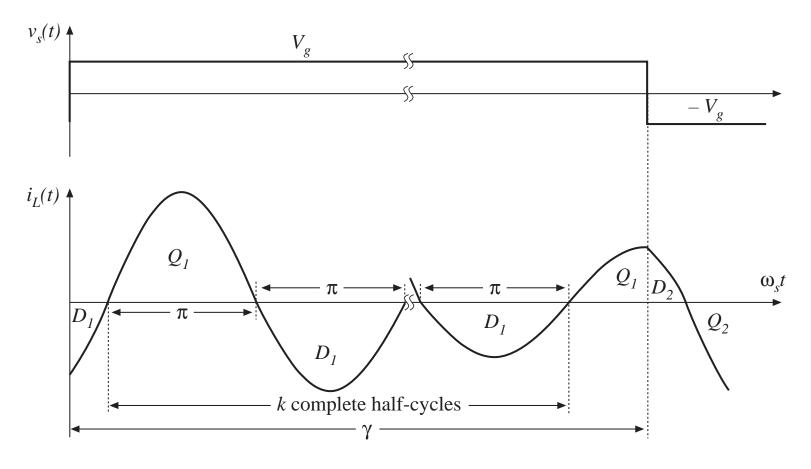

Fundamentals of Power Electronics

Exact steady-state solution, CCM Series resonant converter

$$M^{2}\xi^{2}\sin^{2}\left(\frac{\gamma}{2}\right) + \frac{1}{\xi^{2}}\left(\frac{J\gamma}{2} + (-1)^{k}\right)^{2}\cos^{2}\left(\frac{\gamma}{2}\right) = 1$$

where

$$M = \frac{V}{nV_g} \qquad J = \frac{InR_0}{V_g}$$
$$\gamma = \frac{\omega_0 T_s}{2} = \frac{\pi}{F}$$

- Output characteristic, i.e., the relation between *M* and *J*, is elliptical
- *M* is restricted to the range

$$0 \le M \le \frac{1}{\xi}$$

Fundamentals of Power Electronics

Control-plane characteristics


For a resistive load, eliminate J and solve for M vs. γ

$$M = \frac{\left(\frac{Q\gamma}{2}\right)}{\xi^4 \tan^2\left(\frac{\gamma}{2}\right) + \left(\frac{Q\gamma}{2}\right)^2} \left[(-1)^{k+1} + \sqrt{1 + \frac{\left[\xi^2 - \cos^2\left(\frac{\gamma}{2}\right)\right] \left[\xi^4 \tan^2\left(\frac{\gamma}{2}\right) + \left(\frac{Q\gamma}{2}\right)^2\right]}{\left(\frac{Q\gamma}{2}\right)^2 \cos^2\left(\frac{\gamma}{2}\right)}} \right]$$

Exact, closed-form, valid for any CCM

Discontinuous conduction mode

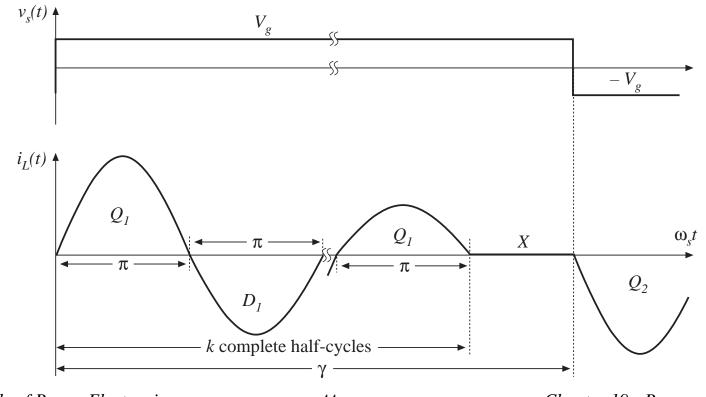Type k DCM: during each half-switching-period, the tank rings for k complete half-cycles. The output diodes then become reverse-biased for the remainder of the half-switching-period.



Fundamentals of Power Electronics

Chapter 19: Resonant Conversion

Steady-state solution: type *k* DCM, odd *k*

$$M = \frac{1}{k}$$

Conditions for operation in type k DCM, odd k:

$$f_s < \frac{f_0}{k}$$
$$\frac{2(k+1)}{\gamma} > J > \frac{2(k-1)}{\gamma}$$


Steady-state solution: type *k* DCM, even *k*

$$J = \frac{2k}{\gamma}$$


Conditions for operation in type k DCM, even k:

$$f_s < \frac{f_0}{k}$$
$$\frac{1}{k-1} > M > \frac{1}{k+1}$$

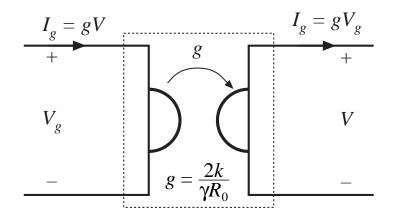gyrator model, SRC operating in an even DCM:




Control plane characteristics, SRC

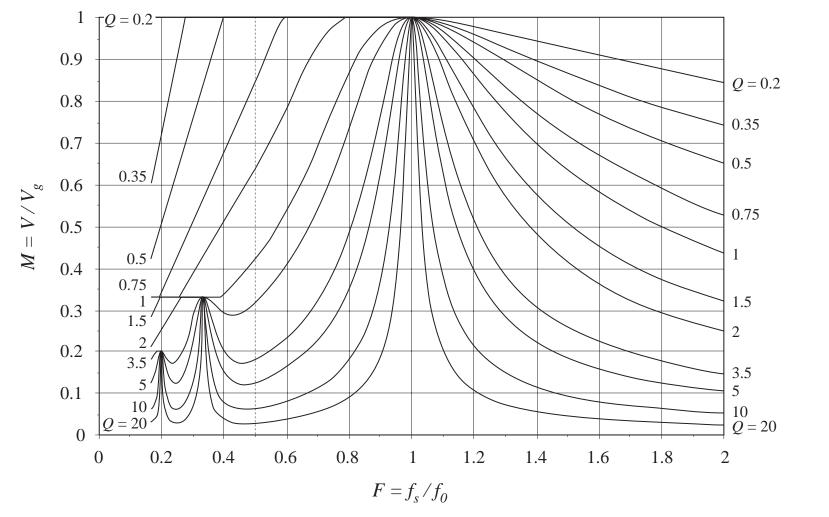


Fundamentals of Power Electronics

Mode boundaries, SRC

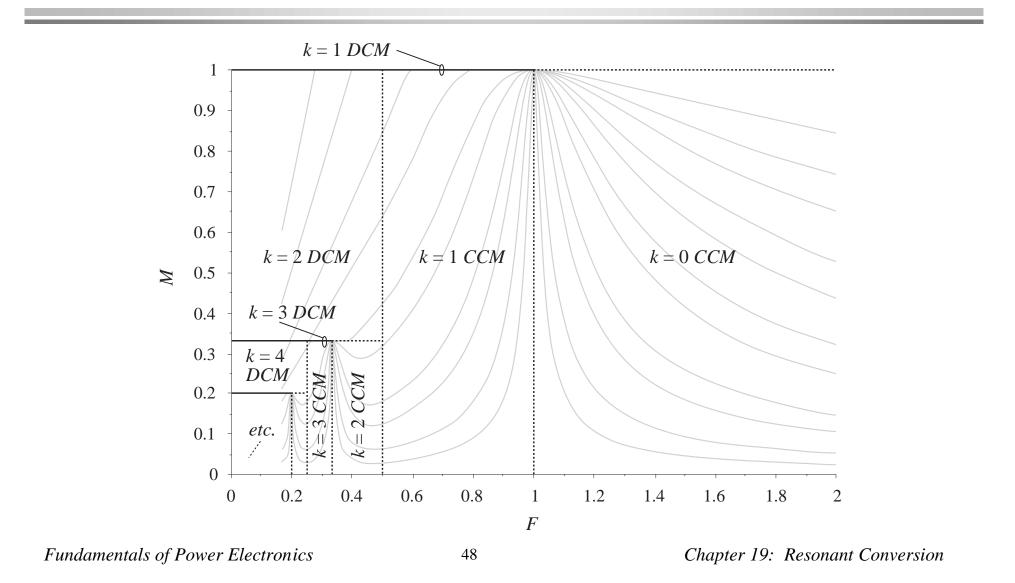


Output characteristics, SRC above resonance

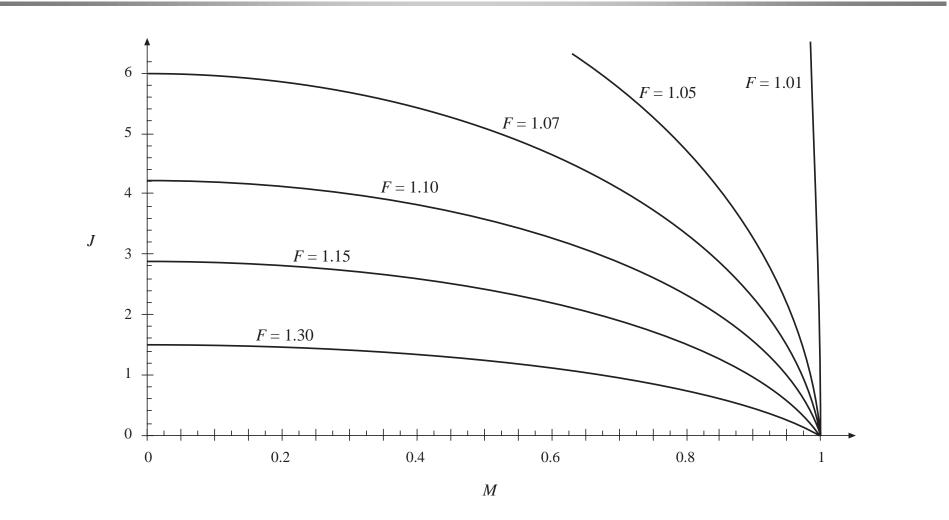


Chapter 19: Resonant Conversion

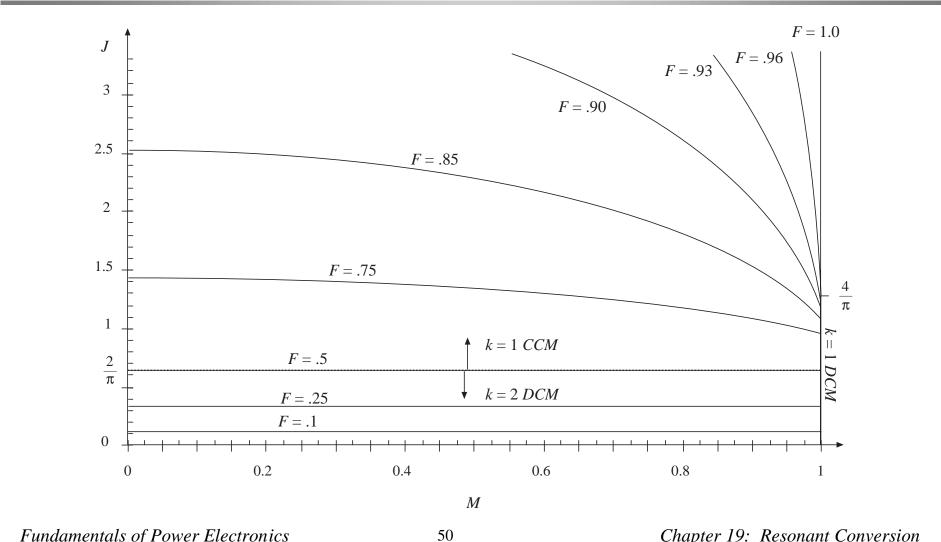Output characteristics, SRC below resonance



Fundamentals of Power Electronics

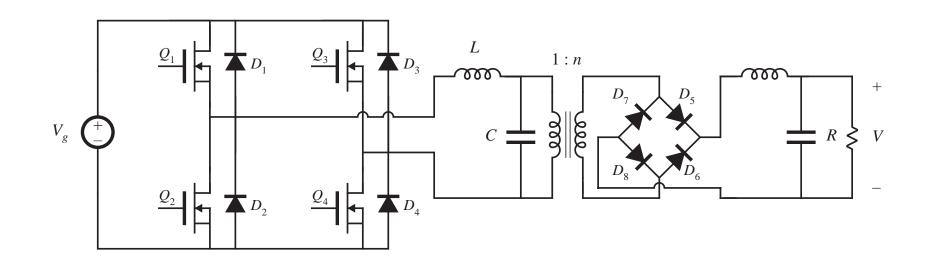19.3.2 Exact characteristics of the parallel resonant converter




Normalized load voltage and current:


$$M = \frac{V}{nV_g} \qquad \qquad J = \frac{InR_0}{V_g}$$

Fundamentals of Power Electronics

Parallel resonant converter in CCM

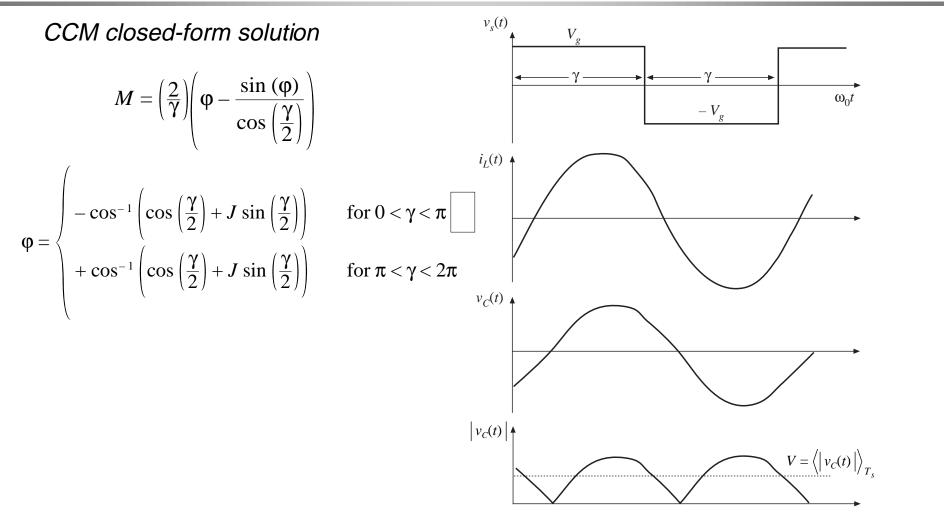


Parallel resonant converter in DCM

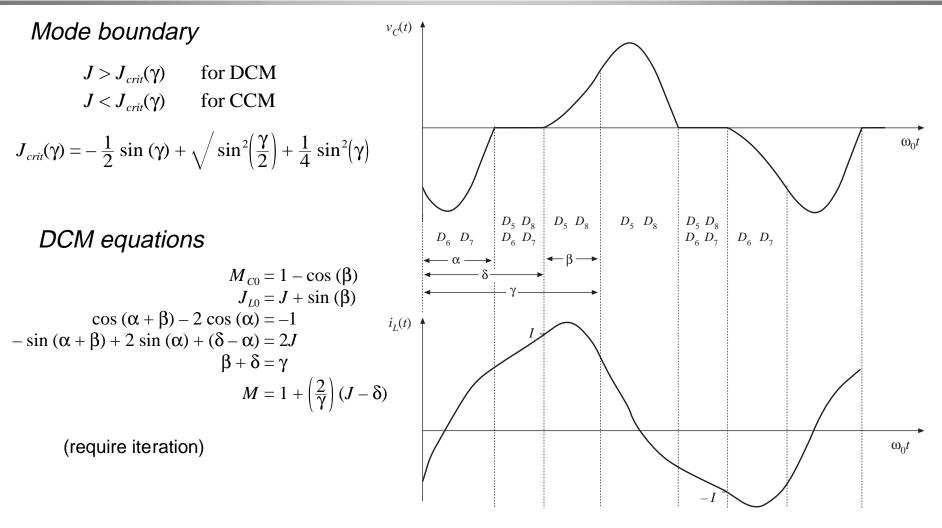


Fundamentals of Power Electronics

Output characteristics of the PRC

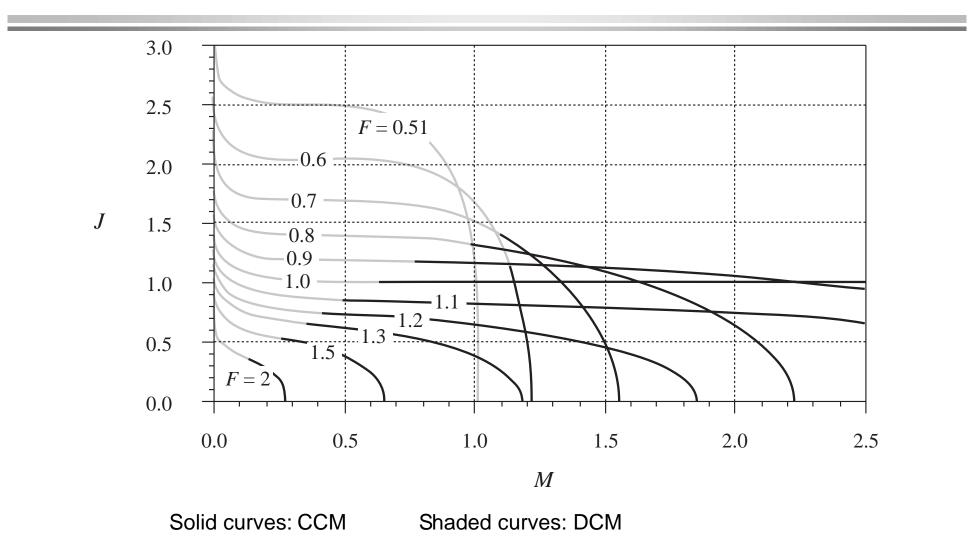

Fundamentals of Power Electronics

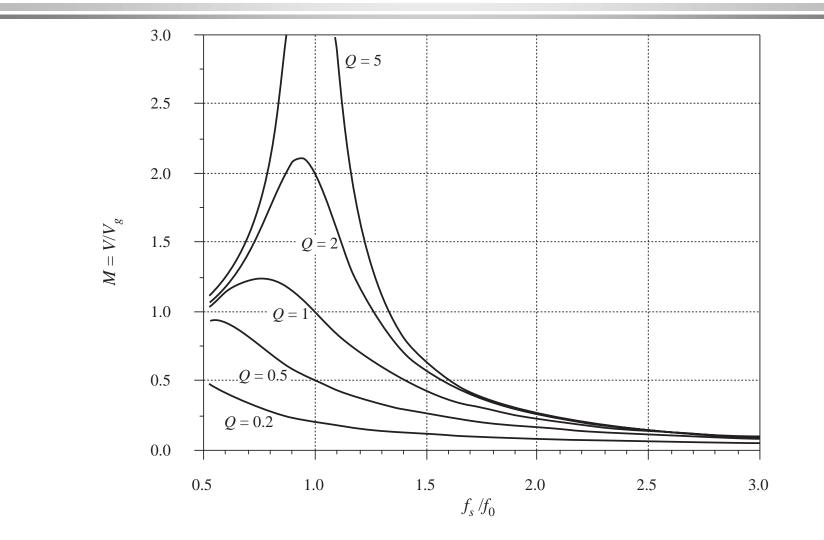Control characteristics of the PRC with resistive load



Fundamentals of Power Electronics

19.4 Soft switching

Soft switching can mitigate some of the mechanisms of switching loss and possibly reduce the generation of EMI

Semiconductor devices are switched on or off at the zero crossing of their voltage or current waveforms:

Zero-current switching: transistor turn-off transition occurs at zero current. Zero-current switching eliminates the switching loss caused by IGBT current tailing and by stray inductances. It can also be used to commutate SCR's.


Zero-voltage switching: transistor turn-on transition occurs at zero voltage. Diodes may also operate with zero-voltage switching. Zero-voltage switching eliminates the switching loss induced by diode stored charge and device output capacitances.

Zero-voltage switching is usually preferred in modern converters.

Zero-voltage transition converters are modified PWM converters, in which an inductor charges and discharges the device capacitances. Zero-voltage switching is then obtained.

19.4.1 Operation of the full bridge below resonance: Zero-current switching

Series resonant converter example

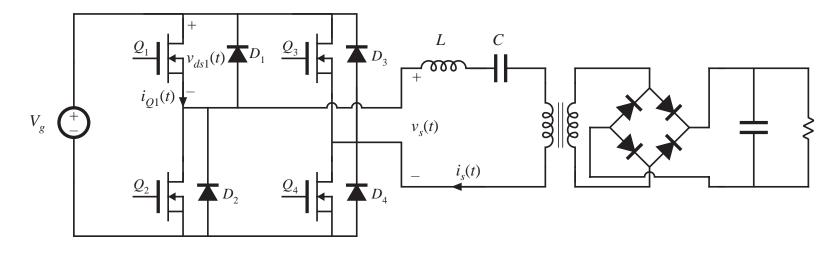


Operation below resonance: input tank current leads voltage Zero-current switching (ZCS) occurs

Tank input impedance


Operation below resonance: tank input impedance Z_i is dominated by tank capacitor.

 $\angle Z_i$ is positive, and tank input current leads tank input voltage.

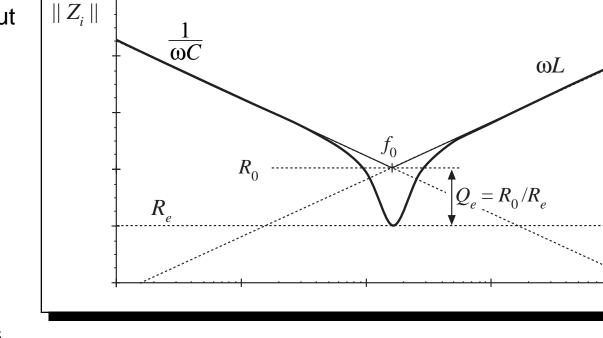Zero crossing of the tank input current waveform $i_s(t)$ occurs before the zero crossing of the voltage $v_s(t)$.




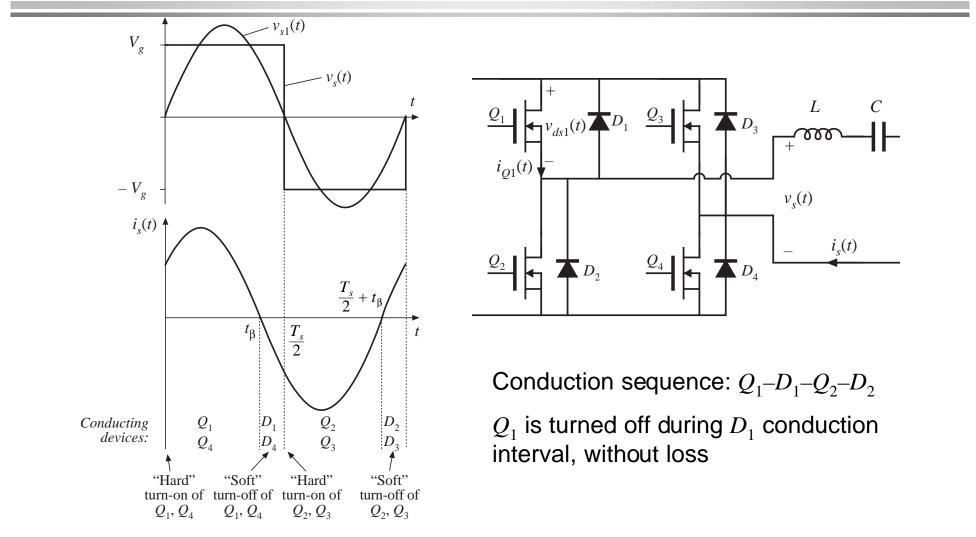
Switch network waveforms, below resonance Zero-current switching



Fundamentals of Power Electronics

ZCS turn-on transition: hard switching

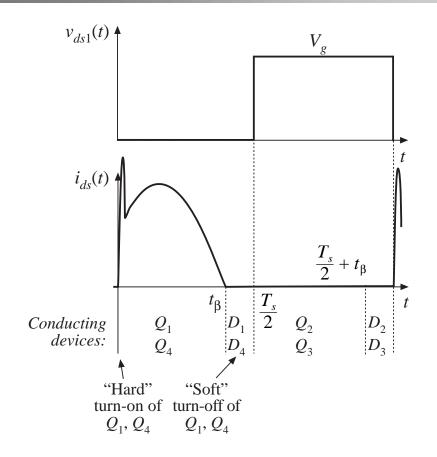


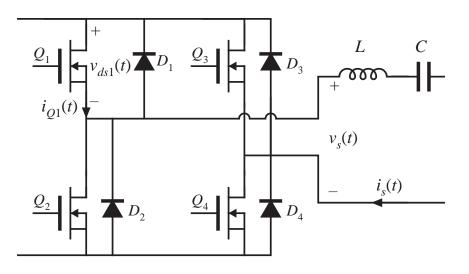

 Q_1 turns on while D_2 is conducting. Stored charge of D_2 and of semiconductor output capacitances must be removed. Transistor turn-on transition is identical to hardswitched PWM, and switching loss occurs.

19.4.2 Operation of the full bridge below resonance: Zero-voltage switching

Series resonant converter example

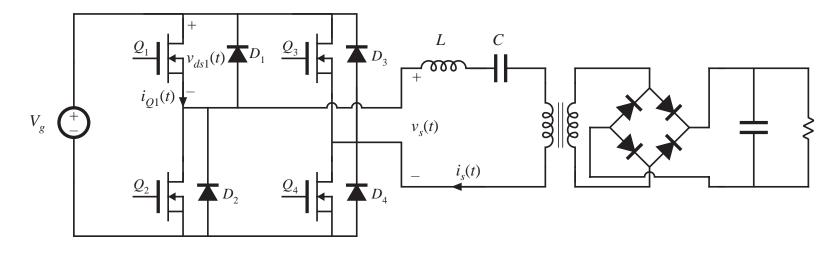


Operation above resonance: input tank current lags voltage Zero-voltage switching (ZVS) occurs

Tank input impedance


Operation above resonance: tank input impedance Z_i is dominated by tank inductor.

 $\angle Z_i$ is negative, and tank input current lags tank input voltage.

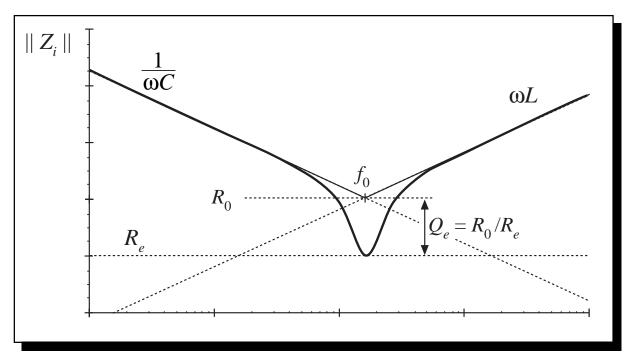Zero crossing of the tank input current waveform $i_s(t)$ occurs after the zero crossing of the voltage $v_s(t)$.




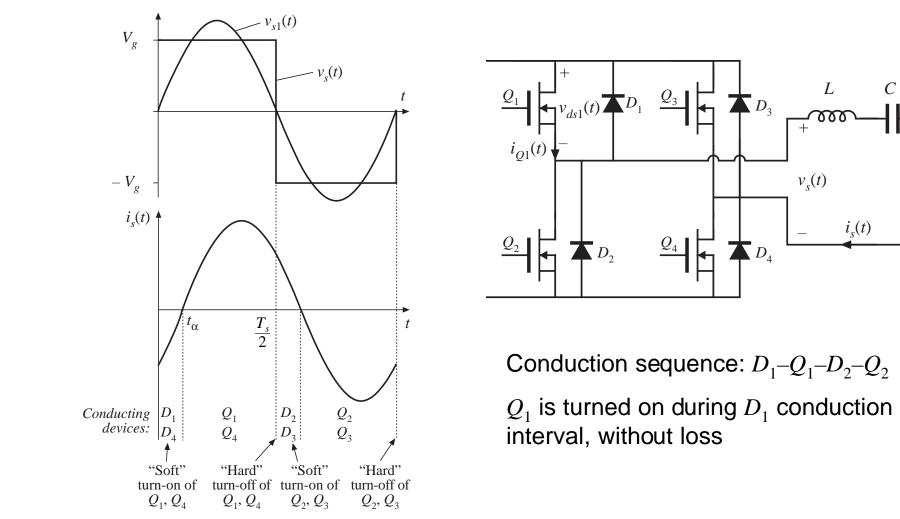
Switch network waveforms, above resonance Zero-voltage switching



Fundamentals of Power Electronics

ZVS turn-off transition: hard switching?

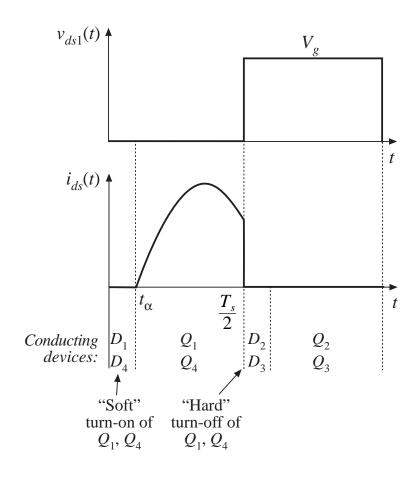


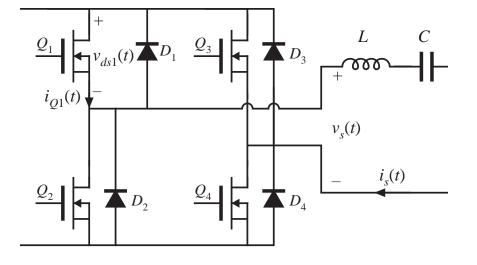

When Q_1 turns off, D_2 must begin conducting. Voltage across Q_1 must increase to V_g . Transistor turn-off transition is identical to hard-switched PWM. Switching loss may occur (but see next slide).

Fundamentals of Power Electronics

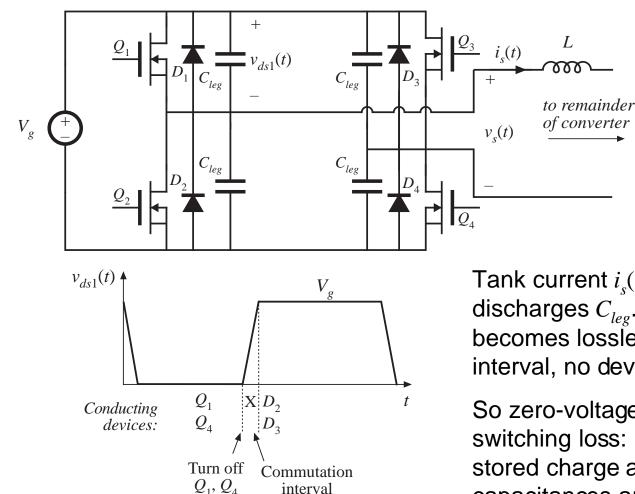Soft switching at the ZVS turn-off transition



interval

Fundamentals of Power Electronics

Introduce small capacitors C_{leg} across each device (or use device output capacitances).

Introduce delay ۲ between turn-off of Q_1 and turn-on of Q_2 .

Tank current $i_s(t)$ charges and discharges C_{leg} . Turn-off transition becomes lossless. During commutation interval, no devices conduct.

So zero-voltage switching exhibits low switching loss: losses due to diode stored charge and device output capacitances are eliminated.

19.4.3 The zero-voltage transition converter

Basic version based on full-bridge PWM buck converter Q_3 L_{c} $i_c(t)$ D_1 000 000 C_{leg} C_{leo} 22 V_{g} 000 +200 C_{leg} C_{leg} $v_2(t)$ ≯ Q_4 $v_2(t)$ V_{g} Can obtain ZVS of all primary-Can turn on Q_1 at zero voltage side MOSFETs and diodes Secondary-side diodes switch at Conducting Q_2 $X D_1$ devices: zero-current, with loss Phase-shift control Turn off Commutation • Q_2 interval

19.5 Load-dependent properties of resonant converters

Resonant inverter design objectives:

- 1. Operate with a specified load characteristic and range of operating points
 - With a nonlinear load, must properly match inverter output characteristic to load characteristic
- 2. Obtain zero-voltage switching or zero-current switching
 - Preferably, obtain these properties at all loads
 - Could allow ZVS property to be lost at light load, if necessary
- 3. Minimize transistor currents and conduction losses
 - To obtain good efficiency at light load, the transistor current should scale proportionally to load current (in resonant converters, it often doesn't!)

Topics of Discussion Section 19.5

Inverter output *i*-*v* characteristics

Two theorems

- Dependence of transistor current on load current
- Dependence of zero-voltage/zero-current switching on load resistance
- Simple, intuitive frequency-domain approach to design of resonant converter

Examples and interpretation

- Series
- Parallel
- LCC

Inverter output characteristics

Let H_{∞} be the open-circuit $(R \rightarrow \infty)$ transfer function:

$$\frac{v_o(j\omega)}{v_i(j\omega)}\bigg|_{R\to\infty} = H_\infty(j\omega)$$


and let Z_{o0} be the output impedance (with $v_i \rightarrow$ short-circuit). Then,

$$v_o(j\omega) = H_{\infty}(j\omega) v_i(j\omega) \frac{\kappa}{R + Z_{o0}(j\omega)}$$

The output voltage magnitude is:

$$\|v_{o}\|^{2} = v_{o}v_{o}^{*} = \frac{\|H_{\infty}\|^{2} \|v_{i}\|^{2}}{\left(1 + \|Z_{o0}\|^{2} / R^{2}\right)}$$

with $R = \| v_o \| / \| i_o \|$ Fundamentals of Power Electronics

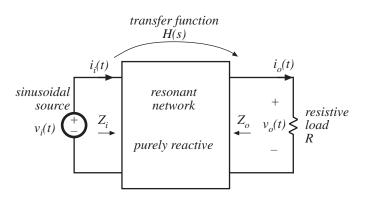


This result can be rearranged to obtain

$$v_{o} \|^{2} + \| i_{o} \|^{2} \| Z_{o0} \|^{2} = \| H_{\infty} \|^{2} \| v_{i} \|^{2}$$

Hence, at a given frequency, the output characteristic (i.e., the relation between $||v_o||$ and $||i_o||$) of any resonant inverter of this class is elliptical.

Inverter output characteristics

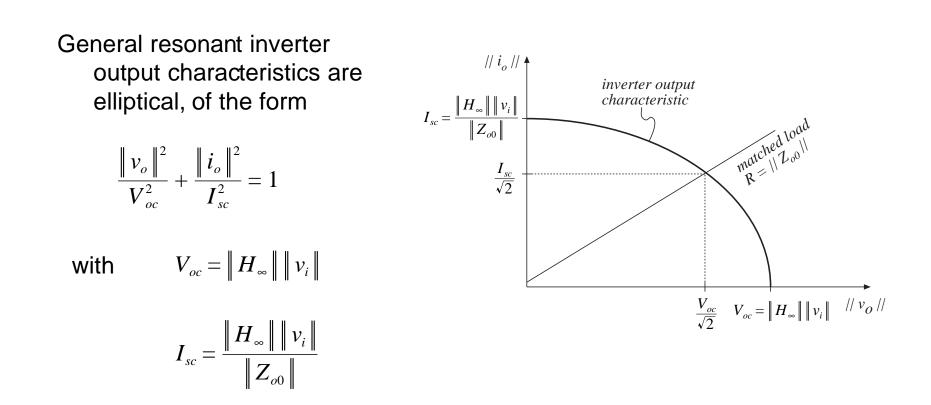


This result is valid provided that *(i)* the resonant network is purely reactive, and *(ii)* the load is purely resistive.


Fundamentals of Power Electronics

Matching ellipse to application requirements


Electronic ballast

Electrosurgical generator

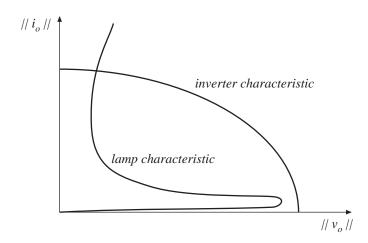

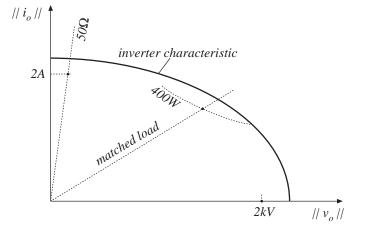

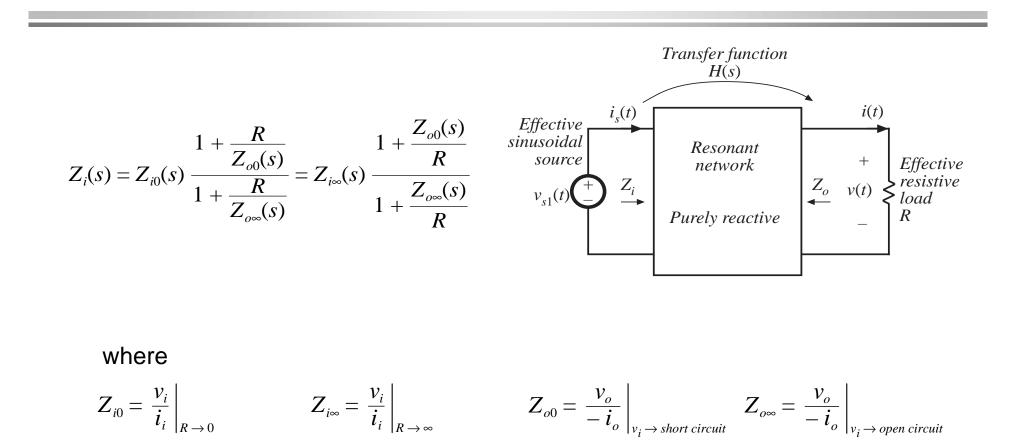Input impedance of the resonant tank network



Other relations

Reciprocity

$$\frac{Z_{i0}}{Z_{i\infty}} = \frac{Z_{o0}}{Z_{o\infty}}$$

Tank transfer function

$$H(s) = \frac{H_{\infty}(s)}{1 + \frac{R}{Z_{o0}}}$$

where $H_{\infty} = \frac{v_o(s)}{s}$

$$v_i(s) \Big|_{R \to \infty}$$
$$\|H_{\infty}\|^2 = Z_{o0} \left(\frac{1}{Z_{i0}} - \frac{1}{Z_{i\infty}}\right)$$

Fundamentals of Power Electronics

If the tank network is purely reactive, then each of its impedances and transfer functions have zero real

parts:


$$Z_{i0} = -Z_{i0}$$
$$Z_{i\infty} = -Z_{i\infty}^{*}$$
$$Z_{o0} = -Z_{o0}^{*}$$
$$Z_{o\infty} = -Z_{o\infty}^{*}$$
$$H_{\infty} = -H_{\infty}^{*}$$

 $7 - 7^*$

Hence, the input impedance magnitude is

$$\|Z_{i}\|^{2} = Z_{i}Z_{i}^{*} = \|Z_{i0}\|^{2} \frac{\left(1 + \frac{R^{2}}{\|Z_{o0}\|^{2}}\right)}{\left(1 + \frac{R^{2}}{\|Z_{o\infty}\|^{2}}\right)}$$

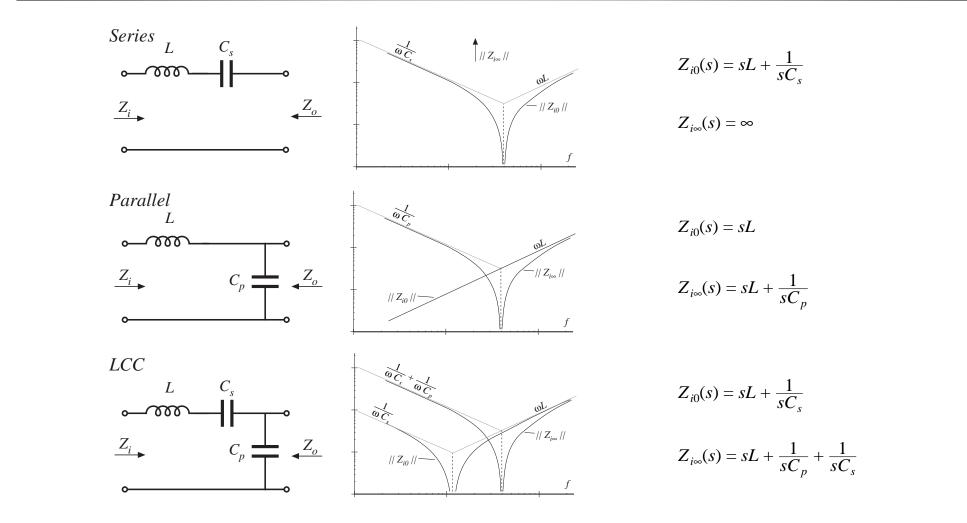Z_{i0} and $Z_{i\infty}$ for 3 common inverters



Fundamentals of Power Electronics

A Theorem relating transistor current variations to load resistance R

Theorem 1: If the tank network is purely reactive, then its input impedance $||Z_i||$ is a monotonic function of the load resistance *R*.

- So as the load resistance *R* varies from 0 to ∞, the resonant network input impedance || *Z_i* || varies monotonically from the short-circuit value || *Z_{i0}* || to the open-circuit value || *Z_{i∞}* ||.
- The impedances $|| Z_{i\infty} ||$ and $|| Z_{i0} ||$ are easy to construct.
- If you want to minimize the circulating tank currents at light load, maximize $|| Z_{i\infty} ||$.
- Note: for many inverters, $||Z_{i\infty}|| < ||Z_{i0}||$! The no-load transistor current is therefore greater than the short-circuit transistor current.

Proof of Theorem 1

Previously shown:

$$\|Z_{i}\|^{2} = \|Z_{i0}\|^{2} \frac{\left(1 + \frac{R}{\|Z_{o0}\|^{2}}\right)}{\left(1 + \frac{R}{\|Z_{o\infty}\|^{2}}\right)}$$

1

⇒ Differentiate: $\frac{d \|Z_i\|^2}{d R} = 2 \|Z_{i0}\|^2 \frac{\left(\frac{1}{\|Z_{o0}\|^2} - \frac{1}{\|Z_{o\infty}\|^2}\right)R}{\left(1 + \frac{R^2}{\|Z_{o\infty}\|^2}\right)^2}$

Derivative has roots at:

(*i*)
$$R = 0$$


(*ii*) $R = \infty$
(*iii*) $\|Z_{o0}\| = \|Z_{o\infty}\|$, or $\|Z_{i0}\| = \|Z_{i\infty}\|$

So the resonant network input impedance is a monotonic function of R, over the range $0 < R < \infty$.

In the special case $|| Z_{i0} || = || Z_{i\infty} ||$, $|| Z_i ||$ is independent of R.

Example: $| | Z_i | |$ of LCC

- for *f* < *f*_m, || *Z_i* || increases with increasing *R*.
- for f > f_m, || Z_i || decreases with increasing R.
- at a given frequency f, || Z_i || is a monotonic function of R.
- It's not necessary to draw the entire plot: just construct $|| Z_{i0} ||$ and $|| Z_{i\infty} ||$.

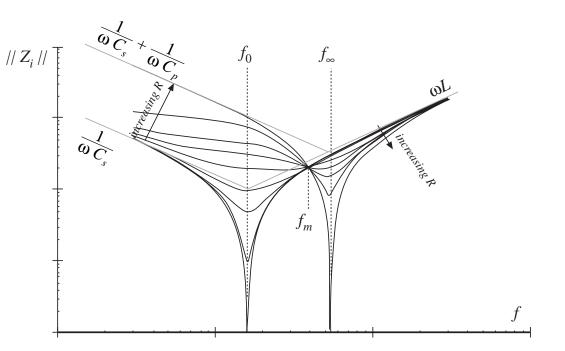

Discussion: LCC

- $|| Z_{i0} ||$ and $|| Z_{i\infty} ||$ both represent series resonant impedances, whose Bode diagrams are easily constructed.
- $\parallel Z_{i0} \parallel$ and $\parallel Z_{i\infty} \parallel$ intersect at frequency f_m .


 $For f < f_m$

then $|| Z_{i0} || < || Z_{i\infty} ||$; hence transistor current decreases as load current decreases


 $For f > f_m$

then $|| Z_{i0} || > || Z_{i\infty} ||$; hence transistor current increases as load current decreases, and transistor current is greater than or equal to short-circuit current for all *R*

Fundamentals of Power Electronics

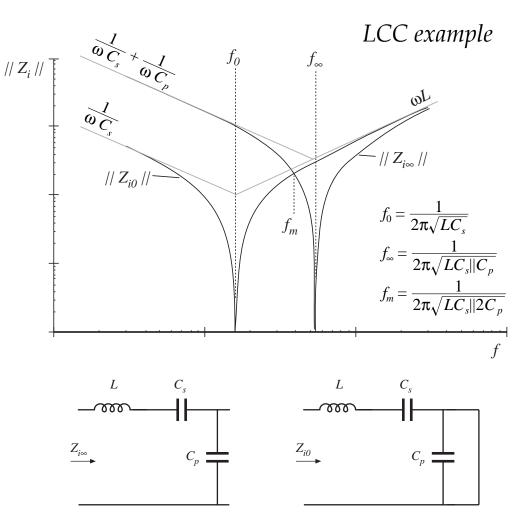

Discussion -series and parallel

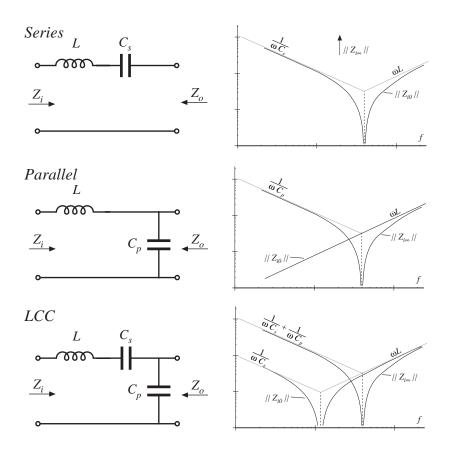

- No-load transistor current = 0, both above and below resonance.
- ZCS below resonance, ZVS above resonance
- Above resonance: no-load transistor current is *greater* than short-circuit transistor current. ZVS.
- Below resonance: no-load transistor current is less than short-circuit current (for $f < f_m$), but determined by $||Z_{i\infty}||$. ZCS.

A Theorem relating the ZVS/ZCS boundary to load resistance R

Theorem 2: If the tank network is purely reactive, then the boundary between zero-current switching and zero-voltage switching occurs when the load resistance R is equal to the critical value R_{crit} , given by

$$R_{crit} = \left\| Z_{o0} \right\| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$

It is assumed that zero-current switching (ZCS) occurs when the tank input impedance is capacitive in nature, while zero-voltage switching (ZVS) occurs when the tank is inductive in nature. This assumption gives a necessary but not sufficient condition for ZVS when significant semiconductor output capacitance is present.

Proof of Theorem 2

Previously shown:

$$Z_i = Z_{i\infty} \frac{1 + \frac{Z_{o0}}{R}}{1 + \frac{Z_{o\infty}}{R}}$$

If ZCS occurs when Z_i is capacitive, while ZVS occurs when Z_i is inductive, then the boundary is determined by $\angle Z_i = 0$. Hence, the critical load R_{crit} is the resistance which causes the imaginary part of Z_i to be zero:

$$\operatorname{Im}(Z_i(R_{crit})) = 0$$

Fundamentals of Power Electronics

Note that $Z_{i\infty}$, Z_{o0} , and $Z_{o\infty}$ have zero real parts. Hence,

$$\operatorname{Im}\left(Z_{i}(R_{crit})\right) = \operatorname{Im}\left(Z_{i\infty}\right)\operatorname{Re}\left(\frac{1 + \frac{Z_{o0}}{R_{crit}}}{1 + \frac{Z_{o\infty}}{R_{crit}}}\right)$$
$$= \operatorname{Im}\left(Z_{i\infty}\right)\operatorname{Re}\left(\frac{1 - \frac{Z_{o0}Z_{o\infty}}{R_{crit}^{2}}}{1 + \frac{\|Z_{o\infty}\|^{2}}{R_{crit}^{2}}}\right)$$

Solution for R_{crit} yields

$$R_{crit} = \left\| Z_{o0} \right\| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$


Discussion — Theorem 2

$$R_{crit} = \left\| Z_{o0} \right\| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$

- Again, $Z_{i\infty}$, Z_{i0} , and Z_{o0} are pure imaginary quantities.
- If $Z_{i\infty}$ and Z_{i0} have the same phase (both inductive or both capacitive), then there is no real solution for R_{crit} .
- Hence, if at a given frequency $Z_{i\infty}$ and Z_{i0} are both capacitive, then ZCS occurs for all loads. If $Z_{i\infty}$ and Z_{i0} are both inductive, then ZVS occurs for all loads.
- If $Z_{i\infty}$ and Z_{i0} have opposite phase (one is capacitive and the other is inductive), then there is a real solution for R_{crit} . The boundary between ZVS and ZCS operation is then given by $R = R_{crit}$.
- Note that $R = ||Z_{o0}||$ corresponds to operation at matched load with maximum output power. The boundary is expressed in terms of this matched load impedance, and the ratio $Z_{i\infty}/Z_{i0}$.

LCC example


- For $f > f_{\infty}$, ZVS occurs for all *R*.
- For $f < f_0$, ZCS occurs for all R.
- For $f_0 < f < f_{\infty}$, ZVS occurs for $R < R_{crit}$, and ZCS occurs for $R > R_{crit}$.
- Note that $R = ||Z_{o0}||$ corresponds to operation at matched load with maximum output power. The boundary is expressed in terms of this matched load impedance, and the ratio $Z_{i\infty} / Z_{i0}$.

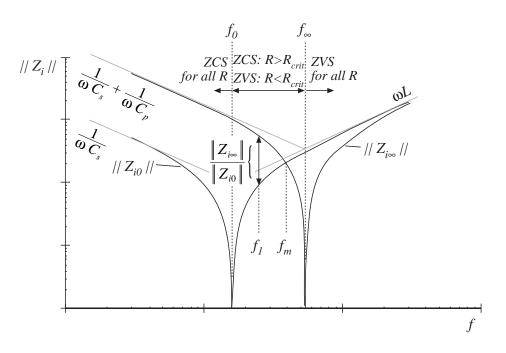


$$R_{crit} = \left\| Z_{o0} \right\| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$

Fundamentals of Power Electronics

LCC example, continued

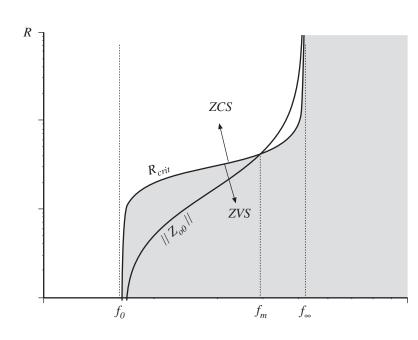

Typical dependence of R_{crit} *and matched-load impedance* $| | Z_{o0} | |$ *on frequency f, LCC example.*

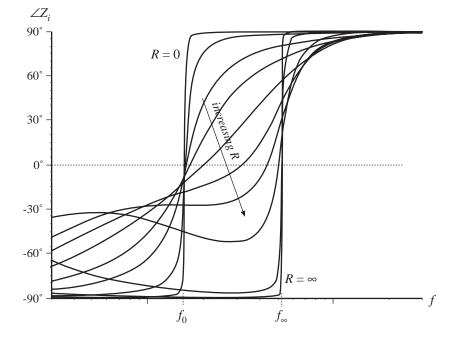

Typical dependence of tank input impedance phase vs. load R and frequency, LCC example.

Fundamentals of Power Electronics

Chapter 19: Resonant Conversion

19.6 Summary of Key Points

- The sinusoidal approximation allows a great deal of insight to be gained into the operation of resonant inverters and dc–dc converters. The voltage conversion ratio of dc–dc resonant converters can be directly related to the tank network transfer function. Other important converter properties, such as the output characteristics, dependence (or lack thereof) of transistor current on load current, and zero-voltageand zero-current-switching transitions, can also be understood using this approximation. The approximation is accurate provided that the effective *Q*-factor is sufficiently large, and provided that the switching frequency is sufficiently close to resonance.
- 2. Simple equivalent circuits are derived, which represent the fundamental components of the tank network waveforms, and the dc components of the dc terminal waveforms.

- 3. Exact solutions of the ideal dc–dc series and parallel resonant converters are listed here as well. These solutions correctly predict the conversion ratios, for operation not only in the fundamental continuous conduction mode, but in discontinuous and subharmonic modes as well.
- Zero-voltage switching mitigates the switching loss caused by diode recovered charge and semiconductor device output capacitances. When the objective is to minimize switching loss and EMI, it is preferable to operate each MOSFET and diode with zero-voltage switching.
- 5. Zero-current switching leads to natural commutation of SCRs, and can also mitigate the switching loss due to current tailing in IGBTs.

- 6. The input impedance magnitude $||Z_i||$, and hence also the transistor current magnitude, are monotonic functions of the load resistance *R*. The dependence of the transistor conduction loss on the load current can be easily understood by simply plotting $||Z_i||$ in the limiting cases as $R \to \infty$ and as $R \to 0$, or $||Z_{i\infty}||$ and $||Z_{i0}||$.
- 7. The ZVS/ZCS boundary is also a simple function of $Z_{i\infty}$ and Z_{i0} . If ZVS occurs at open-circuit and at short-circuit, then ZVS occurs for all loads. If ZVS occurs at short-circuit, and ZCS occurs at open-circuit, then ZVS is obtained at matched load provided that $|| Z_{i\infty} || > || Z_{i0} ||$.
- 8. The output characteristics of all resonant inverters considered here are elliptical, and are described completely by the open-circuit transfer function magnitude $|| H_{\infty} ||$, and the output impedance $|| Z_{o0} ||$. These quantities can be chosen to match the output characteristics to the application requirements.

Chapter 20 Quasi-Resonant Converters

Introduction


- 20.1 The zero-current-switching quasi-resonant switch cell
 - 20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell
 - 20.1.2 The average terminal waveforms
 - 20.1.3 The full-wave ZCS quasi-resonant switch cell
- 20.2 Resonant switch topologies
 - 20.2.1 The zero-voltage-switching quasi-resonant switch
 - 20.2.2 The zero-voltage-switching multiresonant switch
 - 20.2.3 Quasi-square-wave resonant switches
- 20.3 Ac modeling of quasi-resonant converters
- 20.4 Summary of key points

The resonant switch concept


A quite general idea:

- 1. PWM switch network is replaced by a resonant switch network
- 2. This leads to a quasi-resonant version of the original PWM converter

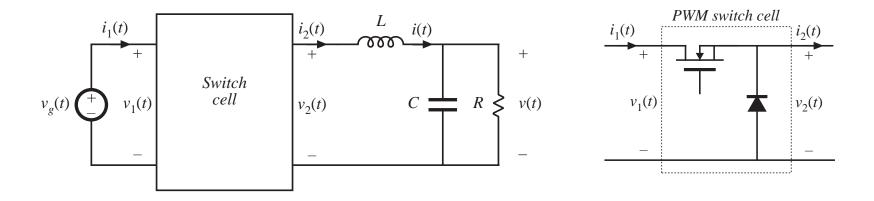Example: realization of the switch cell in the buck converter




Two quasi-resonant switch cells

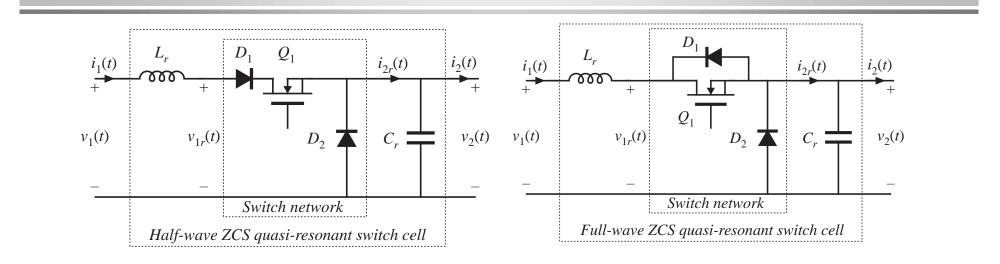

Insert either of the above switch cells into the buck converter, to obtain a ZCS quasi-resonant version of the buck converter. L_r and C_r are small in value, and their resonant frequency f_0 is greater than the switching frequency f_s .

$$f_0 = \frac{1}{2\pi \sqrt{L_r C_r}} = \frac{\omega_0}{2\pi}$$

Fundamentals of Power Electronics

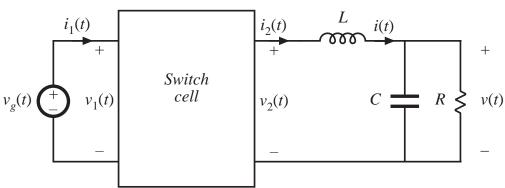

20.1 The zero-current-switching quasi-resonant switch cell

Tank inductor L_r in series with transistor: transistor switches at zero crossings of inductor current waveform


Tank capacitor C_r in parallel with diode D_2 : diode switches at zero crossings of capacitor voltage waveform

Two-quadrant switch is required:

Half-wave: Q_1 and D_1 in series, transistor turns off at first zero crossing of current waveform

Full-wave: Q_1 and D_1 in parallel, transistor turns off at second zero crossing of current waveform

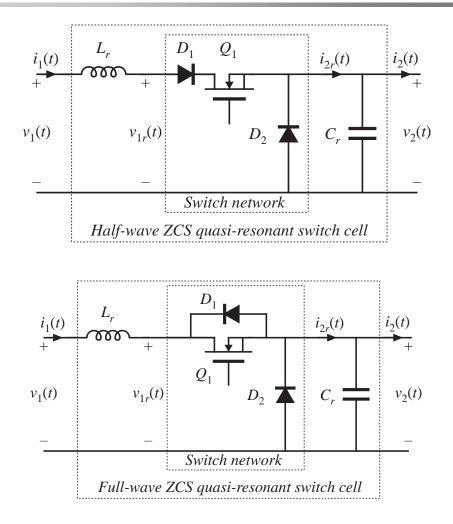Performances of half-wave and full-wave cells differ significantly.



Averaged switch modeling of ZCS cells

It is assumed that the converter filter elements are large, such that their switching ripples are small. Hence, we can make the small ripple approximation as usual, for these elements:

$$i_{2}(t) \approx \left\langle i_{2}(t) \right\rangle_{T_{s}}$$
$$v_{1}(t) \approx \left\langle v_{1}(t) \right\rangle_{T_{s}}$$

In steady state, we can further approximate these quantities by their dc values: $i_{i}(t) \approx L$

$$v_2(t) \approx V_2$$
$$v_1(t) \approx V_1$$

Modeling objective: find the average values of the terminal waveforms

 $\langle v_2(t) \rangle_{T_s}$ and $\langle i_1(t) \rangle_{T_s}$


The switch conversion ratio μ

A generalization of the duty cycle d(t)

The switch conversion ratio μ is the ratio of the average terminal voltages of the switch network. It can be applied to non-PWM switch networks. For the CCM PWM case, $\mu = d$.

If $V/V_g = M(d)$ for a PWM CCM converter, then $V/V_g = M(\mu)$ for the same converter with a switch network having conversion ratio μ .

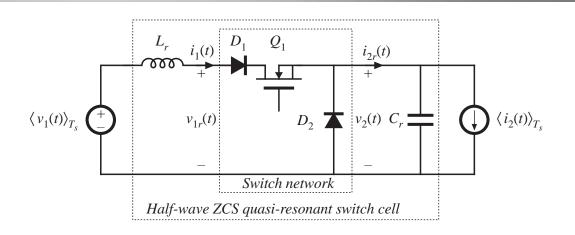Generalized switch averaging, and μ , are defined and discussed in Section 10.3.




$$\frac{i_{2}(t) \approx \left\langle i_{2}(t) \right\rangle_{T_{s}}}{v_{1}(t) \approx \left\langle v_{1}(t) \right\rangle_{T_{s}}} \qquad \mu = \frac{\left\langle v_{2}(t) \right\rangle_{T_{s}}}{\left\langle v_{1r}(t) \right\rangle_{T_{s}}} = \frac{\left\langle i_{1}(t) \right\rangle_{T_{s}}}{\left\langle i_{2r}(t) \right\rangle_{T_{s}}}$$

In steady state:

$$i_2(t) \approx I_2 \qquad \qquad \mu = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$


Chapter 20: Quasi-Resonant Converters

20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell

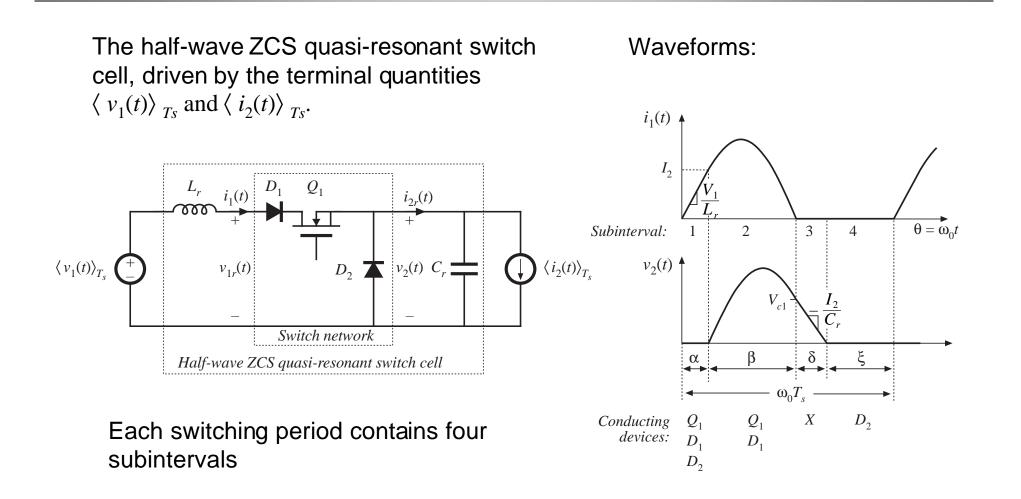

Subinterval 1

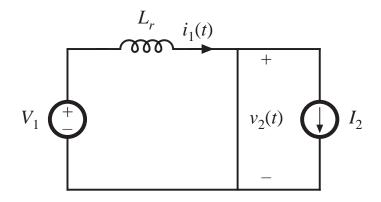Diode D_2 is initially conducting the filter inductor current I_2 . Transistor Q_1 turns on, and the tank inductor current i_1 starts to increase. So all semiconductor devices conduct during this subinterval, and the circuit reduces to:




Circuit equations: $\frac{di_{1}(t)}{dt} = \frac{V_{1}}{L_{r}} \quad \text{with } i_{1}(0) = 0$ Solution: $i_{1}(t) = \frac{V_{1}}{L_{r}} t = \omega_{0} t \frac{V_{1}}{R_{0}}$ where $R_{0} = \sqrt{\frac{L_{r}}{C_{r}}}$

This subinterval ends when diode D_2 becomes reverse-biased. This occurs at time $\omega_0 t = \alpha$, when $i_1(t) = I_2$.

$$i_1(\alpha) = \alpha \frac{V_1}{R_0} = I_2 \qquad \alpha = \frac{I_2 R_0}{V_1}$$

Subinterval 2

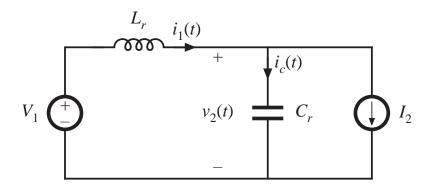Diode D_2 is off. Transistor Q_1 conducts, and the tank inductor and tank capacitor ring sinusoidally. The circuit reduces to:



The circuit equations are

$$L_r \frac{di_1(\omega_0 t)}{dt} = V_1 - v_2(\omega_0 t) \qquad v_2(\alpha) = 0$$

$$C_r \frac{dv_2(\omega_0 t)}{dt} = i_1(\omega_0 t) - I_2 \qquad i_1(\alpha) = I_2$$

The solution is

$$i_1(\omega_0 t) = I_2 + \frac{V_1}{R_0} \sin\left(\omega_0 t - \alpha\right)$$
$$v_2(\omega_0 t) = V_1 \left(1 - \cos\left(\omega_0 t - \alpha\right)\right)$$

The dc components of these waveforms are the dc solution of the circuit, while the sinusoidal components have magnitudes that depend on the initial conditions and on the characteristic impedance R_0 .

Fundamentals of Power Electronics

Subinterval 2 continued

 $i_{1}(\omega_{0}t) = I_{2} + \frac{V_{1}}{R_{0}} \sin\left(\omega_{0}t - \alpha\right)$ $v_{2}(\omega_{0}t) = V_{1}\left(1 - \cos\left(\omega_{0}t - \alpha\right)\right)$ Peak inductor current: $I_{1pk} = I_2 + \frac{V_1}{R_2}$ I_2 2 $\theta = \omega_0 t$ Subinterval: 3 This subinterval ends at the first zero δ crossing of $i_1(t)$. Define β = angular length of subinterval 2. Then $i_1(\alpha + \beta) = I_2 + \frac{V_1}{R_2} \sin(\beta) = 0$ Hence $\beta = \pi + \sin^{-1} \left(\frac{I_2 R_0}{V_1} \right)$ $\sin\left(\beta\right) = -\frac{I_2 R_0}{V}$ $-\frac{\pi}{2} < \sin^{-1}\left(x\right) \le \frac{\pi}{2}$ Must use care to select the correct branch of the arcsine function. Note (from the $i_1(t)$ waveform) that $\beta > \pi$. $I_2 < \frac{V_1}{R}$

Chapter 20: Quasi-Resonant Converters

Boundary of zero current switching

If the requirement

$$I_2 < \frac{V_1}{R_0}$$

is violated, then the inductor current never reaches zero. In consequence, the transistor cannot switch off at zero current.


The resonant switch operates with zero current switching only for load currents less than the above value. The characteristic impedance must be sufficiently small, so that the ringing component of the current is greater than the dc load current.

Capacitor voltage at the end of subinterval 2 is

$$v_2(\alpha + \beta) = V_{c1} = V_1 \left(1 + \sqrt{1 - \left(\frac{I_2 R_0}{V_1}\right)^2} \right)$$

Subinterval 3

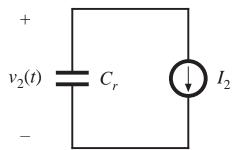All semiconductor devices are off. The circuit reduces to:



The circuit equations are

$$C_r \frac{dv_2(\omega_0 t)}{dt} = -I_2$$
$$v_2(\alpha + \beta) = V_{c1}$$

The solution is

$$v_2(\omega_0 t) = V_{c1} - I_2 R_0 \left(\omega_0 t - \alpha - \beta \right)$$

Fundamentals of Power Electronics

Subinterval 3 ends when the tank capacitor voltage reaches zero, and diode D_2 becomes forward-biased. Define δ = angular length of subinterval 3. Then

$$v_2(\alpha + \beta + \delta) = V_{c1} - I_2 R_0 \delta = 0$$

$$\delta = \frac{V_{c1}}{I_2 R_0} = \frac{V_1}{I_2 R_0} \left(1 - \sqrt{1 - \left(\frac{I_2 R_0}{V_1}\right)^2} \right)$$

Subinterval 4

Subinterval 4, of angular length ξ , is identical to the diode conduction interval of the conventional PWM switch network.

Diode D_2 conducts the filter inductor current I_2

The tank capacitor voltage $v_2(t)$ is equal to zero.

Transistor Q_1 is off, and the input current $i_1(t)$ is equal to zero.

The length of subinterval 4 can be used as a control variable. Increasing the length of this interval reduces the average output voltage.

Maximum switching frequency

The length of the fourth subinterval cannot be negative, and the switching period must be at least long enough for the tank current and voltage to return to zero by the end of the switching period.

The angular length of the switching period is

$$\omega_0 T_s = \alpha + \beta + \delta + \xi = \frac{2\pi f_0}{f_s} = \frac{2\pi}{F}$$

where the normalized switching frequency F is defined as

$$F = \frac{f_s}{f_0}$$

So the minimum switching period is

$$\omega_0 T_s \ge \alpha + \beta + \delta$$

Substitute previous solutions for subinterval lengths:

$$\frac{2\pi}{F} \ge \frac{I_2 R_0}{V_1} + \pi + \sin^{-1} \left(\frac{I_2 R_0}{V_1} \right) + \frac{V_1}{I_2 R_0} \left(1 - \sqrt{1 - \left(\frac{I_2 R_0}{V_1} \right)^2} \right)$$

Fundamentals of Power Electronics

20.1.2 The average terminal waveforms


Averaged switch modeling: we need to determine the average values of $i_1(t)$ and $v_2(t)$. The average switch input current is given by

$$\left\langle i_{1}(t) \right\rangle_{T_{s}} = \frac{1}{T_{s}} \int_{t}^{t+T_{s}} i_{1}(t) dt = \frac{q_{1}+q_{2}}{T_{s}}$$

 q_1 and q_2 are the areas under the current waveform during subintervals 1 and 2. q_1 is given by the triangle area formula:

$$q_1 = \int_0^{\frac{\alpha}{\omega_0}} i_1(t) dt = \frac{1}{2} \left(\frac{\alpha}{\omega_0} \right) \left(I_2 \right)$$

Fundamentals of Power Electronics

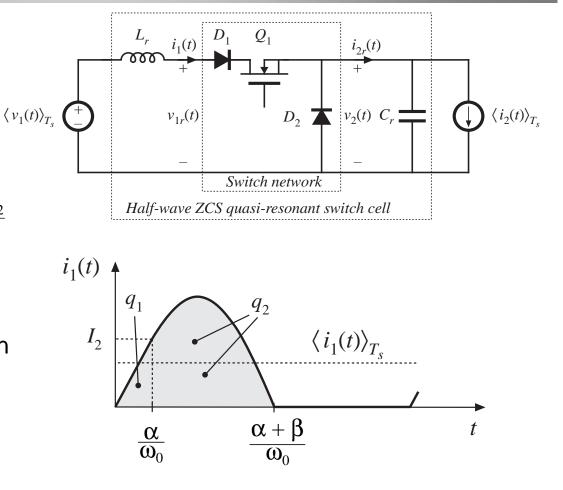

Charge arguments: computation of q_2

$$q_2 = \int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_1(t) dt$$

Node equation for subinterval 2:


$$i_1(t) = i_C(t) + I_2$$

Substitute:

$$q_{2} = \int_{\frac{\alpha}{\omega_{0}}}^{\frac{\alpha+\beta}{\omega_{0}}} i_{C}(t)dt + \int_{\frac{\alpha}{\omega_{0}}}^{\frac{\alpha+\beta}{\omega_{0}}} I_{2}dt$$

Second term is integral of constant I_2 :
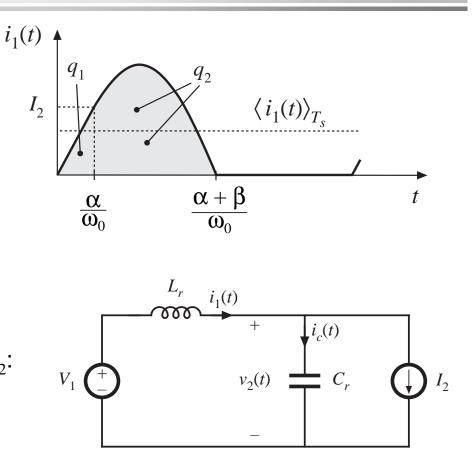
$$\int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} I_2 dt = I_2 \frac{\beta}{\omega_0}$$



Circuit during subinterval 2

Fundamentals of Power Electronics


Charge arguments continued

$$q_{2} = \int_{\underline{\alpha}_{0}}^{\underline{\alpha}+\underline{\beta}} i_{C}(t)dt + \int_{\underline{\alpha}_{0}}^{\underline{\alpha}+\underline{\beta}} I_{2}dt$$

First term: integral of the capacitor current over subinterval 2. This can be related to the change in capacitor voltage :

$$\int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_C(t) dt = C \left(v_2 \left(\frac{\alpha+\beta}{\omega_0} \right) - v_2 \left(\frac{\alpha}{\omega_0} \right) \right)$$
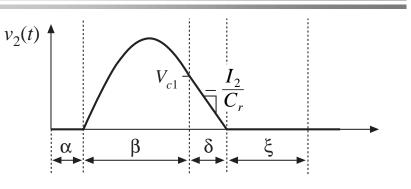
$$\int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_C(t) dt = C \left(V_{c1} - 0 \right) = C V_{c1}$$



Substitute results for the two integrals:

$$q_2 = CV_{c1} + I_2 \frac{\beta}{\omega_0}$$

Substitute into expression for average switch input current:

$$\left\langle i_1(t) \right\rangle_{T_s} = \frac{\alpha I_2}{2\omega_0 T_s} + \frac{CV_{c1}}{T_s} + \frac{\beta I_2}{\omega_0 T_s}$$

Chapter 20: Quasi-Resonant Converters

Switch conversion ratio µ

$$\mu = \frac{\left\langle i_1(t) \right\rangle_{T_s}}{I_2} = \frac{\alpha}{2\omega_0 T_s} + \frac{CV_{c1}}{I_2 T_s} + \frac{\beta}{\omega_0 T_s}$$


Eliminate α , β , V_{c1} using previous results:

$$\mu = F \frac{1}{2\pi} \left[\frac{1}{2} J_s + \pi + \sin^{-1}(J_s) + \frac{1}{J_s} \left(1 + \sqrt{1 - J_s^2} \right) \right]$$

where


$$J_s = \frac{I_2 R_0}{V_1}$$

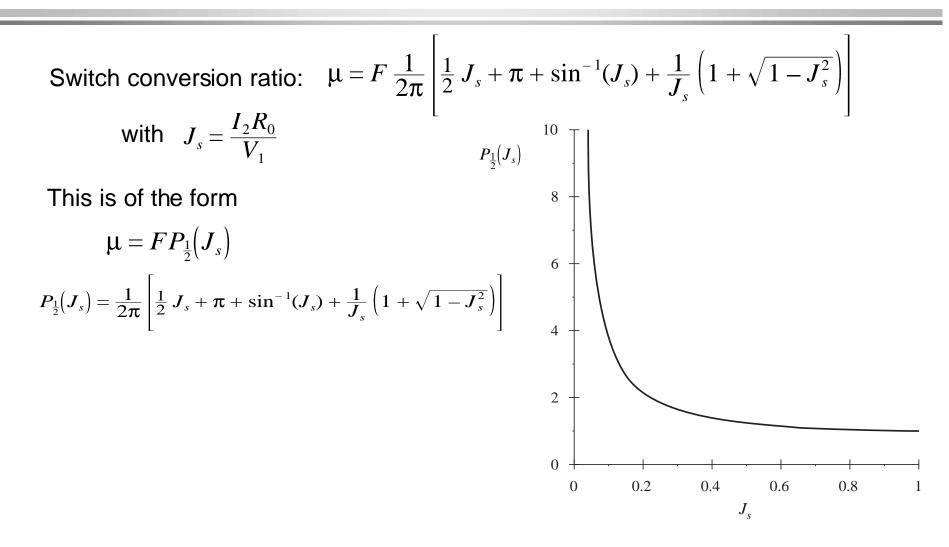Analysis result: switch conversion ratio μ



Fundamentals of Power Electronics

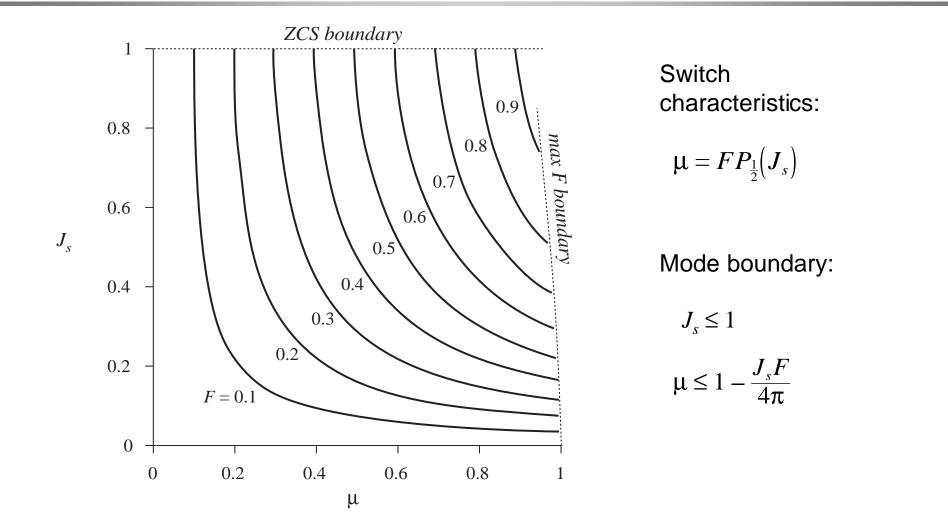Characteristics of the half-wave ZCS resonant switch



Fundamentals of Power Electronics

Buck converter containing half-wave ZCS quasi-resonant switch

Conversion ratio of the buck converter is (from inductor volt-second balance):

$$M = \frac{V}{V_g} = \mu$$


For the buck converter,

$$J_s = \frac{IR_0}{V_g}$$

ZCS occurs when

$$I \leq \frac{V_g}{R_0}$$

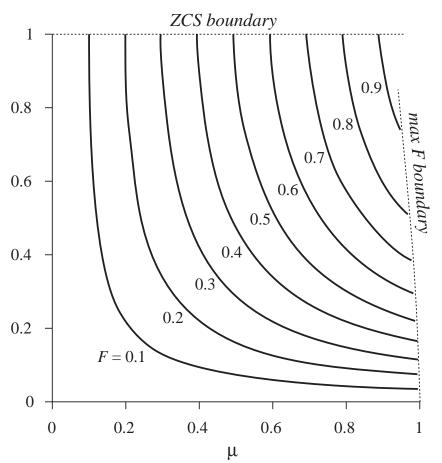
Output voltage varies over the range $0 \le V \le V_g - \frac{FIR_0}{4\pi}$



Fundamentals of Power Electronics


 J_{s}

Boost converter example

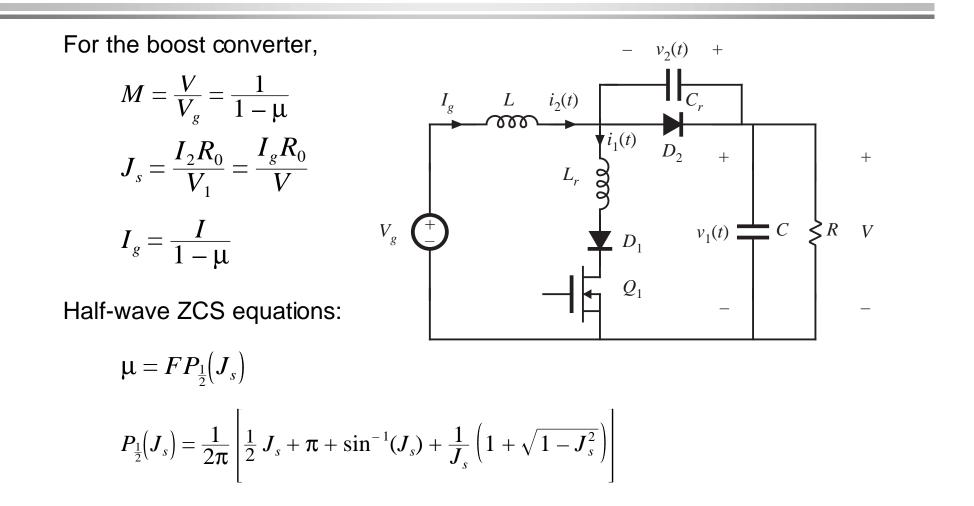

Fundamentals of Power Electronics

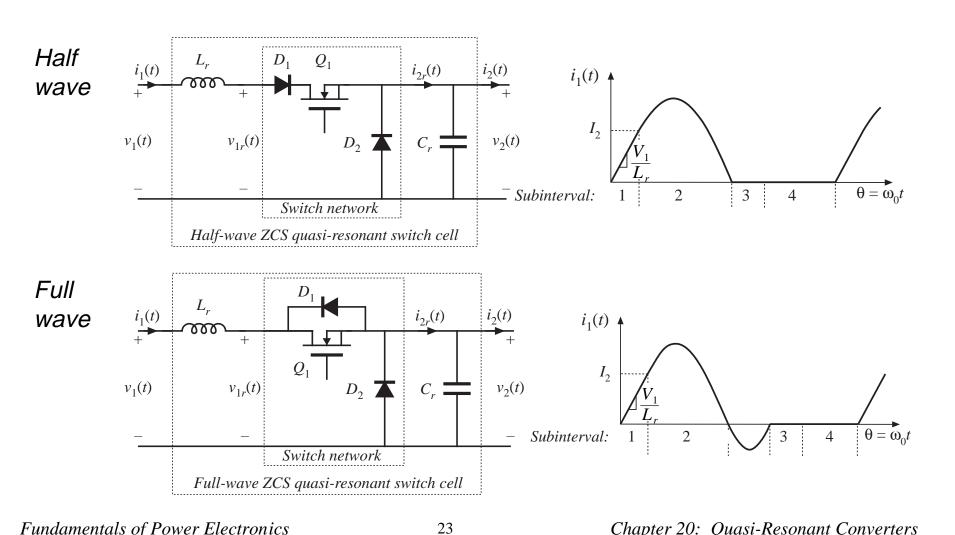20.1.3 The full-wave ZCS quasi-resonant switch cell



Analysis: full-wave ZCS

Analysis in the full-wave case is nearly the same as in the half-wave case. The second subinterval ends at the second zero crossing of the tank inductor current waveform. The following quantities differ:


$$\beta = \begin{cases} \pi + \sin^{-1} \left(J_s \right) & \text{(half wave)} \\ 2\pi - \sin^{-1} \left(J_s \right) & \text{(full wave)} \end{cases}$$
$$V_{c1} = \begin{cases} V_1 \left(1 + \sqrt{1 - J_s^2} \right) & \text{(half wave)} \\ V_1 \left(1 - \sqrt{1 - J_s^2} \right) & \text{(full wave)} \end{cases}$$

In either case, μ is given by

$$\mu = \frac{\left\langle i_1(t) \right\rangle_{T_s}}{I_2} = \frac{\alpha}{2\omega_0 T_s} + \frac{CV_{c1}}{I_2 T_s} + \frac{\beta}{\omega_0 T_s}$$


Fundamentals of Power Electronics

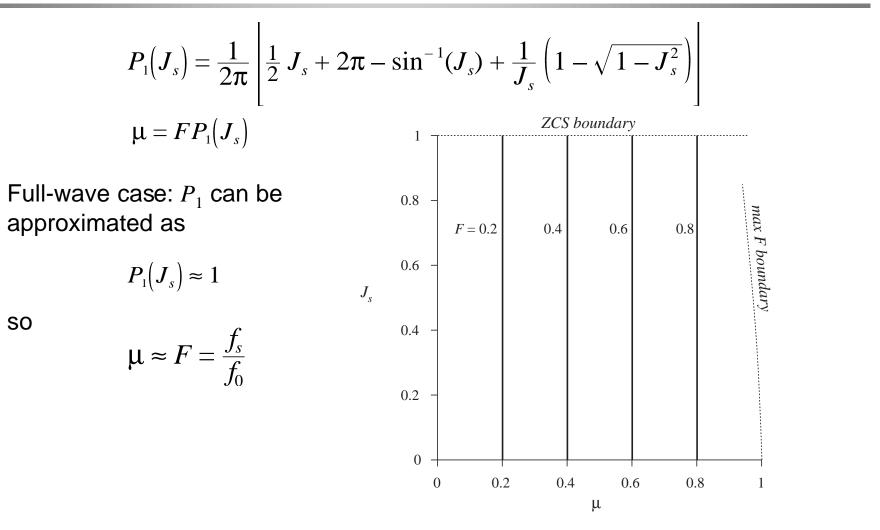Full-wave cell: switch conversion ratio µ



Fundamentals of Power Electronics

20.2 Resonant switch topologies

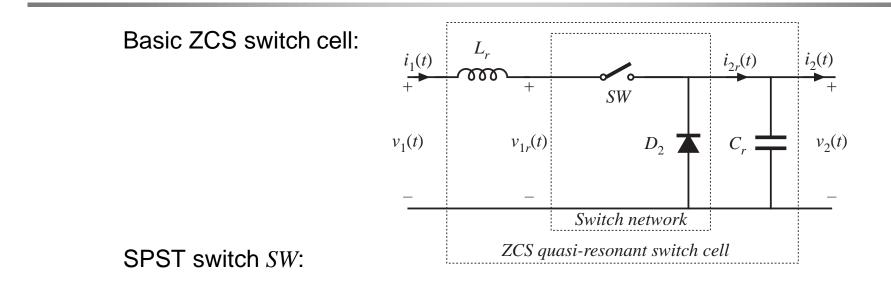

- Voltage-bidirectional two-quadrant switch for half-wave cell
- Current-bidirectional two-quadrant switch for full-wave cell

Connection of resonant elements:


Can be connected in other ways that preserve high-frequency components of tank waveforms

Connection of tank capacitor

Connection of tank capacitor to two other points at ac ground.

This simply changes the dc component of tank capacitor voltage.

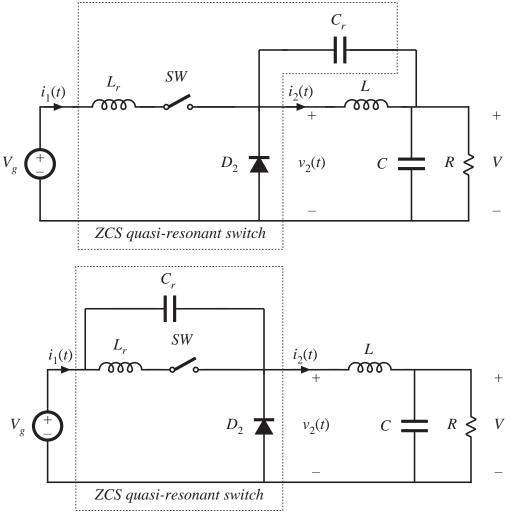The ac highfrequency components of the tank waveforms are unchanged.




A test to determine the topology of a resonant switch network

Replace converter elements by their high-frequency equivalents:

- Independent voltage source V_g : short circuit
- Filter capacitors: short circuits
- Filter inductors: open circuits

The resonant switch network remains.

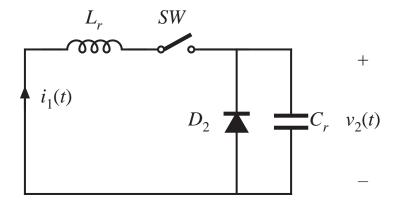
If the converter contains a ZCS quasi-resonant switch, then the result of these operations is



Zero-current and zero-voltage switching

ZCS quasi-resonant switch:

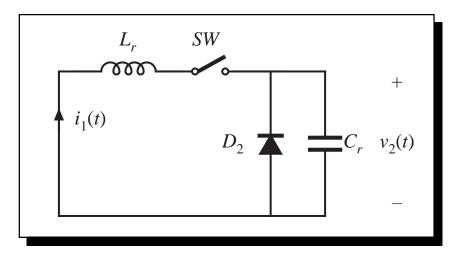
- Tank inductor is in series with switch; hence *SW* switches at zero current
- Tank capacitor is in parallel with diode *D*₂; hence *D*₂ switches at zero voltage




Discussion

- Zero voltage switching of D_2 eliminates switching loss arising from D_2 stored charge.
- Zero current switching of SW: device Q_1 and D_1 output capacitances lead to switching loss. In full-wave case, stored charge of diode D_1 leads to switching loss.
- Peak transistor current is $(1 + J_s) V_g/R_0$, or more than twice the PWM value.

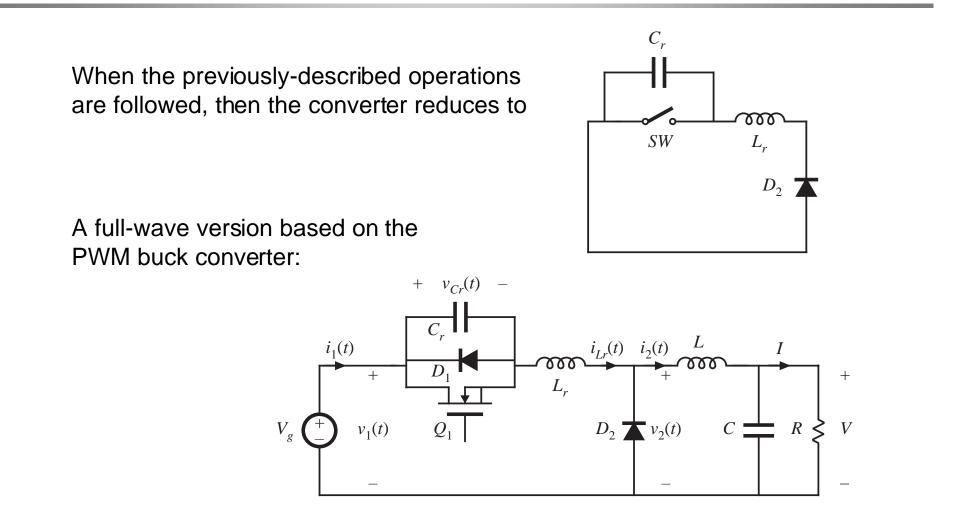
20.2.1 The zero-voltage-switching quasi-resonant switch cell




ZVS quasi-resonant switch cell

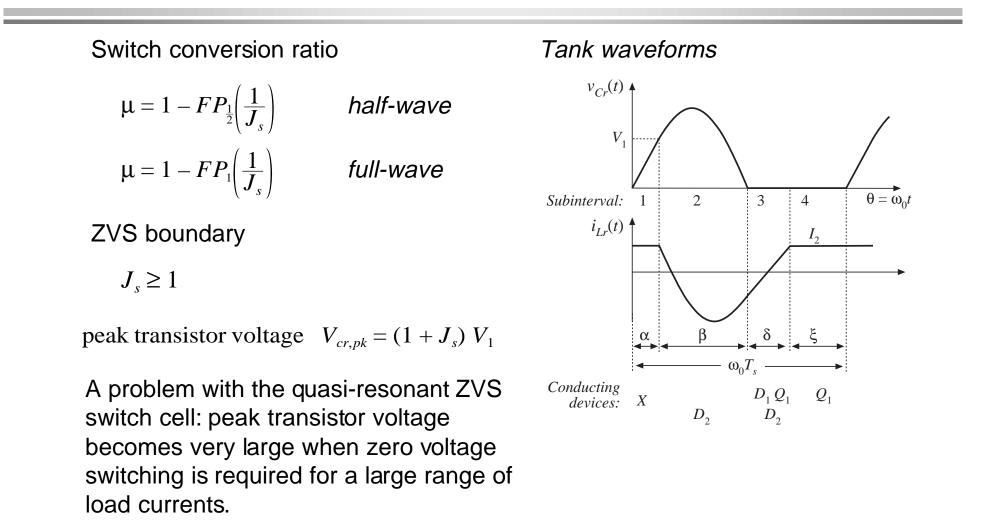


20.2.2 The ZVS multiresonant switch

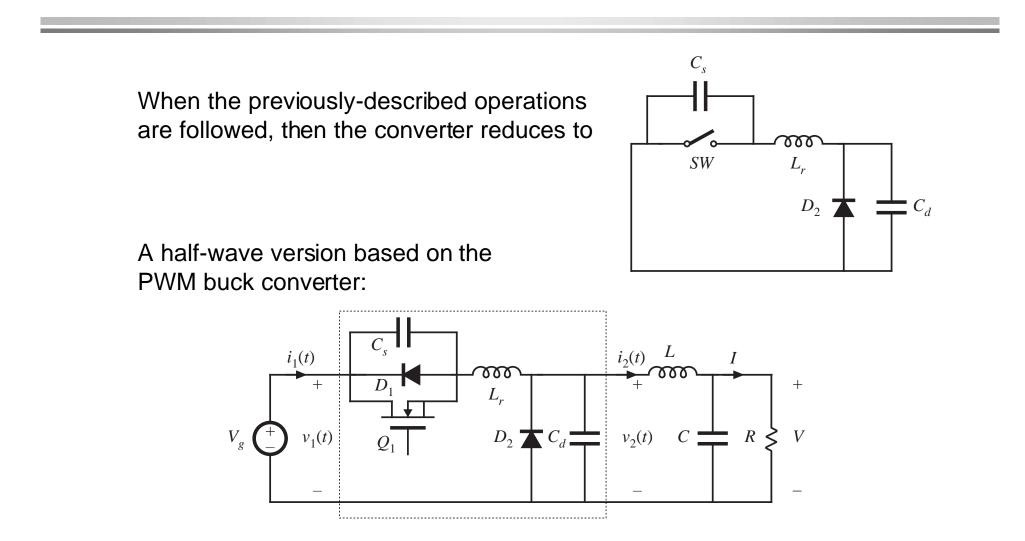

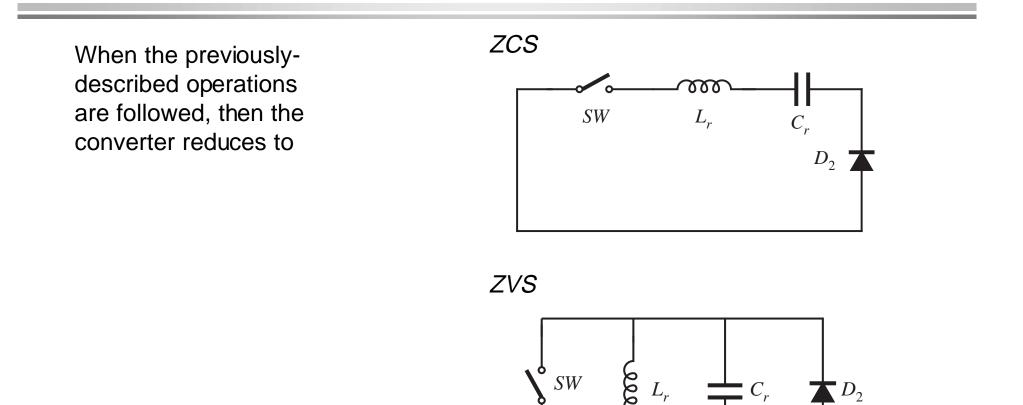20.2.3 Quasi-square-wave resonant switches




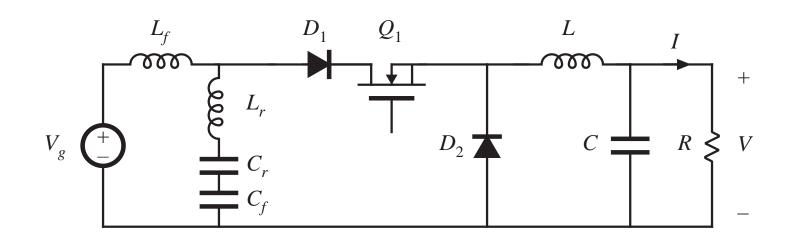A quasi-square-wave ZCS buck with input filter



- The basic ZCS QSW switch cell is restricted to $0 \le \mu \le 0.5$
- Peak transistor current is equal to peak transistor current of PWM cell
- Peak transistor voltage is increased
- Zero-current switching in all semiconductor devices

A quasi-square-wave ZVS buck

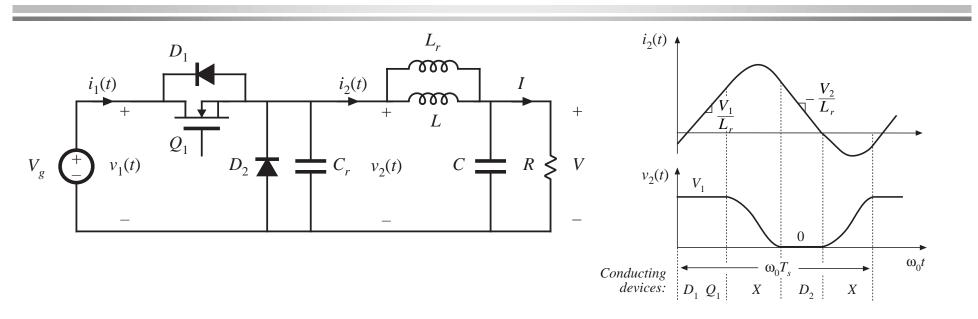

- The basic ZVS QSW switch cell is restricted to $0.5 \le \mu \le 1$
- Peak transistor voltage is equal to peak transistor voltage of PWM cell
- Peak transistor current is increased
- Zero-voltage switching in all semiconductor devices


Fundamentals of Power Electronics

Chapter 20: Quasi-Resonant Converters

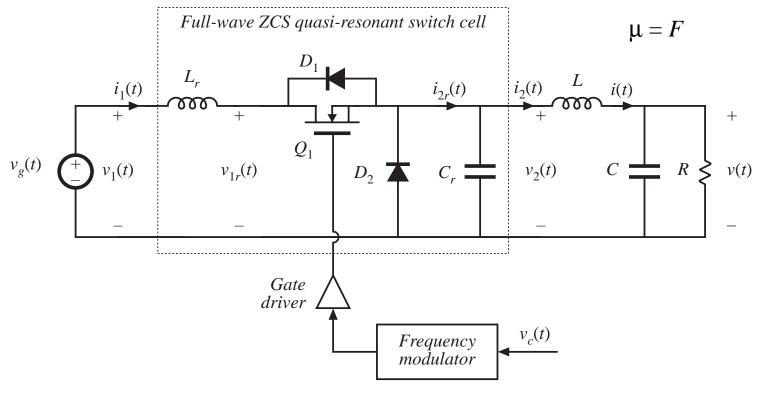
20.3 Ac modeling of quasi-resonant converters

Use averaged switch modeling technique: apply averaged PWM model, with d replaced by μ

Buck example with full-wave ZCS quasi-resonant cell:




Small-signal ac model

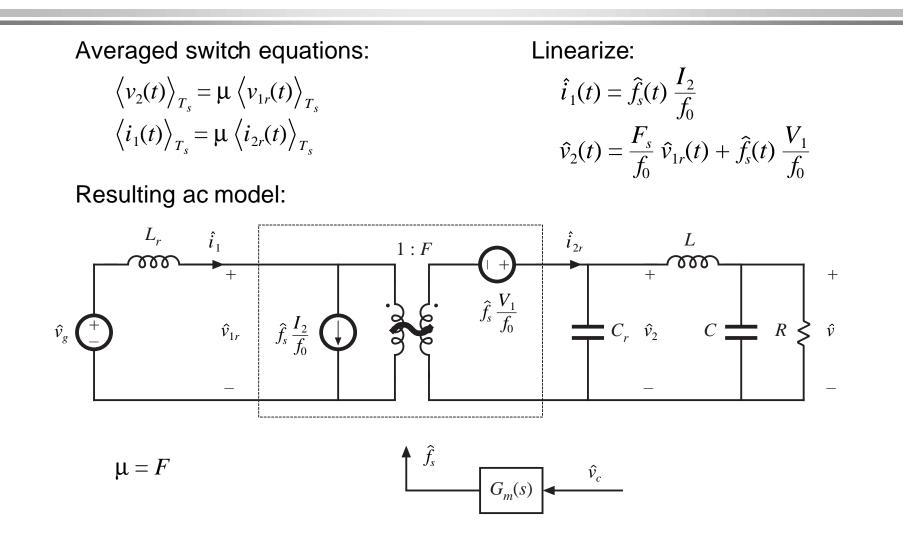


Low-frequency model

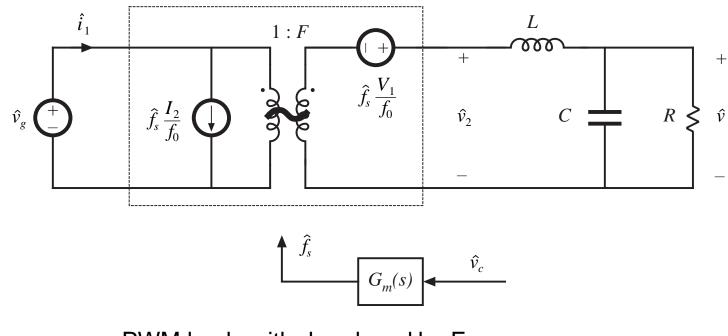Tank dynamics occur only at frequency near or greater than switching frequency —discard tank elements



-same as PWM buck, with d replaced by F

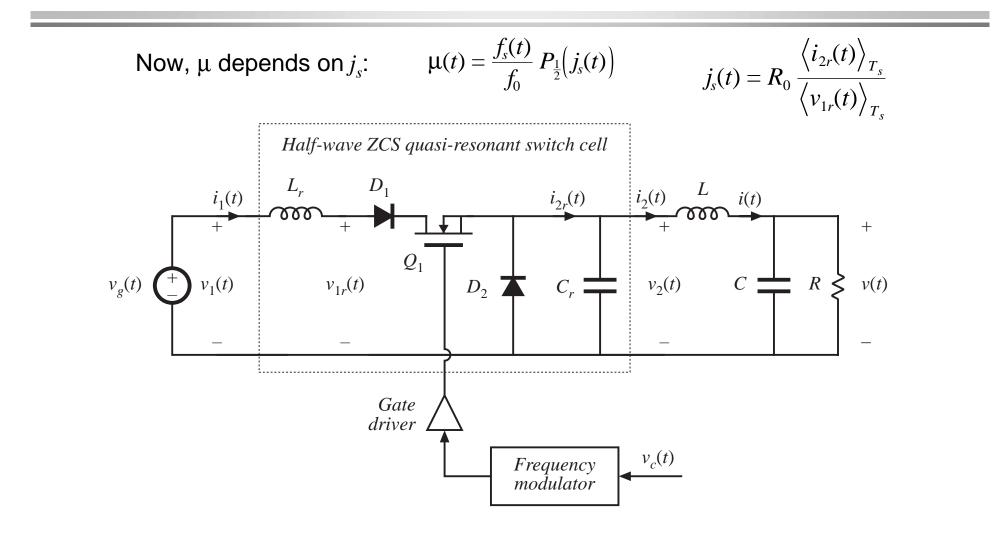Example 2: Half-wave ZCS quasi-resonant buck



Small-signal modeling

Perturbation and linearization of $\mu(v_{1r}, i_{2r}, f_s)$:

$$\hat{\mu}(t) = K_v \hat{v}_{1r}(t) + K_i \hat{i}_{2r}(t) + K_c \hat{f}_s(t)$$
with
$$K_v = -\frac{\partial \mu}{\partial j_s} \frac{R_0 I_2}{V_1^2}$$

$$K_i = -\frac{\partial \mu}{\partial j_s} \frac{R_0}{V_1}$$

$$\frac{\partial \mu}{\partial j_s} = \frac{F_s}{2\pi f_0} \left(\frac{1}{2} - \frac{1 + \sqrt{1 - J_s^2}}{J_s^2}\right)$$

$$K_c = \frac{\mu_0}{F_s}$$


Linearized terminal equations of switch network:

$$\hat{i}_{1}(t) = \hat{\mu}(t) I_{2} + \hat{i}_{2r}(t) \mu_{0}$$
$$\hat{v}_{2}(t) = \mu_{0} \hat{v}_{1r}(t) + \hat{\mu}(t) V_{1}$$


Fundamentals of Power Electronics

Chapter 20: Quasi-Resonant Converters

Equivalent circuit model

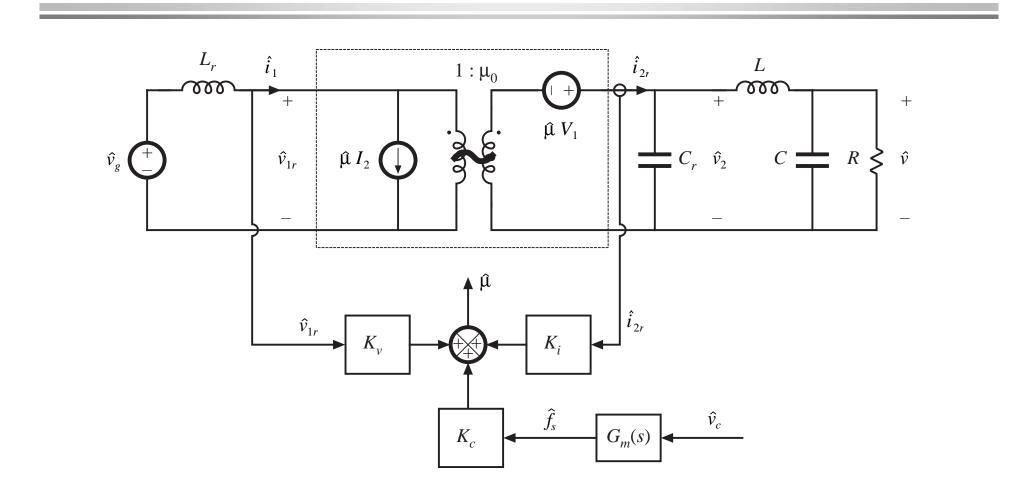

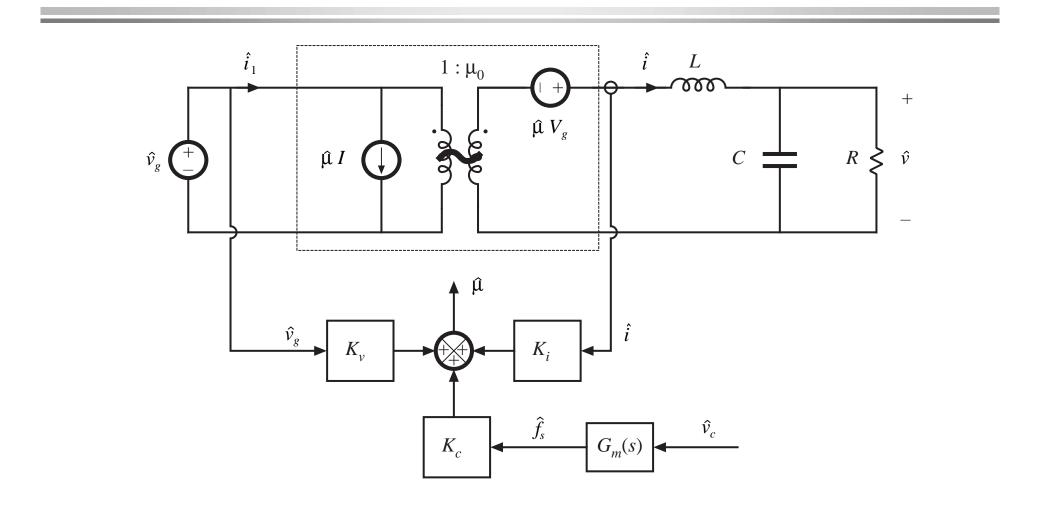Low frequency model: set tank elements to zero




Predicted small-signal transfer functions Half-wave ZCS buck

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{1}{Q} \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$
$$G_{vc}(s) = G_{c0} \frac{1}{1 + \frac{1}{Q} \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Full-wave: poles and zeroes are same as PWM

Half-wave: effective feedback reduces Q-factor and dc gains

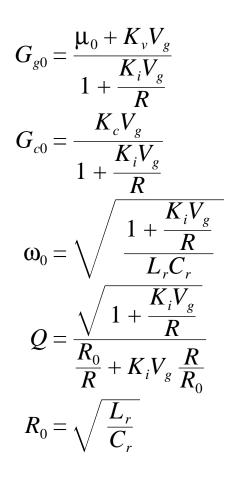

Chapter 20: Quasi-Resonant Converters

20.4 Summary of key points

- 1. In a resonant switch converter, the switch network of a PWM converter is replaced by a switch network containing resonant elements. The resulting hybrid converter combines the properties of the resonant switch network and the parent PWM converter.
- 2. Analysis of a resonant switch cell involves determination of the switch conversion ratio μ . The resonant switch waveforms are determined, and are then averaged. The switch conversion ratio μ is a generalization of the PWM CCM duty cycle *d*. The results of the averaged analysis of PWM converters operating in CCM can be directly adapted to the related resonant switch converter, simply by replacing *d* with μ .
- 3. In the zero-current-switching quasi-resonant switch, diode D_2 operates with zero-voltage switching, while transistor Q_1 and diode D_1 operate with zero-current switching.

- 4. In the zero-voltage-switching quasi-resonant switch, the transistor Q_1 and diode D_1 operate with zero-voltage switching, while diode D_2 operates with zero-current switching.
- 5. Full-wave versions of the quasi-resonant switches exhibit very simple control characteristics: the conversion ratio μ is essentially independent of load current. However, these converters exhibit reduced efficiency at light load, due to the large circulating currents. In addition, significant switching loss is incurred due to the recovered charge of diode D_1 .
- 6. Half-wave versions of the quasi-resonant switch exhibit conversion ratios that are strongly dependent on the load current. These converters typically operate with wide variations of switching frequency.
- 7. In the zero-voltage-switching multiresonant switch, all semiconductor devices operate with zero-voltage switching. In consequence, very low switching loss is observed.

- 8. In the quasi-square-wave zero-voltage-switching resonant switches, all semiconductor devices operate with zero-voltage switching, and with peak voltages equal to those of the parent PWM converter. The switch conversion ratio is restricted to the range $0.5 \le \mu \le 1$.
- 9. The small-signal ac models of converters containing resonant switches are similar to the small-signal models of their parent PWM converters. The averaged switch modeling approach can be employed to show that the quantity d(t) is simply replaced by $\mu(t)$.
- 10. In the case of full-wave quasi-resonant switches, μ depends only on the switching frequency, and therefore the transfer function poles and zeroes are identical to those of the parent PWM converter.
- 11. In the case of half-wave quasi-resonant switches, as well as other types of resonant switches, the conversion ratio μ is a strong function of the switch terminal quantities v_1 and i_2 . This leads to effective feedback, which modifies the poles, zeroes, and gains of the transfer functions.

Appendix 2

Magnetics Design Tables

Geometrical data for several standard ferrite core shapes are listed here. The geometrical constant K_g is a measure of core size, useful for designing inductors and transformers which attain a given copper loss [1]. The K_g method for inductor design is described in Chapter 13. K_g is defined as

$$K_g = \frac{A_c^2 W_A}{MLT} \tag{A2.1}$$

where A_c is the core cross-sectional area, W_A is the window area, and *MLT* is the winding mean-length-per-turn. The geometrical constant K_{gfe} is a similar measure of core size, which is useful for designing ac inductors and transformers when the total copper plus core loss is constrained. The K_{gfe} method for magnetics design is described in Chapter 14. K_{gfe} is defined as

$$K_{gfe} = \frac{W_A A_c^{2(1-1/\beta)}}{MLT l_e^{2/\beta}} u(\beta)$$
(A2.2)

where l_e is the core mean magnetic path length, and β is the core loss exponent:


$$P_{fe} = K_{fe} B_{\max}^{\beta} \tag{A2.3}$$

For modern ferrite materials, β typically lies in the range 2.6 to 2.8. The quantity $u(\beta)$ is defined as

$$u(\beta) = \left[\left(\frac{\beta}{2}\right)^{-\left(\frac{\beta}{\beta+2}\right)} + \left(\frac{\beta}{2}\right)^{\left(\frac{2}{\beta+2}\right)} \right]^{-\left(\frac{\beta+2}{\beta}\right)}$$
(A2.4)

 $u(\beta)$ is equal to 0.305 for $\beta = 2.7$. This quantity varies by roughly 5% over the range $2.6 \le \beta \le 2.8$. Values of K_{gfe} are tabulated for $\beta = 2.7$; variation of K_{gfe} over the range $2.6 \le \beta \le 2.8$ is typically quite small.


A2.1 Pot core data

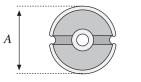




Core type (<i>AH</i>)	Geometrical constant $K_{g_{5}}$	Geometrical constant K_{gfe}	Cross- sectional area A_c	Bobbin winding area W_A	Mean length per turn <i>MLT</i>	Magnetic path length l_m	Thermal resistance R_{th}	Core weight
(mm)	cm ⁵	cm ^x	(cm^2)	(cm^2)	(cm)	(cm)	(°C/W)	(g)
704	0.738.10-6	1.61.10-6	0.070	0.22.10-3	1.46	1.0		0.5
905	0.183.10-3	256.10-6	0.101	0.034	1.90	1.26		1.0
1107	0.667.10-3	554·10 ⁻⁶	0.167	0.055	2.30	1.55		1.8
1408	2.107.10-3	1.1.10-3	0.251	0.097	2.90	2.00	100	3.2
1811	9.45·10 ⁻³	2.6.10-3	0.433	0.187	3.71	2.60	60	7.3
2213	27.1·10 ⁻³	4.9·10 ⁻³	0.635	0.297	4.42	3.15	38	13
2616	69.1·10 ⁻³	8.2.10-3	0.948	0.406	5.28	3.75	30	20
3019	0.180	14.2.10-3	1.38	0.587	6.20	4.50	23	34
3622	0.411	21.7.10-3	2.02	0.748	7.42	5.30	19	57
4229	1.15	41.1.10-3	2.66	1.40	8.60	6.81	13.5	104

A2.2 EE core data

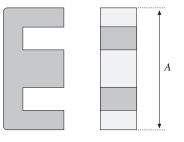


Core type	Geometrical constant	Geometrical constant	Cross- sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Core weight
(A) (mm)	$\frac{K_{g}}{\mathrm{cm}^{5}}$	K_{gfe} cm ^x	A_c (cm ²)	W_A (cm ²)	MLT (cm)	l_m (cm)	(g)
	0.731·10 ⁻³	0.458·10 ⁻³					
EE12	$0.731 \cdot 10^{-5}$	0.458.10*	0.14	0.085	2.28	2.7	2.34
EE16	$2.02 \cdot 10^{-3}$	$0.842 \cdot 10^{-3}$	0.19	0.190	3.40	3.45	3.29
EE19	$4.07 \cdot 10^{-3}$	1.3.10-3	0.23	0.284	3.69	3.94	4.83
EE22	8.26.10-3	1.8.10-3	0.41	0.196	3.99	3.96	8.81
EE30	85.7·10 ⁻³	6.7·10 ⁻³	1.09	0.476	6.60	5.77	32.4
EE40	0.209	11.8·10 ⁻³	1.27	1.10	8.50	7.70	50.3
EE50	0.909	28.4·10 ⁻³	2.26	1.78	10.0	9.58	116
EE60	1.38	36.4·10 ⁻³	2.47	2.89	12.8	11.0	135
EE70/68/19	5.06	127.10-3	3.24	6.75	14.0	9.0	280

A2.3 EC core data

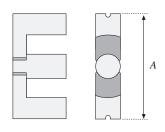


Core type	Geometrical constant	Geometrical constant	Cross- sectional	Bobbin winding	Mean length	Magnetic path	Thermal resistance	Core weight
	77	17	area	area	per turn	length	D	
(A) (mm)	K_{g_5} cm ⁵	K_{gfe} cm ^x	A_c (cm ²)	(cm^2)	MLT (cm)	l_m (cm)	R_{th} (°C/W)	(g)
EC35	0.131	9.9·10 ⁻³	0.843	0.975	5.30	7.74	18.5	35.5
EC41	0.374	19.5·10 ⁻³	1.21	1.35	5.30	8.93	16.5	57.0
EC52	0.914	31.7.10-3	1.80	2.12	7.50	10.5	11.0	111
EC70	2.84	56.2·10 ⁻³	2.79	4.71	12.9	14.4	7.5	256

A2.4 ETD core data

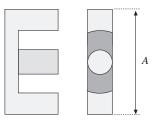

Core type	Geometrical constant	Geometrical constant	Cross- sectional	Bobbin winding	Mean length	Magnetic path	Thermal resistance	Core weight
			area	area	per turn	length		
(A)	K_{g_5}	K_{gfe}	A_{c}	W_A	MLT	l_m	R_{th}	
(mm)	cm [°]	cm ^x	(cm^2)	(cm^2)	(cm)	(cm)	(°C/W)	(g)
ETD29	0.0978	8.5.10-3	0.76	0.903	5.33	7.20		30
ETD34	0.193	13.1.10-3	0.97	1.23	6.00	7.86	19	40
ETD39	0.397	19.8·10 ⁻³	1.25	1.74	6.86	9.21	15	60
ETD44	0.846	30.4.10-3	1.74	2.13	7.62	10.3	12	94
ETD49	1.42	41.0.10-3	2.11	2.71	8.51	11.4	11	124

A2.5 PQ core data

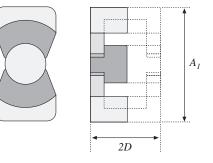


Core type	Geometrical constant	Geometrical constant	Cross- sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Core weight
$(A_1/2D)$ (mm)	$\frac{K_{g_5}}{\mathrm{cm}^5}$	$K_{gfe} \ { m cm}^x$	A_c (cm ²)	W_A (cm ²)	MLT (cm)	l _m (cm)	(g)
PQ 20/16	22.4·10 ⁻³	3.7.10-3	0.62	0.256	4.4	3.74	13
PQ 20/20	33.6.10-3	4.8·10 ⁻³	0.62	0.384	4.4	4.54	15
PQ 26/20	83.9·10 ⁻³	7.2.10-3	1.19	0.333	5.62	4.63	31
PQ 26/25	0.125	9.4·10 ⁻³	1.18	0.503	5.62	5.55	36
PQ 32/20	0.203	11.7.10-3	1.70	0.471	6.71	5.55	42
PQ 32/30	0.384	18.6·10 ⁻³	1.61	0.995	6.71	7.46	55
PQ 35/35	0.820	30.4.10-3	1.96	1.61	7.52	8.79	73
PQ 40/40	1.20	39.1·10 ⁻³	2.01	2.50	8.39	10.2	95

AWG#	Bare area, 10 ⁻³ cm ²	Resistance, 10 ⁻⁶ Ω/cm	Diameter, cm
0000	1072.3	1.608	1.168
000	850.3	2.027	1.040
000	674.2	2.557	0.927
0	534.8	3.224	0.825
1	424.1	4.065	0.735
2	336.3	5.128	0.654
3	266.7	6.463	0.583
4	211.5	8.153	0.519
5	167.7	10.28	0.462
6	133.0	13.0	0.411
7	105.5	16.3	0.366
8	83.67	20.6	0.326
9	66.32	26.0	0.291
10	52.41	32.9	0.267
11	41.60	41.37	0.238
11	33.08	52.09	0.238
13	26.26	69.64	0.190
14	20.02	82.80	0.171
15	16.51	104.3	0.153
16	13.07	131.8	0.137
17	10.39	165.8	0.122
18	8.228	209.5	0.109
19	6.531	263.9	0.0948
20	5.188	332.3	0.0874
21	4.116	418.9	0.0785
22	3.243	531.4	0.0701
23	2.508	666.0	0.0632
24	2.047	842.1	0.0566
25	1.623	1062.0	0.0505
26	1.280	1345.0	0.0452
20 27	1.021	1687.6	0.0432
28	0.8046	2142.7	0.0409
28 29			
	0.6470	2664.3	0.0330 0.0294
30	0.5067	3402.2	
31	0.4013	4294.6	0.0267
32	0.3242	5314.9	0.0241
33	0.2554	6748.6	0.0236
34	0.2011	8572.8	0.0191
35	0.1589	10849	0.0170
36	0.1266	13608	0.0152
37	0.1026	16801	0.0140
38	0.08107	21266	0.0124
39	0.06207	27775	0.0121
40	0.04869	35400	0.0096
41			0.00863
	0.03972	43405	
42	0.03166	54429	0.00762
43	0.02452	70308	0.00685

A2.6 American wire gauge data

Appendix 3: Averaged switch modeling of a CCM SEPIC

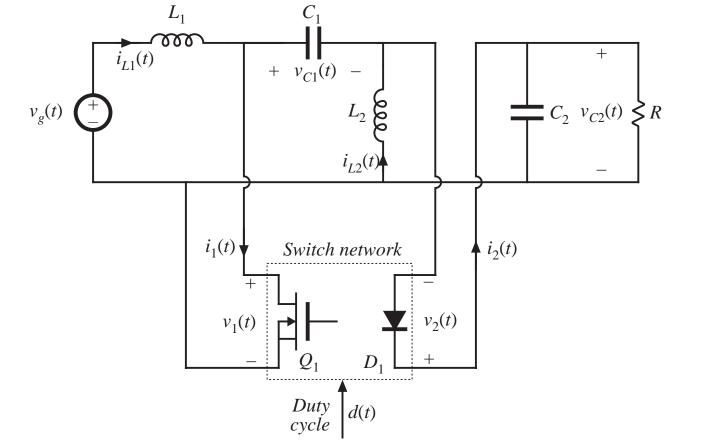SEPIC example: write circuit with switch network explicitly identified



A few points regarding averaged switch modeling


- The switch network can be defined arbitrarily, as long as its terminal voltages and currents are independent, and the switch network contains no reactive elements.
- It is *not* necessary that some of the switch network terminal quantities coincide with inductor currents or capacitor voltages of the converter, or be nonpulsating.
- The object is simply to write the averaged equations of the switch network; i.e., to express the average values of half of the switch network terminal waveforms as functions of

the average values of the remaining switch network terminal waveforms, and


the control input.

SEPIC CCM waveforms

Sketch terminal waveforms of switch network

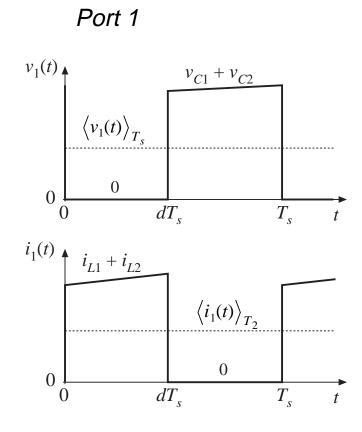

Port 2

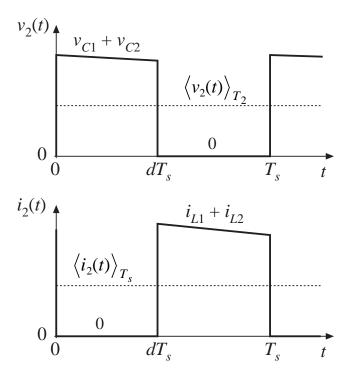

Fundamentals of Power Electronics

Expressions for average values of switch network terminal waveforms

Use small ripple approximation

$$\left\langle v_{1}(t) \right\rangle_{T_{s}} = d'(t) \left(\left\langle v_{C1}(t) \right\rangle_{T_{s}} + \left\langle v_{C2}(t) \right\rangle_{T_{s}} \right)$$

$$\left\langle i_{1}(t) \right\rangle_{T_{s}} = d(t) \left(\left\langle i_{L1}(t) \right\rangle_{T_{s}} + \left\langle i_{L2}(t) \right\rangle_{T_{s}} \right)$$

$$\left\langle v_{2}(t) \right\rangle_{T_{s}} = d(t) \left(\left\langle v_{C1}(t) \right\rangle_{T_{s}} + \left\langle v_{C2}(t) \right\rangle_{T_{s}} \right)$$

$$\left\langle i_{2}(t) \right\rangle_{T_{s}} = d'(t) \left(\left\langle i_{L1}(t) \right\rangle_{T_{s}} + \left\langle i_{L2}(t) \right\rangle_{T_{s}} \right)$$

Need next to eliminate the capacitor voltages and inductor currents from these expressions, to write the equations of the switch network.


Derivation of switch network equations (Algebra steps)

We can write


$$\left\langle i_{L1}(t) \right\rangle_{T_s} + \left\langle i_{L2}(t) \right\rangle_{T_s} = \frac{\left\langle i_1(t) \right\rangle_{T_s}}{d(t)}$$
$$\left\langle v_{C1}(t) \right\rangle_{T_s} + \left\langle v_{C2}(t) \right\rangle_{T_s} = \frac{\left\langle v_2(t) \right\rangle_{T_s}}{d(t)}$$

Hence
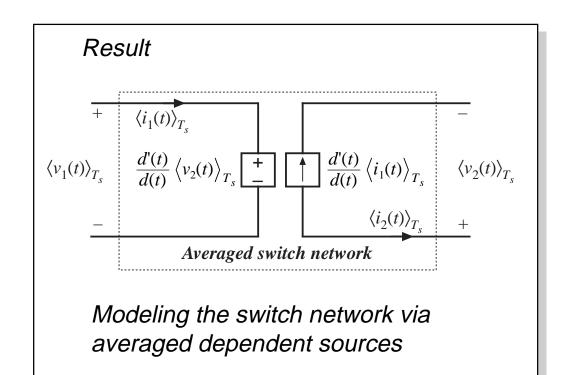
$$\left\langle v_1(t) \right\rangle_{T_s} = \frac{d'(t)}{d(t)} \left\langle v_2(t) \right\rangle_{T_s}$$
$$\left\langle i_2(t) \right\rangle_{T_s} = \frac{d'(t)}{d(t)} \left\langle i_1(t) \right\rangle_{T_s}$$




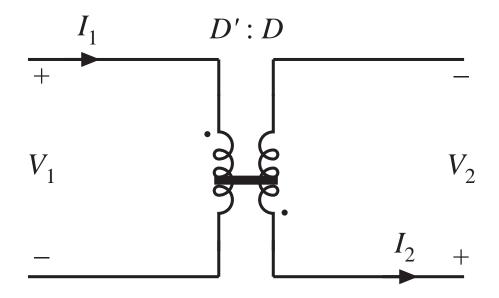Steady-state switch model: Dc transformer model



Steady-state CCM SEPIC model

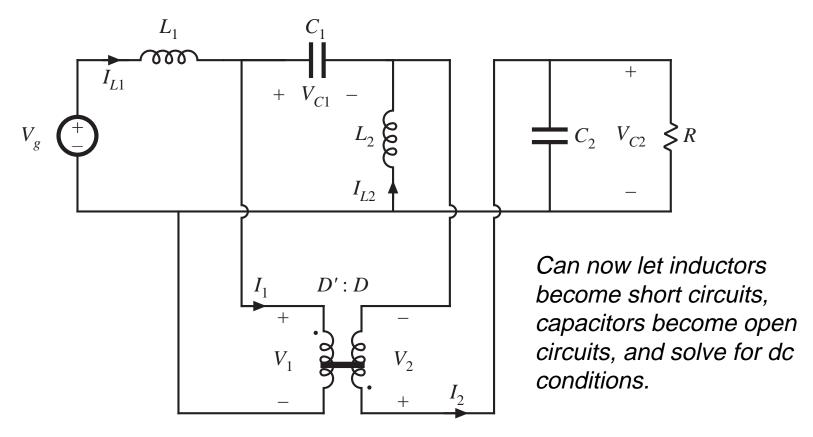Replace switch network with dc transformer model



Small-signal model

Perturb and linearize the switch network averaged waveforms, as usual:

$$d(t) = D + \hat{d}(t)$$
$$\left\langle v_1(t) \right\rangle_{T_s} = V_1 + \hat{v}_1(t)$$
$$\left\langle i_1(t) \right\rangle_{T_s} = I_1 + \hat{i}_1(t)$$
$$\left\langle v_2(t) \right\rangle_{T_s} = V_2 + \hat{v}_2(t)$$
$$\left\langle i_2(t) \right\rangle_{T_s} = I_2 + \hat{i}_2(t)$$

Voltage equation becomes

$$(D+\hat{d})(V_1+\hat{v}_1) = (D'-\hat{d})(V_2+\hat{v}_2)$$

Eliminate nonlinear terms and solve for v_1 terms:

$$\begin{split} \left(V_1 + \hat{v}_1\right) &= \frac{D'}{D} \left(V_2 + \hat{v}_2\right) - \hat{d} \left(\frac{V_1 + V_2}{D}\right) \\ &= \frac{D'}{D} \left(V_2 + \hat{v}_2\right) - \hat{d} \left(\frac{V_1}{DD'}\right) \end{split}$$

Appendix 3: Averaged switch modeling of a CCM SEPIC

Linearization, continued

Current equation becomes


$$(D+\hat{d})(I_2+\hat{i}_2) = (D'-\hat{d})(I_1+\hat{i}_1)$$

Eliminate nonlinear terms and solve for i_2 terms:

$$\begin{aligned} \left(I_2 + \hat{i}_2\right) &= \frac{D'}{D} \left(I_1 + \hat{i}_1\right) - \hat{d} \left(\frac{I_1 + I_2}{D}\right) \\ &= \frac{D'}{D} \left(I_1 + \hat{i}_1\right) - \hat{d} \left(\frac{I_2}{DD'}\right) \end{aligned}$$

Switch network: Small-signal ac model

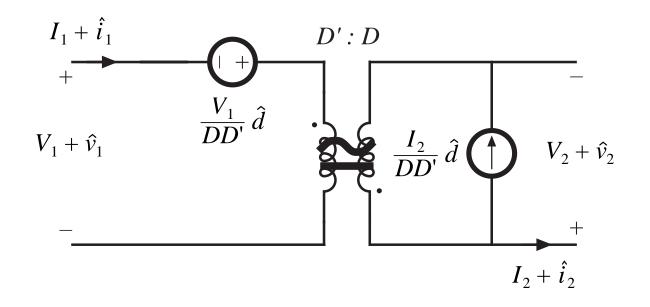Reconstruct equivalent circuit in the usual manner:



Small-signal ac model of the CCM SEPIC

Replace switch network with small-signal ac model:

